



Chip-Scale Energy and Power... and Heat

Dr. Wilfried Haensch

Thomas J. Watson Research Center,
IBM

The views and opinions presented by the invited speakers are their own
and should not be interpreted as representing the official views of DARPA or DoD

Approved For Public Release, Distribution Unlimited

Report Documentation Page			Form Approved OMB No. 0704-0188		
Public reporting burden for the collection of information is estimated to average 1 hour per response, including the time for reviewing instructions, searching existing data sources, gathering and maintaining the data needed, and completing and reviewing the collection of information. Send comments regarding this burden estimate or any other aspect of this collection of information, including suggestions for reducing this burden, to Washington Headquarters Services, Directorate for Information Operations and Reports, 1215 Jefferson Davis Highway, Suite 1204, Arlington VA 22202-4302. Respondents should be aware that notwithstanding any other provision of law, no person shall be subject to a penalty for failing to comply with a collection of information if it does not display a currently valid OMB control number.					
1. REPORT DATE MAR 2009	2. REPORT TYPE		3. DATES COVERED 00-00-2009 to 00-00-2009		
4. TITLE AND SUBTITLE Is Power the new Brick Wall?			5a. CONTRACT NUMBER		
			5b. GRANT NUMBER		
			5c. PROGRAM ELEMENT NUMBER		
6. AUTHOR(S)			5d. PROJECT NUMBER		
			5e. TASK NUMBER		
			5f. WORK UNIT NUMBER		
7. PERFORMING ORGANIZATION NAME(S) AND ADDRESS(ES) IBM, Thomas J. Watson Research Center, Yorktown Heights, NY, 10598			8. PERFORMING ORGANIZATION REPORT NUMBER		
9. SPONSORING/MONITORING AGENCY NAME(S) AND ADDRESS(ES)			10. SPONSOR/MONITOR'S ACRONYM(S)		
			11. SPONSOR/MONITOR'S REPORT NUMBER(S)		
12. DISTRIBUTION/AVAILABILITY STATEMENT Approved for public release; distribution unlimited					
13. SUPPLEMENTARY NOTES					
14. ABSTRACT					
15. SUBJECT TERMS					
16. SECURITY CLASSIFICATION OF:			17. LIMITATION OF ABSTRACT Same as Report (SAR)	18. NUMBER OF PAGES 45	19a. NAME OF RESPONSIBLE PERSON
a. REPORT unclassified	b. ABSTRACT unclassified	c. THIS PAGE unclassified			




IBM Research

Is Power the new Brick Wall?

Wilfried Haensch,

MTO Symposium March 2-5th San Jose 2009

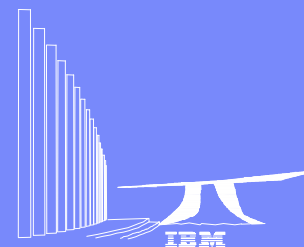


© 2005 IBM Corporation

Outline

- Introduction
- Classical CMOS
 - Devices
 - Power delivery
 - SRAM memory
 - I/Os
- Sub-threshold engineering
 - Does steep SS make sense?
- Adiabatic computing
- Summary
- Acknowledgements

Transistors, performance, power

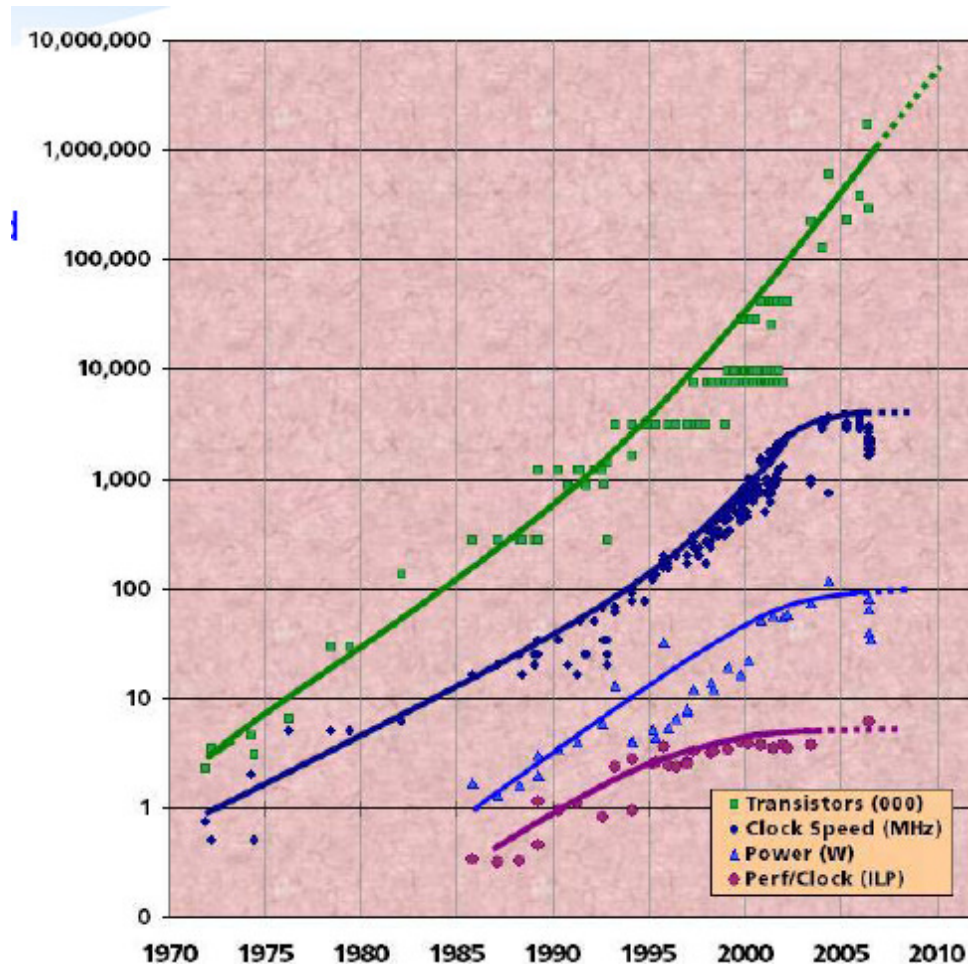
- Density scales at traditional rate
 - Caches get larger and contribute significantly to transistor count
- Clock speed and power level off
 - Single thread performance is power limited
 - Need more efficient cooling solutions
- System performance can pick up with parallelism
 - Many low power cores will deliver same throughput
 - Application dependent solution



Source: Kunle Olukotun, Lance Hammond, Herb Sutter, and Burton Smith

Where does the power go?

Karthick Rajamani, Boulder TVC

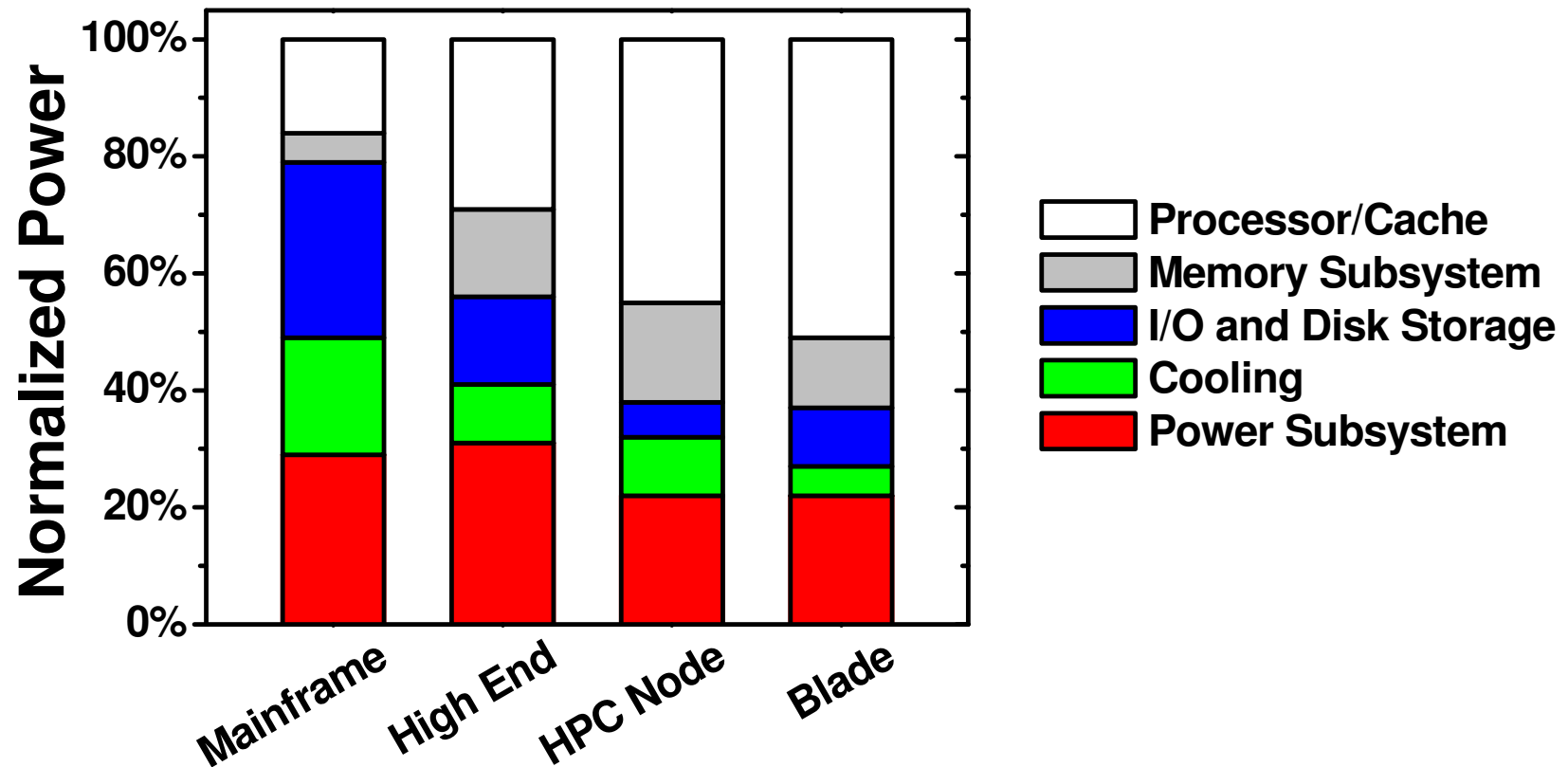

- Power is not only a processor problem. The power problem penetrates the whole system

Classical CMOS

General considerations

■ Circuit


$$P \sim \frac{CV^2}{\tau} \quad \text{Power density}$$

$$\tau \sim \frac{CV}{I} \quad \text{Delay}$$

■ Chip

$$P_{act} \sim fC_{eff}V^2 \quad \text{Power}$$
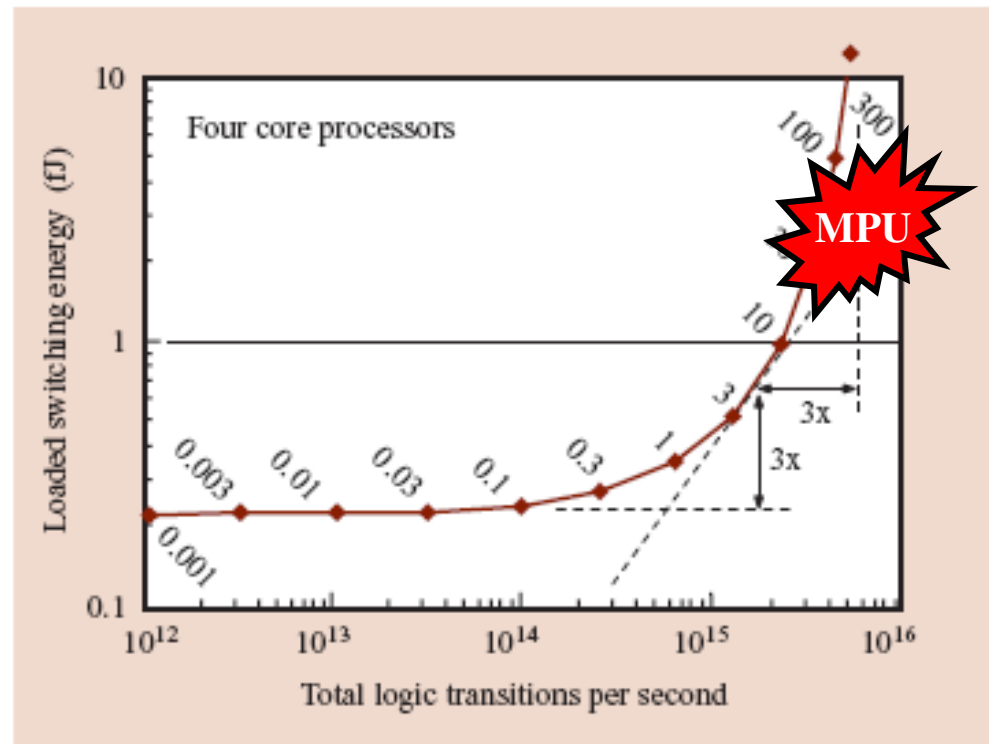
$$f \sim \alpha(V - V_0) \quad \text{Frequency}$$



■ Voltage scaling comes at the cost of performance

General considerations

- Circuit


$$P \sim \frac{CV^2}{\tau} \quad \text{Power density}$$

$$\tau \sim \frac{CV}{I} \quad \text{Delay}$$

- Chip

$$P_{act} \sim fC_{eff}V^2 \quad \text{Power}$$
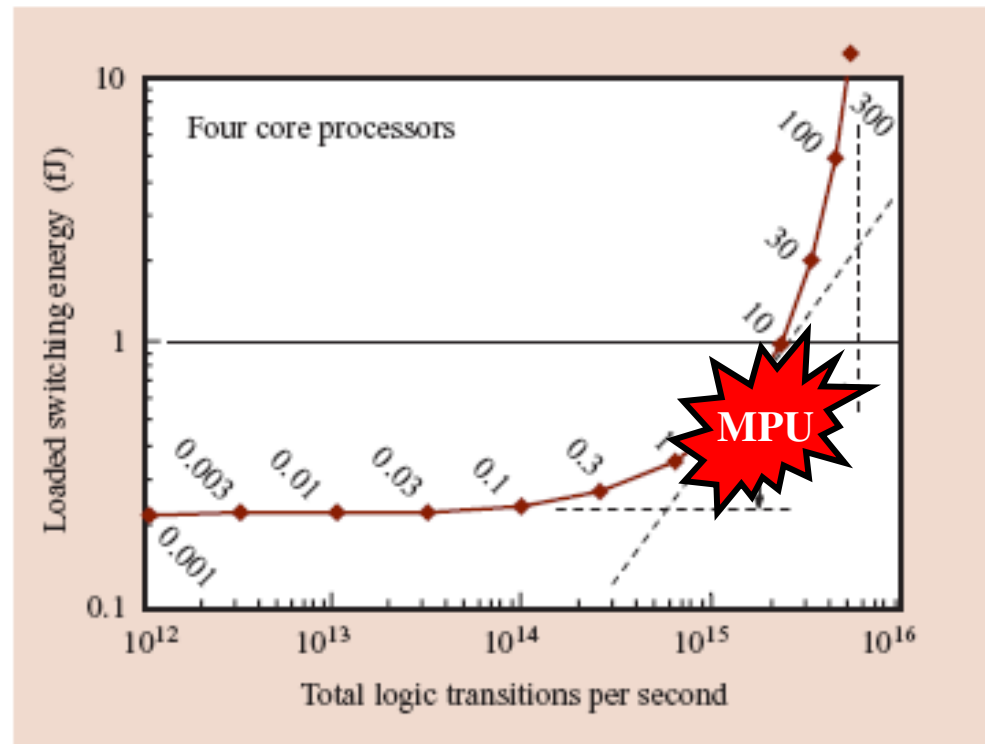
$$f \sim \alpha(V - V_0) \quad \text{Frequency}$$



- Voltage scaling comes at the cost of performance
- Silver bullet: *Low V, low C, high I*

Scaling dilemma

$$I_{off} = I_{V_{th}} 10^{-\frac{V_{th}}{S}}$$

$$I_{on} = C_{inv} v_{sat} (V_{dd} - V_{th} - V_{sat})$$

$$I_{off} \sim 100 \text{ nA}/\mu\text{m}$$

$$S > 60 \text{ mV/dec}$$

$$I_{V_{th}} \sim 300 \mu\text{m/L nA}/\mu\text{m}$$

$$C_{inv} \sim 35 \text{ fF}/\mu\text{m}^2 \sim EOT \sim 0.8 \text{ nm}$$


$$I_{on} \sim 1.5 \text{ mA}/\mu\text{m}$$

$$V_{sat} \sim 0.25 \text{ V}$$

- Simple voltage scaling is challenging

$$V_{th} > 125 \text{ mV}$$

$$V_{dd} - V_{th} > 650 \text{ mV}$$

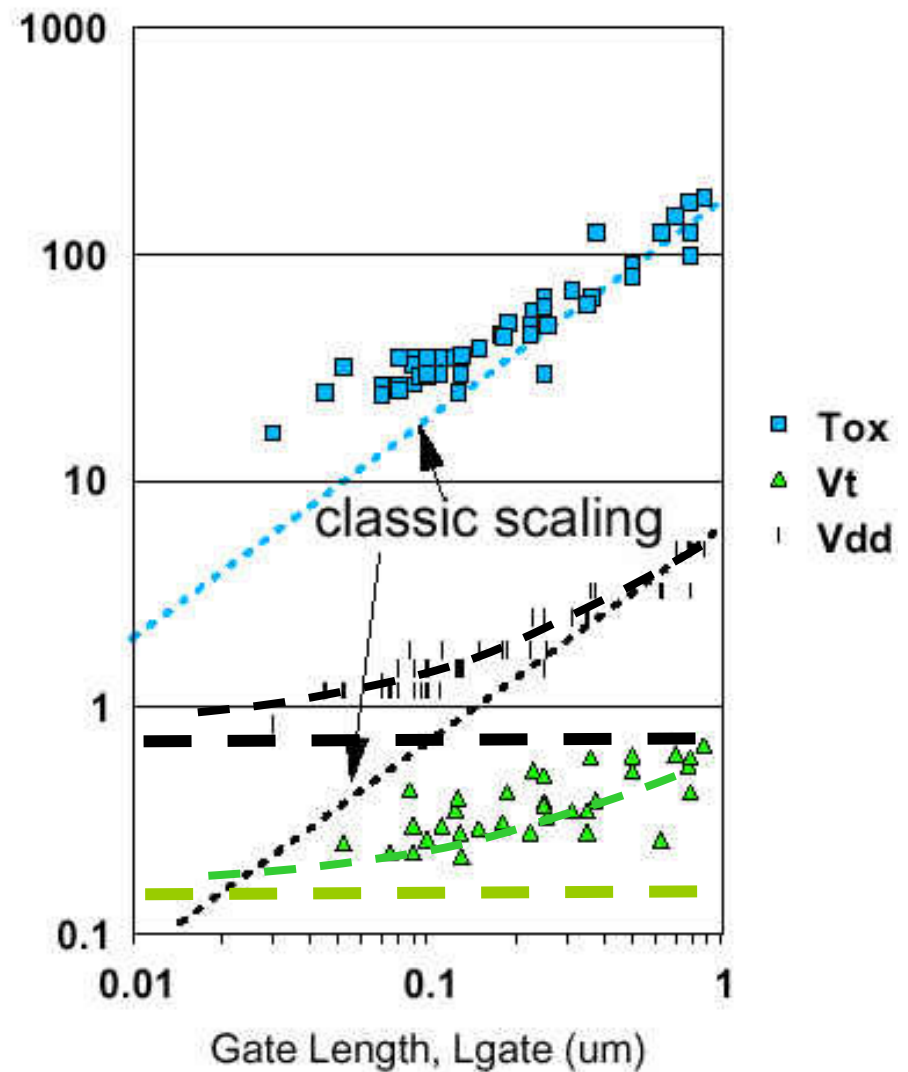



Device choices

I_{on} @ given I_{off}

I_{eff} @ given I_{off}


- Short channel effects will degrade I_{eff} faster than I_{on}

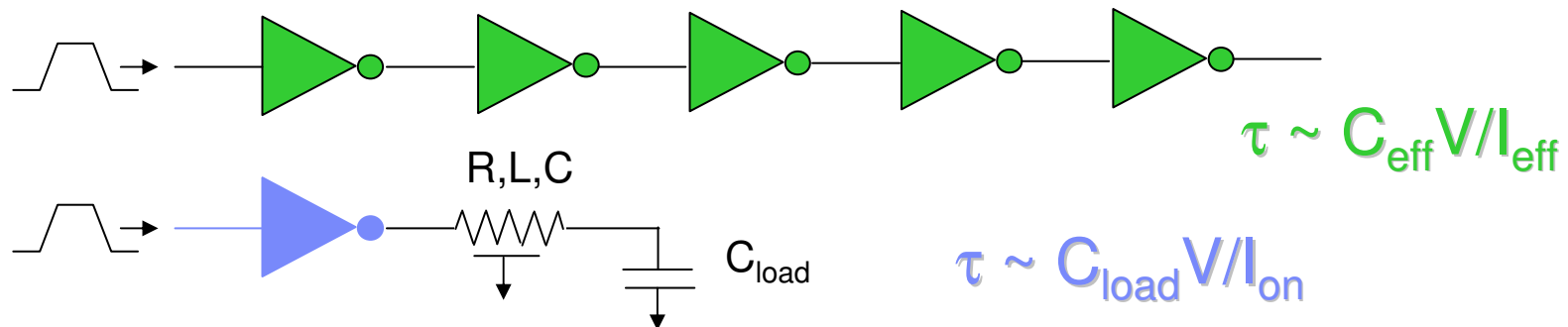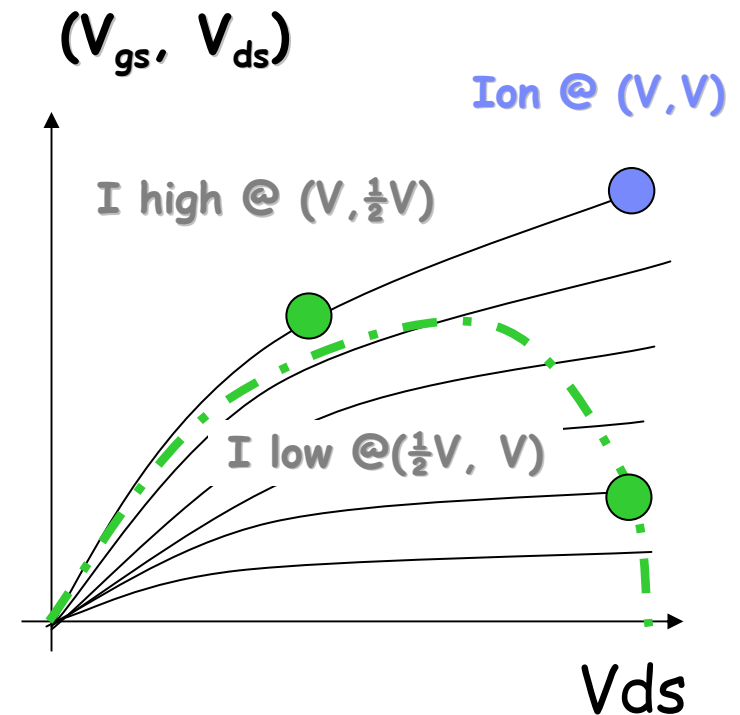- $I_{on} \sim (V - V_{t_{sat}})^\alpha$
- $I_{on} - I_{high} \sim DIBL * V/2$
- $I_{low} \sim (V/2 - V_{t_{sat}})^\alpha$



Si Device Evolution (I)

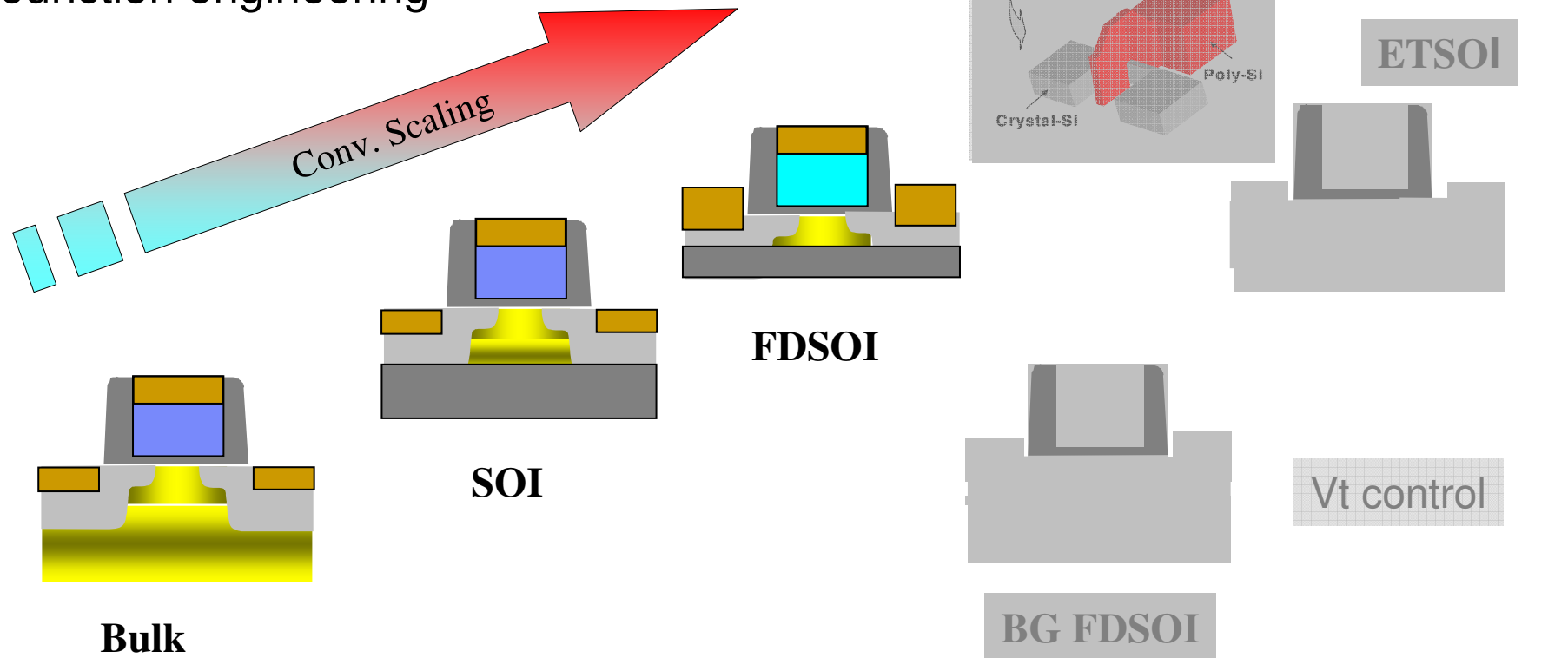
High μ options: liner stress,
eSiGe, SMT, HOT, SSDOI, ..
Gate stack: high-k, Metal gate
Junction engineering



Si Device Evolution (II)


High μ options: liner stress, eSiGe, SMT, HOT, SSDOI, ..
Gate stack: high-k, Metal gate
Junction engineering

Conv. Scaling

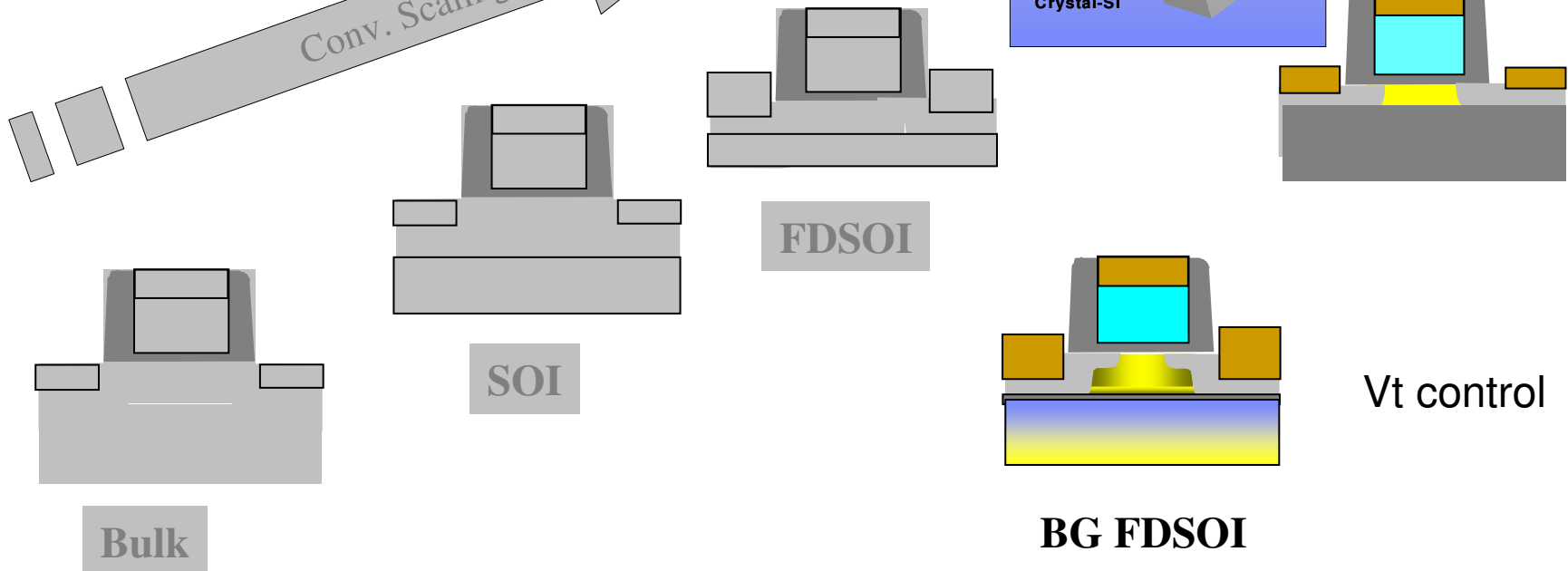


Body control SCE will enable length scaling without aggressive dielectric

FinFET/TriGate

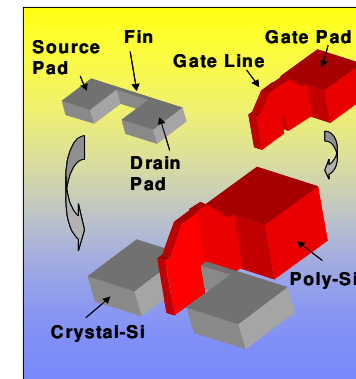


ETSOI

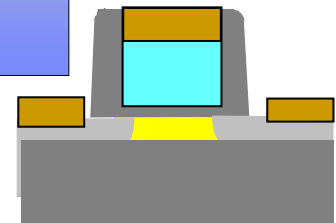


Vt control

BG FDSOI

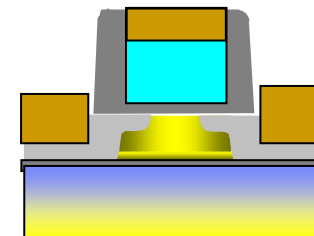


Optimal technology - DIBL

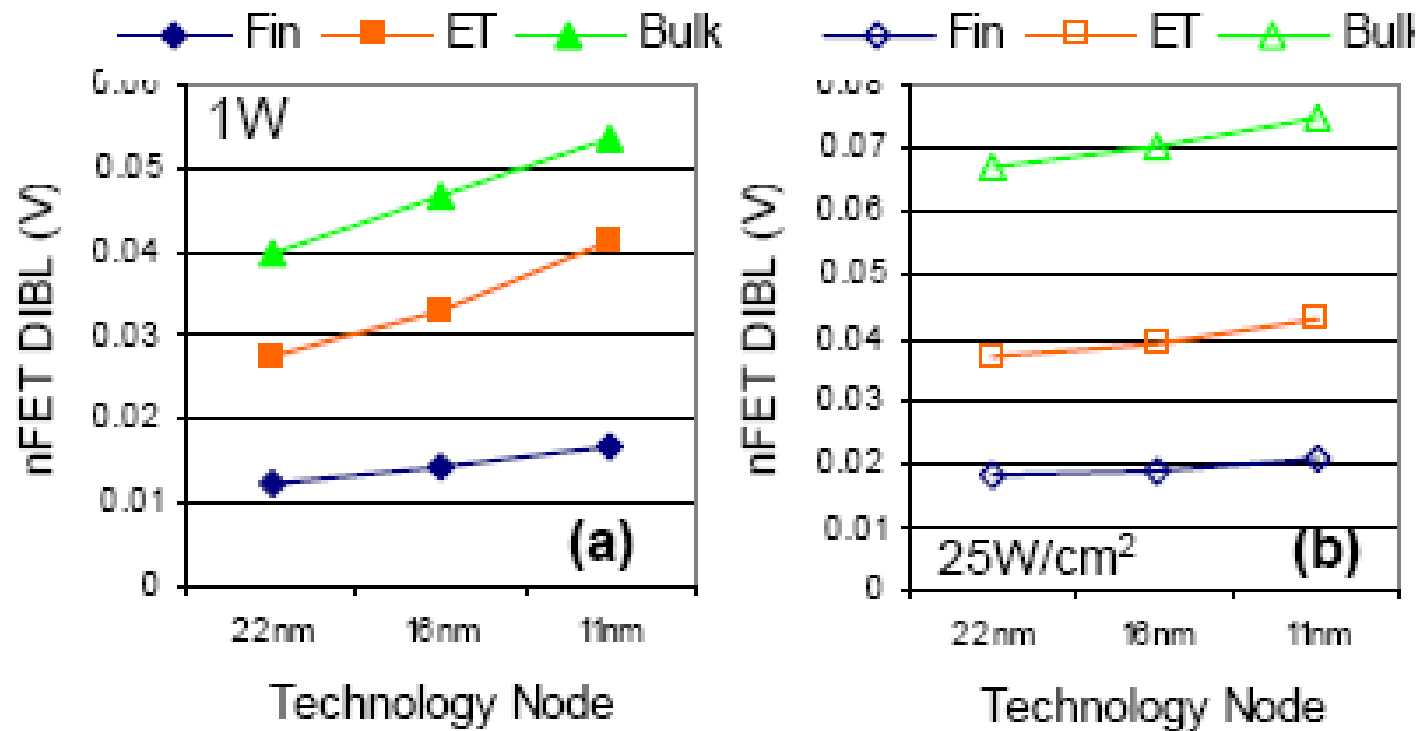


- Low DIBL is more advantageous for power optimized performance

Optimal technology – supply voltage

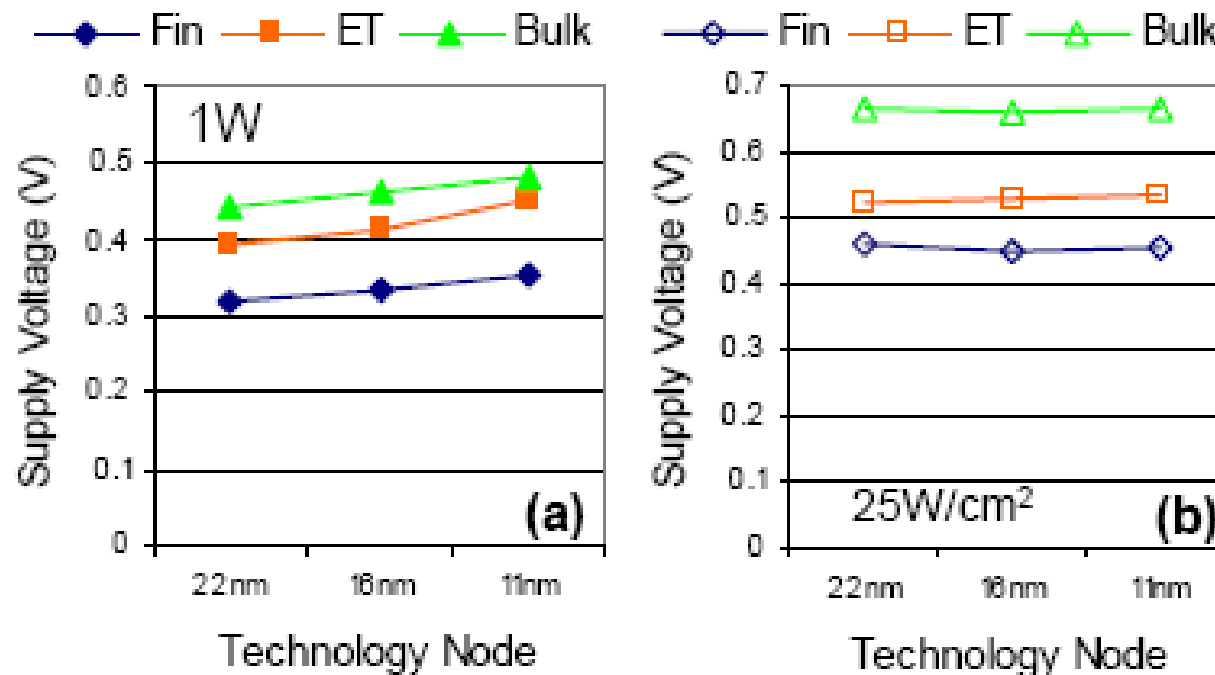


- because it allows reduction of supply voltage for maximum performance

Optimal technology – gate length


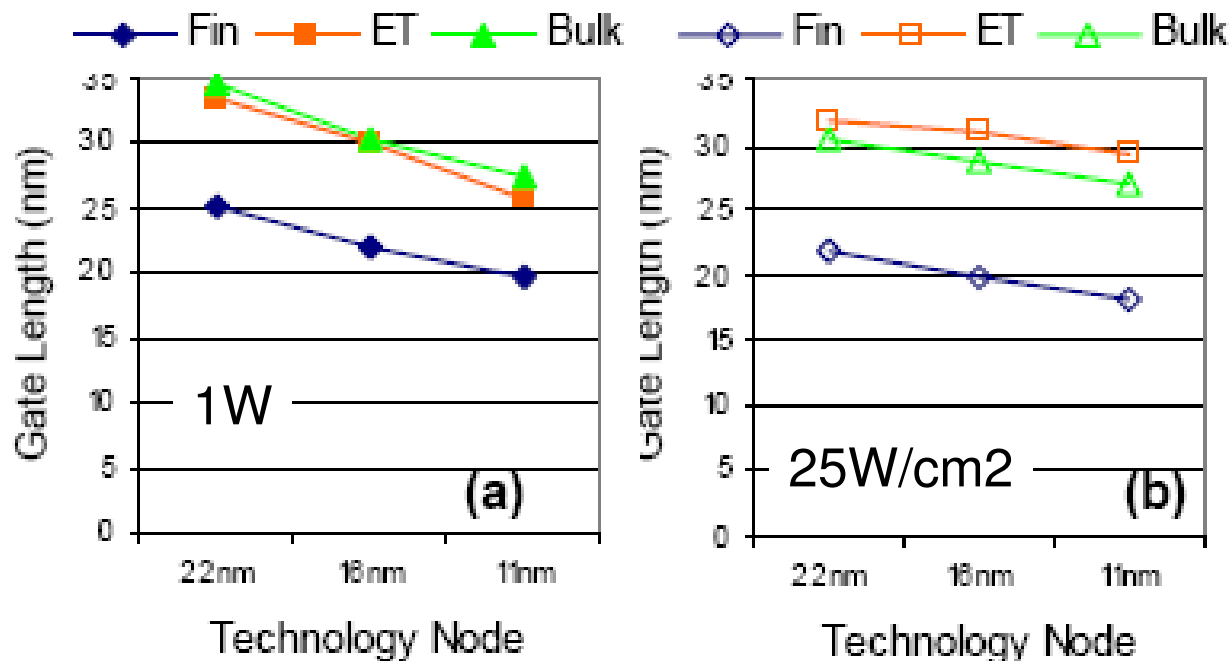


- Superior electrostatics allows shortest gate length for FinFET
- Gate length are longer than expected, no significant difference for low power or high performance

Optimal technology – density

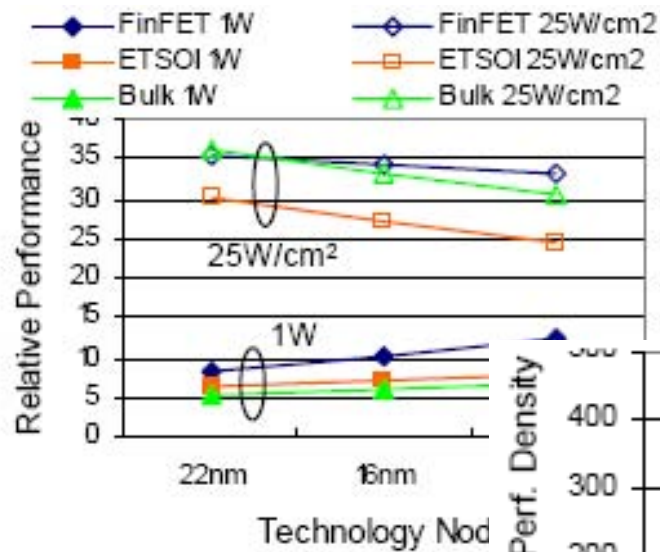


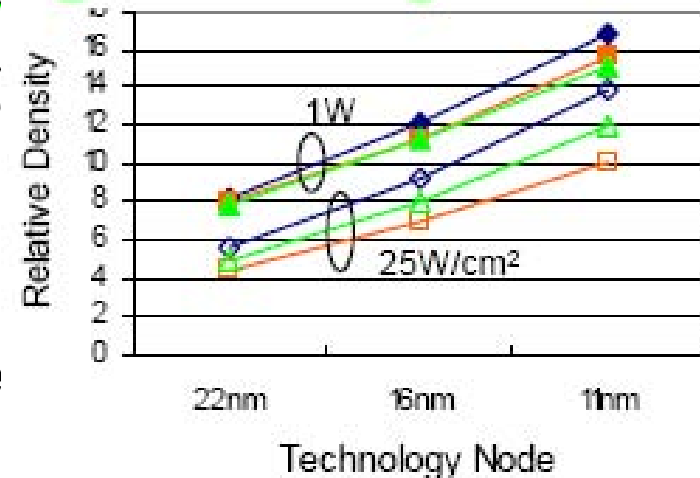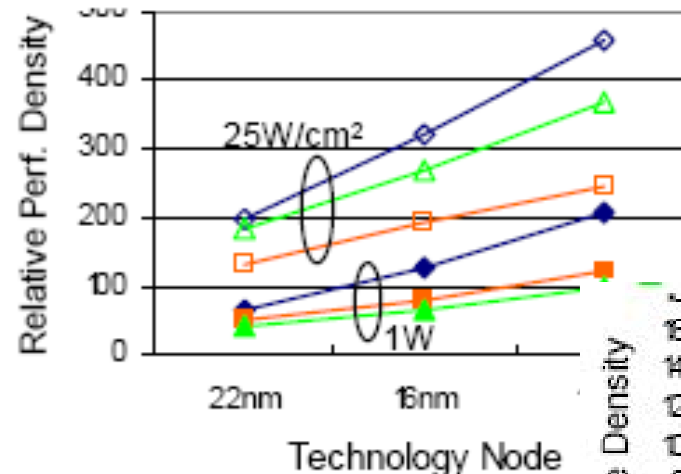- Only moderate gains in single core performance for low power technology



- Performance comes with parallelism and density advantage

Power delivery

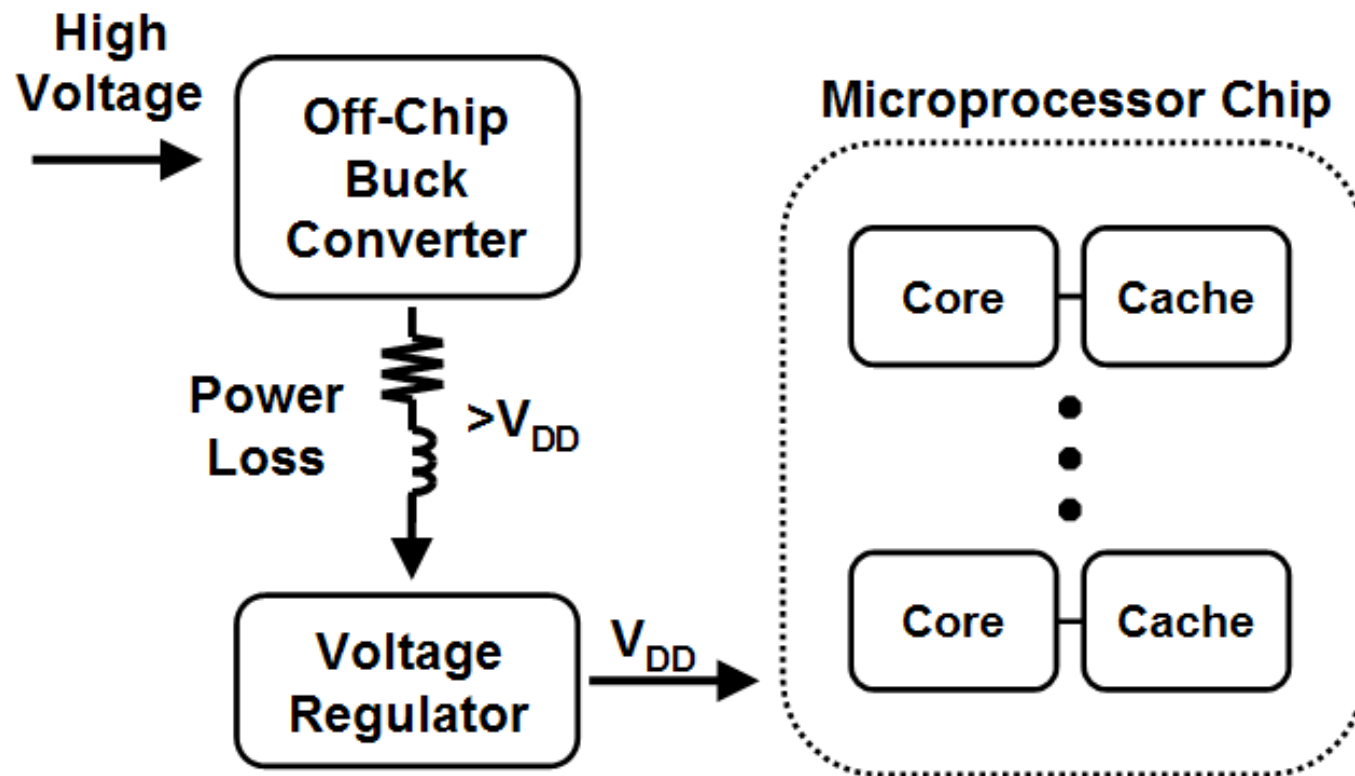

- Bringing high voltage as close to the chip would reduce power loss

The case for high voltage power delivery to ICs

- High voltage power delivery system $\Leftrightarrow$ Put voltage down-converter close to the point of use
 - minimizes power loss
 - improves supply stability


- Power loss

$$\frac{P_{loss}}{P} = \frac{I^2 R}{P} = \frac{(P/V)^2 R}{P} = \frac{PR}{V^2}$$

- Supply stability

$$\frac{\Delta V_L}{V} = \frac{L \frac{dI}{dt}}{V} = \Omega \frac{LP}{V^2}$$

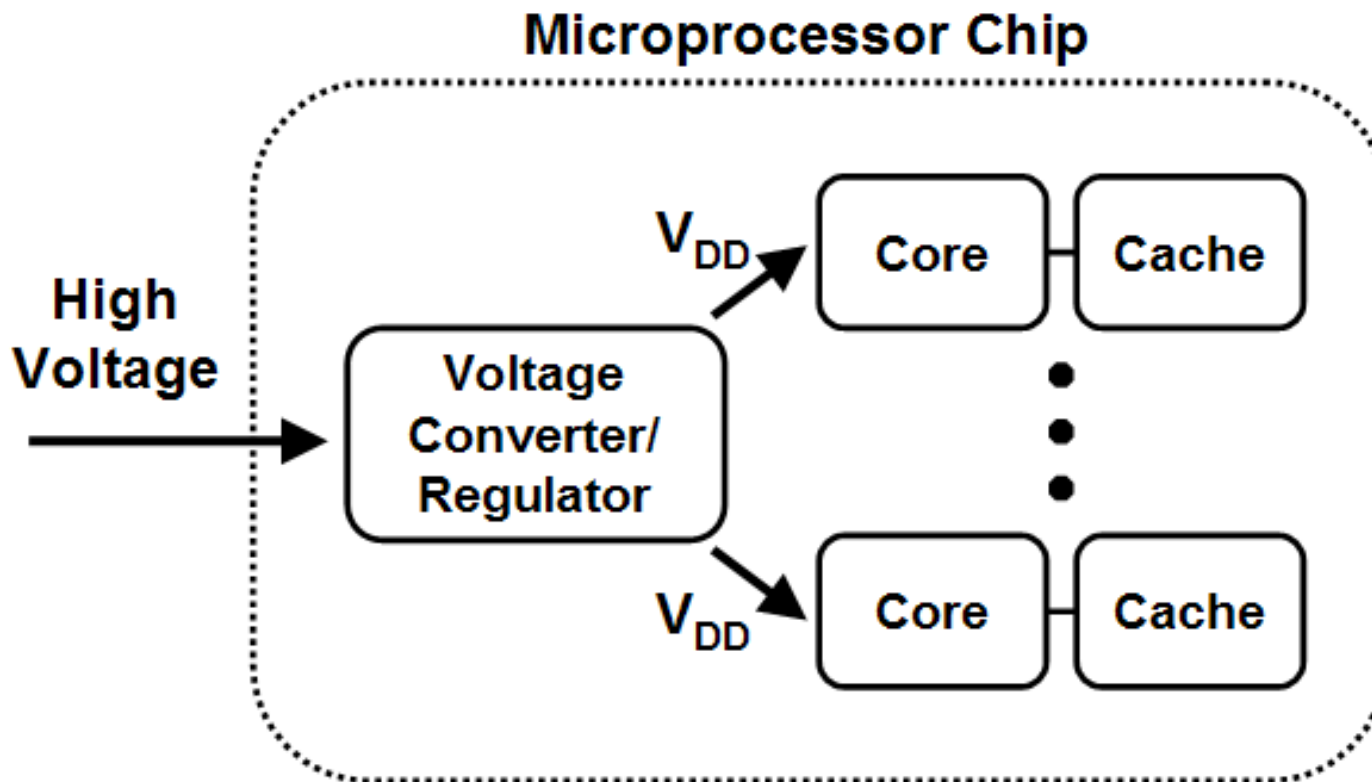
The case for high voltage power delivery to ICs



- Need efficient on-chip converters that are compatible with base CMOS technology


 Data State
 Operation

Total energy = 68

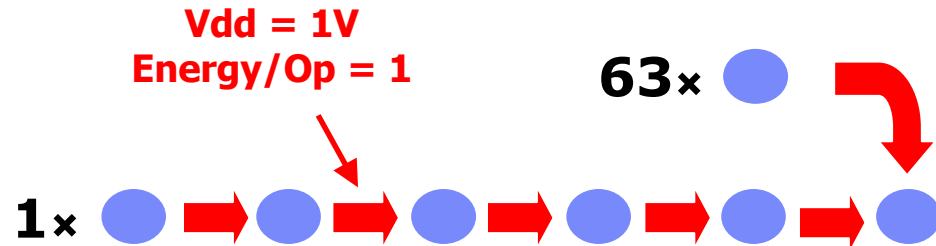


time

Total energy = 15

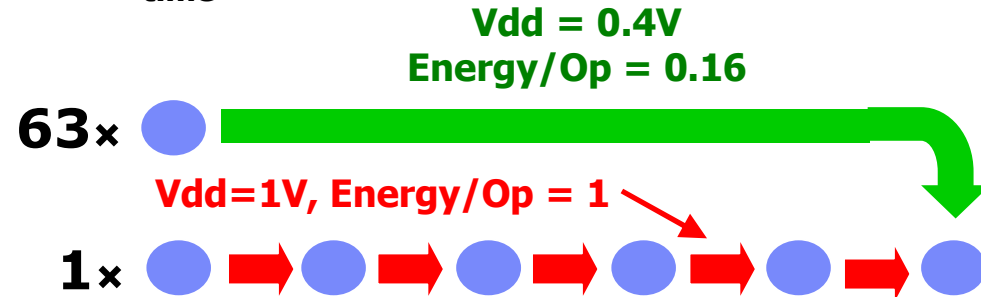


- 19

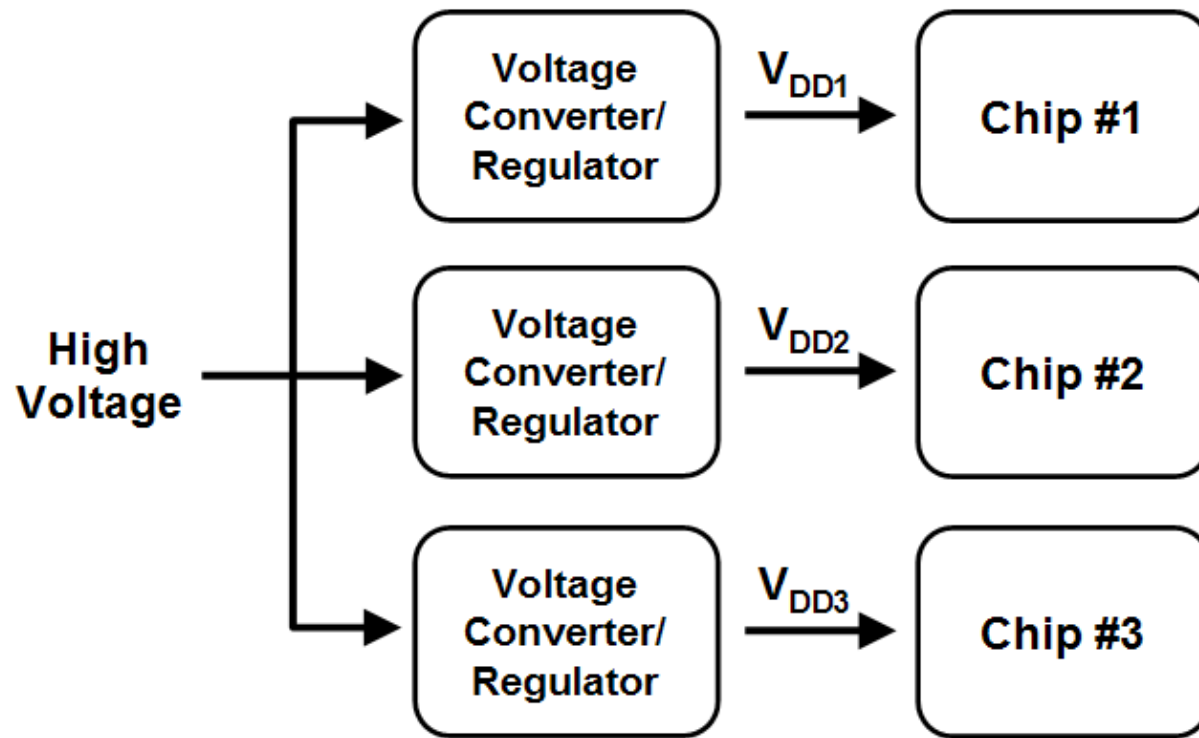The case for high voltage power delivery to ICs



- Due to natural process variations (e. g. L_{gate}) need to regulate supply voltages for individual cores for performance matching

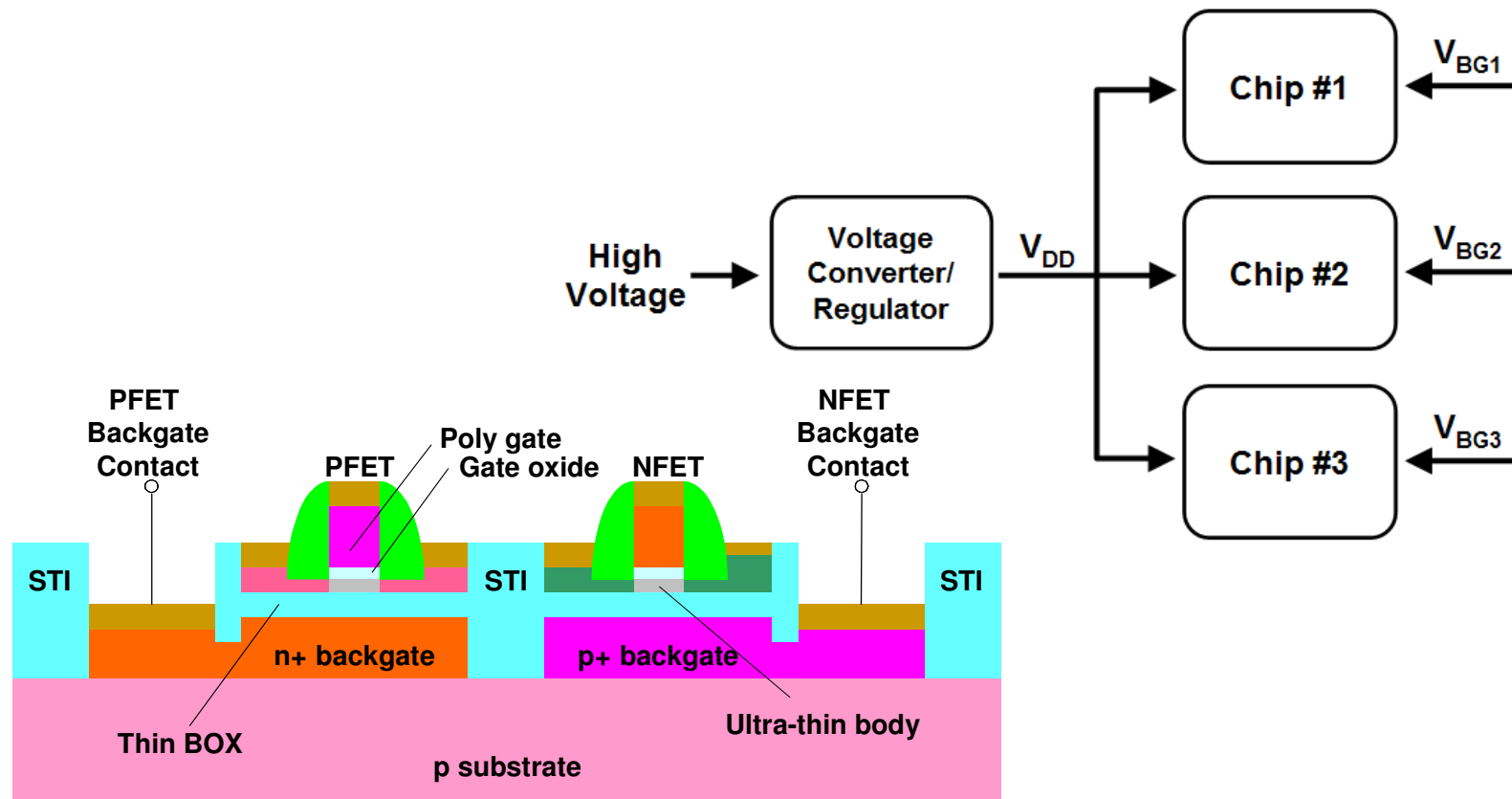
The case for high voltage power delivery to ICs



- Back-gate control would simplify voltage delivery

Obstacles to low-voltage operation

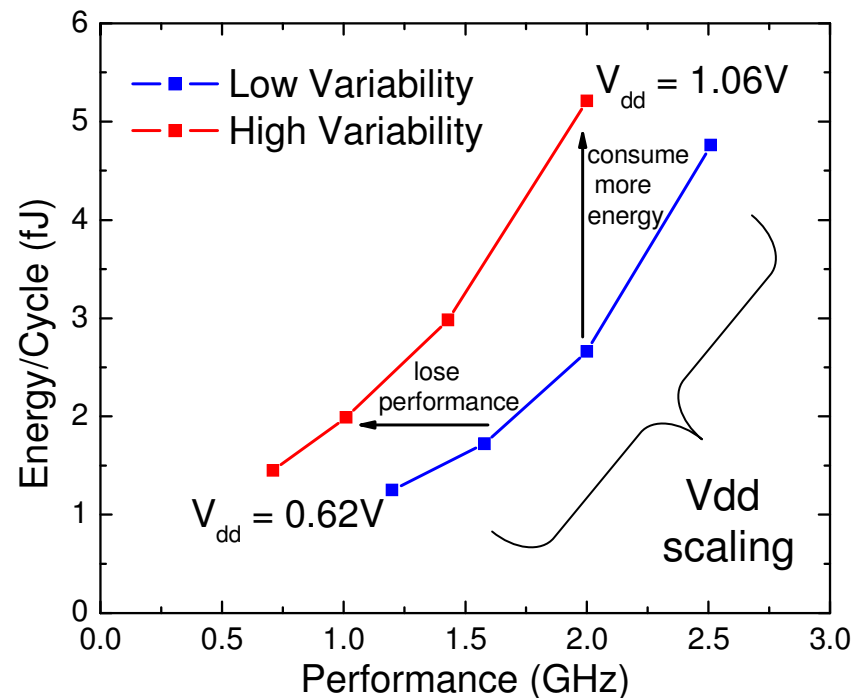- Increased gate delays → circuit design challenge,
- Increased sensitivity to process variability → device design challenge.



- Variability needs to be minimized for low voltage operation.

Noise

■ Resistive noise

- Current is a super-linear function of V_{DD}

$$\frac{I_{on}R}{V_{DD}} \propto \frac{V_{DD}^{1.5}}{V_{DD}} = V_{DD}^{0.5}$$

... scales faster than V_{DD}

■ Capacitive noise

- Charge is directly proportional to V_{DD}

$$\frac{CV_{DD}}{V_{DD}} \propto C$$

... scales with V_{DD}



■ Inductive noise

- Current is a super-linear function of V_{DD}

$$\frac{L \frac{\partial I}{\partial t}}{V_{DD}} \propto \frac{V_{DD}^{1.5}}{V_{DD}} = V_{DD}^{0.5}$$



... scales faster than V_{DD}

Low voltage circuit operation - SRAM

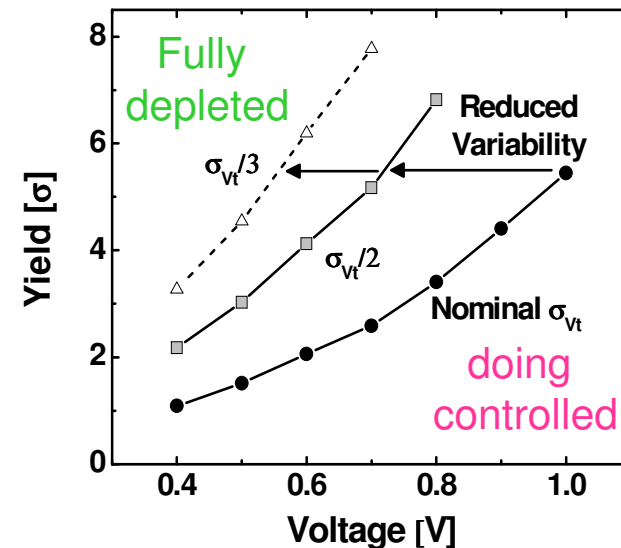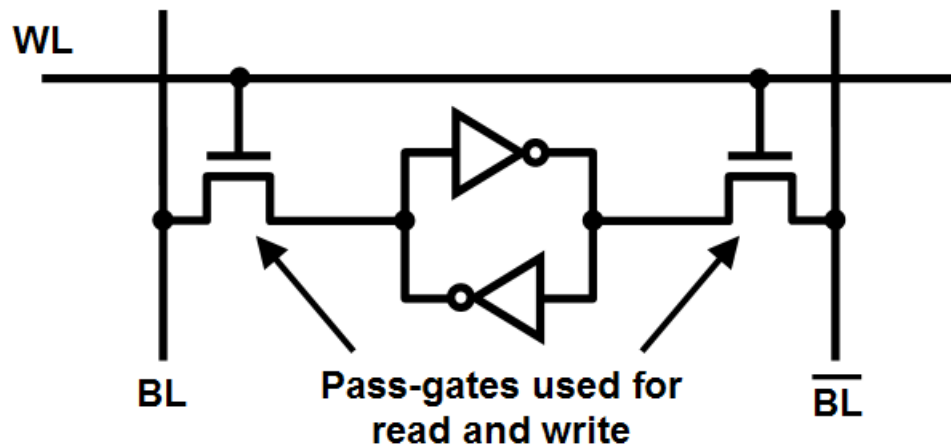

- Read and write operation required a delicate balance of cell devices and threshold mismatch will impact operation window, in particular at low voltages
- Device choices can significantly reduce operating voltage for 6T SRAM cell


Low voltage circuit operation - SRAM

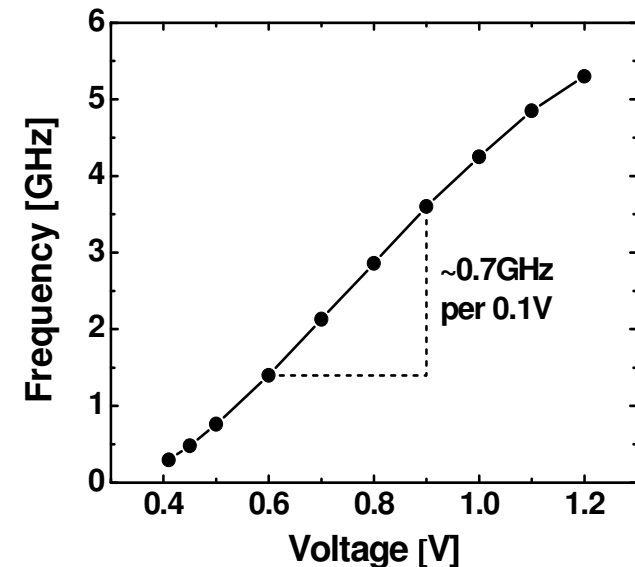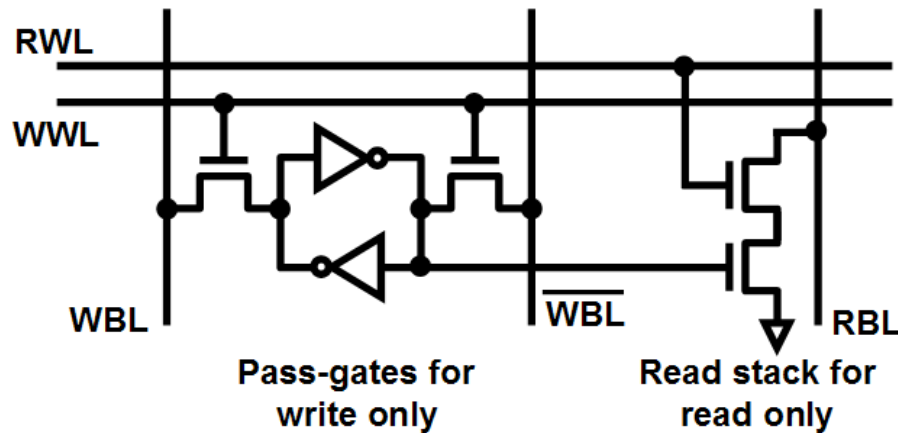

- 8T SRAM cell decouples read and write and opens up operating window for the cell
- Devices can be designed at minimum dimensions, which will benefit cell size


Off-chip bandwidth vs on-chip cache

- What is the real relationship?

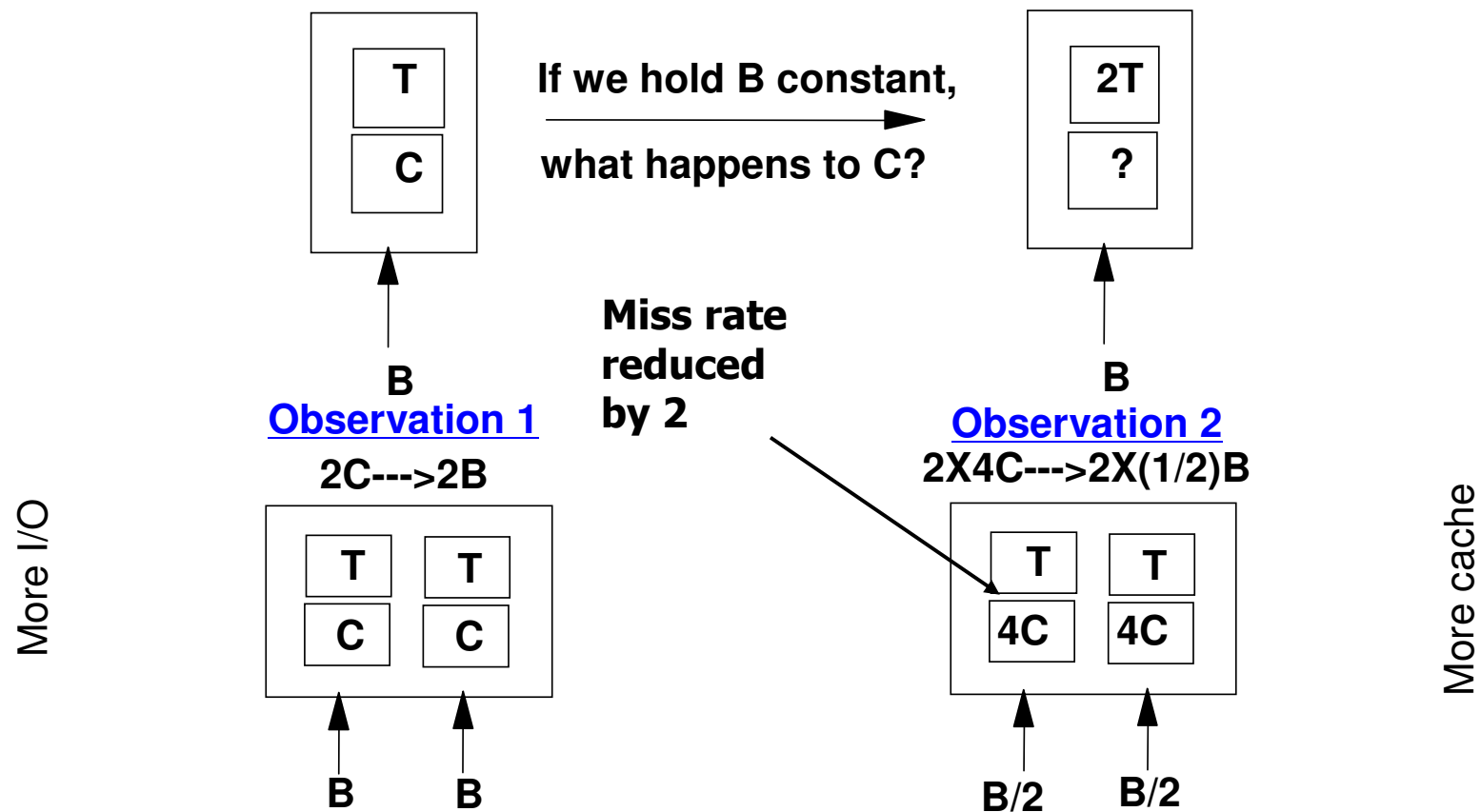

Off-chip bandwidth vs on-chip cache

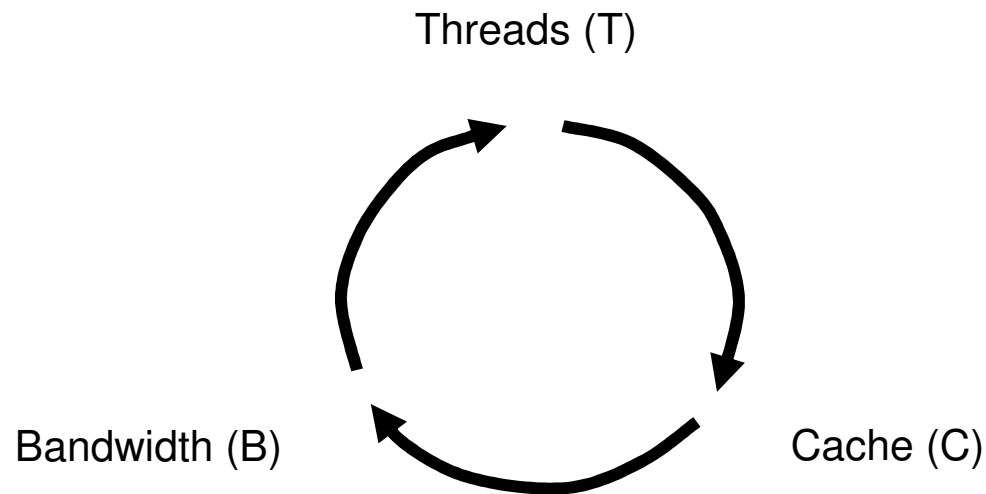- Architecture solution depends on application




Emma's Law:

$$2^{\alpha+\beta} T = (2^{\alpha} B) \times (8^{\beta} C)$$


Low voltage signaling

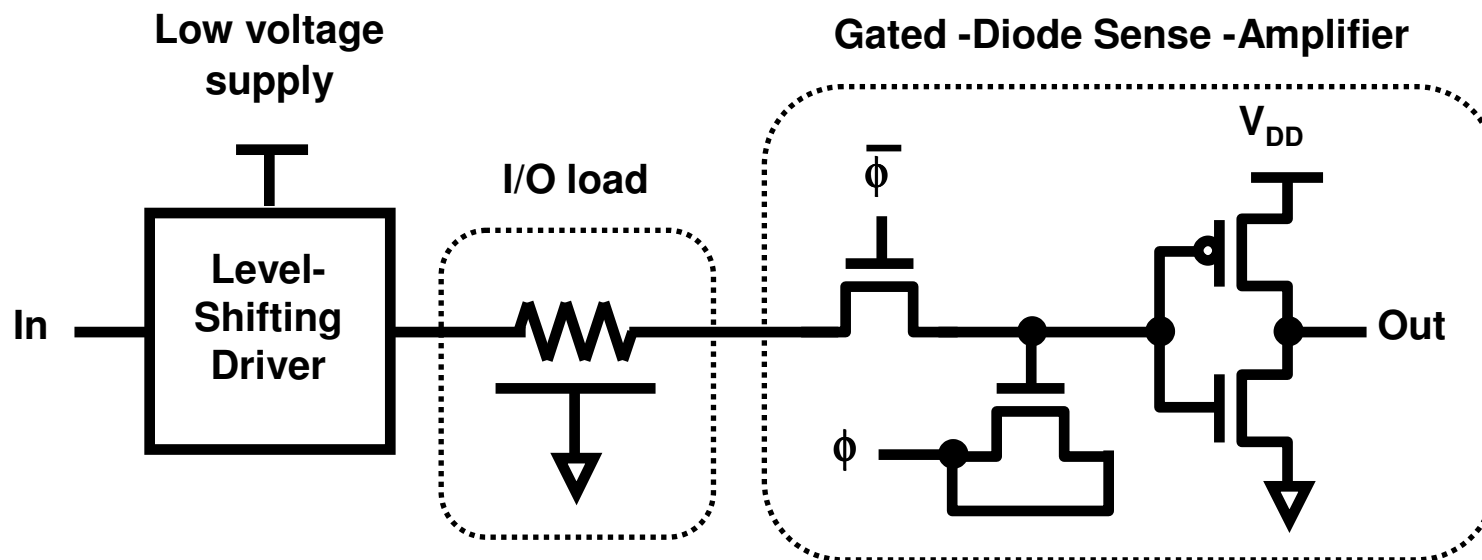- Low voltage (e.g. 0.25V) driver, significantly reduced power consumption on final driver: $\sim (0.25/0.925)^2 = 13.7$
 - Full V_{DD} on the gates of the nMOS drivers for high speed
- Gated diode receiver
 - Recover data back to full V_{DD} swing



Three Dimensional Silicon Integration

Performance

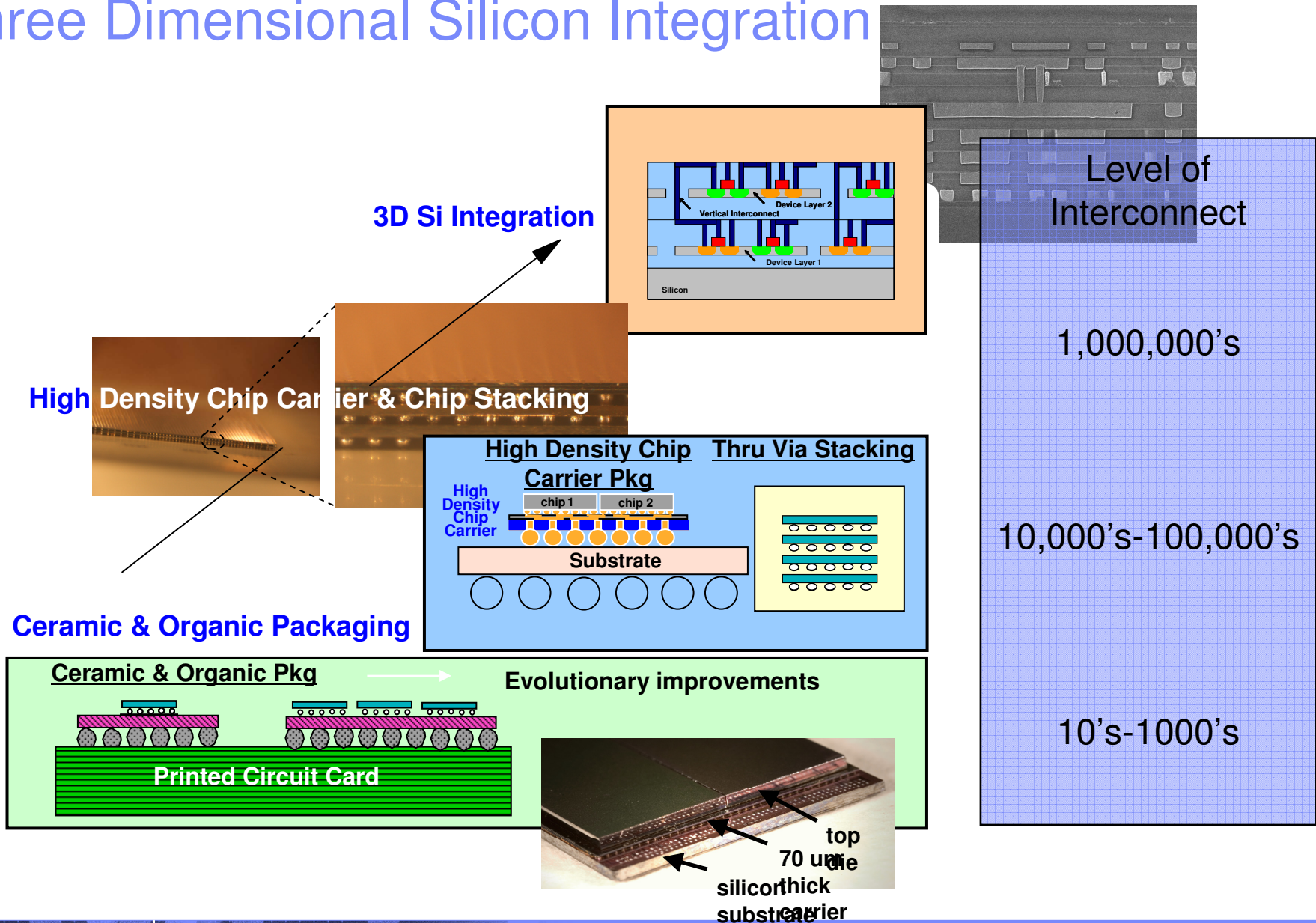

Low voltage scaling

Parameter	1→0.5V	Scaling Factor
Chip operating voltage	0.5	1
Chip operating frequency	0.33	κ
Device density	1	κ^2
Power density	0.056	κ^2
Power line energy loss	0.22–0.44	κ^2
Power line voltage instability	0.07–0.14	κ^2




Sub-Threshold Engineering

Beating the sub-threshold slope limit

$$T \sim \frac{E^2}{\sqrt{E_G}} e^{-B \frac{\sqrt{E_G^3}}{E}} \sim \frac{\sqrt{E_G^3}}{l^2} e^{-B \sqrt{E_G} l}$$

$$S \sim \frac{V_{gs}^2}{2V_{gs} + D(V_{gs}, V_{ds})}$$

Krishna K. Bhwalka et al. 2005

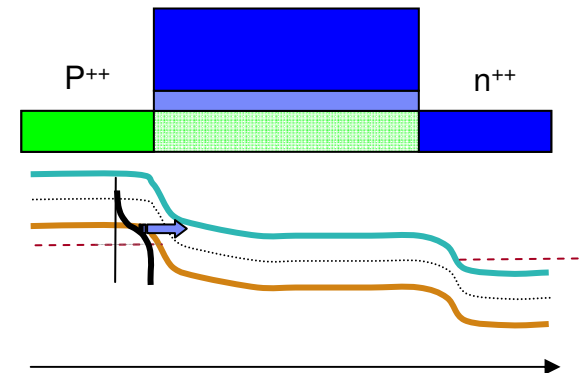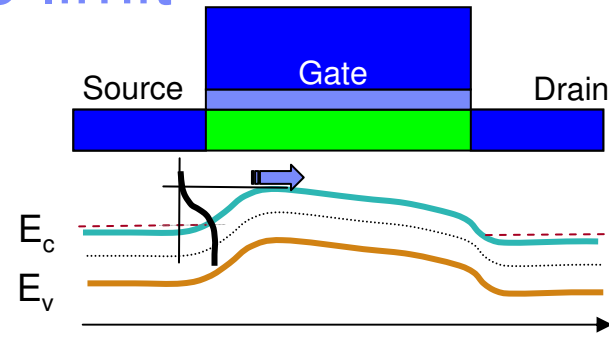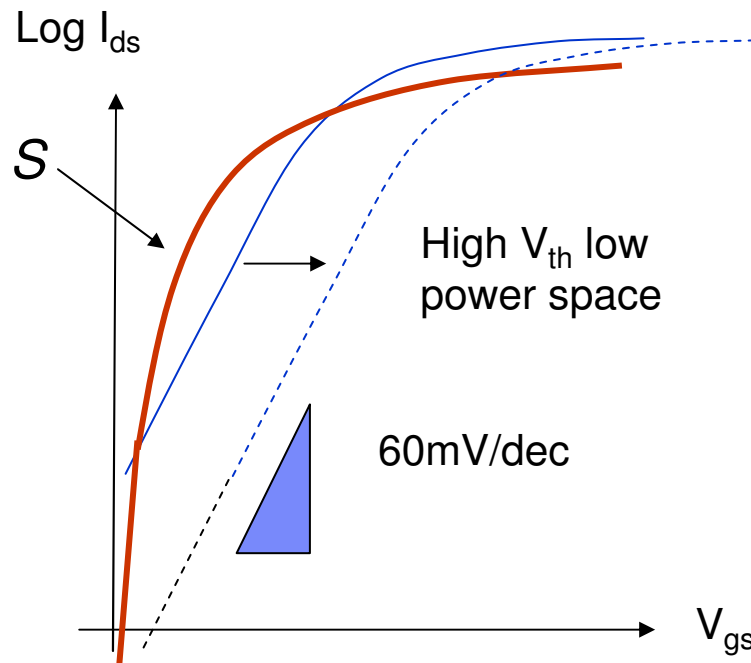



- Tunnel FETs show strong voltage dependence of sub-threshold slope
- On current not yet on par with conventional high performance FETs at comparable voltages

Beating the sub-threshold slope limit

$$T \sim \frac{E^2}{\sqrt{E_G}} e^{-B \frac{\sqrt{E_G^3}}{E}} \sim \frac{\sqrt{E_G^3}}{l^2} e^{-B \sqrt{E_G} l}$$



$$S \sim \frac{V_{gs}^2}{2V_{gs} + D(V_{gs}, V_{ds})}$$

Krishna K. Bhawalka et al. 2005

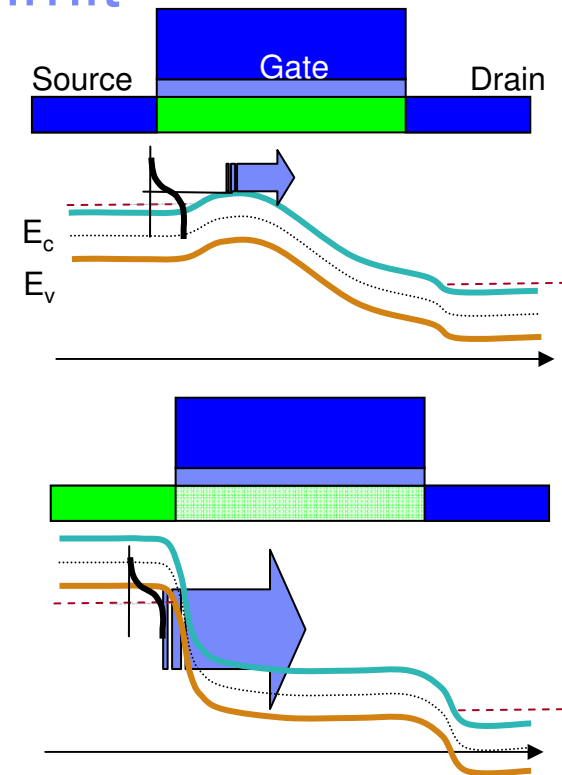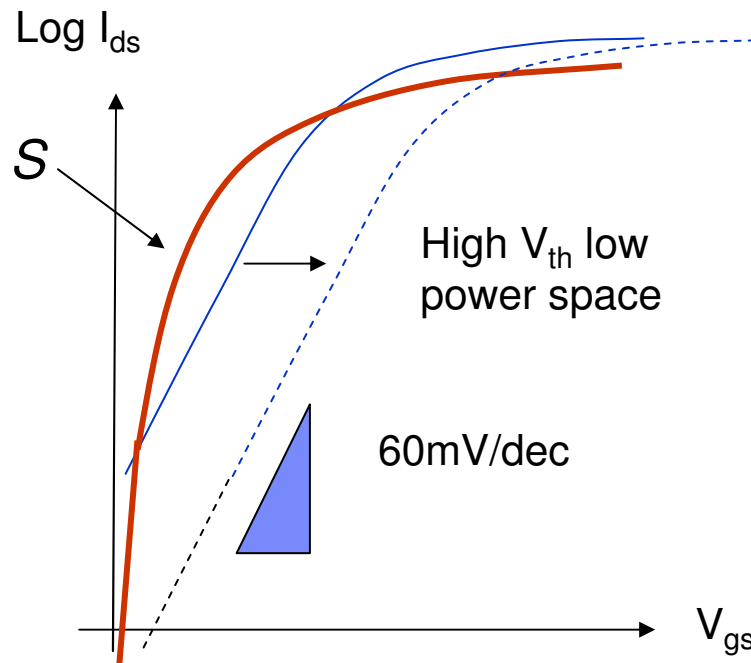



- Tunnel FETs show strong voltage dependence of sub-threshold slope
- On current not yet on par with conventional high performance FETs at comparable voltages

Supply voltage for max performance

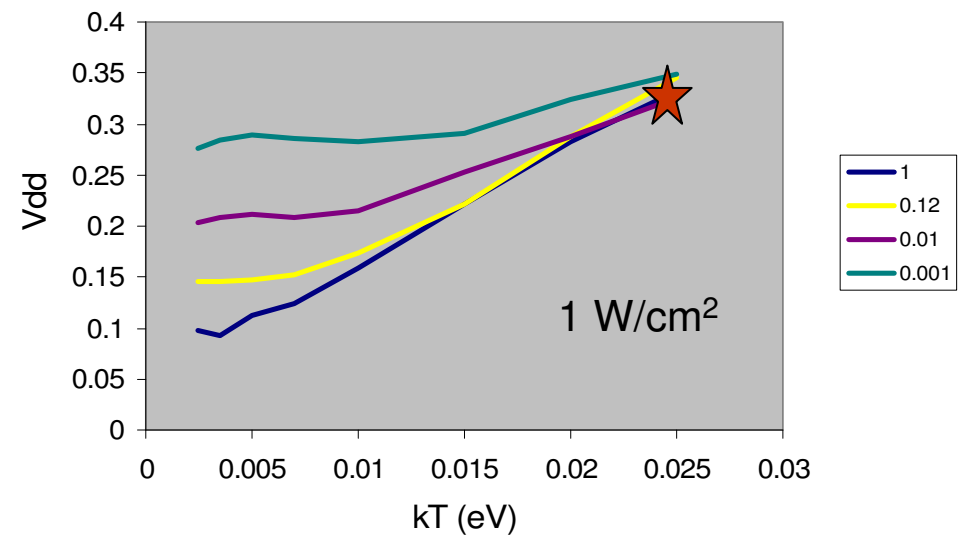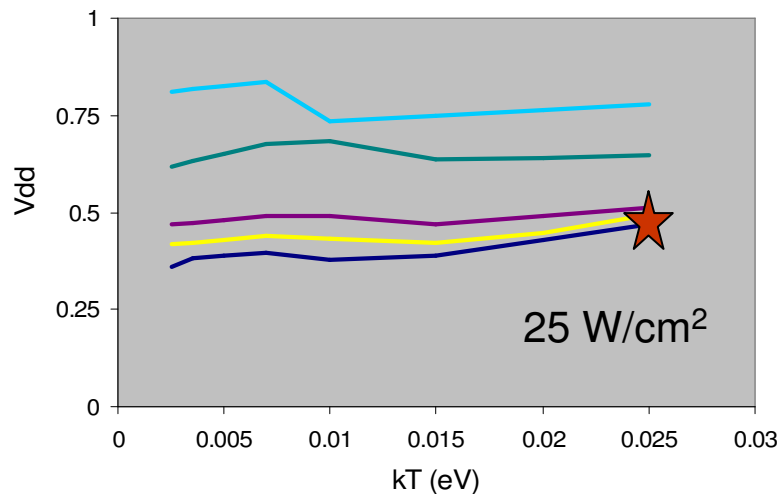



- For high power parts there is little advantage for supply voltage reduction due to steep sub threshold devices
- For low power parts there is a significant power supply reduction potential if drive current equivalent to conventional FET can be achieved

SS Engineering - 22nm node

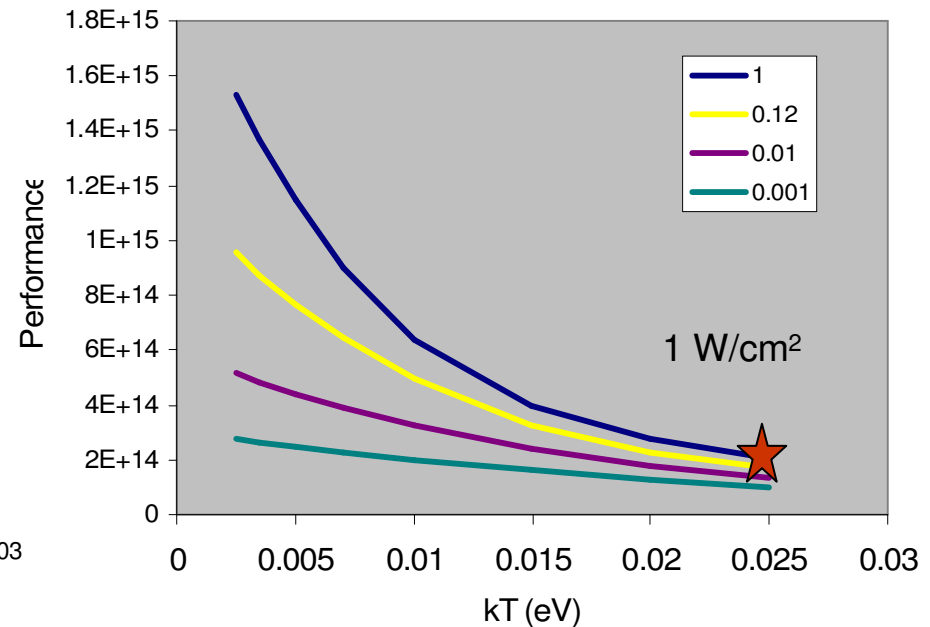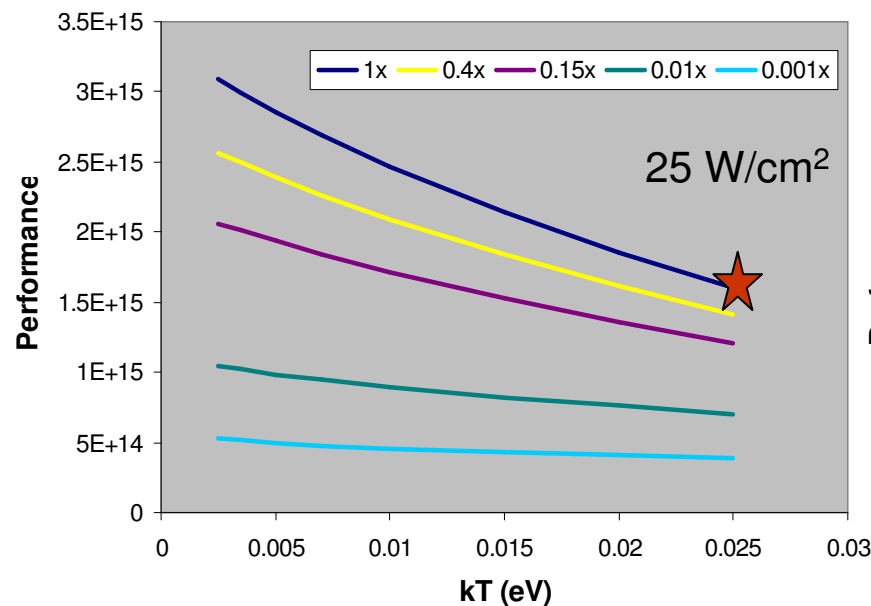

- Performance SS slope trade-off window small for high power case
- For low power space there is a large trade-off window performance versus SS-slope

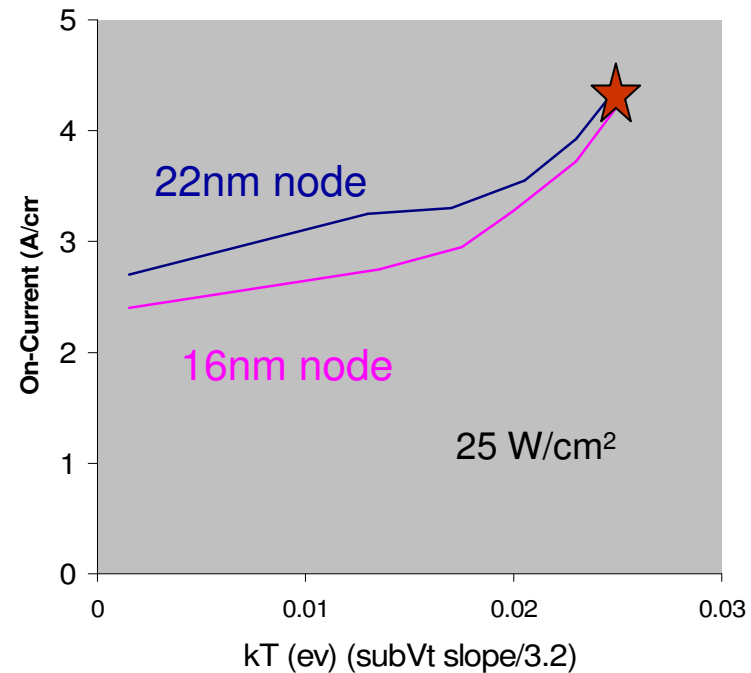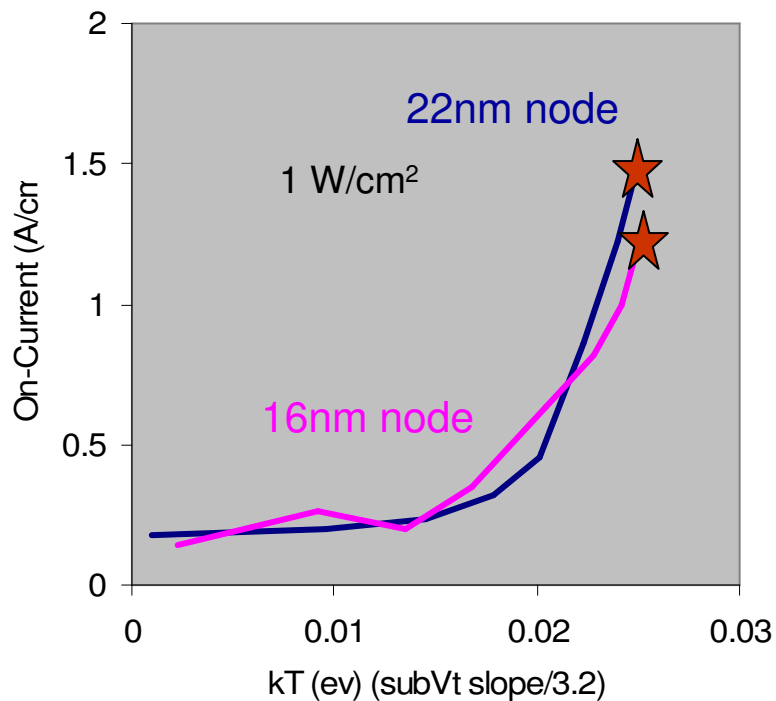On-current vs SS-slope, for constant performance





- High power/ performance: can only tolerate 30% drive current degradation
- Low power / performance: can tolerate x 10 degradation of drive current

Adiabatic Computing

Adiabatic charging

How much energy must be dissipated to charge a capacitor?



Abrupt method

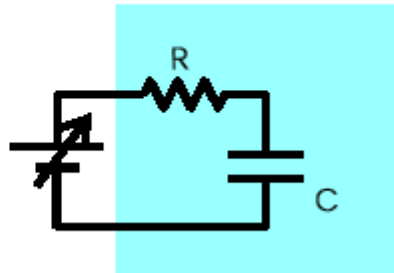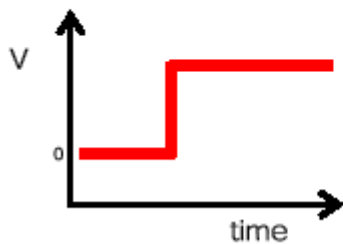

$$E = \frac{1}{2} CV^2$$

Quasi-static Charging

(aka 'adiabatic')

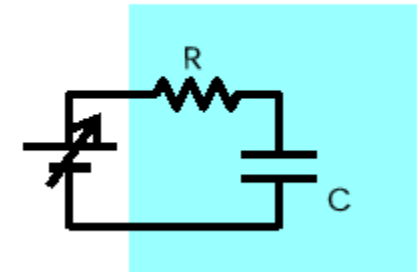
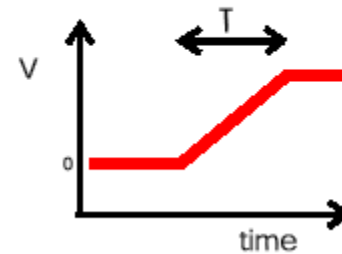


$$E = \frac{1}{2} CV^2 \left(\frac{2RC}{T} \right)$$

This assumes $T \gg RC$.

(There's an extra factor of $\pi^2/8$ for a sinusoidal ramp.)

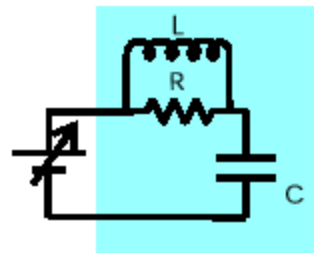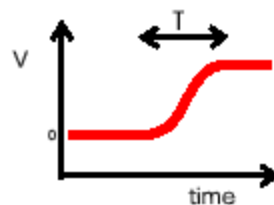Quasi-static Charging + Superconductivity



Charging through a superconductor, which behaves as an inductor and resistor in parallel.

$$E = \frac{\pi^4}{8} CV^2 \frac{RC(L/R)^2}{T^3}$$



This assumes $T \gg RC$ and $T \gg L/R$.

(To implement logic in this system would require superconducting FETs. Such FETs are possible, but there have been very few experimental results.)

Adiabatic computing

- All logic transitions must be directly driven by a clock waveform passing through FETs, Output is cycled back to input
 - Transitions cannot ripple through statically powered gates as in conventional logic.
- The ramp rate of the clock waveforms must be low to save energy.
- Try never to turn on an FET while there is a voltage difference between source and drain, since this would result in dissipation.
 - Requires multiple clock waveforms

Clock Synchronization

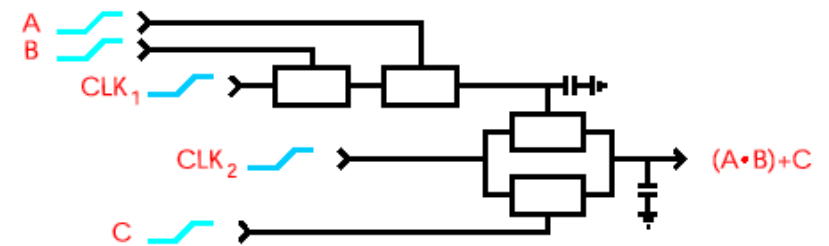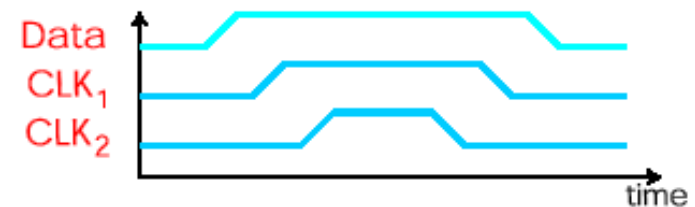


J. S. Hall 'Electroid' Switches)

Adiabatic computing

- If $A = '1'$ and $B = '0'$, or $A = '0'$ and $B = '1'$: Charge oscillates between input and output.
 - In each cycle of the resonator (clock), the logic signal is created and then removed from the output node capacitor.
- If $A = B = '0'$ or $A = B = '1'$: Output decoupled from input, and output kept to ground
 - Clock participates energy, per half cycle
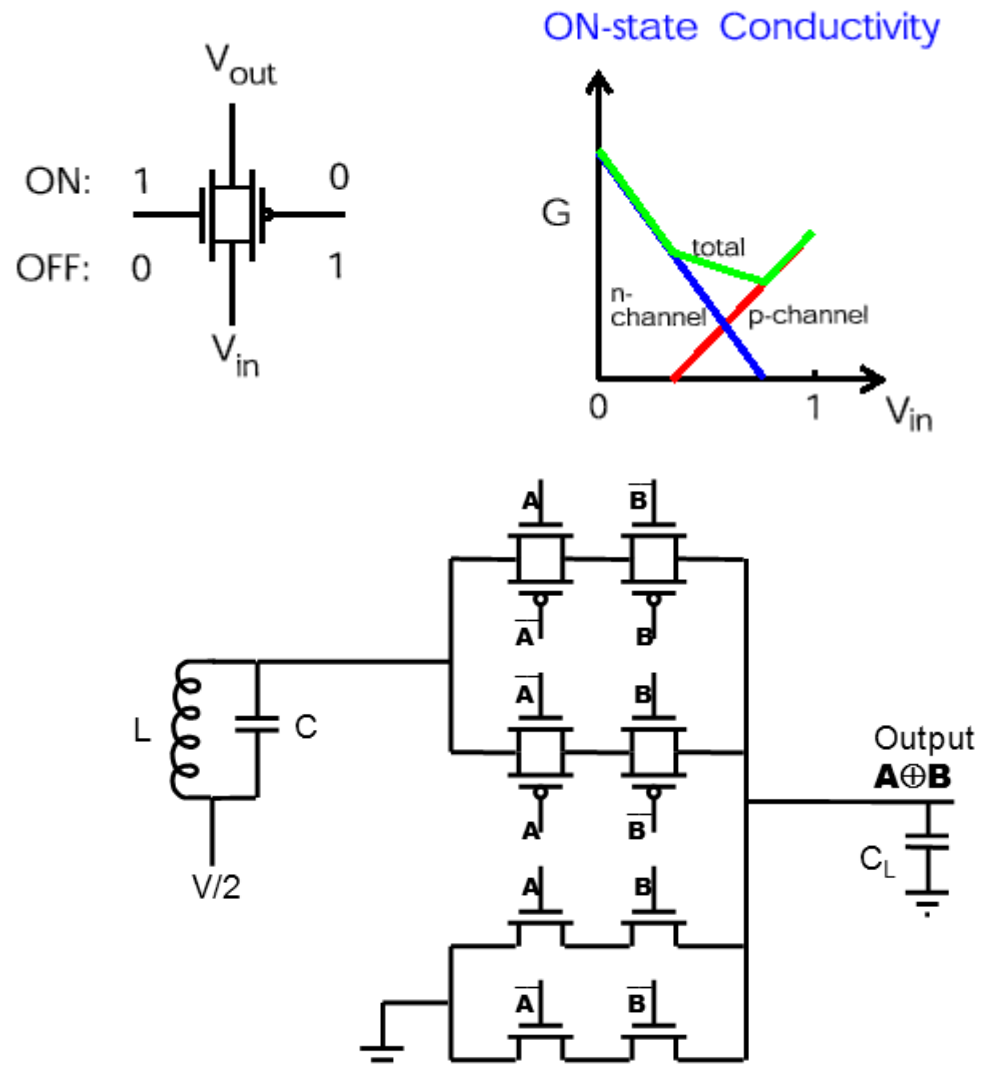
$$E_{diss} = \frac{\pi}{8} \frac{C_L V^2}{Q} = \frac{\pi^2}{4} f R C_L^2 V^2$$




Adiabatic CMOS penalty factors relative to conventional CMOS

	#FETs	CPI	CV ² Energy	comment
Dual Rail	2x	-	2x	Twice as many nodes
Logic density	$\frac{3}{4}x$	-	$\frac{3}{4}x$	Dual rail => no inverters
Uncompute	1.5x	1.5x	2x	Mixed retractile and pipeline
Generate control signals	$\frac{4}{3}x$	-	1.5x	
Clock supply	1x	7x	1.5x	No ripple: drive every transition
$V_{DD} > 2V_T$	1x	-	4x	~double supply voltage
TOTALS	3x	10x	27x	

Incomplete reversibility also sets a lower limit on energy savings.

Compare to adiabatic to CMOS

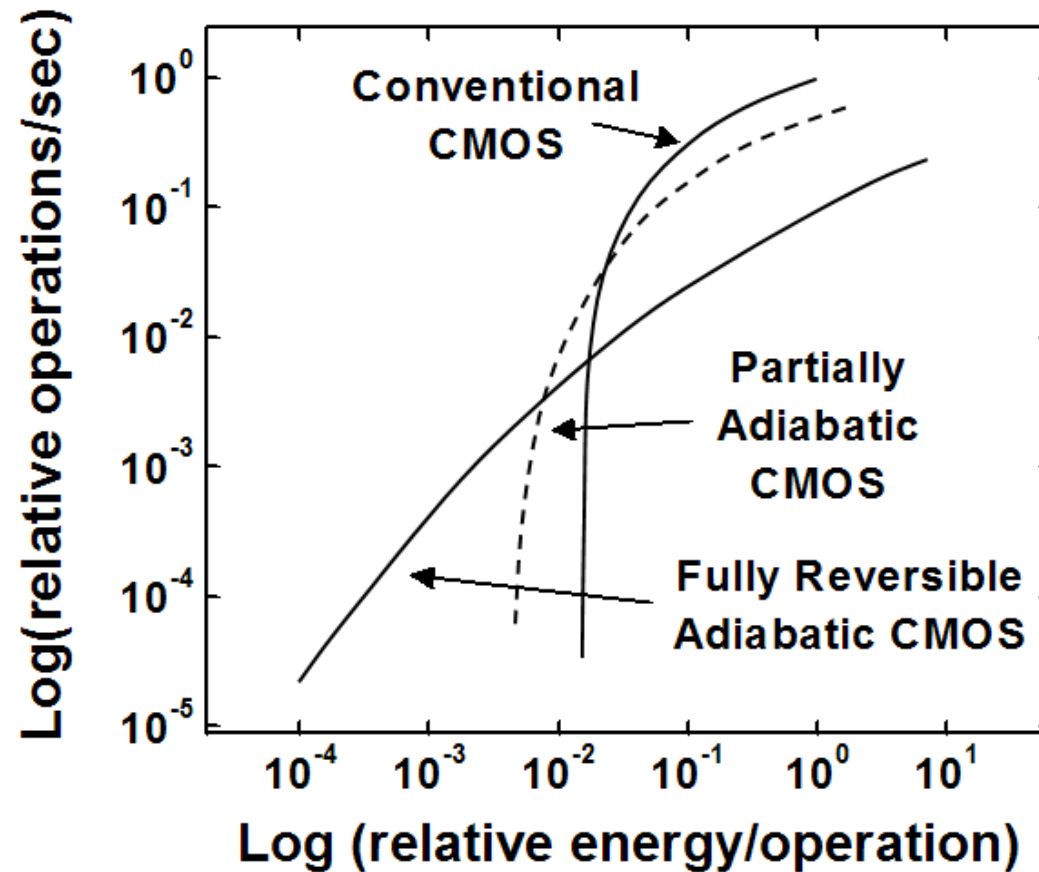

Summary

- Classical CMOS has still life left
 - Fully depleted devices will offer additional knobs for gate length scaling
 - Careful analysis of power delivery and I/Os show opportunities to reduce power losses in the system
 - Low voltage operation is biggest knob for power reduction, however need massive parallelism to get performance back and watch out for a low voltage cache solution
- Sub-threshold engineering
 - Steep sub-threshold devices have their place in the low power applications
 - Need to push devices to obtain at least 10% on current as conventional device
- Adiabatic computing
 - Concepts are there, not clear where application space is
 - This needs further research

Acknowledgement

Leland Chang

Steve Koester

Brian Ji

David Frank

Matt Wordemann