AD-A956 129

(2)

NOSC

NOSC TD 116
Vol 1

NOSC TD 116
Vol 1

Technical Document 116
Volume 1

NUMERICAL ELECTROMAGNETICS CODE (NEC) - METHOD OF MOMENTS

A user-oriented computer code for analysis of the electromagnetic response of antennas and other metal structures

Part I: Program Description-Theory
Part II: Program Description-Code
(Vol 2 contains Part III: User's Guide)

GJ Burke and AJ Pogio
(Lawrence Livermore Laboratory)

January 1981

Prepared by
LAWRENCE LIVERMORE LABORATORY
(Report UCID 18834)

Prepared for
NAVAL ELECTRONIC SYSTEMS COMMAND
(NAVELEX 3041)

Approved for public release; distribution unlimited

NAVAL OCEAN SYSTEMS CENTER
SAN DIEGO, CALIFORNIA 92152

NAVAL OCEAN SYSTEMS CENTER, SAN DIEGO, CA 92152

AN ACTIVITY OF THE NAVAL MATERIAL COMMAND

SL GUILLE, CAPT, USN
Commander

HL BLOOD
Technical Director

ADMINISTRATIVE INFORMATION

Work was performed by GJ Burke and AJ Poggio, of the Lawrence Livermore Laboratory, under MIPR-N0095376MP, as part of Program Element 62543N, Project XF43453401 (NOSC 8105-CM41) for Naval Electronic Systems Command, NAVELEX 3041. This document covers work up to September 1980.

Released by
MS Kvigne, Head
Communications Research and
Technology Division

Under authority of
HD Smith, Head
Communications Systems and
Technology Department

UCID-18834

DTIC QUALITY INSPECTED 4

Accession For
NTIS GRA&I
DTIC TAB
Unannounced
Justification
By
Distribution/
Availability Codes
Dist | Avail and/or Special
A-1

NUMERICAL ELECTROMAGNETICS CODE (NEC) - METHOD OF MOMENTS

PART I: PROGRAM DESCRIPTION - THEORY

G. J. Burke
A. J. Poggio

January 1981

Lawrence Livermore National Laboratory

This is an informal report intended primarily for internal or limited external distribution. The opinions and conclusions stated are those of the author and may or may not be those of the Laboratory.

Work performed under the auspices of the U.S. Department of Energy by the Lawrence Livermore National Laboratory under Contract W-7405-Eng-48.

92-28867



345129

92 11 04 003

DISCLAIMER

This document was prepared as an account of work sponsored by an agency of the United States Government. Neither the United States Government nor the University of California nor any of their employees, makes any warranty, express or implied, or assumes any legal liability or responsibility for the accuracy, completeness, or usefulness of any information, apparatus, product, or process disclosed, or represents that its use would not infringe privately owned rights. Reference herein to any specific commercial products, process, or service by trade name, trademark, manufacturer, or otherwise, does not necessarily constitute or imply its endorsement, recommendation, or favoring by the United States Government or the University of California. The views and opinions of authors expressed herein do not necessarily state or reflect those of the United States Government or the University of California, and shall not be used for advertising or product endorsement purposes.

Printed in the United States of America
Available from
National Technical Information Service
U.S Department of Commerce
5285 Port Royal Road
Springfield, VA 22161

Price Code	Page Range
A01	Microfiche
Papercopy Prices	
A02	001 - 050
A03	051 - 100
A04	101 - 200
A05	201 - 300
A06	301 - 400
A07	401 - 500
A08	501 - 600
A09	601

UNCLASSIFIED

SECURITY CLASSIFICATION OF THIS PAGE (When Data Entered)

REPORT DOCUMENTATION PAGE		READ INSTRUCTIONS BEFORE COMPLETING FORM
1. REPORT NUMBER NOSC Technical Document 116 (TD 116) vol 1	2. GOVT ACCESSION NO.	3. RECIPIENT'S CATALOG NUMBER
4. TITLE (and Subtitle) NUMERICAL ELECTROMAGNETICS CODE (NEC) – METHOD OF MOMENTS; A user-oriented computer code for analysis of the electromagnetic response of antennas and other metal structures		5. TYPE OF REPORT & PERIOD COVERED Technical document Up to September 1980 6. PERFORMING ORG. REPORT NUMBER UCID 18834
7. AUTHOR(s) GJ Burke and AJ Poggio Lawrence Livermore Laboratory		8. CONTRACT OR GRANT NUMBER(s) MIPR-N0095376MP
9. PERFORMING ORGANIZATION NAME AND ADDRESS Naval Ocean Systems Center (Code 8112) San Diego CA 92152		10. PROGRAM ELEMENT, PROJECT, TASK AREA & WORK UNIT NUMBERS PE 62543N, Project XF43453401 (NOSC 8105-CM41)
11. CONTROLLING OFFICE NAME AND ADDRESS Naval Electronic Systems Command NAVELEX 3041 Washington DC 20360		12. REPORT DATE January 1981 – latest revision 13. NUMBER OF PAGES (as revised) Part I-81; Part II-433
14. MONITORING AGENCY NAME & ADDRESS(if different from Controlling Office)		15. SECURITY CLASS. (of this report) Unclassified 15a. DECLASSIFICATION/DOWNGRADING SCHEDULE

16. DISTRIBUTION STATEMENT (of this Report)

Approved for public release; distribution unlimited

17. DISTRIBUTION STATEMENT (of the abstract entered in Block 20, if different from Report)

18. SUPPLEMENTARY NOTES

Volume 1 contains Part I: Program Description -- Theory (revised 2 January 1980)
Part II: Program Description – Code (revised January 1981)
Volume 2 contains Part III: User's Guide (revised 2 January 1980)

19. KEY WORDS (Continue on reverse side if necessary and identify by block number)

Numerical Electromagnetics Code (NEC-2)
Numerical analysis
Antenna response
Electromagnetic radiation

20. ABSTRACT (Continue on reverse side if necessary and identify by block number)

The Numerical Electromagnetics Code (NEC-2) is a computer code for analyzing the electromagnetic response of an arbitrary structure consisting of wires and surfaces in free space or over a ground plane. The analysis is accomplished by the numerical solution of integral equations for induced currents. The solution includes a Numerical Green's Function for partitioned-matrix solution and a treatment for lossy grounds that is accurate for antennas very close to the ground surface. The excitation may be an incident plane wave or a voltage source on a wire, while the output may include current and charge density, electric or magnetic field in the vicinity of the structure, and radiated fields. Other options compute the maximum coupling between antennas and facilitate

DD FORM 1 JAN 73 1473 EDITION OF 1 NOV 65 IS OBSOLETE
S/N 0102-LF-014-6601

UNCLASSIFIED

SECURITY CLASSIFICATION OF THIS PAGE (When Data Entered)

structure input. Hence the code may be used for antenna analysis, EMP, or scattering studies.

Part I of the document includes the equations on which the code is based and a discussion of the approximations and numerical methods used in the numerical solution. Some comparisons to demonstrate the range of accuracy of approximations are also included. Details of the coding and a User's Guide are provided as parts II and III, respectively.

Preface

The Numerical Electromagnetics Code (NEC) has been developed at the Lawrence Livermore Laboratory, Livermore, California, under the sponsorship of the Naval Ocean Systems Center and the Air Force Weapons Laboratory. It is an advanced version of the Antenna Modeling Program (AMP) developed in the early 1970's by MBAssociates for the Naval Research Laboratory, Naval Ship Engineering Center, U.S. Army ECOM/Communications Systems, U.S. Army Strategic Communications Command, and Rome Air Development Center under Office of Naval Research Contract N00014-71-C-0187. The present version of NEC is the result of efforts by G. J. Burke and A. J. Poggio of Lawrence Livermore Laboratory.

The documentation for NEC consists of three volumes:

Part I: NEC Program Description — Theory

Part II: NEC Program Description — Code

Part III: NEC User's Guide

The documentation has been prepared by using the AMP documents as foundations and by modifying those as needed. In some cases this led to minor changes in the original documents while in many cases major modifications were required.

Over the years many individuals have been contributors to AMP and NEC and are acknowledged here as follows:

R. W. Adams
J. N. Brittingham
G. J. Burke
F. J. Deadrick
K. K. Hazard
D. L. Knepp
D. L. Lager
R. J. Lytle
E. K. Miller
J. B. Morton
G. M. Pjerrou
A. J. Poggio
E. S. Selden

The support for the development of NEC-2 at the Lawrence Livermore Laboratory has been provided by the Naval Ocean Systems Center under MIPR-N0095376MP. Cognizant individuals under whom this project was carried out include: J. Rockway and J. Logan. Previous development of NEC also included the support of the Air Force Weapons Laboratory (Project Order 76-090) and was monitored by J. Castillo and TSgt. H. Goodwin.

Work was performed under the auspices of the U.S. Department of Energy under contract No. W-7405-Eng-48. Reference to a company or product name

does not imply approval or recommendation of the product by the University of California or the U.S. Department of Energy to the exclusion of others that may be suitable.

Contents

Section		Page
I.	INTRODUCTION	1
II.	THE INTEGRAL EQUATIONS FOR FREE SPACE	3
	1. The Electric Field Integral Equation (EFIE)	3
	2. The Magnetic Field Integral Equation (MFIE)	5
	3. The EFIE-MFIE Hybrid Equation	7
III.	NUMERICAL SOLUTION	9
	1. Current Expansion on Wires	10
	2. Current Expansion on Surfaces	18
	3. Evaluation of the Fields	20
	4. The Matrix Equation for Current	30
	5. Solution of the Matrix Equation	31
IV.	EFFECT OF A GROUND PLANE	37
	1. The Sommerfeld/Norton Method	38
	2. Numerical Evaluation of the Sommerfeld Integrals	50
	3. The Image and Reflection-Coefficient Methods	55
V.	MODELING OF ANTENNAS	62
	1. Source Modeling	62
	2. Nonradiating Networks	67
	3. Transmission Line Modeling	72
	4. Lumped or Distributed Loading	74
	5. Radiated Field Calculation	75
	6. Antenna Coupling	78
REFERENCES		79

List of Illustrations

Figure		Page
1.	Current Basis Functions and Sum on a Four Segment Wire	13
2.	Segments Covered by the i^{th} Basis Function	13
3.	Detail of the Connection of a Wire to a Surface	20
4.	Current-Filament Geometry for the Thin-Wire Kernel	21
5.	Current Geometry for the Extended Thin-Wire Kernel	24
6.	Coordinates for Evaluating the Field of a Current Element Over Ground	39
7.	Real (a) and Imaginary (b) Parts of I_β^V for $\varepsilon_1/\varepsilon_o = 4$, $\sigma_1 =$ 0.001 mhos/m, frequency = 10 MHz	46
8.	Real (a) and Imaginary (b) Parts of I_z^V for $\varepsilon_1/\varepsilon_o = 4$, $\sigma_1 =$ 0.001 mhos/m, frequency = 10 MHz	47
9.	Real (a) and Imaginary (b) Parts of I_β^H for $\varepsilon_1/\varepsilon_o = 4$, $\sigma_1 =$ 0.001 mhos/m, frequency = 10 MHz	47
10.	Real (a) and Imaginary (b) Parts of I^H for $\varepsilon_1/\varepsilon_o = 4$, $\sigma_1 =$ 0.001 mhos/m, frequency = 10 MHz	48
11.	Real (a) and Imaginary (b) Parts of I_β^H for $\varepsilon_1/\varepsilon_o = 16, \sigma_1 = 0$	49
12.	Grid for Bivariate Interpolation of I's	50
13.	Contour for Evaluation of Bessel Function Form of Sommerfeld Integrals	51
14.	Contour for Evaluation of Hankel Function Form of Sommerfeld Integrals	53
15.	Contour for Hankel Function Form when Real Part k_1 is Large and Imaginary Part k_1 is Small	54
16.	Plane-Wave Reflection at an Interface	57
17.	Biconical Transmission Line Model of Source Region	64
18.	Field Plots for a Linear Dipole, $\Omega = 15$	67
19.	Voltage and Current Reference Directions at Network Ports	69
20.	Network Connection to Segments	69
21.	Network Port and Voltage Source Connected to a Segment	70
22.	Current Distribution on a Two-Wire Transmission Line from NEC Compared with the Ideal Transmission Line Solution	73

Section I
Introduction

The Numerical Electromagnetics Code (NEC-2) is a user-oriented computer code for the analysis of the electromagnetic response of antennas and other metal structures. It is built around the numerical solution of integral equations for the currents induced on the structure by sources or incident fields. This approach avoids many of the simplifying assumptions required by other solution methods and provides a highly accurate and versatile tool for electromagnetic analysis.

The code combines an integral equation for smooth surfaces with one specialized to wires to provide for convenient and accurate modeling of a wide range of structures. A model may include nonradiating networks and transmission lines connecting parts of the structure, perfect or imperfect conductors, and lumped-element loading. A structure may also be modeled over a ground plane that may be either a perfect or imperfect conductor.

The excitation may be either voltage sources on the structure or an incident plane wave of linear or elliptic polarization. The output may include induced currents and charges, near electric or magnetic fields, and radiated fields. Hence, the program is suited to either antenna analysis or scattering and EMP studies. NEC and its predecessor AMP have been used successfully to model a wide range of antennas including complex environments such as ships. Results from modeling several antennas with NEC are shown in refs. 36, 37, and 38 with measured data for comparison.

The integral-equation approach is best suited to structures with dimensions up to several wavelengths. Although there is no theoretical size limit, the numerical solution requires a matrix equation of increasing order as the structure size is increased relative to wavelength. Hence, modeling very large structures may require more computer time and file storage than is practical on a particular machine. In such cases standard high-frequency approximations such as geometrical or physical optics, or geometric theory of diffraction may be more suitable than the integral equation approach used in NEC.

The code NEC-2 is the latest in a series of electromagnetics codes, each of which has built upon the previous one. The first in the series was the code BRACT which was developed at MBAssociates in San Ramon, California, under the funding of the Air Force Space and Missiles Systems Organization (refs. 1 and 2). BRACT was specialized to scattering by arbitrary thin-wire configurations.

The code AMP followed BRACT and was developed at MBAssociates with funding from the Naval Research Laboratory, Naval Ship Engineering Center, U.S. Army ECOM/Communications Systems, U.S. Army Strategic Communications Command, and Rome Air Development Center under Office of Naval Research Contract N00014-71-C-0187. AMP uses the same numerical solution method as BRACT with the addition of the capability of modeling a structure over a ground plane and an option to use file storage to greatly increase the maximum structure size that may be modeled. The program input and output were extensively revised for AMP so that the code could be used with a minimum of learning and computer programming experience. AMP includes extensive documentation to aid in understanding, using, and modifying the code (refs. 3, 4 and 5).

A modeling option specialized to surfaces was added to the wire modeling capabilities of AMP in the AMP2 code (ref. 6). A simplified approximation for large interaction distances was also included in AMP2 to reduce running time for large structures.

The code NEC-1 added to AMP2 a more accurate current expansion along wires and at multiple wire junctions, and an option in the wire modeling technique for greater accuracy on thick wires. A new model for a voltage source was added and several other modifications made for increased accuracy and efficiency.

NEC-2 retains all features of NEC-1 except for a restart option. Major additions in NEC-2 are the Numerical Green's Function for partitioned-matrix solution and a treatment for lossy grounds that is accurate for antennas very close to the ground surface. NEC-2 also includes an option to compute maximum coupling between antennas and new options for structure input.

Part I of this document describes the equations and numerical methods used in NEC. Part III: NEC User's Guide (ref. 7) contains instructions for using the code, including preparation of input and interpretation of output. Part II: NEC Program Description — Code (ref. 8) describes the coding in detail. The user encountering the code for the first time should begin with the User's Guide and try modeling some simple antennas. Part II will be of interest mainly to someone attempting to modify the code. Reading part I will be useful to the new user of NEC-2, however, since an understanding of the theory and solution method will assist in the proper application of the code.

Section II
The Integral Equations For Free Space

The NEC program uses both an electric-field integral equation (EFIE) and a magnetic-field integral equation (MFIE) to model the electromagnetic response of general structures. Each equation has advantages for particular structure types. The EFIE is well suited for thin-wire structures of small or vanishing conductor volume while the MFIE, which fails for the thin-wire case, is more attractive for voluminous structures, especially those having large smooth surfaces. The EFIE can also be used to model surfaces and is preferred for thin structures where there is little separation between a front and back surface. Although the EFIE is specialized to thin wires in this program, it has been used to represent surfaces by wire grids with reasonable success for far-field quantities but with variable accuracy for surface fields. For a structure containing both wires and surfaces the EFIE and MFIE are coupled. This combination of the EFIE and MFIE was proposed and used by Albertsen, Hansen, and Jensen at the Technical University of Denmark (ref. 9) although the details of their numerical solution differ from those in NEC. A rigorous derivation of the EFIE and MFIE used in NEC is given by Poggio and Miller (ref. 10). The equations and their derivation are outlined in the following sections.

1. THE ELECTRIC FIELD INTEGRAL EQUATION (EFIE)

The form of the EFIE used in NEC follows from an integral representation for the electric field of a volume current distribution $\vec{J}$,

$$\vec{E}(\vec{r}) = \frac{-j\eta}{4\pi k} \int_V \vec{J}(\vec{r}') \cdot \overline{\overline{G}}(\vec{r}, \vec{r}')\, dV', \tag{1}$$

where

$$\overline{\overline{G}}(\vec{r}, \vec{r}') = (k^2\overline{\overline{I}} + \nabla\nabla)g(\vec{r}, \vec{r}'),$$

$$g(\vec{r}, \vec{r}') = \exp(-jk|\vec{r} - \vec{r}'|)/|\vec{r} - \vec{r}'|,$$

$$k = \omega\sqrt{\mu_o \varepsilon_o},$$

$$\eta = \sqrt{\mu_o/\varepsilon_o}$$

and the time convention is $\exp(j\omega t)$. $\bar{\bar{I}}$ is the identity dyad $(\hat{x}\hat{x} + \hat{y}\hat{y} + \hat{z}\hat{z})$. When the current distribution is limited to the surface of a perfectly conducting body, equation (1) becomes

$$\vec{E}(\vec{r}) = \frac{-j\eta}{4\pi k} \int_S \vec{J}_s(\vec{r}') \cdot \bar{\bar{G}}(\vec{r}, \vec{r}')\, dA', \tag{2}$$

with $\vec{J}_s$ the surface current density. The observation point $\vec{r}$ is restricted to be off the surface S so that $\vec{r} \neq \vec{r}'$.

If $\vec{r}$ approaches S as a limit, equation (2) becomes

$$\vec{E}(\vec{r}) = \frac{-j\eta}{4\pi k} \oint_S \vec{J}_s(\vec{r}') \cdot \bar{\bar{G}}(\vec{r}, \vec{r}')\, dA', \tag{3}$$

where the principal value integral, $\oint$, is indicated since $g(\vec{r}, \vec{r}')$ is now unbounded.

An integral equation for the current induced on S by an incident field $\vec{E}^I$ can be obtained from equation (3) and the boundary condition for $\vec{r} \in S$,

$$\hat{n}(\vec{r}) \times \left[\vec{E}^s(\vec{r}) + \vec{E}^I(\vec{r}) \right] = 0, \tag{4}$$

where $\hat{n}(\vec{r})$ is the unit normal vector of the surface at $\vec{r}$ and $\vec{E}^s$ is the field due to the induced current $\vec{J}_s$. Substituting equation (3) for $\vec{E}^s$ yields the integral equation,

$$-\hat{n}(\vec{r}) \times \vec{E}^I(\vec{r}) = \frac{-j\eta}{4\pi k}\, \hat{n}(\vec{r}) \times$$

$$\oint_S \vec{J}_s(\vec{r}') \cdot (k^2 \bar{\bar{I}} + \nabla\nabla) g(\vec{r}, \vec{r}')\, dA'. \tag{5}$$

The vector integral in equation (5) can be reduced to a scalar integral equation when the conducting surface S is that of a cylindrical thin wire, thereby making the solution much easier. The assumptions applied for a thin wire, known as the thin-wire approximation, are as follows:

a. Transverse currents can be neglected relative to axial currents on the wire.

b. The circumferential variation in the axial current can be neglected.

c. The current can be represented by a filament on the wire axis.

d. The boundary condition on the electric field need be enforced in the axial direction only.

These widely used approximations are valid as long as the wire radius is much less than the wavelength and much less than the wire length. An alternate kernel for the EFIE, based on an extended thin-wire approximation in which condition c is relaxed, is also included in NEC for wires having too large a radius for the thin-wire approximation (ref. 11).

From assumptions a, b and c, the surface current $\vec{J}_s(\vec{r})$ on a wire of radius a can be replaced by a filamentary current I where

$$I(s)\hat{s} = 2\pi a\vec{J}_s(\vec{r}),$$

s = distance parameter along the wire axis at $\vec{r}$, and

$\hat{s}$ = unit vector tangent to the wire axis at $\vec{r}$.

Equation (5) then becomes

$$-\hat{n}(\vec{r}) \times \vec{E}^I(\vec{r}) = \frac{-j\eta}{4\pi k}\hat{n}(\vec{r}) \times \int_L I(s')\left(k^2\hat{s}' - \nabla\frac{\partial}{\partial s'}\right) g(\vec{r}, \vec{r}')\, ds', \qquad (6)$$

where the integration is over the length of the wire. Enforcing the boundary condition in the axial direction reduces Eq. (6) to the scalar equation,

$$-\hat{s} \cdot \vec{E}^I(\vec{r}) = \frac{-j\eta}{4\pi k}\int_L I(s')\left(k^2\hat{s}\cdot\hat{s}' - \frac{\partial^2}{\partial s\partial s'}\right) g(\vec{r}, \vec{r}')\, ds'. \qquad (7)$$

Since $\vec{r}'$ is now the point at s' on the wire axis while $\vec{r}$ is a point at s on the wire surface $|\vec{r} - \vec{r}'| \geq a$ and the integrand is bounded.

2. THE MAGNETIC FIELD INTEGRAL EQUATION (MFIE)

The MFIE is derived from the integral representation for the magnetic field of a surface current distribution $\vec{J}_s$,

$$\vec{H}^s(\vec{r}) = \frac{1}{4\pi} \int_S \vec{J}_s(\vec{r}') \times \nabla' g(\vec{r}, \vec{r}')\, dA', \tag{8}$$

where the differentiation is with respect to the integration variable $\vec{r}'$. If the current $\vec{J}_s$ is induced by an external incident field $\vec{H}^I$, then the total magnetic field inside the perfectly conducting surface must be zero. Hence, for $\vec{r}$ just inside the surface S,

$$\vec{H}^I(\vec{r}) + \vec{H}^s(\vec{r}) = 0, \tag{9}$$

where $\vec{H}^I$ is the incident field with the structure removed, and $\vec{H}^s$ is the scattered field given by equation (8). The integral equation for $\vec{J}_s$ may be obtained by letting $\vec{r}$ approach the surface point $\vec{r}_o$ from inside the surface along the normal $\hat{n}(\vec{r}_o)$. The surface component of equation (9) with equation (8) substituted for $\vec{H}^s$ is then

$$-\hat{n}(\vec{r}_o) \times \vec{H}^I(\vec{r}_o) = \hat{n}(\vec{r}_o) \times \frac{1}{4\pi} \lim_{\vec{r} \to \vec{r}_o} \int_S \vec{J}_s(\vec{r}') \times \nabla' g(\vec{r}, \vec{r}')\, dA',$$

where $\hat{n}(\vec{r}_o)$ is the outward directed normal vector at $\vec{r}_o$. The limit can be evaluated by using a result of potential theory (ref. 12) to yield the integral equation

$$-\hat{n}(\vec{r}_o) \times \vec{H}^I(\vec{r}_o) = -\frac{1}{2} \vec{J}_s(\vec{r}_o) + \frac{1}{4\pi} \int_S \hat{n}(\vec{r}_o) \times \left[\vec{J}_s(\vec{r}') \times \nabla' g(\vec{r}_o, \vec{r}')\right] dA'. \tag{10}$$

For solution in NEC, this vector integral equation is resolved into two scalar equations along the orthogonal surface vectors $\hat{t}_1$ and $\hat{t}_2$ where

$$\hat{t}_1(\vec{r}_o) \times \hat{t}_2(\vec{r}_o) = \hat{n}(\vec{r}_o).$$

By using the identity $\vec{u} \cdot (\vec{v} \times \vec{w}) = (\vec{u} \times \vec{v}) \cdot \vec{w}$ and noting that $\hat{t}_1 \times \hat{n} = -\hat{t}_2$ and $\hat{t}_2 \times \hat{n} = \hat{t}_1$, the scalar equations can be written,

$$\hat{t}_2(\vec{r}_o) \cdot \vec{H}^I(\vec{r}_o) = -\frac{1}{2}\hat{t}_1(\vec{r}_o) \cdot \vec{J}_s(\vec{r}_o) - \frac{1}{4\pi} \oint_S \hat{t}_2(\vec{r}_o) \cdot \left[\vec{J}_s(\vec{r}') \times \nabla' g(\vec{r}_o, \vec{r}')\right] dA'; \quad (11)$$

$$-\hat{t}_1(\vec{r}_o) \cdot \vec{H}^I(\vec{r}_o) = -\frac{1}{2}\hat{t}_2(\vec{r}_o) \cdot \vec{J}_s(\vec{r}_o) + \frac{1}{4\pi} \oint_S \hat{t}_1(\vec{r}_o) \cdot \left[\vec{J}_s(\vec{r}') \times \nabla' g(\vec{r}_o, \vec{r}')\right] dA'. \quad (12)$$

These two components suffice since there is no normal component of equation (10).

3. THE EFIE-MFIE HYBRID EQUATION

Program NEC uses the EFIE for thin wires and the MFIE for surfaces. For a structure consisting of both wires and surfaces, $\vec{r}$ in equation (7) is restricted to the wires, with the integral for $\vec{E}^s(\vec{r})$, extending over the complete structure. The thin-wire form of the integral in equation (7) is used over wires while the more general form of equation (5) must be used on surfaces. Likewise, $\vec{r}_o$ is restricted to surfaces in equations (11) and (12), with the integrals for $\vec{H}^s(\vec{r})$ extending over the complete structure. On wires the integral is simplified by the thin-wire approximation. The resulting coupled integral equations are, for $\vec{r}$ on wire surfaces,

$$-\hat{s} \cdot \vec{E}^I(\vec{r}) = \frac{-j\eta}{4\pi k} \int_L I(s')\left(k^2 \hat{s} \cdot \hat{s}' - \frac{\partial^2}{\partial s \partial s'}\right) g(\vec{r}, \vec{r}')\, ds' - \frac{j\eta}{4\pi k} \int_{S_1} \vec{J}_s(\vec{r}') \cdot \left[k^2 \hat{s} - \nabla' \frac{\partial}{\partial s}\right] g(\vec{r}, \vec{r}')\, dA', \quad (13)$$

and for $\vec{r}$ on surfaces excluding wires

$$\hat{t}_2(\vec{r}) \cdot \vec{H}^I(\vec{r}) = -\frac{1}{4\pi} \hat{t}_2(\vec{r}) \cdot \int_L I(s')\left(\hat{s}' \times \nabla' g(\vec{r},\vec{r}')\right) ds'$$

$$-\frac{1}{2} \hat{t}_1(\vec{r}) \cdot \vec{J}_s(\vec{r}) -$$

$$\frac{1}{4\pi} \oint_{S_1} \hat{t}_2(\vec{r}) \cdot \left[\vec{J}_s(\vec{r}') \times \nabla' g(\vec{r},\vec{r}')\right] dA', \quad (14)$$

and

$$-\hat{t}_1(\vec{r}) \cdot \vec{H}^I(\vec{r}) = \frac{1}{4\pi} \hat{t}_1(\vec{r}) \cdot \int_L I(s')\left(\hat{s}' \times \nabla' g(\vec{r},\vec{r}')\right) ds'$$

$$-\frac{1}{2} \hat{t}_2(\vec{r}) \cdot \vec{J}_s(\vec{r}) +$$

$$\frac{1}{4\pi} \oint_{S_1} \hat{t}_1(\vec{r}) \cdot \left[\vec{J}_s(\vec{r}') \times \nabla' g(\vec{r},\vec{r}')\right] dA'. \quad (15)$$

The symbol $\int_L$ represents integration over wires while $\oint_{S_1}$ represents integration over surfaces excluding wires. The numerical method used to solve equations (13), (14) and (15) is described in section III.

Section III
Numerical Solution

The integral equations (13), (14), and (15) are solved numerically in NEC by a form of the method of moments. An excellent general introduction to the method of moments can be found in R. F. Harrington's book, Field Computation by Moment Methods (ref. 13). A brief outline of the method follows.

The method of moments applies to a general linear-operator equation,

$$Lf = e, \tag{16}$$

where f is an unknown response, e is a known excitation, and L is a linear operator (an integral operator in the present case). The unknown function f may be expanded in a sum of basis functions, f_j, as

$$f = \sum_{j=1}^{N} \alpha_j f_j \ . \tag{17}$$

A set of equations for the coefficients α_j are then obtained by taking the inner product of equation (16) with a set of weighting functions $|w_i|$,

$$\langle w_i, Lf \rangle = \langle w_i, e \rangle \qquad i = 1, \ldots N \ . \tag{18}$$

Due to the linearity of L equation (17) substituted for f yields,

$$\sum_{j=1}^{N} \alpha_j \langle w_i, Lf_j \rangle = \langle w_i, e \rangle \ , \qquad i = 1, \ldots N \ .$$

This equation can be written in matrix notation as

$$[G]\ [A] = [E] \ , \tag{19}$$

where

$$G_{ij} = \langle w_i, Lf_j \rangle \ ,$$

$$A_j = \alpha_j \ ,$$

$$E_i = \langle w_i, e \rangle \ .$$

The solution is then

$$[A] = [G]^{-1}\,[E] \ .$$

For the solution of equations (13), (14), and (15), the inner product is defined as

$$\langle f, g\rangle = \int_S f(\vec{r})g(\vec{r})dA \ ,$$

where the integration is over the structure surface. Various choices are possible for the weighting functions $\{w_i\}$ and basis functions $\{f_j\}$. When $w_i = f_i$, the procedure is known as Galerkin's method. In NEC the basis and weight functions are different, w_i being chosen as a set of delta functions

$$w_i(\vec{r}) = \delta(\vec{r} - \vec{r}_i) \ ,$$

with $\{\vec{r}_i\}$ a set of points on the conducting surface. The result is a point sampling of the integral equations known as the collocation method of solution. Wires are divided into short straight segments with a sample point at the center of each segment while surfaces are approximated by a set of flat patches or facets with a sample point at the center of each patch.

The choice of basis functions is very important for an efficient and accurate solution. In NEC the support of f_i is restricted to a localized subsection of the surface near $\vec{r}_i$. This choice simplifies the evaluation of the inner-product integral and ensures that the matrix G will be well conditioned. For finite N, the sum of f_j cannot exactly equal a general current distribution so the functions f_i should be chosen as close as possible to the actual current distribution. Because of the nature of the integral-equation kernels, the choice of basis function is much more critical on wires than on surfaces. The functions used in NEC are explained in the following sections.

1. CURRENT EXPANSION ON WIRES

Wires in NEC are modeled by short straight segments with the current on each segment represented by three terms – a constant, a sine, and a cosine. This expansion was first used by Yeh and Mei (ref. 14) and has been shown to provide rapid solution convergence (ref. 15 and 16). It has the added advantage that the fields of the sinusoidal currents are easily evaluated in closed form. The amplitudes of the constant, sine, and cosine terms are related such

that their sum satisfies physical conditions on the local behavior of current and charge at the segment ends. This differs from AMP where the current was extrapolated to the centers of the adjacent segments, resulting in discontinuities in current and charge at the segment ends. Matching at the segment ends improves the solution accuracy, especially at the multiple-wire junctions of unequal length segments where AMP extrapolated to an average length segment, often with inaccurate results.

The total current on segment number j in NEC has the form

$$I_j(s) = A_j + B_j \sin k(s-s_j) + C_j \cos k(s-s_j) \ , \qquad (20)$$

$$|s-s_j| < \Delta_j/2 \ ,$$

where s_j is the value of s at the center of segment j and Δ_j is the length of segment j. Of the three unknown constants A_j, B_j, and C_j, two are eliminated by local conditions on the current leaving one constant, related to the current amplitude, to be determined by the matrix equation. The local conditions are applied to the current and to the linear charge density, q, which is related to the current by the equation of continuity

$$\frac{\partial I}{\partial s} = - j\omega q \ . \qquad (21)$$

At a junction of two segments with uniform radius, the obvious conditions are that the current and charge are continuous at the junction. At a junction of two or more segments with unequal radii, the continuity of current is generalized to Kirchoff's current law that the sum of currents into the junction is zero. The total charge in the vicinity of the junction is assumed to distribute itself on individual wires according to the wire radii, neglecting local coupling effects. T. T. Wu and R. W. P. King (ref. 17) have derived a condition that the linear charge density on a wire at a junction, and hence $\partial I/\partial s$, is determined by

$$\left.\frac{\partial I(s)}{\partial s}\right|_{s \text{ at junction}} = \frac{Q}{\ell n\left(\frac{2}{ka}\right) - \gamma} \ , \qquad (22)$$

where a = wire radius,

$$k = 2\pi/\lambda \ ,$$

$\gamma = 0.5772$ (Euler's constant).

Q is related to the total charge in the vicinity of the junction and is constant for all wires at the junction.

At a free wire end, the current may be assumed to go to zero. On a wire of finite radius, however, the current can flow onto the end cap and hence be nonzero at the wire end. In one study of this effect, a condition relating the current at the wire end to the current derivative was derived (ref. 18). For a wire of radius a, this condition is

$$I(s)\Big|_{s \text{ at end}} = \frac{-(\hat{s}\cdot\hat{n}_c)}{k}\,\frac{J_1(ka)}{J_0(ka)}\,\frac{\partial I(s)}{\partial s}\Big|_{s \text{ at end}},$$

where J_0 and J_1 are Bessel functions of order 0 and 1. The unit vector $\hat{n}_c$ is normal to the end cap. Hence, $\hat{s} \cdot \hat{n}_c$ is +1 if the reference direction, $\hat{s}$, is toward the end, and -1 if $\hat{s}$ is away from the end.

Thus, for each segment two equations are obtained from the two ends:

$$I_j(s_j \pm \Delta_j/2) = \frac{\pm 1}{k}\,\frac{J_1(ka_j)}{J_0(ka_j)}\,\frac{\partial I_j(s)}{\partial s}\Big|_{s = s_j \pm \Delta_j/2} \tag{23}$$

at free ends, and

$$\frac{\partial I_j(s)}{\partial s}\Big|_{s = s_j \pm \Delta_j/2} = \frac{Q_j^{\pm}}{\ell n\left(\frac{2}{ka_j}\right) - \gamma} \tag{24}$$

at junctions. Two additional unknowns Q_j^- and Q_j^+ are associated with the junctions but can be eliminated by Kirchoff's current equation at each junction. The boundary-condition equations provide the additional equation-per-segment to completely determine the current function of equation (20) for every segment.

To apply these conditions, the current is expanded in a sum of basis functions chosen so that they satisfy the local conditions on current and charge in any linear combination. A typical set of basis functions and their sum on a four segment wire are shown in figure 1. For a general segment i in figure 2, the i^{th} basis function has a peak on segment i and extends onto

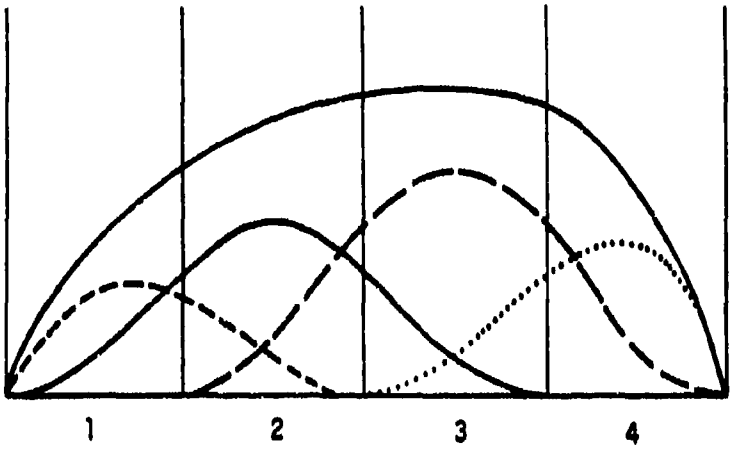


Figure 1. Current Basis Functions and Sum on a Four Segment Wire.

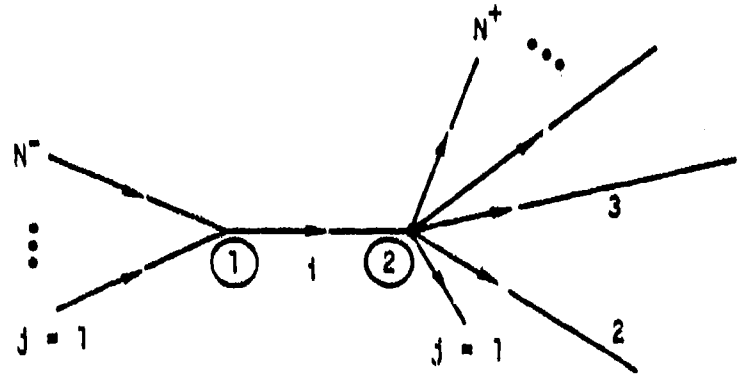


Figure 2. Segments Covered by the i^{th} Basis Function.

every segment connected to i, going to zero with zero derivative at the outer ends of the connected segments.

The general definition of the i^{th} basis function is given below. For the junction and end conditions described above, the following definitions apply for the factors in the segment and conditions:

$$a_i^- = a_i^+ = \left[\ln\left(\frac{2}{ka_i}\right) - \gamma \right]^{-1} , \tag{25}$$

and

$$X_i = J_1(ka_i)/J_o(ka_i) .$$

The condition of zero current at a free end may be obtained by setting X_i to zero.

The portion of the i^{th} basis function on segment i is then

$$f_i^o(s) = A_i^o + B_i^o \sin k(s - s_i) + C_i^o \cos k(s - s_i) \qquad (26)$$

$$|s - s_i| < \Delta_i/2 \ .$$

If $N^- \neq 0$ and $N^+ \neq 0$, end conditions are

$$\frac{\partial}{\partial s} f_i^o(s) \Big|_{s = s_i - \Delta_i/2} = a_i^- Q_i^- \ , \qquad (27)$$

$$\frac{\partial}{\partial s} f_i^o(s) \Big|_{s = s_i + \Delta_i/2} = a_i^+ Q_i^+ \ . \qquad (28)$$

If $N^- = 0$ and $N^+ \neq 0$, end conditions are

$$f_i^o(s_i - \Delta_i/2) = \frac{1}{k} X_i \frac{\partial}{\partial s} f_i^o(s) \Big|_{s = s_i - \Delta_i/2} \qquad (29)$$

$$\frac{\partial}{\partial s} f_i^o(s) \Big|_{s = s_i + \Delta_i/2} = a_i^+ Q_i^+ \ . \qquad (30)$$

If $N^- \neq 0$ and $N^+ = 0$, end conditions are

$$\frac{\partial}{\partial s} f_i^o(s) \Big|_{s = s_i - \Delta_i/2} = a_i^- Q_i^- \ , \qquad (31)$$

$$f_i^o(s_i + \Delta_i/2) = \frac{-1}{k} X_i \frac{\partial}{\partial s} f_i^o(s) \Big|_{s = s_i + \Delta_i/2} \ . \qquad (32)$$

Over segments connected to end 1 of segment i, the i^{th} basis function is

$$f_j^-(s) = A_j^- + B_j^- \sin k(s - s_j) + C_j^- \cos k(s - s_j) \qquad (33)$$

$$|s - s_j| < \Delta_j/2 \quad j = 1, \ldots, N^- \ .$$

End conditions are

$$f_j^-(s_j - \Delta_j/2) = 0 \ , \tag{34}$$

$$\frac{\partial}{\partial s} f_j^-(s) \Big|_{s = s_j - \Delta_j/2} = 0 \ , \tag{35}$$

$$\frac{\partial}{\partial s} f_j^-(s) \Big|_{s = s_j + \Delta_i/2} = a_j^+ Q_i^- \ . \tag{36}$$

Over segments connected to end 2 of segment i, the i^{th} basis function is

$$f_j^+(s) = A_j^+ + B_j^+ \sin k(s - s_j) + C_j^+ \cos k(s - s_j) \tag{37}$$

$$|s - s_j| < \Delta_j/2 \quad j = 1, \ \ldots \ , N^+ \ .$$

End conditions are

$$\frac{\partial}{\partial s} f_j^+(s) \Big|_{s = s_j - \Delta_j/2} = a_j^- Q_i^+ \ , \tag{38}$$

$$f_j^+(s_j + \Delta_j/2) = 0 \ , \tag{39}$$

$$\frac{\partial}{\partial s} f_j^+(s) \Big|_{s = s_j + \Delta_j/2} = 0 \ . \tag{40}$$

Equations (26), (33), and (37), defining the complete basis function, involve $3(N^- + N^+ + 1)$ unknown constants. Of these, $3(N^- + N^+) + 2$ unknowns are eliminated by the end conditions in terms of Q_i^- and Q_i^+ which can then be determined from the two Kirchoff's current equations:

$$\sum_{j=1}^{N^-} f_j^-(s_j + \Delta_j/2) = f_i^o(s_i - \Delta_i/2) \ , \text{ and} \tag{41}$$

$$\sum_{j=1}^{N^+} f_j^+(s_j - \Delta_j/2) = f_i^o(s_i + \Delta_i/2) \ . \tag{42}$$

The complete basis function is then defined in terms of one unknown constant. In this case A_i^o was set to -1 since the function amplitude is arbitrary, being determined by the boundary condition equations. The final result is given below:

$$A_j^- = \frac{a_j^+ Q_i^-}{\sin k \Delta_j} , \tag{43}$$

$$B_j^- = \frac{a_j^+ Q_i^-}{2 \cos k \Delta_j/2} , \tag{44}$$

$$C_j^- = \frac{- a_j^+ Q_i^-}{2 \sin k \Delta_j/2} , \tag{45}$$

$$A_j^+ = \frac{- a_j^- Q_i^+}{\sin k \Delta_j} , \tag{46}$$

$$B_j^+ = \frac{a_j^- Q_i^+}{2 \cos k \Delta_j/2} , \tag{47}$$

$$C_j^+ = \frac{a_j^- Q_i^+}{2 \sin k \Delta_j/2} . \tag{48}$$

For $N^- \neq 0$ and $N^+ \neq 0$,

$$A_i^o = - 1 , \tag{49}$$

$$B_i^o = \left(a_i^- Q_i^- + a_i^+ Q_i^+ \right) \frac{\sin k \Delta_i/2}{\sin k \Delta_i} , \tag{50}$$

$$C_i^o = \left(a_i^- Q_i^- - a_i^+ Q_i^+ \right) \frac{\cos k \Delta_i/2}{\sin k \Delta_i} , \tag{51}$$

$$Q_i^- = \frac{a_i^+(1 - \cos k\,\Delta_i) - P_i^+ \sin k\,\Delta_i}{\left(P_i^- P_i^+ + a_i^- a_i^+\right)\sin k\,\Delta_i + \left(P_i^- a_i^+ - P_i^+ a_i^-\right)\cos k\,\Delta_i}\,, \tag{52}$$

$$Q_i^+ = \frac{a_i^-(\cos k\,\Delta_i - 1) - P_i^- \sin k\,\Delta_i}{\left(P_i^- P_i^+ + a_i^- a_i^+\right)\sin k\,\Delta_i + \left(P_i^- a_i^+ - P_i^+ a_i^-\right)\cos k\,\Delta_i}\,. \tag{53}$$

For $N^- = 0$ and $N^+ \neq 0$,

$$A_i^o = -1\,, \tag{54}$$

$$B_i^o = \frac{\sin k\,\Delta_i/2}{\cos k\,\Delta_i - X_i \sin k\,\Delta_i} + a_i^+ Q_i^+ \frac{\cos k\,\Delta_i/2 - X_i \sin k\,\Delta_i/2}{\cos k\,\Delta_i - X_i \sin k\,\Delta_i}\,, \tag{55}$$

$$C_i^o = \frac{\cos k\,\Delta_i/2}{\cos k\,\Delta_i - X_i \sin k\,\Delta_i} + a_i^+ Q_i^+ \frac{\sin k\,\Delta_i/2 + X_i \cos k\,\Delta_i/2}{\cos k\,\Delta_i - X_i \sin k\,\Delta_i}\,, \tag{56}$$

$$Q_i^+ = \frac{\cos k\,\Delta_i - 1 - X_i \sin k\,\Delta_i}{\left(a_i^+ + X_i P_i^+\right)\sin k\,\Delta_i + \left(a_i^+ X_i - P_i^+\right)\cos k\,\Delta_i} \tag{57}$$

For $N^- \neq 0$ and $N^+ = 0$,

$$A_i^o = -1\,, \tag{58}$$

$$B_i^o = \frac{-\sin k\,\Delta_i/2}{\cos k\,\Delta_i - X_i \sin k\,\Delta_i} + a_i^- Q_i^- \frac{\cos k\,\Delta_i/2 - X_i \sin k\,\Delta_i/2}{\cos k\,\Delta_i - X_i \sin k\,\Delta_i}\,, \tag{59}$$

$$C_i^o = \frac{\cos k\,\Delta_i/2}{\cos k\,\Delta_i - X_i \sin k\,\Delta_i} - a_i^- Q_i^- \frac{\sin k\,\Delta_i/2 + X_i \cos k\,\Delta_i/2}{\cos k\,\Delta_i - X_i \sin k\,\Delta_i}\,, \tag{60}$$

$$Q_i^- = \frac{1 - \cos k\,\Delta_i + X_i \sin k\,\Delta_i}{\left(a_i^- - X_i P_i^-\right)\sin k\,\Delta_i + \left(P_i^- + X_i a_i^-\right)\cos k\,\Delta_i}\,. \tag{61}$$

For all cases,

$$P_i^- = \sum_{j=1}^{N^-} \left(\frac{1 - \cos k \Delta_j}{\sin k \Delta_j} \right) a_j^+ , \tag{62}$$

$$P_i^+ = \sum_{j=1}^{N^+} \left(\frac{\cos k \Delta_j - 1}{\sin k \Delta_j} \right) a_j^- , \tag{63}$$

where the sum for P_i^- is over segments connected to end 1 of segment i, and the sum for P_i^+ is over segments connected to end 2. If $N^- = N^+ = 0$, the complete basis function is

$$f_i^o = \frac{\cos k(s - s_i)}{\cos k \Delta_i/2 - X_i \sin \Delta_i/2} - 1 . \tag{64}$$

When a segment end is connected to a ground plane or to a surface modeled with the MFIE, the end condition on both the total current and the last basis function is

$$\frac{\partial}{\partial s} I_j(s) \Big|_{s = s_j \pm \Delta_j/2} = 0 ,$$

replacing the zero current condition at a free end. This condition does not require a separate treatment, however, but is obtained by computing the last basis function as if the last segment is connected to its image segment on the other side of the surface.

It should be noted that in AMP, the basis function f_i has unit value at the center of segment i and zero value at the centers of connected segments although it does extend onto the connected segments. As a result, the amplitude of f_i is the total current at the center of segment i. This is not true in NEC so the current at the center of segment i must be computed by summing the contributions of all basis functions extending onto segment i.

2. CURRENT EXPANSION ON SURFACES

Surfaces on which the MFIE is used are modeled by small flat patches. The surface current on each patch is expanded in a set of pulse functions except in the region of wire connection, as will be described later. The pulse function expansion for N_p patches is

$$\vec{J}_s(\vec{r}) = \sum_{j=1}^{N_P} (J_{1j}\,\vec{\ell}_{1j} + J_{2j}\,\vec{\ell}_{2j})\,V_j(\vec{r}) \ , \tag{65}$$

where

$$\vec{\ell}_{1j} = \vec{\ell}_1(\vec{r}_j) \ ,$$

$$\vec{\ell}_{2j} = \vec{\ell}_2(\vec{r}_j) \ ,$$

$\vec{r}_j$ = position of the center of patch number j ,

$V_j(\vec{r})$ = 1 for $\vec{r}$ on patch j and 0 otherwise.

The constants J_{1j} and J_{2j}, representing average surface-current density over the patch, are determined by the solution of the linear system of equations derived from the integral equations. The integrals for fields, due to the pulse basis functions, are evaluated numerically in a single step so that for integration, the pulses could be reduced to delta functions at the patch centers. That this simple approximation of the current yields good accuracy is one of the advantages of the MFIE for surfaces.

A more realistic representation of the surface current is needed, however, in the region where a wire connects to the surface. The treatment used in NEC, affecting the four coplanar patches about the connection point, is quite similar to that used by Albertsen et al. (ref. 9). In the region of the wire connection, the surface current contains a singular component due to the current flowing from the wire onto the surface. The total surface current should satisfy the condition,

$$\nabla_s \cdot \vec{J}_s(x,y) = J_o(x,y) + I_o\delta(x,y) \ ,$$

where the local coordinates x and y are defined in figure 3, ∇_s denotes surface divergence, $J_o(x,y)$ is a continuous function in the region ABCD, and I_o is the current at the base of the wire flowing onto the surface. One expansion which meets this requirement is

$$\vec{J}_s(x,y) = I_o\vec{f}(x,y) + \sum_{j=1}^{4} g_j(x,y)(\vec{J}_j - I_o\,\vec{f}_j) \ , \tag{66}$$

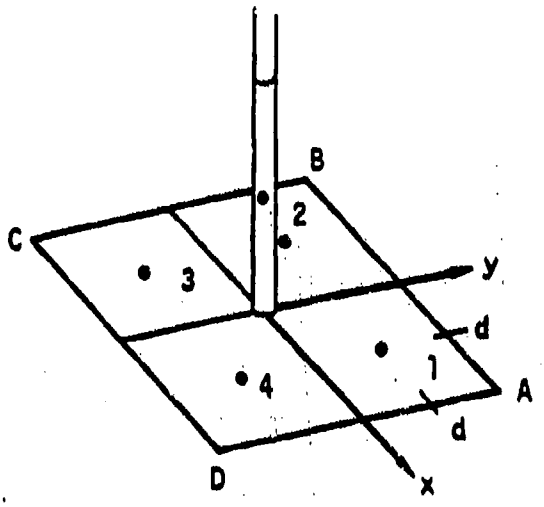


Figure 3. Detail of the Connection of a Wire to a Surface.

where

$$\vec{f}(x,y) = \frac{x\hat{x} + y\hat{y}}{2\pi(x^2 + y^2)} ,$$

$$\vec{J}_j = \vec{J}_s(x_j,y_j) ,$$

$$\vec{f}_j = \vec{f}(x_j,y_j) , \text{ and}$$

$(x_j,y_j) = (x,y)$ at the center of patch j. The interpolation functions $g_j(x,y)$ are chosen such that: $g_j(x,y)$ is differentiable on ABCD; $g_j(x_i,y_i) = \delta_{ij}$; and $\sum_{j=1}^{4} g_j(x,y) = 1$. The specific functions used in NEC are as follows:

$$g_1(x,y) = \frac{1}{4d^2}(d+x)(d+y) \qquad g_2(x,y) = \frac{1}{4d^2}(d-x)(d+y)$$

$$g_3(x,y) = \frac{1}{4d^2}(d-x)(d-y) \qquad g_4(x,y) = \frac{1}{4d^2}(d+x)(d-y)$$

Equation (66) is used when computing the electric field at the center of the connected wire segment due to the surface current on the four surrounding patches. In computing the field on any other segments or on any patches, the pulse-function form is used for all patches including those at the connection point. This saves integration time and is sufficiently accurate for the greater source to observation-point separations involved.

3. EVALUATION OF THE FIELDS

The current on each wire segment has the form

$$I_i(s) = A_i + B_i \sin k(s - s_i) + C_i \cos k(s - s_i) \qquad (67)$$

$$|s - s_i| < \Delta_i/2 ,$$

where $k = \omega\sqrt{\mu_o\epsilon_o}$, and Δ_i is the segment length. The solution requires the evaluation of the electric field at each segment due to this current. Three

approximations of the integral equation kernel are used: a thin-wire form for most cases, an extended thin-wire form for thick wires, and a current element approximation for large interaction distances. In each case the evaluation of the field is greatly simplified by the use of formulas for the fields of the constant and sinusoidal current components.

The accuracy of the thin-wire approximation for a wire of radius a and length Δ depends on ka and Δ/a. Studies have shown that the thin-wire approximation leads to errors of less than 1% for Δ/a greater than 8 (ref. 11). Furthermore, in the numerical solution of the EFIE, the wire is divided into segments less than about 0.1λ in length to obtain an adequate representation of current distribution thus restricting ka to less than about 0.08. The extended thin-wire approximation is applicable to shorter and thicker segments, resulting in errors less than 1% for Δ/a greater than 2.

For the thin-wire kernel, the source current is approximated by a filament on the segment axis while the observation point is on the surface of the observation segment. The fields are evaluated with the source segment on the axis of a local cylindrical-coordinate system as illustrated in figure 4.

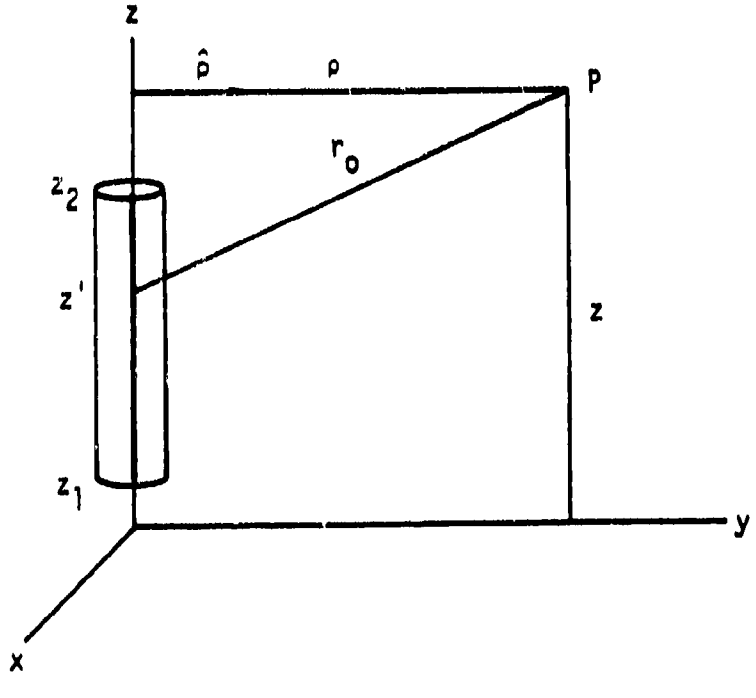


Figure 4. Current-Filament Geometry for the Thin-Wire Kernel.

Then with

$$G_o = \exp(-jkr_o)/r_o \ , \tag{68}$$

$$r_o = \left[\rho^2 + (z - z')^2\right]^{1/2} \ , \tag{69}$$

the ρ and z components of the electric field at P due to a sinusoidal current filament of arbitrary phase,

$$I = \sin(kz' - \Theta_o) \ , \ z_1 < z' < z_2 \ , \tag{70}$$

are

$$E_\rho^f(\rho,z) = \frac{-j\eta}{2k^2\lambda\rho}\left[(z'-z)\ I\ \frac{\partial G_o}{\partial z'} + I\ G_o - (z'-z)\ G_o\ \frac{\partial I}{\partial z'}\right]_{z_1}^{z_2} \ , \tag{71}$$

$$E_z^f(\rho,z) = \frac{j\eta}{2k^2\lambda}\left[G_o\ \frac{\partial I}{\partial z'} - I\ \frac{\partial G_o}{\partial z'}\right]_{z_1}^{z_2} \ . \tag{72}$$

For a current that is constant over the length of the segment with strength I, the fields are

$$E_\rho^f(\rho,z) = \frac{I}{\lambda}\ \frac{j\eta}{2k^2}\ \left[\frac{\partial G_o}{\partial \rho}\right]_{z_1}^{z_2} \ , \tag{73}$$

$$E_z^f(\rho,z) = -\frac{I}{\lambda}\ \frac{j\eta}{2k^2}\ \left\{\left[\frac{\partial G_o}{\partial z'}\right]_{z_1}^{z_2} + k^2 \int_{z_1}^{z_2} G_o\ dz'\right\} \ . \tag{74}$$

These field expressions are exact for the specified currents. The integral over z' of G_o is evaluated numerically in NEC.

Substituting sine and cosine currents and evaluating the derivatives yields the following equations for the fields. For

$$I = I_o \begin{pmatrix} \sin kz' \\ \cos kz' \end{pmatrix} , \tag{75}$$

$$E_\rho^f(\rho,z) = \frac{-I_o}{\lambda} \frac{j\eta}{2k^2\rho} G_o \left\{ k(z-z') \begin{pmatrix} \cos kz' \\ -\sin kz' \end{pmatrix} \right. \tag{76}$$

$$\left. + \left[1 - (z-z')^2(1+jkr_o) \frac{1}{r_o^2} \right] \begin{pmatrix} \sin kz' \\ \cos kz' \end{pmatrix} \right\} \Bigg|_{z_1}^{z_2} ,$$

$$E_z^f(\rho,z) = \frac{I_o}{\lambda} \frac{j\eta}{2k^2} G_o \left\{ k \begin{pmatrix} \cos kz' \\ -\sin kz' \end{pmatrix} \right. \tag{77}$$

$$\left. - (1+jkr_o)(z-z') \frac{1}{r_o^2} \begin{pmatrix} \sin kz' \\ \cos kz' \end{pmatrix} \right\} \Bigg|_{z_1}^{z_2} .$$

For a constant current of strength I_o,

$$E_\rho^f(\rho,z) = - \frac{I_o}{\lambda} \frac{j\eta\rho}{2k^2} \left[(1+jkr_o) \frac{G_o}{r_o^2} \right]_{z_1}^{z_2} , \tag{78}$$

$$E_z^f(\rho,z) = - \frac{I_o}{\lambda} \frac{j\eta}{2k^2} \left\{ \left[(1+jkr_o)(z-z') \frac{G_o}{r_o^2} \right]_{z_1}^{z_2} \right. \tag{79}$$

$$\left. + k^2 \int_{z_1}^{z_2} G_o \, dz' \right\} .$$

Despite the seemingly crude approximation, the thin-wire kernel does accurately represent the effect of wire radius for wires that are sufficiently thin. The accuracy range was studied by Poggio and Adams (ref. 11) where an

extended thin-wire kernel was developed for wires that are too thick for the thin-wire approximation.

The derivation of the extended thin-wire kernel starts with the current on the surface of the source segment with surface density,

$$J(z') = I(z')/(2\pi a) ,$$

where a is the radius of the source segment. The geometry for evaluation of the fields is shown in figure 5. A current filament of strength $Id\phi/(2\pi)$ is integrated over ϕ with

$$\rho' = [\rho^2 + a^2 - 2a\rho \cos \phi]^{1/2} , \tag{80}$$

$$r = [\rho'^2 + (z-z')^2]^{1/2} . \tag{81}$$

Thus, the z component of the field of the current tube is

$$E_z^t(\rho,z) = \frac{1}{2\pi} \int_0^{2\pi} E_z^f(\rho',z)d\phi . \tag{82}$$

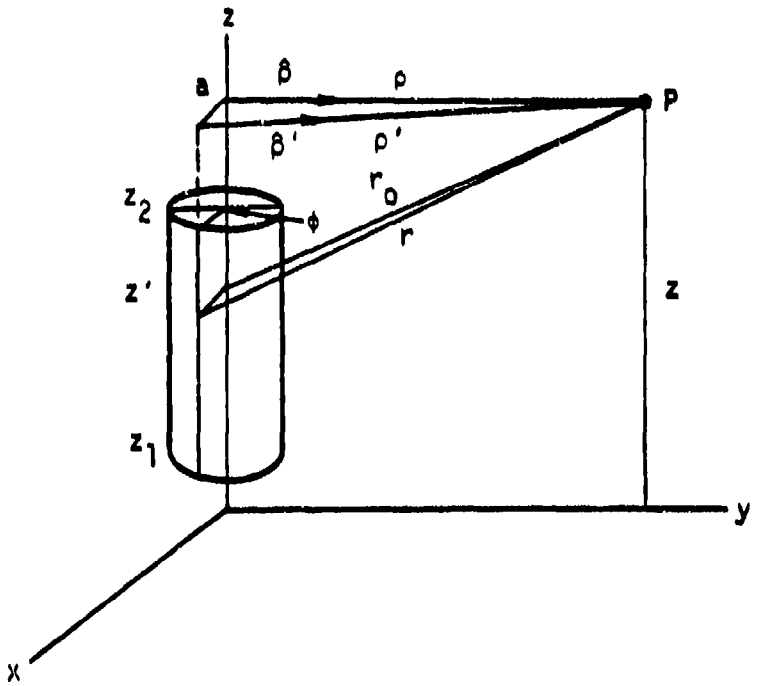


Figure 5. Current Geometry for the Extended Thin-Wire Kernel.

For the ρ component of field, the change in the direction of $\hat{\beta}'$ must be considered. The field in the direction $\hat{\beta}$ is

$$E_\rho^t(\rho,z) = \frac{1}{2\pi}\int_0^{2\pi} E_\rho^f(\rho',z)(\hat{\beta}\cdot\hat{\beta}')d\phi \ , \tag{83}$$

where

$$\hat{\beta}\cdot\hat{\beta}' = \frac{\rho - a\cos\phi}{\rho'} = \frac{\partial\rho'}{\partial\rho}$$

The integrals over ϕ in equations (82) and (83) cannot be evaluated in closed form. Poggio and Adams, however, have evaluated them as a series in powers of a^2 (ref. 11). The first term in the series gives the thin-wire kernel. For the extended thin-wire kernel, the second term involving a^2 is retained with terms of order a^4 neglected. As with the thin-wire kernel, the field observation point is on the segment surface. Hence, when evaluating the field on the source segment, $\rho = a$.

The field equations with the extended thin-wire approximation are given below. For a sinusoidal current of equation (70),

$$E_\rho(\rho,z) = \frac{-j\eta}{2k^2\lambda}\left[(z'-z)I\frac{\partial G_2}{\partial z'} + IG_2 - (z'-z)G_2\frac{\partial I}{\partial z'}\right]_{z_1}^{z_2} , \tag{84}$$

$$E_z(\rho,z) = \frac{j\eta}{2k^2\lambda}\left[G_1\frac{\partial I}{\partial z'} - I\frac{\partial G_1}{\partial z'}\right]_{z_1}^{z_2} , \tag{85}$$

For a constant current of strength I_o,

$$E_\rho(\rho,z) = \frac{I}{\lambda}\frac{j\eta}{2k^2}\left[\frac{\partial G_1}{\partial \rho}\right]_{z_1}^{z_2}, \tag{86}$$

$$E_z(\rho,z) = -\frac{I}{\lambda}\frac{j\eta}{2k^2}\left\{\left[\frac{\partial G_1}{\partial z'}\right]_{z_1}^{z_2} + k^2\left[1-\frac{(ka)^2}{4}\right]\int_{z_1}^{z_2} G_o\,dz' - \frac{(ka)^2}{4}\left[\frac{\partial G_o}{\partial z'}\right]_{z_1}^{z_2}\right\}. \tag{87}$$

The term G_1 is the series approximation of

$$G_1^t = \frac{1}{2\pi}\int_o^{2\pi} G\,d\phi, \tag{88}$$

where

$$G = \exp(-jkr)/r.$$

Neglecting terms of order a^4,

$$G_1 = G_o\left\{1 - \frac{a^2}{2r_o^2}(1+jkr_o) + \frac{a^2\rho^2}{4r_o^4}\left[3(1+jkr_o) - k^2r_o^2\right]\right\}, \tag{89}$$

$$\frac{\partial G_1}{\partial z'} = \frac{(z-z')}{r_o^2}G_o\left\{(1+jkr_o) - \frac{a^2}{2r_o^2}\left[3(1+jkr_o) - k^2r_o^2\right] - \frac{a^2\rho^2}{4r_o^4}\left[jk^3r_o^3 + 6k^2r_o^2 - 15(1+jkr_o)\right]\right\}, \tag{90}$$

$$\frac{\partial G_1}{\partial \rho} = -\frac{\rho G_o}{r_o^2}\left\{(1+jkr_o) - \frac{a^2}{r_o^2}\left[3(1+jkr_o) - k^2 r_o^2\right]\right.$$

$$\left. - \frac{a^2\rho^2}{4r_o^4}\left[jk^3 r_o^3 + 6k^2 r_o^2 - 15(1+jkr_o)\right]\right\} . \tag{91}$$

The term G_2 is the series approximation of

$$G_2^t = \frac{1}{2\pi}\int_o^{2\pi} \frac{\rho - a\cos\phi}{\rho'^2} G\, d\phi . \tag{92}$$

To order a^2,

$$G_2 = \frac{G_o}{\rho}\left\{1 + \frac{a^2\rho^2}{4r_o^4}\left[3(1+jkr_o) - k^2 r_o^2\right]\right\} , \tag{93}$$

$$\frac{\partial G_2}{\partial z'} = \frac{(z-z')}{\rho r_o^2} G_o \left\{(1+jkr_o) - \frac{a^2\rho^2}{4r_o^4}\left[jk^3 r_o^3 + 6k^2 r_o^2 - 15(1+jkr_o)\right]\right\} . \tag{94}$$

Equation (86) makes use of the relation

$$(\hat{\rho}\cdot\hat{\rho}')\frac{\partial G}{\partial \rho'} = \frac{\partial G}{\partial \rho'}\frac{\partial \rho'}{\partial \rho} = \frac{\partial G}{\partial \rho} , \tag{95}$$

while equation (87) follows from

$$G_1 = \left[1 - \frac{(ka)^2}{4} - \frac{a^2}{4}\frac{\partial^2}{\partial z'^2}\right] G_o . \tag{96}$$

When the observation point is within the wire ($\rho<a$), a series expansion in ρ rather than a is used for G_o and G_2. For G_1 this simply involves interchanging ρ and a in equations (89) and (90). Then for $\rho < a$, with

$$r_a = \left[a^2 + (z-z')^2\right]^{1/2} , \tag{97}$$

$$G_a = \exp(-jkr_a)/r_a \ , \tag{98}$$

the expressions for G_1, G_2 and their derivatives are

$$G_1 = G_a \left\{ 1 - \frac{\rho^2}{2r_a^2}(1+jkr_a) + \frac{a^2\rho^2}{4r_a^4}\left[3(1+jkr_a) - k^2r_a^2\right]\right\} \ , \tag{99}$$

$$\begin{aligned}\frac{\partial G_1}{\partial z'} = \frac{(z-z')}{r_a^2} G_a \Bigg\{ & (1+jkr_a) - \frac{\rho^2}{2r_a^2}\left[3(1+jkr_a) - k^2r_a^2\right] \\ & - \frac{a^2\rho^2}{4r_a^4}\left[jk^3r_a^3 + 6k^2r_a^2 - 15(1+jkr_a)\right]\Bigg\} \ ,\end{aligned} \tag{100}$$

$$\frac{\partial G_1}{\partial \rho} = -\frac{\rho}{r_a^2} G_a \left\{ (1+jkr_a) - \frac{a^2}{2r_a^2}\left[3(1+jkr_a) - k^2r_a^2\right]\right\} \ , \tag{101}$$

$$G_2 = -\frac{\rho}{2r_a^2} G_a (1+jkr_a) \ , \tag{102}$$

$$\frac{\partial G_2}{\partial z'} = -\frac{(z-z')\rho}{2r_a^4} G_a \left[3(1+jkr_a) - k^2r_a^2\right] \ . \tag{103}$$

Special treatment of bends in wires is required when the extended thin-wire kernel is used. The problem stems from the cancellation of terms evaluated at z_1 and z_2 in the field equations when segments are part of a continuous wire. The current expansion in NEC results in a current having a continuous value and derivative along a wire without junctions. This ensures that for two adjacent segments on a straight wire, the contributions to the z component of electric field at z_2 of the first segment exactly cancel the contributions from z_1, representing the same point, for the second segment. For a straight wire of several segments, the only contributions to E_z with either the thin-wire or extended thin-wire kernel come from the two wire ends and the integral of G_o along the wire. For the ρ component of field or either component at a bend, while there is not complete cancellation, there may be partial cancellation of large end contributions.

The cancellation of end terms makes necessary a consistent treatment of the current on both sides of a bend for accurate evaluation of the field. This is easily accomplished with the thin-wire kernel since the current filament on the wire axis is physically continuous around a bend. However, the current tube assumed for the extended thin-wire kernel cannot be continuous around its complete circumference at a bend. This was found to reduce the solution accuracy when the extended thin-wire kernel was used for bent wires.

To avoid this problem in NEC, the thin-wire form of the end terms in equations (71) through (74) is always used at a bend or change in radius. The extended thin-wire kernel is used only at segment ends where two parallel segments join, or at free ends. The switch from extended thin-wire form to the thin-wire form is made from one end of a segment to the other rather than between segments where the cancellation of terms is critical.

When segments are separated by a large distance, the interaction may be computed with sufficient accuracy by treating the segment current as an infinitesimal current element at the segment center. In spherical coordinates, with the segment at the origin along the $\Theta = 0$ axis, the electric field is

$$E_r(r,\Theta) = \frac{M\eta}{2\pi r^2} \exp(-jkr)\left(1 - \frac{j}{kr}\right) \cos\Theta \ ,$$

$$E_\Theta(r,\Theta) = \frac{M\eta}{4\pi r^2} \exp(-jkr)\left(1+jkr - \frac{1}{kr}\right) \sin\Theta \ .$$

The dipole moment M for a constant current I on a segment of length Δ_i is

$$M = I\ \Delta_i \ .$$

For a current $I \cos[k(s - s_i)]$ with $|s - s_i| < \Delta_i/2$,

$$M = \frac{2I}{k} \sin(k\Delta_i/2) \ ,$$

while for a current $I \sin[k(s - s_i)]$,

$$M = 0 \ .$$

Use of this approximation saves a significant amount of time in evaluating the interaction matrix elements for large structures. The minimum interaction distance at which it is used is selected by the user in NEC. A default distance of one wavelength is set, however.

For each of the three methods of computing the field at a segment due to the current on another segment, the field is evaluated on the surface of the observation segment. Rather than choosing a fixed point on the segment surface, the field is evaluated at the cylindrical coordinates ρ', z with the source segment at the origin. If the center point on the axis of the observation segment is at ρ, z, then

$$\rho' = \left[\rho^2 + a_o^2\right]^{1/2} ,$$

where a_o is the radius of the observation segment. Also, the component of E_ρ tangent to the observation segment is computed as

$$\vec{E}_\rho \cdot \hat{s} = (\hat{\rho}\cdot\hat{s}) \frac{\rho}{\rho'} E_\rho .$$

Inclusion of the factor ρ/ρ', which is the cosine of the angle between $\hat{\rho}$ and $\hat{\rho}'$, is necessary for accurate results at bends in thick wires.

4. THE MATRIX EQUATION FOR CURRENT

For a structure having N_s wire segments and N_p patches, the order of the matrix in equation (19) is $N = N_s + 2N_p$. In NEC the wire segment equations occur first in the linear system so that, in terms of submatrices, the equation has the form

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} I_w \\ I_p \end{bmatrix} = \begin{bmatrix} E_w \\ H_p \end{bmatrix} ,$$

with equations derived from equation (14) in odd numbered rows in the lower set and equation (15) in even rows. I_w is then the column vector of segment

basis function amplitudes, and I_p is the patch-current amplitudes (J_{1j}, J_{2j}, $j=1,\ldots,N_p$). The elements of E_w are the left-hand side of equation (13) evaluated at segment centers, while H_p contains, alternately, the left-hand sides of equations (14) and (15) evaluated at patch centers.

A matrix element A_{ij} in submatrix A represents the electric field at the center of segment i due to the j^{th} segment basis function, centered on segment j. A matrix element D_{ij} in submatrix D represents a tangential magnetic field component at patch k due to a surface-current pulse on patch ℓ where

$$k = \text{Int}\left[(i-1)/2\right] + 1 ,$$

$$\ell = \text{Int}\left[(j-1)/2\right] + 1 ,$$

and Int[] indicates truncation. The source pulse is in the direction $\hat{t}_1$ when j is odd, and direction $\hat{t}_2$ when j is even. When $k = \ell$ the contribution of the surface integral is zero since the vector product is zero on the flat patch surface, although a ground image may produce a contribution. However, for $k = \ell$, there is a contribution of $\pm$ 1/2 from the coefficient of $\vec{J}_s(\vec{r})$ in equation (14) or (15). Matrix elements in submatrices B and C represent electric fields due to surface-current pulses and magnetic fields due to segment basis functions, respectively. These present no special problems since the source and observation points are always separated.

5. SOLUTION OF THE MATRIX EQUATION

The matrix equation,

$$[G]\,[I] = [E] , \tag{104}$$

is solved in NEC by Gauss elimination (ref. 19). The basic step is factorization of the matrix G into the product of an upper triangular matrix U and a lower triangle matrix L where

$$G = [L]\,[U] .$$

The matrix equation is then

$$[L]\,[U]\,[I] = [E] , \tag{105}$$

from which the solution, I, is computed in two steps as

$$[L]\,[F] = [E]\ , \tag{106}$$

and

$$[U]\,[I] = [F]\ . \tag{107}$$

Equation (106) is first solved for F by forward substitution, and equation (107) is then solved for I by backward substitution.

The major computational effort is factoring G into L and U. This takes approximately $1/3\ N^3$ multiplication steps for a matrix of order N compared to N^3 for inversion of G by the Gauss-Jordan method. Solution of equations (106) and (107), making use of the triangular properties of L and U, takes approximately as many multiplications as would be required for multiplication of G^{-1} by the column vector E. The factored matrices L and U are saved in NEC since the solution for induced current may be repeated for a number of different excitations. This, then, requires only the repeated solution of equations (106) and (107).

Computation of the elements of the matrix G and solution of the matrix equation are the two most time-consuming steps in computing the response of a structure, often accounting for over 90% of the computation time. This may be reduced substantially by making use of symmetries of the structure, either symmetry about a plane, or symmetry under rotation.

In rotational symmetry, a structure having M sectors is unchanged when rotated by any multiple of 360/M degrees. If the equations for all segments and patches in the first sector are numbered first and followed by successive sectors in the same order, the matrix equation can be expanded in submatrices in the form

$$\begin{bmatrix} A_1 & A_2 & A_3 & \cdots & A_{M-1} & A_M \\ A_M & A_1 & A_2 & \cdots & A_{M-2} & A_{M-1} \\ A_{M-1} & A_M & A_1 & & A_{M-3} & A_{M-2} \\ \vdots & & & & \vdots & \vdots \\ A_2 & A_3 & A_4 & & A_M & A_1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ \vdots \\ I_M \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \\ E_3 \\ \vdots \\ E_M \end{bmatrix} \tag{108}$$

If there are N_c equations in each sector, E_i and I_i are N_c element column vectors of the excitations and currents in sector i. A_i is a submatrix of order N_c containing the interaction fields in sector 1 due to currents in sector i. Due to symmetry, this is the same as the fields in sector k due to currents in sector i + k, resulting in the repetition pattern shown. Thus only matrix elements in the first row of submatrices need be computed, reducing the time to fill the matrix by a factor of 1/M.

The time to solve the matrix equation can also be reduced by expanding the excitation subvectors in a discrete Fourier series as

$$E_i = \sum_{k=1}^{M} S_{ik} E_k \qquad i=1,\ldots,M \ , \tag{109}$$

$$E_i = \frac{1}{M} \sum_{k=1}^{M} S_{ik}^{*} E_k \qquad i=1,\ldots,M \ , \tag{110}$$

where

$$S_{ik} = \exp\left[j2\pi(i-1)(k-1)/M\right] \ , \tag{111}$$

$j=\sqrt{-1}$, and * indicates the conjugate of the complex number. Examining a component in the expansion,

$$E = \begin{bmatrix} S_{1k} E_k \\ S_{2k} E_k \\ \cdot \\ \cdot \\ \cdot \\ S_{Mk} E_k \end{bmatrix} \ , \tag{112}$$

it is seen that the excitation differs from sector to sector only by a uniform phase shift. This excitation of a rotationally symmetric structure results in a solution having the same form as the excitation, i.e.,

$$I = \begin{bmatrix} S_{1k}\, I_k \\ S_{2k}\, I_k \\ \vdots \\ S_{Mk}\, I_k \end{bmatrix} . \qquad (113)$$

It can be shown that this relation between solution and excitation holds for any matrix having the form of that in equation (108). Substituting these components of E and I into equation (108) yields the following matrix equation of order N_c relating I_k to E_k:

$$\left[S_{1k}\, A_1 + S_{2k}\, A_2 + \ldots + S_{Mk}\, A_M\right] \left[I_k\right] = S_{1k} \left[E_k\right] . \qquad (114)$$

The solution for the total excitation is then obtained by an inverse transformation,

$$I_i = \sum_{k=1}^{M} S_{ik}\, I_k \qquad i=1, \ldots, M . \qquad (115)$$

The solution procedure, then, is first to compute the M submatrices A_i and Fourier-transform these to obtain

$$A_i = \sum_{k=1}^{M} S_{ik}\, A_k \qquad i=1, \ldots, M . \qquad (116)$$

The matrices A_i, of order N_c, are then each factored into upper and lower triangular matrices by the Gauss elimination method. For each excitation vector, the transformed subvectors are then computed by equation (110) and the transformed current subvectors are obtained by solving the M equations,

$$[A_i]\, [I_i] = [E_i] . \qquad (117)$$

The total solution is then given by equation (115).

The same procedure can be used for structures that have planes of symmetry. The Fourier transform is then replaced by even and odd excitations about each symmetry plane. All equations remain the same with the exception

that the matrix S with elements S_{ij}, given by equation (111), is replaced by the following matrices:

For one plane of symmetry,

$$S = \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix};$$

For two orthogonal planes of symmetry,

$$S = \begin{bmatrix} 1 & 1 & 1 & 1 \\ 1 & -1 & 1 & -1 \\ 1 & 1 & -1 & -1 \\ 1 & -1 & -1 & 1 \end{bmatrix};$$

and for three orthogonal symmetry planes,

$$S = \begin{bmatrix} 1 & 1 & 1 & 1 & 1 & 1 & 1 & 1 \\ 1 & -1 & 1 & -1 & 1 & -1 & 1 & -1 \\ 1 & 1 & -1 & -1 & 1 & 1 & -1 & -1 \\ 1 & -1 & -1 & 1 & 1 & -1 & -1 & 1 \\ 1 & 1 & 1 & 1 & -1 & -1 & -1 & -1 \\ 1 & -1 & 1 & -1 & -1 & 1 & -1 & 1 \\ 1 & 1 & -1 & -1 & -1 & -1 & 1 & 1 \\ 1 & -1 & -1 & 1 & -1 & 1 & 1 & -1 \end{bmatrix}.$$

For either rotational or plane symmetry, the procedure requires factoring of M matrices of order N_c rather than one matrix of order MN_c. Each excitation then requires the solution of the M matrix equations. Since the time for factoring is approximately proportional to the cube of the matrix order and the time for solution is proportional to the square of the order, the symmetry results in a reduction of factor time by M^{-2} and in solution time by M^{-1}. The time to compute the transforms is generally small compared to the time for matrix operations since it is proportional to a lower power of N_c. Symmetry also reduces the number of locations required for matrix storage by M^{-1} since only the first row of submatrices need be stored. The transformed matrices, A_i, can replace the matrices A_i as they are computed.

NEC includes a provision to generate and factor an interaction matrix and save the result on a file. A later run, using the file, may add to the structure and solve the complete model without unnecessary repetition of calculations. This procedure is called the Numerical Green's Function (NGF) option since the effect is as if the free space Green's function in NEC were replaced by the Green's function for the structure on the file. The NGF is particularly useful for a large structure, such as a ship, on which various antennas will be added or modified. It also permits taking advantage of partial symmetry since a NGF file may be written for the symmetric part of a structure, taking advantage of the symmetry to reduce computation time. Unsymmetric parts can then be added in a later run.

For the NGF solution the matrix is partitioned as

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \end{bmatrix},$$

where A is the interaction matrix for the initial structure, D is the matrix for the added structure, and B and C represent mutual interactions. The current is computed as

$$I_2 = \left[D - CA^{-1}B\right]^{-1} \left[E_2 - CA^{-1} E_1\right] ,$$

$$I_1 = A^{-1} E_1 - A^{-1} BI_2 ,$$

after the factored matrix A has been read from the NGF file along with other necessary data.

Electrical connections between the new structure and the old (NGF) structure require special treatment. If a new wire or patch connects to an old wire the current basis function for the old wire segment is changed by the modified condition at the junction. The old basis function is given zero amplitude by adding a new equation having all zeros except for a one in the column of the old basis function. A new column is added for the corrected basis function. When a new wire connects to an old patch the patch must be divided into four new patches to apply the connection condition of equation (51). Hence both the current basis function and match point for the old patch are replaced.

Section IV
Effect of a Ground Plane

In the integral equation formulation used in NEC, a ground plane changes the solution in three ways: (1) by modifying the current distribution through near-field interaction; (2) by changing the field illuminating the structure; and (3) by changing the reradiated field. Effects (2) and (3) are easily analyzed by plane-wave reflection as a direct ray and a ray reflected from the ground. The reradiated field is not a plane wave when it reflects from the ground, but, as can be seen from reciprocity, plane-wave reflection gives the correct far-zone field. Analysis of the near-field interaction effect is, however, much more difficult.

In Section II, the kernels of the integral equations are free-space Green's functions, representing the E or H field at a point $\vec{r}$ due to an infinitesimal electric current element at $\vec{r}'$. When a ground is present the free space Green's functions must be replaced by Green's functions for the ground problem. The solution for the fields of current elements in the presence of a ground plane was developed by Arnold Sommerfeld (ref. 20). While this solution has been used directly in integral-equation computer codes, excessive computation time greatly limits its use. Numerous approximations to the Sommerfeld solution have been developed that require less time for evaluation but all have limited applicability.

The NEC code has three options for grounds. The most accurate for lossy grounds uses the Sommerfeld solution for interaction distances less than one wavelength and an asymptotic expansion for larger distances. To keep the solution time reasonable, a grid of values of the Sommerfeld solution is generated and interpolation is used to find specific values. This method is presently implemented only for wires in NEC but could be extended to patches. The solution for a perfectly conducting ground is much simpler since the ground may be replaced by the image of the currents above it. The third option models a lossy ground by a modified image method using the Fresnel plane-wave reflection coefficients. While specular reflection does not accurately describe the behavior of near fields, the approximation has been found to provide useful results for structures that are not too near to the ground (refs. 21, 22). The attraction of this method is its simplicity and speed of computation which are the same as for the image method for perfect ground.

1. THE SOMMERFELD/NORTON METHOD

The Sommerfeld/Norton ground option in NEC originated with the code WFLLL2A (ref. 23) which uses numerical evaluation of the Sommerfeld integrals for ground fields when the interaction distance is small and uses Norton's asymptotic approximations (ref. 24) for larger distances. Since evaluation of the Sommerfeld integrals is very time consuming, a code, SOMINT, was developed (ref. 25) which uses bivariate interpolation in a table of pre-computed Sommerfeld integral values to obtain the field values needed for integration over current distributions. This method greatly reduces the required computation time. NEC uses a similar interpolation method with modifications to allow wires closer to the air-ground interface and to further reduce computation time. Although the code WFLLL2A allows wires both above and below the interface, both NEC and SOMINT are presently restricted to wires on the free-space side. The method used in NEC to evaluate the field over ground is described below, and the numerical evaluation of the Sommerfeld integrals to fill the interpolation grid is discussed in Section IV-2.

The electric field above an air-ground interface due to an infinitesimal current element of strength Iℓ also above the interface, with parameters shown in figure 6, is given by the following expressions:

$$E_\rho^V = C_1 \frac{\partial^2}{\partial\rho\partial z}\left[G_{22} - G_{21} + k_1^2 V_{22}\right] , \tag{118}$$

$$E_z^V = C_1\left(\frac{\partial^2}{\partial z^2} + k_2^2\right)\left(G_{22} - G_{21} + k_1^2 V_{22}\right) , \tag{119}$$

$$E_\rho^H = C_1 \cos\phi\left[\frac{\partial^2}{\partial\rho^2}\left(G_{22} - G_{21} + k_2^2 V_{22}\right) + k_2^2\left(G_{22} - G_{21} + U_{22}\right)\right] , \tag{120}$$

$$E_\phi^H = -C_1 \sin\phi\left[\frac{1}{\rho}\frac{\partial}{\partial\rho}\left(G_{22} - G_{21} + k_2^2 V_{22}\right) + k_2^2\left(G_{22} - G_{21} + U_{22}\right)\right] , \tag{121}$$

$$E_z^H = C_1 \cos\phi \frac{\partial^2}{\partial z\partial\rho}\left(G_{22} + G_{21} - k_1^2 V_{22}\right) , \tag{122}$$

$$C_1 = \frac{-j\omega I\ell\mu_o}{4\pi k_2^2} , \tag{123}$$

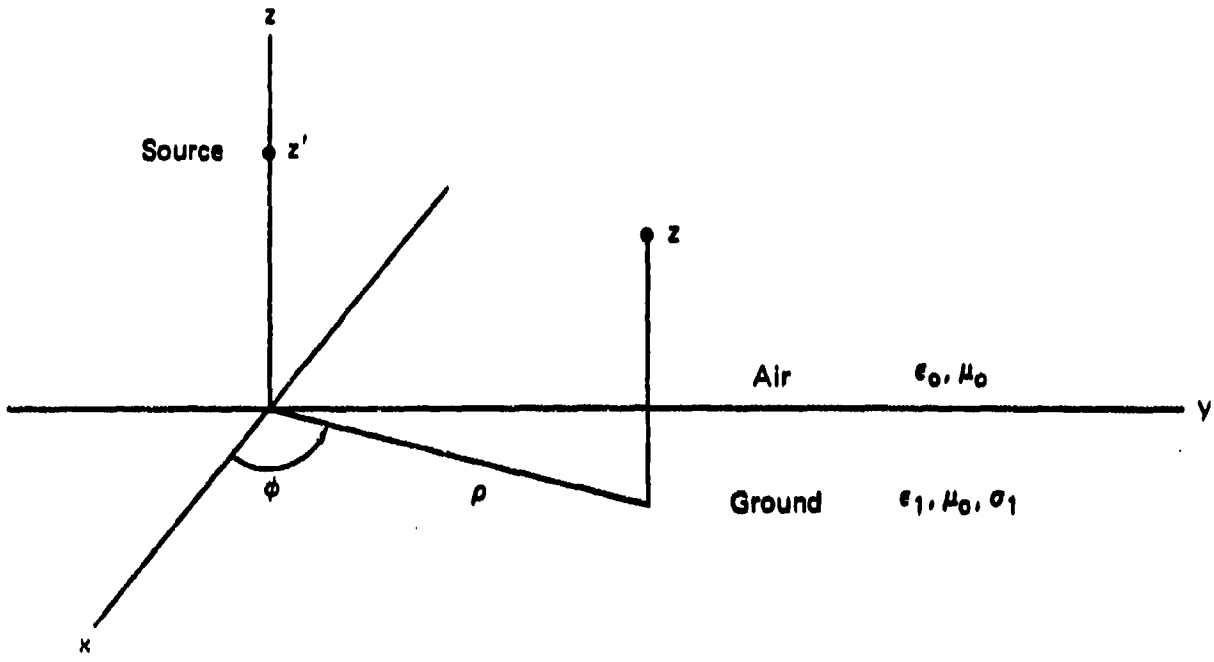


Figure 6. Coordinates for Evaluating the Field of a Current Element Over Ground.

$$k_1^2 = \omega^2 \mu_o \epsilon_o \left(\frac{\epsilon_1}{\epsilon_o} - \frac{j\sigma_1}{\omega \epsilon_o} \right) , \tag{124}$$

$$k_2^2 = \omega^2 \mu_o \epsilon_o , \tag{125}$$

where the superscript indicates a vertical (V) or horizontal (H) current element and the subscript indicates the cylindrical component of the field vector. The horizontal current element is along the x axis.

G_{22} and G_{21} are the free space and image Green's functions

$$G_{22} = \exp(-jk_2 R_2)/R_2 , \tag{126}$$

$$G_{21} = \exp(-jk_2 R_1)/R_1 , \tag{127}$$

where

$$R_1 = \left[\rho^2 + (z + z')^2 \right]^{1/2} , \tag{128}$$

$$R_2 = \left[\rho^2 + (z - z')^2 \right]^{1/2} , \tag{129}$$

and U_{22} and V_{22} are Sommerfeld integrals involving the zeroth order Bessel function, J_o

$$U_{22} = 2\int_o^\infty \frac{\exp[-\gamma_2(z + z')]\ J_o(\lambda\rho)\lambda d\lambda}{\gamma_1 + \gamma_2} \quad , \tag{130}$$

$$V_{22} = 2\int_o^\infty \frac{\exp[-\gamma_2(z + z')]\ J_o(\lambda\rho)\lambda d\lambda}{k_1^2\,\gamma_2 + k_2^2\,\gamma_1} \quad , \tag{131}$$

where

$$\gamma_1 = \left(\lambda^2 - k_1^2\right)^{1/2} \quad , \tag{132}$$

$$\gamma_2 = \left(\lambda^2 - k_2^2\right)^{1/2} \quad . \tag{133}$$

In NEC we need to compute the fields due to current filaments with arbitrary length and orientation by combining the field components in equations (118) through (122) and integrating over current distributions composed of constant, sine, and cosine components. Direct numerical integration over the segments is difficult due to singularities in the fields. G_{22} has a $1/R_2$ singularity while G_{21}, U_{22} and V_{22} each have $1/R_1$ singularities. The derivatives in the field expressions result in $1/R_3$ singularities with a triplet-like behavior in the field components parallel to the current filament. The resulting cancellation makes accurate numerical integration near the singularity very difficult.

The free-space field has a similar singularity, but as discussed in Section III-3, the integral over a straight filament may be evaluated in closed form for a sinusoidal current with free-space wavelength and involves only a numerical integration of G_{22} for a constant current. The dominant singular component of the ground field may be integrated in the same way. The terms involving G_{22} in equation (118) through (122) are, in fact, the field of the current element in free space, and their integral is obtained from the free-space routines in NEC.

The remaining terms represent the field due to ground and are singular at $R_1 = 0$. The singularities in U_{22} and V_{22} result from the failure of the integrals in equations (130) and (131) to converge without the exponential and

Bessel functions as ρ and $z + z'$ go to zero. The singular behavior of U_{22} and V_{22} as ρ and $z + z'$ go to zero may be found by setting $\gamma_1 = \gamma_2 = \lambda$ since the dominant contributions to the integrals for small ρ and $z + z'$ come from λ much greater than k_1 or k_2. Here, however, we only replace γ_1 by γ_2 and use the integrals

$$V_{22} \approx 2\int_o^\infty \frac{\exp[-\gamma_2(z + z')]\ J_o(\lambda\rho)\lambda d\lambda}{\gamma_2(k_1^2 + k_2^2)} = \frac{2G_{21}}{k_1^2 + k_2^2} \ , \tag{134}$$

$$U_{22} \approx \int_o^\infty \frac{\exp[-\gamma_2(z + z')]\ J_o(\lambda\rho)\lambda d\lambda}{\gamma_2} = G_{21} \tag{135}$$

$$|k_1|\rho << 1, \quad |k_1|(z + z') << 1,$$

which have the correct singular behavior and can be combined with the G_{21} terms. The field components due to ground [equation (108) through (122) without the G_{22} terms] may then be written as

$$G_\rho^V = C_1 \frac{\partial^2}{\partial\rho\partial z} k_1^2 V'_{22} + C_1 \frac{k_1^2 - k_2^2}{k_1^2 + k_2^2} \frac{\partial^2}{\partial\rho\partial z} G_{21} \ , \tag{136}$$

$$G_z^V = C_1\left(\frac{\partial^2}{\partial z^2} + k_2^2\right) k_1^2 V'_{22} + C_1 \frac{k_1^2 - k_2^2}{k_1^2 + k_2^2}\left(\frac{\partial^2}{\partial z^2} + k_2^2\right) G_{21} \tag{137}$$

$$G_\rho^H = C_1 \cos\phi \left(\frac{\partial^2}{\partial\rho^2} k_2^2 V'_{22} + k_2^2 U'_{22}\right) - C_1 \cos\phi \frac{k_1^2 - k_2^2}{k_1^2 + k_2^2}\left(\frac{\partial^2}{\partial\rho^2} + k_2^2\right) G_{21} \ , \tag{138}$$

$$G_\phi^H = -C_1 \sin\phi \left(\frac{1}{\rho}\frac{\partial}{\partial\rho} k_2^2 V'_{22} + k_2^2 U'_{22}\right) + C_1 \sin\phi \frac{k_1^2 - k_2^2}{k_1^2 + k_2^2}\left(\frac{1}{\rho}\frac{\partial}{\partial\rho} + k_2^2\right) G_{21} \ , \tag{139}$$

$$G_z^H = -\cos\phi \; G_\rho^V \; , \tag{140}$$

where

$$U'_{22} = U_{22} - \frac{2k_2^2}{k_2^2 + k_1^2} \; G_{21} \; ,$$

$$= 2\int_o^\infty \left[\frac{1}{\gamma_1 + \gamma_2} - \frac{k_2^2}{\gamma_2 (k_1^2 + k_2^2)} \right] \exp[-\gamma_2 (z + z')] \tag{141}$$

$$\times J_o(\lambda\rho)\lambda d\lambda \quad ,$$

$$V'_{22} = V_{22} - \frac{2}{k_1^2 + k_2^2} \; G_{21} \; ,$$

$$= 2\int_o^\infty \left[\frac{1}{k_1^2 \gamma_2 + k_2^2 \gamma_1} - \frac{1}{\gamma_2 \; k_1^2 + k_2^2} \right] \tag{142}$$

$$\times \exp[-\gamma_2 (z + z')] \; J_o(\lambda\rho)\lambda d\lambda \quad .$$

In equations (136) through (140) the dominant singular component has been subtracted out of V_{22} and combined with G_{21}. The integral for V'_{22} converges without the exponential or Bessel function factors and remains finite as ρ and $z + z'$ go to zero. The derivatives of V'_{22} in the field expressions have $1/R_1$ singularities, but this is much less of a problem for numerical integration than the previous $1/R_1^3$ singularity. The singularity could be taken out of U_{22} also, but, instead, a term is taken out that results in the final terms in equations (136) through (139) being the image field multiplied by $(k_1^2 - k_2^2)/(k_1^2 + k_2^2)$. The integral over the current filament of these image terms is evaluated by the free-space equations leaving only the U'_{22} and V'_{22} terms to be integrated numerically. U'_{22} still has a $1/R_1$ singularity, but that is no worse than the derivatives of V'_{22}. With the thin-wire approximation, R_1 is never less than the wire radius so the integration is not difficult in practical cases.

The components left for numerical integration over the current distribution are then

$$F_\rho^V = C_1 \frac{\partial^2}{\partial\rho\partial z} k_1^2 V'_{22} , \tag{143}$$

$$F_z^V = C_1\left(\frac{\partial^2}{\partial z^2} + k_2^2\right) k_1^2 V'_{22} , \tag{144}$$

$$F_\rho^H = C_1\cos\phi\left(\frac{\partial^2}{\partial\rho^2} k_2^2 V'_{22} + k_2^2 U'_{22}\right) , \tag{145}$$

$$F_\phi^H = -C_1\sin\phi\left(\frac{1}{\rho}\frac{\partial}{\partial\rho} k_2^2 V'_{22} + k_2^2 U'_{22}\right) , \tag{146}$$

$$F_z^H = -\cos\phi\ F_\rho^V . \tag{147}$$

Since the integrals in equations (141) and (142) cannot be evaluated in closed form the following terms must be evaluated by numerical integration over λ:

$$\frac{\partial^2 V'_{22}}{\partial\rho^2} = \int_o^\infty D_2 \exp\left[-\gamma_2(z + z')\right] J''_o(\lambda\rho)\lambda^3 d\lambda , \tag{148}$$

$$\frac{\partial^2 V'_{22}}{\partial z^2} = \int_o^\infty D_2 \gamma_2^2 \exp\left[-\gamma_2(z + z')\right] J_o(\lambda\rho)\lambda d\lambda , \tag{149}$$

$$\frac{\partial^2 V'_{22}}{\partial\rho\partial z} = -\int_o^\infty D_2\gamma_2 \exp\left[-\gamma_2(z + z')\right] J'_o(\lambda\rho)\lambda^2 d\lambda , \tag{150}$$

$$\frac{1}{\rho}\frac{\partial V'_{22}}{\partial\rho} = \frac{1}{\rho}\int_o^\infty D_2 \exp\left[-\gamma_2(z + z')\right] J'_o(\lambda\rho)\lambda^2 d\lambda , \tag{151}$$

$$V'_{22} = \int_o^\infty D_2 \exp\left[-\gamma_2(z + z')\right] J_o(\lambda\rho)\lambda d\lambda , \tag{152}$$

$$U'_{22} = \int_o^\infty D_1 \exp\left[-\gamma_2(z + z')\right] J_o(\lambda\rho)\lambda d\lambda , \tag{153}$$

where

$$D_1 = \frac{2}{\gamma_2 + \gamma_2} - \frac{2\,k_2^2}{\gamma_2(k_1^2 + k_2^2)} \quad , \tag{154}$$

$$D_2 = \frac{2}{k_1^2\,\gamma_2 + k_2^2\,\gamma_1} - \frac{2}{\gamma_2(k_1^2 + k_2^2)} \quad . \tag{155}$$

Evaluating these integrals over λ for each point needed in the numerical integration over the current distribution is slow on even the fastest computers. Hence an interpolation technique is used for the remaining field components as was done in the code SOMINT for the total field due to ground. Since the integrals depend only on ρ and $z + z'$ a grid of values is generated for the field components of equations (143) through (146) and bivariate interpolation is used to obtain values for integration over a current distribution.

To facilitate interpolation in the region of the $1/R_1$ singularity, the components are divided by a function having a similar singularity and interpolation is performed on the ratio. The field components of equations (143) through (146) are divided by $\exp(-jkR_1)/R_1$ for all values of R_1 to remove the singularity and the free-space phase factor before interpolation. The factors $\sin\phi$ or $\cos\phi$ are also omitted until after interpolation to avoid introducing the ϕ dependence. The surfaces to which interpolation is applied are then

$$I_\rho^V = C_1\,R_1\,\exp(jkR_1)\,\frac{\partial^2}{\partial\rho\partial z}\,k_1^2\,V_{22}' \quad , \tag{156}$$

$$I_z^V = C_1\,R_1\,\exp(jkR_1)\left(\frac{\partial^2}{\partial z^2} + k_2^2\right)k_1^2\,V_{22}' \quad , \tag{157}$$

$$I_\rho^H = C_1\,R_1\,\exp(jkR_1)\left(\frac{\partial^2}{\partial\rho^2}\,k_2^2\,V_{22}' + k_2^2\,U_{22}'\right) \quad , \tag{158}$$

$$I_\phi^H = -\,C_1\,R_1\,\exp(jkR_1)\left(\frac{1}{\rho}\,\frac{\partial}{\partial\rho}\,k_2^2\,V_{22}' + k_2^2\,U_{22}'\right) \quad . \tag{159}$$

After interpolation on the smoothed surfaces the results are multiplied by the omitted factors to give the correct values.

With the singularity removed, interpolation may be used for arbitrarily small values of ρ and $z + z'$. The values for $R_1 = 0$ in the interpolation grid must be found as limits for R_1 approaching zero, however, since the integrals

do not converge in this case. When ρ and $z + z'$ approach zero the dominant contributions in equations (148) through (153) come from large λ. Hence the singular behavior can be found by setting γ_1 and γ_2 equal to λ. First, however, it is necessary to approximate D_1 and D_2 for $|\lambda| >> |k_1|$ as

$$D_1 = C_2/\lambda \ , \ C_2 = \frac{k_1^2 - k_2^2}{k_1^2 + k_2^2} \ , \tag{160}$$

$$D_2 = C_3/\lambda^3, \ C_3 = \frac{k_2^2\left(k_1^2 - k_2^2\right)}{\left(k_1^2 + k_2^2\right)^2} \ . \tag{161}$$

For $|k_1|\rho << 1$ and $|k_1|(z + z') << 1$ the integrals become

$$\frac{\partial^2 V'_{22}}{\partial \rho^2} \approx C_3 \int_o^\infty \exp\left[-\lambda(z + z')\right] J''_o(\lambda\rho)\, d\lambda \ , \tag{162}$$

$$= C_3\left[\frac{1 - \sin\theta}{\cos^2\theta} - 1\right] \frac{1}{R_1} \ ,$$

$$\frac{\partial^2 V'_{22}}{\partial z^2} \approx C_3 \int_o^\infty \exp\left[-\lambda(z + z')\right] J_o(\lambda\rho) d\lambda = \frac{C_3}{R_1} \ , \tag{163}$$

$$\frac{\partial^2 V'_{22}}{\partial \rho \partial z} \approx - C_3 \int_o^\infty \exp\left[-\lambda(z + z')\right] J'_o(\lambda\rho) d\lambda = \frac{C_3(1 - \sin\theta)}{R_1 \cos\theta} \ , \tag{164}$$

$$\frac{1}{\rho}\frac{V'_{22}}{\partial \rho} \approx \frac{C_3}{\rho} \int_o^\infty \exp\left[-\lambda(z + z')\right] J'_o(\lambda\rho) \frac{1}{\lambda} d\lambda = \frac{-C_3(1 - \sin\theta)}{R_1 \cos^2\theta} \ , \tag{165}$$

$$U'_{22} \approx C_2 \int_o^\infty \exp\left[-\lambda(z + z')\right] J_o(\lambda\rho)\, d\lambda = \frac{C_2}{R_1} \ , \tag{166}$$

where

$$R_1 = \left[\rho^2 + (z + z')^2\right]^{1/2} \ , \tag{167}$$

$$\theta = \tan^{-1}\left[(z + z')/\rho\right] \ . \tag{168}$$

V'_{22} remains finite as R_1 goes to zero and hence is neglected. Equations (156) through (159) for R_1 approaching zero are then

$$I_\rho^V = C_1 C_3 k_1^2 \left(\frac{1 - \sin\theta}{\cos\theta}\right) , \tag{169}$$

$$I_z^V = C_1 C_3 k_1^2 , \tag{170}$$

$$I_\rho^H = C_1 k_2^2 \left[C_2 - C_3 + C_3\left(\frac{1 - \sin\theta}{\cos^2\theta}\right)\right] , \tag{171}$$

$$I_\phi^H = -C_1 k_2^2 \left[C_2 - C_3\left(\frac{1 - \sin\theta}{\cos^2\theta}\right)\right] . \tag{172}$$

Since the limiting values as R_1 goes to zero are functions of θ it is necessary to use R_1 and θ as the interpolation variables rather than ρ and $z + z'$.

Figures 7 through 10 are plots of the surfaces to which interpolation is applied for typical ground parameters. The width of the region of relatively rapid variation along the R_1 axis appears to be proportional to the wavelength

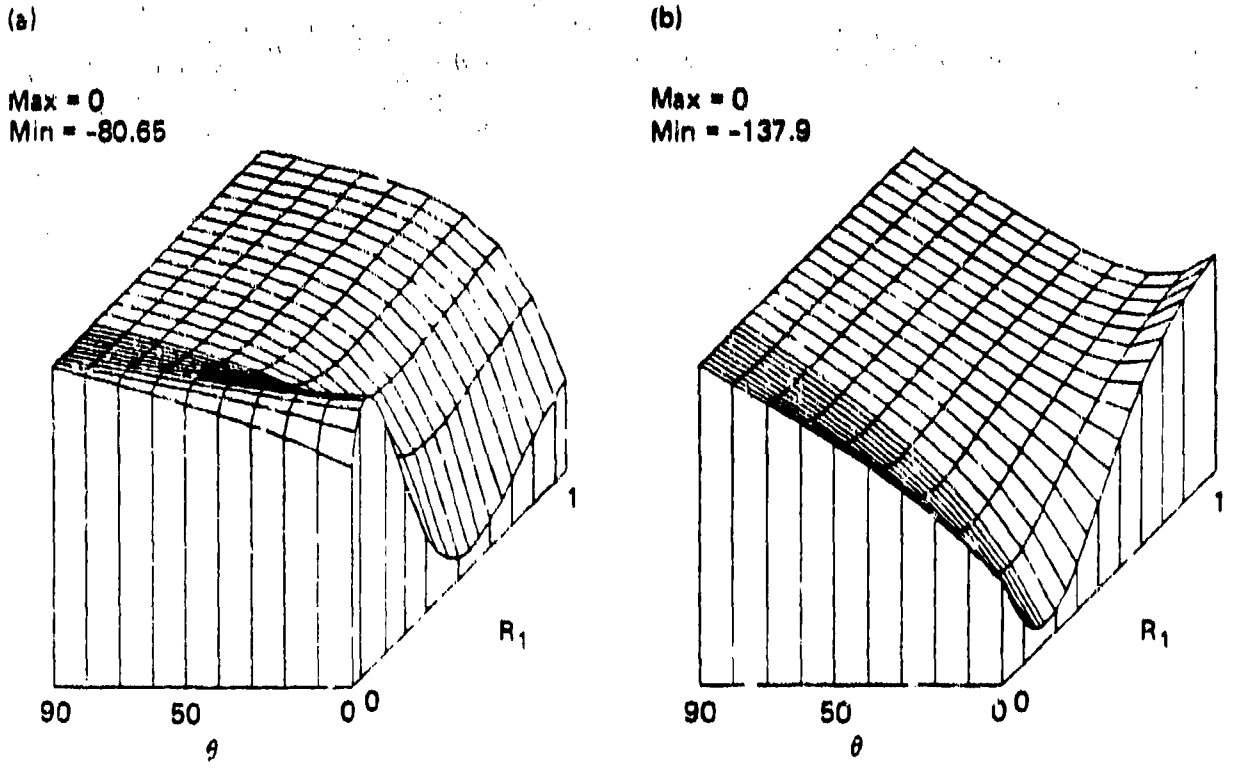


Figure 7. Real (a) and Imaginary (b) Parts of I_ρ^V for $\varepsilon_1/\varepsilon_o = 4$, $\sigma_1 = 0.001$ mhos/m, frequency = 10 MHz.

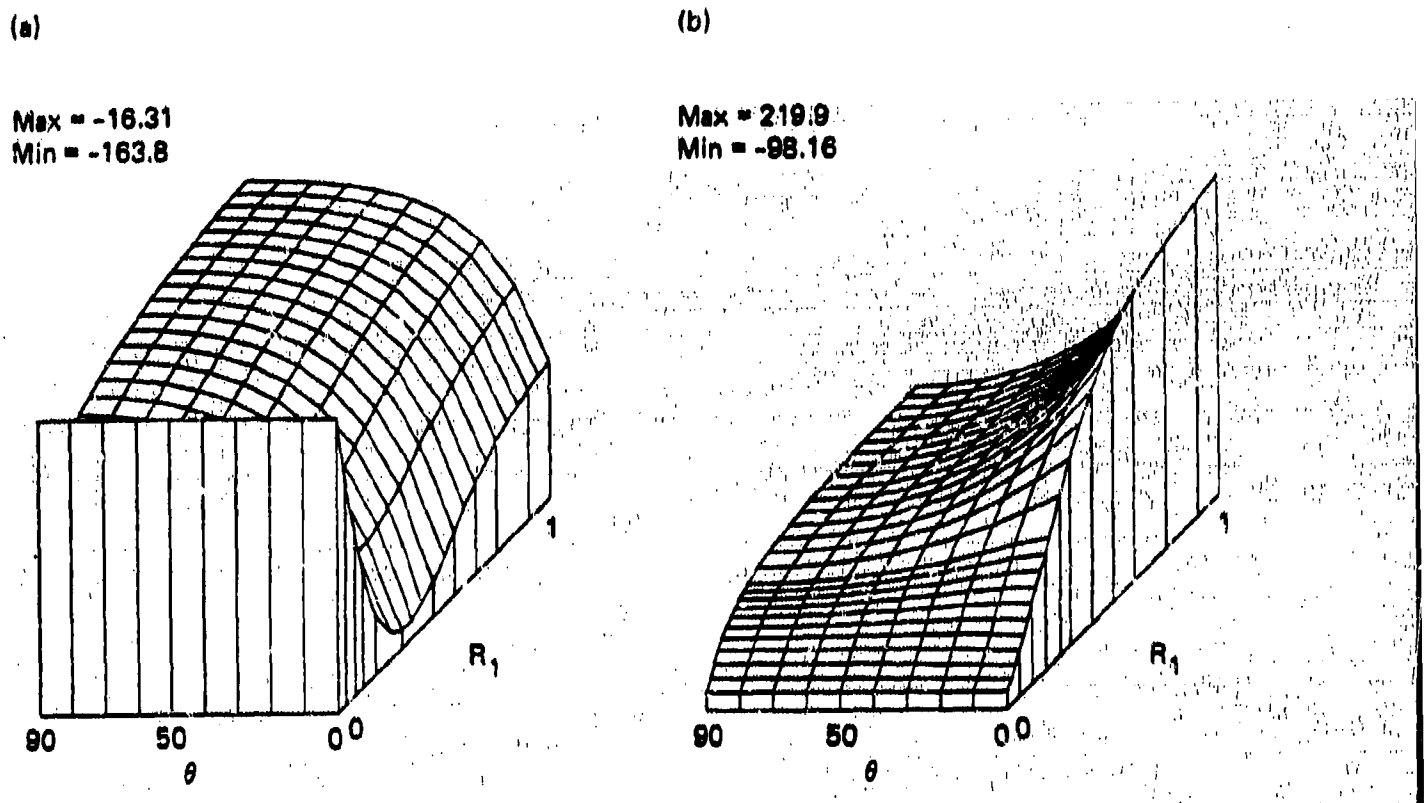


Figure 8. Real (a) and Imaginary (b) Parts of I_z^V for $\varepsilon_1/\varepsilon_o = 4$, $\sigma_1 = 0.001$ mhos/m, frequency = 10 MHz.

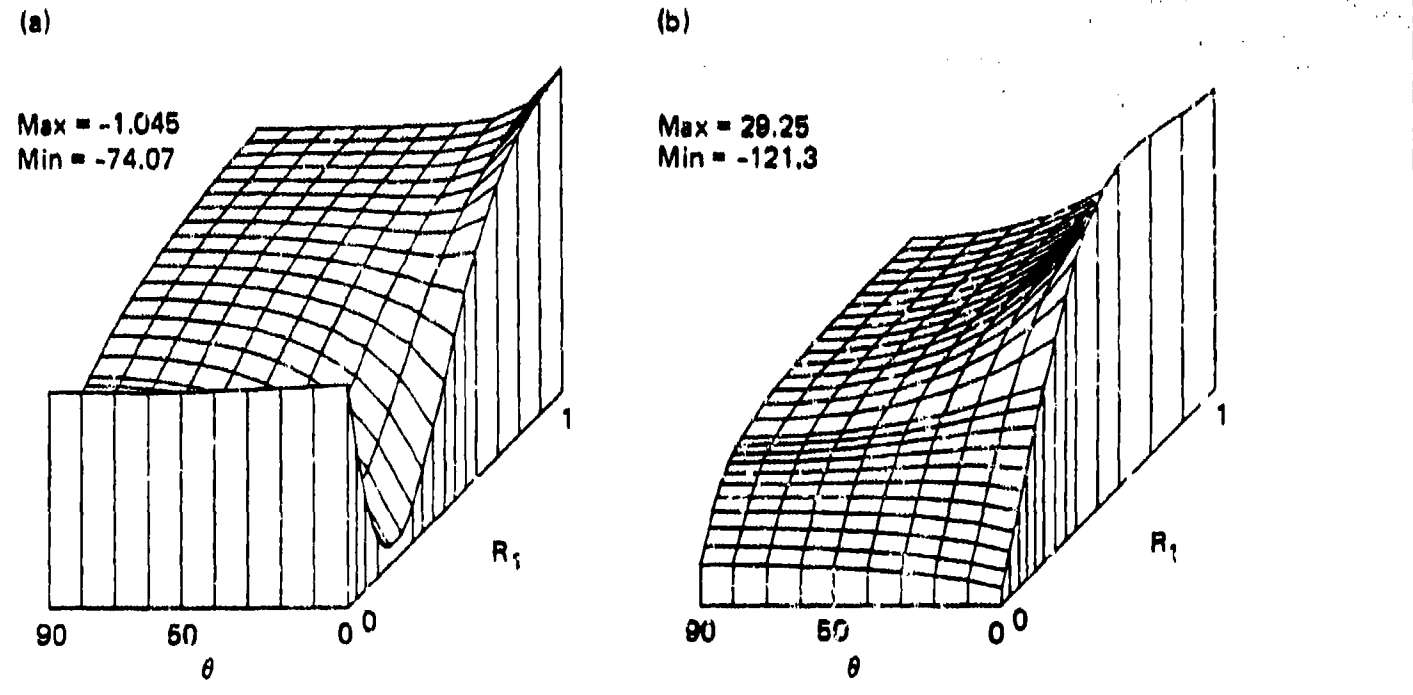


Figure 9. Real (a) and Imaginary (b) Parts of I_ρ^H for $\varepsilon_1/\varepsilon_o = 4$, $\sigma_1 = 0.001$ mhos/m, frequency = 10 MHz.

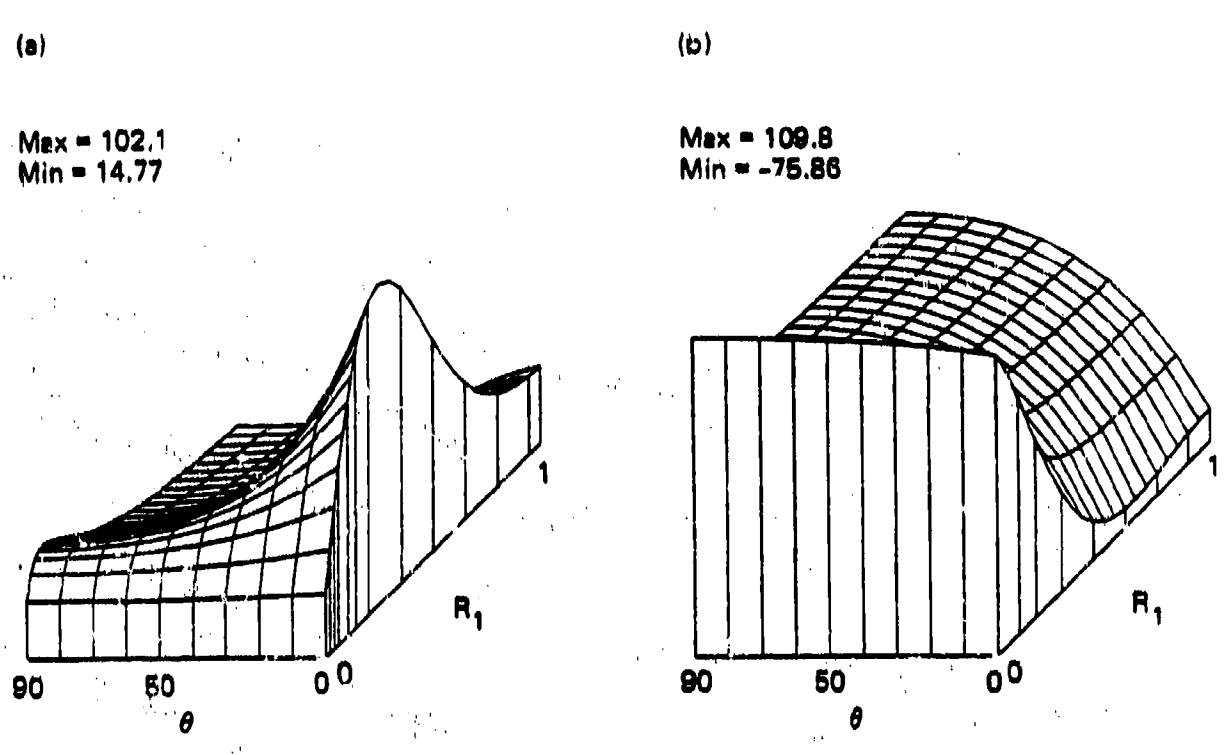


Figure 10. Real (a) and Imaginary (b) Parts of I_ϕ^H for $\varepsilon_1/\varepsilon_o = 4$, $\sigma_1 = 0.001$ mhos/m, frequency = 10 MHz.

in the lower medium and hence is concentrated closer to $R_1 = 0$ for larger dielectric constants. At a finite R_1, the functions approach zero as ε_1 and σ_1 become large. When loss is small the strong wave in the lower medium results in a significant evanescent wave along the interface in the upper medium as shown in figure 11.

In NEC the interpolation region from 0 to 1 wavelength in R_1 is divided into three grids, as shown in figure 12, on which bivariate cubic interpolation is used. For a given point, the correct grid region is determined and cubic surfaces in R_1 and θ, fit to a 4-point by 4-point region containing the desired point, are evaluated for each of the four quantities I_ρ^V, I_z^V, I_ρ^H, and I_ϕ^H. The grid point spacings used are:

Grid	ΔR_1	$\Delta\theta$
1	0.02λ	10°
2	0.05λ	5°
3	0.1λ	10°

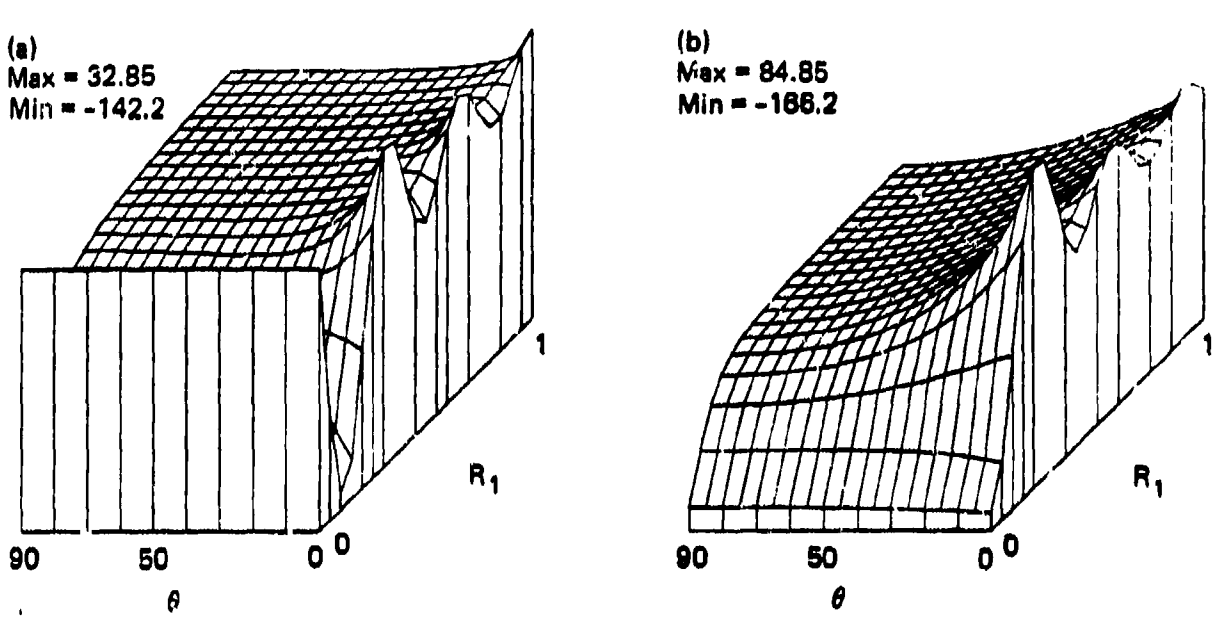


Figure 11. Real (a) and Imaginary (b) Parts of I_ρ^H for $\epsilon_1/\epsilon_o = 16$, $\sigma_1 = 0$.

These were determined by numerical tests to keep relative errors of interpolation generally in the range of 10^{-3} to 10^{-4}. A smaller ΔR_1 could be needed in grid 2 for large ϵ_1 and small σ_1 to handle the rapidly oscillating evanescent wave, but this is easily changed in the code.

The field evaluation in NEC uses variable-interval-width Romberg integration over the current distribution. At each integrand evaluation, the components I_ρ^V, I_z^V, I_ρ^H, and I_ϕ^H are obtained by interpolation, and the field components are combined according to the direction of the current. The numerical integral is then combined with the free-space field and with the image field multiplied by $(k_1^2 - k_2^2)/(k_1^2 + k_2^2)$ to obtain the total field over ground.

When R_1 from the observation point to the center of a wire segment is greater than one wavelength, the field is evaluated by Norton's asymptotic approximations (ref. 26) rather than the above method. Norton's formulas are given in Part II of this manual under subroutine GWAVE. Although they are less accurate than the Sommerfeld integral forms and require longer to evaluate than the interpolation, their use permits truncating the interpolation tables. Another approximation used for R_1 greater than a wavelength is to treat the current distribution on a segment as a lumped current element with the correct moment rather than integrating over the current distribution.

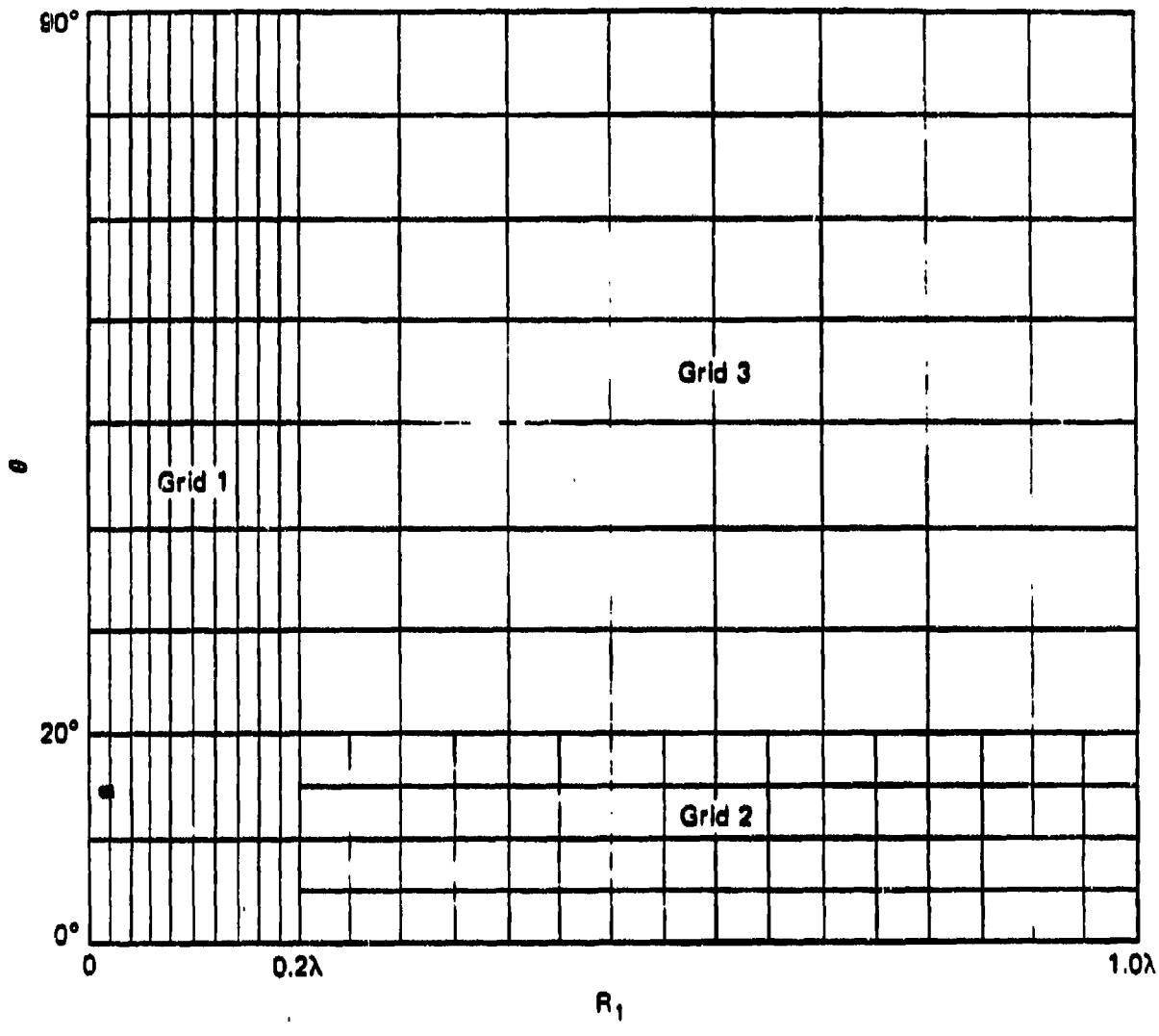


Fig. 12. Grid for Bivariate Interpolation of I's.

2. NUMERICAL EVALUATION OF THE SOMMERFELD INTEGRALS

The integrals in equations (148) through (153) are evaluated by numerical integration along contours in the complex λ plane. Although these integrals differ from the usual Sommerfeld integrals in the D_1 and D_2 terms, they are the same in the properties important to numerical integration — the locations of poles and branch cuts and the exponential behavior of the Bessel and exponential functions. The behavior of the integrands and numerical methods for evaluating the integrals are discussed in detail by Lytle and Lager

(ref. 27). This section describes the particular method used in NEC, which is basically the same as in the code WFLLL2A.

Since the integrands of the six integrals are similar, V'_{22} will be considered as typical. The integrands have branch cuts from $\pm k_1$ to infinity and $\pm k_2$ to infinity due to the square roots in γ_1 and γ_2 respectively. The branch cuts are chosen to be vertical, as shown in figure 13. The implications of this choice of branch cuts and the choice of Reimann sheets are discussed in ref. 27.

The key to rapid convergence in the numerical integration is to exploit the exponential behavior of the exponential and Bessel functions for large λ. The integration contour is deformed from the real axis into the complex plane, avoiding branch cuts and taking account of poles, to optimize convergence. With the vertical branch cuts chosen, there are no real poles on the primary Reimann sheet although virtual poles from D_1 or D_2 result in a near singularity in the region of $\pm k_2$ when k_1 approaches k_2 (free-space limit). Hence the integration contour should avoid the real axis in this region.

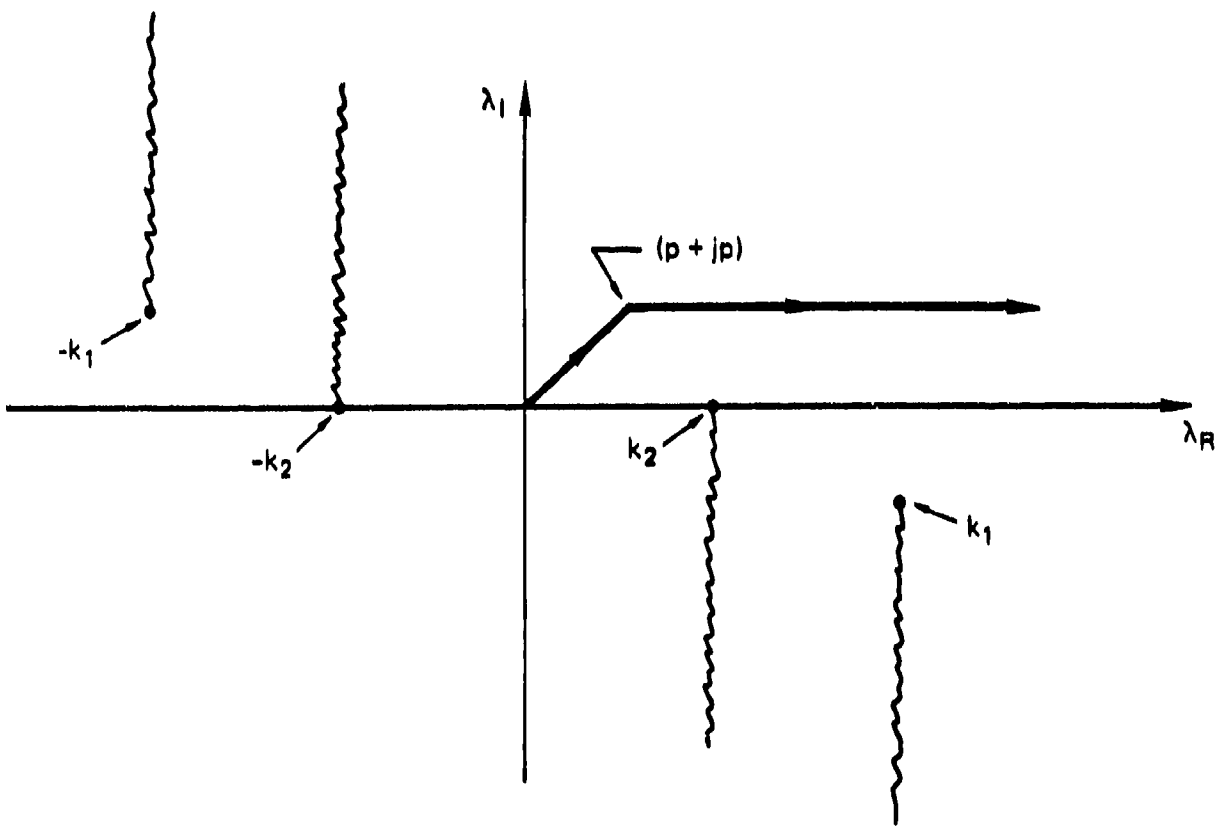


Figure 13. Contour for Evaluation of Bessel Function Form of Sommerfeld Integrals.

The contour used with the form of the integrals in equations (148) through (153) is shown in figure 13. The dominant factor for convergence in this case is the exponential function as λ_R increases. The Bessel function oscillates with slow convergence for increasing λ_R and grows exponentially as $|\lambda_I|$ increases. Hence it is of little help in convergence but restricts the contour to small $\rho|\lambda_I|$. The break in the contour is at $\lambda = p + jp$ where p is the minimum of $1/\rho$ and $1/(z + z')$.

Integration along this contour becomes difficult when $(z + z')/\rho$ is small since there may be many oscillations of the Bessel function before convergence. In this case an alternate form of the integrals is used which for V'_{22} is

$$V'_{22} = \frac{1}{2}\int_{-\infty}^{\infty} D_2 \exp\left[-\gamma_2(z + z')\right] H_o^{(2)}(\lambda\rho)\lambda d\lambda \ . \qquad (173)$$

Since the Hankel function of type 2 decays exponentially as λ_I becomes negative, it provides rapid convergence without the exp $-\gamma_2(z + z')$ factor. The behavior of the integrand can be seen from the large argument approximation

$$\exp\left[-\gamma_2(z + z')\right] H_o^{(2)}(\lambda\rho) \approx \sqrt{\frac{2j}{\pi\lambda\rho}} \left\{\exp -\lambda[\pm (z + z') + j\rho]\right\} \ ,$$

where, for the vertical branch cuts, the ± sign is

$$+ \text{ for } \lambda_R > -k_2 \text{ and } \lambda_I > 0 \ ,$$
$$+ \text{ for } \lambda_R > k_2 \text{ and } \lambda_I < 0 \ ,$$
$$- \text{ otherwise.}$$

Thus, an integration path having

$$\lambda_I < 0$$

and

$$\lambda_I/\lambda_R = -\rho/(z + z') \text{ for } \lambda_R > k_2$$

or

$$\lambda_I/\lambda_R = \rho/(z + z') \text{ for } \lambda_R < k_2$$

results in exponential convergence with little oscillation. The basic contour used with the Hankel function form is shown in figure 14 where

$$a = -j\ 0.4\ k_2 \ ,$$
$$b = (0.6 + j\ 0.2)k_2 \ ,$$

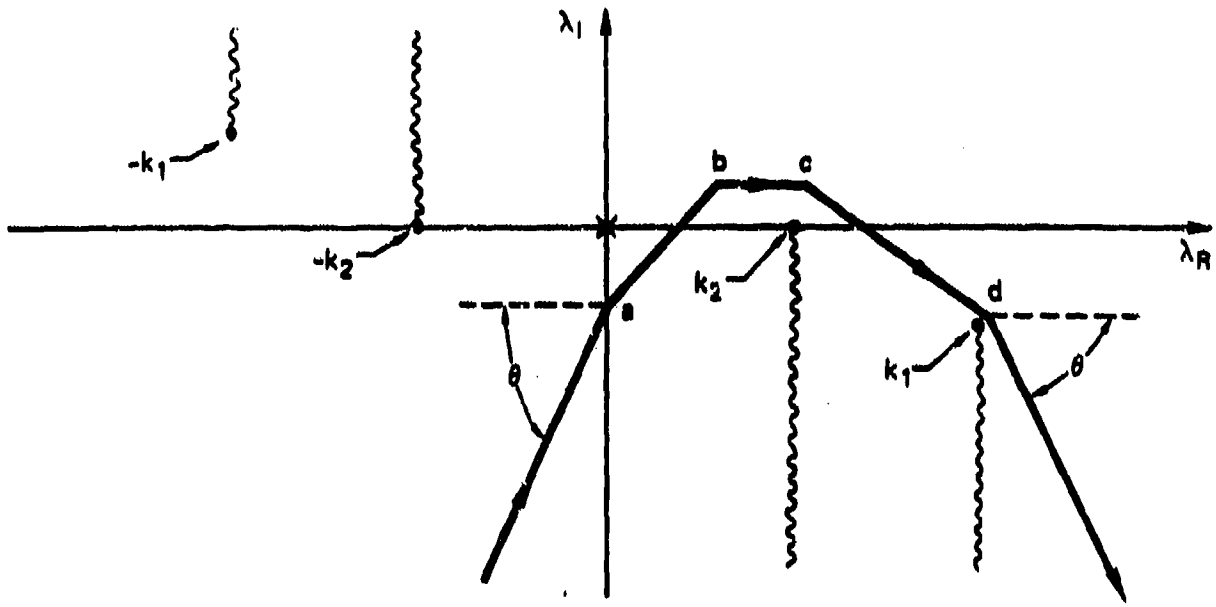


Figure 14. Contour for Evaluation of Hankel Function Form of Sommerfeld Integrals.

$$c = (1.02 + j\ 0.2)k_2 \ ,$$
$$d = 1.01\ k_{1_R} + j\ 0.99\ k_{1_I} \ ,$$
$$\theta = \tan^{-1}\left(\frac{\rho}{z + z'}\right) \ .$$

To avoid the near singularity as k_1 approaches k_2, the real part of d is not allowed to be less than 1.1 k_2. This contour provides rapid convergence except when z + z' is small, $|k_1\rho|$ is large, and k_{1_I}/k_{1_R} is small. There may then be many oscillations between c and d with little convergence. In such a case the contour in figure 15 is used where

$$e = k_1 + (-0.1 + j\ 0.2) \ ,$$
$$f = k_1 + (0.1 + j\ 0.2) \ .$$

The Hankel function form of the integrals provides rapid convergence for small z + z' including the case of z = z' = 0. For small ρ, however, the pole at $\lambda\rho = 0$ requires special treatment. In NEC the Hankel function form with the contour of figure 14 or 15 is used when ρ is greater than (z + z')/2 and the Bessel function form is used otherwise.

Integration along the contours is accomplished by adaptive interval-width Romberg integration. On the sections going to infinity, adaptive Romberg

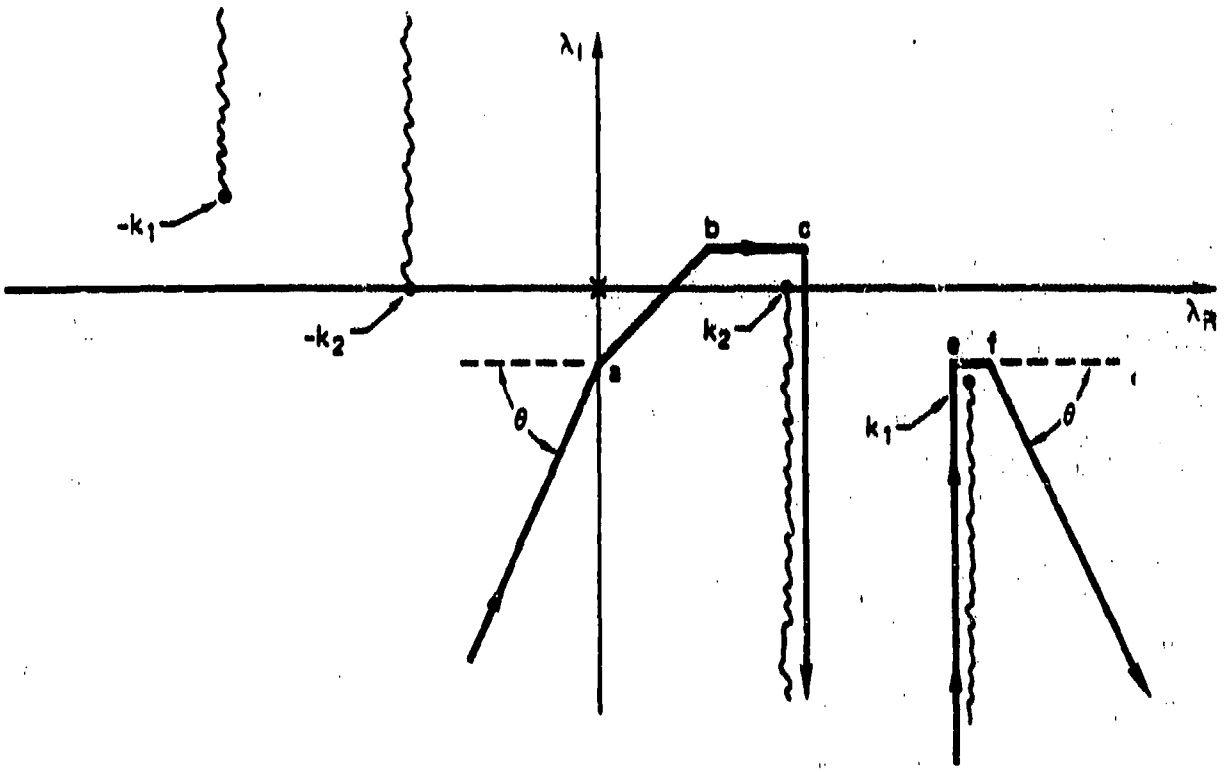


Figure 15. Contour for Hankel Function Form when Real Part k_1 is Large and Imaginary Part k_1 is Small.

integration is applied to successive subsections of length p, where p is the minimum of $0.2\pi/\rho$ or $0.2\pi/(z + z')$, and Shanks' nonlinear transformation (ref. 28) is applied to the sequence of partial sums to accelerate convergence. When ρ and $z + z'$ are both small, the integration interval, p, may be large since the exponential and Bessel functions change slowly and the remaining factors are easily integrated once λ becomes large. For the Bessel function form of the integrals the minimum for $R_1 = [\rho^2 + (z + z')^2]^{1/2}$ is limited only by the maximum number size for the computer. For the Hankel function form the minimum R_1 is about 10^{-5} wavelengths due to the pole at $\lambda\rho = 0$. Either ρ or $z + z'$ may be zero.

The numerical integration results for small R_1 were checked against results from a series approximation (ref. 25) and were in very close agreement. For larger values of R_1 the results from different integration contours were compared as a validation test. Results for the modified Sommerfeld integrals were also checked with normal integrals used in the code WFLLL2A. Earlier studies for the code WFLLL2A, which is capable of computing the field across

the interface, verified the continuity of the computed tangential E field across the interface (ref. 44).

The average time required to evaluate the integrals for a given ρ and $z + z'$ on a CDC 7600 computer is about 0.06 s. Thus about 15 s are required to fill the interpolation grid. Once the grid has been computed and stored, the time to fill an interaction matrix, using interpolation and the Norton formulas, is about four times that for free space.

3. THE IMAGE AND REFLECTION-COEFFICIENT METHODS

The use of a reflected image is a simple and fast way to model the effect of a ground plane. If the ground is perfectly conducting, the structure and its image are exactly equivalent to the structure over the ground. Since use of the image only doubles the time to compute the field, it is always used with a perfect ground. NEC also includes an image approximation for a finitely conducting ground in which the image fields are modified by the Fresnel plane-wave reflection coefficients. Although this is far from exact for a finite ground, it has been shown to provide useful results for structures that are not too near to the ground (refs. 21 and 22). When it can be used, the reflection coefficient method is about twice as fast as the Sommerfeld/Norton method and avoids the need of computing the interpolation grid.

Implementation of the image and reflection coefficient methods in the code is very simple. The Green's function for a perfectly conducting ground is the sum of the free-space Green's function of the source current element and the negative of the free-space Green's function of the image of the source reflected in the ground plane. For the electric field, with free-space Green's dyad $\overline{\overline{G}}\ (\vec{r},\vec{r}')$ defined in equation (1), the Green's dyad for a perfect ground is

$$\overline{\overline{G}}_{pg}(\vec{r},\vec{r}') = \overline{\overline{G}}\ (\vec{r},\vec{r}') + \overline{\overline{G}}_I\ (\vec{r},\vec{r}')\ , \tag{174}$$

where

$$\overline{\overline{G}}_I\ (\vec{r},\vec{r}') = -\overline{\overline{I}}_r \cdot \overline{\overline{G}}\ (\vec{r},\overline{\overline{I}}_r \cdot \vec{r}')\ , \tag{175}$$

$$\overline{\overline{I}}_r = \hat{x}\hat{x} + \hat{y}\hat{y} - \hat{z}\hat{z}\ .$$

$\overline{\overline{I}}_r$ is a dyad that produces a reflection in the $z = 0$ plane when used in a dot product. For the magnetic field with free-space Green's dyad

$$\overline{\overline{\Gamma}}\ (\vec{r},\vec{r}') = \overline{\overline{I}} \times \nabla'\ g\ (\vec{r},\vec{r}') \tag{176}$$

the Green's dyad over a perfect ground is

$$\bar{\bar{\Gamma}}_{pg} = \bar{\bar{\Gamma}}(\vec{r},\vec{r}') + \bar{\bar{\Gamma}}_I(\vec{r},\vec{r}') \tag{177}$$

$$\bar{\bar{\Gamma}}_I(\vec{r},\vec{r}') = -\bar{\bar{I}}_r \cdot \bar{\bar{\Gamma}}(\vec{r},\bar{\bar{I}}_r \cdot \vec{r}') \tag{178}$$

The reflection coefficient method for finitely conducting ground uses the image fields modified by the Fresnel reflection coefficients. The Fresnel reflection coefficients, which are strictly correct only for an infinite plane-wave field, depend on the polarization of the incident field with respect to the plane of incidence (i.e., the plane containing the normal to the ground and the vector in the direction of propagation of the wave). The two cases are illustrated in figure 16 where the wave with E in the plane of incidence is termed vertically polarized and E normal to the plane of incidence as horizontally polarized. The Fresnel reflection coefficient for vertically polarized waves is

$$R_V = \frac{\cos\Theta - Z_R\sqrt{1 - Z_R^2 \sin^2\Theta}}{\cos\Theta + Z_R\sqrt{1 - Z_R^2 \sin^2\Theta}}, \tag{179}$$

where


$$\cos\Theta = -\hat{k} \cdot \hat{z},$$

$$Z_R = \left(\frac{\epsilon_1}{\epsilon_o} - j\frac{\sigma_1}{\omega\epsilon_o}\right)^{-1/2}.$$


The reflected fields are then

$$\vec{E}_R^{v} = -R_V\left(\bar{\bar{I}}_R \cdot \vec{E}^{v}\right),$$

$$\vec{H}_R^{v} = R_V \vec{H}^{v}.$$

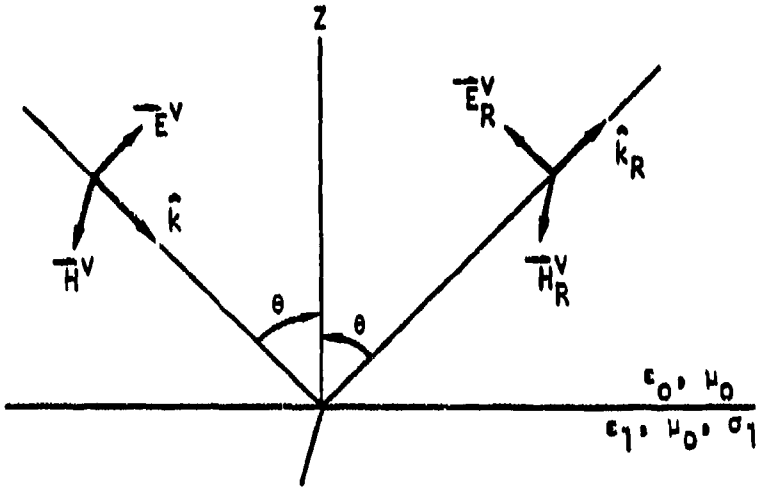

Reflection of Vertically Polarized Wave

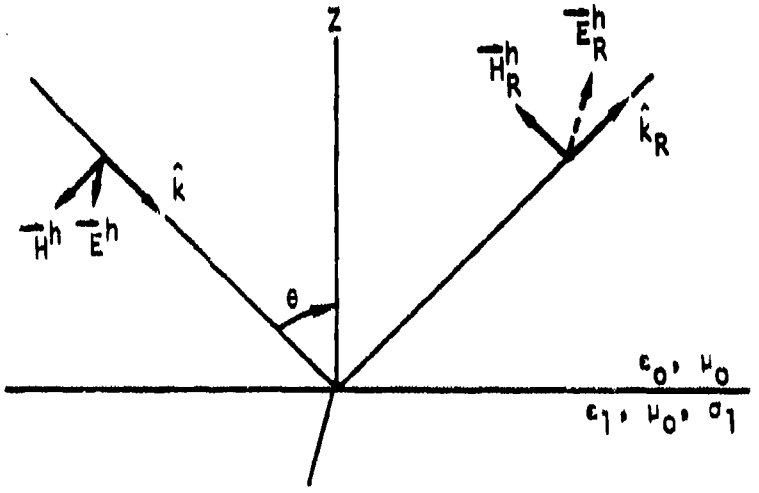

Reflection of Horizontally Polarized Wave

Figure 16. Plane-Wave Reflection at an Interface.

For horizontally polarized waves, the reflection coefficient is

$$R_H = \frac{-\left(Z_R \cos\Theta - \sqrt{1 - Z_R^2 \sin^2\Theta}\right)}{Z_R \cos\Theta + \sqrt{1 - Z_R^2 \sin^2\Theta}}, \tag{180}$$

and

$$\vec{E}_R^h = - R_H \vec{E}^h ,$$

$$\vec{H}_R^h = R_H \left(\bar{\bar{I}}_R \cdot \vec{H}^h\right) .$$

An arbitrarily polarized incident plane wave must be resolved into horizontal and vertical components to determine the reflected field. Thus, if $\hat{\beta}$ is the unit vector normal to the plane of incidence, the reflected field due to an incident field $\vec{E}$ is

$$\begin{aligned} \vec{E}_R &= R_H(\vec{E}_I \cdot \hat{\beta})\hat{\beta} + R_V \left[\vec{E}_I - (\vec{E}_I \cdot \hat{\beta})\hat{\beta}\right] \\ &= R_V \vec{E}_I + (R_H - R_V)(\vec{E}_I \cdot \hat{\beta})\hat{\beta} , \end{aligned} \tag{181}$$

where $\vec{E}_I$ is the incident field reflected in a perfectly conducting ground, or the field due to the image of the source. Use of the image field in equation (181) accounts for the changes in sign and vector direction of the incident field that were shown explicitly for the vertically and horizontally polarized cases. For the magnetic field,

$$\vec{H}_R = R_H \vec{H}_I + (R_V - R_H)(\vec{H}_I \cdot \hat{\beta})\hat{\beta} , \tag{182}$$

with $\vec{H}_I$ the field of the image of the source.

Applying the Fresnel reflection coefficients to the near fields, the electric field at $\vec{r}$ due to the image of a current element at $\vec{r}'$ can be written

$$\begin{aligned} \bar{\bar{G}}_R(\vec{r},\vec{r}') &= R_V \bar{\bar{G}}_I(\vec{r},\vec{r}') \\ &\quad + (R_H - R_V)\left[\bar{\bar{G}}_I(\vec{r},\vec{r}') \cdot \hat{\beta}\right]\hat{\beta} , \end{aligned} \tag{183}$$

where

$$\hat{\rho} = \vec{\rho}/|\vec{\rho}| \ ,$$

$$\vec{\rho} = (\vec{r} - \vec{r}') \times \hat{z} \ ,$$

and $\overline{\overline{G}}_I$ is the Green's function for the image of the source in a perfect ground as defined in equation (175). For magnetic field, the Green's dyad for the modified image is

$$\overline{\overline{\Gamma}}_R(\vec{r},\vec{r}') = R_H \overline{\overline{\Gamma}}_I(\vec{r},\vec{r}') + (R_V - R_H)\left[\overline{\overline{\Gamma}}_I(\vec{r},\vec{r}') \cdot \hat{\rho}\right]\hat{\rho} \ . \qquad (184)$$

The Green's functions for electric and magnetic fields over an imperfectly conducting ground, resulting from the reflection coefficient approximation are then

$$\overline{\overline{G}}_g(\vec{r},\vec{r}') = \overline{\overline{G}}(\vec{r},\vec{r}') + \overline{\overline{G}}_R(\vec{r},\vec{r}') \ , \qquad (185)$$

$$\overline{\overline{\Gamma}}_g(\vec{r},\vec{r}') = \overline{\overline{\Gamma}}(\vec{r},\vec{r}') + \overline{\overline{\Gamma}}_R(\vec{r},\vec{r}') \ . \qquad (186)$$

Use of the Green's function's $\overline{\overline{G}}_g$ and $\overline{\overline{\Gamma}}_g$ results in a straightforward extension of the EFIE and MFIE for structures over an imperfect ground.

NEC also includes a reflection coefficient approximation for a radial wire ground screen, as used by Miller and Deadrick (ref. 29). This is based on an approximation developed by Wait (ref. 30) for the surface impedance of the radial-wire ground screen on an imperfectly conducting ground, as the parallel combination of the surface impedance, ζ_1, of the ground plane

$$\zeta_1 = \left(\frac{j\mu_o\omega}{\sigma_1 + j\epsilon_1\omega}\right)^{1/2} \ ,$$

and an approximate surface impedance Z_g of the ground screen

$$Z_g(\rho) = \frac{j\mu_o\omega\rho}{N} \ln\left(\frac{\rho}{NC_o}\right) \ .$$

The ground screen impedance assumes a parallel wire grid having the wire spacing that the radial wires have at a distance ρ from the center. N is the number of radial wires in the screen, and C_o is the radius of the wires. The surface impedance of the ground screen on an imperfect ground is then

$$\zeta_e = \frac{\zeta_1 Z_g}{\zeta_1 + Z_g} .$$

From the definition of surface impedance,

$$E_{tangential} = \zeta_e H_{tangential}$$

at the surface. Using the fact that E and H in the incident wave are related by η the free-space impedance, reflection coefficients are derived as

$$R_H = \frac{\eta - \zeta_e \cos \Theta}{\eta + \zeta_e \cos \Theta} ,$$

and

$$R_V = \frac{\eta \cos \Theta - \zeta_e}{\eta \cos \Theta + \zeta_e} .$$

This is the form the Fresnel reflection coefficients take when the index of refraction is large compared to unity ($|Z_R|^2 << 1$). This condition is satisfied in most realistic problems; furthermore, the surface-impedance boundary condition is a valid approximation only when the refractive index of the ground is large compared to unity. The surface impedance is used in conjunction with the reflection coefficient method previously discussed to provide an approximate model of a radial-wire ground screen.

Due to the assumption of specular reflection, only the properties of the ground directly under a vertical antenna will affect its current distribution. At the origin of the radial-wire ground screen, the impedance is zero (Z_g is not allowed to be negative) so the impedance and current distribution of a vertical antenna at the origin will be the same as over a perfect conductor. The far fields, however, will demonstrate the effect of the screen as the specular point moves away from the origin. For antennas other than the vertical

antenna, it should be pointed out that the inherent polarization sensitivity of the screen (i.e., E parallel or perpendicular to the ground wires) has not been considered in this approximation. When limited accuracy can be accepted this ground screen approximation provides a large time saving over explicit modeling with the Sommerfeld/Norton method since the ground screen does not increase the number of unknowns in the matrix equation.

Section V
Modeling of Antennas

Previous sections have dealt with the problem of determining the current induced on a structure by an arbitrary excitation. We now consider some specific problems in modeling antennas and scatterers, including models for a voltage source on a wire, lumped and distributed loads, nonradiating networks, and transmission lines. Calculations of some observable quantities are also covered including input impedance, radiated field, and antenna gain.

1. SOURCE MODELING

The approach used in NEC is applicable to a number of electromagnetic analysis problems. For receiving antennas and EMP studies, the excitation is the field of an incident plane wave and the desired response is the induced current at one or more points on the structure. In scattering analysis the excitation is still an incident plane wave, but the desired response is the field radiated by the induced currents. In the case of a wire transmitting antenna, however, the excitation is generally a voltage source on the wire. The antenna source problem has received a considerable amount of attention in the literature. A rather thorough exposition on the appropriate source configuration for the linear dipole antenna has been given by King (ref. 31). The delta-function source, which may be visualized as an infinitesimally thin, circumferential belt of axially directed electric field [or, alternatively, as a frill of magnetic current at the antenna feed point (ref. 32)], is convenient mathematically, but of somewhat questionable physical realizability. Since the excitation can be specified only at discrete points in NEC, a delta-function source is not feasible.

A useful source model, however, is an electric field specified at a single match point. For a voltage source of strength V on segment i, the element in the excitation vector corresponding to the applied electric field at the center of segment i is set to

$$E_i = \frac{V}{\Delta_i} \quad , \tag{187}$$

where Δ_i is the length of segment i. The direction of E_i is toward the positive end of the voltage source so that it pushes charge in the same direction as the source. The field at other match points is set to zero.

The actual effective voltage is the line integral of the applied field along the wire. This cannot be determined beforehand since the field is known only at segment centers, but can be determined after the solution for current by integrating the scattered field produced by the current. For equal length segments in the vicinity of the source this field, which must be the negative of the applied field at every point on the wire, is nearly constant over segment i and drops sharply at the segment ends. This results in an actual voltage of approximately $\Delta_i E_i$ as assumed in equation (187). When the source segment and adjacent segments are not of equal length, however, the actual voltage, obtained by integrating the scattered field, may differ from the intended value.

Ideally, this source model applies a voltage V between the ends of the source segment. Hence, the antenna input admittance could be computed as the current at the segment ends or, in an unsymmetric case, the average of the current at the two ends, divided by the applied voltage. In practice the segment is sufficiently short so that the current variation over its length is small and the current at the center can be used rather than the ends. When segment lengths in the source region are unequal, the computed input admittance may be inaccurate due to the discrepancy between the actual and assumed voltages. Use of the actual voltage, obtained by integrating the near field, will generally give an accurate admittance although it will require additional effort for computation.

An alternate source model that is less sensitive to the equality of segment lengths in the source region is based on a discontinuity in the derivative of current. This source model is similar to one used by Andreasen and Harris (ref. 33), and its use in a program similar to NEC was reported by Adams, Poggio, and Miller (ref. 24). For this model, the source region is viewed as a biconical transmission line with feed point at the source location, as illustrated in figure 17. The voltage between a point at s and the symmetric point on the other side of the line is then related to the derivative of the current by the transmission line equation,

$$V(s) = - jZ_o \frac{\partial I(ks)}{\partial (ks)} \quad , \tag{188}$$

where Z_o is the characteristic impedance of the transmission line. The characteristic impedance of a biconical transmission line of half-angle Θ is

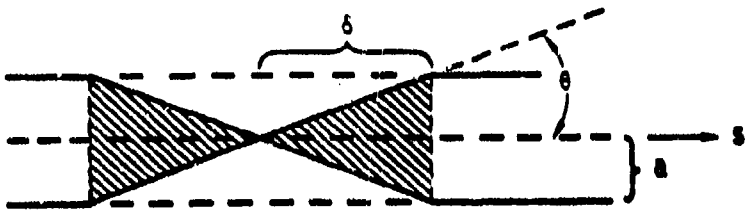


Figure 17. Biconical Transmission Line Model of Source Region.

$$Z_o = 120\ \ell n\left(\cot\frac{\Theta}{2}\right) ,$$

or for small angles,

$$Z_o \approx 120\ \ell n\left(\frac{2}{\Theta}\right) . \tag{189}$$

For a source on a wire, however, the proper choice for δ in figure 17, defining the angle Θ, is unclear. Adams at al. (ref. 24) used an average value of Z_o obtained by averaging equation (189) for δ ranging from zero to d as

$$Z_{avg} = \frac{1}{d}\int_o^d 120\ \ell n\left(\frac{2\delta}{a}\right) d\delta$$

$$= 120\left[\ell n\left(\frac{2d}{a}\right) - 1\right] ,$$

where d is set equal to the distance from the source location at the segment end to the match point at the segment center. The voltage across the line is then

$$V(s) = -\,j\ 120\left[\ell n\left(\frac{2d}{a}\right) - 1\right]\frac{\partial I(ks)}{\partial(ks)} .$$

Allowing for a current unsymmetric about the source, the voltage V_o of a source at s_o is related to a discontinuity in current derivative as

$$\lim_{\varepsilon\to o}\left[\left.\frac{\partial I(ks)}{\partial(ks)}\right|_{s = s_o + \varepsilon} - \left.\frac{\partial I(ks)}{\partial(ks)}\right|_{s = s_o - \varepsilon}\right] =$$

$$\frac{-jV_o}{60\left[\ell n\left(\frac{2d}{a}\right) - 1\right]} . \tag{190}$$

This discontinuity in current derivative is introduced into NEC by modifying the current expansion on the wire. The normal expansion for N_s wire segments is

$$I(s) = \sum_{j=1}^{N_s} \alpha_j \, f_j(s) \ ,$$

where the basis functions, f_j, are defined in section III-1 such that $I(s)$ has continuous value and derivative along wires, and satisfies Kirchoff's law and a condition on charge density at junctions.

For a current-slope-discontinuity source at the first end of segment ℓ, the current expansion is modified to

$$I(s) = \sum_{j=1}^{N_s} \alpha_j \, f_j(s) + \beta_\ell \, f_\ell^*(s) \ , \qquad (191)$$

where f_ℓ^* is a basis function for segment ℓ, as defined in section III-1, but computed as if the first end of segment ℓ were a free end and the segment radius were zero. Hence, f_ℓ^* goes to zero with nonzero derivative at the source location.

If f_ℓ^* on segment ℓ is

$$f_\ell^*(s) = A_\ell^* + B_\ell^* \sin k(s - s_\ell) + C_\ell^* \cos k(s - s_\ell)$$

$$\times |s - s_\ell| < \Delta_\ell/2 \ ,$$

then

$$\frac{\partial}{\partial(ks)} f_\ell^*(s) \Big|_{s = s_\ell - \Delta_\ell/2} = B_\ell^* \cos(k\Delta_\ell/2) + C_\ell^* \sin(k\Delta_\ell/2) \ .$$

Since the sum of the normal basis functions has continuous value and derivative at $s = s_\ell - \Delta_\ell/2$, the current in equation (191) has a discontinuity in derivative of

$$\lim_{\varepsilon \to o} \left\{ \frac{\partial}{\partial(ks)} I(s) \Big|_{s = s_\ell - \Delta_\ell/2 + \varepsilon} - \frac{\partial}{\partial(ks)} I(s) \Big|_{s = s_\ell - \Delta_\ell/2 - \varepsilon} \right\} =$$

$$\beta_\ell \left\{ B_\ell^* \cos(k\Delta_\ell/2) + C_\ell^* \sin(k\Delta_\ell/2) \right\} .$$

Hence, from equation (190), a source voltage of V_o requires a value of β_ℓ in the current expansion of

$$\beta_\ell = \frac{-jV_o}{60}\left\{\left[\ell n\left(\frac{\Delta_\ell}{a_\ell}\right) - 1\right]\left[B_\ell^* \cos(k\Delta_\ell/2) + C_\ell^* \sin(k\Delta_\ell/2)\right]\right\}^{-1} . \tag{192}$$

The linear system for the current expansion constants, obtained by substituting equation (191) for f in equation (18), is

$$\sum_{j=1}^{N_s} \alpha_j \langle w_i, Lf_j \rangle = \langle w_i, e \rangle - \beta_\ell \langle w_i, f_\ell^* \rangle . \tag{193}$$

$$i = 1, \ldots N_s$$

In matrix notation, corresponding to equation (19),

$$[G]\,[A] = [E] + \beta_\ell\,[F] , \tag{194}$$

where F_i is the excitation for segment or patch equation number i due to the field of f_ℓ^*, and E_i is the excitation for segment or patch equation number i from other sources (if there are any). The interaction matrix G is independent of this source as it is of other sources. The solution for the expansion coefficients is then

$$[A] = [G^{-1}]\left\{[E] + \beta_\ell\,[F]\right\} ,$$

where A supplies the coefficients α_j in equation (191) to determine the current. This method is easily extended to several sources. The modified basis function f_ℓ^* appears to introduce an asymmetry into the current, but this is not the case since the other basis function amplitudes are free to adjust accordingly.

The current-slope-discontinuity source results in an effective applied field that is much more localized in the source region than that of the constant-field source defined by equation (187). The difference is shown in near-field plots for the two source models in figure 18, taken from Adams

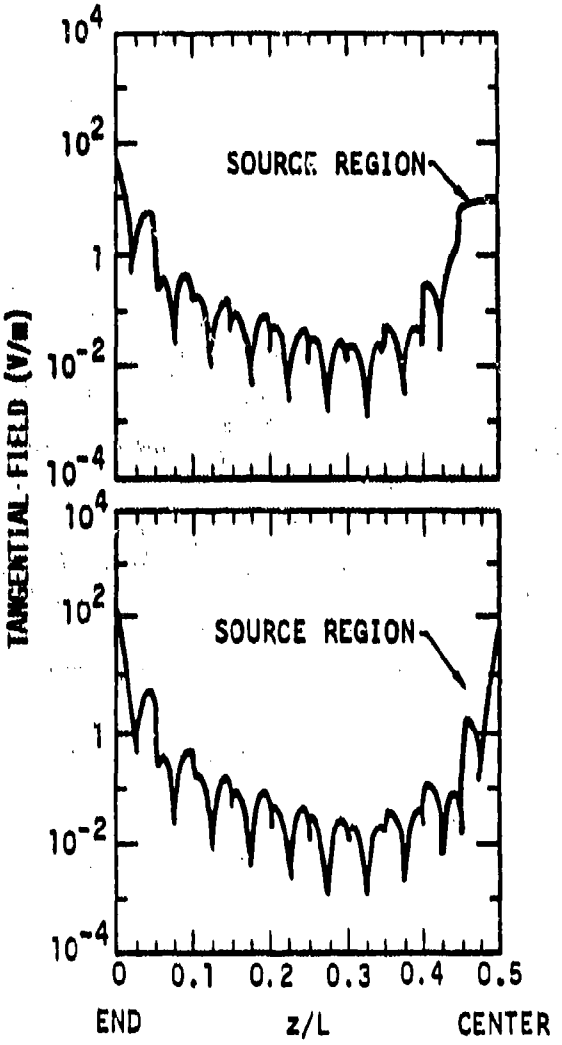


Figure 18. Field Plots for a Linear Dipole, Ω=15.

et al. (ref. 24). The near fields are for a half wavelength dipole antenna with Ω = 15 [Ω = 2ℓn(L/a), L = length, a = radius] and with 10 segments on half of the antenna covered by the plots. The constant-field source is seen to result in a nearly rectangular field distribution in the source region while the field of the slope-discontinuity source approaches a delta function. The integrals of these two source-field distributions yield approximately the same voltages, however.

With the slope-discontinuity-source model, the input admittance is the ratio of the current at the segment end, where the source is located, to the source voltage. Adams et al. also present results showing the effect on admittance of varying the source-segment length relative to the lengths of adjacent segments, showing that the slope-discontinuity source is much less sensitive to segment length than is the constant-field source. The two segments on opposite sides of the source must have equal lengths and radii, however. For very short segment lengths, the slope-discontinuity model may break down although, as with the constant-field source, the correct admittance can be obtained by integrating the near field to obtain the source voltage.

2. NONRADIATING NETWORKS

Antennas often include transmission lines, lumped circuit networks, or a combination of both connecting between different parts or elements. When the currents on transmission lines or at network ports are balanced, the resulting fields cancel and can often be neglected, greatly simplifying the

modeling problem. The solution procedure used in NEC is to compute a driving-point-interaction matrix from the complete segment-interaction matrix. The driving-point matrix relates the voltages and currents at network connection points as required by the electromagnetic interactions. The driving-point-interaction equations are then solved together with the network or transmission line equations to obtain the induced currents and voltages. In this way the larger segment-interaction matrix is not changed by addition or modification of networks or transmission lines.

The solution described below assumes an electromagnetic interaction matrix equation of the form,

$$[G]\,[I] = -[E]\ , \tag{195}$$

where E_i is the exciting electric field on wire segment i and I_i is the current at the center of segment i. In NEC the interaction equation has the form,

$$[G]\,[A] = -[E]\ ,$$

where A_i is the amplitude of the i^{th} basis function f_i in the current expansion,

$$I(s) = \sum_{i=1}^{N_s} A_i\, f_i(s)\ .$$

The same solution technique can be used, however, by computing I from A whenever I is needed. This must be done in computing the elements of the inverse of G, G^{-1}_{ij}, which below represent the current on segment i due to a unit field on segment j.

A model consisting of N_s segments will be assumed with a general M-port network connected to segments 1 through M. The network is described by the admittance equations,

$$\sum_{j=1}^{M} Y_{ij}\, V_j = I^t_i \qquad i=1,\ \ldots,\ M\ , \tag{196}$$

where V_i and I^t_i are the voltage and current at port i, with reference directions as shown in figure 19.

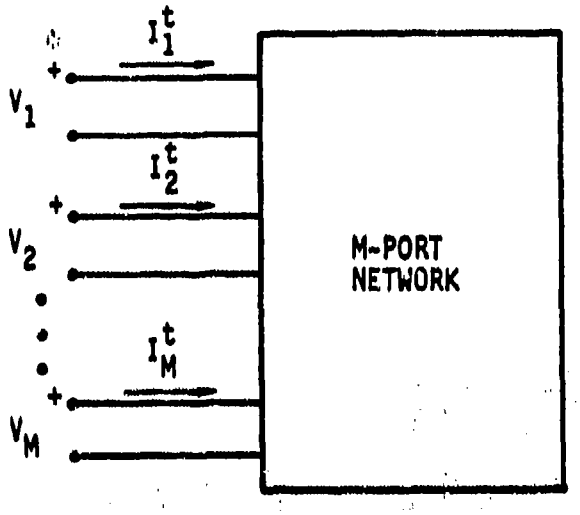


Figure 19. Voltage and current Reference Directions at Network Ports.

The connection of a network port to a segment is illustrated in figure 20. The segment is broken, and the port is connected so that

$$I_i^t = - I_i \ , \tag{197}$$

where I_i is the segment current. Figure 21 shows a voltage source of strength V_i connected across the network port at segment i. In this case,

$$I_i^t = I_i^s - I_i \ , \tag{198}$$

In either case, the port voltage may be related to the applied field on the segment by the constant-field voltage source model of equation (187).

We will assume that segments 1 through M_1 are connected to network ports without voltage sources, and segments $M_1 + 1$ through M are connected to network ports with voltage sources. The remaining segments have no network

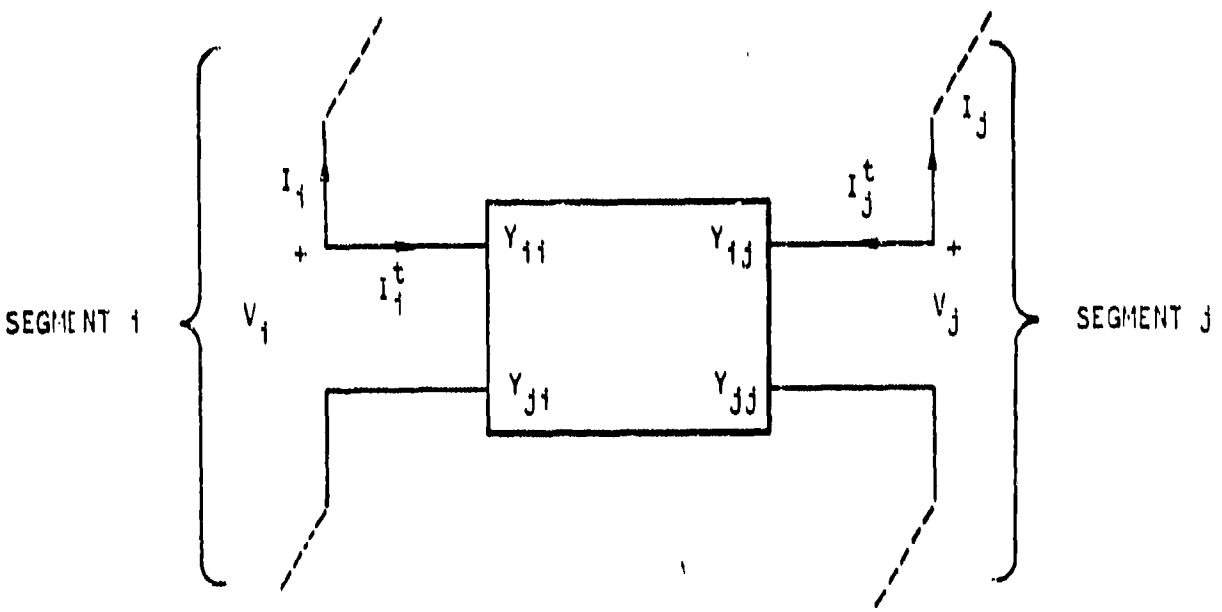


Figure 20. Network Connection to Segments.

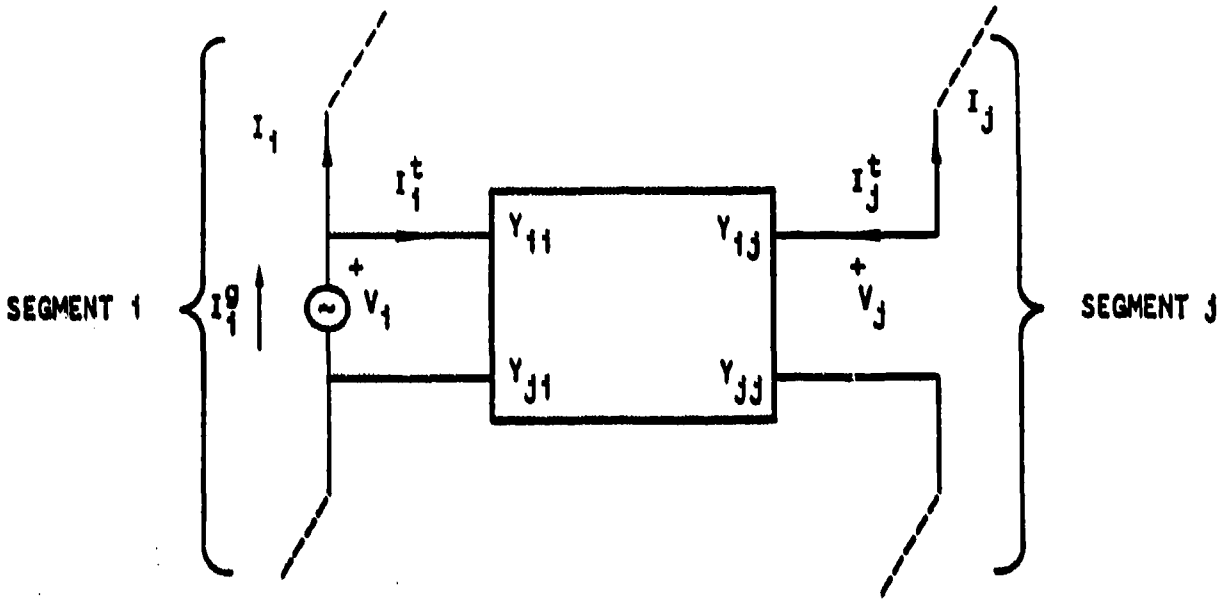


Figure 21. Network Port and Voltage Source Connected to a Segment.

connections but may have voltage sources. In addition all of the segments may be excited by an incident field represented by E_i^I on segment i. The total field on segment i is then

$$E_i = \frac{V_i}{\Delta_i} + E_i^I ,$$

where V_i is a gap voltage, due either to a network port or voltage source, and Δ_i is the segment length.

Equation (195) may be solved for current as

$$I_i = - \sum_{j=1}^{N_s} G_{ij}^{-1} E_j \qquad i=1, \ldots, N_s , \tag{199}$$

where G_{ij}^{-1} is the $(i,j)^{th}$ element of the inverse of matrix G. Before evaluating equation (199), however, the unknown port voltages, V_i, for $i = 1,\ldots,M_1$ must be determined. Hence, equation (199) is written with all known quantities on the right-hand side as

$$\sum_{j=1}^{M_1} G_{ij}^{-1} E_j^P + I_i = B_i \qquad i=1, \ldots, M_1 , \tag{200}$$

where

$$E_j^P = \frac{V_i}{\Delta_j} ,$$

and

$$B_i = - \sum_{j=1}^{M_1} G_{ij}^{-1} E_j^I - \sum_{j=M_1+1}^{N_s} G_{ij}^{-1} E_j .$$

Similarly, the network equations (196) are written using equation (197) as

$$\sum_{j=1}^{M_1} Y'_{ij} E_j^P + I_i = C_i \qquad i=1, \ldots, M_1 , \tag{201}$$

where

$$Y'_{ij} = \Delta_j Y_{ij} ,$$

$$C_i = - \sum_{j=M_1+1}^{M} Y_{ij} V_j .$$

The current is then eliminated between equations (200) and (201) to yield

$$\sum_{j=1}^{M_1} \left(G_{ij}^{-1} - Y'_{ij} \right) E_j^P = B_i - C_i \qquad i=1, \ldots, M_1 . \tag{202}$$

The solution procedure is then to solve equation (202) for E_j^P for $j = 1,\ldots,M_1$. Then, with the complete excitation vector determined, use equation (199) to determine I_i for $i = 1,\ldots,N_s$. Finally, the remaining network equations with equation (198) are used to compute the generator currents as

$$I_i^S = \sum_{j=1}^{M} Y_{ij} V_j + I_i \qquad i=M_1+1, \ldots M . \tag{203}$$

The currents I_i^S determine the input admittances seen by the sources.

In NEC the general M-port network used here is restricted to multiple two-port networks, each connecting a pair of segments.

3. TRANSMISSION LINE MODELING

Transmission lines interconnecting parts of an antenna may be modeled either explicitly by including the transmission line wires in the thin-wire model, or implicitly by the method described in the preceding section for nonradiating networks. For an implicit model, the short-circuit-admittance parameters of the transmission line viewed as a two-port network are

$$Y_{11} = Y_{22} = -j\, Y_o \cot(k\ell) ,$$

$$Y_{12} = Y_{21} = j\, Y_o \csc(k\ell) ,$$

where Y_o is the characteristic admittance of the line, k is the wave number $(2\pi/\lambda)$, and ℓ is the length of the line. If a separate admittance element is connected across the end of a transmission line, its admittance is added to the self-admittance of that network port.

The implicit model is limited, however, in that it neglects interaction between the transmission line and the antenna and its environment. This approximation is justified if the currents in the line are balanced, i.e., in a log periodic dipole antenna, and in general if the transmission line lies in an electric symmetry plane. The balance can be upset, however, if the transmission line is connected to an unbalanced load or by unsymmetric interactions. If the unbalance is significant, the transmission line can be modeled explicitly by including the wires in the thin-wire model. The explicit model is completely general, and yields accurate results since the sine, cosine, and constant current expansion in NEC is a good representation of the sinusoidal transmission line currents. The accuracy is demonstrated in figure 22 for transmission lines terminated in short circuit, open circuit, and matched loads.

The explicit transmission line model is, of course, less efficient in computer time and storage because of the additional segments required. In cases where the physical line presence does have a significant effect on the results, the effect may be modeled by explicitly modeling a single conductor of the line while using the implicit model to represent the balanced current component.

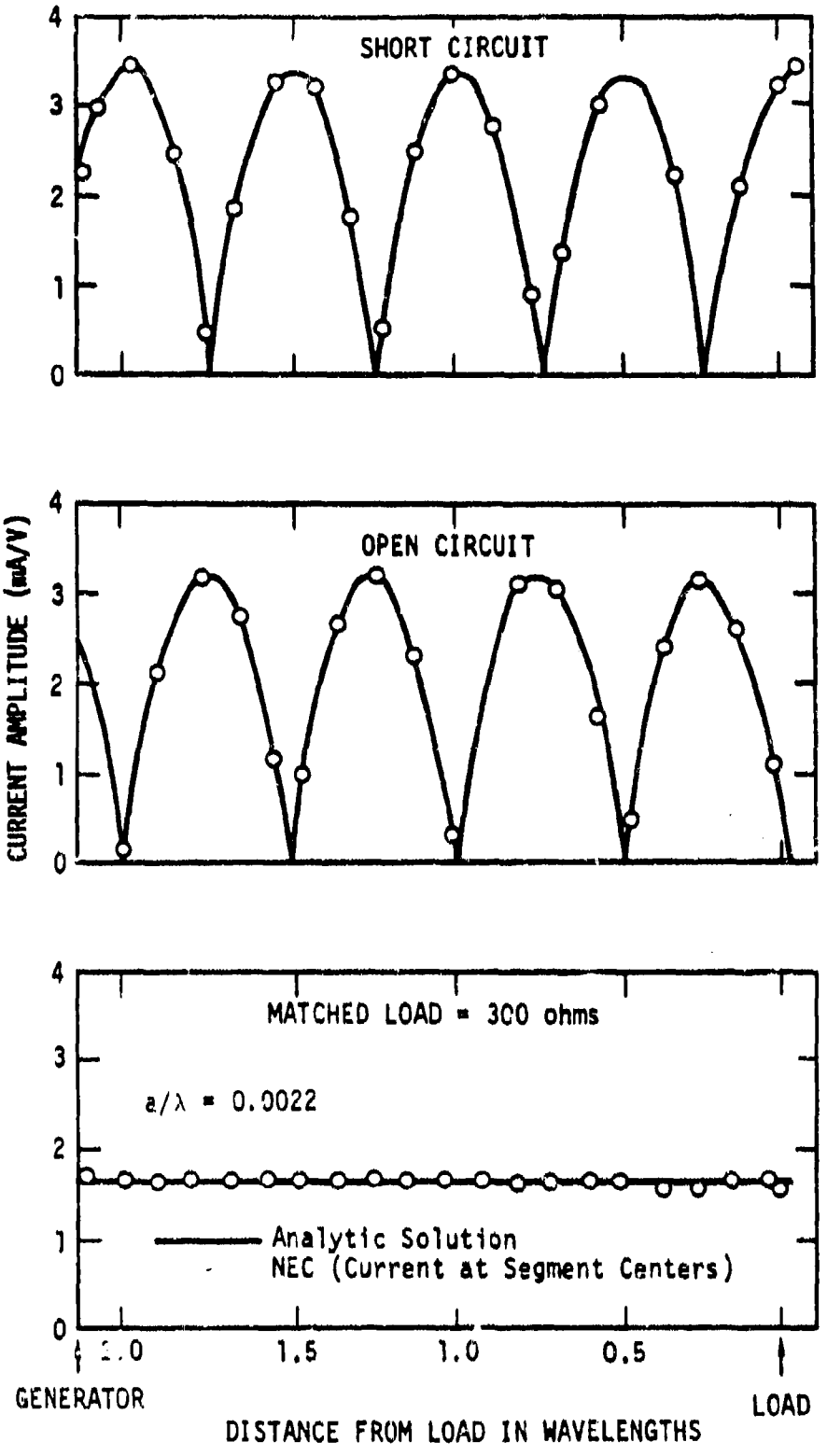


Figure 22. Current Distribution on a Two-Wire Transmission Line from NEC Compared with the Ideal Transmission Line Solution.

4. LUMPED OR DISTRIBUTED LOADING

Thus far, we have assumed that all structures to be modeled are perfect electric conductors. The EFIE is easily extended to imperfect conductors by modifying the boundary condition from equation (4) to

$$\hat{n}(\vec{r}) \times \left[\vec{E}^{L}(\vec{r}) + \vec{E}^{I}(\vec{r})\right] = Z_s(\vec{r})\left[\hat{n}(\vec{r}) \times \vec{J}_s(\vec{r})\right] ,$$

where $Z_s(\vec{r})$ is the surface impedance at $\vec{r}$ on the conducting surface. For a wire, the boundary condition is

$$\hat{s} \cdot \left[\vec{E}^{s}(\vec{r}) + \vec{E}^{I}(\vec{r})\right] = Z_w(s)\ I(s) ,$$

with $\vec{r}$ and $\hat{s}$ the position vector and tangent vector at s on the wire and $Z_w(s)$ the impedance per-unit-length at s. The matrix equation can then be written,

$$\sum_{j=1}^{N_s} G_{ij}\ \alpha_j = -E_i + \frac{Z_i}{\Delta_i} I_i \qquad i=1, \ldots, N_s , \tag{204}$$

where

α_j = amplitude of basis function j,

E_i = the incident field on segment i,

I_i = current at the center of segment i,

Z_i = total impedance of segment i,

Δ_i = length of segment i.

The impedance term can be viewed as a constant field model of a voltage source, as described in section V-1, where the voltage is proportional to current. It is assumed that the current is essentially constant, with value I_i, over the length of the segment, which is a reasonable assumption for the electrically short segments used in the integral equation solution.

The impedance term can be combined with the matrix by expressing I_i in terms of the α_j as

$$I_i = \sum_{j=1}^{N_s} \alpha_j \left(A_j^i + C_j^i \right) ,$$

where A_j^i and C_j^i are the coefficients of the constant and cosine terms, respectively, in the section of basis function j extending onto segment i. If basis function j does not extend onto segment i, then A_j^i and C_j^i are zero. The matrix equation modified by loading is then

$$\sum_{j=1}^{N_s} G'_{ij} \alpha_j = - E_i \qquad i=1, \ldots, N_s , \tag{205}$$

where

$$G'_{ij} = G_{ij} - \frac{Z_i}{\Delta_i} \left(A_j^i + C_j^i \right) . \tag{206}$$

For a lumped circuit element, Z_i is computed from the circuit equations. For a distributed impedance, Z_i represents the impedance of a length Δ_i of wire, which in the case of a round wire of finite conductivity is given by

$$Z_i = \frac{j\Delta_i}{a_i} \sqrt{\frac{\omega\mu}{2\pi\sigma}} \left[\frac{\mathrm{Ber}(q) + j\ \mathrm{Bei}(q)}{\mathrm{Ber}'(q) + j\ \mathrm{Bei}'(q)} \right] ,$$

where

$q = (\omega\mu\sigma)^{1/2}\ a_i$,

a_i = wire radius,

σ = wire conductivity,

Ber, Bei = Kelvin functions.

This expression takes account of the limited penetration of the field into an imperfect conductor.

5. RADIATED FIELD CALCULATION

The radiated field of an antenna or reradiated field of a scatterer can be computed from the induced current by using a simplified form of equation (1) valid far from the current distribution. The far-field approximation, valid when the distance from the current distribution to the observation

point is large compared to both the wavelength and the dimensions of the current distribution, treats the distance $|\vec{r} - \vec{r}'|$ as constant within the integral except in the phase term, $\exp(-jk|\vec{r} - \vec{r}'|)$. For a structure consisting of a wire portion with contour L and current distribution $\vec{I}(s)$, and a surface portion S with current $\vec{J}_s(\vec{r})$, the far-zone field is

$$\vec{E}(\vec{r}_o) = \frac{jk\eta}{4\pi} \frac{\exp(-jkr_o)}{r_o} \times \left\{ \int_L \left[\left(\hat{k} \cdot \vec{I}(s) \right) \hat{k} - \vec{I}(s) \right] \exp(j\vec{k}\cdot\vec{r}) ds + \int_S \left[\left(\hat{k} \cdot \vec{J}_s(\vec{r}) \right) \hat{k} - \vec{J}_s(\vec{r}) \right] \exp(j\vec{k}\cdot\vec{r}) dA \right\} , \quad (207)$$

where $\vec{r}_o$ is the position of the observation point $\hat{k} = \vec{r}_o / |\vec{r}_o|$, $k = 2\pi/\lambda$, and $\vec{k} = k\hat{k}$. The first integral can be evaluated in closed form over each straight wire segment for the constant, sine, and cosine components of the basis functions, and reduces to a summation over the wire segments. With the surface current on each patch represented by a delta function at the patch center, the second integral becomes a summation over the patches.

The radiation pattern of an antenna can be computed by exciting the antenna with a voltage source and using equation (207) to compute the radiated field for a set of directions in space. Alternatively, since the transmitting and receiving patterns are required by reciprocity to be the same, the pattern can be determined by exciting the antenna with plane-waves incident from the same directions and computing the currents at the source point. The solution procedure in NEC does not guarantee reciprocity, however, since the different expansion and weighting functions may produce asymmetry in the matrix. Large differences between the receiving and transmitting patterns or a significant lack of reciprocity in bistatic scattering are indications of inaccuracy in the solution, possibly from too coarse a segmentation of the wires or surfaces.

The power gain of an antenna in the direction specified by the spherical coordinates (Θ,ϕ) is defined as

$$G_p(\Theta,\phi) = 4\pi \frac{P(\Theta,\phi)}{P_{in}} ,$$

where $P(\Theta,\phi)$ is the power radiated per unit solid angle in the direction (Θ,ϕ), and P_{in} is the total power accepted by the antenna from the source. P_{in} is computed from the voltage and current at the source as

$$P_{in} = \frac{1}{2} \mathrm{Re}(VI^*) ,$$

and

$$P(\Theta,\phi) = \frac{1}{2} R^2 \mathrm{Re}(\vec{E} \times \vec{H}^*) = \frac{R^2}{2\eta} (\vec{E} \cdot \vec{E}^*) .$$

$\vec{E}$ is obtained from equation (207) with $\vec{r}_o$ in the direction (Θ,ϕ), and $r_o = R$. Directive gain is similarly defined as

$$G_d(\Theta,\phi) = 4\pi \frac{P(\Theta,\phi)}{P_{rad}} ,$$

where P_{rad} is the total power radiated by the antenna,

$$P_{rad} = P_{in} - P_{loss} ,$$

and P_{loss} is the total ohmic loss in the antenna.

The radiated field of an antenna over ground is modified by the ground interaction, as discussed in section IV. When the range from the antenna to the observer, R, approaches infinity, the Sommerfeld formulation for the field reduces exactly to a direct field determined by equation (207) and a field from the image modified by the Fresnel reflection coefficient. In some cases, however, when the observer is at a finite distance from the antenna, the field components proportional to $1/R^2$ may be significant. While the $1/R$ terms are generally much larger than the $1/R^2$ terms at practical observation distances from an antenna, the $1/R$ terms vanish at grazing angles over an imperfect ground plane leaving only the $1/R^2$ terms, dominated by a term known as the ground wave. The ground wave is, of course, included in Sommerfeld's expressions. Norton's asymptotic approximations (ref. 26) are used, however, since they are more easily evaluated and give adequate accuracy. Norton's formulas, which are in Part II of this manual under subroutine GWAVE, are valid for R greater than a few wavelengths and to second order in k_1^2/k_2^2. When the ground wave is included, the field has radial as well as transverse components.

6. ANTENNA COUPLING

Coupling between antennas is often a parameter of interest, especially when a receiving system must be protected from a nearby transmitter. Maximum power transfer between antennas occurs when the source impedance and receiver load impedance are conjugate-matched to their antennas. Determination of this condition is complicated by the antenna interaction, however, since the input impedance of one antenna depends on the load connected to the other antenna. NEC-2 includes an algorithm for determining the matched loads and maximum coupling by a method that was added to special versions of the previous codes NEC-1 and AMP (ref. 34).

The coupling problem can be solved in closed form by the Linville method (ref. 35), a technique used in rf amplifier design. The first step is to determine the two-port admittance parameters for the coupled antennas by exciting each antenna with the other short-circuited and computing the self and mutual admittances from the currents computed by NEC. The maximum coupling is then

$$G_{MAX} = \frac{1}{L}\left[1 - (1-L^2)^{1/2}\right] ,$$

where

$$L = \frac{|Y_{12}Y_{21}|}{2\mathrm{Re}(Y_{11})\ \mathrm{Re}(Y_{22}) - \mathrm{Re}(Y_{12}Y_{21})} .$$

The matched load admittance on antenna 2 for maximum coupling is

$$Y_L = \left[\frac{1-\rho}{1+\rho} + 1\right] \mathrm{Re}(Y_{22}) - Y_{22} ,$$

where

$$\rho = \frac{G_{MAX}(Y_{12}Y_{21})^*}{|Y_{12}Y_{21}|} ,$$

and the corresponding input admittance of antenna 1 is

$$Y_{IN} = Y_{11} - \frac{Y_{21}Y_{12}}{Y_L + Y_{22}} .$$

References

1. Miller, E. K. et al., *Final Technical Report on the Log-Periodic Scattering Array Program*, MBAssociates Report No. MB-R-70/105, Contract No. F04701-68-C-0188, 1970.
2. *RCS Computer Program BRACT, Log-Periodic Scattering Array Program - II*, MBAssociates Report No. MB-R-69/46, Contract No. F04701-68-C-0188, 1969.
3. *Antenna Modeling Program - Composite User's Manual*, MBAssociates Report No. MB-R-74/46, 1974.
4. *Antenna Modeling Program - Engineering Manual*, MBAssociates Report No. MB-R-74/62, 1974.
5. *Antenna Modeling Program - Systems Manual*, MBAssociates Report No. MB-R-74/62, 1974.
6. *Antenna Modeling Program - Supplementary Computer Program Manual (AMP2)*, MBAssociates Report No. MB-R-75/4, 1975.
7. *Numerical Electromagnetic Code (NEC-1) Part III: NEC User's Guide*, Lawrence Livermore Laboratory, 1977.
8. *Numerical Electromagnetic Code (NEC-1) Part II: NEC Program Description - Code*, Lawrence Livermore Laboratory, 1977.
9. Albertsen, N. C., Hansen, J. E., and Jensen, N. E., *Computation of Spacecraft Antenna Radiation Patterns*, The Technical University of Denmark, Lyngby, Denmark, June 1972.
10. Poggio, A. J. and Miller, E. K., "Integral Equation Solutions of Three-Dimensional Scattering Problems," Chapt. IV in *Computer Techniques for Electromagnetics*, edited by R. Mittra, Pergamon Press, New York, 1973.
11. Poggio, A. J. and Adams, R. W., *Approximations for Terms Related to the Kernel in Thin-Wire Integral Equations*, UCRL-51985, Lawrence Livermore Laboratory, CA, December 19, 1975.
12. Van Bladel, J., *Electromagnetic Fields*, McGraw-Hill, New York, 1964.
13. Harrington, R. F., *Field Computation by Moment Methods*, MacMillan, New York, 1968.
14. Yeh, Y. S. and Mei, K. K., "Theory of Conical Equiangular Spiral Antennas," *Part I - Numerical Techniques, IEEE Trans. Ant. and Prop., AP-15*, 1967, p. 634.

15. Neureuther, A. R. et al., "A Comparison of Numerical Methods for Thin Wire Antennas," *Presented at the 1968 Fall URSI Meeting*, Dept. of Electrical Engineering and Computer Sciences, University of California, Berkeley, 1968.

16. Miller, E. K. et al., *An Evaluation of Computer Programs Using Integral Equations for the Electromagnetic Analysis of Thin Wire Structures*, UCRL-75566, Lawrence Livermore Laboratory, CA, March 1974.

17. Wu, T. T. and King, R. W. P., "The Tapered Antenna and Its Application to the Junction Problem for Thin Wires," *IEEE Trans. Ant. and Prop.*, *AP-24*, No. 1, pp. 42-45, January 1976.

18. Poggio, A. J., *Integral Representations for Fields Due to Sources on Open Surfaces with Applications to End Caps*, UCRL-51723, Lawrence Livermore Laboratory, CA, December 16, 1974.

19. Ralston, A., *A First Course in Numerical Analysis*, McGraw-Hill, New York 1965.

20. Sommerfeld, A., *Partial Differential Equations in Physics*, Academic Press, New York, 1964.

21. Burke, G. J., Miller, E. K., and Poggio, A. J., *Dielectric Ground Interactions with a Log-Periodic Antenna*, Final Report, ECOM-0285-F, U.S. Army Electronics Command, Fort Monmouth, N.J., 1971 (contract DAAB07-70-C-0285).

22. Miller, E. K., Poggio, A. J., Burke, G. J., and Selden, E. S., *Analysis of Wire Antennas in the Presence of a Conducting Half Space: Part I. The Vertical Antenna in Free Space. Part II. The Horizontal Antenna in Free Space*, UCRL-73217, Lawrence Livermore Laboratory, CA, 1972. (Also in *Canadian J. Phys.*)

23. Lager, D. L. and Lytle, R. J., *Fortran Subroutines for the Numerical Evaluation of Sommerfeld Integrals Unter Anderem*, UCRL-51821, Lawrence Livermore Laboratory, CA, May 21, 1975.

24. Adams, R. W., Poggio, A. J., and Miller, E. K., *Study of a New Antenna Source Model*, UCRL-51693, Lawrence Livermore Laboratory, CA, October 28, 1974.

25. Brittingham, J. N., Miller, E. K., and Okada, J. T., *SOMINT: An Improved Model for Studying Conducting Objects Near Lossy Half-Spaces*, UCRL-52423, Lawrence Livermore Laboratory, CA, February 24, 1978.

26. Norton, K. A., "The Propagation of Radio Waves Over the Surface of the Earth and in the Upper Atmosphere," *Proceedings of the Institute of Radio Engineers*, Vol. 26, No. 9, Sept. 1937.

27. Lytle, R. J. and Lager, D. L., *Numerical Evaluation of Sommerfeld Integrals*, UCRL-51688, Lawrence Livermore Laboratory, CA, October 23, 1974.

28. Shanks, D., "Non-Linear Transformations of Divergent and Slowly Convergent Sequences," *J. Math. Phys.*, 24, 1 (1955).

29. Miller, E. K. and Deadrick, F. J., *Computer Evaluation of Loran-C Antennas*, UCRL-51464, Lawrence Livermore Laboratory, CA, Oct. 17, 1973.

30. Wait, J. R., "Characteristics of Antennas Over Lossy Earth," *Antenna Theory, Part II*, R. E. Collin and F. J. Zucker, Eds., McGraw-Hill, New York, pp. 386-437, 1969.

31. King, R. W., *The Theory of Linear Antennas*, Harvard Univ. Press, Cambridge, Massachusetts, 1956.

32. Otto, D. V., "The Admittance of Cylindrical Antennas Driven from a Coaxial Line," *Radio Sci.*, Vol. 2, No. 9, pp. 1031-1042, 1967.

33. Andreasen, M. G. and Harris, F. G., *Analyses of Wire Antennas of Arbitrary Configuration by Precise Theoretical Numerical Techniques*, Tech. Rept. ECOM 0631-F, Granger Associates, Palo Alto, California, Contract DAAB07-67-C-0631, 1968.

34. Logan, J. C. and Rockway, J. W., *Computer Techniques for Shipboard Topside Antenna Modeling Below UHF*, TN-3284, Naval Electronics Laboratory Center, November 17, 1976.

35. Rubin, D., *The Linville Method of High Frequency Transistor Amplifier Design*, Naval Weapons Center, Research Department, NWCCL TP 845, Corona Laboratories, Corona, California, March 1969.

36. Burke, G. J. and Poggio, A. J., *Computer Analysis of the Twin-Whip Antenna*, UCRL-52080, Lawrence Livermore Laboratory, CA, June 1, 1976.

37. Burke, G. J. and Poggio, A. J., *Computer Analysis of the Bottom-Fed Fan Antenna*, UCRL-52109 Lawrence Livermore Laboratory, CA, August 19, 1976.

38. Deadrick, F. J., Burke, G. J., and Poggio, A. J., *Computer Analysis of the Trussed-Whip and Discone-Cage Antennas*, UCRL-52201, January 6, 1977.

RAC/gw


UCID- 18834

NUMERICAL ELECTROMAGNETICS CODE (NEC) - METHOD OF MOMENTS

PART II: PROGRAM DESCRIPTION - CODE

G. J. Burke
A. J. Poggio

January 1981

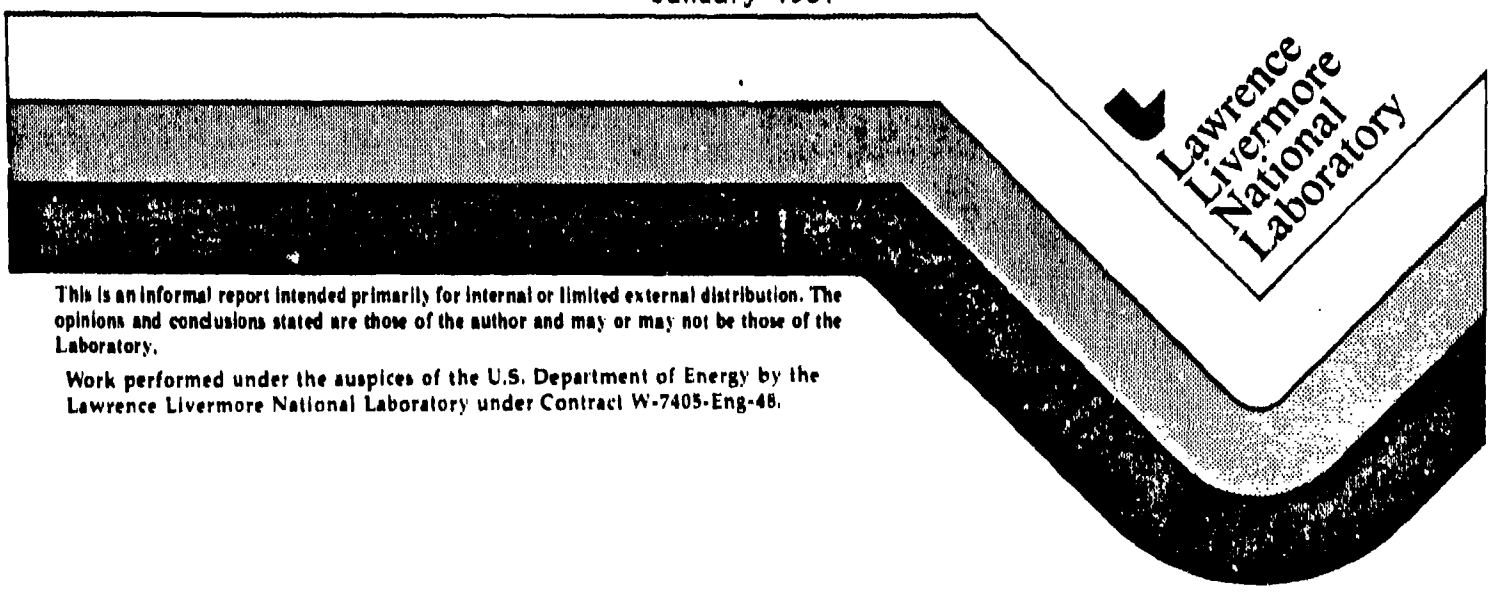

This is an informal report intended primarily for internal or limited external distribution. The opinions and conclusions stated are those of the author and may or may not be those of the Laboratory.

Work performed under the auspices of the U.S. Department of Energy by the Lawrence Livermore National Laboratory under Contract W-7405-Eng-48.

Preface

The Numerical Electromagnetics Code (NEC) has been developed at the Lawrence Livermore Laboratory, Livermore, California, under the sponsorship of the Naval Ocean Systems Center and the Air Force Weapons Laboratory. It is an advanced version of the Antenna Modeling Program (AMP) developed in the early 1970's by MBAssociates for the Naval Research Laboratory, Naval Ship Engineering Center, U.S. Army FCOM/Communications Systems, U.S. Army Strategic Communications Command, and Rome Air Development Center under Office of Naval Research Contract N00014-71-C-0187. The present version of NEC is the result of efforts by G. J. Burke and A. J. Poggio of Lawrence Livermore Laboratory.

The documentaton for NEC consists of three parts:

Part I: NEC Program Description - Theory

Part II: NEC Program Description - Code

Part III: NEC User's Guide

The documentation has been prepared by using the AMP documents as foundations and by modifying those as needed. In some cases this led to minor changes in the original documents while in many cases major modifications were required.

Over the years many individuals have been contributors to AMP and NEC and are acknowledged here as follows:

R. W. Adams	R. J. Lytle
J. N. Brittingham	E. K. Miller
G. J. Burke	J. B. Morton
F. J. Deadrick	G. M. Pjerrou
K. K. Hazard	A. J. Poggio
D. L. Knepp	E. S. Selden
D. L. Lager	

The support for the development of NEC-2 at the Lawrence Livermore Laboratory has been provided by the Naval Ocean Systems Center under MIPR-N0095376MP. Cognizant individuals under whom this project was carried out include: J. Rockway and J. Logan. Previous development of NEC also included the support of the Air Force Weapons Laboratory (Project Order 76-090) and was monitored by J. Castillo and TSgt. H. Goodwin.

Work was performed under the auspices of the U.S. Department of Energy under contract No. W-7405-Eng-48. Reference to a company or product name

does not imply approval or recommendation of the product by the University of California or the U.S. Department of Energy to the exclusion of others that may be suitable.

Contents

Section		Page
	List of Illustrations	vii
	Abstract	viii
I.	INTRODUCTION	1
II.	CODE DESCRIPTION	2
	MAIN	3
	ARC	29
	ATGN2	31
	BLCKOT	32
	CABC	34
	CANG	38
	CMNGF	39
	CMSET	47
	CMSS	53
	CMSW	57
	CMWS	63
	CMWW	67
	CONECT	71
	COUPLE	80
	DATAGN	83
	DBIO	90
	EFLD	91
	EKSC	100
	EKSCX	102
	ENF	105
	ETMNS	106
	FACGF	116
	FACIO	120
	FACTR	123
	FACTRS	128
	FBAR	132
	FBLOCK	135

Section	Page
FBNGF	139
FFLD	142
FFLDS	151
GF	153
GFIL	155
GFLD	159
GFOUT	169
GH	172
GWAVE	174
GX	183
GXX	184
HFK	186
HINTG	189
HSFLD	194
HSFLX	198
INTRP	202
INTX	209
ISEGNO	216
LFACTR	217
LOAD	222
LTSOLV	227
LUNSCR	231
MOVE	234
NEFLD	239
NETWK	244
NFPAT	258
NHFLD	261
PATCH	265
PCINT	271
PRNT	278
QDSRC	282

Section Page

RDPAT 286
REBLK 297
REFLC 299
ROM2 306
SBF 310
SECOND 314
SFLDS 315
SOLGF 321
SOLVE 326
SOLVES 329
TBF 333
TEST 339
TRIO 341
UNERE 343
WIRE 348
ZINT 351

III. COMMON BLOCKS 355

IV. SYSTEM LIBRARY FUNCTIONS USED BY NEC 370

V. ARRAY DIMENSION LIMITATIONS 371

VI. OVERVIEW OF NUMERICAL GREEN'S FUNCTION OPERATION 377

VII. OVERVIEW OF MATRIX OPERATIONS USING FILE STORAGE 381

VIII. NEC SUBROUTINE LINKAGE 385

IX. SOMNEC 390

1. SOMNEC Code Description 390

SOMNEC 391
BESSEL 397
EVLUA 402
GSHANK 407
HANKEL 413
LAMBDA 418

Section Page

ROM1 420
SAOA 423
SECOND 427
TEST 427
2. Common Blocks in SOMNEC 428
3. Array Dimension Limitations 430
4. SOMNEC Subroutine Linkage 431
References 433

List of Illustrations

Figure		Page
1	Flow Diagram of Main Program Input Section	4
2	Flow Diagram of Main Program Computation Section	5
3	Structure for Illustrating Segment Connection Data	72
4	Coordinate Parameters for the Incident Plane Wave	108
5	Coordinate Parameters for Current Element	110
6	Coordinate Systems Used to Evaluate Norton's Expressions for the Ground Wave Fields in the NEC Program	160
7	Coordinates for Evaluating H Field of a Segment	199
8	Options for Transmission Line Connection	247
9	Sorting Procedure for Segments Having Network Connection	248
10	Patches at a Wire Connection Point	272
11	Coordinates of Segment i	356
12	Matrix Structure for the NGF Solution	379
13	NGF File Usage for ICASX = 2	383
14	NGF File Usage for ICASX = 3 or 4	384
15	NEC Subroutine Linkage Chart	386
16	Block Definitions for NEC Subroutine Linkage Chart	388
17	SOMNEC Subroutine Linkage Chart	432

Abstract

The Numerical Electromagnetics Code (NEC-2) is a computer code for analyzing the electromagnetic response of an arbitrary structure consisting of wires and surfaces in free space or over a ground plane. The analysis is accomplished by the numerical solution of integral equations for induced currents. The excitation may be an incident plane wave or a voltage source on a wire, while the output may include current and charge density, electric or magnetic field in the vicinity of the structure, and radiated fields. Hence, the code may be used for antenna analysis or scattering and EMP studies.

This document is Part II of a three-part report. It contains a detailed description of the Fortran coding, including the definitions of variables and constants, and a listing of the code. The other two documents cover the equations and numerical methods (Part I) and instructions for use of the code (Part III).

KEY WORDS FOR DD FORM 1473:

EM scattering

EMP

Wire Model

Method of moments

Section I
Introduction

The Numerical Electromagnetics Code (NEC-2)* is a user-oriented computer code for the analysis of the electromagnetic response of antennas and other metal structures. It is built around the numerical solution of integral equations for the currents induced on the structure by sources or incident fields. This approach avoids many of the simplifying assumptions required by other solution methods and provides a highly accurate and versatile tool for electromagnetic analysis.

The code combines an integral equation for smooth surfaces with one specialized to wires to provide for convenient and accurate modeling of a wide range of structures. A model may include nonradiating networks and transmission lines connecting parts of the structure, perfect or imperfect conductors, and lumped-element loading. A structure may also be modeled over a ground plane that may be either a perfect or imperfect conductor.

The excitation may be either voltage sources on the structure or an incident plane wave of linear or elliptic polarization. The output may include induced currents and charges, near electric or magnetic fields, and radiated fields. Hence, the program is suited to either antenna analysis or scattering and EMP studies.

This document is Vol. II of a three-part report on NEC. It contains a detailed description of the Fortran coding. Section II contains for each routine: (1) a statement of purpose, (2) a narrative description of the methodology, (3) definitions of variables and constants, and (4) a listing of the code. The remaining sections cover the common blocks, system library functions, array dimension limitations, and subroutine linkage.
The information in Vol. II will be of use mainly to persons attempting to modify the code or to use it on a computer system with which the delivered deck is not compatible.

Vol. I describes the equations and numerical methods used in NEC and Vol. III contains instructions for using the code, including preparation of input data and interpretation of output. Persons attempting to use NEC for the first time should start by reading Vol. III. Vol. I will help the new user to understand the capabilities and limitations of NEC.

*NEC-2 will be abbreviated to NEC elsewhere in this volume.

Section II
Code Description

In this section, each routine in NEC is described in detail. The main program is described first and is followed by the subroutines in alphabetical order. For each routine, there is a brief statement of its purpose, a description of the code, an alphabetized listing and definition of important variables and constants, and a listing of the code. Variables that are in common blocks, and hence occur in several routines, are usually omitted from the lists for individual routines. They are defined in Section III under their common block labels.

Following line MA 495 in the main program, all quantities of length have been normalized to wavelength. Current is normalized to wavelength throughout the solution. This changes the appearance of many of the equations. In particular the wave number, $k = 2\pi/\lambda$, usually appears as 2π.

MAIN

PURPOSE

To handle input and output and to call the appropriate subroutines.

METHOD

The structure of MAIN is shown in the flow charts of Figures 1 and 2 where Figure 1 represents the first half of the code to about line MA 459. Comment cards are read and printed after line MA 72 and subroutine DATAGN is called at MA 90 to read and process structure data. If a Numerical Green's Function (NGF) file was read in DATAGN then subroutine FBNFG is called to determine whether file storage is needed for the matrix and to allocate core storage. When a NGF has not been read the mode of matrix storage cannot be determined until line MA 464 since it depends on whether a NFG file is to be written.

The box labeled "Read data card" in Figure 1 refers to the READ statement at MA 139. Any of the types of data cards in Table 1 may be read at this point to set parameters or to request execution of the solution part of the code.

The integer variables IGØ and IFLOW are keys to the operation of the code. IGØ indicates the stage of completion of the solution as listed in Table 2. When a card requesting execution is read (NE, NH, RP, WG, or XQ) the solution part of the code (Figure 2) is entered at the point determined by IGØ (see MA 385, MA 420, MA 429, and MA 457). After the current has been computed IGØ is given the value five. If subsequent data cards change parameters, the value of IGØ is reduced to the value in Table 1 to indicate the point beyond which the solution must be repeated. For example, when an EX card is read IGØ is set equal to three if it was greater than three but is not changed if it was less than three. For cards that request execution "ex." is shown in Table 1.

IFLOW is used to indicate the type of the previous data card. When several cards of the same type can be used together (CP, LD, NT, TL, and EX for voltage sources) a counter is incremented and data is added to arrays if the card is the same as the previous card as indicated by IFLOW. If the previous card was different the counter is initialized and previous data in the arrays is destroyed. IFLOW is also used to indicate what type of card

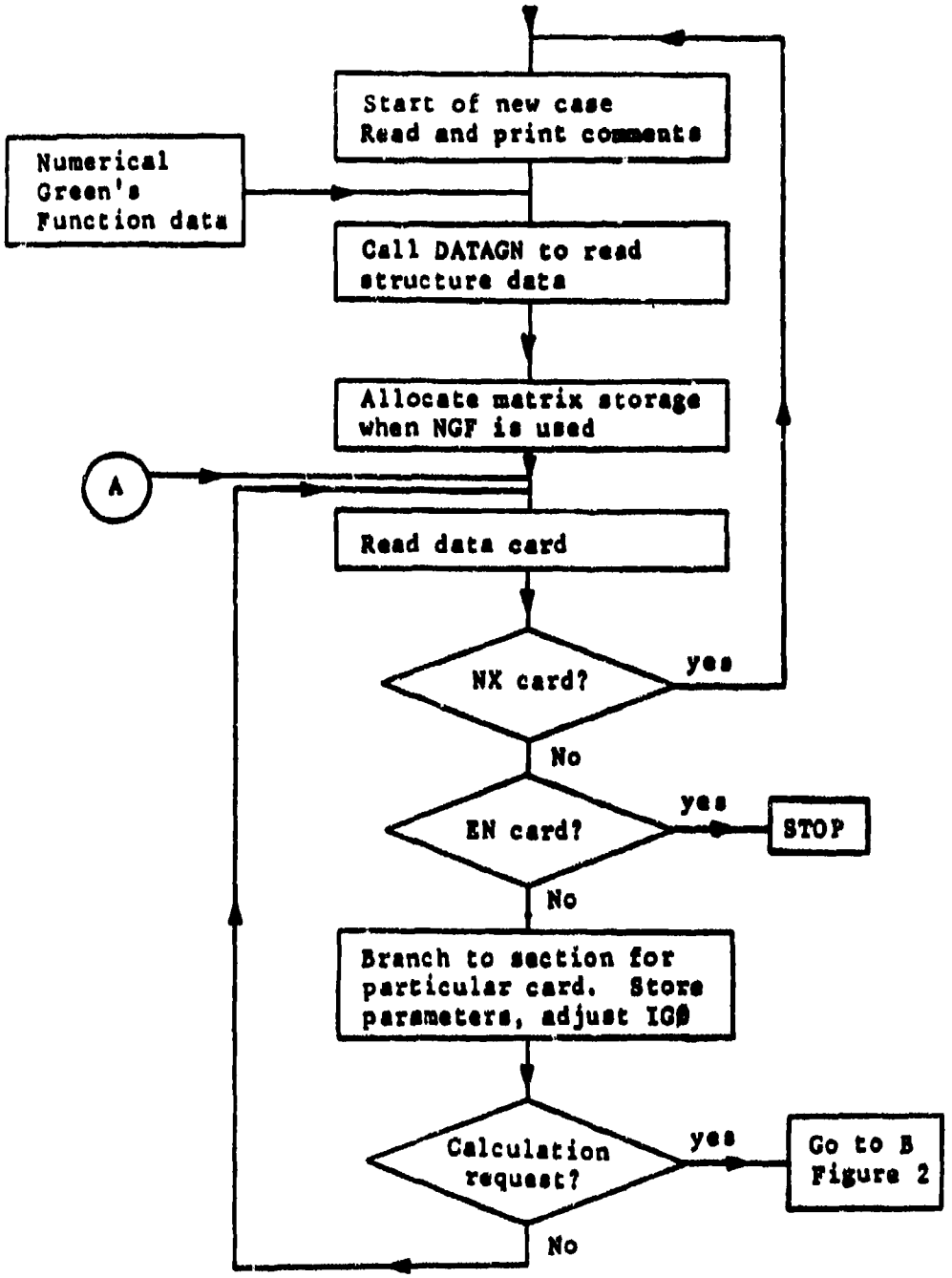


Figure 1. Flow Diagram of Main Program Input Section

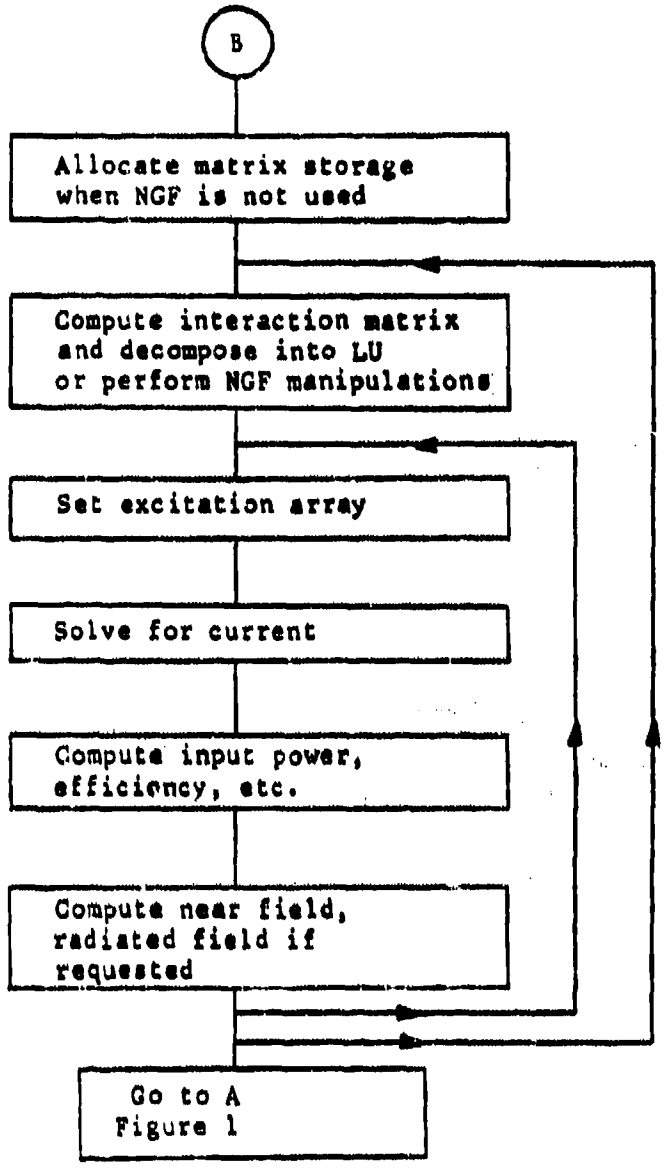


Figure 2. Flow Diagram of Main Program Computation Section

TABLE 1

	I	AIN(I)	GO TO	Line	IGØ	IFLOW
1	21	CP	304	202	-	2
2	19	EK	320	194	2	1
3	13	EN	STØP	166	-	-
4	5	EX	24	275	3	5
5	2	FR	16	172	1	1
6	9	GD	34	389	-	9
7	4	GN	21	245	2	4
8	16	KH	305	187	2	1
9	3	LD	17	221	2	3
10	8	NE	32	370	ex.*	8
11	17	NH	208	368	ex.*	8
12	6	NT	28	321	3	6
13	12	NX	1	69	1	1
14	18	PQ	319	358	-	-
15	15	PT	31	348	-	-
16	10	RP	36	398	ex.	10
17	14	TL	28	321	3	6
18	20	WG	322	424	ex.	12
19	7	XQ	37	433	ex.	7 or 11

* NE and NH do not cause execution when multiple frequencies have been requested on the FR card. This allows computation of both near fields and radiated fields in a frequency loop.

Table 2.

IGO	Completion Point
1	Start
2	Frequency has been set and geometry scaled to wavelength
3	Interaction matrix filled and factored
4,5	Current computed and printed

requested the solution (NE, RP, etc.). Cards such as RP may be stacked together but are not stored since they are acted upon as they are encountered.

The solution part of the code contains a loop over frequency starting at MA 463 and a loop over incident field direction starting at MA 562. FBLOCK is called at MA 465 to determine whether file storage is required for the matrix. From MA 466 to MA 493 the structure data are scaled from units of meters to wavelength or from one wavelength to the next when frequency is changed. Subroutine LOAD is called at MA 497 to fill array ZARRAY for the given frequency. At MA 520 the Sommerfeld interpolation tables are read from file TAPE21 if this option is used. NXA(1) is set to zero at MA 67 so the test ensures that the tape is read only once.

When the NGF option is not in use the matrix is filled by subroutine CMSET at MA 537 and factored by subroutine FACTRS at MA 540. When the NGF is used the equivalent steps are performed by CMNGF and FACGF. If a NGF file is to be written, subroutine GFOUT is called at MA 557 to write TAPE20.

Subroutine ETMNS, called at MA 582, fills the excitation array and the current is computed in subroutine NETWK called at MA 611. If transmission lines or two port networks are used NETWK combines the network equations with driving-point interaction equations derived from the primary interaction matrix. Otherwise the current is computed directly from the primary matrix.

The remainder of MAIN prints the currents and calls subroutines for near fields, radiated fields or coupling.

SYMBOL DICTIONARY:

AIN	= mnemonic from data card
ATST	= array of possible data card mnemonics
CMAG	= magnitude of the current in amperes
COM	= array to store text from comment cards
CURI	= current on segment I in amperes
CVEL	= (velocity of light) (10^{-6}) in meters/second
DELFRQ	= frequency increment (additive or multiplicative)
DPH	= far-field ϕ angle increment in degrees (input quantity)
DTH	= far-field θ angle increment in degrees (input quantity)

DXNR, DYNR, DZNR = near-field observation point increments (input quantities with multiple meanings -- see NE card)

EPH = current component in direction $\hat{t}_2$ on patch

EPHA = phase angle of EPH

EPHM = magnitude of EPH

EPSC = complex dielectric constant of ground $\epsilon_c = \epsilon_r - j\sigma/\omega\epsilon_0$.)

EPSCF = ϵ_c read from file TAPE21

EPSR = ϵ_r

EPSR2 = ϵ_r for outer ground region

ETH = current component in direction $\hat{t}_1$ on patch

ETHA = phase angle of ETH

ETHM = magnitude of ETH

EX = $\hat{x}$ component of current on a patch

EXTIM = time at start of run (seconds)

EY = $\hat{y}$ component of current on a patch

EZ = $\hat{z}$ component of current on a patch

FJ = $\sqrt{-1}$

FMHZ = frequency in MHz

FMHZS = frequency in MHz

FNORM = multiply used array; stores impedances for printing of the normalized impedance or stores currents in the receiving pattern case for printing normalized receiving pattern

FR = (next frequency)/(present frequency)

FR2 = (FR)(FR)

GNOR = if non-zero, equals gain normalization factor (dB) from RP card

HPOL = array containing polarization types (Hollerith)

IAVP = input integer flag used in average gain logic (RP card)

IAX = input integer flag specifying gain type (RP card)

IB11 = location in array CM for start of storage of submatrix B when NGF is used

IC11 = location in array CM for start of storage of submatrix C when NGF is used

ID11	=	location in CM for submatrix D
IEXK	=	flag to select the extended thin-wire kernel
IFAR	=	input integer flag specifying type of field calculation and type of ground system in far field (RP card)
IFLOW	=	integer flag used to distinguish various input sections
IFRQ	=	input integer flag specifying type of frequency stepping (FR card)
IGO	=	integer to indicate stage of completion of the solution
INC	=	incident field loop index
INOR	=	input integer flag used for normalized gain request (RP card)
IPD	=	input integer flag selects gain type for normalization (RP card)
IPED	=	input integer flag used for impedance normalization request (EX card)
IPTAG	=	input integer for print control equal to segment tag number (PT card)
IPTAGF	=	input integer for print control specifying segment placement in a set of equal tags (PT card)
IPTAGT	=	same function as IPTAGF (input, PT card)
IPTFLG	=	input integer flag specifying type of print control (PT card)
IPTAQ, IPTAQF, IPTAQT, IPTFLQ	=	same as above four variables but for PQ card
IRESRV	=	length of array CM in complex numbers
IRNGF	=	storage in array CM that is reserved for later use when a NGF file is written
ISANT	=	array of segment numbers for voltage sources
ISAVE	=	segment number for normalized receiving pattern calculation

ISEG1 (I) ISEG2 (I)	=	segment numbers of end 1 and end 2 of the i^{th} network connection
ITMP1 to ITMP5	=	temporary storage
IX	=	array for matrix pivot element information
IX11	=	location in CM of the start of an array in the NGF solution
IXTYP	=	excitation type from EX card
KCOM	=	number of comment cards read
LDTAG	=	tag number of loaded segment
LDTAGF	=	number of first loaded segment in set of segments having given tag
LDTAGT	=	last loaded segment
LDTYP	=	loading type
LOADMX	=	maximum number of loading cards
MASYM	=	flag to request matrix asymmetry calculation
MHZ	=	frequency loop index
MPCNT	=	counter for data cards
NCOUP	=	number of excitation points for coupling calculation
NCSEG NCTAG	=	excitation segment for coupling calculation
NEAR	=	increment option for near field points
NEQ	=	order of the primary interaction matrix
NEQ2	=	number of new unknowns in NGF mode
NETMX	=	maximum number of network data cards
NFEH	=	0 for near E field, 1 for near H
NFRQ	=	number of frequency steps
NONET	=	number of network data cards
NORMF	=	dimension of FNORM
NPHI	=	number of phi steps in incident field
NPHIC	=	loop index for phi in incident field
NPRINT	=	print control flag for subroutine NETWK
NRX NRY NRZ	=	number of steps in near field evaluation loops
NSANT	=	number of voltage sources
NSMAX	=	maximum number of voltage sources

MAIN

NTHI	=	number of theta steps in incident field
NTHIC	=	loop index for theta in incident field
PH	=	phase angle of current or charge (degrees)
PHISS	=	initial ϕ value for incident field
PIN	=	P_{in} = total power supplied to a structure by all voltage sources (Σ R#(VI*)/2). For a Hertzian dipole source $P_{in} = \eta(\pi/3)\lvert I\ell/\lambda\rvert^2$.
PLOSS	=	power lost in distributed and point structure loads in watts
PNET	=	array contains Hollerith transmission line type
RFLD	=	if non-zero, equal to input far-field observation distance in meters
RKH	=	minimum separation for use of approximate interaction equations
SCRWLT	=	input length of radials in radial wire screen (GN card) in meters
SCRWRT	=	radius of wires in radial wire ground screen in meters
SIG	=	conductivity of ground (σ in mhos/meter on GN card)
SIG2	=	conductivity of second medium in mhos/meter (GN and GD card)
TA	=	$\pi/180$
THETIS	=	initial θ for incident field
THETS	=	initial θ for radiated field
TIM	=	matrix computation time (seconds)
TMP1 to TMP6	=	temporary input variables
XPR1 to XPR6	=	input quantities for incident field or Hertzian dipole illumination
ZLC, ZLI, ZLR	=	input quantities for loading
ZPNORM	=	impedance normalization quantity

CONSTANTS

1.E-20	=	used as small value test

1.745329252	=	$\pi/180$
2367.067	=	$2\pi\eta_0$
59.96	=	$1/(2\pi c\epsilon_0)$
299.8	=	$c/10^6$

```
      PROGRAM NEC(INPUT,TAPE5=INPUT,OUTPUT,TAPE11,TAPE12,TAPE13,TAPE14,
     1TAPE15,TAPE16,TAPE20,TAPE21)
C
C     NUMERICAL ELECTROMAGNETICS CODE (NEC2)  DEVELOPED AT LAWRENCE
C     LIVERMORE LAB., LIVERMORE, CA.  (CONTACT G. BURKE, 415-422-8414)
C     FILE CREATED 4/11/80.
C
C                ***********NOTICE**********
C     THIS COMPUTER CODE MATERIAL WAS PREPARED AS AN ACCOUNT OF WORK
C     SPONSORED BY THE UNITED STATES GOVERNMENT.  NEITHER THE UNITED
C     STATES NOR THE UNITED STATES DEPARTMENT OF ENERGY, NOR ANY OF
C     THEIR EMPLOYEES, NOR ANY OF THEIR CONTRACTORS, SUBCONTRACTORS, OR
C     THEIR EMPLOYEES, MAKES ANY WARRANTY, EXPRESS OR IMPLIED, OR
C     ASSUMES ANY LEGAL LIABILITY OR RESPONSIBILITY FOR THE ACCURACY,
C     COMPLETENESS OR USEFULNESS OF ANY INFORMATION, APPARATUS, PRODUCT
C     OR PROCESS DISCLOSED, OR REPRESENTS THAT ITS USE WOULD NOT
C     INFRINGE PRIVATELY-OWNED RIGHTS.
C
      INTEGER  AIN,ATST,PNET,HPOL
      COMPLEX  CM,FJ,VSANT,ETH,EPH,ZRATI,CUR,CURI,ZARRAY,ZRATI2
      COMPLEX  EX,EY,EZ,ZPED,VQD,VQDS,T1,Y11A,Y12A,EPSC,U,U2,XX1,XX2
      COMPLEX  AR1,AR2,AR3,EPSCF,FRATI
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),
     1SI(300),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),
     2ITAG(300),ICONX(300),WLAM,IPSYM
      COMMON /CMB/CM(4000)
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,
     1ICASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL
      COMMON/SAVE/IP(600),KCOM,COM(13,5),EPSR,SIG,SCRWLT,SCRWRT,FMHZ
      COMMON /CRNT/ AIR(300),AII(300),BIR(300),BII(300),CIR(300),
     1 CII(300),CUR(900)
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR,
     1IPERF,T1,T2
      COMMON /ZLOAD/ ZARRAY(300),NLOAD,NLODF
      COMMON/YPARM/NCOUP,ICOUP,NCTAG(5),NCSEG(5),Y11A(5),Y12A(20)
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(50),NSCON,
     1IPCON(10),NPCON
      COMMON/VSORC/VQD(30),VSANT(30),VQDS(30),IVQD(30),ISANT(30),
     1IQDS(30),NVQD,NSANT,NQDS
      COMMON/NETCX/ZPED,PIN,PNLS,NEQ,NPEQ,NEQ2,NONET,NTSOL,NPRINT,
     1MASYM,ISEG1(30),ISEG2(30),X11R(30),X11I(30),X12R(30),X12I(30),
     1X22R(30),X22I(30),NTYP(30)
      COMMON/FPAT/NTH,NPH,IPD,IAVP,INOR,IAX,THETS,PHIS,DTH,DPH,
     1RFLD,GNOR,CLT,CHT,EPSR2,SIG2,IXTYP,XPR6,PINR,PNLR,PLOSS,
     1NEAR,NFEH,NRX,NRY,NRZ,XNR,YNR,ZNR,DXNR,DYNR,DZNR
      COMMON /GGRID/ AR1(11,10,4),AR2(17,5,4),AR3(9,8,4),EPSCF,DXA(3),
     1DYA(3),XSA(3),YSA(3),NXA(3),NYA(3)
      COMMON/GWAV/U,U2,XX1,XX2,R1,R2,ZMH,ZPH
      DIMENSION CAB(1),SAB(1),X2(1),Y2(1),Z2(1)
      DIMENSION LDTYP(30),LDTAG(30),LDTAGF(30),LDTAGT(30),ZLR(30),
     1ZLI(30),ZLC(30)
      DIMENSION ATST(21),PNET(6),HPOL(3),IX(600)
      DIMENSION FNORM(200)
      DIMENSION T1X(1),T1Y(1),T1Z(1),T2X(1),T2Y(1),T2Z(1)
      EQUIVALENCE (CAB,ALP),(SAB,BET),(X2,SI),(Y2,ALP),(Z2,BET)
      EQUIVALENCE (T1X,SI),(T1Y,ALP),(T1Z,BET),(T2X,ICON1),(T2Y,ICON2),
     1 (T2Z,ITAG)
      DATA ATST/2HCE,2HFR,2HLD,2HGN,2HEX,2HNT,2HXQ,2HNE,2HGD,2HRP,2HCM,
     1 2HNX,2HEN,2HTL,2HPT,2HKH,2HNH,2HPQ,2HEK,2HWG,2HCP/
      DATA HPOL/6HLINEAR,5HRIGHT,4HLEFT/
      DATA PNET/6H      ,2H  ,6HSTRAIG,2HHT,6HCROSSE,1HD/
      DATA TA/1.745329252E-02/,CVEL/299.8/
      DATA LOADMX,NSMAX,NETMX/30,30,30/,NORMF/200/
```

```
      CALL SECOND(EXTIM)                                                MA  64
      FJ=(0.,1.)                                                        MA  65
      LD=300                                                            MA  66
      NXA(1)=0                                                          MA  67
      IRESRV=4000                                                       MA  68
    1 KCOM=0                                                            MA  69
    2 KCOM=KCOM+1                                                       MA  70
      IF (KCOM.GT.5) KCOM=5                                             MA  71
      READ(5,125)AIN,(COM(I,KCOM),I=1,13)                               MA  72
      IF(KCOM.GT.1)GO TO 3                                              MA  73
      PRINT 126                                                         MA  74
      PRINT 127                                                         MA  75
      PRINT 128                                                         MA  76
    3 PRINT 129, (COM(I,KCOM),I=1,13)                                   MA  77
      IF (AIN.EQ.ATST(11)) GO TO 2                                      MA  78
      IF (AIN.EQ.ATST(1)) GO TO 4                                       MA  79
      PRINT 130                                                         MA  80
      STOP                                                              MA  81
    4 CONTINUE                                                          MA  82
      DO 5 I=1,LD                                                       MA  83
    5 ZARRAY(I)=(0.,0.)                                                 MA  84
      MPCNT=0                                                           MA  85
      IMAT=0                                                            MA  86
C                                                                       MA  87
C     SET UP GEOMETRY DATA IN SUBROUTINE DATAGN                         MA  88
C                                                                       MA  89
      CALL  DATAGN                                                      MA  90
      IFLOW=1                                                           MA  91
      IF(IMAT.EQ.0)GO TO 326                                            MA  92
C                                                                       MA  93
C     CORE ALLOCATION FOR ARRAYS B, C, AND D FOR N.G.F. SOLUTION        MA  94
C                                                                       MA  95
      NEQ=N1+2*M1                                                       MA  96
      NEQ2=N-N1+2*(M-M1)+NSCON+2*NPCON                                  MA  97
      CALL FBNGF(NEQ,NEQ2,IRESRV,IB11,IC11,ID11,IX11)                   MA  98
      GO TO 6                                                           MA  99
  326 NEQ=N+2*M                                                         MA 100
      NEQ2=0                                                            MA 101
      IB11=1                                                            MA 102
      IC11=1                                                            MA 103
      ID11=1                                                            MA 104
      IX11=1                                                            MA 105
      ICASX=0                                                           MA 106
    6 NPEQ=NP+2*MP                                                      MA 107
      PRINT 135                                                         MA 108
C                                                                       MA 109
C     DEFAULT VALUES FOR INPUT PARAMETERS AND FLAGS                     MA 110
C                                                                       MA 111
      IGO=1                                                             MA 112
      FMHZS=CVEL                                                        MA 113
      NFRQ=1                                                            MA 114
      RKH=1.                                                            MA 115
      IEXK=0                                                            MA 116
      IXTYP=0                                                           MA 117
      NLOAD=0                                                           MA 118
      NONET=0                                                           MA 119
      NEAR=-1                                                           MA 120
      IPTFLG=-2                                                         MA 121
      IPTFLQ=-1                                                         MA 122
      IFAR=-1                                                           MA 123
      ZRATI=(1.,0.)                                                     MA 124
      IPED=0                                                            MA 125
      IRNGF=C                                                           MA 126
      NCOUP=0                                                           MA 127
```

```
      ICOUP=0                                                           MA 128
      IF(ICASX.GT.0)GO TO 14                                            MA 129
      FMHZ=CVEL                                                         MA 130
      NLODF=0                                                           MA 131
      KSYMP=1                                                           MA 132
      NRADL=0                                                           MA 133
      IPERF=0                                                           MA 134
C                                                                       MA 135
C     MAIN INPUT SECTION - STANDARD READ STATEMENT - JUMPS TO APPRO-    MA 136
C     PRIATE SECTION FOR SPECIFIC PARAMETER SET UP                      MA 137
C                                                                       MA 138
14    READ(5,136)AIN,ITMP1,ITMP2,ITMP3,ITMP4,TMP1,TMP2,TMP3,TMP4,TMP5, MA 139
     1TMP6                                                              MA 140
      MPCNT=MPCNT+1                                                     MA 141
      PRINT 137, MPCNT,AIN,ITMP1,ITMP2,ITMP3,ITMP4,TMP1,TMP2,TMP3,TMP4, MA 142
     1TMP5,TMP6                                                         MA 143
      IF (AIN.EQ.ATST(2)) GO TO 16                                      MA 144
      IF (AIN.EQ.ATST(3)) GO TO 17                                      MA 145
      IF (AIN.EQ.ATST(4)) GO TO 21                                      MA 146
      IF (AIN.EQ.ATST(5)) GO TO 24                                      MA 147
      IF (AIN.EQ.ATST(6)) GO TO 28                                      MA 148
      IF (AIN.EQ.ATST(14)) GO TO 28                                     MA 149
      IF (AIN.EQ.ATST(15)) GO TO 31                                     MA 150
      IF (AIN.EQ.ATST(18)) GO TO 319                                    MA 151
      IF (AIN.EQ.ATST(7)) GO TO 37                                      MA 152
      IF (AIN.EQ.ATST(8)) GO TO 32                                      MA 153
      IF (AIN.EQ.ATST(17)) GO TO 208                                    MA 154
      IF (AIN.EQ.ATST(9)) GO TO 34                                      MA 155
      IF (AIN.EQ.ATST(10)) GO TO 36                                     MA 156
      IF (AIN.EQ.ATST(16)) GO TO 305                                    MA 157
      IF (AIN.EQ.ATST(19)) GO TO 320                                    MA 158
      IF (AIN.EQ.ATST(12)) GO TO 1                                      MA 159
      IF (AIN.EQ.ATST(20)) GO TO 322                                    MA 160
      IF (AIN.EQ.ATST(21)) GO TO 304                                    MA 161
      IF (AIN.NE.ATST(13)) GO TO 15                                     MA 162
      CALL SECOND(TMP1)                                                 MA 163
      TMP1=TMP1-EXTIM                                                   MA 164
      PRINT 201,TMP1                                                    MA 165
      STOP                                                              MA 166
15    PRINT 138                                                         MA 167
      STOP                                                              MA 168
C                                                                       MA 169
C     FREQUENCY PARAMETERS                                              MA 170
C                                                                       MA 171
16    IFRQ=ITMP1                                                        MA 172
      IF(ICASX.EQ.0)GO TO 8                                             MA 173
      PRINT 303,AIN                                                     MA 174
      STOP                                                              MA 175
8     NFRQ=ITMP2                                                        MA 176
      IF (NFRQ.EQ.0) NFRQ=1                                             MA 177
      FMHZ=TMP1                                                         MA 178
      DELFRQ=TMP2                                                       MA 179
      IF(IPED.EQ.1)ZPNORM=0.                                            MA 180
      IGO=1                                                             MA 181
      IFLOW=1                                                           MA 182
      GO TO 14                                                          MA 183
C                                                                       MA 184
C     MATRIX INTEGRATION LIMIT                                          MA 185
C                                                                       MA 186
305   RKH=TMP1                                                          MA 187
      IF(IGO.GT.2)IGO=2                                                 MA 188
      IFLOW=1                                                           MA 189
      GO TO 14                                                          MA 190
C                                                                       MA 191
```

```
      C     EXTENDED THIN WIRE KERNEL OPTION                          MA 192
      C                                                               MA 193
  320 IEXK=1                                                          MA 194
      IF(ITMP1.EQ.-1)IEXK=0                                           MA 195
      IF(IGO.GT.2)IGO=2                                               MA 196
      IFLOW=1                                                         MA 197
      GO TO 14                                                        MA 198
      C                                                               MA 199
      C     MAXIMUM COUPLING BETWEEN ANTENNAS                         MA 200
      C                                                               MA 201
  304 IF(IFLOW.NE.2)NCOUP=0                                           MA 202
      ICOUP=0                                                         MA 203
      IFLOW=2                                                         MA 204
      IF(ITMP2.EQ.0)GO TO 14                                          MA 205
      NCOUP=NCOUP+1                                                   MA 206
      IF(NCOUP.GT.5)GO TO 312                                         MA 207
      NCTAG(NCOUP)=ITMP1                                              MA 208
      NCSEG(NCOUP)=ITMP2                                              MA 209
      IF(ITMP4 EQ.0)GO TO 14                                          MA 210
      NCOUP=NCOUP+1                                                   MA 211
      IF(NCOUP.GT.5)GO TO 312                                         MA 212
      NCTAG(NCOUP)=ITMP3                                              MA 213
      NCSEG(NCOUP)=ITMP4                                              MA 214
      GO TO 14                                                        MA 215
  312 PRINT 313                                                       MA 216
      STOP                                                            MA 217
      C                                                               MA 218
      C     LOADING PARAMETERS                                        MA 219
      C                                                               MA 220
   17 IF (IFLOW.EQ.3) GO TO 18                                        MA 221
      NLOAD=0                                                         MA 222
      IFLOW=3                                                         MA 223
      IF (IGO.GT.2) IGO=2                                             MA 224
      IF (ITMP1.EQ.(-1)) GO TO 14                                     MA 225
   18 NLOAD=NLOAD+1                                                   MA 226
      IF (NLOAD.LE.LOADMX) GO TO 19                                   MA 227
      PRINT 139                                                       MA 228
      STOP                                                            MA 229
   19 LDTYP(NLOAD)=ITMP1                                              MA 230
      LDTAG(NLOAD)=ITMP2                                              MA 231
      IF (ITMP4.EQ.0) ITMP4=ITMP3                                     MA 232
      LDTAGF(NLOAD)=ITMP3                                             MA 233
      LDTAGT(NLOAD)=ITMP4                                             MA 234
      IF (ITMP4.GE.ITMP3) GO TO 20                                    MA 235
      PRINT 140, NLOAD,ITMP3,ITMP4                                    MA 236
      STOP                                                            MA 237
   20 ZLR(NLOAD)=TMP1                                                 MA 238
      ZLI(NLOAD)=TMP2                                                 MA 239
      ZLC(NLOAD)=TMP3                                                 MA 240
      GO TO 14                                                        MA 241
      C                                                               MA 242
      C     GROUND PARAMETERS UNDER THE ANTENNA                       MA 243
      C                                                               MA 244
   21 IFLOW=4                                                         MA 245
      IF(ICASX.EQ.0)GO TO 10                                          MA 246
      PRINT 303,AIN                                                   MA 247
      STOP                                                            MA 248
   10 IF (IGO.GT.2) IGO=2                                             MA 249
      IF (ITMP1.NE.(-1)) GO TO 22                                     MA 250
      KSYMP=1                                                         MA 251
      NRADL=0                                                         MA 252
      IPERF=0                                                         MA 253
      GO TO 14                                                        MA 254
   22 IPERF=ITMP1                                                     MA 255
```

```
      NRADL=ITMP2                                                       MA 256
      KSYMP=2                                                           MA 257
      EPSR=TMP1                                                         MA 258
      SIG=TMP2                                                          MA 259
      IF (NRADL.EQ.0) GO TO 23                                          MA 260
      IF(IPERF.NE.2)GO TO 314                                           MA 261
      PRINT 390                                                         MA 262
      STOP                                                              MA 263
314   SCRWLT=TMP3                                                       MA 264
      SCRWRT=TMP4                                                       MA 265
      GO TO 14                                                          MA 266
23    EPSR2=TMP3                                                        MA 267
      SIG2=TMP4                                                         MA 268
      CLT=TMP5                                                          MA 269
      CHT=TMP6                                                          MA 270
      GO TO 14                                                          MA 271
C                                                                       MA 272
C     EXCITATION PARAMETERS                                             MA 273
C                                                                       MA 274
24    IF (IFLOW.EQ.5) GO TO 25                                          MA 275
      NSANT=0                                                           MA 276
      NVQD=0                                                            MA 277
      IPED=0                                                            MA 278
      IFLOW=5                                                           MA 279
      IF (IGO.GT.3) IGO=3                                               MA 280
25    MASYM=ITMP4/10                                                    MA 281
      IF (ITMP1.GT.0.AND.ITMP1.NE.5) GO TO 27                           MA 282
      IXTYP=ITMP1                                                       MA 283
      NTSOL=0                                                           MA 284
      IF(IXTYP.EQ.0)GO TO 205                                           MA 285
      NVQD=NVQD+1                                                       MA 286
      IF(NVQD.GT.NSMAX)GO TO 206                                        MA 287
      IVQD(NVQD)=ISEGNO(ITMP2,ITMP3)                                    MA 288
      VQD(NVQD)=CMPLX(TMP1,TMP2)                                        MA 289
      IF(CABS(VQD(NVQD)).LT.1.E-20)VQD(NVQD)=(1.,0.)                    MA 290
      GO TO 207                                                         MA 291
205   NSANT=NSANT+1                                                     MA 292
      IF (NSANT.LE.NSMAX) GO TO 26                                      MA 293
206   PRINT 141                                                         MA 294
      STOP                                                              MA 295
26    ISANT(NSANT)=ISEGNO(ITMP2,ITMP3)                                  MA 296
      VSANT(NSANT)=CMPLX(TMP1,TMP2)                                     MA 297
      IF (CABS(VSANT(NSANT)).LT.1.E-20) VSANT(NSANT)=(1.,0.)            MA 298
207   IPED=ITMP4-MASYM*10                                               MA 299
      ZPNORM=TMP3                                                       MA 300
      IF (IPED.EQ.1.AND.ZPNORM.GT.0) IPED=2                             MA 301
      GO TO 14                                                          MA 302
27    IF (IXTYP.EQ.0.OR.IXTYP.EQ.5) NTSOL=0                             MA 303
      IXTYP=ITMP1                                                       MA 304
      NTHI=ITMP2                                                        MA 305
      NPHI=ITMP3                                                        MA 306
      XPR1=TMP1                                                         MA 307
      XPR2=TMP2                                                         MA 308
      XPR3=TMP3                                                         MA 309
      XPR4=TMP4                                                         MA 310
      XPR5=TMP5                                                         MA 311
      XPR6=TMP6                                                         MA 312
      NSANT=0                                                           MA 313
      NVQD=0                                                            MA 314
      THETIS=XPR1                                                       MA 315
      PHISS=XPR2                                                        MA 316
      GO TO 14                                                          MA 317
C                                                                       MA 318
C     NETWORK PARAMETERS                                                MA 319
```

```
320 C                                                                   MA 320
321 28      IF (IFLOW.EQ.6) GO TO 29                                    MA 321
322         NONET=0                                                     MA 322
323         NTSOL=0                                                     MA 323
324         IFLOW=6                                                     MA 324
325         IF (IGO.GT.3) IGO=3                                         MA 325
326         IF (ITMP2.EQ.(-1)) GO TO 14                                 MA 326
327 29      NONET=NONET+1                                               MA 327
328         IF (NONET.LE.NETMX) GO TO 30                                MA 328
329         PRINT 142                                                   MA 329
330         STOP                                                        MA 330
331 30      NTYP(NONET)=2                                               MA 331
332         IF (AIN.EQ.ATST(6)) NTYP(NONET)=1                           MA 332
333         ISEG1(NONET)=ISEGNO(ITMP1,ITMP2)                            MA 333
334         ISEG2(NONET)=ISEGNO(ITMP3,ITMP4)                            MA 334
335         X11R(NONET)=TMP1                                            MA 335
336         X11I(NONET)=TMP2                                            MA 336
337         X12R(NONET)=TMP3                                            MA 337
338         X12I(NONET)=TMP4                                            MA 338
339         X22R(NONET)=TMP5                                            MA 339
340         X22I(NONET)=TMP6                                            MA 340
341         IF (NTYP(NONET).EQ.1.OR.TMP1.GT.0.) GO TO 14                MA 341
342         NTYP(NONET)=3                                               MA 342
343         X11R(NONET)=-TMP1                                           MA 343
344         GO TO 14                                                    MA 344
345 C                                                                   MA 345
346 C       PRINT CONTROL FOR CURRENT                                   MA 346
347 C                                                                   MA 347
348 31      IPTFLG=ITMP1                                                MA 348
349         IPTAG=ITMP2                                                 MA 349
350         IPTAGF=ITMP3                                                MA 350
351         IPTAGT=ITMP4                                                MA 351
352         IF(ITMP3.EQ.0.AND.IPTFLG.NE.-1)IPTFLG=-2                    MA 352
353         IF (ITMP4.EQ.0) IPTAGT=IPTAGF                               MA 353
354         GO TO 14                                                    MA 354
355 C                                                                   MA 355
356 C       PRINT CONTROL FOR CHARGE                                    MA 356
357 C                                                                   MA 357
358 319     IPTFLQ=ITMP1                                                MA 358
359         IPTAQ=ITMP2                                                 MA 359
360         IPTAQF=ITMP3                                                MA 360
361         IPTAQT=ITMP4                                                MA 361
362         IF(ITMP3.EQ.0.AND.IPTFLQ.NE.-1)IPTFLQ=-2                    MA 362
363         IF(ITMP4.EQ.0)IPTAQT=IPTAQF                                 MA 363
364         GO TO 14                                                    MA 364
365 C                                                                   MA 365
366 C       NEAR FIELD CALCULATION PARAMETERS                           MA 366
367 C                                                                   MA 367
368 208     NFEH=1                                                      MA 368
369         GO TO 209                                                   MA 369
370 32      NFEH=0                                                      MA 370
371 209     IF (.NOT.(IFLOW.EQ.6.AND.NFRQ.NE.1)) GO TO 33               MA 371
372         PRINT 143                                                   MA 372
373 33      NEAR=ITMP1                                                  MA 373
374         NRX=ITMP2                                                   MA 374
375         NRY=ITMP3                                                   MA 375
376         NRZ=ITMP4                                                   MA 376
377         XNR=TMP1                                                    MA 377
378         YNR=TMP2                                                    MA 378
379         ZNR=TMP3                                                    MA 379
380         DXNR=TMP4                                                   MA 380
381         DYNR=TMP5                                                   MA 381
382         DZNR=TMP6                                                   MA 382
383         IFLOW=6                                                     MA 383
```

```
      IF (NFRQ.NE.1) GO TO 14                                          MA 384
      GO TO (41,46,53,71,72), IGO                                      MA 385
C                                                                      MA 386
C     GROUND REPRESENTATION                                            MA 387
C                                                                      MA 388
34    EPSR2=TMP1                                                       MA 389
      SIG2=TMP2                                                        MA 390
      CLT=TMP3                                                         MA 391
      CHT=TMP4                                                         MA 392
      IFLOW=9                                                          MA 393
      GO TO 14                                                         MA 394
C                                                                      MA 395
C     STANDARD OBSERVATION ANGLE PARAMETERS                            MA 396
C                                                                      MA 397
36    IFAR=ITMP1                                                       MA 398
      NTH=ITMP2                                                        MA 399
      NPH=ITMP3                                                        MA 400
      IF (NTH.EQ.0) NTH=1                                              MA 401
      IF (NPH.EQ.0) NPH=1                                              MA 402
      IPD=ITMP4/10                                                     MA 403
      IAVP=ITMP4-IPD*10                                                MA 404
      INOR=IPD/10                                                      MA 405
      IPD=IPD-INOR*10                                                  MA 406
      IAX=INOR/10                                                      MA 407
      INOR=INOR-IAX*10                                                 MA 408
      IF (IAX.NE.0) IAX=1                                              MA 409
      IF (IPD.NE.0) IPD=1                                              MA 410
      IF (NTH.LT.2.OR.NPH.LT.2) IAVP=0                                 MA 411
      IF (IFAR.EQ.1) IAVP=0                                            MA 412
      THETS=TMP1                                                       MA 413
      PHIS=TMP2                                                        MA 414
      DTH=TMP3                                                         MA 415
      DPH=TMP4                                                         MA 416
      RFLD=TMP5                                                        MA 417
      GNOR=TMP6                                                        MA 418
      IFLOW=10                                                         MA 419
      GO TO (41,46,53,71,78), IGO                                      MA 420
C                                                                      MA 421
C     WRITE NUMERICAL GREEN'S FUNCTION TAPE                            MA 422
C                                                                      MA 423
322   IFLOW=12                                                         MA 424
      IF(ICASX.EQ.0)GO TO 301                                          MA 425
      PRINT 302                                                        MA 426
      STOP                                                             MA 427
301   IRNGF=IRESRV/2                                                   MA 428
      GO TO (41,46,52,52,52),IGO                                       MA 429
C                                                                      MA 430
C     EXECUTE CARD  -  CALC. INCLUDING RADIATED FIELDS                 MA 431
C                                                                      MA 432
37    IF (IFLOW.EQ.10.AND.ITMP1.EQ.0) GO TO 14                         MA 433
      IF (NFRQ.EQ.1.AND.ITMP1.EQ.0.AND.IFLOW.GT.7) GO TO 14            MA 434
      IF (ITMP1.NE.0) GO TO 39                                         MA 435
      IF (IFLOW.GT.7) GO TO 38                                         MA 436
      IFLOW=7                                                          MA 437
      GO TO 40                                                         MA 438
38    IFLOW=11                                                         MA 439
      GO TO 40                                                         MA 440
39    IFAR=0                                                           MA 441
      RFLD=0                                                           MA 442
      IPD=0                                                            MA 443
      IAVP=0                                                           MA 444
      INOR=0                                                           MA 445
      IAX=0                                                            MA 446
      NTH=91                                                           MA 447
```

```
      NPH=1                                                              MA 448
      THETS=0.                                                           MA 449
      PHIS=0.                                                            MA 450
      DTH=1.0                                                            MA 451
      DPH=0.                                                             MA 452
      IF (ITMP1.EQ.2) PHIS=90.                                           MA 453
      IF (ITMP1.NE.3) GO TO 40                                           MA 454
      NPH=2                                                              MA 455
      DPH=90.                                                            MA 456
   40 GO TO (41,46,53,71,78), IGO                                        MA 457
C                                                                        MA 458
C     END OF THE MAIN INPUT SECTION                                      MA 459
C                                                                        MA 460
C     BEGINNING OF THE FREQUENCY DO LOOP                                 MA 461
C                                                                        MA 462
   41 MHZ=1                                                              MA 463
C     CORE ALLOCATION FOR PRIMARY INTERACTON MATRIX.  (A)                MA 464
      IF(IMAT.EQ.0)CALL FBLOCK(NPEQ,NEQ,IRESRV,IRNGF,IPSYM)              MA 465
   42 IF (MHZ.EQ.1) GO TO 44                                             MA 466
      IF (IFRQ.EQ.1) GO TO 43                                            MA 467
      FMHZ=FMHZ+DELFRQ                                                   MA 468
      GO TO 44                                                           MA 469
   43 FMHZ=FMHZ*DELFRQ                                                   MA 470
   44 FR=FMHZ/FMHZS                                                      MA 471
      WLAM=CVEL/FMHZ                                                     MA 472
      PRINT 145, FMHZ,WLAM                                               MA 473
      PRINT 196,RKH                                                      MA 474
      IF(IEXK.EQ.1)PRINT 321                                             MA 475
C     FREQUENCY SCALING OF GEOMETRIC PARAMETERS                          MA 476
      FMHZS=FMHZ                                                         MA 477
      IF(N.EQ.0)GO TO 306                                                MA 478
      DO 45 I=1,N                                                        MA 479
      X(I)=X(I)*FR                                                       MA 480
      Y(I)=Y(I)*FR                                                       MA 481
      Z(I)=Z(I)*FR                                                       MA 482
      SI(I)=SI(I)*FR                                                     MA 483
   45 BI(I)=BI(I)*FR                                                     MA 484
  306 IF(M.EQ.0)GO TO 307                                                MA 485
      FR2=FR*FR                                                          MA 486
      J=LD+1                                                             MA 487
      DO 245 I=1,M                                                       MA 488
      J=J-1                                                              MA 489
      X(J)=X(J)*FR                                                       MA 490
      Y(J)=Y(J)*FR                                                       MA 491
      Z(J)=Z(J)*FR                                                       MA 492
  245 BI(J)=BI(J)*FR2                                                    MA 493
  307 IGO=2                                                              MA 494
C     STRUCTURE SEGMENT LOADING                                          MA 495
   46 PRINT 146                                                          MA 496
      IF(NLOAD.NE.0) CALL LOAD(LDTYP,LDTAG,LDTAGF,LDTAGT,ZLR,ZLI,ZLC)    MA 497
      IF(NLOAD.EQ.0.AND.NLODF.EQ.0)PRINT 147                             MA 498
      IF(NLOAD.EQ.0.AND.NLODF.NE.0)PRINT 327                             MA 499
C     GROUND PARAMETER                                                   MA 500
      PRINT 148                                                          MA 501
      IF (KSYMP.EQ.1) GO TO 49                                           MA 502
      FRATI=(1.,0.)                                                      MA 503
      IF (IPERF.EQ.1) GO TO 48                                           MA 504
      IF(SIG.LT.0.)SIG=-SIG/(59.96*WLAM)                                 MA 505
      EPSC=CMPLX(EPSR,-SIG*WLAM*59.96)                                   MA 506
      ZRATI=1./CSQRT(EPSC)                                               MA 507
      U=ZRATI                                                            MA 508
      U2=U*U                                                             MA 509
      IF (NRADL.EQ.0) GO TO 47                                           MA 510
      SCRWL=SCRWLT/WLAM                                                  MA 511
```

```
512         SCRWR=SCRWRT/WLAM                                                 MA 512
513         T1=FJ*2567.067/FLOAT(NRADL)                                       MA 513
514         T2=SCRWR*FLOAT(NRADL)                                             MA 514
515         PRINT 170, NRADL,SCRWLT,SCRWRT                                    MA 515
516         PRINT 149                                                         MA 516
517 47      IF(IPERF.EQ.2)GO TO 328                                           MA 517
518         PRINT 391                                                         MA 518
519         GO TO 329                                                         MA 519
520 328     IF(NXA(1).EQ.0)READ(21)AR1,AR2,AR3,EPSCF,DXA,DYA,XSA,YSA,NXA,NYA  MA 520
521         FRATI=(EPSC-1.)/(EPSC+1.)                                         MA 521
522         IF(CABS((EPSCF-EPSC)/EPSC).LT.1.E-3)GO TO 330                     MA 522
523         PRINT 393,EPSCF,EPSC                                              MA 523
524         STOP                                                              MA 524
525 330     PRINT 392                                                         MA 525
526 329     PRINT 150, EPSR,SIG,EPSC                                          MA 526
527         GO TO 50                                                          MA 527
528 48      PRINT 151                                                         MA 528
529         GO TO 50                                                          MA 529
530 49      PRINT 152                                                         MA 530
531 50      CONTINUE                                                          MA 531
532 C * * *                                                                   MA 532
533 C       FILL AND FACTOR PRIMARY INTERACTION MATRIX                        MA 533
534 C                                                                         MA 534
535         CALL SECOND (TIM1)                                                MA 535
536         IF(ICASX.NE.0)GO TO 324                                           MA 536
537         CALL CMSET(NEQ,CM,RKH,IEXK)                                       MA 537
538         CALL SECOND (TIM2)                                                MA 538
539         TIM=TIM2-TIM1                                                     MA 539
540         CALL FACTRS(NPEQ,NEQ,CM,IP,IX,I1,I2,I3,I4)                        MA 540
541         GO TO 323                                                         MA 541
542 C                                                                         MA 542
543 C       N.G.F. - FILL B, C, AND D AND FACTOR D-C(INV(A)B)                  MA 543
544 C                                                                         MA 544
545 324     CALL CMNGF(CM(IB11),CM(IC11),CM(ID11),NPBX,NEQ,NEQ2,RKH,IEXK)     MA 545
546         CALL SECOND (TIM2)                                                MA 546
547         TIM=TIM2-TIM1                                                     MA 547
548         CALL FACGF(CM,CM(IB11),CM(IC11),CM(ID11),CM(IX11),IP,IX,NP,N1,MP, MA 548
549        1M1,NEQ,NEQ2)                                                      MA 549
550 323     CALL SECOND (TIM1)                                                MA 550
551         TIM2=TIM1-TIM2                                                    MA 551
552         PRINT 153, TIM,TIM2                                               MA 552
553         IGO=3                                                             MA 553
554         NTSOL=0                                                           MA 554
555         IF(IFLOW.NE.12)GO TO 53                                           MA 555
556 C       WRITE N.G.F. FILE                                                 MA 556
557 52      CALL GFOUT                                                        MA 557
558         GO TO 14                                                          MA 558
559 C                                                                         MA 559
560 C       EXCITATION SET UP (RIGHT HAND SIDE, -E INC.)                      MA 560
561 C                                                                         MA 561
562 53      NTHIC=1                                                           MA 562
563         NPHIC=1                                                           MA 563
564         INC=1                                                             MA 564
565         NPRINT=0                                                          MA 565
566 54      IF (IXTYP.EQ.0.OR.IXTYP.EQ.5) GO TO 56                            MA 566
567         IF (IPTFLG.LE.0.OR.IXTYP.EQ.4) PRINT 154                          MA 567
568         TMP5=TA*XPR5                                                      MA 568
569         TMP4=TA*XPR4                                                      MA 569
570         IF (IXTYP.NE.4) GO TO 55                                          MA 570
571         TMP1=XPR1/WLAM                                                    MA 571
572         TMP2=XPR2/WLAM                                                    MA 572
573         TMP3=XPR3/WLAM                                                    MA 573
574         TMP6=XPR6/(WLAM*WLAM)                                             MA 574
575         PRINT 156, XPR1,XPR2,XPR3,XPR4,XPR5,XPR6                          MA 575
```

```
      GO TO 56                                                          MA 576
55    TMP1=TA*XPR1                                                      MA 577
      TMP2=TA*XPR2                                                      MA 578
      TMP3=TA*XPR3                                                      MA 579
      TMP6=XPR6                                                         MA 580
      IF (IPTFLG.LE.0) PRINT 155, XPR1,XPR2,XPR3,HPOL(IXTYP),XPR6       MA 581
56    CALL ETMNS (TMP1,TMP2,TMP3,TMP4,TMP5,TMP6,IXTYP,CUR)              MA 582
C                                                                       MA 583
C     MATRIX SOLVING  (NETWK CALLS SOLVES)                              MA 584
C                                                                       MA 585
      IF (NONET.EQ.0.OR.INC.GT.1) GO TO 60                              MA 586
      PRINT 158                                                         MA 587
      ITMP3=0                                                           MA 588
      ITMP1=NTYP(1)                                                     MA 589
      DO 59 I=1,2                                                       MA 590
      IF (ITMP1.EQ.3) ITMP1=2                                           MA 591
      IF (ITMP1.EQ.2) PRINT 159                                         MA 592
      IF (ITMP1.EQ.1) PRINT 160                                         MA 593
      DO 58 J=1,NONET                                                   MA 594
      ITMP2=NTYP(J)                                                     MA 595
      IF ((ITMP2/ITMP1).EQ.1) GO TO 57                                  MA 596
      ITMP3=ITMP2                                                       MA 597
      GO TO 58                                                          MA 598
57    ITMP4=ISEG1(J)                                                    MA 599
      ITMP5=ISEG2(J)                                                    MA 600
      IF (ITMP2.GE.2.AND.X11I(J).LE.0.) X11I(J)=WLAM*SQRT((X(ITMP5)-    MA 601
     1 X(ITMP4))**2+(Y(ITMP5)-Y(ITMP4))**2+(Z(ITMP5)-Z(ITMP4))**2)      MA 602
      PRINT 157, ITAG(ITMP4),ITMP4,ITAG(ITMP5),ITMP5,X11R(J),X11I(J),   MA 603
     1X12R(J),X12I(J),X22R(J),X22I(J),PNET(2*ITMP2-1),PNET(2*ITMP2)     MA 604
58    CONTINUE                                                          MA 605
      IF (ITMP3.EQ.0) GO TO 60                                          MA 606
      ITMP1=ITMP3                                                       MA 607
59    CONTINUE                                                          MA 608
60    CON INUE                                                          MA 609
      IF (INC.GT.1.AND.IPTFLG.GT.0) NPRINT=1                            MA 610
      CALL NETWK(CM,CM(IB11),CM(IC11),CM(ID11),IP,CUR)                  MA 611
      NTSOL=1                                                           MA 612
      IF (IPED.EQ.0) GO TO 61                                           MA 613
      ITMP1=MHZ+4*(MHZ-1)                                               MA 614
      IF (ITMP1.GT.(NORMF-3)) GO TO 61                                  MA 615
      FNORM(ITMP1)=REAL(ZPED)                                           MA 616
      FNORM(ITMP1+1)=AIMAG(ZPED)                                        MA 617
      FNORM(ITMP1+2)=CABS(ZPED)                                         MA 618
      FNORM(ITMP1+3)=CANG(ZPED)                                         MA 619
      IF (IPED.EQ.2) GO TO 61                                           MA 620
      IF (FNORM(ITMP1+2).GT.ZPNORM) ZPNORM=FNORM(ITMP1+2)               MA 621
61    CONTINUE                                                          MA 622
C                                                                       MA 623
C     PRINTING STRUCTURE CURRENTS                                       MA 624
C                                                                       MA 625
      IF(N.EQ.0)GO TO 308                                               MA 626
      IF (IPTFLG.EQ.(-1)) GO TO 63                                      MA 627
      IF (IPTFLG.GT.0) GO TO 62                                         MA 628
      PRINT 161                                                         MA 629
      PRINT 162                                                         MA 630
      GO TO 63                                                          MA 631
62    IF (IPTFLG.EQ.3.OR.INC.GT.1) GO TO 63                             MA 632
      PRINT 163, XPR3,HPOL(IXTYP),XPR6                                  MA 633
63    PLOSS=0.                                                          MA 634
      ITMP1=0                                                           MA 635
      JUMP=IPTFLG+1                                                     MA 636
      DO 69 I=1,N                                                       MA 637
      CURI=CUR(I)*WLAM                                                  MA 638
      CMAG=CABS(CURI)                                                   MA 639
```

```
      PH=CANG(CURI)                                                    MA 640
      IF (NLOAD.EQ.0.AND.NLODF.EQ.0) GO TO 64                          MA 641
      IF (ABS(REAL(ZARRAY(I))).LT.1.E-20) GO TO 64                     MA 642
      PLOSS=PLOSS+.5*CMAG*CMAG*REAL(ZARRAY(I))*SI(I)                   MA 643
64    IF (JUMP) 68,69,65                                               MA 644
65    IF (IPTAG.EQ.0) GO TO 66                                         MA 645
      IF (ITAG(I).NE.IPTAG) GO TO 69                                   MA 646
66    ITMP1=ITMP1+1                                                    MA 647
      IF (ITMP1.LT.IPTAGF.OR.ITMP1.GT.IPTAGT) GO TO 69                 MA 648
      IF (IPTFLG.EQ.0) GO TO 68                                        MA 649
      IF (IPTFLG.LT.2.OR.INC.GT.NORMF) GO TO 67                        MA 650
      FNORM(INC)=CMAG                                                  MA 651
      ISAVE=I                                                          MA 652
67    IF (IPTFLG.NE.3) PRINT 164, XPR1,XPR2,CMAG,PH,I                  MA 653
      GO TO 69                                                         MA 654
68    PRINT 165, I,ITAG(I),X(I),Y(I),Z(I),SI(I),CURI,CMAG,PH           MA 655
69    CONTINUE                                                         MA 656
      IF(IPTFLQ.EQ.(-1))GO TO 308                                      MA 657
      PRINT 315                                                        MA 658
      ITMP1=0                                                          MA 659
      FR=1.E-6/FMHZ                                                    MA 660
      DO 316 I=1,N                                                     MA 661
      IF(IPTFLQ.EQ.(-2))GO TO 318                                      MA 662
      IF(IPTAQ.EQ.0)GO TO 317                                          MA 663
      IF(ITAG(I).NE.IPTAQ)GO TO 316                                    MA 664
317   ITMP1=ITMP1+1                                                    MA 665
      IF(ITMP1.LT.IPTAQF.OR.ITMP1.GT.IPTAQT)GO TO 316                  MA 666
318   CURI=FR*CMPLX(-BII(I),BIR(I))                                    MA 667
      CMAG=CABS(CURI)                                                  MA 668
      PH=CANG(CURI)                                                    MA 669
      PRINT 165,I,ITAG(I),X(I),Y(I),Z(I),SI(I),CURI,CMAG,PH            MA 670
316   CONTINUE                                                         MA 671
308   IF(M.EQ.0)GO TO 310                                              MA 672
      PRINT 197                                                        MA 673
      J=N-2                                                            MA 674
      ITMP1=LD+1                                                       MA 675
      DO 309 I=1,M                                                     MA 676
      J=J+3                                                            MA 677
      ITMP1=ITMP1-1                                                    MA 678
      EX=CUR(J)                                                        MA 679
      EY=CUR(J+1)                                                      MA 680
      EZ=CUR(J+2)                                                      MA 681
      ETH=EX*T1X(ITMP1)+EY*T1Y(ITMP1)+EZ*T1Z(ITMP1)                    MA 682
      EPH=EX*T2X(ITMP1)+EY*T2Y(ITMP1)+EZ*T2Z(ITMP1)                    MA 683
      ETHM=CABS(ETH)                                                   MA 684
      ETHA=CANG(ETH)                                                   MA 685
      EPHM=CABS(EPH)                                                   MA 686
      EPHA=CANG(EPH)                                                   MA 687
309   PRINT 198,I,X(ITMP1),Y(ITMP1),Z(ITMP1),ETHM,ETHA,EPHM,EPHA,EX,EY, MA 688
     1 EZ                                                              MA 689
310   IF (IXTYP.NE.0.AND.IXTYP.NE.5) GO TO 70                          MA 690
      TMP1=PIN-PNLS-PLOSS                                              MA 691
      TMP2=100.*TMP1/PIN                                               MA 692
      PRINT 166, PIN,TMP1,PLOSS,PNLS,TMP2                              MA 693
70    CONTINUE                                                         MA 694
      IGO=4                                                            MA 695
      IF(NCOUP.GT.0)CALL COUPLE(CUR,WLAM)                              MA 696
      IF (IFLOW.NE.7) GO TO 71                                         MA 697
      IF (IXTYP.GT.0.AND.IXTYP.LT.4) GO TO 113                         MA 698
      IF (NFRQ.NE.1) GO TO 120                                         MA 699
      PRINT 135                                                        MA 700
      GO TO 14                                                         MA 701
71    IGO=5                                                            MA 702
C                                                                      MA 703
```

```
704 C     NEAR FIELD CALCULATION                                          MA 704
705 C                                                                     MA 705
706 72    IF (NEAR.EQ.(-1)) GO TO 78                                      MA 706
707       CALL NFPAT                                                      MA 707
708       IF (MHZ.EQ.NFRQ) NEAR=-1                                        MA 708
709       IF (NFRQ.NE.1) GO TO 78                                         MA 709
710       PRINT 135                                                       MA 710
711       GO TO 14                                                        MA 711
712 C                                                                     MA 712
713 C     STANDARD FAR FIELD CALCULATION                                  MA 713
714 C                                                                     MA 714
715 78    IF(IFAR.EQ.-1)GO TO 113                                         MA 715
716       PINR=PIN                                                        MA 716
717       PNLR=PNLS                                                       MA 717
718       CALL RDPAT                                                      MA 718
719 113   IF (IXTYP.EQ.0.OR.IXTYP.GE.4) GO TO 119                         MA 719
720       NTHIC=NTHIC+1                                                   MA 720
721       INC=INC+1                                                       MA 721
722       XPR1=XPR1+XPR4                                                  MA 722
723       IF (NTHIC.LE.NTHI) GO TO 54                                     MA 723
724       NTHIC=1                                                         MA 724
725       XPR1=THETIS                                                     MA 725
726       XPR2=XPR2+XPR5                                                  MA 726
727       NPHIC=NPHIC+1                                                   MA 727
728       IF (NPHIC.LE.NPHI) GO TO 54                                     MA 728
729       NPHIC=1                                                         MA 729
730       XPR2=PHISS                                                      MA 730
731       IF (IPTFLG.LT.2) GO TO 119                                      MA 731
732 C     NORMALIZED RECEIVING PATTERN PRINTED                            MA 732
733       ITMP1=NTHI*NPHI                                                 MA 733
734       IF (ITMP1.LE.NORMF) GO TO 114                                   MA 734
735       ITMP1=NORMF                                                     MA 735
736       PRINT 181                                                       MA 736
737 114   TMP1=FNORM(1)                                                   MA 737
738       DO 115 J=2,ITMP1                                                MA 738
739       IF (FNORM(J).GT.TMP1) TMP1=FNORM(J)                             MA 739
740 115   CONTINUE                                                        MA 740
741       PRINT 182, TMP1,XPR3,HPOL(IXTYP),XPR6,ISAVE                     MA 741
742       DO 118 J=1,NPHI                                                 MA 742
743       ITMP2=NTHI*(J-1)                                                MA 743
744       DO 116 I=1,NTHI                                                 MA 744
745       ITMP3=I+ITMP2                                                   MA 745
746       IF (ITMP3.GT.ITMP1) GO TO 117                                   MA 746
747       TMP2=FNORM(ITMP3)/TMP1                                          MA 747
748       TMP3=DB20(TMP2)                                                 MA 748
749       PRINT 183, XPR1,XPR2,TMP3,TMP2                                  MA 749
750       XPR1=XPR1+XPR4                                                  MA 750
751 116   CONTINUE                                                        MA 751
752 117   XPR1=THETIS                                                     MA 752
753       XPR2=XPR2+XPR5                                                  MA 753
754 118   CONTINUE                                                        MA 754
755       XPR2=PHISS                                                      MA 755
756 119   IF (MHZ.EQ.NFRQ) IFAR=-1                                        MA 756
757       IF (NFRQ.NE.1) GO TO 120                                        MA 757
758       PRINT 135                                                       MA 758
759       GO TO 14                                                        MA 759
760 120   MHZ=MHZ+1                                                       MA 760
761       IF (MHZ.LE.NFRQ) GO TO 42                                       MA 761
762       IF (IPED.EQ.0) GO TO 123                                        MA 762
763       IF(NVQD.LT.1)GO TO 199                                          MA 763
764       PRINT 184,IVQD(NVQD),ZPNORM                                     MA 764
765       GO TO 204                                                       MA 765
766 199   PRINT 184, ISANT(NSANT),ZPNORM                                  MA 766
767 204   ITMP1=NFRQ                                                      MA 767
```

```
      IF (ITMP1.LE.(NORMF/4)) GO TO 121                                  MA 768
      ITMP1=NORMF/4                                                      MA 769
      PRINT 185                                                          MA 770
121   IF (IFRQ.EQ.0) TMP1=FMHZ-(NFRQ-1)*DELFRQ                           MA 771
      IF (IFRQ.EQ.1) TMP1=FMHZ/(DELFRQ**(NFRQ-1))                        MA 772
      DO 122 I=1,ITMP1                                                   MA 773
      ITMP2=I+4*(I-1)                                                    MA 774
      TMP2=FNORM(ITMP2)/ZPNORM                                           MA 775
      TMP3=FNORM(ITMP2+1)/ZPNORM                                         MA 776
      TMP4=FNORM(ITMP2+2)/ZPNORM                                         MA 777
      TMP5=FNORM(ITMP2+3)                                                MA 778
      PRINT 186, TMP1,FNORM(ITMP2),FNORM(ITMP2+1),FNORM(ITMP2+2),        MA 779
     1FNORM(ITMP2+3),TMP2,TMP3,TMP4,TMP5                                 MA 780
      IF (IFRQ.EQ.0) TMP1=TMP1+DELFRQ                                    MA 781
      IF (IFRQ.EQ.1) TMP1=TMP1*DELFRQ                                    MA 782
122   CONTINUE                                                           MA 783
      PRINT 135                                                          MA 784
123   CONTINUE                                                           MA 785
      NFRQ=1                                                             MA 786
      MHZ=1                                                              MA 787
      GO TO 14                                                           MA 788
125   FORMAT (A2,13A6)                                                   MA 789
126   FORMAT  (1H1)                                                      MA 790
127   FORMAT (///,33X,36H**********************************,//,36X,      MA 791
     1 31HNUMERICAL ELECTROMAGNETICS CODE,//,33X,                        MA 792
     2 36H**********************************)                           MA 793
128   FORMAT (////,37X,24H- - - - COMMENTS - - - -,//)                   MA 794
129   FORMAT (25X,13A6)                                                  MA 795
130   FORMAT (///,10X,34HINCORRECT LABEL FOR A COMMENT CARD)             MA 796
135   FORMAT (/////)                                                     MA 797
136   FORMAT (A2,I3,3I5,6E10.3)                                          MA 798
137   FORMAT (1X, 19H***** DATA CARD NO.,I3,3X,A2,1X,I3,3(1X,I5),        MA 799
     1 6(1X,E12.5))                                                      MA 800
138   FORMAT (///,10X,45HFAULTY DATA CARD LABEL AFTER GEOMETRY SECTION)  MA 801
139   FORMAT (///,10X,48HNUMBER OF LOADING CARDS EXCEEDS STORAGE ALLOTTE MA 802
     1D)                                                                 MA 803
140   FORMAT (///,10X,31HDATA FAULT ON LOADING CARD NO.=,I5,5X,11HITAG S MA 804
     1TEP1=,I5,29H  IS GREATER THAN ITAG STEP2=,I5)                      MA 805
141   FORMAT (///,10X,51HNUMBER OF EXCITATION CARDS EXCEEDS STORAGE ALLO MA 806
     1TTED)                                                              MA 807
142   FORMAT (///,10X,48HNUMBER OF NETWORK CARDS EXCEEDS STORAGE ALLOTTE MA 808
     1D)                                                                 MA 809
143   FORMAT(///,10X,79HWHEN MULTIPLE FREQUENCIES ARE REQUESTED, ONLY ON MA 810
     1E NEAR FIELD CARD CAN BE USED -,/,10X,22HLAST CARD READ IS USED)   MA 811
145   FORMAT (////,33X,33H- - - - - - FREQUENCY - - - - - -,//,36X,10HFR MA 812
     1EQUENCY=,E11.4,4H MHZ,/,36X,11HWAVELENGTH=,E11.4,7H METERS)        MA 813
146   FORMAT (///,30X,40H - - - STRUCTURE IMPEDANCE LOADING - - -)       MA 814
147   FORMAT (/ ,35X,26HTHIS STRUCTURE IS NOT LOADED)                    MA 815
148   FORMAT (///,34X,31H- - - ANTENNA ENVIRONMENT - - -,/)              MA 816
149   FORMAT (40X,21HMEDIUM UNDER SCREEN -)                              MA 817
150   FORMAT (40X,27HRELATIVE DIELECTRIC CONST.=,F7.3,/,40X,13HCONDUCTIV MA 818
     1ITY=,E10.3,11H MHOS/METER,/,40X,28HCOMPLEX DIELECTRIC CONSTANT=,   MA 819
     12E12.5)                                                            MA 820
151   FORMAT (  42X,14HPERFECT GROUND)                                   MA 821
152   FORMAT (  44X,10HFREE SPACE)                                       MA 822
153   FORMAT (///,32X,25H- - - MATRIX TIMING - - -,//,24X,5HFILL=,F9.3,  MA 823
     115H SEC.,  FACTOR=,F9.3,5H SEC.)                                   MA 824
154   FORMAT (///,40X,22H- - - EXCITATION - - -)                         MA 825
155   FORMAT (/,4X,10HPLANE WAVE,4X,6HTHETA=,F7.2,11H DEG,  PHI=,F7.2,   MA 826
     1 11H DEG,  ETA=,F7.2,13H DEG,  TYPE -,A6,15H=  AXIAL RATIO=,F6.3) MA 827
156   FORMAT (/,31X,17HPOSITION (METERS),14X,18HORIENTATION (DEG)=/,28X, MA 828
     11HX,12X,1HY,12X,1HZ,10X,5HALPHA,5X,4HBETA,4X,13HDIPOLE MOMENT,//   MA 829
     2 ,4X,14HCURRENT SOURCE,1X,3(3X,F10.5),1X,2(3X,F7.2),4X,F8.3)       MA 830
157   FORMAT (4X,4(I5,1X),6(3X,E11.4),3X,A6,A2)                          MA 831
```

```
  158   FORMAT (///,44X,24H- - - NETWORK DATA - - -)                          MA 832
  159   FORMAT (/,6X,18H- FROM -    - TO -,11X,17HTRANSMISSION LINE,15X,36    MA 833
       1H- -  SHUNT ADMITTANCES (MHOS) -  -,14X,4HLINE,/,6X,21HTAG  SEG.     MA 834
       2   TAG  SEG.,6X,9HIMPEDANCE,6X,6HLENGTH,12X,11H- END ONE -,17X,11H   MA 835
       3- END TWO -,12X,4HTYPE,/    ,6X,21HNO.   NO.   NO.   NO.,9X,4HOHMS   MA 836
       4,8X,6HMETERS,9X, 4HREAL,10X,5HIMAG.,9X,4HREAL,10X,5HIMAG.)           MA 837
  160   FORMAT (/,6X,8H- FROM -,4X,6H- TO -,26X,45H- - ADMITTANCE MATRIX      MA 838
       1 ELEMENTS (MHOS) - -,/    ,6X,21HTAG SEG.   TAG SEG.,13X,9H(ON       MA 839
       2E,ONE),19X,    9H(ONE,TWO),19X,9H(TWO,TWO),/ ,6X,21HNO.   NO.   NO  MA 840
       3.   NO.,8X,4HREAL,10X,5HIMAG.,9X,4HREAL,10X,5HIMAG.,9X,4HREAL,      MA 841
       4 10X,5HIMAG.)                                                        MA 842
  161   FORMAT (///,29X,33H- - - CURRENTS AND LOCATION - - -,//,33X,24HDIS    MA 843
       1TANCES IN WAVELENGTHS)                                               MA 844
  162   FORMAT (  //,2X,4HSEG.,2X,3HTAG,4X,21HCOORD. OF SEG. CENTER,5X,      MA 845
       1 4HSEG.,12X,26H- - - CURRENT (AMPS) - - -,/,2X,3HNO.,3X,3HNO.,       MA 846
       2 5X,1HX,8X,1HY,8X,1HZ,6X,6HLENGTH,5X,4HREAL,8X,5HIMAG.,7X,4HMAG.,    MA 847
       3 8X,5HPHASE)                                                         MA 848
  163   FORMAT (///,33X,40H- - - RECEIVING PATTERN PARAMETERS - - -,/  ,43    MA 849
       1X,4HETA=,F7.2,8H DEGREES,/,43X,6HTYPE -,A6,/,43X,12HAXIAL RATIO=,    MA 850
       2 F6.3,//    ,11X,5HTHETA,6X,3HPHI,10X,13H- CURRENT  -,9X,3HSEG,/    MA 851
       3,11X,5H(DEG),5X,5H(DEG),7X,9HMAGNITUDE,4X,5HPHASE,6X,3HNO.,/)        MA 852
  164   FORMAT (10X,2(F7.2,3X),1X,E11.4,3X,F7.2,4X,I5)                        MA 853
  165   FORMAT (1X,2I5,3F9.4,F9.5,1X,3E12.4,F9.3)                             MA 854
  166   FORMAT (///,40X,24H- - - POWER BUDGET - - -,//    ,43X,15HINPUT PO    MA 855
       1WER   =,E11.4,6H WATTS,/ ,43X,15HRADIATED POWER=,E11.4,6H WATTS,/    MA 856
       2 ,43X,15HSTRUCTURE LOSS=,E11.4,6H WATTS,/ ,43X,15HNETWORK LOSS  =,   MA 857
       3  E11.4,6H WATTS,/,43X,15HEFFICIENCY    =, F7.2,8H PERCENT)          MA 858
  170   FORMAT (40X,25HRADIAL WIRE GROUND SCREEN,/,40X,   I5,6H WIRES,/,40    MA 859
       1X,12HWIRE LENGTH=,F8.2,7H METERS,/,40X,12HWIRE RADIUS=,E10.3,7H ME   MA 860
       2TERS)                                                                MA 861
  181   FORMAT (///,4X,51HRECEIVING PATTERN STORAGE TOO SMALL,ARRAY TRUNCA    MA 862
       1TED)                                                                 MA 863
  182   FORMAT (///,32X,40H- - - NORMALIZED RECEIVING PATTERN - - -,/,41X,    MA 864
       1 21HNORMALIZATION FACTOR=,E11.4,/,41X,4HETA=,F7.2,8H DEGREES,/,41X   MA 865
       2,6HTYPE -,A6,/,41X,12HAXIAL RATIO=,F6.3,/,41X,12HSEGMENT NO.=,I5,/   MA 866
       3/,21X,5HTHETA,6X,3HPHI,9X,13H- PATTERN  -,/,21X,5H(DEG),5X,5H(DEG    MA 867
       4),8X,2HDB,8X,9HMAGNITUDE,/)                                          MA 868
  183   FORMAT (20X,2(F7.2,3X),1X,F7.2,4X,E11.4)                              MA 869
  184   FORMAT (///,36X,32H- - - INPUT IMPEDANCE DATA - - -,/   ,45X,18HSO    MA 870
       1URCE SEGMENT NO.,I4,/  ,45X,21HNORMALIZATION FACTOR=,E12.5,//        MA 871
       2,7X,5HFREQ.,13X,34H- - UNNORMALIZED IMPEDANCE - -,21X,   32H-        MA 872
       3 - NORMALIZED IMPEDANCE - -,/    ,19X,10HRESISTANCE,4X,9HREACTA      MA 873
       4NCE,6X,9HMAGNITUDE,4X,5HPHASE,7X,10HRESISTANCE,4X,9HREACTANCE,6X,    MA 874
       5 9HMAGNITUDE,4X,5HPHASE,/    ,8X,3HMHZ,11X,4HOHMS,10X,4HOHMS,11X,    MA 875
       6 4HOHMS,5X,7HDEGREES,47X,7HDEGREES,/)                                MA 876
  185   FORMAT (///,4X,62HSTORAGE FOR IMPEDANCE NORMALIZATION TOO SMALL, A    MA 877
       1RRAY TRUNCATED)                                                      MA 878
  186   FORMAT (3X,F9.3,2X,2(2X,E12.5),3X,E12.5,2X,F7.2,2X,2(2X,E12.5),3X,    MA 879
       1 E12.5,2X,F7.2)                                                      MA 880
  196   FORMAT(   ////,20X,55HAPPROXIMATE INTEGRATION EMPLOYED FOR SEGMENT    MA 881
       1S MORE THAN,F8.3,18H WAVELENGTHS APART)                              MA 882
  197   FORMAT(   ///,41X,38H- - - - SURFACE PATCH CURRENTS - - - -,//,       MA 883
       1 50X,23HDISTANCE IN WAVELENGTHS,/,50X,21HCURRENT IN AMPS/METER,      MA 884
       1 //,28X,26H- - SURFACE COMPONENTS - -,19X,34H- - - RECTANGULAR COM   MA 885
       1PONENTS - - -,/,6X,12HPATCH CENTER,6X,16HTANGENT VECTOR 1,3X,        MA 886
       116HTANGENT VECTOR 2,11X,1HX,19X,1HY,19X,1HZ,/,5X,1HX,6X,1HY,6X,      MA 887
       11HZ,5X,4HMAG.,7X,5HPHASE,3X,4HMAG.,7X,5HPHASE,3(4X,4HREAL,6X,        MA 888
       1 6HIMAG. ))                                                          MA 889
  198   FORMAT(1X,I4,/,1X,3F7.3,2(E11.4,F8.2),6E10.2)                         MA 890
  201   FORMAT(/,11H RUN TIME =,F10.3)                                        MA 891
  315   FORMAT(///,34X,28H- - - CHARGE DENSITIES - - -,//,36X,                MA 892
       1 24HDISTANCES IN WAVELENGTHS,///,2X,4HSEG.,2X,3HTAG,4X,              MA 893
       2 21HCOORD. OF SEG. CENTER,5X,4HSEG.,10X,                             MA 894
       3 31HCHARGE DENSITY (COULOMBS/METER),/,2X,3HNO.,3X,3HNO.,5X,1HX,8X,   MA 895
```

```
      4 1HY,8X,1HZ,6X,6HLENGTH,5X,4HREAL,8X,5HIMAG.,7X,4HMAG.,8X,5HPHASE) MA 896
  321  FORMAT( /,20X,42HTHE EXTENDED THIN WIRE KERNEL WILL BE USED)       MA 897
  303  FORMAT(/,9H ERROR - ,A2,32H CARD IS NOT ALLOWED WITH N.G.F.)       MA 898
  327  FORMAT(/,35X,31H LOADING ONLY IN N.G.F. SECTION)                   MA 899
  302  FORMAT(48H ERROR - N.G.F. IN USE.  CANNOT WRITE NEW N.G.F.)        MA 900
  313  FORMAT(/,62H NUMBER OF SEGMENTS IN COUPLING CALCULATION (CP) EXCEE MA 901
     1DS LIMIT)                                                          MA 902
  390  FORMAT(78H RADIAL WIRE G. S. APPROXIMATION MAY NOT BE USED WITH SO MA 903
     1MMERFELD GROUND OPTION)                                            MA 904
  391  FORMAT(40X,52HFINITE GROUND.  REFLECTION COEFFICIENT APPROXIMATION MA 905
     1)                                                                  MA 906
  392  FORMAT(40X,35HFINITE GROUND.  SOMMERFELD SOLUTION)                 MA 907
  393  FORMAT(/,29H ERROR IN GROUND PARAMETERS -,/,41H COMPLEX DIELECTRIC MA 908
     1 CONSTANT FROM FILE IS,2E12.5,/,32X,9HREQUESTED,2E12.5)            MA 909
       END                                                               MA 910-
```

ARC

PURPOSE

To fill COMMON/DATA/ with segment coordinates for a circular arc of segments.

METHOD

The formal parameters specify the number of segments, radius of the arc, starting angle, final angle and wire radius. Segment coordinates are computed for the arc in the x, z plane with a left hand rotation about the y axis.

SYMBOL DICTIONARY

ANG	= angle of point on the arc (radians, zero on x axis)
ANG1	= angle at first end
ANG2	= angle at second end
DANG	= angle covered by each segment
IST	= number of initial segment
ITG	= tag number assigned to each segment
NS	= number of segments
RAD	= wire radius
RADA	= arc radius
TA	= π/180
XS1	= x coordinate of first end of segment
XS2	= x coordinate of second end of segment
ZS1	= z coordinate of first end of segment
ZS2	= z coordinate of second end of segment

CONSTANTS

.01745329252	= π/180
360.00001	= test for angle greater than 360 degrees

```
      SUBROUTINE ARC (ITG,NS,RADA,ANG1,ANG2,RAD)                        AR   1
C                                                                       AR   2
C     ARC GENERATES SEGMENT GEOMETRY DATA FOR AN ARC OF NS SEGMENTS     AR   3
C                                                                       AR   4
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 AR   5
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( AR   6
     2300),WLAM,IPSYM                                                   AR   7
      DIMENSION X2(1), Y2(1), Z2(1)                                     AR   8
      EQUIVALENCE (X2,SI), (Y2,ALP), (Z2,BET)                           AR   9
      DATA TA/.01745329252/                                             AR  10
      IST=N+1                                                           AR  11
      N=N+NS                                                            AR  12
      NP=N                                                              AR  13
      MP=M                                                              AR  14
      IPSYM=0                                                           AR  15
      IF (NS.LT.1) RETURN                                               AR  16
      IF (ABS(ANG2-ANG1).LT.360.00001) GO TO 1                          AR  17
      PRINT 3                                                           AR  18
      STOP                                                              AR  19
    1 ANG=ANG1*TA                                                       AR  20
      DANG=(ANG2-ANG1)*TA/NS                                            AR  21
      XS1=RADA*COS(ANG)                                                 AR  22
      ZS1=RADA*SIN(ANG)                                                 AR  23
      DO 2 I=IST,N                                                      AR  24
      ANG=ANG+DANG                                                      AR  25
      XS2=RADA*COS(ANG)                                                 AR  26
      ZS2=RADA*SIN(ANG)                                                 AR  27
      X(I)=XS1                                                          AR  28
      Y(I)=0.                                                           AR  29
      Z(I)=ZS1                                                          AR  30
      X2(I)=XS2                                                         AR  31
      Y2(I)=0.                                                          AR  32
      Z2(I)=ZS2                                                         AR  33
      XS1=XS2                                                           AR  34
      ZS1=ZS2                                                           AR  35
      BI(I)=RAD                                                         AR  36
    2 ITAG(I)=ITG                                                       AR  37
      RETURN                                                            AR  38
C                                                                       AR  39
    3 FORMAT (40H ERROR -- ARC ANGLE EXCEEDS 360. DEGREES)              AR  40
      END                                                               AR  41
```

ATGN2

PURPOSE

To return zero when both arguments of a two-argument arctangent function are zero. (Most standard arctangent functions give an error return when both arguments are zero.)

METHOD

System function ATAN2 is used except when both arguments are zero, in which case the value zero is returned. The value returned is the angle (in radians) whose sine is X and cosine is Y.

SYMBOL DICTIONARY

X = first argument

Y = second argument

CODE LISTING

```
      FUNCTION ATGN2 (X,Y)                                              AT   1
C                                                                       AT   2
C     ATGN2 IS ARCTANGENT FUNCTION MODIFIED TO RETURN 0. WHEN X=Y=0.    AT   3
C                                                                       AT   4
      IF (X) 3,1,3                                                      AT   5
1     IF (Y) 3,2,3                                                      AT   6
2     ATGN2=0.                                                          AT   7
      RETURN                                                            AT   8
3     ATGN2=ATAN2(X,Y)                                                  AT   9
      RETURN                                                            AT  10
      END                                                               AT  11-
```

BLCKOT

PURPOSE

To control the writing and reading of matrix blocks on files for the out-of-core matrix solution. The routine also checks for the end-of-file condition during reading.

METHOD

The routine uses a binary read and write with implied DO loops for reading and writing variable length strings into and out of various core locations. The end-of-file condition is checked by a call to function ENF. If an unexpected end of file is detected (governed by NEOF) the program stops.

CODING

BL9 - BL12 Write a record on file NUNIT.

BL14 - BL20 Read NBLKS records from NUNIT, and check for end of file.

BL21 - BL24 Code if end of file detected.

SYMBOL DICTIONARY

AR = matrix array

ENF = external function (checks end-of-file condition)

I = DO loop index

I1, I2 = implied DO loop limits, inclusive matrix locations written from or read into

J = implied DO index

NBLKS = number of records to be read

NEOF = EOF check flag, also used to trace the call to BLCKOT

NUNIT = file number

CONSTANT

777 = NEOF when EOF is expected by calling program

```
      SUBROUTINE BLCKOT (AR,NUNIT,IX1,IX2,NBLKS,NEOF)                    BL    1
C                                                                        BL    2
C     BLCKOT CONTROLS THE READING AND WRITING OF MATRIX BLOCKS ON FILES  BL    3
C     FOR THE OUT-OF-CORE MATRIX SOLUTION.                               BL    4
C                                                                        BL    5
      LOGICAL ENF                                                        BL    6
      COMPLEX AR                                                         BL    7
      DIMENSION AR(1)                                                    BL    8
      I1=(IX1+1)/2                                                       BL    9
      I2=(IX2+1)/2                                                       BL   10
1     WRITE (NUNIT) (AR(J),J=I1,I2)                                      BL   11
      RETURN                                                             BL   12
      ENTRY BLCKIN                                                       BL   13
      I1=(IX1+1)/2                                                       BL   14
      I2=(IX2+1)/2                                                       BL   15
      DO 2 I=1,NBLKS                                                     BL   16
      READ (NUNIT) (AR(J),J=I1,I2)                                       BL   17
      IF (ENF(NUNIT)) GO TO 3                                            BL   18
2     CONTINUE                                                           BL   19
      RETURN                                                             BL   20
3     PRINT 4, NUNIT,NBLKS,NEOF                                          BL   21
      IF (NEOF.NE.777) STOP                                              BL   22
      NEOF=0                                                             BL   23
      RETURN                                                             BL   24
C                                                                        BL   25
4     FORMAT (13H  EOF ON UNIT,I3,8H  NBLKS= ,I3,8H  NEOF= ,I5)          BL   26
      END                                                                BL   27-
```

CABC

PURPOSE

To compute the coefficients in the current function on each segment, given the basis function amplitudes. Surface current components are also computed.

METHOD

The total current on segment i is

$$I_i(s) = A_i + B_i \sin [k(s - s_i)] + C_i \cos [k(s - s_i)] ,$$

where s is distance along the wire, and $s = s_i$ at the center of segment i. The coefficients A_i, B_i, and C_i are the sums of the corresponding coefficients in the portion of each basis function that extends onto segment i.

CODING

CB35 Call to TBF computes components of basis function I.

CB36 - CB43 The basis function components are multiplied by the basis function amplitude from array CURX and summed for each segment.

CB45 - CB63 For a current slope discontinuity source, the special basis function with discontinuous slope, from which the exciting electric field was computed, is recomputed and added to the current coefficients. The call to TBF, with the second argument zero and ICON1(I) temporarily zero, computes a basis function going to zero with non-zero derivative at end one of segment I.

CB64 - CB65 Total current at the center of each segment is computed and stored in place of the basis function amplitudes.

CB66 - CB79 The $\hat{t}_1$ and $\hat{t}_2$ components of surface current for each patch are expanded to x, y, and z components.

SYMBOL DICTIONARY

AR, AI = real and imaginary parts of the basis function amplitude

CCJ, CCX = -j/60

CS1, CS2 = $\hat{t}_1$ and $\hat{t}_2$ components of surface current on a patch

CURD = amplitude of the special basis function for a current slope discontinuity source

CURX = input array of basis function amplitudes that are replaced by values of current at segment centers

J = number of a segment onto which a basis function extends

JCO1, JCO2 = array locations of the $\hat{t}_1$ and $\hat{t}_2$ surface current components for a patch

JX = DO loop index; temporary storage of connection number

K = array location for patch geometry data

SH = (half segment length)/λ

TP = 2π

```
      SUBROUTINE CABC (CURX)                                                CB   1
C                                                                           CB   2
C     CABC COMPUTES COEFFICIENTS OF THE CONSTANT (A), SINE (B), AND         CB   3
C     COSINE (C) TERMS IN THE CURRENT INTERPOLATION FUNCTIONS FOR THE       CB   4
C     CURRENT VECTOR CUR.                                                   CB   5
C                                                                           CB   6
      COMPLEX CUR,CURX,VQDS,CURD,CCJ,VSANT,VQD,CS1,CS2                      CB   7
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300    CB   8
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX(    CB   9
     2300),WLAM,IPSYM                                                       CB  10
      COMMON /CRNT/ AIR(300),AII(300),BIR(300),BII(300),CIR(300),CII(300    CB  11
     1),CUR(900)                                                            CB  12
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(50),NSCON,IP    CB  13
     1CON(10),NPCON                                                         CB  14
      COMMON /VSORC/ VQD(30),VSANT(30),VQDS(30),IVQD(30),ISANT(30),IQDS(    CB  15
     130),NVQD,NSANT,NQDS                                                   CB  16
      COMMON /ANGL/ SALP(300)                                               CB  17
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1)              CB  18
      DIMENSION CURX(1), CCJX(2)                                            CB  19
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON    CB  20
     12), (T2Z,ITAG)                                                        CB  21
      EQUIVALENCE (CCJ,CCJX)                                                CB  22
      DATA TP/6.283185308/,CCJX/0.,-0.01666666667/                          CB  23
      IF (N.EQ.0) GO TO 6                                                   CB  24
      DO 1 I=1,N                                                            CB  25
      AIR(I)=0.                                                             CB  26
      AII(I)=0.                                                             CB  27
      BIR(I)=0.                                                             CB  28
      BII(I)=0.                                                             CB  29
      CIR(I)=0.                                                             CB  30
    1 CII(I)=0.                                                             CB  31
      DO 2 I=1,N                                                            CB  32
      AR=REAL(CURX(I))                                                      CB  33
      AI=AIMAG(CURX(I))                                                     CB  34
      CALL TBF (I,1)                                                        CB  35
      DO 2 JX=1,JSNO                                                        CB  36
      J=JCO(JX)                                                             CB  37
      AIR(J)=AIR(J)+AX(JX)*AR                                               CB  38
      AII(J)=AII(J)+AX(JX)*AI                                               CB  39
      BIR(J)=BIR(J)+BX(JX)*AR                                               CB  40
      BII(J)=BII(J)+BX(JX)*AI                                               CB  41
      CIR(J)=CIR(J)+CX(JX)*AR                                               CB  42
    2 CII(J)=CII(J)+CX(JX)*AI                                               CB  43
      IF (NQDS.EQ.0) GO TO 4                                                CB  44
      DO 3 IS=1,NQDS                                                        CB  45
      I=IQDS(IS)                                                            CB  46
      JX=ICON1(I)                                                           CB  47
      ICON1(I)=0                                                            CB  48
      CALL TBF (I,0)                                                        CB  49
      ICON1(I)=JX                                                           CB  50
      SH=SI(I)*.5                                                           CB  51
      CURD=CCJ*VQDS(IS)/((ALOG(2.*SH/BI(I))-1.)*(BX(JSNO)*COS(TP*SH)+CX(    CB  52
     1JSNO)*SIN(TP*SH))*WLAM)                                               CB  53
      AR=REAL(CURD)                                                         CB  54
      AI=AIMAG(CURD)                                                        CB  55
      DO 3 JX=1,JSNO                                                        CB  56
      J=JCO(JX)                                                             CB  57
      AIR(J)=AIR(J)+AX(JX)*AR                                               CB  58
      AII(J)=AII(J)+AX(JX)*AI                                               CB  59
      BIR(J)=BIR(J)+BX(JX)*AR                                               CB  60
      BII(J)=BII(J)+BX(JX)*AI                                               CB  61
      CIR(J)=CIR(J)+CX(JX)*AR                                               CB  62
    3 CII(J)=CII(J)+CX(JX)*AI                                               CB  63
    4 DO 5 I=1,N                                                            CB  64
```

```
 5      CURX(I)=CMPLX(AIR(I)+CIR(I),AII(I)+CII(I))                        CB  65
 6      IF (M.EQ.0) RETURN                                                CB  66
C       CONVERT SURFACE CURRENTS FROM T1,T2 COMPONENTS TO X,Y,Z COMPONENTS CB  67
        K=LD-M                                                            CB  68
        JCO1=N+2*M+1                                                      CB  69
        JCO2=JCO1+M                                                       CB  70
        DO 7 I=1,M                                                        CB  71
        K=K+1                                                             CB  72
        JCO1=JCO1-2                                                       CB  73
        JCO2=JCO2-3                                                       CB  74
        CS1=CURX(JCO1)                                                    CB  75
        CS2=CURX(JCO1+1)                                                  CB  76
        CURX(JCO2)=CS1*T1X(K)+CS2*T2X(K)                                  CB  77
        CURX(JCO2+1)=CS1*T1Y(K)+CS2*T2Y(K)                                CB  78
 7      CURX(JCO2+2)=CS1*T1Z(K)+CS2*T2Z(K)                                CB  79
        RETURN                                                            CB  80
        END                                                               CB  81-
```

CANG

PURPOSE

To calculate the phase angle of a complex number in degrees.

METHOD

$z = x + jy$

$\phi = [\arctan (y/x)]\ 57.29577951$

SYMBOL DICTIONARY

AIMAG = external routine (imaginary part of complex number)

ATGN2 = external routine (arctan for all quadrants)

CANG = ϕ

REAL = external routine (real part of a complex number)

Z = input complex quantity

CONSTANT

57.29577951 conversion from radians to degrees

CODE LISTING

```
1       FUNCTION CANG (Z)                                              CA   1
2 C                                                                    CA   2
3 C     CANG RETURNS THE PHASE ANGLE OF A COMPLEX NUMBER IN DEGREES.   CA   3
4 C                                                                    CA   4
5       COMPLEX Z                                                      CA   5
6       CANG=ATGN2(AIMAG(Z),REAL(Z))*57.29577951                       CA   6
7       RETURN                                                         CA   7
8       END                                                            CA   8-
```

CMNGF

PURPOSE

To compute and store the matrices B, C and D for the NGF solution.

METHOD

The structure of matrices B, C and D is described in Section VI. The coding to fill these matrices is involved due to their complex structure, as shown in Figure 12 of Section VI. The complexity is increased by the need to divide the matrices into blocks of rows when they are stored on files (see Section VII).

Much of the coding in CMNGF has to do with connections between new and NGF segments and patches. When a new segment or patch connects to a NGF segment the basis function associated with the NGF segment is modified due to the new junction condition. The amplitude of the modified basis function is a new unknown associated with the B' and D' sections of the matrix. The modified basis function may extend onto other NGF segments that may or may not connect directly to new segments. Also, the basis function of the new segment extends onto the NGF segment to which it connects. Hence fields must be computed for the currents on some NGF segments as well as all new segments.

Comments in the code should be of some help in understanding the procedure. The notation D(WS) in the comments corresponds to D_{sw} in Figure 12. Some parts of the code are explained below.

CG61 - CG70 TRIO computes the components of all basis functions on segment J, where J is a new segment, and stores the coefficients in COMMON/SEGJ/. The array JCO contains the basis-function numbers which ordinarily are the matrix columns associated with the basis functions. If the basis function is for a new segment then JCO is set at CG66 to the column relative to the beginning of the matrix B. If the basis function is for a NGF segment modified by the connection, then JCO is set at CG68 to the column in B'_{ww} relative to the beginning of B. Thus the calls to CMWW and CMWS may store contributions in B'_{ww} and B'_{sw} as well as B_{ww} and B_{sw}.

CG90 - CG108 In this section the fields are evaluated for NGF segments that connect to new segments or patches. TRIO finds all basis functions that contribute to the current on the segment. For a component of a new basis function IR is set to the column in B_{ww} at CG95. For a component of a modified basis function IR is set to the column in B'_{ww}, relative to the start of B, at CG99. If the basis function component is for a NGF basis function that has not been modified the test at CG98 skips to the end of the loop. The arrays in COMMON/SEGJ/ are adjusted from CG101 to CG104 so that CMWW and CMWS will store the matrix element contributions in the correct locations.

CG109 - CG119 If a NGF segment connects to a new segment on one end and to a NGF patch on the opposite end the modified basis function extends onto the patch as a singular component of the patch current. The field due to this component on the patch is added to the matrix element of the modified basis function at CG119.

CG122-CG136 This is similar to CG90 to CG108, but evaluates fields of NGF segments that get contributions from modified basis functions, but do not connect directly to new segments. TBF is called, rather than TRIO to compute modified basis function J on all segments on which it exists. New segments and NGF segments for which contributions have already been evaluated are skipped at CG133 and CG134.

CG165 - CG263 Filling C and D is similar to that for B but fields must be evaluated for all NGF segments and patches as well as new segments and patches.

SYMBOL DICTIONARY

CB = array for matrix B

CC = array for matrix C

CD = array for matrix D

IEXKX = flag to select extended thin-wire kernel

MIEQ = number of patch equations in NGF

MEQ = total number of patch equations

NB = row dimension of CB. CB will contain only one block of B when ICASX = 3 or 4

NC = row dimension of CC (C transposed)

ND = row dimension of CD (D transposed)

NEQN = starting column of D_{ws}, relative to start of C

NEQP = starting column of zeros after D'_{ww}, relative to start of D

NEQS = starting column of D'_{ww}, relative to start of D

NEQSP = starting column of D'_{ww}, relative to start of C

RKHX = minimum range for using the lumped current approximation for the field of a segment

```
      SUBROUTINE CMNGF (CB,CC,CD,NB,NC,ND,RKHX,IEXKX)                    CG   1
C     CMNGF FILLS INTERACTION MATRICIES B, C, AND D FOR N.G.F. SOLUTION  CG   2
      COMPLEX CB,CC,CD,ZARRAY,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC        CG   3
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 CG   4
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( CG   5
     2300),WLAM,IPSYM                                                   CG   6
      COMMON /ZLOAD/ ZARRAY(300),NLOAD,NLODF                            CG   7
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(30),NSCON,IP CG   8
     1CON(10),NPCON                                                     CG   9
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ CG  10
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                           CG  11
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I CG  12
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                               CG  13
      DIMENSION CB(NB,1), CC(NC,1), CD(ND,1)                            CG  14
      RKH=RKHX                                                          CG  15
      IEXK=IEXKX                                                        CG  16
      M1EQ=2*M1                                                         CG  17
      M2EQ=M1EQ+1                                                       CG  18
      MEQ=2*M                                                           CG  19
      NEQP=ND-NPCON*2                                                   CG  20
      NEQS=NEQP-NSCON                                                   CG  21
      NEQSP=NEQS+NC                                                     CG  22
      NEQN=NC+N-N1                                                      CG  23
      ITX=1                                                             CG  24
      IF (NSCON.GT.0) ITX=2                                             CG  25
      IF (ICASX.EQ.1) GO TO 1                                           CG  26
      REWIND 12                                                         CG  27
      REWIND 14                                                         CG  28
      REWIND 15                                                         CG  29
      IF (ICASX.GT.2) GO TO 5                                           CG  30
1     DO 4 J=1,ND                                                       CG  31
      DO 2 I=1,ND                                                       CG  32
2     CD(I,J)=(0.,0.)                                                   CG  33
      DO 3 I=1,NB                                                       CG  34
      CB(I,J)=(0.,0.)                                                   CG  35
3     CC(I,J)=(0.,0.)                                                   CG  36
4     CONTINUE                                                          CG  37
5     IST=N-N1+1                                                        CG  38
      IT=NPBX                                                           CG  39
      ISV=-NPBX                                                         CG  40
C     LOOP THRU 24 FILLS B.  FOR ICASX=1 OR 2 ALSO FILLS D(WW), D(WS)   CG  41
      DO 24 IBLK=1,NBBX                                                 CG  42
      ISV=ISV+NPBX                                                      CG  43
      IF (IBLK.EQ.NBBX) IT=NLBX                                         CG  44
      IF (ICASX.LT.3) GO TO 7                                           CG  45
      DO 6 J=1,ND                                                       CG  46
      DO 6 I=1,IT                                                       CG  47
6     CB(I,J)=(0.,0.)                                                   CG  48
7     I1=ISV+1                                                          CG  49
      I2=ISV+IT                                                         CG  50
      IN2=I2                                                            CG  51
      IF (IN2.GT.N1) IN2=N1                                             CG  52
      IM1=I1-N1                                                         CG  53
      IM2=I2-N1                                                         CG  54
      IF (IM1.LT.1) IM1=1                                               CG  55
      IMX=1                                                             CG  56
      IF (I1.LE.N1) IMX=N1-I1+2                                         CG  57
      IF (N2.GT.N) GO TO 12                                             CG  58
C     FILL B(WW),B(WS).  FOR ICASX=1,2 FILL D(WW),D(WS)                 CG  59
      DO 11 J=N2,N                                                      CG  60
      CALL TRIO (J)                                                     CG  61
      DO 9 I=1,JSNO                                                     CG  62
      JSS=JCO(I)                                                        CG  63
      IF (JSS.LT.N2) GO TO 8                                            CG  64
```

```
C     SET JCO WHEN SOURCE IS NEW BASIS FUNCTION ON NEW SEGMENT
      JCO(I)=JSS-N1
      GO TO 9
C     SOURCE IS PORTION OF MODIFIED BASIS FUNCTION ON NEW SEGMENT
8     JCO(I)=NEQS+ICONX(JSS)
9     CONTINUE
      IF (I1.LE.IN2) CALL CMWW (J,I1,IN2,CB,NB,CB,NB,0)
      IF (IM1.LE.IM2) CALL CMWS (J,IM1,IM2,CB(IMX,1),NB,CB,NB,0)
      IF (ICASX.GT.2) GO TO 11
      CALL CMWW (J,N2,N,CD,ND,CD,ND,1)
      IF (M2.LE.M) CALL CMWS (J,M2EQ,MEQ,CD(1,IST),ND,CD,ND,1)
C     LOADING IN D(WW)
      IF (NLOAD.EQ.0) GO TO 11
      IR=J-N1
      EXK=ZARRAY(J)
      DO 10 I=1,JSNO
      JSS=JCO(I)
10    CD(JSS,IR)=CD(JSS,IR)-(AX(I)+CX(I))*EXK
11    CONTINUE
12    IF (NSCON.EQ.0) GO TO 20
C     FILL B(WW)PRIME
      DO 19 I=1,NSCON
      J=ISCON(I)
C     SOURCES ARE NEW OR MODIFIED BASIS FUNCTIONS ON OLD SEGMENTS WHICH
C     CONNECT TO NEW SEGMENTS
      CALL TRIO (J)
      JSS=0
      DO 15 IX=1,JSNO
      IR=JCO(IX)
      IF (IR.LT.N2) GO TO 13
      IR=IR-N1
      GO TO 14
13    IR=ICONX(IR)
      IF (IR.EQ.0) GO TO 15
      IR=NEQS+IR
14    JSS=JSS+1
      JCO(JSS)=IR
      AX(JSS)=AX(IX)
      BX(JSS)=BX(IX)
      CX(JSS)=CX(IX)
15    CONTINUE
      JSNO=JSS
      IF (I1.LE.IN2) CALL CMWW (J,I1,IN2,CB,NB,CB,NB,0)
      IF (IM1.LE.IM2) CALL CMWS (J,IM1,IM2,CB(IMX,1),NB,CB,NB,0)
C     SOURCE IS SINGULAR COMPONENT OF PATCH CURRENT THAT IS PART OF
C     MODIFIED BASIS FUNCTION FOR OLD SEGMENT THAT CONNECTS TO A NEW
C     SEGMENT ON END OPPOSITE PATCH.
      IF (I1.LE.IN2) CALL CMSW (J,I,I1,IN2,CB,CB,0,NB,-1)
      IF (NLODF.EQ.0) GO TO 17
      JX=J-ISV
      IF (JX.LT.1.OR.JX.GT.IT) GO TO 17
      EXK=ZARRAY(J)
      DO 16 IX=1,JSNO
      JSS=JCO(IX)
16    CB(JX,JSS)=CB(JX,JSS)-(AX(IX)+CX(IX))*EXK
C     SOURCES ARE PORTIONS OF MODIFIED BASIS FUNCTION J ON OLD SEGMENTS
C     EXCLUDING OLD SEGMENTS THAT DIRECTLY CONNECT TO NEW SEGMENTS.
17    CALL TBF (J,1)
      JSX=JSNO
      JSNO=1
      IR=JCO(1)
      JCO(1)=NEQS+I
      DO 18 IX=1,JSX
      IF (I*.EQ.1) GO TO 18
```

```
      IR=JCO(IX)                                                        CG 129
      AX(1)=AX(IX)                                                      CG 130
      BX(1)=BX(IX)                                                      CG 131
      CX(1)=CX(IX)                                                      CG 132
   18 IF (IR.GT.N1) GO TO 19                                            CG 133
      IF (ICONX(IR).NE.0) GO TO 19                                      CG 134
      IF (I1.LE.IN2) CALL CMWW (IR,I1,IN2,CB,NB,CB,NB,0)                CG 135
      IF (IM1.LE.IM2) CALL CMWS (IR,IM1,IM2,CB(IMX,1),NB,CB,NB,0)       CG 136
C     LOADING FOR B(WW)PRIME                                            CG 137
      IF (NLODF.EQ.0) GO TO 19                                          CG 138
      JX=IR-ISV                                                         CG 139
      IF (JX.LT.1.OR.JX.GT.IT) GO TO 19                                 CG 140
      EXK=ZARRAY(IR)                                                    CG 141
      JSS=JCO(1)                                                        CG 142
      CB(JX,JSS)=CB(JX,JSS)-(AX(1)+CX(1))*EXK                           CG 143
   19 CONTINUE                                                          CG 144
   20 IF (NPCON.EQ.0) GO TO 22                                          CG 145
      JSS=NEQP                                                          CG 146
C     FILL B(SS)PRIME TO SET OLD PATCH BASIS FUNCTIONS TO ZERO FOR      CG 147
C     PATCHES THAT CONNECT TO NEW SEGMENTS                              CG 148
      DO 21 I=1,NPCON                                                   CG 149
      IX=IPCON(I)*2+N1-ISV                                              CG 150
      IR=IX-1                                                           CG 151
      JSS=JSS+1                                                         CG 152
      IF (IR.GT.0.AND.IR.LE.IT) CB(IR,JSS)=(1.,0.)                      CG 153
      JSS=JSS+1                                                         CG 154
      IF (IX.GT.0.AND.IX.LE.IT) CB(IX,JSS)=(1.,0.)                      CG 155
   21 CONTINUE                                                          CG 156
   22 IF (M2.GT.M) GO TO 23                                             CG 157
C     FILL B(SW) AND B(SS)                                              CG 158
      IF (I1.LE.IN2) CALL CMSW (M2,M,I1,IN2,CB(1,IST),CB,N1,NB,0)       CG 159
      IF (IM1.LE.IM2) CALL CMSS (M2,M,IM1,IM2,CB(IMX,IST),NB,0)         CG 160
   23 IF (ICASX.EQ.1) GO TO 24                                          CG 161
      WRITE (14) ((CB(I,J),I=1,IT),J=1,ND)                              CG 162
   24 CONTINUE                                                          CG 163
C     FILLING B COMPLETE.  START ON C AND D                             CG 164
      IT=NPBL                                                           CG 165
      ISV=-NPBL                                                         CG 166
      DO 43 IBLK=1,NBBL                                                 CG 167
      ISV=ISV+NPBL                                                      CG 168
      ISVV=ISV+NC                                                       CG 169
      IF (IBLK.EQ.NBBL) IT=NLBL                                         CG 170
      IF (ICASX.LT.3) GO TO 27                                          CG 171
      DO 26 J=1,IT                                                      CG 172
      DO 25 I=1,NC                                                      CG 173
   25 CC(I,J)=(0.,0.)                                                   CG 174
      DO 26 I=1,ND                                                      CG 175
   26 CD(I,J)=(0.,0.)                                                   CG 176
   27 I1=ISVV+1                                                         CG 177
      I2=ISVV+IT                                                        CG 178
      IN1=I1-M1EQ                                                       CG 179
      IN2=I2-M1EQ                                                       CG 180
      IF (IN2.GT.N) IN2=N                                               CG 181
      IM1=I1-N                                                          CG 182
      IM2=I2-N                                                          CG 183
      IF (IM1.LT.M2EQ) IM1=M2EQ                                         CG 184
      IF (IM2.GT.MEQ) IM2=MEQ                                           CG 185
      IMX=1                                                             CG 186
      IF (IN1.LE.IN2) IMX=NEQN-I1+2                                     CG 187
      IF (ICASX.LT.3) GO TO 32                                          CG 188
      IF (N2.GT.N) GO TO 32                                             CG 189
C     SAME AS DO 24 LOOP TO FILL D(WW) FOR ICASX GREATER THAN 2         CG 190
      DO 31 J=N2,N                                                      CG 191
      CALL TRIO (J)                                                     CG 192
```

```
      DO 29 I=1,JSNO                                                    CG 193
      JSS=JCO(I)                                                        CG 194
      IF (JSS.LT.N2) GO TO 28                                           CG 195
      JCO(I)=JSS-N1                                                     CG 196
      GO TO 29                                                          CG 197
   28 JCO(I)=NEQS+ICONX(JSS)                                            CG 198
   29 CONTINUE                                                          CG 199
      IF (IN1.LE.IN2) CALL CMWW (J,IN1,IN2,CD,ND,CD,ND,1)               CG 200
      IF (IM1.LE.IM2) CALL CMWS (J,IM1,IM2,CD(1,IMX),ND,CD,ND,1)        CG 201
      IF (NLOAD.EQ.0) GO TO 31                                          CG 202
      IR=J-N1-ISV                                                       CG 203
      IF (IR.LT.1.OR.IR.GT.IT) GO TO 31                                 CG 204
      EXK=ZARRAY(J)                                                     CG 205
      DO 30 I=1,JSNO                                                    CG 206
      JSS=JCO(I)                                                        CG 207
   30 CD(JSS,IR)=CD(JSS,IR)-(AX(I)+CX(I))*EXK                           CG 208
   31 CONTINUE                                                          CG 209
   32 IF (M2.GT.M) GO TO 33                                             CG 210
C     FILL D(SW) AND D(SS)                                              CG 211
      IF (IN1.LE.IN2) CALL CMSW (M2,M,IN1,IN2,CD(IST,1),CD,N1,ND,1)     CG 212
      IF (IM1.LE.IM2) CALL CMSS (M2,M,IM1,IM2,CD(IST,IMX),ND,1)         CG 213
   33 IF (N1.LT.1) GO TO 39                                             CG 214
C     FILL C(WW),C(WS), D(WW)PRIME, AND D(WS)PRIME.                     CG 215
      DO 37 J=1,N1                                                      CG 216
      CALL TRIO (J)                                                     CG 217
      IF (NSCON.EQ.0) GO TO 36                                          CG 218
      DO 35 IX=1,JSNO                                                   CG 219
      JSS=JCO(IX)                                                       CG 220
      IF (JSS.LT.N2) GO TO 34                                           CG 221
      JCO(IX)=JSS+M1EQ                                                  CG 222
      GO TO 35                                                          CG 223
   34 IR=ICONX(JSS)                                                     CG 224
      IF (IR.NE.0) JCO(IX)=NEQSP+IR                                     CG 225
   35 CONTINUE                                                          CG 226
   36 IF (IN1.LE.IN2) CALL CMWW (J,IN1,IN2,CC,NC,CD,ND,ITX)             CG 227
      IF (IM1.LE.IM2) CALL CMWS (J,IM1,IM2,CC(1,IMX),NC,CD(1,IMX),ND,ITX CG 228
     1)                                                                 CG 229
   37 CONTINUE                                                          CG 230
      IF (NSCON.EQ.0) GO TO 39                                          CG 231
C     FILL C(WW)PRIME                                                   CG 232
      DO 38 IX=1,NSCON                                                  CG 233
      IR=ISCON(IX)                                                      CG 234
      JSS=NEQS+IX-ISV                                                   CG 235
      IF (JSS.GT.0.AND.JSS.LE.IT) CC(IR,JSS)=(1.,0.)                    CG 236
   38 CONTINUE                                                          CG 237
   39 IF (NPCON.EQ.0) GO TO 41                                          CG 238
      JSS=NEQP-ISV                                                      CG 239
C     FILL C(SS)PRIME                                                   CG 240
      DO 40 I=1,NPCON                                                   CG 241
      IX=IPCON(I)*2+N1                                                  CG 242
      IR=IX-1                                                           CG 243
      JSS=JSS+1                                                         CG 244
      IF (JSS.GT.0.AND.JSS.LE.IT) CC(IR,JSS)=(1.,0.)                    CG 245
      JSS=JSS+1                                                         CG 246
      IF (JSS.GT.0.AND.JSS.LE.IT) CC(IX,JSS)=(1.,0.)                    CG 247
   40 CONTINUE                                                          CG 248
   41 IF (M1.LT.1) GO TO 42                                             CG 249
C     FILL C(SW) AND C(SS)                                              CG 250
      IF (IN1.LE.IN2) CALL CMSW (1,M1,IN1,IN2,CC(N2,1),CC,0,NC,1)       CG 251
      IF (IM1.LE.IM2) CALL CMSS (1,M1,IM1,IM2,CC(N2,IMX),NC,1)          CG 252
   42 CONTINUE                                                          CG 253
      IF (ICASE.EQ.1) GO TO 43                                          CG 254
      WRITE (12) ((CD(J,I),J=1,ND),I=1,IT)                              CG 255
      WRITE (15) ((CC(J,I),J=1,NC),I=1,IT)                              CG 256
```

```
257 43    CONTINUE                                                  CG 257
258       IF(ICASX.EQ.1)RETURN                                      CG 258
259       REWIND 12                                                 CG 259
260       REWIND 14                                                 CG 260
261       REWIND 15                                                 CG 261
262       RETURN                                                    CG 262
263       END                                                       CG 263-
```

CMSET

PURPOSE

To control the filling of the interaction matrix.

METHOD

The linear equations resulting from the moment method solution of equations 13, 14 and the negative of equation 15 in Part I are written as

$$\sum_{j=1}^{N} a_j A_{ij} + \sum_{j=1}^{2M} b_j B_{ij} = E_i, \qquad i = 1, \ldots N$$

$$\sum_{j=1}^{N} c_j C_{kj} + \sum_{j=1}^{2M} d_j D_{kj} = H_k, \qquad k = 1, \ldots 2M$$

where N = number of segments

M = number of patches

$A_{ij} = \hat{s}_i \cdot (\bar{E}$ at $\bar{r}_i$ due to segment basis function j)

$B_{ij} = \hat{s}_i \cdot (\bar{E}$ at $\bar{r}_i$ due to current on patch $[(j + 1)/2]$ in direction $\hat{u}_j$)

$C_{kj} = -\hat{v}_k \cdot (\bar{H}$ at $\bar{P}_{[(k+1)/2]}$ due to segment basis function j) $\cdot S_{[(k+1)/2]}$

$D_{kj} = -\hat{v}_k \cdot (\bar{H}$ at $\bar{P}_{[(k+1)/2]}$ due to current on patch $[(j+1)/2]$ in direction $\hat{u}_j$) $S_{[(k+1)/2]} + \frac{1}{2} \sigma_{kj}$

$E_i = -\hat{s}_i \cdot$ (incident electric field at $\bar{r}_i$)

$H_k = \hat{v}_k \cdot$ (incident magnetic field at $\bar{P}_{[(k+1)/2]}$) $S_{[(k+1)/2]}$

$\bar{r}_i$ = position of the center of segment i

$\bar{p}_i$ = position of the center of patch i

$\hat{s}_i$ = unit vector in the direction of segment i

$$\hat{u}_i = \left\{ \begin{matrix} \hat{t}_1 \text{ if i is odd} \\ \hat{t}_2 \text{ if i is even} \end{matrix} \right\} \text{ for patch } [(i+1)/2]$$

$$\hat{v}_i = \left\{ \begin{matrix} \hat{t}_2 \text{ if i is odd} \\ \hat{t}_1 \text{ if i is even} \end{matrix} \right\} \text{ for patch } [(i+1)/2]$$

$s_i = 1$ if $\hat{t}_1 \times \hat{t}_2 = \hat{n}$ on patch i

-1 if $\hat{t}_1 \times \hat{t}_2 = -\hat{n}$ on patch i

$\sigma_{kj} = -1$ if $k = j =$ odd

$+1$ if $k = j =$ even

0 if $k \neq j$

The basis function amplitudes a_j, b_j, c_j and d_j are determined later by solving the matrix equation of order N + 2M.

The matrix elements are computed by calling subroutines CMWW, CMSW, CMWS, and CMSS for the elements of A, B, C and D respectively. For A and C the components of all basis functions that extend across segment J are computed by calling TRIO at CM 52. CMWW and CMWS are then called to compute the components of A or C due to these basis function components on segment J.

If segment j, with length Δ_j, is loaded with impedance Z_j the elements of A are modified as $A_{jk} = A_{jk} - \frac{Z_j}{\Delta j}$ X (value of basis function k at the center of segment j) for k = the numbers of all basis functions that extend onto segment j. The summation over values of k (k = JSS) for loading on segment J occurs at CM 68.

The submatrices are stored in the array CM in transposed form. All references to rows and columns, here, apply to the nontransposed matrices. Thus "row" in this discussion refers to the second index of CM in the code.

For a structure without symmetry the submatrices are stored in the order

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

If the complete matrix is too large for the array CM then blocks of rows are filled and written on file 11. A block may then contain rows from A and B, rows from C and D or a combination. The row of CM at which C and D start is computed as IST.

For a structure having p symmetric sections the submatrices are stored in the form

$$\begin{bmatrix} A_1 & B_1 & A_2 & B_2 & \cdots & A_p & B_p \\ C_1 & D_1 & C_2 & D_2 & & C_p & D_p \end{bmatrix}$$

where $\begin{bmatrix} A_i & B_i \\ C_i & D_i \end{bmatrix}$

represents A_i in the first row of submatrices in equation 108 of Part I. Each call to CMWW and CMWS may fill elements of A_i or C_i for any value of i. The column indices in array JCO are adjusted at CM 55 to allow for the columns occupied by the B_i and D_i matrices. B_i and D_i are filled for each value of i in the loop from CM 75 to CM 81. The Fourier transform of the submatrices, or the transform for planar symmetry (equation 116 of Part I) is computed from CM 85 to CM 100.

SYMBOL DICTIONARY

- CM = array for the matrix
- I1 = number of first equation in a block (patch equation +N for patches)
- I2 = number of the last equation in a block
- IEXCX = 1 to use extended thin wire kernel on wires, 0 otherwise
- IM1 = number of first patch equation in a block

IM2 = number of last patch equation in a block

IN2 = number of the last segment equation in a block

IOUT = number of real numbers in a block for output

IPR = row in CM (second index) for segment J

IST = row in CM of the first patch equation

ISV = I1 - 1

IT = number of rows in a block

IXBLK1 = block number

JM1 = number of first patch in a symmetric section

JM2 = number of the last patch in a symmetric section

JST = column in CM of the first patch equation for a symmetric block

MP2 = number of patch equations

NEQ = total number of equations

NOP = number of symmetric sections

NPEQ = number of equations in a symmetric section

NROW = row dimensions of the transposed CM array

RKHX = minimum interaction distance at which the infinitesimal dipole approximation is used for the field of a segment

ZAJ = Z_j/Δ_j

```
      SUBROUTINE CMSET (NROW,CM,RKHX,IEXKX)                              CM   1
C                                                                        CM   2
C     CMSET SETS UP THE COMPLEX STRUCTURE MATRIX IN THE ARRAY CM         CM   3
C                                                                        CM   4
      COMPLEX CM,ZARRAY,ZAJ,ETK,ETS,ETC,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC, CM   5
     1EZC,SSX,D,DETER                                                    CM   6
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 CM   7
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( CM   8
     2300),WLAM,IPSYM                                                    CM   9
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I CM  10
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                 CM  11
      COMMON /SMAT/ SSX(16,16)                                           CM  12
      COMMON /SCRATM/ D(600)                                             CM  13
      COMMON /ZLOAD/ ZARRAY(300),NLOAD,NLODF                             CM  14
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(50),NSCON,IP CM  15
     1CON(10),NPCON                                                      CM  16
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ CM  17
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                             CM  18
      DIMENSION CM(NROW,1)                                               CM  19
      MP2=2*MP                                                           CM  20
      NPEQ=NP+MP2                                                        CM  21
      NEQ=N+2*M                                                          CM  22
      NOP=NEQ/NPEQ                                                       CM  23
      IF (ICASE.GT.2) REWIND 11                                          CM  24
      RKH=RKHX                                                           CM  25
      IEXK=IEXKX                                                         CM  26
      IOUT=2*NPBLK*NROW                                                  CM  27
      IT=NPBLK                                                           CM  28
C                                                                        CM  29
C     CYCLE OVER MATRIX BLOCKS                                           CM  30
C                                                                        CM  31
      DO 13 IXBLK1=1,NBLOKS                                              CM  32
      ISV=(IXBLK1-1)*NPBLK                                               CM  33
      IF (IXBLK1.EQ.NBLOKS) IT=NLAST                                     CM  34
      DO 1 I=1,NROW                                                      CM  35
      DO 1 J=1,IT                                                        CM  36
    1 CM(I,J)=(0.,0.)                                                    CM  37
      I1=ISV+1                                                           CM  38
      I2=ISV+IT                                                          CM  39
      IN2=I2                                                             CM  40
      IF (IN2.GT.NP) IN2=NP                                              CM  41
      IM1=I1-NP                                                          CM  42
      IM2=I2-NP                                                          CM  43
      IF (IM1.LT.1) IM1=1                                                CM  44
      IST=1                                                              CM  45
      IF (I1.LE.NP) IST=NP-I1+2                                          CM  46
      IF (N.EQ.0) GO TO 5                                                CM  47
C                                                                        CM  48
C     WIRE SOURCE LOOP                                                   CM  49
C                                                                        CM  50
      DO 4 J=1,N                                                         CM  51
      CALL TRIO (J)                                                      CM  52
      DO 2 I=1,JSNO                                                      CM  53
      IJ=JCO(I)                                                          CM  54
    2 JCO(I)=((IJ-1)/NP)*MP2+IJ                                          CM  55
      IF (I1.LE.IN2) CALL CMWW (J,I1,IN2,CM,NROW,CM,NROW,1)              CM  56
      IF (IM1.LE.IM2) CALL CMWS (J,IM1,IM2,CM(1,IST),NROW,CM,NROW,1)     CM  57
      IF (NLOAD.EQ.0) GO TO 4                                            CM  58
C                                                                        CM  59
C     MATRIX ELEMENTS MODIFIED BY LOADING                                CM  60
C                                                                        CM  61
      IF (J.GT.NP) GO TO 4                                               CM  62
      IPR=J-ISV                                                          CM  63
      IF (IPR.LT.1.OR.IPR.GT.IT) GO TO 4                                 CM  64
```

```
      ZAJ=ZARRAY(J)                                                     CM  65
      DO 3 I=1,JSNO                                                     CM  66
      JSS=JCO(I)                                                        CM  67
3     CM(JSS,IPR)=CM(JSS,IPR)-(AX(I)+CX(I))*ZAJ                         CM  68
4     CONTINUE                                                          CM  69
5     IF (M.EQ.0) GO TO 7                                               CM  70
C     MATRIX ELEMENTS FOR PATCH CURRENT SOURCES                         CM  71
      JM1=1-MP                                                          CM  72
      JM2=0                                                             CM  73
      JST=1-MP2                                                         CM  74
      DO 6 I=1,NOP                                                      CM  75
      JM1=JM1+MP                                                        CM  76
      JM2=JM2+MP                                                        CM  77
      JST=JST+NPEQ                                                      CM  78
      IF (I1.LE.IN2) CALL CMSW (JM1,JM2,I1,IN2,CM(JST,1),CM,0,NROW,1)   CM  79
      IF (IM1.LE.IM2) CALL CMSS (JM1,JM2,IM1,IM2,CM(JST,IST),NROW,1)    CM  80
6     CONTINUE                                                          CM  81
7     IF (ICASE.EQ.1) GO TO 13                                          CM  82
      IF (ICASE.EQ.3) GO TO 12                                          CM  83
C     COMBINE ELEMENTS FOR SYMMETRY MODES                               CM  84
      DO 11 I=1,IT                                                      CM  85
      DO 11 J=1,NPEQ                                                    CM  86
      DO 8 K=1,NOP                                                      CM  87
      KA=J+(K-1)*NPEQ                                                   CM  88
8     D(K)=CM(KA,I)                                                     CM  89
      DETER=D(1)                                                        CM  90
      DO 9 KK=2,NOP                                                     CM  91
9     DETER=DETER+D(KK)                                                 CM  92
      CM(J,I)=DETER                                                     CM  93
      DO 11 K=2,NOP                                                     CM  94
      KA=J+(K-1)*NPEQ                                                   CM  95
      DETER=D(1)                                                        CM  96
      DO 10 KK=2,NOP                                                    CM  97
10    DETER=DETER+D(KK)*SSX(K,KK)                                       CM  98
      CM(KA,I)=DETER                                                    CM  99
11    CONTINUE                                                          CM 100
      IF (ICASE.LT.3) GO TO 13                                          CM 101
C     WRITE BLOCK FOR OUT-OF-CORE CASES.                                CM 102
12    CALL BLCKOT (CM,11,1,IOUT,1,31)                                   CM 103
13    CONTINUE                                                          CM 104
      IF (ICASE.GT.2) REWIND 11                                         CM 105
      RETURN                                                            CM 106
      END                                                               CM 107-
```

CMSS

PURPOSE

To compute and store matrix elements representing the H field at patch centers due to the current on patches.

METHOD

CMSS computes the matrix elements D_{kj} defined in the description of subroutine CMSET. Subroutine HINTG is called to compute the magnetic field at the center of patch I due to current on patch J. H due to the current $\hat{t}_1$ on patch J is stored in EXK, EYK and EZK, while H due to current $\hat{t}_2$ is stored in EXS, EYS and EZS. The term $0.5\ \sigma_{kj}$ in D_{kj} is added at CM 61 and CM 62 for odd and even equations. The matrix elements are stored in array CM from SS63 to SS78 in either normal or transposed order. Elements for both the even and odd equations are stored if both equations are within the block.

SYMBOL DICTIONARY

CM	= array for matrix storage
G11	= D_{kj} for k odd, j odd
G12	= D_{kj} for k odd, j even
G21	= D_{kj} for k even, j odd
G22	= D_{kj} for k even, j even
I1	= patch number for first equation
I2	= patch number for last equation
ICOMP	= equation number for the odd numbered equation for observation patch I
III	= location of the odd numbered equation in CM
II2	= location of the even numbered equation in CM
IL	= array location for coordinates of patch I
IM1	= patch equation number for first equation in block
IM2	= patch equation number for last equation in block
ITRP	= 0 or 1 to select normal or transposed filling of CM
J1	= number of first source patch
J2	= number of last source patch

JJ1	= column in non-transposed matrix, of the first equation for patch J
JJ2	= column of second equation for patch J
JL	= array location for coordinates of patch J
NROW	= row dimension of CM
T1XI, T1YI, T1ZI T2XI, T2YI, T2ZI T1XJ, T1YJ, T1ZJ T2XJ, T2YJ, T2ZJ	= x, y and z components of $\hat{t}_1$ or $\hat{t}_2$ for patch I or J
XI, YI, ZI	= coordinates of center of patch I

```
      SUBROUTINE CMSS (J1,J2,IM1,IM2,CM,NROW,ITRP)                      SS   1
C     CMSS COMPUTES MATRIX ELEMENTS FOR SURFACE-SURFACE INTERACTIONS.   SS   2
      COMPLEX G11,G12,G21,G22,CM,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC    SS   3
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 SS   4
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( SS   5
     2300),WLAM,IPSYM                                                   SS   6
      COMMON /ANGL/ SALP(300)                                           SS   7
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ SS   8
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                           SS   9
      DIMENSION CM(NROW,1)                                              SS  10
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1)          SS  11
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON SS  12
     12), (T2Z,ITAG)                                                    SS  13
      EQUIVALENCE (T1XJ,CABJ), (T1YJ,SABJ), (T1ZJ,SALPJ), (T2XJ,B), (T2Y SS  14
     1J,IND1), (T2ZJ,IND2)                                              SS  15
      LDP=LD+1                                                          SS  16
      I1=(IM1+1)/2                                                      SS  17
      I2=(IM2+1)/2                                                      SS  18
      ICOMP=I1*2-3                                                      SS  19
      II1=-1                                                            SS  20
      IF (ICOMP+2.LT.IM1) II1=-2                                        SS  21
C     LOOP OVER OBSERVATION PATCHES                                     SS  22
      DO 5 I=I1,I2                                                      SS  23
      IL=LDP-I                                                          SS  24
      ICOMP=ICOMP+2                                                     SS  25
      II1=II1+2                                                         SS  26
      II2=II1+1                                                         SS  27
      T1XI=T1X(IL)*SALP(IL)                                             SS  28
      T1YI=T1Y(IL)*SALP(IL)                                             SS  29
      T1ZI=T1Z(IL)*SALP(IL)                                             SS  30
      T2XI=T2X(IL)*SALP(IL)                                             SS  31
      T2YI=T2Y(IL)*SALP(IL)                                             SS  32
      T2ZI=T2Z(IL)*SALP(IL)                                             SS  33
      XI=X(IL)                                                          SS  34
      YI=Y(IL)                                                          SS  35
      ZI=Z(IL)                                                          SS  36
      JJ1=-1                                                            SS  37
C     LOOP OVER SOURCE PATCHES                                          SS  38
      DO 5 J=J1,J2                                                      SS  39
      JL=LDP-J                                                          SS  40
      JJ1=JJ1+2                                                         SS  41
      JJ2=JJ1+1                                                         SS  42
      S=BI(JL)                                                          SS  43
      XJ=X(JL)                                                          SS  44
      YJ=Y(JL)                                                          SS  45
      ZJ=Z(JL)                                                          SS  46
      T1XJ=T1X(JL)                                                      SS  47
      T1YJ=T1Y(JL)                                                      SS  48
      T1ZJ=T1Z(JL)                                                      SS  49
      T2XJ=T2X(JL)                                                      SS  50
      T2YJ=T2Y(JL)                                                      SS  51
      T2ZJ=T2Z(JL)                                                      SS  52
      CALL HINTG (XI,YI,ZI)                                             SS  53
      G11=-(T2XI*EXK+T2YI*EYK+T2ZI*EZK)                                 SS  54
      G12=-(T2XI*EXS+T2YI*EYS+T2ZI*EZS)                                 SS  55
      G21=-(T1XI*EXK+T1YI*EYK+T1ZI*EZK)                                 SS  56
      G22=-(T1XI*EXS+T1YI*EYS+T1ZI*EZS)                                 SS  57
      IF (I.NE.J) GO TO 1                                               SS  58
      G11=G11+.5                                                        SS  59
      G22=G22+.5                                                        SS  60
    1 IF (ITRP.NE.0) GO TO 3                                            SS  61
C     NORMAL FILL                                                       SS  62
      IF (ICOMP.LT.IM1) GO TO 2                                         SS  63
      CM(II1,JJ1)=G11                                                   SS  64
```

```
      CM(II1,JJ2)=G12                                                   SS  65
   2  IF (ICOMP.GE.IM2) GO TO 5                                         SS  66
      CM(II2,JJ1)=G21                                                   SS  67
      CM(II2,JJ2)=G22                                                   SS  68
      GO TO 5                                                           SS  69
C     TRANSPOSED FILL                                                   SS  70
   3  IF (ICOMP.LT.IM1) GO TO 4                                         SS  71
      CM(JJ1,II1)=G11                                                   SS  72
      CM(JJ2,II1)=G12                                                   SS  73
   4  IF (ICOMP.GE.IM2) GO TO 5                                         SS  74
      CM(JJ1,II2)=G21                                                   SS  75
      CM(JJ2,II2)=G22                                                   SS  76
   5  CONTINUE                                                          SS  77
      RETURN                                                            SS  78
      END                                                               SS  79-
```

CMSW

PURPOSE

To compute and store matrix elements representing the electric field at segment centers due to the current on patches.

METHOD

SW30 - SW35 Coordinates of observation segment are stored.

SW36 - SW42 If either end of the observation segment connects to a surface IPCH is set to the number of the first of the four patches at the connection point.

SW48 - SW57 Coordinates of the source patch are stored in COMMON/DATAJ/.

SW61 - SW86 IF IPCH = J then patch J is the first patch at the point where segment I connects to the surface. Subroutine PCINT is called to integrate the current over the four patches at the connection point. The current on the patches includes the eight basis functions of the four patches and a portion of the basis function from the segment. Hence contributions to nine matrix elements are generated and stored in array EMEL. The field due to the segment basis function extending onto the patches is stored in array CW at SW76 or SW78. The fields due to the first patch basis function, EMEL(1) and EMEL(5), are then stored in array CM at SW80 and SW81 or at SW83 and SW84. ICGO is then incremented. For the next three times through the loop over J the call to PCINT is skipped at SW63 and the remaining values in EMEL are stored.

SW88 - SW96 If segment I and patch J are not connected, subroutine UNERE is called to compute the electric field due to the current on the patch with the current treated as Hertzian dipoles in the directions $\hat{t}_1$ and $\hat{t}_2$. The matrix elements are stored in CM.

SW102 - SW138 This is a special section of code to compute the electric field due to the component of a segment basis function that extends onto connected patches. It is used at line CG112 of subroutine CMNGF for the case where the connected segment and patches are in the NGF file and a new segment is connected to the outer end of the NGF segment modifying its basis function. Subroutine PCINT is called to evaluate the nine matrix elements. Only EMEL(9) is used since the patch basis functions have not been modified.

SYMBOL DICTIONARY

CABI	= x component of $\hat{t}$ in direction of segment I
CM	= array for E due to patch basis functions
CW	= array for E due to segment basis function extending onto surface at connection point
EMEL	= array of matrix elements from integrating over surface
FSIGN	= ±1 depending on which end of segment connects to surface
I1	= number of first observation segment
I2	= number of last observation segment
ICGØ	= index for matrix elements at connection point
IL	= index for segment basis function in CW
IP	= 1 for direct field, 2 for image in ground
IPCH	= number of first patch connecting to a segment
ITRP	= 0 for normal matrix fill 1 for transposed fill -1 for special NGF case
J	= source patch
J1	= first source patch
J2	= last source patch
JL	= index for source patch in CM
JS	= index for patch coordinates
K	= index in CM or CW for observation segment
NCW	= index offset for CW

NEQS	= number of equations excluding NGF
NROW	= row dimensions of CM and CW
PI	= pi
PX	= $\sin k(s - s_0)$ for s at the end of the segment
PY	= $\cos k(s - s_0)$ connected to the surface
SABI	= y component of $\hat{i}$ in direction of segment I
SALPI	= z component of $\hat{i}$ in direction of segment I
XI, YI, ZI	= center of observation segment

```
      SUBROUTINE CMSW (J1,J2,I1,I2,CM,CW,NCW,NROW,ITRP)                  SW   1
C     COMPUTES MATRIX ELEMENTS FOR E ALONG WIRES DUE TO PATCH CURRENT    SW   2
      COMPLEX CM,ZRATI,ZRATI2,T1,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC,EME SW   3
     1L,CW,FRATI                                                         SW   4
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 SW   5
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( SW   6
     2300),WLAM,IPSYM                                                    SW   7
      COMMON /ANGL/ SALP(300)                                            SW   8
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR, SW   9
     1IPERF,T1,T2                                                        SW  10
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ SW  11
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                            SW  12
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(80),NSCON,IP SW  13
     1CON(10),NPCON                                                      SW  14
      DIMENSION CAB(1), SAB(1), CM(NROW,1), CW(NROW,1)                   SW  15
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1), EMEL(9)  SW  16
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON SW  17
     1), (T2Z,ITAG), (CAB,ALP), (SAB,BET)                                SW  18
      EQUIVALENCE (T1XJ,CABJ), (T1YJ,SABJ), (T1ZJ,SALPJ), (T2XJ,B), (T2Y SW  19
     1J,IND1), (T2ZJ,IND2)                                               SW  20
      DATA PI/3.141592654/                                               SW  21
      LDP=LD+1                                                           SW  22
      NEQS=N-N1+2*(M-M1)                                                 SW  23
      IF (ITRP.LT.0) GO TO 13                                            SW  24
      K=0                                                                SW  25
      ICGO=1                                                             SW  26
C     OBSERVATION LOOP                                                   SW  27
      DO 12 I=I1,I2                                                      SW  28
      K=K+1                                                              SW  29
      XI=X(I)                                                            SW  30
      YI=Y(I)                                                            SW  31
      ZI=Z(I)                                                            SW  32
      CABI=CAB(I)                                                        SW  33
      SABI=SAB(I)                                                        SW  34
      SALPI=SALP(I)                                                      SW  35
      IPCH=0                                                             SW  36
      IF (ICON1(I).LT.10000) GO TO 1                                     SW  37
      IPCH=ICON1(I)-10000                                                SW  38
      FSIGN=-1.                                                          SW  39
1     IF (ICON2(I).LT.10000) GO TO 2                                     SW  40
      IPCH=ICON2(I)-10000                                                SW  41
      FSIGN=1.                                                           SW  42
2     JL=0                                                               SW  43
C     SOURCE LOOP                                                        SW  44
      DO 12 J=J1,J2                                                      SW  45
      JS=LDP-J                                                           SW  46
      JL=JL+2                                                            SW  47
      T1XJ=T1X(JS)                                                       SW  48
      T1YJ=T1Y(JS)                                                       SW  49
      T1ZJ=T1Z(JS)                                                       SW  50
      T2XJ=T2X(JS)                                                       SW  51
      T2YJ=T2Y(JS)                                                       SW  52
      T2ZJ=T2Z(JS)                                                       SW  53
      XJ=X(JS)                                                           SW  54
      YJ=Y(JS)                                                           SW  55
      ZJ=Z(JS)                                                           SW  56
      S=BI(JS)                                                           SW  57
C     GROUND LOOP                                                        SW  58
      DO 12 IP=1,KSYMP                                                   SW  59
      IPGND=IP                                                           SW  60
      IF (IPCH.NE.J.AND.ICGO.EQ.1) GO TO 9                               SW  61
      IF (IP.EQ.2) GO TO 9                                               SW  62
      IF (ICGO.GT.1) GO TO 6                                             SW  63
      CALL PCINT (XI,YI,ZI,CABI,SABI,SALPI,EMEL)                         SW  64
```

```
      PY=PI*SI(I)*FSIGN                                                 SW  65
      PX=SIN(PY)                                                        SW  66
      PY=COS(PY)                                                        SW  67
      EXC=EMEL(9)*FSIGN                                                 SW  68
      CALL TRIO (I)                                                     SW  69
      IF (I.GT.N1) GO TO 3                                              SW  70
      IL=NEQS+ICONX(I)                                                  SW  71
      GO TO 4                                                           SW  72
3     IL=I-NCW                                                          SW  73
      IF (I.LE.NP) IL=((IL-1)/NP)*2*MP+IL                               SW  74
4     IF (ITRP.NE.0) GO TO 5                                            SW  75
      CW(K,IL)=CW(K,IL)+EXC*(AX(JSNO)+BX(JSNO)*PX+CX(JSNO)*PY)          SW  76
      GO TO 6                                                           SW  77
5     CW(IL,K)=CW(IL,K)+EXC*(AX(JSNO)+BX(JSNO)*PX+CX(JSNO)*PY)          SW  78
6     IF (ITRP.NE.0) GO TO 7                                            SW  79
      CM(K,JL-1)=EMEL(ICGO)                                             SW  80
      CM(K,JL)=EMEL(ICGO+4)                                             SW  81
      GO TO 8                                                           SW  82
7     CM(JL-1,K)=EMEL(ICGO)                                             SW  83
      CM(JL,K)=EMEL(ICGO+4)                                             SW  84
8     ICGO=ICGO+1                                                       SW  85
      IF (ICGO.EQ.5) ICGO=1                                             SW  86
      GO TO 11                                                          SW  87
9     CALL UNERE (XI,YI,ZI)                                             SW  88
      IF (ITRP.NE.0) GO TO 10                                           SW  89
C     NORMAL FILL                                                       SW  90
      CM(K,JL-1)=CM(K,JL-1)+EXK*CABI+EYK*SABI+EZK*SALPI                 SW  91
      CM(K,JL)=CM(K,JL)+EXS*CABI+EYS*SABI+EZS*SALPI                     SW  92
      GO TO 11                                                          SW  93
C     TRANSPOSED FILL                                                   SW  94
10    CM(JL-1,K)=CM(JL-1,K)+EXK*CABI+EYK*SABI+EZK*SALPI                 SW  95
      CM(JL,K)=CM(JL,K)+EXS*CABI+EYS*SABI+EZS*SALPI                     SW  96
11    CONTINUE                                                          SW  97
12    CONTINUE                                                          SW  98
      RETURN                                                            SW  99
C     FOR OLD SEG. CONNECTING TO OLD PATCH ON ONE END AND NEW SEG. ON   SW 100
C     OTHER END INTEGRATE SINGULAR COMPONENT (9) OF SURFACE CURRENT ONLY SW 101
13    IF (J1.LT.I1.OR.J1.GT.I2) GO TO 16                                SW 102
      IPCH=ICON1(J1)                                                    SW 103
      IF (IPCH.LT.10000) GO TO 14                                       SW 104
      IPCH=IPCH-10000                                                   SW 105
      FSIGN=-1.                                                         SW 106
      GO TO 15                                                          SW 107
14    IPCH=ICON2(J1)                                                    SW 108
      IF (IPCH.LT.10000) GO TO 16                                       SW 109
      IPCH=IPCH-10000                                                   SW 110
      FSIGN=1.                                                          SW 111
15    IF (IPCH.GT.M1) GO TO 16                                          SW 112
      JS=LDP-IPCH                                                       SW 113
      IPGND=1                                                           SW 114
      T1XJ=T1X(JS)                                                      SW 115
      T1YJ=T1Y(JS)                                                      SW 116
      T1ZJ=T1Z(JS)                                                      SW 117
      T2XJ=T2X(JS)                                                      SW 118
      T2YJ=T2Y(JS)                                                      SW 119
      T2ZJ=T2Z(JS)                                                      SW 120
      XJ=X(JS)                                                          SW 121
      YJ=Y(JS)                                                          SW 122
      ZJ=Z(JS)                                                          SW 123
      S=B1(JS)                                                          SW 124
      XI=X(J1)                                                          SW 125
      YI=Y(J1)                                                          SW 126
      ZI=Z(J1)                                                          SW 127
      CABI=CAB(J1)                                                      SW 128
```

```
      SABI=SAB(J1)                                                    SW 129
      SALPI=SALP(J1)                                                  SW 130
      CALL PCINT (XI,YI,ZI,CABI,SABI,SALPI,EMEL)                      SW 131
      PY=PI*SI(J1)*FSIGN                                              SW 132
      PX=SIN(PY)                                                      SW 133
      PY=COS(PY)                                                      SW 134
      EXC=EMEL(8)*FSIGN                                               SW 135
      IL=JCO(JSNO)                                                    SW 136
      K=J1-I1+1                                                       SW 137
      CW(K,IL)=CW(K,IL)+EXC*(AX(JSNO)+BX(JSNO)*PX+CX(JSNO)*PY)        SW 138
   16 RETURN                                                          SW 139
      END                                                             SW 140-
```

CMWS

PURPOSE

To compute and store matrix elements representing the magnetic field at patch centers due to the current on wire segments.

METHOD

Matrix elements are computed for patch equations numbered I1 through I2 with the source segment J. For odd numbered equations the matrix element represents the first term on the right side of equation 14 of Part I. For even numbered equations it is the negative of the first term on the right side of equation 15. For equation I1 and for all odd numbered equations subroutine HSFLD is called to compute the H field at the center of the patch due to constant, sin $k(s - s_0)$ and cos $k(s - s_0)$ currents on segment J. The required component of the field, $-\hat{t}_2 \cdot \bar{H}$ or $-\hat{t}_1 \cdot \bar{H}$ for odd or even equations respectively, is computed from WS49 to WS51. Multiplication by SALP(JS) reverses the sign when $(\hat{t}_1, \hat{t}_2, \hat{n})$ has a left-hand orientation on a patch formed by reflection. The field component for each basis function component on segment J is computed and stored for WS56 through WS75. Storage of the matrix elements is similar to that in subroutine CMWW.

SYMBOL DICTIONARY

CM	= array for matrix elements
CW	= array for matrix elements (NGF only)
ETK, ETS, ETC	= $-\hat{t}_2 \cdot \bar{H}$ or $-\hat{t}_1 \cdot \bar{H}$ due to current of constant, sin $k(s - s_0)$, or cos $k(s - s_0)$ respectively
I	= equation number
I1	= number of first equation
I2	= number of second equation
IK	= 0 if I is even, 1 if I is odd
IPATCH	= patch number for equation I
IPR	= relative matrix location for equation I. Position in complete matrix depends on the address of CM in the call to CMWS

ITRP = 0 for non-transposed fill
1 for transposed fill
2 for transposed fill for NGF

J = source segment number

JS = location in COMMON/DATA/ of parameters for patch J

JX = matrix index for a particular basis function

LDP = LD + 1

NR = row dimension of CM

NW = row dimension of CW

TX, TY, TZ = x, y, and z components of $\hat{t}_1$ or $\hat{t}_2$

XI, YI, ZI = x, y and z coordinates of the center of the patch at which the field is computed

```
      SUBROUTINE CMWS (J,I1,I2,CM,NR,CW,NW,ITRP)                        WS   1
C                                                                       WS   2
C     CMWS COMPUTES MATRIX ELEMENTS FOR WIRE-SURFACE INTERACTIONS       WS   3
C                                                                       WS   4
      COMPLEX CM,CW,ETK,ETS,ETC,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC     WS   5
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 WS   6
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( WS   7
     2300),WLAM,IPSYM                                                   WS   8
      COMMON /ANGL/ SALP(300)                                           WS   9
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(50),NSCON,IP WS  10
     1CON(10),NPCON                                                     WS  11
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ WS  12
     1S,EXC,EYC,EZC,RKH,ISEG,IND1,IND2,IPGND                           WS  13
      DIMENSION CM(NR,1), CW(NW,1), CAB(1), SAB(1)                      WS  14
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1)          WS  15
      EQUIVALENCE (CAB,ALP), (SAB,BET), (T1X,SI), (T1Y,ALP), (T1Z,BET)  WS  16
      EQUIVALENCE (T2X,ICON1), (T2Y,ICON2), (T2Z,ITAG)                  WS  17
      LDP=LD+1                                                          WS  18
      S=SI(J)                                                           WS  19
      B=BI(J)                                                           WS  20
      XJ=X(J)                                                           WS  21
      YJ=Y(J)                                                           WS  22
      ZJ=Z(J)                                                           WS  23
      CABJ=CAB(J)                                                       WS  24
      SABJ=SAB(J)                                                       WS  25
      SALPJ=SALP(J)                                                     WS  26
C                                                                       WS  27
C     OBSERVATION LOOP                                                  WS  28
C                                                                       WS  29
      IPR=0                                                             WS  30
      DO 9 I=I1,I2                                                      WS  31
      IPR=IPR+1                                                         WS  32
      IPATCH=(I+1)/2                                                    WS  33
      IK=I-(I/2)*2                                                      WS  34
      IF (IK.EQ.0.AND.IPR.NE.1) GO TO 1                                 WS  35
      JS=LDP-IPATCH                                                     WS  36
      XI=X(JS)                                                          WS  37
      YI=Y(JS)                                                          WS  38
      ZI=Z(JS)                                                          WS  39
      CALL HSFLD (XI,YI,ZI,0.)                                          WS  40
      IF (IK.EQ.0) GO TO 1                                              WS  41
      TX=T2X(JS)                                                        WS  42
      TY=T2Y(JS)                                                        WS  43
      TZ=T2Z(JS)                                                        WS  44
      GO TO 2                                                           WS  45
1     TX=T1X(JS)                                                        WS  46
      TY=T1Y(JS)                                                        WS  47
      TZ=T1Z(JS)                                                        WS  48
2     ETK=-(EXK*TX+EYK*TY+EZK*TZ)*SALP(JS)                              WS  49
      ETS=-(EXS*TX+EYS*TY+EZS*TZ)*SALP(JS)                              WS  50
      ETC=-(EXC*TX+EYC*TY+EZC*TZ)*SALP(JS)                              WS  51
C                                                                       WS  52
C     FILL MATRIX ELEMENTS.  ELEMENT LOCATIONS DETERMINED BY CONNECTION WS  53
C     DATA.                                                             WS  54
C                                                                       WS  55
      IF (ITRP.NE.0) GO TO 4                                            WS  56
C     NORMAL FILL                                                       WS  57
      DO 3 IJ=1,JSNO                                                    WS  58
      JX=JCO(IJ)                                                        WS  59
3     CM(IPR,JX)=CM(IPR,JX)+ETK*AX(IJ)+ETS*BX(IJ)+ETC*CX(IJ)            WS  60
      GO TO 9                                                           WS  61
4     IF (ITRP.EQ.2) GO TO 6                                            WS  62
C     TRANSPOSED FILL                                                   WS  63
      DO 5 IJ=1,JSNO                                                    WS  64
```

CMWS

```
      JX=JCO(IJ)                                                        WS  65
    5 CM(JX,IPR)=CM(JX,IPR)+ETK*AX(IJ)+ETS*BX(IJ)+ETC*CX(IJ)            WS  66
      GO TO 9                                                           WS  67
C     TRANSPOSED FILL - C(WS) AND D(WS)PRIME (=CW)                      WS  68
    6 DO 8 IJ=1,JSNO                                                    WS  69
      JX=JCO(IJ)                                                        WS  70
      IF (JX.GT.NR) GO TO 7                                             WS  71
      CM(JX,IPR)=CM(JX,IPR)+ETK*AX(IJ)+ETS*BX(IJ)+ETC*CX(IJ)            WS  72
      GO TO 8                                                           WS  73
    7 JX=JX-NR                                                          WS  74
      CW(JX,IPR)=CW(JX,IPR)+ETK*AX(IJ)+ETS*BX(IJ)+ETC*CX(IJ)            WS  75
    8 CONTINUE                                                          WS  76
    9 CONTINUE                                                          WS  77
      RETURN                                                            WS  78
      END                                                               WS  79
```

CMWW

PURPOSE

To call subroutines to compute the electric field at segment centers due to current on other segments and to store matrix elements in array locations.

METHOD

WW17 - WW24	Parameters of source segment (J) are stored in COMMON/DATAJ/.
WW27 - WW43	First end of segment J is tested to determine whether the extended thin wire approximation can be used. It cannot be used at a junction of more than two wires (WW30), at a bend (WW37), at a change in radius (WW38), or at the base of a non-vertical segment connected to the ground (WW33).
WW44 - WW60	Second end of segment J is tested.
WW66	Loop over observation segments ranges from I1 to I2. The index IPR starts at 1 so the matrix element for I1 is stored in the first row or column of the array CM. The location in the complete matrix is determined by the address given for CM when CMWW is called.
WW76	EFLD computes the electric fields at (XI, YI, ZI) due to segment J and stores them in COMMON/DATAJ/.
WW77 - WW79	Electric field tangent to segment I is computed.
WW84 - WW103	Matrix elements are formed by combining the field components.
WW86 - WW88	Matrix elements are stored in non-transposed order.
WW92 - WW94	Matrix elements are stored in transposed order.
WW97 - WW104	When the source segment is from a NGF file the matrix elements will normally be stored in submatrix C of the NGF matrix structure. When the segment connects to a new segment, however, contributions to submatrix D result. The C and D contributions are stored in CM and CW, respectively, in transposed order.

SYMBOL DICTIONARY

AI	= radius of observation segment
CABI	= x component of unit vector in direction of segment
CM	= array for matrix elements
CW	= array for matrix elements (NGF only)
ETK, ETS, ETC	= E field tangent to segment I due to current of constant, $\sin k(s - s_0)$ and $\cos k(s - s_0)$ distribution, respectively, on segment J.
I1	= first observation segment
I2	= final observation segment
IJ	= 0 for special treatment when I = J
IPR	= relative matrix location for observation point
ITRP	= 0 for non-transposed fill 1 for transposed fill 2 for transposed fill for NGF
J	= source segment number
JX	= matrix index for a particular basis function
NR	= row dimension of CM
NW	= row dimension of CW
SABI	= y component of unit vector in direction of segment
SALPI	= z component of unit vector in direction of segment
XI, YI, ZI	= coordinates of center of segment I.

CONSTANTS

0.999999	= test for collinear segments

```
      SUBROUTINE CMWW (J,I1,I2,CM,NR,CW,NW,ITRP)                        WW    1
C                                                                       WW    2
C     CMWW COMPUTES MATRIX ELEMENTS FOR WIRE-WIRE INTERACTIONS          WW    3
C                                                                       WW    4
      COMPLEX CM,CW,ETK,ETS,ETC,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC     WW    5
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 WW    6
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( WW    7
     2300),WLAM,IPSYM                                                   WW    8
      COMMON /ANGL/ SALP(300)                                           WW    9
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(80),NSCON,IP WW   10
     1CON(10),NPCON                                                     WW   11
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ WW   12
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                           WW   13
      DIMENSION CM(NP,1), CW(NW,1), CAB(1), SAB(1)                      WW   14
      EQUIVALENCE (CAB,ALP), (SAB,BET)                                  WW   15
C     SET SOURCE SEGMENT PARAMETERS                                     WW   16
      S=SI(J)                                                           WW   17
      B=BI(J)                                                           WW   18
      XJ=X(J)                                                           WW   19
      YJ=Y(J)                                                           WW   20
      ZJ=Z(J)                                                           WW   21
      CABJ=CAB(J)                                                       WW   22
      SABJ=SAB(J)                                                       WW   23
      SALPJ=SALP(J)                                                     WW   24
      IF (IEXK.EQ.0) GO TO 16                                           WW   25
C     DECIDE WETHER EXT. T.W. APPROX. CAN BE USED                       WW   26
      IPR=ICON1(J)                                                      WW   27
      IF (IPR) 1,6,2                                                    WW   28
    1 IPR=-IPR                                                          WW   29
      IF (-ICON1(IPR).NE.J) GO TO 7                                     WW   30
      GO TO 4                                                           WW   31
    2 IF (IPR.NE.J) GO TO 3                                             WW   32
      IF (CABJ*CABJ+SABJ*SABJ.GT.1.E-8) GO TO 7                         WW   33
      GO TO 5                                                           WW   34
    3 IF (ICON2(IPR).NE.J) GO TO 7                                      WW   35
    4 XI=ABS(CABJ*CAB(IPR)+SABJ*SAB(IPR)+SALPJ*SALP(IPR))               WW   36
      IF (XI.LT.0.999999) GO TO 7                                       WW   37
      IF (ABS(BI(IPR)/B-1.).GT.1.E-6) GO TO 7                           WW   38
    5 IND1=0                                                            WW   39
      GO TO 8                                                           WW   40
    6 IND1=1                                                            WW   41
      GO TO 8                                                           WW   42
    7 IND1=2                                                            WW   43
    8 IPR=ICON2(J)                                                      WW   44
      IF (IPR) 9,14,10                                                  WW   45
    9 IPR=-IPR                                                          WW   46
      IF (-ICON2(IPR).NE.J) GO TO 15                                    WW   47
      GO TO 12                                                          WW   48
   10 IF (IPR.NE.J) GO TO 11                                            WW   49
      IF (CABJ*CABJ+SABJ*SABJ.GT.1.E-8) GO TO 15                        WW   50
      GO TO 13                                                          WW   51
   11 IF (ICON1(IPR).NE.J) GO TO 15                                     WW   52
   12 XI=ABS(CABJ*CAB(IPR)+SABJ*SAB(IPR)+SALPJ*SALP(IPR))               WW   53
      IF (XI.LT.0.999999) GO TO 15                                      WW   54
      IF (ABS(BI(IPR)/B-1.).GT.1.E-6) GO TO 15                          WW   55
   13 IND2=0                                                            WW   56
      GO TO 16                                                          WW   57
   14 IND2=1                                                            WW   58
      GO TO 16                                                          WW   59
   15 IND2=2                                                            WW   60
   16 CONTINUE                                                          WW   61
C                                                                       WW   62
C     OBSERVATION LOOP                                                  WW   63
C                                                                       WW   64
```

```
      IPR=0                                                              WW  65
      DO 23 I=I1,I2                                                      WW  66
      IPR=IPR+1                                                          WW  67
      IJ=I-J                                                             WW  68
      XI=X(I)                                                            WW  69
      YI=Y(I)                                                            WW  70
      ZI=Z(I)                                                            WW  71
      AI=BI(I)                                                           WW  72
      CABI=CAB(I)                                                        WW  73
      SABI=SAB(I)                                                        WW  74
      SALPI=SALP(I)                                                      WW  75
      CALL EFLD (XI,YI,ZI,AI,IJ)                                         WW  76
      ETK=EXK*CABI+EYK*SABI+EZK*SALPI                                    WW  77
      ETS=EXS*CABI+EYS*SABI+EZS*SALPI                                    WW  78
      ETC=EXC*CABI+EYC*SABI+EZC*SALPI                                    WW  79
C                                                                        WW  80
C     FILL MATRIX ELEMENTS.  ELEMENT LOCATIONS DETERMINED BY CONNECTION  WW  81
C     DATA.                                                              WW  82
C                                                                        WW  83
      IF (ITRP.NE.0) GO TO 18                                            WW  84
C     NORMAL FILL                                                        WW  85
      DO 17 IJ=1,JSNO                                                    WW  86
      JX=JCO(IJ)                                                         WW  87
17    CM(IPR,JX)=CM(IPR,JX)+ETK*AX(IJ)+ETS*BX(IJ)+ETC*CX(IJ)             WW  88
      GO TO 23                                                           WW  89
18    IF (ITRP.EQ.2) GO TO 20                                            WW  90
C     TRANSPOSED FILL                                                    WW  91
      DO 19 IJ=1,JSNO                                                    WW  92
      JX=JCO(IJ)                                                         WW  93
19    CM(JX,IPR)=CM(JX,IPR)+ETK*AX(IJ)+ETS*BX(IJ)+ETC*CX(IJ)             WW  94
      GO TO 23                                                           WW  95
C     TRANS. FILL FOR C(WW) - TEST FOR ELEMENTS FOR D(WW)PRIME.  (=CW)   WW  96
20    DO 22 IJ=1,JSNO                                                    WW  97
      JX=JCO(IJ)                                                         WW  98
      IF (JX.GT.NR) GO TO 21                                             WW  99
      CM(JX,IPR)=CM(JX,IPR)+ETK*AX(IJ)+ETS*BX(IJ)+ETC*CX(IJ)             WW 100
      GO TO 22                                                           WW 101
21    JX=JX-NR                                                           WW 102
      CW(JX,IPR)=CW(JX,IPR)+ETK*AX(IJ)+ETS*BX(IJ)+ETC*CX(IJ)             WW 103
22    CONTINUE                                                           WW 104
23    CONTINUE                                                           WW 105
      RETURN                                                             WW 106
      END                                                                WW 107-
```

CONECT

PURPOSE

To locate segment ends that contact each other or contact the center of a surface patch.

METHOD

The ends of each segment are identified as end 1 and end 2, defined during geometry input. The connection data for segment I is stored in array variables ICON1 (I) for end 1 and ICON2 (I) for end 2.

Four conditions are possible at each segment end: (1) no connection (a free end), (2) connection to one or more other segments, (3) connection to a ground plane, or (4) connection to a surface modeled with patches. These conditions are indicated in the following way for end 1 of segment I:

(1) no connection . . . . . ICON1 (I) = 0
(2) connection to segment J . . . . . ICON1 (I) = ±J
(3) connection to a ground plane . . . . . ICON1 (I) = I
(4) connection to patch K . . . . . ICON1 (I) = 10000 + k

In case 2, if segment J has the same reference direction as segment I (end 2 of segment J connected to end 1 of segment I), the sign is positive. For opposed reference directions (end 1 to end 1) the sign is negative. If several segments connect to end 1 of segment I, then J is the number of the next connected segment in sequence.

If segment I connects to patch K, the segment end must coincide with the patch center. Patch K is then divided into four patches numbered K through K + 3 by a call to subroutine SUBPH.

The connection data is illustrated in the following listing for the six segments in the structure in figure 3.

ICON1 (I)	I	ICON2 (I)
10000 + K	1	2
1	2	3
4	3	0
0	4	-5
0	5	6
2	6	0

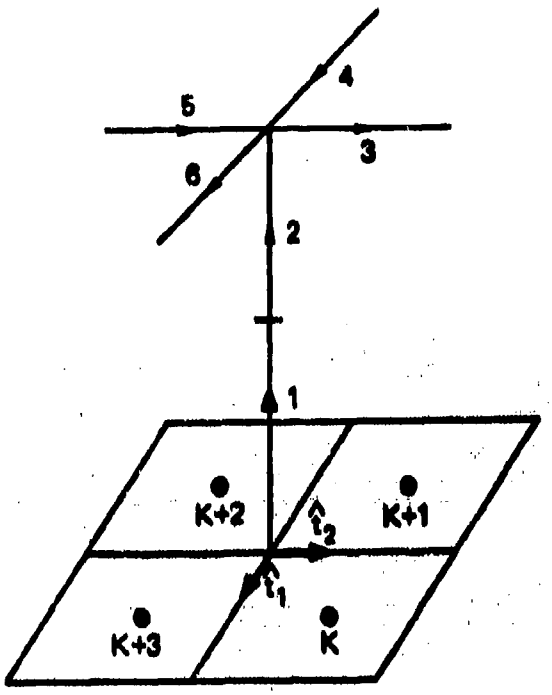


Figure 3. Structure for Illustrating Segment Connection Data.

Connections between patches are not checked, since, except where a wire connects to a surface, the current expansion function on a patch does not extend beyond that patch.

CODING

CN16 - CN27 Initialize and adjust symmetry conditions if necessary when ground is present.

CN40 - CN46 Check whether end 1 of segment I is below ground plane (error) or contacting ground plane. If the separation of the segment end and the ground is less than SMIN multiplied by the segment length, ICON1 is set to I and the z coordinate of the segment end is set to exactly zero.

CN49 - CN60 Check other segments from I + 1 through N and then 1 through I - 1, until a connected end is found. The separation of segment ends is determined by the sum of the separations in x, y, and z to save time.

CN95 - CN126 Search for segments connected to patches. Only new patches (not NGF) are checked. If a connection is found the patch is divided into four patches at its present location in the data arrays and patches following it are shifted up by three locations. This is done by calling SUBPH, an entry point of subroutine PATCH.

CN129 - CN162 Search for new segments connected to NGF patches. If a connection is found four patches, covering the area of the original patch, are added to the end of the data arrays by calling SUBPH. The original patch retains its location but the s coordinate at its center is changed to 10000.

CN182 - CN258 The loop through 44 locates segments connected to junctions.

CN183 - CN190 Parameters are initialized to find all segments connected to first end of segment J.

CN191 - CN215 Connected segments are located. If the number of any connected segment is less than J the loop is exited at CN200. Thus each junction is processed only once.

CN216 - CN230 The connected ends are set to the average of their previous values to ensure that they have identical values.

CN232 - CN244 If the junction includes new segments (NSFLG = 1) and IX is a NGF segment an equation number, NSCON, is assigned for the modified basis function of segment IX. The equation number is stored in array ICONX and the segment number is stored in ISCON.

CN245 - CN247 Segment numbers are printed for junctions of three or more segments.

CN248 - CN257 The loop is initialized for the second end of segment J and the steps from CN191 on are repeated.

CN262 - CN275 Equation numbers for modified basis functions are assigned for old segments that connect to new patches.

SYMBOL DICTIONARY

IGND = 1 to adjust symmetry for ground and set ICON (I) = I; -1 to adjust symmetry only; 0 for no ground

CONECT

JMAX	=	maximum number of segments connected to a junction
NPMAX	=	maximum number of NGF patches connecting to new segments
NSFLG	=	1 if the junction includes any new segments when NGF is in use
NSMAX	=	maximum number of NGF segments connecting to new segments
SEP	=	approximate separation of segment ends
SLEN	=	maximum separation allowed for connection
SMIN	=	maximum separation as a fraction of segment length
XI1, YI1, ZI1	=	coordinates of end 1 of segment
XI2, YI2, ZI2	=	coordinates of end 2 of segment
XS, YS, ZS	=	coordinates of patch center

CONSTANT

1.E-3	=	maximum separation tolerance for connected segments as fraction of segment length.

```
      SUBROUTINE CONECT (IGND)                                          CN   1
C                                                                       CN   2
C     CONNECT SETS UP SEGMENT CONNECTION DATA IN ARRAYS ICON1 AND ICON2  CN   3
C     BY SEARCHING FOR SEGMENT ENDS THAT ARE IN CONTACT.                CN   4
C                                                                       CN   5
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 CN   6
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( CN   7
     2300),WLAM,IPSYM                                                   CN   8
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(50),NSCON,IP CN   9
     1CON(10),NPCON                                                     CN  10
      DIMENSION X2(1), Y2(1), Z2(1)                                     CN  11
      EQUIVALENCE (X2,SI), (Y2,ALP), (Z2,BET)                           CN  12
      DATA JMAX/30/,SMIN/1.E-3/,NSMAX/50/,NPMAX/10/                     CN  13
      NSCON=0                                                           CN  14
      NPCON=0                                                           CN  15
      IF (IGND.EQ.0) GO TO 3                                            CN  16
      PRINT 54                                                          CN  17
      IF (IGND.GT.0) PRINT 55                                           CN  18
      IF (IPSYM.NE.2) GO TO 1                                           CN  19
      NP=2*NP                                                           CN  20
      MP=2*MP                                                           CN  21
1     IF (IABS(IPSYM).LE.2) GO TO 2                                     CN  22
      NP=N                                                              CN  23
      MP=M                                                              CN  24
2     IF (NP.GT.N) STOP                                                 CN  25
      IF (NP.EQ.N.AND.MP.EQ.M) IPSYM=0                                  CN  26
3     IF (N.EQ.0) GO TO 26                                              CN  27
      DO 15 I=1,N                                                       CN  28
      ICONX(I)=0                                                        CN  29
      XI1=X(I)                                                          CN  30
      YI1=Y(I)                                                          CN  31
      ZI1=Z(I)                                                          CN  32
      XI2=X2(I)                                                         CN  33
      YI2=Y2(I)                                                         CN  34
      ZI2=Z2(I)                                                         CN  35
      SLEN=SQRT((XI2-XI1)**2+(YI2-YI1)**2+(ZI2-ZI1)**2)*SMIN            CN  36
C                                                                       CN  37
C     DETERMINE CONNECTION DATA FOR END 1 OF SEGMENT.                   CN  38
C                                                                       CN  39
      IF (IGND.LT.1) GO TO 5                                            CN  40
      IF (ZI1.GT.-SLEN) GO TO 4                                         CN  41
      PRINT 56, I                                                       CN  42
      STOP                                                              CN  43
4     IF (ZI1.GT.SLEN) GO TO 5                                          CN  44
      ICON1(I)=I                                                        CN  45
      Z(I)=0.                                                           CN  46
      GO TO 9                                                           CN  47
5     IC=I                                                              CN  48
      DO 7 J=2,N                                                        CN  49
      IC=IC+1                                                           CN  50
      IF (IC.GT.N) IC=1                                                 CN  51
      SEP=ABS(XI1-X(IC))+ABS(YI1-Y(IC))+ABS(ZI1-Z(IC))                  CN  52
      IF (SEP.GT.SLEN) GO TO 6                                          CN  53
      ICON1(I)=-IC                                                      CN  54
      GO TO 8                                                           CN  55
6     SEP=ABS(XI1-X2(IC))+ABS(YI1-Y2(IC))+ABS(ZI1-Z2(IC))               CN  56
      IF (SEP.GT.SLEN) GO TO 7                                          CN  57
      ICON1(I)=IC                                                       CN  58
      GO TO 8                                                           CN  59
7     CONTINUE                                                          CN  60
      IF (I.LT.N2.AND.ICON1(I).GT.10000) GO TO 8                        CN  61
      ICON1(I)=0                                                        CN  62
C                                                                       CN  63
C     DETERMINE CONNECTION DATA FOR END 2 OF SEGMENT.                   CN  64
```

```
      C                                                                 CN  65
    8     IF (ICOND.LT.1) GO TO 12                                      CN  66
    9     IF (ZI2.GT.-SLEN) GO TO 10                                    CN  67
          PRINT 56, I                                                   CN  68
          STOP                                                          CN  69
   10     IF (ZI2.GT.SLEN) GO TO 12                                     CN  70
          IF (ICON1(I).NE.I) GO TO 11                                   CN  71
          PRINT 57, I                                                   CN  72
          STOP                                                          CN  73
   11     ICON2(I)=I                                                    CN  74
          Z2(I)=0.                                                      CN  75
          GO TO 15                                                      CN  76
   12     IC=I                                                          CN  77
          DO 14 J=2,N                                                   CN  78
          IC=IC+1                                                       CN  79
          IF (IC.GT.N) IC=1                                             CN  80
          SEP=ABS(XI2-X(IC))+ABS(YI2-Y(IC))+ABS(ZI2-Z(IC))              CN  81
          IF (SEP.GT.SLEN) GO TO 13                                     CN  82
          ICON2(I)=IC                                                   CN  83
          GO TO 15                                                      CN  84
   13     SEP=ABS(XI2-X2(IC))+ABS(YI2-Y2(IC))+ABS(ZI2-Z2(IC))           CN  85
          IF (SEP.GT.SLEN) GO TO 14                                     CN  86
          ICON2(I)=-IC                                                  CN  87
          GO TO 15                                                      CN  88
   14     CONTINUE                                                      CN  89
          IF (I.LT.N2.AND.ICON2(I).GT.10000) GO TO 15                   CN  90
          ICON2(I)=0                                                    CN  91
   15     CONTINUE                                                      CN  92
          IF (M.EQ.0) GO TO 26                                          CN  93
      C   FIND WIRE-SURFACE CONNECTIONS FOR NEW PATCHES                 CN  94
          IX=LD+1-M1                                                    CN  95
          I=M2                                                          CN  96
   16     IF (I.GT.M) GO TO 20                                          CN  97
          IX=IX-1                                                       CN  98
          XS=X(IX)                                                      CN  99
          YS=Y(IX)                                                      CN 100
          ZS=Z(IX)                                                      CN 101
          DO 18 ISEG=1,N                                                CN 102
          XI1=X(ISEG)                                                   CN 103
          YI1=Y(ISEG)                                                   CN 104
          ZI1=Z(ISEG)                                                   CN 105
          XI2=X2(ISEG)                                                  CN 106
          YI2=Y2(ISEG)                                                  CN 107
          ZI2=Z2(ISEG)                                                  CN 108
          SLEN=(ABS(XI2-XI1)+ABS(YI2-YI1)+ABS(ZI2-ZI1))*SMIN            CN 109
      C   FOR FIRST END OF SEGMENT                                      CN 110
          SEP=ABS(XI1-XS)+ABS(YI1-YS)+ABS(ZI1-ZS)                       CN 111
          IF (SEP.GT.SLEN) GO TO 17                                     CN 112
      C   CONNECTION - DIVIDE PATCH INTO 4 PATCHES AT PRESENT ARRAY LOC. CN 113
          ICON1(ISEG)=10000+I                                           CN 114
          IC=0                                                          CN 115
          CALL SUBPH (I,IC,XI1,YI1,ZI1,XI2,YI2,ZI2,XA,YA,ZA,XS,YS,ZS)   CN 116
          GO TO 19                                                      CN 117
   17     SEP=ABS(XI2-XS)+ABS(YI2-YS)+ABS(ZI2-ZS)                       CN 118
          IF (SEP.GT.SLEN) GO TO 18                                     CN 119
          ICON2(ISEG)=10000+I                                           CN 120
          IC=0                                                          CN 121
          CALL SUBPH (I,IC,XI1,YI1,ZI1,XI2,YI2,ZI2,XA,YA,ZA,XS,YS,ZS)   CN 122
          GO TO 19                                                      CN 123
   18     CONTINUE                                                      CN 124
   19     I=I+1                                                         CN 125
          GO TO 16                                                      CN 126
      C   REPEAT SEARCH FOR NEW SEGMENTS CONNECTED TO NGF PATCHES.      CN 127
   20     IF (M1.EQ.0.OR.N2.GT.N) GO TO 26                              CN 128
```

```
      IX=LD+1                                                                  CN 129
      I=1                                                                      CN 130
   21 IF (I.GT.M1) GO TO 25                                                    CN 131
      IX=IX-1                                                                  CN 132
      XS=X(IX)                                                                 CN 133
      YS=Y(IX)                                                                 CN 134
      ZS=Z(IX)                                                                 CN 135
      DO 23 ISEG=N2,N                                                          CN 136
      XI1=X(ISEG)                                                              CN 137
      YI1=Y(ISEG)                                                              CN 138
      ZI1=Z(ISEG)                                                              CN 139
      XI2=X2(ISEG)                                                             CN 140
      YI2=Y2(ISEG)                                                             CN 141
      ZI2=Z2(ISEG)                                                             CN 142
      SLEN=(ABS(XI2-XI1)+ABS(YI2-YI1)+ABS(ZI2-ZI1))*SMIN                       CN 143
      SEP=ABS(XI1-XS)+ABS(YI1-YS)+ABS(ZI1-ZS)                                  CN 144
      IF (SEP.GT.SLEN) GO TO 22                                                CN 145
      ICON1(ISEG)=10001+M                                                      CN 146
      IC=1                                                                     CN 147
      NPCON=NPCON+1                                                            CN 148
      IPCON(NPCON)=I                                                           CN 149
      CALL SUBPH (I,IC,XI1,YI1,ZI1,XI2,YI2,ZI2,XA,YA,ZA,XS,YS,ZS)              CN 150
      GO TO 24                                                                 CN 151
   22 SEP=ABS(XI2-XS)+ABS(YI2-YS)+ABS(ZI2-ZS)                                  CN 152
      IF (SEP.GT.SLEN) GO TO 23                                                CN 153
      ICON2(ISEG)=10001+M                                                      CN 154
      IC=1                                                                     CN 155
      NPCON=NPCON+1                                                            CN 156
      IPCON(NPCON)=I                                                           CN 157
      CALL SUBPH (I,IC,XI1,YI1,ZI1,XI2,YI2,ZI2,XA,YA,ZA,XS,YS,ZS)              CN 158
      GO TO 24                                                                 CN 159
   23 CONTINUE                                                                 CN 160
   24 I=I+1                                                                    CN 161
      GO TO 21                                                                 CN 162
   25 IF (NPCON.LE.NPMAX) GO TO 26                                             CN 163
      PRINT 62, NPMAX                                                          CN 164
      STOP                                                                     CN 165
   26 PRINT 58, N,NP,IPSYM                                                     CN 166
      IF (M.GT.0) PRINT 61, M,MP                                               CN 167
      ISEG=(N+M)/(NP+MP)                                                       CN 168
      IF (ISEG.EQ.1) GO TO 30                                                  CN 169
      IF (IPSYM) 28,27,29                                                      CN 170
   27 STOP                                                                     CN 171
   28 PRINT 59, ISEG                                                           CN 172
      GO TO 30                                                                 CN 173
   29 IC=ISEG/2                                                                CN 174
      IF (ISEG.EQ.8) IC=3                                                      CN 175
      PRINT 60, IC                                                             CN 176
   30 IF (N.EQ.0) GO TO 48                                                     CN 177
      PRINT 50                                                                 CN 178
      ISEG=0                                                                   CN 179
C     ADJUST CONNECTED SEG. ENDS TO EXACTLY COINCIDE.  PRINT JUNCTIONS         CN 180
C     OF 3 OR MORE SEG.  ALSO FIND OLD SEG. CONNECTING TO NEW SEG.             CN 181
      DO 44 J=1,N                                                              CN 182
      IEND=-1                                                                  CN 183
      JEND=-1                                                                  CN 184
      IX=ICON1(J)                                                              CN 185
      IC=1                                                                     CN 185
      JCO(1)=-J                                                                CN 187
      XA=X(J)                                                                  CN 188
      YA=Y(J)                                                                  CN 189
      ZA=Z(J)                                                                  CN 190
   31 IF (IX.EQ.0) GO TO 43                                                    CN 191
      IF (IX.EQ.J) GO TO 43                                                    CN 192
```

```
      IF (IX.GT.10000) GO TO 43                                         CN 193
      NSFLG=0                                                           CN 194
   32 IF (IX) 33,49,34                                                  CN 195
   33 IX=-IX                                                            CN 196
      GO TO 35                                                          CN 197
   34 JEND=-JEND                                                        CN 198
   35 IF (IX.EQ.J) GO TO 37                                             CN 199
      IF (IX.LT.J) GO TO 43                                             CN 200
      IC=IC+1                                                           CN 201
      IF (IC.GT.JMAX) GO TO 49                                          CN 202
      JCO(IC)=IX*JEND                                                   CN 203
      IF (IX.GT.N1) NSFLG=1                                             CN 204
      IF (JEND.EQ.1) GO TO 36                                           CN 205
      XA=XA+X(IX)                                                       CN 206
      YA=YA+Y(IX)                                                       CN 207
      ZA=ZA+Z(IX)                                                       CN 208
      IX=ICON1(IX)                                                      CN 209
      GO TO 32                                                          CN 210
   36 XA=XA+X2(IX)                                                      CN 211
      YA=YA+Y2(IX)                                                      CN 212
      ZA=ZA+Z2(IX)                                                      CN 213
      IX=ICON2(IX)                                                      CN 214
      GO TO 32                                                          CN 215
   37 SEP=IC                                                            CN 216
      XA=XA/SEP                                                         CN 217
      YA=YA/SEP                                                         CN 218
      ZA=ZA/SEP                                                         CN 219
      DO 39 I=1,IC                                                      CN 220
      IX=JCO(I)                                                         CN 221
      IF (IX.GT.0) GO TO 38                                             CN 222
      IX=-IX                                                            CN 223
      X(IX)=XA                                                          CN 224
      Y(IX)=YA                                                          CN 225
      Z(IX)=ZA                                                          CN 226
      GO TO 39                                                          CN 227
   38 X2(IX)=XA                                                         CN 228
      Y2(IX)=YA                                                         CN 229
      Z2(IX)=ZA                                                         CN 230
   39 CONTINUE                                                          CN 231
      IF (N1.EQ.0) GO TO 42                                             CN 232
      IF (NSFLG.EQ.0) GO TO 42                                          CN 233
      DO 41 I=1,IC                                                      CN 234
      IX=IABS(JCO(I))                                                   CN 235
      IF (IX.GT.N1) GO TO 41                                            CN 236
      IF (ICONX(IX).NE.0) GO TO 41                                      CN 237
      NSCON=NSCON+1                                                     CN 238
      IF (NSCON.LE.NSMAX) GO TO 40                                      CN 239
      PRINT 62, NSMAX                                                   CN 240
      STOP                                                              CN 241
   40 ISCON(NSCON)=IX                                                   CN 242
      ICONX(IX)=NSCON                                                   CN 243
   41 CONTINUE                                                          CN 244
   42 IF (IC.LT.3) GO TO 43                                             CN 245
      ISEG=ISEG+1                                                       CN 246
      PRINT 51, ISEG,(JCO(I),I=1,IC)                                    CN 247
   43 IF (IEND.EQ.1) GO TO 44                                           CN 248
      IEND=1                                                            CN 249
      JEND=1                                                            CN 250
      IX=ICON2(J)                                                       CN 251
      IC=1                                                              CN 252
      JCO(1)=J                                                          CN 253
      XA=X2(J)                                                          CN 254
      YA=Y2(J)                                                          CN 255
      ZA=Z2(J)                                                          CN 256
```

```
      GO TO 31                                                          CN 257
   44 CONTINUE                                                          CN 258
      IF (ISEG.EQ.0) PRINT 52                                           CN 259
      IF (N1.EQ.0.OR.M1.EQ.M) GO TO 48                                  CN 260
C     FIND OLD SEGMENTS THAT CONNECT TO NEW PATCHES                     CN 261
      DO 47 J=1,N1                                                      CN 262
      IX=ICON1(J)                                                       CN 263
      IF (IX.LT.10000) GO TO 45                                         CN 264
      IX=IX-10000                                                       CN 265
      IF (IX.GT.M1) GO TO 46                                            CN 266
   45 IX=ICON2(J)                                                       CN 267
      IF (IX.LT.10000) GO TO 47                                         CN 268
      IX=IX-10000                                                       CN 269
      IF (IX.LT.M2) GO TO 47                                            CN 270
   46 IF (ICONX(J).NE.0) GO TO 47                                       CN 271
      NSCON=NSCON+1                                                     CN 272
      ISCON(NSCON)=J                                                    CN 273
      ICONX(J)=NSCON                                                    CN 274
   47 CONTINUE                                                          CN 275
   48 CONTINUE                                                          CN 276
      RETURN                                                            CN 277
   49 PRINT 53, IX                                                      CN 278
      STOP                                                              CN 279
C                                                                       CN 280
   50 FORMAT (//,9X,27H- MULTIPLE WIRE JUNCTIONS -,/,1X,8HJUNCTION,4X,36 CN 281
     1HSEGMENTS  (- FOR END 1, + FOR END 2))                            CN 282
   51 FORMAT (1X,I5,5X,20I5,/,(11X,20I5))                               CN 283
   52 FORMAT (2X,4HNONE)                                                CN 284
   53 FORMAT (47H CONNECT - SEGMENT CONNECTION ERROR FOR SEGMENT,I5)     CN 285
   54 FORMAT (/,3X,23HGROUND PLANE SPECIFIED.)                          CN 286
   55 FORMAT (/,3X,46HWHERE WIRE ENDS TOUCH GROUND, CURRENT WILL BE ,38H CN 287
     1INTERPOLATED TO IMAGE IN GROUND PLANE../)                         CN 288
   56 FORMAT (30H GEOMETRY DATA ERROR-- SEGMENT,I5,21H EXTENDS BELOW GRO CN 289
     1UND)                                                              CN 290
   57 FORMAT (29H GEOMETRY DATA ERROR--SEGMENT,I5,16H LIES IN GROUND ,6H CN 291
     1PLANE.)                                                           CN 292
   58 FORMAT (/,3X,20HTOTAL SEGMENTS USED=,I5,5X,12HNO. SEG. IN ,17HA SY CN 293
     1MMETRIC CELL=,I5,5X,14HSYMMETRY FLAG=,I3)                         CN 294
   59 FORMAT (14H STRUCTURE HAS,I4,25H FOLD ROTATIONAL SYMMETRY,/)      CN 295
   60 FORMAT (14H STRUCTURE HAS,I2,19H PLANES OF SYMMETRY,/)            CN 296
   61 FORMAT (3X,19HTOTAL PATCHES USED=,I5,8X,32HNO. PATCHES IN A SYMMET CN 297
     1RIC CELL=,I5)                                                     CN 298
   62 FORMAT (82H ERROR -- NO. NEW SEGMENTS CONNECTED TO N.G.F. SEGMENTSO CN 299
     1R PATCHES EXCEEDS LIMIT OF,I5)                                    CN 300
      END                                                               CN 301-
```

COUPLE

PURPOSE

To compute the maximum coupling between pairs of segments.

METHOD

If a coupling calculation has been requested (CP card) subroutine COUPLE is called each time that the current is computed for a new excitation. The code from CP10 to CP12 checks that the excitation is a single applied-field voltage source on the segment specified in NCTAG and NCSEG. If the excitation is correct the input admittance and mutual admittances to all other segments specified in NCTAG and NCSEG are stored in Y11A and Y12A from CP13 to CP22.

When all segments have been excited (ICOUP = NCOUP) the second part of the code, from CP24 to CP58 is executed to evaluate the equations in Section V.6 of Part I.

SYMBOL DICTIONARY

C = L (see Part I, Section V.6)
CUR = array of values of current at the centers of segments
DBC = 10 $\log(G_{MAX})$
GMAX = G_{MAX}
ISG1 = segment number
ISG2 = segment number
J1 = index of Y_{12} in array Y12A
J2 = index of Y_{21} in array Y12A
K = segment number
RHO = ρ
WLAM = wavelength
Y11 = Y_{11}
Y12 = $(Y_{12} + Y_{21})/2$
Y22 = Y_{22}
YIN = Y_{IN}
YL = Y_{L}
ZIN = $1/Y_{IN}$
ZL = $1/Y_{L}$

```
      SUBROUTINE COUPLE (CUR,WLAM)                                      CP   1
C                                                                       CP   2
C     COUPLE COMPUTES THE MAXIMUM COUPLING BETWEEN PAIRS OF SEGMENTS.   CP   3
C                                                                       CP   4
      COMPLEX Y11A,Y12A,CUR,Y11,Y12,Y22,YL,YIN,ZL,ZIN,RHO,VQD,VSANT,VQDS CP   5
      COMMON /YPARM/ NCOUP,ICOUP,NCTAG(5),NCSEG(5),Y11A(5),Y12A(20)     CP   6
      COMMON /VSORC/ VQD(30),VSANT(30),VQDS(30),IVQD(30),ISANT(30),IQDS( CP   7
     130),NVQD,NSANT,NQDS                                               CP   8
      DIMENSION CUR(1)                                                  CP   9
      IF (NSANT.NE.1.OR.NVQD.NE.0) RETURN                               CP  10
      J=ISEGNO(NCTAG(ICOUP+1),NCSEG(ICOUP+1))                           CP  11
      IF (J.NE.ISANT(1)) RETURN                                         CP  12
      ICOUP=ICOUP+1                                                     CP  13
      ZIN=VSANT(1)                                                      CP  14
      Y11A(ICOUP)=CUR(J)*WLAM/ZIN                                       CP  15
      L1=(ICOUP-1)*(NCOUP-1)                                            CP  16
      DO 1 I=1,NCOUP                                                    CP  17
      IF (I.EQ.ICOUP) GO TO 1                                           CP  18
      K=ISEGNO(NCTAG(I),NCSEG(I))                                       CP  19
      L1=L1+1                                                           CP  20
      Y12A(L1)=CUR(K)*WLAM/ZIN                                          CP  21
1     CONTINUE                                                          CP  22
      IF (ICOUP.LT.NCOUP) RETURN                                        CP  23
      PRINT 6                                                           CP  24
      NPM1=NCOUP-1                                                      CP  25
      DO 5 I=1,NPM1                                                     CP  26
      ITT1=NCTAG(I)                                                     CP  27
      ITS1=NCSEG(I)                                                     CP  28
      ISG1=ISEGNO(ITT1,ITS1)                                            CP  29
      L1=I+1                                                            CP  30
      DO 5 J=L1,NCOUP                                                   CP  31
      ITT2=NCTAG(J)                                                     CP  32
      ITS2=NCSEG(J)                                                     CP  33
      ISG2=ISEGNO(ITT2,ITS2)                                            CP  34
      J1=J+(I-1)*NPM1-1                                                 CP  35
      J2=I+(J-1)*NPM1                                                   CP  36
      Y11=Y11A(I)                                                       CP  37
      Y22=Y11A(J)                                                       CP  38
      Y12=.5*(Y12A(J1)+Y12A(J2))                                        CP  39
      YIN=Y12*Y12                                                       CP  40
      DBC=CABS(YIN)                                                     CP  41
      C=DBC/(2.*REAL(Y11)*REAL(Y22)-REAL(YIN))                          CP  42
      IF (C.LT.0..OR.C.GT.1.) GO TO 4                                   CP  43
      IF (C.LT..01) GO TO 2                                             CP  44
      GMAX=(1.-SQRT(1.-C*C))/C                                          CP  45
      GO TO 3                                                           CP  46
2     GMAX=.5*(C+.25*C*C*C)                                             CP  47
3     RHO=GMAX*CONJG(YIN)/DBC                                           CP  48
      YL=((1.-RHO)/(1.+RHO)+1.)*REAL(Y22)-Y22                           CP  49
      ZL=1./YL                                                          CP  50
      YIN=Y11-YIN/(Y22+YL)                                              CP  51
      ZIN=1./YIN                                                        CP  52
      DBC=DB10(GMAX)                                                    CP  53
      PRINT 7, ITT1,ITS1,ISG1,ITT2,ITS2,ISG2,DBC,ZL,ZIN                 CP  54
      GO TO 5                                                           CP  55
4     PRINT 8, ITT1,ITS1,ISG1,ITT2,ITS2,ISG2,C                          CP  56
5     CONTINUE                                                          CP  57
      RETURN                                                            CP  58
C                                                                       CP  59
6     FORMAT (///,36X,26H- - - ISOLATION DATA - - -,//,6X,24H- - COUPLIN CP  60
     1G BETWEEN - - -,8X,7HMAXIMUM,15X,32H- - - FOR MAXIMUM COUPLING - - - CP  61
     2,/,12X,4HSEG.,14X,4HSEG.,3X,8HCOUPLING,4X,25HLOAD IMPEDANCE (2ND S CP  62
     3EG.),7X,15HINPUT IMPEDANCE,/,2X,8HTAG/SEG.,3X,3HNO.,4X,8HTAG/SEG., CP  63
     43X,3HNO.,6X,4H(DB),8X,4HREAL,9X,5HIMAG.,9X,4HREAL,8X,5HIMAG.)     CP  64
```

```
 65 7     FORMAT (2(1X,I4,1X,I4,1X,I5,2X),F9.3,2X,2(2X,E12.5,1X,E12.5))      CP  65
 66 8     FORMAT (2(1X,I4,1X,I4,1X,I5,2X)45H**ERROR** COUPLING IS NOT BETWEE CP  66
 67      1N 0 AND 1. (=,E12.5,1H))                                           CP  67
 68       END                                                                CP  68-
```

DATAGN

PURPOSE

To read structure input data and set segment and patch data.

METHOD

The main READ statement is at DA35. The READ statement at DA65 is for the continuation of wire data (GC card following GW), and the READ at DA133 is for the continuation of surface patch data (SC following SP or SM).

The first input parameter GM determines the function of the card as indicated in the following table:

GM	GØ TØ	FUNCTION
GA	8	define wire arc
GC	6	continuation of wire data
GE	29	end of geometry data
GF	27	read NGF file
GM	26	rotate or translate structure
GR	19	rotate about Z axis (symmetry)
GS	21	scale structure
GW	3	define straight wire
GX	18	reflect in coordinate planes (symmetry)
SC	10	continuation of patch data
SM	13	define multiple surface patches
SP	9	define surface patch

The functions of the other input parameters depend on the type of data card and can be determined from the data card descriptions in Part III of this manual.

Subroutines are called to perform many of the operations requested by the data cards. Coding in DATAGN performs other operations, prints information and checks for input errors. After a GE card is read subroutine CONECT is called at DA211 to find electrical connections of segments. Segment and patch data is printed from DA217 to DA256. Line DA241 tests for segments of zero length ($<10^{-20}$) or zero radius ($<10^{-101}$).

SYMBOL DICTIONARY

Variables have multiple uses which depend on the type of input card being processed.

```
      SUBROUTINE DATAGN                                                 DA   1
C                                                                       DA   2
C     DATAGN IS THE MAIN ROUTINE FOR INPUT OF GEOMETRY DATA.            DA   3
C                                                                       DA   4
      INTEGER GM,ATST                                                   DA   5
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 DA   6
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( DA   7
     2300),WLAM,IPSYM                                                   DA   8
      COMMON /ANGL/ SALP(300)                                           DA   9
      DIMENSION X2(1), Y2(1), Z2(1), T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y DA  10
     1(1), T2Z(1), ATST(12), IFX(2), IFY(2), IFZ(2), CAB(1), SAB(1), IPT DA  11
     2(4)                                                               DA  12
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON DA  13
     12), (T2Z,ITAG), (X2,SI), (Y2,ALP), (Z2,BET), (CAB,ALP), (SAB,BET) DA  14
      DATA ATST/2HGW,2HGX,2HGR,2HGS,2HGE,2HGM,2HSP,2HSM,2HGF,2HGA,2HSC,2 DA  15
     1HGC/                                                              DA  16
      DATA IFX/1H ,1HX/,IFY/1H ,1HY/,IFZ/1H ,1HZ/                       DA  17
      DATA TA/0.01745329252/,TD/57.29577951/,IPT/1HP,1HR,1HT,1HQ/       DA  18
      IPSYM=0                                                           DA  19
      NWIRE=0                                                           DA  20
      N=0                                                               DA  21
      NP=0                                                              DA  22
      M=0                                                               DA  23
      MP=0                                                              DA  24
      N1=0                                                              DA  25
      N2=1                                                              DA  26
      M1=0                                                              DA  27
      M2=1                                                              DA  28
      ISCT=0                                                            DA  29
      IPHD=0                                                            DA  30
C                                                                       DA  31
C     READ GEOMETRY DATA CARD AND BRANCH TO SECTION FOR OPERATION       DA  32
C     REQUESTED                                                         DA  33
C                                                                       DA  34
1     READ (5,42) GM,ITG,NS,XW1,YW1,ZW1,XW2,YW2,ZW2,RAD                 DA  35
      IF (N+M.GT.LD) GO TO 37                                           DA  36
      IF (GM.EQ.ATST(9)) GO TO 27                                       DA  37
      IF (IPHD.EQ.1) GO TO 2                                            DA  38
      PRINT 40                                                          DA  39
      PRINT 41                                                          DA  40
      IPHD=1                                                            DA  41
2     IF (GM.EQ.ATST(11)) GO TO 10                                      DA  42
      ISCT=0                                                            DA  43
      IF (GM.EQ.ATST(1)) GO TO 3                                        DA  44
      IF (GM.EQ.ATST(2)) GO TO 18                                       DA  45
      IF (GM.EQ.ATST(3)) GO TO 19                                       DA  46
      IF (GM.EQ.ATST(4)) GO TO 21                                       DA  47
      IF (GM.EQ.ATST(7)) GO TO 9                                        DA  48
      IF (GM.EQ.ATST(8)) GO TO 13                                       DA  49
      IF (GM.EQ.ATST(5)) GO TO 29                                       DA  50
      IF (GM.EQ.ATST(6)) GO TO 26                                       DA  51
      IF (GM.EQ.ATST(10)) GO TO 8                                       DA  52
      GO TO 38                                                          DA  53
C                                                                       DA  54
C     GENERATE SEGMENT DATA FOR STRAIGHT WIRE.                          DA  55
C                                                                       DA  56
3     NWIRE=NWIRE+1                                                     DA  57
      I1=N+1                                                            DA  58
      I2=N+NS                                                           DA  59
      PRINT 43, NWIRE,XW1,YW1,ZW1,XW2,YW2,ZW2,RAD,NS,I1,I2,ITG          DA  60
      IF (RAD.EQ.0) GO TO 4                                             DA  61
      XS1=1.                                                            DA  62
      YS1=1.                                                            DA  63
      GO TO 7                                                           DA  64
```

```
      4     READ (5,42) GM,IX,IY,XS1,YS1,ZS1                                  DA  65
            IF (GM.EQ.AYST(12)) GO TO 6                                       DA  66
      5     PRINT 48                                                          DA  67
            STOP                                                              DA  68
      6     PRINT 51, XS1,YS1,ZS1                                             DA  69
            IF (YS1.EQ.0.OR.ZS1.EQ.0) GO TO 5                                 DA  70
            RAD=YS1                                                           DA  71
            YS1=(ZS1/YS1)**(1./(NS-1.))                                       DA  72
      7     CALL WIRE (XW1,YW1,ZW1,XW2,YW2,ZW2,RAD,XS1,YS1,NS,ITG)            DA  73
            GO TO 1                                                           DA  74
      C                                                                       DA  75
      C     GENERATE SEGMENT DATA FOR WIRE ARC                                DA  76
      C                                                                       DA  77
      8     NWIRE=NWIRE+1                                                     DA  78
            I1=N+1                                                            DA  79
            I2=N+NS                                                           DA  80
            PRINT 38, NWIRE,XW1,YW1,ZW1,XW2,NS,I1,I2,ITG                      DA  81
            CALL ARC (ITG,NS,XW1,YW1,ZW1,XW2)                                 DA  82
            GO TO 1                                                           DA  83
      C                                                                       DA  84
      C     GENERATE SINGLE NEW PATCH                                         DA  85
      C                                                                       DA  86
      9     I1=M+1                                                            DA  87
            NS=NS+1                                                           DA  88
            IF (ITG.NE.0) GO TO 17                                            DA  89
            PRINT 51, I1,IPT(NS),XW1,YW1,ZW1,XW2,YW2,ZW2                      DA  90
            IF (NS.EQ.2.OR.NS.EQ.4) ISCT=1                                    DA  91
            IF (NS.GT.1) GO TO 14                                             DA  92
            XW2=XW2*TA                                                        DA  93
            YW2=YW2*TA                                                        DA  94
            GO TO 16                                                          DA  95
     10     IF (ISCT.EQ.0) GO TO 17                                           DA  96
            I1=M+1                                                            DA  97
            NS=NS+1                                                           DA  98
            IF (ITG.NE.0) GO TO 17                                            DA  99
            IF (NS.NE.2.AND.NS.NE.4) GO TO 17                                 DA 100
            XS1=X4                                                            DA 101
            YS1=Y4                                                            DA 102
            ZS1=Z4                                                            DA 103
            XS2=X3                                                            DA 104
            YS2=Y3                                                            DA 105
            ZS2=Z3                                                            DA 106
            X3=XW1                                                            DA 107
            Y3=YW1                                                            DA 108
            Z3=ZW1                                                            DA 109
            IF (NS.NE.4) GO TO 11                                             DA 110
            X4=XW2                                                            DA 111
            Y4=YW2                                                            DA 112
            Z4=ZW2                                                            DA 113
     11     XW1=XS1                                                           DA 114
            YW1=YS1                                                           DA 115
            ZW1=ZS1                                                           DA 116
            XW2=XS2                                                           DA 117
            YW2=YS2                                                           DA 118
            ZW2=ZS2                                                           DA 119
            IF (NS.EQ.4) GO TO 12                                             DA 120
            X4=XW1+X3-XW2                                                     DA 121
            Y4=YW1+Y3-YW2                                                     DA 122
            Z4=ZW1+Z3-ZW2                                                     DA 123
     12     PRINT 51, I1,IPT(NS),XW1,YW1,ZW1,XW2,YW2,ZW2                      DA 124
            PRINT 39, X3,Y3,Z3,X4,Y4,Z4                                       DA 125
            GO TO 16                                                          DA 126
      C                                                                       DA 127
      C     GENERATE MULTIPLE-PATCH SURFACE                                   DA 128
```

```
      C                                                                 DA 129
   13 I1=M+1                                                            DA 130
      PRINT 59, I1,IPT(2),XW1,YW1,ZW1,XW2,YW2,ZW2,ITG,NS                DA 131
      IF (ITG.LT.1.OR.NS.LT.1) GO TO 17                                 DA 132
   14 READ (5,42) GM,IX,IY,X3,Y3,Z3,X4,Y4,Z4                           DA 133
      IF (NS.NE.2.AND.ITG.LT.1) GO TO 18                                DA 134
      X4=XW1+X3-XW2                                                     DA 135
      Y4=YW1+Y3-YW2                                                     DA 136
      Z4=ZW1+Z3-ZW2                                                     DA 137
   15 PRINT 39, X3,Y3,Z3,X4,Y4,Z4                                       DA 138
      IF (GM.NE.ATST(11)) GO TO 17                                      DA 139
   16 CALL PATCH (ITG,NS,XW1,YW1,ZW1,XW2,YW2,ZW2,X3,Y3,Z3,X4,Y4,Z4)     DA 140
      GO TO 1                                                           DA 141
   17 PRINT 60                                                          DA 142
      STOP                                                              DA 143
      C                                                                 DA 144
      C     REFLECT STRUCTURE ALONG X,Y, OR Z AXES OR ROTATE TO FORM CYLINDER. DA 145
      C                                                                 DA 146
   18 IY=NS/10                                                          DA 147
      IZ=NS-IY*10                                                       DA 148
      IX=IY/10                                                          DA 149
      IY=IY-IX*10                                                       DA 150
      IF (IX.NE.0) IX=1                                                 DA 151
      IF (IY.NE.0) IY=1                                                 DA 152
      IF (IZ.NE.0) IZ=1                                                 DA 153
      PRINT 44, IFX(IX+1),IFY(IY+1),IFZ(IZ+1),ITG                       DA 154
      GO TO 20                                                          DA 155
   19 PRINT 45, NS,ITG                                                  DA 156
      IX=-1                                                             DA 157
   20 CALL REFLC (IX,IY,IZ,ITG,NS)                                      DA 158
      GO TO 1                                                           DA 159
      C                                                                 DA 160
      C     SCALE STRUCTURE DIMENSIONS BY FACTOR XW1.                   DA 161
      C                                                                 DA 162
   21 IF (N.LT.N2) GO TO 23                                             DA 163
      DO 22 I=N2,N                                                      DA 164
      X(I)=X(I)*XW1                                                     DA 165
      Y(I)=Y(I)*XW1                                                     DA 166
      Z(I)=Z(I)*XW1                                                     DA 167
      X2(I)=X2(I)*XW1                                                   DA 168
      Y2(I)=Y2(I)*XW1                                                   DA 169
      Z2(I)=Z2(I)*XW1                                                   DA 170
   22 BI(I)=BI(I)*XW1                                                   DA 171
   23 IF (M.LT.M2) GO TO 25                                             DA 172
      YW1=XW1*XW1                                                       DA 173
      IX=LD+1-M                                                         DA 174
      IY=LD-M1                                                          DA 175
      DO 24 I=IX,IY                                                     DA 176
      X(I)=X(I)*XW1                                                     DA 177
      Y(I)=Y(I)*XW1                                                     DA 178
      Z(I)=Z(I)*XW1                                                     DA 179
   24 BI(I)=BI(I)*YW1                                                   DA 180
   25 PRINT 46, XW1                                                     DA 181
      GO TO 1                                                           DA 182
      C                                                                 DA 183
      C     MOVE STRUCTURE OR REPRODUCE ORIGINAL STRUCTURE IN NEW POSITIONS. DA 184
      C                                                                 DA 185
   26 PRINT 47, ITG,NS,XW1,YW1,ZW1,XW2,YW2,ZW2,RAD                      DA 186
      XW1=XW1*TA                                                        DA 187
      YW1=YW1*TA                                                        DA 188
      ZW1=ZW1*TA                                                        DA 189
      CALL MOVE (XW1,YW1,ZW1,XW2,YW2,ZW2,INT(RAD+.5),NS,ITG)            DA 190
      GO TO 1                                                           DA 191
      C                                                                 DA 192
```

```
      C     READ NUMERICAL GREEN'S FUNCTION TAPE                                    DA 193
      C                                                                             DA 194
   27       IF (N+M.EQ.0) GO TO 28                                                  DA 195
            PRINT 52                                                                DA 196
            STOP                                                                    DA 197
   28       CALL GFIL (ITG)                                                         DA 198
            NPSAV=NP                                                                DA 199
            MPSAV=MP                                                                DA 200
            IPSAV=IPSYM                                                             DA 201
            GO TO 1                                                                 DA 202
      C                                                                             DA 203
      C     TERMINATE STRUCTURE GEOMETRY INPUT.                                     DA 204
      C                                                                             DA 205
   29       IX=N1+M1                                                                DA 206
            IF (IX.EQ.0) GO TO 30                                                   DA 207
            NP=N                                                                    DA 208
            MP=M                                                                    DA 209
            IPSYM=0                                                                 DA 210
   30       CALL CONECT (ITG)                                                       DA 211
            IF (IX.EQ.0) GO TO 31                                                   DA 212
            NP=NPSAV                                                                DA 213
            MP=MPSAV                                                                DA 214
            IPSYM=IPSAV                                                             DA 215
   31       IF (N+M.GT.LD) GO TO 37                                                 DA 216
            IF (N.EQ.0) GO TO 33                                                    DA 217
            PRINT 53                                                                DA 218
            PRINT 54                                                                DA 219
            DO 32 I=1,N                                                             DA 220
            XW1=X2(I)-X(I)                                                          DA 221
            YW1=Y2(I)-Y(I)                                                          DA 222
            ZW1=Z2(I)-Z(I)                                                          DA 223
            X(I)=(X(I)+X2(I))*.5                                                    DA 224
            Y(I)=(Y(I)+Y2(I))*.5                                                    DA 225
            Z(I)=(Z(I)+Z2(I))*.5                                                    DA 226
            XW2=XW1*XW1+YW1*YW1+ZW1*ZW1                                             DA 227
            YW2=SQRT(XW2)                                                           DA 228
            YW2=(XW2/YW2+YW2)*.5                                                    DA 229
            SI(I)=YW2                                                               DA 230
            CAB(I)=XW1/YW2                                                          DA 231
            SAB(I)=YW1/YW2                                                          DA 232
            XW2=ZW1/YW2                                                             DA 233
            IF (XW2.GT.1.) XW2=1.                                                   DA 234
            IF (XW2.LT.-1.) XW2=-1.                                                 DA 235
            SALP(I)=XW2                                                             DA 236
            XW2=ASIN(XW2)*TD                                                        DA 237
            YW2=ATGN2(YW1,XW1)*TD                                                   DA 238
            PRINT 55, I,X(I),Y(I),Z(I),SI(I),XW2,YW2,BI(I),ICON1(I),I,ICON2(I)      DA 239
           1,ITAG(I)                                                                DA 240
            IF (SI(I).GT.1.E-20.AND.BI(I).GT.1.E-101) GO TO 32                      DA 241
            PRINT 56                                                                DA 242
            STOP                                                                    DA 243
   32       CONTINUE                                                                DA 244
   33       IF (M.EQ.0) GO TO 35                                                    DA 245
            PRINT 57                                                                DA 246
            J=LD+1                                                                  DA 247
            DO 34 I=1,M                                                             DA 248
            J=J-1                                                                   DA 249
            XW1=(T1Y(J)*T2Z(J)-T1Z(J)*T2Y(J))*SALP(J)                               DA 250
            YW1=(T1Z(J)*T2X(J)-T1X(J)*T2Z(J))*SALP(J)                               DA 251
            ZW1=(T1X(J)*T2Y(J)-T1Y(J)*T2X(J))*SALP(J)                               DA 252
            PRINT 58, I,X(J),Y(J),Z(J),XW1,YW1,ZW1,BI(J),T1X(J),T1Y(J),T1Z(J),      DA 253
           1T2X(J),T2Y(J),T2Z(J)                                                    DA 254
   34       CONTINUE                                                                DA 255
   35       RETURN                                                                  DA 256
```

```
      PRINT 48                                                          DA 257
      PRINT 49, GM,ITG,NS,XW1,YW1,ZW1,XW2,YW2,ZW2,RAD                   DA 258
      STOP                                                              DA 259
      PRINT 50                                                          DA 260
      STOP                                                              DA 261
C                                                                       DA 262
   48 FORMAT (1X,I5,2X,12HARC RADIUS =,F9.5,2X,4HFROM,F8.3,3H TO,F8.3,6H DA 263
     1 DEGREES,11X,F11.5,2X,I5,4X,I5,1X,I5,3X,I5)                       DA 264
   49 FORMAT (6X,3F11.5,1X,3F11.5)                                      DA 265
   50 FORMAT (////,33X,35H- - - STRUCTURE SPECIFICATION - - -,//,37X,28H DA 266
     1COORDINATES MUST BE INPUT IN,/,37X,29HMETERS OR BE SCALED TO METER DA 267
     2S,/,37X,31HBEFORE STRUCTURE INPUT IS ENDED,//)                    DA 268
   41 FORMAT (2X,4HWIRE,79X,6HNO. OF,4X,5HFIRST,2X,4HLAST,5X,3HTAG,/,2X, DA 269
     13HNO.,8X,2HX1,9X,2HY1,9X,2HZ1,10X,2HX2,9X,2HY2,9X,2HZ2,6X,6HRADIUS DA 270
     2,3X,4HSEG.,5X,4HSEG.,3X,4HSEG.,5X,3HNO.)                          DA 271
   42 FORMAT (A2,I3,I5,7F10.5)                                          DA 272
   43 FORMAT (1X,I5,3F11.5,1X,4F11.5,2X,I5,4X,I5,1X,I5,3X,I5)           DA 273
   44 FORMAT (6X,34HSTRUCTURE REFLECTED ALONG THE AXES,3(1X,A1),22H.  TA DA 274
     1GS INCREMENTED BY,I5)                                             DA 275
   45 FORMAT (6X,30HSTRUCTURE ROTATED ABOUT Z-AXIS,I3,30H TIMES.  LABLES DA 276
     1 INCREMENTED BY,I5)                                               DA 277
   46 FORMAT (6X,26HSTRUCTURE SCALED BY FACTOR,F10.5)                   DA 278
   47 FORMAT (6X,49HTHE STRUCTURE HAS BEEN MOVED, MOVE DATA CARD IS -/6X DA 279
     1,I3,I5,7F10.5)                                                    DA 280
   48 FORMAT (25H GEOMETRY DATA CARD ERROR)                             DA 281
   49 FORMAT (1X,A2,I3,I5,7F10.5)                                       DA 282
   50 FORMAT (69H NUMBER OF WIRE SEGMENTS AND SURFACE PATCHES EXCEEDS DI DA 283
     1MENSION LIMIT.)                                                   DA 284
   51 FORMAT (1X,I5,A1,F10.5,2F11.5,1X,3F11.5)                          DA 285
   52 FORMAT (44H ERROR - GF MUST BE FIRST GEOMETRY DATA CARD)          DA 286
   53 FORMAT (////33X,33H- - - - SEGMENTATION DATA - - - -,//,40X,21HCOO DA 287
     1RDINATES IN METERS,//,25X,50HI+ AND I- INDICATE THE SEGMENTS BEFOR DA 288
     2E AND AFTER I,//)                                                 DA 289
   54 FORMAT (2X,4HSEG.,3X,26HCOORDINATES OF SEG. CENTER,5X,4HSEG.,5X,18 DA 290
     1HORIENTATION ANGLES,4X,4HWIRE,4X,15HCONNECTION DATA,3X,3HTAG,/,2Y, DA 291
     23HNO.,7X,1HX,9X,1HY,9X,1HZ,7X,6HLENGTH,5X,5HALPHA,5X,4HBETA,6X,6HR DA 292
     3ADIUS,4X,2HI-,3X,1HI,4X,2HI+,4X,3HNO.)                            DA 293
   55 FORMAT (1X,I5,4F10.5,1X,3F10.5,1X,3I5,2X,I5)                      DA 294
   56 FORMAT (19H SEGMENT DATA ERROR)                                   DA 295
   57 FORMAT (////,44X,30H- - - SURFACE PATCH DATA - - -,//,49X,21HCOORD DA 296
     1INATES IN METERS,//,1X,5HPATCH,5X,22HCOORD. OF PATCH CENTER,7X,18H DA 297
     2UNIT NORMAL VECTOR,6X,5HPATCH,12X,34HCOMPONENTS OF UNIT TANGENT VE DA 298
     3CTORS,/,2X,3HNO.,6X,1HX,9X,1HY,9X,1HZ,9X,1HX,7X,1HY,7X,1HZ,7X,4HAR DA 299
     4EA,7X,2HX1,6X,2HY1,6X,2HZ1,7X,2HX2,6X,2HY2,6X,2HZ2)               DA 300
   58 FORMAT (1X,I4,3F10.5,1X,3F8.4,F10.5,1X,3F8.4,1X,3F8.4)            DA 301
   59 FORMAT (1X,I5,A1,F10.5,2F11.5,1X,3F11.5,5X,9HSURFACE -,I4,3H BY,I3 DA 302
     1,8H PATCHES)                                                      DA 303
   60 FORMAT (17H PATCH DATA ERROR)                                     DA 304
   61 FORMAT (9X,43HABOVE WIRE IS TAPERED.  SEG. LENGTH RATIO =,F9.5,/,3 DA 305
     13X,11HRADIUS FROM,F9.5,3H TO,F9.5)                                DA 306
      END                                                               DA 307-
```

DB10

PURPOSE

To convert an input magnitude quantity (field) or magnitude squared quantity (power) into decibels.

METHOD

For a squared quantity, the decibel conversion is

$$Q_{db} = 10 \log_{10} Q^2 \quad (Q^2 \text{ input}) ,$$

and for an unsquared quantity,

$$Q_{db} = 20 \log_{10} Q .$$

DB10 is used for the squared quantity while the entry DB20 is used for the quantity which is not squared.

SYMBOL DICTIONARY

ALOG10 = external routine (log to the base 10)

DB10 = Q_{db}

F = scaling term

X = input quantity

CONSTANT

-999.99 = returned for an input less than 10^{-20}

CODE LISTING

```
      FUNCTION DB10 (X)                                                  DB   1
C                                                                        DB   2
C     FUNCTION DB--- RETURNS DB FOR MAGNITUDE (FIELD) OR MAG**2 (POWER) I DB   3
C                                                                        DB   4
      F=10.                                                              DB   5
      GO TO 1                                                            DB   6
      ENTRY DB20                                                         DB   7
      F=20.                                                              DB   8
1     IF (X.LT.1.E-20) GO TO 2                                           DB   9
      DB10=F*ALOG10(X)                                                   DB  10
      RETURN                                                             DB  11
2     DB10=-999.99                                                       DB  12
      RETURN                                                             DB  13
      END                                                                DB  14-
```

EFLD

PURPOSE

To compute the near electric field due to constant, sine, and cosine current distributions on a segment in free space or over ground.

METHOD

The electric field is computed at the point XI, YI, ZI due to the segment defined by parameters in COMMON/DATAJ/. Either the thin wire or extended thin wire formulas may be used. When a ground is present, the code is executed twice in a loop. In the second pass, the field of the image of the segment is computed, multiplied by the reflection coefficients, and added to the direct field. The reflection coefficients for the reflected ray from the center of the source segment are used for the entire segment.

The field is evaluated in a cylindrical coordinate system with the source segment at the origin, along the z axis. The ρ coordinate of the field evaluation point is computed for the surface of the observation segment as

$$\rho' = (\rho^2 + a^2)^{1/2},$$

where ρ is the distance from the axis of the source segment to (XI, YI, ZI) and a is the radius of the observation segment. The field is computed in ρ and z components as

$$\bar{E} = E_\rho(\bar{\rho}/\rho') + E_z\hat{z} .$$

Use of ρ' avoids a singularity when (XI, YI, ZI) is the center of the source segment. In the addition of field components, $\bar{\rho}/\rho'$ is used rather than $\hat{\rho}$, since E_ρ is the field in the direction $\hat{\rho}'$ to one side of the observation segment.

When the Sommerfeld/Norton option is used for an antenna over ground the electric field at $\bar{r}$ due to the current on a segment is evaluated in three terms as

$$\bar{E}(\bar{r}) = \bar{E}_D(\bar{r}) + \frac{k_1^2 - k_2^2}{k_1^2 + k_2^2}\bar{E}_I(\bar{r}) + \bar{E}_S(\bar{r})$$

$\bar{E}_D$ is the direct field of the segment in the absence of ground, and $\bar{E}_I$ is the field of the image of the segment reflected in a perfectly conducting ground. These field comonents are evaluated in EFLD between EF19 and EF150. The factor $(k_1^2 - k_2^2)/(k_1^2 + k_2^2)$ is contained in the variable FRATI.

The field $\bar{E}_S$, due to the Sommerfeld integrals is evaluated from EF155 to EF227. If the separation of the observation point and the center of the source segment is less than one wavelength, subroutine ROM2 is called at EF191 to integrate over the segment. DMIN is set to the magnitude of the first two terms in $\bar{E}$ divided by 100 as a lower limit on the denominator of the relative error test in the numerical integration. This relaxes the relative accuracy requirement when $\bar{E}_S$ is small compared to the first two terms.

If the separation of the source segment and observation point is greater than a wavelength, SFLDS is called at EF197 to evaluate $\bar{E}_S$ by the Norton approximation.

To compute $\bar{E}_S$ with the thin wire approximation applied in a manner consistent with that for $\bar{E}_I$, the field is evaluated at a point displaced normal to the image of the source segment and normal to the separation $\bar{R}$. If the direction of the image of the source segment is $\hat{j}$ the displacement is $\bar{D}$ where

$$\bar{D} = \pm a\hat{d} \text{ for } \hat{z} \cdot \hat{d} \gtrless 0$$

$$\hat{d} = (\hat{j} \times \bar{R})/|\hat{j} \times \bar{R}|$$

$$a = \text{radius of observation segment}$$

This displaced observation point (XO, YO, ZO) is computed from EF166 to EF181. Some of the complexity is needed to make the result independent of orientation of segments relative to the coordinate axes.

To adjust the ρ component of field for the factor $|\bar{\rho}/\rho'|$ the field $\bar{E}'$ is computed as

$$\bar{E}' = F\bar{E} + (1 - F)(\bar{E} \cdot \hat{j})\hat{j}$$

where $F = [\rho^2/(\rho^2 + a^2)]^{1/2}$

$$\rho^2 = |\bar{R}|^2 - (\bar{R} \cdot \hat{j})^2$$

This is done from EF204 to EF218 but is skipped if F (DMIN) is greater than 0.95.

CODING

EF23	Loop over direct and image fields.
EF29 - EF31	Components of $\bar{\rho}$.
EF33 - EF40	Components of $\bar{\rho}/\rho'$ computed.
EF46 - EF62	Electric field of the segment computed by infinitesimal dipole approximation.
EF68	Field computed by thin wire approximation.
EF70	Field computed by extended thin wire approximation.
EF72 - EF80	Field converted to x, y, and z components.
EF89 - EF111	Reflection coefficients computed.
EF112 - EF129	Image fields modified by reflection coefficients.
EF130 - EF138	Reflected fields added to direct fields.

SYMBOL DICTIONARY

AI	= radius of segment on which field is evaluated
CTH	= cos θ; θ = angle from axis of infinitesimal dipole or angle between the reflecting ray and vertical
EGND	= components of $\bar{E}_S$ (see EQUIVALENCE statement)
EPX, EPY	= x and y components of $(\bar{E} \cdot \hat{\rho})\hat{\rho}$ (see PX)
ETA	= $\eta = (\mu_o/\epsilon_o)^{1/2}$
IJ	= IJX = flag to indicate field evaluation point is on the source segment (IJ = 0)
PI	= π

PX, PY = x and y components of unit vector normal to the plane of incidence of the reflected wave ($\hat{p}$)

R = distance from field evaluation point to the center of the source segment

REFPS = reflection coefficient for a horizontally polarized field

REFS = reflection coefficient for a vertically polarized field

RFL = +1 for direct field, -1 for reflected field

RH = ρ'

RHOSPC = distance from coordinate origin to the point where the ray from the source to (XI, YI, ZI) reflects from the ground

RHOX, RHOY, RHOZ = x, y, and z components of $\bar{\rho}$ or $\bar{\rho}/\rho'$ or $\hat{j} \times \bar{R}$

RMAG = $2\pi R$ or R or dipole moment for sin ks current

SALPR = z component of unit vector in the direction of the source segment or its image

SHAF = half of segment length

TERC, TERS, TERK = ρ component of field due to cos ks, sin ks, and constant currents, respectively

TEZC, TEZS, TEZK = z component of field due to cos ks, sin ks, and constant current, respectively

TP = 2π

TXC, TYC, TZC, TXS, TYS, TZS, TXK, TYK, TZK = x, y, and z components of field due to cos ks, sin ks, and constant current

XI, YI, ZI = x, y, z coordinates of field evaluation point

XIJ, YIJ, ZIJ = components of distance from source to observation point

XO, YO, ZO = coordinates of field evaluation point for E_s

XSPEC, YSPEC = x, y coordinates of ground plane reflection point

XYMAG = horizontal distance from center of source segment to observation point

ZP = projection of the vector from the source segment (XI, YI, ZI) onto the axis of the source segment

ZRATX = temporary storage for ZRATI

ZRSIN = $(1 - Z_R^2 \sin^2 \theta)^{1/2}$ for ground

ZSCRN = quantity used in computing reflection coefficient for radial wire ground screen

CONSTANT

3.141592654 = π

376.73 = $\eta = \sqrt{\mu_0/\epsilon_0}$

6.283185308 = 2π

```
      SUBROUTINE EFLD (XI,YI,ZI,AI,IJ)                                  EF   1
C                                                                       EF   2
C     COMPUTE NEAR E FIELDS OF A SEGMENT WITH SINE, COSINE, AND         EF   3
C     CONSTANT CURRENTS.  GROUND EFFECT INCLUDED.                       EF   4
C                                                                       EF   5
      COMPLEX TXK,TYK,TZK,TXS,TYS,TZS,TXC,TYC,TZC,EXK,EYK,EZK,EXS,EYS,EZ EF   6
     1S,EXC,EYC,EZC,EPX,EPY,ZRATI,REFS,REFPS,ZRSIN,ZRATX,T1,ZSCRN,ZRATI2 EF   7
     2,TEZS,TERS,TEZC,TERC,TEZK,TERK,EGND,FRATI                         EF   8
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ EF   9
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                           EF  10
      COMMON /GND/ ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR EF  11
     1,IPERF,T1,T2                                                      EF  12
      COMMON /INCOM/ XO,YO,ZO,SN,XSN,YSN,ISNOR                          EF  13
      DIMENSION EGND(9)                                                 EF  14
      EQUIVALENCE (EGND(1),TXK), (EGND(2),TYK), (EGND(3),TZK), (EGND(4), EF  15
     1TXS), (EGND(5),TYS), (EGND(6),TZS), (EGND(7),TXC), (EGND(8),TYC),  EF  16
     2(EGND(9),TZC)                                                     EF  17
      DATA ETA/376.73/,PI/3.141592654/,TP/6.283185308/                  EF  18
      XIJ=XI-XJ                                                         EF  19
      YIJ=YI-YJ                                                         EF  20
      IJX=IJ                                                            EF  21
      RFL=-1.                                                           EF  22
      DO 12 IP=1,KSYMP                                                  EF  23
      IF (IP.EQ.2) IJX=1                                                EF  24
      RFL=-RFL                                                          EF  25
      SALPR=SALPJ*RFL                                                   EF  26
      ZIJ=ZI-RFL*ZJ                                                     EF  27
      ZP=XIJ*CABJ+YIJ*SABJ+ZIJ*SALPR                                    EF  28
      RHOX=XIJ-CABJ*ZP                                                  EF  29
      RHOY=YIJ-SABJ*ZP                                                  EF  30
      RHOZ=ZIJ-SALPR*ZP                                                 EF  31
      RH=SQRT(RHOX*RHOX+RHOY*RHOY+RHOZ*RHOZ+AI*AI)                      EF  32
      IF (RH.GT.1.E-10) GO TO 1                                         EF  33
      RHOX=0.                                                           EF  34
      RHOY=0.                                                           EF  35
      RHOZ=0.                                                           EF  36
      GO TO 2                                                           EF  37
1     RHOX=RHOX/RH                                                      EF  38
      RHOY=RHOY/RH                                                      EF  39
      RHOZ=RHOZ/RH                                                      EF  40
2     R=SQRT(ZP*ZP+RH*RH)                                               EF  41
      IF (R.LT.RKH) GO TO 3                                             EF  42
C                                                                       EF  43
C     LUMPED CURRENT ELEMENT APPROX. FOR LARGE SEPARATIONS              EF  44
C                                                                       EF  45
      RMAG=TP*R                                                         EF  46
      CTH=ZP/R                                                          EF  47
      PX=RH/R                                                           EF  48
      TXK=CMPLX(COS(RMAG),-SIN(RMAG))                                   EF  49
      PY=TP*R*R                                                         EF  50
      TYK=ETA*CTH*TXK*CMPLX(1.,-1./RMAG)/PY                             EF  51
      TZK=ETA*PX*TXK*CMPLX(1.,RMAG-1./RMAG)/(2.*PY)                     EF  52
      TEZK=TYK*CTH-TZK*PX                                               EF  53
      TERK=TYK*PX+TZK*CTH                                               EF  54
      RMAG=SIN(PI*S)/PI                                                 EF  55
      TEZC=TEZK*RMAG                                                    EF  56
      TERC=TERK*RMAG                                                    EF  57
      TEZK=TEZK*S                                                       EF  58
      TERK=TERK*S                                                       EF  59
      TXS=(0.,0.)                                                       EF  60
      TYS=(0.,0.)                                                       EF  61
      TZS=(0.,0.)                                                       EF  62
      GO TO 6                                                           EF  63
3     IF (IEXK.EQ.1) GO TO 4                                            EF  64
```

```
      C                                                                 EF  65
      C     EKSC FOR THIN WIRE APPROX. OR EKSCX FOR EXTENDED T.W. APPROX.  EF  66
      C                                                                 EF  67
            CALL EKSC (S,ZP,RH,TP,IJX,TEZS,TERS,TEZC,TERC,TEZK,TERK)    EF  68
            GO TO 5                                                     EF  69
    4       CALL EKSCX (B,S,ZP,RH,TP,IJX,IND1,IND2,TEZS,TERS,TEZC,TERC,TEZK,TE EF  70
           1RK)                                                         EF  71
    5       TXS=TEZS*CABJ+TERS*RHOX                                     EF  72
            TYS=TEZS*SABJ+TERS*RHOY                                     EF  73
            TZS=TEZS*SALPR+TERS*RHOZ                                    EF  74
    6       TXK=TEZK*CABJ+TERK*RHOX                                     EF  75
            TYK=TEZK*SABJ+TERK*RHOY                                     EF  76
            TZK=TEZK*SALPR+TERK*RHOZ                                    EF  77
            TXC=TEZC*CABJ+TERC*RHOX                                     EF  78
            TYC=TEZC*SABJ+TERC*RHOY                                     EF  79
            TZC=TEZC*SALPR+TERC*RHOZ                                    EF  80
            IF (IP.NE.2) GO TO 11                                       EF  81
            IF (IPERF.GT.0) GO TO 10                                    EF  82
            ZRATX=ZRATI                                                 EF  83
            RMAG=R                                                      EF  84
            XYMAG=SQRT(XIJ*XIJ+YIJ*YIJ)                                 EF  85
      C                                                                 EF  86
      C     SET PARAMETERS FOR RADIAL WIRE GROUND SCREEN.               EF  87
      C                                                                 EF  88
            IF (NRADL.EQ.0) GO TO 7                                     EF  89
            XSPEC=(XI*ZJ+ZI*XJ)/(ZI+ZJ)                                 EF  90
            YSPEC=(YI*ZJ+ZI*YJ)/(ZI+ZJ)                                 EF  91
            RHOSPC=SQRT(XSPEC*XSPEC+YSPEC*YSPEC+T2*T2)                  EF  92
            IF (RHOSPC.GT.SCRWL) GO TO 7                                EF  93
            ZSCRN=T1*RHOSPC*ALOG(RHOSPC/T2)                             EF  94
            ZRATX=(ZSCRN*ZRATI)/(ETA*ZRATI+ZSCRN)                       EF  95
    7       IF (XYMAG.GT.1.E-6) GO TO 8                                 EF  96
      C                                                                 EF  97
      C     CALCULATION OF REFLECTION COEFFICIENTS WHEN GROUND IS SPECIFIED. EF  98
      C                                                                 EF  99
            PX=0.                                                       EF 100
            PY=0.                                                       EF 101
            CTH=1.                                                      EF 102
            ZRSIN=(1.,0.)                                               EF 103
            GO TO 9                                                     EF 104
    8       PX=-YIJ/XYMAG                                               EF 105
            PY=XIJ/XYMAG                                                EF 106
            CTH=ZIJ/RMAG                                                EF 107
            ZRSIN=CSQRT(1.-ZRATX*ZRATX*(1.-CTH*CTH))                    EF 108
    9       REFS=(CTH-ZRATX*ZRSIN)/(CTH+ZRATX*ZRSIN)                    EF 109
            REFPS=-(ZRATX*CTH-ZRSIN)/(ZRATX*CTH+ZRSIN)                  EF 110
            REFPS=REFPS-REFS                                            EF 111
            EPY=PX*TXK+PY*TYK                                           EF 112
            EPX=PX*EPY                                                  EF 113
            EPY=PY*EPY                                                  EF 114
            TXK=REFS*TXK+REFPS*EPX                                      EF 115
            TYK=REFS*TYK+REFPS*EPY                                      EF 116
            TZK=REFS*TZK                                                EF 117
            EPY=PX*TXS+PY*TYS                                           EF 118
            EPX=PX*EPY                                                  EF 119
            EPY=PY*EPY                                                  EF 120
            TXS=REFS*TXS+REFPS*EPX                                      EF 121
            TYS=REFS*TYS+REFPS*EPY                                      EF 122
            TZS=REFS*TZS                                                EF 123
            EPY=PX*TXC+PY*TYC                                           EF 124
            EPX=PX*EPY                                                  EF 125
            EPY=PY*EPY                                                  EF 126
            TXC=REFS*TXC+REFPS*EPX                                      EF 127
            TYC=REFS*TYC+REFPS*EPY                                      EF 128
```

```
      TZC=REFS*TZC                                                      EF 129
10    EXK=EXK-TXK*FRATI                                                 EF 130
      EYK=EYK-TYK*FRATI                                                 EF 131
      EZK=EZK-TZK*FRATI                                                 EF 132
      EXS=EXS-TXS*FRATI                                                 EF 133
      EYS=EYS-TYS*FRATI                                                 EF 134
      EZS=EZS-TZS*FRATI                                                 EF 135
      EXC=EXC-TXC*FRATI                                                 EF 136
      EYC=EYC-TYC*FRATI                                                 EF 137
      EZC=EZC-TZC*FRATI                                                 EF 138
      GO TO 12                                                          EF 139
11    EXK=TXK                                                           EF 140
      EYK=TYK                                                           EF 141
      EZK=TZK                                                           EF 142
      EXS=TXS                                                           EF 143
      EYS=TYS                                                           EF 144
      EZS=TZS                                                           EF 145
      EXC=TXC                                                           EF 146
      EYC=TYC                                                           EF 147
      EZC=TZC                                                           EF 148
12    CONTINUE                                                          EF 149
      IF (IPERF.EQ.2) GO TO 13                                          EF 150
      RETURN                                                            EF 151
C                                                                       EF 152
C     FIELD DUE TO GROUND USING SOMMERFELD/NORTON                       EF 153
C                                                                       EF 154
13    SN=SQRT(CABJ*CABJ+SABJ*SABJ)                                      EF 155
      IF (SN.LT.1.E-5) GO TO 14                                         EF 156
      XSN=CABJ/SN                                                       EF 157
      YSN=SABJ/SN                                                       EF 158
      GO TO 15                                                          EF 159
14    SN=0.                                                             EF 160
      XSN=1.                                                            EF 161
      YSN=0.                                                            EF 162
C                                                                       EF 163
C     DISPLACE OBSERVATION POINT FOR THIN WIRE APPROXIMATION            EF 164
C                                                                       EF 165
15    ZIJ=ZI+ZJ                                                         EF 166
      SALPR=-SALPJ                                                      EF 167
      RHOX=SABJ*ZIJ-SALPR*YIJ                                           EF 168
      RHOY=SALPR*XIJ-CABJ*ZIJ                                           EF 169
      RHOZ=CABJ*YIJ-SABJ*XIJ                                            EF 170
      RH=RHOX*RHOX+RHOY*RHOY+RHOZ*RHOZ                                  EF 171
      IF (RH.GT.1.E-10) GO TO 16                                        EF 172
      XO=XI-AI*YSN                                                      EF 173
      YO=YI+AI*XSN                                                      EF 174
      ZO=ZI                                                             EF 175
      GO TO 17                                                          EF 176
16    RH=AI/SQRT(RH)                                                    EF 177
      IF (RHOZ.LT.0.) RH=-RH                                            EF 178
      XO=XI+RH*RHOX                                                     EF 179
      YO=YI+RH*RHOY                                                     EF 180
      ZO=ZI+RH*RHOZ                                                     EF 181
17    R=XIJ*XIJ+YIJ*YIJ+ZIJ*ZIJ                                         EF 182
      IF (R.GT..95) GO TO 18                                            EF 183
C                                                                       EF 184
C     FIELD FROM INTERPOLATION IS INTEGRATED OVER SEGMENT               EF 185
C                                                                       EF 186
      ISNOR=1                                                           EF 187
      DMIN=EXK*CONJG(EXK)+EYK*CONJG(EYK)+EZK*CONJG(EZK)                 EF 188
      DMIN=.01*SQRT(DMIN)                                               EF 189
      SHAF=.5*S                                                         EF 190
      CALL ROM2 (-SHAF,SHAF,EGND,DMIN)                                  EF 191
      GO TO 19                                                          EF 192
```

```
      C                                                                 EF 193
      C     NORTON FIELD EQUATIONS AND LUMPED CURRENT ELEMENT APPROXIMATION EF 194
      C                                                                 EF 195
   18 ISNOR=2                                                           EF 196
      CALL SFLDS (0.,EGND)                                              EF 197
      GO TO 22                                                          EF 198
   19 ZP=XIJ*CABJ+YIJ*SABJ+ZIJ*SALPR                                    EF 199
      RH=R-ZP*ZP                                                        EF 200
      IF (RH.GT.1.E-10) GO TO 20                                        EF 201
      DMIN=0.                                                           EF 202
      GO TO 21                                                          EF 203
   20 DMIN=SQRT(RH/(RH+AI*AI))                                          EF 204
   21 IF (DMIN.GT..95) GO TO 22                                         EF 205
      PX=1.-DMIN                                                        EF 206
      TERK=(TXK*CABJ+TYK*SABJ+TZK*SALPR)*PX                             EF 207
      TXK=DMIN*TXK+TERK*CABJ                                            EF 208
      TYK=DMIN*TYK+TERK*SABJ                                            EF 209
      TZK=DMIN*TZK+TERK*SALPR                                           EF 210
      TERS=(TXS*CABJ+TYS*SABJ+TZS*SALPR)*PX                             EF 211
      TXS=DMIN*TXS+TERS*CABJ                                            EF 212
      TYS=DMIN*TYS+TERS*SABJ                                            EF 213
      TZS=DMIN*TZS+TERS*SALPR                                           EF 214
      TERC=(TXC*CABJ+TYC*SABJ+TZC*SALPR)*PX                             EF 215
      TXC=DMIN*TXC+TERC*CABJ                                            EF 216
      TYC=DMIN*TYC+TERC*SABJ                                            EF 217
      TZC=DMIN*TZC+TERC*SALPR                                           EF 218
   22 EXK=EXK+TXK                                                       EF 219
      EYK=EYK+TYK                                                       EF 220
      EZK=EZK+TZK                                                       EF 221
      EXS=EXS+TXS                                                       EF 222
      EYS=EYS+TYS                                                       EF 223
      EZS=EZS+TZS                                                       EF 224
      EXC=EXC+TXC                                                       EF 225
      EYC=EYC+TYC                                                       EF 226
      EZC=EZC+TZC                                                       EF 227
      RETURN                                                            EF 228
      END                                                               EF 229-
```

EKSC

PURPOSE

To compute the electric field due to current filaments with sin kz, cos kz and constant distributions.

METHOD

Equations 71 through 74 in Part I are used. The current filament is located at the origin of a cylindrical coordinate system, oriented along the z axis, and extending from $-\Delta/2$ to $\Delta/2$. The field is computed in ρ and z components.

SYMBOL DICTIONARY

CINT = $\int_{-\Delta/2}^{\Delta/2} \cos(kr)/r \, dz$

CON = CONX = $j\eta/(8\pi^2)$, $\eta = \sqrt{\mu_0/\epsilon_0}$

CS = $\cos(k\Delta/2)$

ERS, EZS, ERC, EZC, ERK, EZK = ρ and z components of field due to sin kz, cos kz, and constant (S, C, K, respectively) current distributions extending from $z = -\Delta/2$ to $z = \Delta/2$

GP1, GP2 = $-(1 + jkr)\, G_0/r^2$ for $z = -\Delta/2$ and $\Delta/2$, respectively, where $G_0 = \exp(-jkr)/r$

GZ1, GZ2 = G_0 for $z = -\Delta/2$ and $\Delta/2$, respectively

GZP1, GZP2 = $\partial G_0/\partial z$ at EK21, EK22 and $\partial G_0/\partial \rho$ at EK28, EK29 for $z = -\Delta/2$ and $\Delta/2$, respectively

IJ = IJX = 0 to indicate that the field point is on the source segment

RH = ρ coordinate of field point

RHK = $k\rho$ ($k = 2\pi/\lambda$, $\lambda = 1$)

RKB2 = $(k\rho)^2$

S = Δ

SH = $\Delta/2$

SHK = $k\Delta/2$

$$SINT = \int_{-\Delta/2}^{\Delta/2} \sin(kr)/r \, dz$$

SS = sin (kΔ/2)

XK = k = 2π/λ, where λ = 1

Z = z coordinate of field point

Z1 = -Δ/2 - z

Z2 = Δ/2 - z

ZPK = kz

CONSTANT

$4.771341189 = \eta/(8\pi^2)$

CODE LISTING

```
      SUBROUTINE EKSC (S,Z,RH,XK,IJ,EZS,ERS,EZC,ERC,EZK,ERK)              EK   1
C     COMPUTE E FIELD OF SINE, COSINE, AND CONSTANT CURRENT FILAMENTS BY  EK   2
C     THIN WIRE APPROXIMATION.                                            EK   3
      COMPLEX CON,GZ1,GZ2,GP1,GP2,GZP1,GZP2,EZS,ERS,EZC,ERC,EZK,ERK       EK   4
      COMMON /TMI/ ZPK,RKB2,IJX                                           EK   5
      DIMENSION CONX(2)                                                   EK   6
      EQUIVALENCE (CONX,CON)                                              EK   7
      DATA CONX/0.,4.771341189/                                           EK   8
      IJX=IJ                                                              EK   9
      ZPK=XK*Z                                                            EK  10
      RHK=XK*RH                                                           EK  11
      RKB2=RHK*RHK                                                        EK  12
      SH=.5*S                                                             EK  13
      SHK=XK*SH                                                           EK  14
      SS=SIN(SHK)                                                         EK  15
      CS=COS(SHK)                                                         EK  16
      Z2=SH-Z                                                             EK  17
      Z1=-(SH+Z)                                                          EK  18
      CALL GX (Z1,RH,XK,GZ1,GP1)                                          EK  19
      CALL GX (Z2,RH,XK,GZ2,GP2)                                          EK  20
      GZP1=GP1*Z1                                                         EK  21
      GZP2=GP2*Z2                                                         EK  22
      EZS=CON*((GZ2-GZ1)*CS*XK-(GZP2+GZP1)*SS)                            EK  23
      EZC=-CON*((GZ2+GZ1)*SS*XK+(GZP2-GZP1)*CS)                           EK  24
      ERK=CON*(GP2-GP1)*RH                                                EK  25
      CALL INTX (-SHK,SHK,RHK,IJ,CINT,SINT)                               EK  26
      EZK=-CON*(GZP2-GZP1+XK*XK*CMPLX(CINT,-SINT))                        EK  27
      GZP1=GZP1*Z1                                                        EK  28
      GZP2=GZP2*Z2                                                        EK  29
      IF (RH.LT.1.E-10) GO TO 1                                           EK  30
      ERS=-CON*((GZP2+GZP1+GZ2+GZ1)*SS-(Z2*GZ2-Z1*GZ1)*CS*XK)/RH          EK  31
      ERC=-CON*((GZP2-GZP1+GZ2-GZ1)*CS+(Z2*GZ2+Z1*GZ1)*SS*XK)/RH          EK  32
      RETURN                                                              EK  33
    1 ERS=(0.,0.)                                                         EK  34
      ERC=(0.,0.)                                                         EK  35
      RETURN                                                              EK  36
      END                                                                 EK  37-
```

EKSCX

PURPOSE

To compute the electric field due to current distributions of sin kz, cos kz, and constant on the surface of a cylinder by the extended thin wire approximation.

METHOD

Equations 84 through 87 in Part I are used. The current tube is centered on the origin of a cylindrical coordinate system, oriented along the z axis and extending from $-\Delta/2$ to $\Delta/2$. The field is computed in ρ and z components.

If INX1 = 2, the field contributions from end 1 of the segment ($z = -\Delta/2$) are evaluated by the thin wire approximation for a current filament on the cylinder axis. INX2 has the same meaning for end 2 of the segment ($z = \Delta/2$). The thin-wire approximation is used at an end when there is a bend or change in radius from that end to the next segment.

When the ρ coordinate of the field point (RHX) is less than the radius of the current tube (BX), then RHX and BX are interchanged and a flag, IRA, is set to 1 to cause alternate forms for G_1 and its derivatives to be used in routine GXX.

SYMBOL DICTIONARY

A2 = B^2

B = radius of the current tube

BK = kB, where $k = 2\pi/\lambda$, $\lambda = 1$

BK2 = $(BK)^2/4$

BX = radius of the current tube

CINT = $\int_{-\Delta/2}^{\Delta/2} \cos(kr)/r \, dz$

CON = CONX = $j\eta/(8\pi^2)$, where $\eta = \sqrt{\mu_0/\varepsilon_0}$

CS = cos (kΔ/2)

ERS, EZS, ERC, EZC, ERK, EZK = ρ and z components of field due to sin kz, cos kz, and constant (S, C, K, respectively) current distributions extending from $z = -\Delta/2$ to $z = \Delta/2$.

GR1, GR2 = G_2 for $z = -\Delta/2$ and $\Delta/2$, respectively

GRK1, GRK2 = $\partial G_1/\partial \rho$

GRP1, GRP2 = $\partial G_2/\partial z'$

GZ1, GZ2 = G_1

GZP1, GZP2 = $\partial G_1/\partial z'$

GZZ1, GZZ2 = $\partial G_0/\partial z'$

IJ = IJX = 0 to indicate that the field point is on the source segment

INX1, INX2 = 2 to use the thin wire form at end 1 or end 2, respectively

IRA = 1 to indicate RHX < BX

RH = ρ coordinate of the field point or wire radius

RHK = k(RH)

RHX = ρ coordinate of the field point

RKB2 = $(RHK)^2$

S = Δ

SH = $\Delta/2$

SHK = $k\Delta/2$

SINT = $\int_{-\Delta/2}^{\Delta/2} \sin(kr)/r \, dz$

SS = $\sin(k\Delta/2)$

XK = $k = 2\pi/\lambda$, $\lambda = 1$

Z = z coordinate of field point

Z1 = $-\Delta/2 - z$

Z2 = $\Delta/2 - z$

ZPK = kz

CONSTANT

4.77134118 = $\eta/(8\pi^2)$

EKSCX

```
      SUBROUTINE EKSCX (BX,S,Z,RHX,XK,IJ,INX1,INX2,EZS,ERS,EZC,ERC,EZK,E EX   1
     1RK)                                                               EX   2
C     COMPUTE E FIELD OF SINE, COSINE, AND CONSTANT CURRENT FILAMENTS BY EX   3
C     EXTENDED THIN WIRE APPROXIMATION.                                 EX   4
      COMPLEX CON,GZ1,GZ2,GZP1,GZP2,GR1,GR2,GRP1,GRP2,EZS,EZC,ERS,ERC,GR EX   5
     1K1,GRK2,EZK,ERK,GZZ1,GZZ2                                         EX   6
      COMMON /TMI/ ZPK,RKB2,IJX                                         EX   7
      DIMENSION CONX(2)                                                 EX   8
      EQUIVALENCE (CONX,CON)                                            EX   9
      DATA CONX/0.,4.771341189/                                         EX  10
      IF (RHX.LT.BX) GO TO 1                                            EX  11
      RH=RHX                                                            EX  12
      B=BX                                                              EX  13
      IRA=0                                                             EX  14
      GO TO 2                                                           EX  15
1     RH=BX                                                             EX  16
      B=RHX                                                             EX  17
      IRA=1                                                             EX  18
2     SH=.5*S                                                           EX  19
      IJX=IJ                                                            EX  20
      ZPK=XK*Z                                                          EX  21
      RHK=XK*RH                                                         EX  22
      RKB2=RHK*RHK                                                      EX  23
      SHK=XK*SH                                                         EX  24
      SS=SIN(SHK)                                                       EX  25
      CS=COS(SHK)                                                       EX  26
      Z2=SH-Z                                                           EX  27
      Z1=-(SH+Z)                                                        EX  28
      A2=B*B                                                            EX  29
      IF (INX1.EQ.2) GO TO 3                                            EX  30
      CALL GXX (Z1,RH,B,A2,XK,IRA,GZ1,GZP1,GR1,GRP1,GRK1,GZZ1)          EX  31
      GO TO 4                                                           EX  32
3     CALL GX (Z1,RHX,XK,GZ1,GRK1)                                      EX  33
      GZP1=GRK1*Z1                                                      EX  34
      GR1=GZ1/RHX                                                       EX  35
      GRP1=GZP1/RHX                                                     EX  36
      GRK1=GRK1*RHX                                                     EX  37
      GZZ1=(0.,0.)                                                      EX  38
4     IF (INX2.EQ.2) GO TO 5                                            EX  39
      CALL GXX (Z2,RH,B,A2,XK,IRA,GZ2,GZP2,GR2,GRP2,GRK2,GZZ2)          EX  40
      GO TO 6                                                           EX  41
5     CALL GX (Z2,RHX,XK,GZ2,GRK2)                                      EX  42
      GZP2=GRK2*Z2                                                      EX  43
      GR2=GZ2/RHX                                                       EX  44
      GRP2=GZP2/RHX                                                     EX  45
      GRK2=GRK2*RHX                                                     EX  46
      GZZ2=(0.,0.)                                                      EX  47
6     EZS=CON*((GZ2-GZ1)*CS*XK-(GZP2+GZP1)*SS)                          EX  48
      EZC=-CON*((GZ2+GZ1)*SS*XK+(GZP2-GZP1)*CS)                         EX  49
      ERS=-CON*((Z2*GRP2+Z1*GRP1+GR2+GR1)*SS-(Z2*GR2-Z1*GR1)*CS*XK)     EX  50
      ERC=-CON*((Z2*GRP2-Z1*GRP1+GR2-GR1)*CS+(Z2*GR2+Z1*GR1)*SS*XK)     EX  51
      ERK=CON*(GRK2-GRK1)                                               EX  52
      CALL INTX (-SHK,SHK,RHK,IJ,CINT,SINT)                             EX  53
      BK=B*XK                                                           EX  54
      BK2=BK*BK*.25                                                     EX  55
      EZK=-CON*(GZP2-GZP1+XK*XK*(1.-BK2)*CMPLX(CINT,-SINT)-BK2*(GZZ2-GZZ EX  56
     11))                                                               EX  57
      RETURN                                                            EX  58
      END                                                               EX  59-
```

ENF

PURPOSE

To check for an end of file.

METHOD

ENF uses the standard Fortran end-of-file test and returns the logical values .TRUE. or .FALSE. This separate function is used for convenience in adapting the code to particular computers, since the Fortran end-of-file test statements often differ between computers. The form of ENF here is for CDC computers.

SYMBOL DICTIONARY

ENF = logical value: .TRUE. if end of file was encountered; .FALSE. otherwise

NUNIT = logical unit number

CODE LISTING

```
      1       LOGICAL FUNCTION ENF(NUNIT)                          EN    1
      2       IF (EOF,NUNIT) 1,2                                   EN    2
      3 1     ENF=.TRUE.                                           EN    3
      4       RETURN                                               EN    4
      5 2     ENF=.FALSE.                                          EN    5
      6       RETURN                                               EN    6
      7       END                                                  EN    7-
```

ETMNS

PURPOSE

To fill the array representing the right-hand side of the matrix equation with the negative of the electric field tangent to the segments and with the tangential magnetic field on the surfaces.

METHOD

The array E represents the right-hand side of the matrix equation. For the i^{th} segment, the right-hand side is the negative of the applied electric field component tangent to the segment, and is stored in location i in array E. For the i^{th} surface patch, there are two rows in the matrix equation (from the two components of the vector equations) with locations N + 2i - 1 and N + 2i, where N is the total number of wire segments. The contents of E for these locations are

$$E\ (N + 2i - 1) = -\hat{t}_1 \cdot (\hat{n} \times \bar{H}_i) = \pm t_2 \cdot \bar{H}_i$$

$$E\ (N + 2i) = \hat{t}_2 \cdot (\hat{n} \times \bar{H}_i) = \pm t_1 \cdot \bar{H}_i$$

where $\bar{H}_i$ is the magnetic field applied to patch i. The forms on the right are used in the code with the plus sign applying when ($\hat{t}_1$, $\hat{t}_2$, $\hat{n}$) forms a right-hand system and the minus sign when left-hand. To avoid the need to check ($\hat{t}_1$, $\hat{t}_2$, $\hat{n}$), the sign is stored in array SALP where, for patch i, SALP (LD + 1 - i) = ±1 according to ($\hat{t}_1$, $\hat{t}_2$, $\hat{n}$), with LD the length of the arrays in COMMON/DATA/. If the structure has symmetry, the entries in E are reordered by subroutine SOLVES.

The parameter IPR selects the type of excitation; the meanings of other parameters depend on the option selected by IPR and are explained below. The excitations associated with IPR values are:

IPR = 0 applied field voltage source
1 incident plane wave, linear polarization
2 incident plane wave, right-hand elliptic polarization
3 incident plane wave, left-hand elliptic polarization
4 infinitesimal current element source
5 current slope discontinuity voltage source

CODING

ET29 - ET34 Applied field voltage source (IPR = 0).

ET36 - ET38 QDSRC is called for each current slope discontinuity voltage source (IPR = 5).

ET44 - ET160 Incident plane wave. The direction of propagation and polarization of the wave are illustrated in figure 4 in which $\hat{p}$ is the unit vector normal to $\hat{k}$ in the plane defined by $\hat{k}$ and $\hat{z}$. The plane wave as a function of position $\bar{r}$ is

$$\bar{E}^I(\bar{r}) = \bar{E}_0 \exp(-j\bar{k}\cdot\bar{r})$$

$$\bar{H}^I(\bar{r}) = \frac{1}{\eta}\hat{k} \times \bar{E}_0 \exp(-j\bar{k}\cdot\bar{r})$$

where

$\bar{k} = (2\pi/\lambda)\hat{k}$

$\hat{k}$ = unit vector in direction of propagation

$\bar{E}_0 = \hat{E}_1$ for linear polarization

$= (\hat{E}_1 - jA\hat{E}_2)$ for right-hand elliptical polarization

$= (\hat{E}_1 + jA\hat{E}_2)$ for left-hand elliptical polarization

A = ellipse axes ratio

$\hat{E}_2 = \hat{k} \times \hat{E}_1$

ET44 - ET58 P1 = θ

P2 = ϕ

P3 = ξ

PX, PY, PZ = x, y, z components of $\hat{E}_1$

WX, WY, WZ = $\hat{k}$

QX, QY, QZ = $\hat{E}_2 = \hat{k} \times \hat{E}_1$

ET61 - ET68 Ground reflection coefficients computed:

RRH = reflection coefficient for E normal to the plane of incidence

RRV = reflection coefficient for E in the plane of incidence

ET70 - ET108 Linearly polarized wave (IPR = 1).

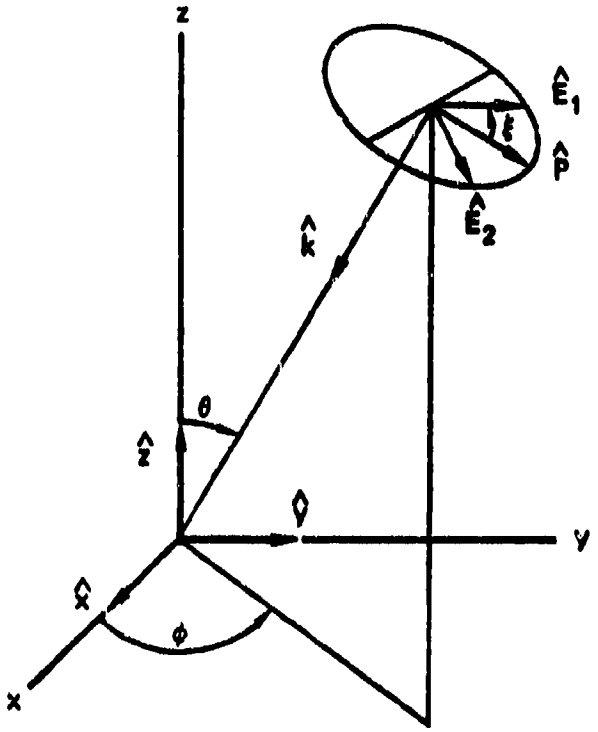


Figure 4. Coordinate Parameters for the Incident Plane Wave.

ET71 - ET73 Direct illumination of segments by E field. ARG = $-\bar{k} \cdot \bar{r}_1$, where $\bar{r}_1$ = center point of segment I. E(I) = $-(\hat{E}_1 \cdot \hat{l})$ $\exp(-j\bar{k} \cdot \bar{r}_1)$, where $\hat{l}$ = unit vector in the direction of segment I.

ET75 - ET82 Illumination of segments by the ground reflected field. CX, CY, CZ = reflected E field

ET84 - ET93 Direct H field illumination of patches.

ET95 - ET108 Illumination of patches by the ground reflected field. CX, CY, CZ = reflected H field

ET113 - ET159 Elliptically polarized wave (IPR = 2 or 3). P6 = ellipse axes ratio = A.

ET116 - ET121 Direct E field illumination of segments. CX, CY, CZ = $\hat{E}_1 \pm jA\hat{E}_2$ (+ for left-hand polarization, - for right-hand)

ET123 - ET130 Illumination of segments by the ground reflected E field.

ET132 - ET144 Illumination of patches by the direct H field. CX, CY, CZ = $\hat{k} \times \bar{E}_0$

ET146 - ET159 Illumination of patches by ground reflected H field.

ET164 - ET225 Infinitesimal current element source (IPR = 4). A current element of moment $I_0\ell$ at the origin of a spherical coordinate system, as shown in figure 5, produces field components

$$\bar{E}_R(\bar{R}) = I_0\ell \frac{\eta}{2\pi} \exp(-jkR) \left(1 - \frac{1}{kR}\right) \frac{1}{R^2} \cos\theta \, \hat{R}$$

$$\bar{E}_\theta(\bar{R}) = I_0\ell \frac{\eta}{4\pi} \exp(-jkR) \left[\frac{jk}{R} + \left(1 - \frac{1}{kR}\right) \frac{1}{R^2}\right] \sin\theta \, \hat{\theta}$$

$$H_\phi = \frac{I_0\ell}{4\pi} \exp(-jkR) \left(\frac{1}{R^2} + \frac{jk}{R}\right) \sin\theta$$

If the location and orientation of segment i and the current element with respect to the x, y, z coordinate system are

$\bar{r}_i$ = location of segment i
$\hat{i}$ = orientation of segment i
$\bar{D}$ = location of current element
$\hat{d}$ = orientation of current element

then

$\bar{R} = \bar{r}_i - \bar{D}$
$\hat{R} = \bar{R} / |\bar{R}|$
$\cos\theta = \hat{R} \cdot \hat{d}$
$\sin\theta = [1 - \cos^2\theta]^{1/2}$

The orientation of the current element is defined by its angle of elevation above the x-y plane, a, and the angle from the x axis to its projection on the x-y plane, b. Thus, $\hat{d} = \cos a \cos b \, \hat{x} + \cos a \sin b \, \hat{y} + \sin a \, \hat{z}$. The $\hat{R}$ and $\hat{\theta}$ field components are converted to $\hat{\rho}$ and $\hat{d}$ components E_ρ and E_d, where

$$E_d = E_R \cos\theta - E_\theta \sin\theta$$

$$E_\rho = E_R \sin\theta + E_\theta \cos\theta$$

and the excitation computed as

$$E(I) = -\hat{i} \cdot (E_d \hat{d} + E_\rho \hat{\rho}) \, .$$

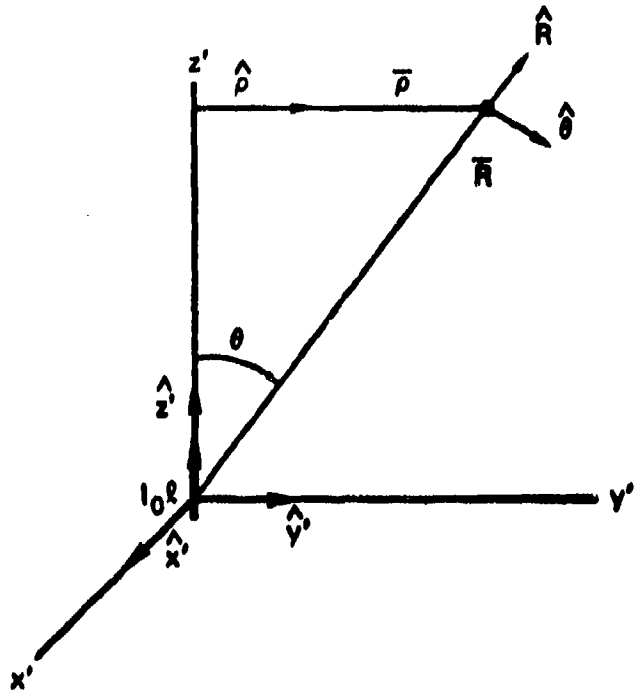


Figure 5. Coordinate Parameters for Current Element.

ET164 - ET225 P1, P2, P3 = x, y, z coordinates of current element ($\bar{D}$)

P4 = a

P5 = b

P6 = $I_0\ell/\lambda^2$

ET164 - ET169 WX, WY, WZ = x, y, and z components of $\hat{d}$

DS = $(\eta/2\pi)\ I_0\ell/\lambda^2$

DSH = $(1/4\pi)\ I_0\ell/\lambda^2$

ET173 Start of loop over all segments and patches.

ET176 - ET179 For patches,

IS = location of patch data in geometry arrays

I1, I2 = locations to be filled in E

ET180 - ET182 PX, PY, PZ = $\bar{R}/\lambda$

ET183 - ET193 R = $|\bar{R}/\lambda|$

PX, PY, PZ = $\hat{R}$

CTH = cos θ

STH = sin θ

QX, QY, QZ = $\hat{R} - (\hat{d} \cdot \hat{R})\hat{d}$

ET196 - ET204 QX, QY, QZ = $\hat{\rho}$

T1 = exp(-jk R)

ET206 - ET215 E field on segments

T2 = $(1 - j/kR)\lambda^2/R^2$

ER = E_R

ET = E_θ

ERH = E_ρ

EZH = E_z

CX, CY, CZ = x, y, z components of total E field

ET216 - ET224 H field on patches

PX, PY, PZ = $\hat{d} \times \hat{\rho} = \hat{\phi}$

T2 = $\pm H_\phi$

CX, CY, CZ = $\pm \bar{H}^I$

CONSTANTS

1.E-30 = tolerance in test for zero

2.654420938E-3 = $1/\eta = \sqrt{\varepsilon_0/\mu_0}$

59.958 = $\eta/2\pi$

6.283185308 = 2π

```
      SUBROUTINE ETMNS (P1,P2,P3,P4,P5,P6,IPR,E)                        ET   1
C                                                                       ET   2
C     ETMNS FILLS THE ARRAY E WITH THE NEGATIVE OF THE ELECTRIC FIELD   ET   3
C     INCIDENT ON THE STRUCTURE.  E IS THE RIGHT HAND SIDE OF THE MATRIX ET   4
C     EQUATION.                                                         ET   5
C                                                                       ET   6
      COMPLEX E,CX,CY,CZ,VSANT,TX1,TX2,ER,ET,EZH,ERH,VQD,VQDS,ZRATI,ZRAT ET   7
     1I2,RRV,RRH,T1,TT1,TT2,FRATI                                       ET   8
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 ET   9
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( ET  10
     2300),WLAM,IPSYM                                                   ET  11
      COMMON /ANGL/ SALP(300)                                           ET  12
      COMMON /VSORC/ VQD(30),VSANT(30),VQDS(30),IVQD(30),ISANT(30),IQDS( ET  13
     130),NVQD,NSANT,NQDS                                               ET  14
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR, ET  15
     1IPERF,T1,T2                                                       ET  16
      DIMENSION CAB(1), SAB(1), E(600)                                  ET  17
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1)          ET  18
      EQUIVALENCE (CAB,ALP), (SAB,BET)                                  ET  19
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON ET  20
     12), (T2Z,ITAG)                                                    ET  21
      DATA TP/6.283185308/,RETA/2.654420938E-3/                         ET  22
      NEQ=N+2*M                                                         ET  23
      NQDS=0                                                            ET  24
      IF (IPR.GT.0.AND.IPR.NE.5) GO TO 5                                ET  25
C                                                                       ET  26
C     APPLIED FIELD OF VOLTAGE SOURCES FOR TRANSMITTING CASE            ET  27
C                                                                       ET  28
      DO 1 I=1,NEQ                                                      ET  29
1     E(I)=(0.,0.)                                                      ET  30
      IF (NSANT.EQ.0) GO TO 3                                           ET  31
      DO 2 I=1,NSANT                                                    ET  32
      IS=ISANT(I)                                                       ET  33
2     E(IS)=-VSANT(I)/(SI(IS)*WLAM)                                     ET  34
3     IF (NVQD.EQ.0) RETURN                                             ET  35
      DO 4 I=1,NVQD                                                     ET  36
      IS=IVQD(I)                                                        ET  37
4     CALL QDSRC (IS,VQD(I),E)                                          ET  38
      RETURN                                                            ET  39
5     IF (IPR.GT.3) GO TO 19                                            ET  40
C                                                                       ET  41
C     INCIDENT PLANE WAVE, LINEARLY POLARIZED.                          ET  42
C                                                                       ET  43
      CTH=COS(P1)                                                       ET  44
      STH=SIN(P1)                                                       ET  45
      CPH=COS(P2)                                                       ET  46
      SPH=SIN(P2)                                                       ET  47
      CET=COS(P3)                                                       ET  48
      SET=SIN(P3)                                                       ET  49
      PX=CTH*CPH*CET-SPH*SET                                            ET  50
      PY=CTH*SPH*CET+CPH*SET                                            ET  51
      PZ=-STH*CET                                                       ET  52
      WX=-STH*CPH                                                       ET  53
      WY=-STH*SPH                                                       ET  54
      WZ=-CTH                                                           ET  55
      QX=WY*PZ-WZ*PY                                                    ET  56
      QY=WZ*PX-WX*PZ                                                    ET  57
      QZ=WX*PY-WY*PX                                                    ET  58
      IF (KSYMP.EQ.1) GO TO 7                                           ET  59
      IF (IPERF.EQ.1) GO TO 6                                           ET  60
      RRV=CSQRT(1.-ZRATI*ZRATI*STH*STH)                                 ET  61
      RRH=ZRATI*CTH                                                     ET  62
      RRH=(RRH-RRV)/(RRH+RRV)                                           ET  63
      RRV=ZRATI*RRV                                                     ET  64
```

```
      RRV=-(CTH-RRV)/(CTH+RRV)                                                  ET  65
      GO TO 7                                                                   ET  66
 6    RRV=-(1.,0.)                                                             ET  67
      RRH=-(1.,0.)                                                             ET  68
 7    IF (IPR.GT.1) GO TO 13                                                    ET  69
      IF (N.EQ.0) GO TO 10                                                      ET  70
      DO 8 I=1,N                                                                ET  71
      ARG=-TP*(WX*X(I)+WY*Y(I)+WZ*Z(I))                                         ET  72
 8    E(I)=-(PX*CAB(I)+PY*SAB(I)+PZ*SALP(I))*CMPLX(COS(ARG),SIN(ARG))           ET  73
      IF (KSYMP.EQ.1) GO TO 10                                                  ET  74
      TT1=(PY*CPH-PX*SPH)*(RRH-RRV)                                             ET  75
      CX=RRV*PX-TT1*SPH                                                         ET  76
      CY=RRV*PY+TT1*CPH                                                         ET  77
      CZ=-RRV*PZ                                                                ET  78
      DO 9 I=1,N                                                                ET  79
      ARG=-TP*(WX*X(I)+WY*Y(I)-WZ*Z(I))                                         ET  80
 9    E(I)=E(I)-(CX*CAB(I)+CY*SAB(I)+CZ*SALP(I))*CMPLX(COS(ARG),SIN(ARG)        ET  81
     1)                                                                         ET  82
 10   IF (M.EQ.0) RETURN                                                        ET  83
      I=LD+1                                                                    ET  84
      I1=N-1                                                                    ET  85
      DO 11 IS=1,M                                                              ET  86
      I=I-1                                                                     ET  87
      I1=I1+2                                                                   ET  88
      I2=I1+1                                                                   ET  89
      ARG=-TP*(WX*X(I)+WY*Y(I)+WZ*Z(I))                                         ET  90
      TT1=CMPLX(COS(ARG),SIN(ARG))*SALP(I)*RETA                                 ET  91
      E(I2)=(QX*T1X(I)+QY*T1Y(I)+QZ*T1Z(I))*TT1                                 ET  92
 11   E(I1)=(QX*T2X(I)+QY*T2Y(I)+QZ*T2Z(I))*TT1                                 ET  93
      IF (KSYMP.EQ.1) RETURN                                                    ET  94
      TT1=(QY*CPH-QX*SPH)*(RRV-RRH)                                             ET  95
      CX=-(RRH*QX-TT1*SPH)                                                      ET  96
      CY=-(RRH*QY+TT1*CPH)                                                      ET  97
      CZ=RRH*QZ                                                                 ET  98
      I=LD+1                                                                    ET  99
      I1=N-1                                                                    ET 100
      DO 12 IS=1,M                                                              ET 101
      I=I-1                                                                     ET 102
      I1=I1+2                                                                   ET 103
      I2=I1+1                                                                   ET 104
      ARG=-TP*(WX*X(I)+WY*Y(I)-WZ*Z(I))                                         ET 105
      TT1=CMPLX(COS(ARG),SIN(ARG))*SALP(I)*RETA                                 ET 106
      E(I2)=E(I2)+(CX*T1X(I)+CY*T1Y(I)+CZ*T1Z(I))*TT1                           ET 107
 12   E(I1)=E(I1)+(CX*T2X(I)+CY*T2Y(I)+CZ*T2Z(I))*TT1                           ET 108
      RETURN                                                                    ET 109
C                                                                               ET 110
C     INCIDENT PLANE WAVE. ELLIPTIC POLARIZATION.                               ET 111
C                                                                               ET 112
 13   TT1=-(0.,1.)*P6                                                          ET 113
      IF (IPR.EQ.3) TT1=-TT1                                                    ET 114
      IF (N.EQ.0) GO TO 16                                                      ET 115
      CX=PX+TT1*QX                                                              ET 116
      CY=PY+TT1*QY                                                              ET 117
      CZ=PZ+TT1*QZ                                                              ET 118
      DO 14 I=1,N                                                               ET 119
      ARG=-TP*(WX*X(I)+WY*Y(I)+WZ*Z(I))                                         ET 120
 14   E(I)=-(CX*CAB(I)+CY*SAB(I)+CZ*SALP(I))*CMPLX(COS(ARG),SIN(ARG))           ET 121
      IF (KSYMP.EQ.1) GO TO 16                                                  ET 122
      TT2=(CY*CPH-CX*SPH)*(RRH-RRV)                                             ET 123
      CX=RRV*CX-TT2*SPH                                                         ET 124
      CY=RRV*CY+TT2*CPH                                                         ET 125
      CZ=-RRV*CZ                                                                ET 126
      DO 15 I=1,N                                                               ET 127
      ARG=-TP*(WX*X(I)+WY*Y(I)-WZ*Z(I))                                         ET 128
```

```
      E(I)=E(I)-(CX*CAB(I)+CY*SAB(I)+CZ*SALP(I))*CMPLX(COS(ARG),SIN(ARG)  ET 129
     1)                                                                   ET 130
   16 IF (M.EQ.0) RETURN                                                  ET 131
      CX=QX-TT1*PX                                                        ET 132
      CY=QY-TT1*PY                                                        ET 133
      CZ=QZ-TT1*PZ                                                        ET 134
      I=LD+1                                                              ET 135
      I1=N-1                                                              ET 136
      DO 17 IS=1,M                                                        ET 137
      I=I-1                                                               ET 138
      I1=I1+2                                                             ET 139
      I2=I1+1                                                             ET 140
      ARG=-TP*(WX*X(I)+WY*Y(I)+WZ*Z(I))                                   ET 141
      TT2=CMPLX(COS(ARG),SIN(ARG))*SALP(I)*RETA                           ET 142
      E(I2)=(CX*T1X(I)+CY*T1Y(I)+CZ*T1Z(I))*TT2                           ET 143
   17 E(I1)=(CX*T2X(I)+CY*T2Y(I)+CZ*T2Z(I))*TT2                           ET 144
      IF (KSYMP.EQ.1) RETURN                                              ET 145
      TT1=(CY*CPH-CX*SPH)*(RRV-RRH)                                       ET 146
      CX=-(RRH*CX-TT1*SPH)                                                ET 147
      CY=-(RRH*CY+TT1*CPH)                                                ET 148
      CZ=RRH*CZ                                                           ET 149
      I=LD+1                                                              ET 150
      I1=N-1                                                              ET 151
      DO 18 IS=1,M                                                        ET 152
      I=I-1                                                               ET 153
      I1=I1+2                                                             ET 154
      I2=I1+1                                                             ET 155
      ARG=-TP*(WX*X(I)+WY*Y(I)-WZ*Z(I))                                   ET 156
      TT1=CMPLX(COS(ARG),SIN(ARG))*SALP(I)*RETA                           ET 157
      E(I2)=E(I2)+(CX*T1X(I)+CY*T1Y(I)+CZ*T1Z(I))*TT1                     ET 158
   18 E(I1)=E(I1)+(CX*T2X(I)+CY*T2Y(I)+CZ*T2Z(I))*TT1                     ET 159
      RETURN                                                              ET 160
C                                                                         ET 161
C     INCIDENT FIELD OF AN ELEMENTARY CURRENT SOURCE.                     ET 162
C                                                                         ET 163
   19 WZ=COS(P4)                                                          ET 164
      WX=WZ*COS(P5)                                                       ET 165
      WY=WZ*SIN(P5)                                                       ET 166
      WZ=SIN(P4)                                                          ET 167
      DS=P6*59.958                                                        ET 168
      DSH=P6/(2.*TP)                                                      ET 169
      NPM=N+M                                                             ET 170
      IS=LD+1                                                             ET 171
      I1=N-1                                                              ET 172
      DO 24 I=1,NPM                                                       ET 173
      II=I                                                                ET 174
      IF (I.LE.N) GO TO 20                                                ET 175
      IS=IS-1                                                             ET 176
      II=IS                                                               ET 177
      I1=I1+2                                                             ET 178
      I2=I1+1                                                             ET 179
   20 PX=X(II)-P1                                                         ET 180
      PY=Y(II)-P2                                                         ET 181
      PZ=Z(II)-P3                                                         ET 182
      RS=PX*PX+PY*PY+PZ*PZ                                                ET 183
      IF (RS.LT.1.E-30) GO TO 24                                          ET 184
      R=SQRT(RS)                                                          ET 185
      PX=PX/R                                                             ET 186
      PY=PY/R                                                             ET 187
      PZ=PZ/R                                                             ET 188
      CTH=PX*WX+PY*WY+PZ*WZ                                               ET 189
      STH=SQRT(1.-CTH*CTH)                                                ET 190
      QX=PX-WX*CTH                                                        ET 191
      QY=PY-WY*CTH                                                        ET 192
```

```
      QZ=PZ-WZ*CTH                                                      ET 193
      ARG=SQRT(QX*QX+QY*QY+QZ*QZ)                                       ET 194
      IF (ARG.LT.1.E-30) GO TO 21                                       ET 195
      QX=QX/ARG                                                         ET 196
      QY=QY/ARG                                                         ET 197
      QZ=QZ/ARG                                                         ET 198
      GO TO 22                                                          ET 199
21    QX=1.                                                             ET 200
      QY=0.                                                             ET 201
      QZ=0.                                                             ET 202
22    ARG=-TP*R                                                         ET 203
      TT1=CMPLX(COS(ARG),SIN(ARG))                                      ET 204
      IF (I.GT.N) GO TO 23                                              ET 205
      TT2=CMPLX(1.,-1./(R*TP))/RS                                       ET 206
      ER=DS*TT1*TT2*CTH                                                 ET 207
      ET=.5*DS*TT1*((0.,1.)*TP/R+TT2)*STH                               ET 208
      EZH=ER*CTH-ET*STH                                                 ET 209
      ERH=ER*STH+ET*CTH                                                 ET 210
      CX=EZH*WX+ERH*QX                                                  ET 211
      CY=EZH*WY+ERH*QY                                                  ET 212
      CZ=EZH*WZ+ERH*QZ                                                  ET 213
      E(I)=-(CX*CAB(I)+CY*SAB(I)+CZ*SALP(I))                            ET 214
      GO TO 24                                                          ET 215
23    PX=WY*QZ-WZ*QY                                                    ET 216
      PY=WZ*QX-WX*QZ                                                    ET 217
      PZ=WX*QY-WY*QX                                                    ET 218
      TT2=DSH*TT1*CMPLX(1./R,TP)/R*STH*SALP(II)                         ET 219
      CX=TT2*PX                                                         ET 220
      CY=TT2*PY                                                         ET 221
      CZ=TT2*PZ                                                         ET 222
      E(I2)=CX*T1X(II)+CY*T1Y(II)+CZ*T1Z(II)                            ET 223
      E(I1)=CX*T2X(II)+CY*T2Y(II)+CZ*T2Z(II)                            ET 224
24    CONTINUE                                                          ET 225
      RETURN                                                            ET 226
      END                                                               ET 227-
```

FACGF

PURPOSE

To perform the steps in the NGF solution that do not depend on the excitation vector.

METHOD

The NGF solution procedure is discussed in Section VI. The steps performed in FACGF are to evaluate $A^{-1}B$ and $D - CA^{-1}B$. The matrix $D - CA^{-1}B$ is then factored into triangular matrices L and U. The procedure is complicated by the possible need to use file storage for the matrices. The comments in the code and the tables for ICASX = 2, 3 and 4 in Section VII offer a fairly complete description of the procedure.

SYMBOL DICTIONARY

A	= array for matrix A (L U factors) or block of A if file storage is used
B	= array for B or block of B
BX	= array for B when $A^{-1}B$ is being computed with ICASX = 2. The array B starts at the beginning of CM in this case. BX leaves room for A_F at the beginning of CM
C	= array for C or block of C (matrix transposed)
D	= array for D or block of D (matrix transposed)
IBFL	= file on which B is stored
ICASS	= saved value of ICASE
IP	= pivot index array
IX	= data on row interchanges in LFACTR
M1	= number of patches in the NGF
MP	= number of patches in a symmetric section in the NGF
N1	= number of segments in the NGF
N1C	= number of columns in C (same as order of A)
N1CP	= N1C + 1
N2C	= order of matrix D
NBLSYS	= saved value of NBLSYM
NIC	= index increment
NLSYS	= saved value of NLSYM

NP = number of segments in a symmetric section in the NGF

NPSYS = saved value of NPSYM

SUM = summation variable for matrix products

```
      SUBROUTINE FACGF (A,B,C,D,BX,IP,IX,NP,N1,MP,M1,N1C,N2C)                FG   1
C     FACGF COMPUTES AND FACTORS D-C(INV(A)B).                               FG   2
      COMPLEX A,B,C,D,BX,SUM                                                 FG   3
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I     FG   4
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                     FG   5
      DIMENSION A(1), B(N1C,1), C(N1C,1), D(N2C,1), BX(N1C,1), IP(1), IX     FG   6
     1(1)                                                                    FG   7
      IF (N2C.EQ.0) RETURN                                                   FG   8
      IBFL=14                                                                FG   9
      IF (ICASX.LT.3) GO TO 1                                                FG  10
C     CONVERT B FROM BLOCKS OF ROWS ON T14 TO BLOCKS OF COL. ON T16          FG  11
      CALL REBLK (B,C,N1C,NPBX,N2C)                                          FG  12
      IBFL=16                                                                FG  13
1     NPB=NPBL                                                               FG  14
      IF (ICASX.EQ.2) REWIND 14                                              FG  15
C     COMPUTE INV(A)B AND WRITE ON TAPE14                                    FG  16
      DO 2 IB=1,NBBL                                                         FG  17
      IF (IB.EQ.NBBL) NPB=NLBL                                               FG  18
      IF (ICASX.GT.1) READ (IBFL) ((BX(I,J),I=1,N1C),J=1,NPB)                FG  19
      CALL SOLVES (A,IP,BX,N1C,NPB,NP,N1,MP,M1,13,13)                        FG  20
      IF (ICASX.EQ.2) REWIND 14                                              FG  21
      IF (ICASX.GT.1) WRITE (14) ((BX(I,J),I=1,N1C),J=1,NPB)                 FG  22
2     CONTINUE                                                               FG  23
      IF (ICASX.EQ.1) GO TO 3                                                FG  24
      REWIND 11                                                              FG  25
      REWIND 12                                                              FG  26
      REWIND 15                                                              FG  27
      REWIND IBFL                                                            FG  28
3     NPC=NPBL                                                               FG  29
C     COMPUTE D-C(INV(A)B) AND WRITE ON TAPE11                               FG  30
      DO 8 IC=1,NBBL                                                         FG  31
      IF (IC.EQ.NBBL) NPC=NLBL                                               FG  32
      IF (ICASX.EQ.1) GO TO 4                                                FG  33
      READ (15) ((C(I,J),I=1,N1C),J=1,NPC)                                   FG  34
      READ (12) ((D(I,J),I=1,N2C),J=1,NPC)                                   FG  35
      REWIND 14                                                              FG  36
4     NPB=NPBL                                                               FG  37
      NIC=0                                                                  FG  38
      DO 7 IB=1,NBBL                                                         FG  39
      IF (IB.EQ.NBBL) NPB=NLBL                                               FG  40
      IF (ICASX.GT.1) READ (14) ((B(I,J),I=1,N1C),J=1,NPB)                   FG  41
      DO 6 I=1,NPB                                                           FG  42
      II=1+NIC                                                               FG  43
      DO 6 J=1,NPC                                                           FG  44
      SUM=(0.,0.)                                                            FG  45
      DO 5 K=1,N1C                                                           FG  46
5     SUM=SUM+B(K,I)*C(K,J)                                                  FG  47
6     D(II,J)=D(II,J)-SUM                                                    FG  48
7     NIC=NIC+NPBL                                                           FG  49
      IF (ICASX.GT.1) WRITE (11) ((D(I,J),I=1,N2C),J=1,NPBL)                 FG  50
8     CONTINUE                                                               FG  51
      IF (ICASX.EQ.1) GO TO 9                                                FG  52
      REWIND 11                                                              FG  53
      REWIND 12                                                              FG  54
      REWIND 14                                                              FG  55
      REWIND 15                                                              FG  56
9     N1CP=N1C+1                                                             FG  57
C     FACTOR D-C(INV(A)B)                                                    FG  58
      IF (ICASX.GT.1) GO TO 10                                               FG  59
      CALL FACTR (N2C,D,IP(N1CP),N2C)                                        FG  60
      GO TO 13                                                               FG  61
10    IF (ICASX.EQ.4) GO TO 12                                               FG  62
      NPB=NPBL                                                               FG  63
      IC=0                                                                   FG  64
```

```
      DO 11 IB=1,NBBL                                                   FG  65
      IF (IB.EQ.NBBL) NPB=NLBL                                          FG  66
      II=IC+1                                                           FG  67
      IC=IC+N2C*NPB                                                     FG  68
11    READ (11) (B(I,1),I=II,IC)                                        FG  69
      REWIND 11                                                         FG  70
      CALL FACTR (N2C,B,IP(N1CP),N2C)                                   FG  71
      NIC=N2C*N2C                                                       FG  72
      WRITE (11) (B(I,1),I=1,NIC)                                       FG  73
      REWIND 11                                                         FG  74
      GO TO 13                                                          FG  75
12    NBLSYS=NBLSYM                                                     FG  76
      NPSYS=NPSYM                                                       FG  77
      NLSYS=NLSYM                                                       FG  78
      ICASS=ICASE                                                       FG  79
      NBLSYM=NBBL                                                       FG  80
      NPSYM=NPBL                                                        FG  81
      NLSYM=NLBL                                                        FG  82
      ICASE=3                                                           FG  83
      CALL FACIO (B,N2C,1,IX(N1CP),11,12,16,11)                         FG  84
      CALL LUNSCR (B,N2C,1,IP(N1CP),IX(N1CP),12,11,16)                  FG  85
      NBLSYM=NBLSYS                                                     FG  86
      NPSYM=NPSYS                                                       FG  87
      NLSYM=NLSYS                                                       FG  88
      ICASE=ICASS                                                       FG  89
13    RETURN                                                            FG  90
      END                                                               FG  91-
```

FACIO

PURPOSE

To read and write matrix blocks needed for the LU decomposition.

METHOD

Sequential access is used on all files. The matrix is initially stored on file IU1 in blocks of columns of the transposed matrix. The block size is such that two blocks will fit into the array A for the Gauss elimination process. If the matrix were divided into four blocks, the order for reading the blocks into core would be

Blocks	
1, 2	1 and 2 will be completely factored
1, 3	3 and 4 partially factored
1, 4	
2, 3	factorization of 3 completed
2, 4	4 partially factored
3, 4	factorization complete

IU1 is the initial input file. Partially factored blocks are read from file IFILE3 and written to IFILE4 where IFILE3 = IU3 and IFILE4 = IU4 when IXBLK1 is odd, and IFILE3 = IU4 and IFILE4 = IU3 when IXBLK1 is even. Completed blocks are written to file IU2. Although the last block may be shorter than other blocks the same number of words is read or written. The excess words are ignored in subroutine LFACTR.

Subroutine LFACTR is called to perform the Gauss elimination. For a symmetric structure the loop from F018 to F043 factors each submatrix.

SYMBOL DICTIONARY

A	= array for matrix storage
I1	= location in A of beginning of block 1
I2	= location in A of end of block 1
I3	= location in A of beginning of block 2
I4	= location in A of end of block 2
IFILE3	= input file
IFILE4	= output file
IP	= array for pivot element indices

IT	= number of words in a matrix block
IU1, IU2, IU3, IU4	= file numbers
IXBLK1	= number of first block stored in A
IXBLK2	= number of second block stored in A
KA	= first location in IP for submatrix KK
NBM	= number of blocks minus one
NOP	= number of submatrices for symmetry
NROW	= number of rows in a block
T1, T2, TIME	= variables to sum total time spent in LFACTR

FACIO

```
      SUBROUTINE FACIO (A,NROW,NOP,IP,IU1,IU2,IU3,IU4)                  FO   1
C                                                                       FO   2
C     FACIO CONTROLS I/O FOR OUT-OF-CORE FACTORIZATION                  FO   3
C                                                                       FO   4
      COMPLEX A                                                         FO   5
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I FO   6
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                FO   7
      DIMENSION A(NROW,1), IP(NROW)                                     FO   8
      IT=2*NPSYM*NROW                                                   FO   9
      NBM=NBLSYM-1                                                      FO  10
      I1=1                                                              FO  11
      I2=IT                                                             FO  12
      I3=I2+1                                                           FO  13
      I4=2*IT                                                           FO  14
      TIME=0.                                                           FO  15
      REWIND IU1                                                        FO  16
      REWIND IU2                                                        FO  17
      DO 3 KK=1,NOP                                                     FO  18
      KA=(KK-1)*NROW+1                                                  FO  19
      IFILE3=IU1                                                        FO  20
      IFILE4=IU3                                                        FO  21
      DO 2 IXBLK1=1,NBM                                                 FO  22
      REWIND IU3                                                        FO  23
      REWIND IU4                                                        FO  24
      CALL BLCKIN (A,IFILE3,I1,I2,1,17)                                 FO  25
      IXBP=IXBLK1+1                                                     FO  26
      DO 1 IXBLK2=IXBP,NBLSYM                                           FO  27
      CALL BLCKIN (A,IFILE3,I3,I4,1,18)                                 FO  28
      CALL SECOND (T1)                                                  FO  29
      CALL LFACTR (A,NROW,IXBLK1,IXBLK2,IP(KA))                         FO  30
      CALL SECOND (T2)                                                  FO  31
      TIME=TIME+T2-T1                                                   FO  32
      IF (IXBLK2.EQ.IXBP) CALL BLCKOT (A,IU2,I1,I2,1,19)                FO  33
      IF (IXBLK1.EQ.NBM.AND.IXBLK2.EQ.NBLSYM) IFILE4=IU2                FO  34
      CALL BLCKOT (A,IFILE4,I3,I4,1,20)                                 FO  35
1     CONTINUE                                                          FO  36
      IFILE3=IU3                                                        FO  37
      IFILE4=IU4                                                        FO  38
      IF ((IXBLK1/2)*2.NE.IXBLK1) GO TO 2                               FO  39
      IFILE3=IU4                                                        FO  40
      IFILE4=IU3                                                        FO  41
2     CONTINUE                                                          FO  42
3     CONTINUE                                                          FO  43
      REWIND IU1                                                        FO  44
      REWIND IU2                                                        FO  45
      REWIND IU3                                                        FO  46
      REWIND IU4                                                        FO  47
      PRINT 4, TIME                                                     FO  48
      RETURN                                                            FO  49
C                                                                       FO  50
4     FORMAT (35H CP TIME TAKEN FOR FACTORIZATION = ,E12.5)             FO  51
      END                                                               FO  52-
```

FACTR

PURPOSE

To factor a complex matrix into a lower triangular and an upper triangular matrix using the Gauss-Doolittle technique. The matrix in this case is a transposed matrix. The factored matrix is used by subroutine SOLVE to determine the solution of the matrix equation Ax = B.

METHOD

The algorithm used in this routine is presented by A. Ralston (ref. 1). The decomposition of the matrix A is such that A = LU, where L is a lower triangular matrix with 1's down the diagonal, and U is an upper triangular matrix. The L and U matrices overwrite the matrix A. The computations to obtain L and U are done using one complex scratch vector (D) and one integer vector (IP) that keep track of row interchanges when elements are positioned for size. If positioning for size is not taken into account, the general procedure is

$$a_{11} = u_{11}$$

$$a_{i1} = \ell_{i1}u_{11} \quad i = 2, \ldots, n$$

which gives the first column of the L and U matrices. Then

$$a_{12} = u_{12}$$

$$a_{22} = \ell_{21}u_{12} + u_{22}$$

$$a_{i2} = \ell_{i1}u_{12} + \ell_{i2}u_{22} \quad i = 3, \ldots, n$$

gives the second column. The computations for the successive columns continue in this way. The general equations for the r^{th} column are

$$a_{1r} = u_{1r}$$

$$a_{2r} = \ell_{21}u_{1r} + u_{2r}$$

$$\vdots$$

$$a_{rr} = \ell_{r1}u_{1r} + \ell_{r2}u_{2r} + \ldots + \ell_{r,r-1}u_{r-1,r} + u_{rr}$$

$$a_{ir} = \ell_{i1}u_{1r} + \ldots + \ell_{ir}u_{rr}, \quad i = r + 1, \ldots, n$$

There are only two differences in the coding used in FACTR and the coding suggested by Ralston. The first is that double precision variables are not used for the accumulation of sums, since for the size and conditioning of the matrices anticipated in core, the computer word length is sufficient to insure accuracy. The second difference is that the row and column indices of the A matrix in the routine have been interchanged to handle the transposed matrix.

CODING

The coding is divided into five steps which correspond to the steps given by Ralston.

FA14 Loop over columns (rows with the interchanged indices used in the routine).

FA18 - FA20 Fill D vector with column (row) of A.

FA24 - FA35 Solution for u_{ir} ($i = 1,\ldots,r$) in the above equations taking into account positioning.

FA40 - FA54 Selecting largest value for positioning.

FA58 - FA62 Solution for ℓ_{ir} ($i = r + 1,\ldots,n$) in the above equations.

FA64 - FA66 Printing of small pivot elements.

SYMBOL DICTIONARY

A = input transposed matrix overwritten with calculated L^T and U^T matrices

CONJG = external routine (conjugate of a complex number)

D = scratch vector

DMAX = maximum value in D

ELMAG = intermediate variable

I = DO loop index

IFLG = small pivot flag

IP = integer vector storing positioning information

J = DO loop index

JP1 = J + 1

K = DO loop index

N = order of matrix being factored

NDIM = dimensions of the array where the matrix is stored. NDIM $\geq$ N

PJ = intermediate variable

PR = intermediate variable

R = DO loop index

REAL = external routine (real part of complex number)

RM1 = R - 1

RP1 = R + 1

```
      SUBROUTINE FACTR (N,A,IP,NDIM)                                    FA   1
C                                                                       FA   2
C     SUBROUTINE TO FACTOR A MATRIX INTO A UNIT LOWER TRIANGULAR MATRIX  FA   3
C     AND AN UPPER TRIANGULAR MATRIX USING THE GAUSS-DOOLITTLE ALGORITHM FA   4
C     PRESENTED ON PAGES 411-418 OF A. RALSTON--A FIRST COURSE IN       FA   5
C     NUMERICAL ANALYSIS.  COMMENTS BELOW REFER TO COMMENTS IN RALSTONS  FA   6
C     TEXT.    (MATRIX TRANSPOSED.                                      FA   7
C                                                                       FA   8
      COMPLEX A,D,ARJ                                                   FA   9
      DIMENSION A(NDIM,NDIM), IP(NDIM)                                  FA  10
      COMMON /SCRATM/ D(600)                                            FA  11
      INTEGER R,RM1,RP1,PJ,PR                                           FA  12
      IFLG=0                                                            FA  13
      DO 9 R=1,N                                                        FA  14
C                                                                       FA  15
C     STEP 1                                                            FA  16
C                                                                       FA  17
      DO 1 K=1,N                                                        FA  18
      D(K)=A(R,K)                                                       FA  19
1     CONTINUE                                                          FA  20
C                                                                       FA  21
C     STEPS 2 AND 3                                                     FA  22
C                                                                       FA  23
      RM1=R-1                                                           FA  24
      IF (RM1.LT.1) GO TO 4                                             FA  25
      DO 3 J=1,RM1                                                      FA  26
      PJ=IP(J)                                                          FA  27
      ARJ=D(PJ)                                                         FA  28
      A(R,J)=ARJ                                                        FA  29
      D(PJ)=D(J)                                                        FA  30
      JP1=J+1                                                           FA  31
      DO 2 I=JP1,N                                                      FA  32
      D(I)=D(I)-A(J,I)*ARJ                                              FA  33
2     CONTINUE                                                          FA  34
3     CONTINUE                                                          FA  35
4     CONTINUE                                                          FA  36
C                                                                       FA  37
C     STEP 4                                                            FA  38
C                                                                       FA  39
      DMAX=REAL(D(R)*CONJG(D(R)))                                       FA  40
      IP(R)=R                                                           FA  41
      RP1=R+1                                                           FA  42
      IF (RP1.GT.N) GO TO 6                                             FA  43
      DO 5 I=RP1,N                                                      FA  44
      ELMAG=REAL(D(I)*CONJG(D(I)))                                      FA  45
      IF (ELMAG.LT.DMAX) GO TO 5                                        FA  46
      DMAX=ELMAG                                                        FA  47
      IP(R)=I                                                           FA  48
5     CONTINUE                                                          FA  49
6     CONTINUE                                                          FA  50
      IF (DMAX.LT.1.E-10) IFLG=1                                        FA  51
      PR=IP(R)                                                          FA  52
      A(R,R)=D(PR)                                                      FA  53
      D(PR)=D(R)                                                        FA  54
C                                                                       FA  55
C     STEP 5                                                            FA  56
C                                                                       FA  57
      IF (RP1.GT.N) GO TO 8                                             FA  58
      ARJ=1./A(R,R)                                                     FA  59
      DO 7 I=RP1,N                                                      FA  60
      A(R,I)=D(I)*ARJ                                                   FA  61
7     CONTINUE                                                          FA  62
8     CONTINUE                                                          FA  63
      IF (IFLG.EQ.0) GO TO 9                                            FA  64
```

```
      PRINT 10, R,DMAX                                                  FA  65
      IFLG=0                                                            FA  66
    9 CONTINUE                                                          FA  67
      RETURN                                                            FA  68
C                                                                       FA  69
   10 FORMAT (1H ,6HPIVOT(,I3,2H)=,E16.8)                               FA  70
      END                                                               FA  71-
```

FACTRS

PURPOSE

To call the appropriate subroutines for the LU decomposition of a matrix.

METHOD

The operation of FACTRS depends on the mode of storage of the matrix as determined by the value of ICASE (see COMMON/MATPAR/ in Section III). For ICASE = 1 subroutine FACTR is called at FS16 to factor the matrix. For ICASE = 2 FACTR is called for each of the NOP submatrices. If ICASE = 3 FACIO and LUNSCR are called at FS23 and FS24. FACIO reads the matrix from file IU1 and writes the result on file IU2. LUNSCR leaves the final result on file IU3.

For ICASE = 4 (symmetry, submatrices fit in core) or ICASE = 5 (symmetry, submatrices do not fit in core) the matrix elements on file IU1 are written in a new order on file IU2 from FS29 to FS46. The sequence of data on file IU1 is

column 1 of submatrix 1
column 1 of submatrix 2
⋮
column 1 of submatrix NOP
column 2 of submatrix 1
⋮
column 2 of submatrix NOP
column 3 of submatrix 1
⋮
column NPBLK of submatrix NOP

The matrices are written onto file IU2 in the sequence

column 1 of submatrix 1
column 2 of submatrix 1
⋮

column NPBLK of submatrix 1
column 1 of submatrix 2

⋮

column NPBLK of submatrix NOP

For ICASE = 4 each submatrix is then read into memory at FS58 and decomposed into LU factors by calling FACTR at FS60. The factored matrices are written to file IU3 at FS61.

For ICASE = 5 the matrices are transferred from file IU2 to IU1 at FS76 to FS77. Subroutine FACIO is then called to factor all of the NOP submatrices. The result is left on file IU2. LUNSCR reorders the rows of each matrix and leaves the result on IU3.

SYMBOL DICTIONARY

A	= array for matrix storage
I2	= number of words in a block
ICOLS	= number of columns in a block
IP	= array for pivot element indices
IR1, IR2, IRR1, IRR2	= row indices for reordering columns
IU1, IU2, IU3, IU4	= file numbers
IX	= array of pivot element data
KA	= starting location of a submatrix in the array
NOP	= number of symmetric sections
NP	= number of equations for each symmetric section (order of submatrix)
NROW	= total number of equations (NP x NOP)

```
      SUBROUTINE FACTRS (NP,NROW,A,IP,IX,IU1,IU2,IU3,IU4)                FS    1
C                                                                        FS    2
C     FACTRS, FOR SYMMETRIC STRUCTURE, TRANSFORMS SUBMATRICIES TO FORM   FS    3
C     MATRICIES OF THE SYMMETRIC MODES AND CALLS ROUTINE TO FACTOR       FS    4
C     MATRICIES.  IF NO SYMMETRY, THE ROUTINE IS CALLED TO FACTOR THE    FS    5
C     COMPLETE MATRIX.                                                   FS    6
C                                                                        FS    7
      COMPLEX A                                                          FS    8
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I FS    9
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                 FS   10
      DIMENSION A(1), IP(NROW), IX(NROW)                                 FS   11
      NOP=NROW/NP                                                        FS   12
      IF (ICASE.GT.2) GO TO 2                                            FS   13
      DO 1 KK=1,NOP                                                      FS   14
      KA=(KK-1)*NP+1                                                     FS   15
    1 CALL FACTR (NP,A(KA),IP(KA),NROW)                                  FS   16
      RETURN                                                             FS   17
    2 IF (ICASE.GT.3) GO TO 3                                            FS   18
C                                                                        FS   19
C     FACTOR SUBMATRICIES, OR FACTOR COMPLETE MATRIX IF NO SYMMETRY      FS   20
C     EXISTS.                                                            FS   21
C                                                                        FS   22
      CALL FACIO (A,NROW,NOP,IX,IU1,IU2,IU3,IU4)                         FS   23
      CALL LUNSCR (A,NROW,NOP,IP,IX,IU2,IU3,IU4)                         FS   24
      RETURN                                                             FS   25
C                                                                        FS   26
C     REWRITE THE MATRICES BY COLUMNS ON TAPE 13                         FS   27
C                                                                        FS   28
    3 I2=2*NPBLK*NROW                                                    FS   29
      REWIND IU2                                                         FS   30
      DO 5 K=1,NOP                                                       FS   31
      REWIND IU1                                                         FS   32
      ICOLS=NPBLK                                                        FS   33
      IR2=K*NP                                                           FS   34
      IR1=IR2-NP+1                                                       FS   35
      DO 5 L=1,NBLOKS                                                    FS   36
      IF (NBLOKS.EQ.1.AND.K.GT.1) GO TO 4                                FS   37
      CALL BLCKIN (A,IU1,1,I2,1,602)                                     FS   38
      IF (L.EQ.NBLOKS) ICOLS=NLAST                                       FS   39
    4 IRR1=IR1                                                           FS   40
      IRR2=IR2                                                           FS   41
      DO 5 ICOLDX=1,ICOLS                                                FS   42
      WRITE (IU2) (A(I),I=IRR1,IRR2)                                     FS   43
      IRR1=IRR1+NROW                                                     FS   44
      IRR2=IRR2+NROW                                                     FS   45
    5 CONTINUE                                                           FS   46
      REWIND IU1                                                         FS   47
      REWIND IU2                                                         FS   48
      IF (ICASE.EQ.5) GO TO 8                                            FS   49
      REWIND IU3                                                         FS   50
      IRR1=NP*NP                                                         FS   51
      DO 7 KK=1,NOP                                                      FS   52
      IR1=1-NP                                                           FS   53
      IR2=0                                                              FS   54
      DO 6 I=1,NP                                                        FS   55
      IR1=IR1+NP                                                         FS   56
      IR2=IR2+NP                                                         FS   57
    6 READ (IU2) (A(J),J=IR1,IR2)                                        FS   58
      KA=(KK-1)*NP+1                                                     FS   59
      CALL FACTR (NP,A,IP(KA),NP)                                        FS   60
      WRITE (IU3) (A(I),I=1,IRR1)                                        FS   61
    7 CONTINUE                                                           FS   62
      REWIND IU2                                                         FS   63
      REWIND IU3                                                         FS   64
```

```
      RETURN                                                        FS  65
    8 I2=2*NPSYM*NP                                                 FS  66
      DO 10 KK=1,NOP                                                FS  67
      J2=NPSYM                                                      FS  68
      DO 10 L=1,NBLSYM                                              FS  69
      IF (L.EQ.NBLSYM) J2=NLSYM                                     FS  70
      IR1=1-NP                                                      FS  71
      IR2=0                                                         FS  72
      DO 9 J=1,J2                                                   FS  73
      IR1=IR1+NP                                                    FS  74
      IR2=IR2+NP                                                    FS  75
    9 READ (IU2) (A(I),I=IR1,IR2)                                   FS  76
   10 CALL BLCKOT (A,IU1,1,I2,1,193)                                FS  77
      REWIND IU1                                                    FS  78
      CALL FACIO (A,NP,NOP,IX,IU1,IU2,IU3,IU4)                      FS  79
      CALL LUNSCR (A,NP,NOP,IP,IX,IU2,IU3,IU4)                      FS  80
      RETURN                                                        FS  81
      END                                                           FS  82-
```

FBAR

PURPOSE

To compute the Sommerfeld attenuation function for Norton's asymptotic field approximations.

METHOD

The value returned for FBAR is

$$F(P) = 1 - j\sqrt{\pi P}\exp(-P)\left[1 - \mathrm{erf}(j\sqrt{P})\right]$$

where erf(z) is the error function. If $|j\sqrt{P}| \le 3$ the value of $\mathrm{erf}(j\sqrt{P})$ is computed from the series

$$\mathrm{erf}(z) = \frac{2}{\sqrt{\pi}}\sum_{n=0}^{\infty}\frac{(-1)^n z^{2n+1}}{n!(2n+1)}$$

For $|j\sqrt{P}| > 3$, F(P) is evaluated from the first six terms of the asymptotic expansion

$$\sqrt{\pi}\, z\exp(z^2)\left(1 - \mathrm{erf}(z)\right) \approx 1 + \sum_{M=1}^{\infty}(-1)^M\frac{1\cdot 3\cdots(2M-1)}{(2z^2)^M}$$

for $z \to \infty$, $|\arg(z)| < \frac{3\pi}{4}$

SYMBOL DICTIONARY

ACCS = relative convergence test value
FJ = $j = \sqrt{-1}$
MINUS = 1 if Re(z) < 0
P = P
POW = $(-1)^n z^{2n+1}/n!$
SMS = magnitude squared of series
SP = $\sqrt{\pi}$
SUM = series value

TERM = term in the series

TMS = $|\text{TERM}|^2$

TOSP = $2/\sqrt{\pi}$

Z = $j\sqrt{P}$

ZS = z^2

FBAR

```
      1       COMPLEX FUNCTION FBAR(P)                                          FR   1
      2 C                                                                       FR   2
      3 C     FBAR IS SOMMERFELD ATTENUATION FUNCTION FOR NUMERICAL DISTANCE P  FR   3
      4 C                                                                       FR   4
      5       COMPLEX Z,ZS,SUM,POW,TERM,P,FJ                                    FR   5
      6       DIMENSION FJX(2)                                                  FR   6
      7       EQUIVALENCE (FJ,FJX)                                              FR   7
      8       DATA TOSP/1.128379167/,ACCS/1.E-12/,SP/1.772453851/,FJX/0.,1./     FR   8
      9       Z=FJ*CSQRT(P)                                                     FR   9
     10       IF (CABS(Z).GT.3.) GO TO 3                                        FR  10
     11 C                                                                       FR  11
     12 C     SERIES EXPANSION                                                  FR  12
     13 C                                                                       FR  13
     14       ZS=Z*Z                                                            FR  14
     15       SUM=Z                                                             FR  15
     16       POW=Z                                                             FR  16
     17       DO 1 I=1,100                                                      FR  17
     18       POW=-POW*ZS/FLOAT(I)                                              FR  18
     19       TERM=POW/(2.*I+1.)                                                FR  19
     20       SUM=SUM+TERM                                                      FR  20
     21       TMS=REAL(TERM*CONJG(TERM))                                        FR  21
     22       SMS=REAL(SUM*CONJG(SUM))                                          FR  22
     23       IF (TMS/SMS.LT.ACCS) GO TO 2                                      FR  23
     24 1     CONTINUE                                                          FR  24
     25 2     FBAR=1.-(1.-SUM*TOSP)*Z*CEXP(ZS)*SP                               FR  25
     26       RETURN                                                            FR  26
     27 C                                                                       FR  27
     28 C     ASYMPTOTIC EXPANSION                                              FR  28
     29 C                                                                       FR  29
     30 3     IF (REAL(Z).GE.0.) GO TO 4                                        FR  30
     31       MINUS=1                                                           FR  31
     32       Z=-Z                                                              FR  32
     33       GO TO 5                                                           FR  33
     34 4     MINUS=0                                                           FR  34
     35 5     ZS=.5/(Z*Z)                                                       FR  35
     36       SUM=(0.,0.)                                                       FR  36
     37       TERM=(1.,0.)                                                      FR  37
     38       DO 6 I=1,6                                                        FR  38
     39       TERM=-TERM*(2.*I-1.)*ZS                                           FR  39
     40 6     SUM=SUM+TERM                                                      FR  40
     41       IF (MINUS.EQ.1) SUM=SUM-2.*SP*Z*CEXP(Z*Z)                         FR  41
     42       FBAR=-SUM                                                         FR  42
     43       RETURN                                                            FR  43
     44       END                                                               FR  44-
```

FBLOCK

PURPOSE

To set parameters for storage of the interaction matrix.

METHOD

FBLOCK sets values of the parameters ICASE through NLSYM in COMMON/MATPAR/. The input parameters NROW and NCOL are the number of rows and columns in the non-transposed matrix. IMAX is the number of matrix elements that can be stored in the array in COMMON/CMB/. If a NGF file will be written (WG card) then IRNGF complex locations are reserved for future use. If a NGF file has not been requested then IRNGF is zero.

If (NROW)(NCOL) $\leq$ IMAX - IRNGF the complete matrix can be stored in COMMON/CMB/. ICASE is then 1 for no symmetry or 2 for symmetry. If the structure has symmetry and one submatrix fits in core but not the complete matrix,

$$(NROW)(NCOL) > IMAX - IRNGF$$
$$NROW^2 \leq IMAX - IRNGF,$$

then ICASE is 4.

If the matrix cannot fit in core for the LU decomposition then it is divided into blocks of rows (columns of the transposed matrix) for transfer between core and file storage. The blocks are made as large as possible so that one block fits into IMAX - IRNGF locations and two blocks fit into IMAX locations. Since two blocks are needed in core only during the Gauss elimination process this makes at least IRNGF locations available during the NGF solution.

CODING

FB10 - FB17	ICASE = 1 or 2
FB20 - FB32	ICASE = 3
FB34 - FB40	ICASE = 4 or 5, block parameters for whole matrix
FB42 - FB48	ICASE = 4, block parameters for submatrices
FB49 - FB58	ICASE = 5, block parameters for submatrices

FB65 - FB71 S matrix for rotational symmetry (Equation III of Part I)

FB75 - FB88 S matrix for plane symmetry

SYMBOL DICTIONARY

ARG = $2\pi(I - 1)(J - 1)/NOP$

IMAX = number of complex numbers that can be stored in COMMON/CMB/

IMX1 = IMAX - IRNGF

IPSYM = parameter from COMMON/DATA/

IRNGF = array storage reserved for NGF

KA = number of planes of symmetry

NCOL = number of columns in matrix

NOP = number of symmetric sections

NROW = number of rows in matrix

PHAZ = $2\pi/NOP$

```
      SUBROUTINE FBLOCK (NROW,NCOL,IMAX,IRNGF,IPSYM)                    FB   1
C     FBLOCK SETS PARAMETERS FOR OUT-OF-CORE SOLUTION FOR THE PRIMARY   FB   2
C     MATRIX (A)                                                        FB   3
      COMPLEX SSX,DETER                                                 FB   4
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I FB   5
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                FB   6
      COMMON /SMAT/ SSX(16,16)                                          FB   7
      IMX1=IMAX-IRNGF                                                   FB   8
      IF (NROW*NCOL.GT.IMX1) GO TO 2                                    FB   9
      NBLOKS=1                                                          FB  10
      NPBLK=NROW                                                        FB  11
      NLAST=NROW                                                        FB  12
      IMAT=NROW*NCOL                                                    FB  13
      IF (NROW.NE.NCOL) GO TO 1                                         FB  14
      ICASE=1                                                           FB  15
      RETURN                                                            FB  16
1     ICASE=2                                                           FB  17
      GO TO 5                                                           FB  18
2     IF (NROW.NE.NCOL) GO TO 3                                         FB  19
      ICASE=3                                                           FB  20
      NPBLK=IMAX/(2*NCOL)                                               FB  21
      NPSYM=IMX1/NCOL                                                   FB  22
      IF (NPSYM.LT.NPBLK) NPBLK=NPSYM                                   FB  23
      IF (NPBLK.LT.1) GO TO 12                                          FB  24
      NBLOKS=(NROW-1)/NPBLK                                             FB  25
      NLAST=NROW-NBLOKS*NPBLK                                           FB  26
      NBLOKS=NBLOKS+1                                                   FB  27
      NBLSYM=NBLOKS                                                     FB  28
      NPSYM=NPBLK                                                       FB  29
      NLSYM=NLAST                                                       FB  30
      IMAT=NPBLK*NCOL                                                   FB  31
      PRINT 14, NBLOKS,NPBLK,NLAST                                      FB  32
      GO TO 11                                                          FB  33
3     NPBLK=IMAX/NCOL                                                   FB  34
      IF (NPBLK.LT.1) GO TO 12                                          FB  35
      IF (NPBLK.GT.NROW) NPBLK=NROW                                     FB  36
      NBLOKS=(NROW-1)/NPBLK                                             FB  37
      NLAST=NROW-NBLOKS*NPBLK                                           FB  38
      NBLOKS=NBLOKS+1                                                   FB  39
      PRINT 14, NBLOKS,NPBLK,NLAST                                      FB  40
      IF (NROW*NROW.GT.IMX1) GO TO 4                                    FB  41
      ICASE=4                                                           FB  42
      NBLSYM=1                                                          FB  43
      NPSYM=NROW                                                        FB  44
      NLSYM=NROW                                                        FB  45
      IMAT=NROW*NROW                                                    FB  46
      PRINT 15                                                          FB  47
      GO TO 5                                                           FB  48
4     ICASE=5                                                           FB  49
      NPSYM=IMAX/(2*NROW)                                               FB  50
      NBLSYM=IMX1/NROW                                                  FB  51
      IF (NBLSYM.LT.NPSYM) NPSYM=NBLSYM                                 FB  52
      IF (NPSYM.LT.1) GO TO 12                                          FB  53
      NBLSYM=(NROW-1)/NPSYM                                             FB  54
      NLSYM=NROW-NBLSYM*NPSYM                                           FB  55
      NBLSYM=NBLSYM+1                                                   FB  56
      PRINT 16, NBLSYM,NPSYM,NLSYM                                      FB  57
      IMAT=NPSYM*NROW                                                   FB  58
5     NOP=NCOL/NROW                                                     FB  59
      IF (NOP*NROW.NE.NCOL) GO TO 13                                    FB  60
      IF (IPSYM.GT.0) GO TO 7                                           FB  61
C                                                                       FB  62
C     SET UP SSX MATRIX FOR ROTATIONAL SYMMETRY.                        FB  63
C                                                                       FB  64
```

```
      PHAZ=6.2831853072/NOP                                              FB  65
      DO 6 I=2,NOP                                                       FB  66
      DO 6 J=I,NOP                                                       FB  67
      ARG=PHAZ*FLOAT(I-1)*FLOAT(J-1)                                     FB  68
      SSX(I,J)=CMPLX(COS(ARG),SIN(ARG))                                  FB  69
    6 SSX(J,I)=SSX(I,J)                                                  FB  70
      GO TO 11                                                           FB  71
C                                                                        FB  72
C     SET UP SSX MATRIX FOR PLANE SYMMETRY                               FB  73
C                                                                        FB  74
    7 KK=1                                                               FB  75
      SSX(1,1)=(1.,0.)                                                   FB  76
      IF ((NOP.EQ.2).OR.(NOP.EQ.4).OR.(NOP.EQ.8)) GO TO 8                FB  77
      STOP                                                               FB  78
    8 KA=NOP/2                                                           FB  79
      IF (NOP.EQ.8) KA=3                                                 FB  80
      DO 10 K=1,KA                                                       FB  81
      DO 9 I=1,KK                                                        FB  82
      DO 9 J=1,KK                                                        FB  83
      DETER=SSX(I,J)                                                     FB  84
      SSX(I,J+KK)=DETER                                                  FB  85
      SSX(I+KK,J+KK)=-DETER                                              FB  86
    9 SSX(I+KK,J)=DETER                                                  FB  87
   10 KK=KK*2                                                            FB  88
   11 RETURN                                                             FB  89
   12 PRINT 17, NROW,NCOL                                                FB  90
      STOP                                                               FB  91
   13 PRINT 18, NROW,NCOL                                                FB  92
      STOP                                                               FB  93
C                                                                        FB  94
   14 FORMAT (//35H MATRIX FILE STORAGE -  NO. BLOCKS=,I5,19H COLUMNS PE FB  95
     1R BLOCK=,I5,23H COLUMNS IN LAST BLOCK=,I5)                         FB  96
   15 FORMAT (25H SUBMATRICIES FIT IN CORE)                              FB  97
   16 FORMAT (38H SUBMATRIX PARTITIONING -  NO. BLOCKS=,I5,19H COLUMNS P FB  98
     1ER BLOCK=,I5,23H COLUMNS IN LAST BLOCK=,I5)                        FB  99
   17 FORMAT (40H ERROR - INSUFFICIENT STORAGE FOR MATRIX,2I5)           FB 100
   18 FORMAT (28H SYMMETRY ERROR - NROW,NCOL=,2I5)                       FB 101
      END                                                                FB 102-
```

FBNGF

PURPOSE

To set parameters for storage of the matrices B, C and D for the NGF solution.

METHOD

The modes of matrix storage for the NGF solution are described in Section VIII. FBNGF choses the smallest ICASX (1 through 4) possible given the size of the matrices A, B, C and D and the space available in the array CM in COMMON/CMB/. If B, C and D must be divided into blocks (ICASX = 3 or 4) the blocks are chosen are large as possible to minimise the number of input and output requests. Parameters specifying the number and size of blocks are stored in COMMON/MATPAR/ (see Section III).

FBNGF also sets the locations in CM at which storage of B, C and D start. For example, CM(IC11) is passed from the main program to subroutines CMNGF and FACGF as the starting location of array C.

SYMBOL DICTIONARY

IB11 = location in CM at which storage of B starts

IC11 = location in CM at which storage of C starts

ID11 = location in CM at which storage of D starts

IMAT = number of complex numbers in A_F

IR = space available (complex numbers) in CM when A_F is not being used.

IRESRV = total length of CM

IRESX = space availabe in CM when A_F is being used

IX11 = location in CM at which storage of B starts when $A^{-1}B$ is computed (A_F occupies space in CM)

NBCD = number of complex numbers in B, C and D combined

NBLN = number of complex numbers in B or C

NDLN = length of D

NEQ = number of rows in B, columns in C

NEQ2 = number of columns in B or D, rows in C or D

```
      SUBROUTINE FBNGF (NEQ,NEQ2,IRESRV,IB11,IC11,ID11,IX11)                FN   1
C     FBNGF SETS THE BLOCKING PARAMETERS FOR THE B, C, AND D ARRAYS FOR     FN   2
C     OUT-OF-CORE STORAGE.                                                  FN   3
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I    FN   4
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                    FN   5
      IRESX=IRESRV-IMAT                                                     FN   6
      NBLN=NEQ*NEQ2                                                         FN   7
      NDLN=NEQ2*NEQ2                                                        FN   8
      NBCD=2*NBLN+NDLN                                                      FN   9
      IF (NBCD.GT.IRESX) GO TO 1                                            FN  10
      ICASX=1                                                               FN  11
      IB11=IMAT+1                                                           FN  12
      GO TO 2                                                               FN  13
1     IF (ICASE.LT.3) GO TO 3                                               FN  14
      IF (NBCD.GT.IRESRV.OR.NBLN.GT.IRESX) GO TO 3                          FN  15
      ICASX=2                                                               FN  16
      IB11=1                                                                FN  17
2     NBBX=1                                                                FN  18
      NPBX=NEQ                                                              FN  19
      NLBX=NEQ                                                              FN  20
      NBBL=1                                                                FN  21
      NPBL=NEQ2                                                             FN  22
      NLBL=NEQ2                                                             FN  23
      GO TO 5                                                               FN  24
3     IR=IRESRV                                                             FN  25
      IF (ICASE.LT.3) IR=IRESX                                              FN  26
      ICASX=3                                                               FN  27
      IF (NDLN.GT.IR) ICASX=4                                               FN  28
      NBCD=2*NEQ+NEQ2                                                       FN  29
      NPBL=IR/NBCD                                                          FN  30
      NLBL=IR/(2*NEQ2)                                                      FN  31
      IF (NLBL.LT.NPBL) NPBL=NLBL                                           FN  32
      IF (ICASE.LT.3) GO TO 4                                               FN  33
      NLBL=IRESX/NEQ                                                        FN  34
      IF (NLBL.LT.NPBL) NPBL=NLBL                                           FN  35
4     IF (NPBL.LT.1) GO TO 6                                                FN  36
      NBBL=(NEQ2-1)/NPBL                                                    FN  37
      NLBL=NEQ2-NBBL*NPBL                                                   FN  38
      NBBL=NBBL+1                                                           FN  39
      NBLN=NEQ*NPBL                                                         FN  40
      IR=IR-NBLN                                                            FN  41
      NPBX=IR/NEQ2                                                          FN  42
      IF (NPBX.GT.NEQ) NPBX=NEQ                                             FN  43
      NBBX=(NEQ-1)/NPBX                                                     FN  44
      NLBX=NEQ-NBBX*NPBX                                                    FN  45
      NBBX=NBBX+1                                                           FN  46
      IB11=1                                                                FN  47
      IF (ICASE.LT.3) IB11=IMAT+1                                           FN  48
5     IC11=IB11+NBLN                                                        FN  49
      ID11=IC11+NBLN                                                        FN  50
      IX11=IMAT+1                                                           FN  51
      PRINT 11, NEQ2                                                        FN  52
      IF (ICASX.EQ.1) RETURN                                                FN  53
      PRINT 8, ICASX                                                        FN  54
      PRINT 9, NBBX,NPBX,NLBX                                               FN  55
      PRINT 10, NBBL,NPBL,NLBL                                              FN  56
      RETURN                                                                FN  57
6     PRINT 7, IRESRV,IMAT,NEQ,NEQ2                                         FN  58
      STOP                                                                  FN  59
C                                                                           FN  60
7     FORMAT (55H ERROR - INSUFFICIENT STORAGE FOR INTERACTION MATRICIES    FN  61
     1,24H  IRESRV,IMAT,NEQ,NEQ2 =,4I5)                                     FN  62
8     FORMAT (48H FILE STORAGE FOR NEW MATRIX SECTIONS -  ICASX =,I2)       FN  63
9     FORMAT (19H B FILLED BY ROWS -,15X,12HNO. BLOCKS =,I3,3X,16HROWS P    FN  64
```

```
      1ER BLOCK =,I3,3X,20HROWS IN LAST BLOCK =,I3)                          FN  65
10     FORMAT (32H B BY COLUMNS, C AND D BY ROWS -,2X,12HNO. BLOCKS =,I3,     FN  66
     14X,15HR/C PER BLOCK =,I3,4X,19HR/C IN LAST BLOCK =,I3)                 FN  67
11     FORMAT (///,35H N.G.F. - NUMBER OF NEW UNKNOWNS IS,I4)                 FN  68
       END                                                                    FN  69-
```

FFLD

PURPOSE

To calculate the radiated electric field due to the currents on wires and surfaces in free space or over ground. The range factor $\exp(-jkr_0)/(r_0/\lambda)$ is omitted.

METHOD

Equation (126) of Part I is used to evaluate the radiated field of wires and surfaces. The surface part of the equation is evaluated in subroutine FFLDS, however. For wires, the field equation is

$$\bar{E}(\bar{r}_0) = \frac{j\eta \exp(-jkr_0)}{4\pi\, r_0/\lambda} (\hat{k}\hat{k} - \bar{\bar{I}}) \cdot \bar{F}(\bar{r}_0)$$

$$\bar{F}(\bar{r}_0) = 2\pi \int_L \exp(j\bar{k} \cdot \bar{r})\, [\bar{I}(s)/\lambda]\, ds/\lambda$$

where

$r_0 = |\bar{r}_0|$
$\hat{k} = \bar{r}_0/|\bar{r}_0|$
$k = 2\pi/\lambda$
$\bar{k} = k\hat{k}$
$\bar{I}(s)$ = current on the wire at s
$\bar{\bar{I}}$ = identity dyad
L = contour of the wire
$\bar{r}$ = position of the point at s on the wire

The dot product with the dyad $\hat{k}\hat{k} - \bar{\bar{I}}$ results in the component of $\bar{F}$ transverse to $\hat{k}$. This is accomplished in the code by computing the dot products with the unit vectors $\hat{\theta}$ and $\hat{\phi}$, normal to $\hat{k}$.

For a wire structure consisting of N straight segments, $\bar{r}$ on segment i is replaced by

$$\bar{r} = \bar{r}_i + \lambda t \hat{u}_i ,$$

where

$\bar{r}_i$ = location of the center of segment i
$\bar{u}_i$ = unit vector in the direction of segment i

Then, $\bar{F}$ is evaluated as

$$\bar{F}(\bar{r}_0) = \sum_{i=1}^{N} \exp(j\bar{k} \cdot \bar{r}_i)\ \bar{Q}_i$$

$$Q_i = 2\pi\hat{u}_i \int_{-\Delta_i/2}^{\Delta_i/2} \exp[j2\pi t(\hat{k} \cdot \hat{u}_i)]\ I_i(t)/\lambda\ dt$$

where Δ_i is the length of segment i normalized to λ. With

$$I_i(t)/\lambda = A_i + B_i \sin(2\pi t) + C_i \cos(2\pi t)\ ,$$

the integral can be evaluated as

$$\bar{Q}_i = \hat{u}_i \left\{ A_i \frac{2 \sin(\pi w_i \Delta_i)}{w_i} - jB_i \left[\frac{\sin[\pi(1 - w_i)\Delta_i]}{(1 - w_i)} - \frac{\sin[\pi(1 + w_i)\Delta_i]}{(1 + w_i)} \right] + C_i \left[\frac{\sin[\pi(1 - w_i)\Delta_i]}{(1 - w_i)} + \frac{\sin[\pi(1 + w_i)\Delta_i]}{(1 + w_i)} \right] \right\},$$

where $w_i = -\hat{k} \cdot \hat{u}_i$.

The effect of a ground is included by computing the field of the image of each segment and modifying it by the Fresnel reflection coefficients. The coding here differs from section II-4 of Part I in some respects. Rather than reflecting each segment in the ground plane, the direction of observation, $\hat{k}$, is reflected for the image calculation. Thus, the sign of the z component of $\hat{k}$ is changed at the start of the image calculation. The z component of the image field must also be changed in sign at the end of the calculation. Also, the change in sign of the image field due to the change in sign of charge on the image is combined with the reflection coefficients. Thus, the reflection coefficients are the negative of those in Part I.

The code allows for a change in ground height and electrical parameters at a fixed radial distance from the origin (circular cliff) or at a fixed distance in x (linear cliff). In these cases, the reflection point of the ray from the center of each segment is computed, and the reflection coefficients and phase lag are computed for the appropriate ground. Effects from the region of change, such as diffraction from the edge, are not included,

however. A radial wire ground screen may also be included by the reflection coefficient approximation described in section II-4 of Part I.

CODING

FF30 - FF164 Calculation of field due to segments.
FF34 - FF164 Loop over direct and image fields.
FF38 - FF63 Reflection coefficients computed.
FF64 $\hat{k}$ reflected in ground for image.
FF65 - FF70 Direct fields saved, and CIX, CIY, CIZ initialized before image calculation.
FF75 - FF96 Field of segment I computed.
FF102 - FF104 Summation of fields for direct field or uniform ground.
FF110 - FF149 Appropriate reflection coefficient determined and field summed for reflected field from two-medium ground or radial-wire ground screen.
FF156 - FF159 Image field multiplied by reflection coefficients for uniform ground and added to direct field.
FF161 - FF163 Reflected field added to direct field for two-medium ground or radial wire ground.
FF166 - FF167 Dot products of $\overline{F}$ with $\hat{\theta}$ and $\hat{\phi}$ for wires only.
FF169 - FF208 Calculation of field due to surface patches.
FF177 - FF203 Loop over direct and image fields.
FF179 $\hat{k}$ reflected for image.
FF180 FFLDS calculates field.
FF186 - FF202 Field multiplied by reflection coefficients for uniform ground only.

SYMBOL DICTIONARY

A = 2 sin $(\pi w_i \Delta_i)/w_i$ (a series is used for small w_i)
ARG = $\overline{k} \cdot \overline{r}_i$
B = coefficient of B_i in $\overline{Q}_i$
BOO = sin $[\pi(1 - w_i)\Delta_i]/[\pi(1 - w_i)\Delta_i]$
BOT = $\pi(1 - w_i)\Delta_i$
C = coefficient of C_i in $\overline{Q}_i$
CAB, SAB, SALP = x, y, z components of $\hat{u}_i$

CCX, CCY, CCZ = variables for summation of x, y, and z components of $\bar{F}$

CDP = $(\bar{F} \cdot \hat{\phi})(R_V - R_H)$

CIX, CIY, CIZ = variables for summation of x, y, and z components of $\bar{F}$

CONST = CONSX = $-j\eta/4\pi$

D = distance of ray reflection point from origin

DARG = phase increment due to change in ground level

EL = $\pi\Delta_i$

EPH = ϕ component of $(r_0/\lambda)\exp(jkr_0)\ \bar{E}(\bar{r}_0)$

ETH = θ component of $(r_0/\lambda)\exp(jkr_0)\ \bar{E}(\bar{r}_0)$

ETA = $\eta = \sqrt{\mu/\epsilon}$

EX, EY, EZ = $(r_0/\lambda)\exp(jkr_0)\ \bar{E}(\bar{r}_0)$ for patches

EXA = Q_i

GX, GY, GZ = $(r_0/\lambda)\exp(jkr_0)\ \bar{E}(\bar{r}_0)$ for direct and reflected fields of patches

I = segment number

OMEGA = w_i

PHI = ϕ

PHX, PHY = x and y components of $\hat{\phi}$

PI = π

RFL = ± 1 for direct or image field of patch

RI = imaginary part of Q_i

ROX, ROY, ROZ = x, y, and z components of $\hat{k}$

ROZS = saved value of ROZ

RR = real part of Q_i

RRH = $-R_H$

RRH1 = $-R_H$ for first ground medium

RRH2 = $-R_H$ for second ground medium

RRV = $-R_V$

RRV1 = $-R_V$ for first ground medium

RRV2 = $-R_V$ for second ground medium

RRZ = z component of $\hat{k}$

SILL = $\pi w_i \Delta_i$

THET = θ (angle from vertical to $\hat{k}$)

THX, THY, THZ = $\hat{\theta}$

TIX, TIY, TIZ = Q_i for image in ground

TOO = $\sin[\pi(1 + w_i)\Delta_i]/[\pi(1 + w_i)\Delta_i]$

TOP = $\pi(1 + w_i)\Delta_i$

TP = 2π

TTHET = $\tan \theta$

ZRATI = $[\varepsilon_r - j\sigma/(\omega\varepsilon_0)]^{-1/2}$ ε_r, σ = ground parameters

ZRSIN = $[1 - (ZRATI)^2 \sin^2 \theta]^{1/2}$

ZSCRN = surface impedance of ground with radial wire ground screen

CONSTANTS

-29.97922085 = $-j\eta/(4\pi)$

3.141592654 = π

376.73 = η

6.283185308 = 2π

```
      SUBROUTINE FFLD (THET,PHI,ETH,EPH)                                FF   1
C                                                                       FF   2
C     FFLD CALCULATES THE FAR ZONE RADIATED ELECTRIC FIELDS,            FF   3
C     THE FACTOR EXP(J*K*R)/(R/LAMDA) NOT INCLUDED                      FF   4
C                                                                       FF   5
      COMPLEX CIX,CIY,CIZ,EXA,ETH,EPH,CONST,CCX,CCY,CCZ,CDP,CUR         FF   6
      COMPLEX ZRATI,ZRSIN,RRV,RRH,RRV1,RRH1,RRV2,RRH2,ZRATI2,TIX,TIY,TIZ FF   7
     1,T1,ZSCRN,EX,EY,EZ,GX,GY,GZ,FRATI                                 FF   8
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 FF   9
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( FF  10
     2300),WLAM,IPSYM                                                   FF  11
      COMMON /ANGL/ SALP(300)                                           FF  12
      COMMON /CRNT/ AIR(300),AII(300),BIR(300),BII(300),CIR(300),CII(300 FF  13
     1),CUR(900)                                                        FF  14
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR, FF  15
     1IPERF,T1,T2                                                       FF  16
      DIMENSION CAB(1), SAB(1), CONSX(2)                                FF  17
      EQUIVALENCE (CAB,ALP), (SAB,BET), (CONST,CONSX)                   FF  18
      DATA PI,TP,ETA/3.141592654,6.283185308,376.73/                    FF  19
      DATA CONSX/0.,-29.97922085/                                       FF  20
      PHX=-SIN(PHI)                                                     FF  21
      PHY=COS(PHI)                                                      FF  22
      ROZ=COS(THET)                                                     FF  23
      ROZS=ROZ                                                          FF  24
      THX=ROZ*PHY                                                       FF  25
      THY=-ROZ*PHX                                                      FF  26
      THZ=-SIN(THET)                                                    FF  27
      ROX=-THZ*PHY                                                      FF  28
      ROY=THZ*PHX                                                       FF  29
      IF (N.EQ.0) GO TO 20                                              FF  30
C                                                                       FF  31
C     LOOP FOR STRUCTURE IMAGE IF ANY                                   FF  32
C                                                                       FF  33
      DO 19 K=1,KSYMP                                                   FF  34
C                                                                       FF  35
C     CALCULATION OF REFLECTION COEFFECIENTS                            FF  36
C                                                                       FF  37
      IF (K.EQ.1) GO TO 4                                               FF  38
      IF (IPERF.NE.1) GO TO 1                                           FF  39
C                                                                       FF  40
C     FOR PERFECT GROUND                                                FF  41
C                                                                       FF  42
      RRV=-(1.,0.)                                                      FF  43
      RRH=-(1.,0.)                                                      FF  44
      GO TO 2                                                           FF  45
C                                                                       FF  46
C     FOR INFINITE PLANAR GROUND                                        FF  47
C                                                                       FF  48
    1 ZRSIN=CSQRT(1.-ZRATI*ZRATI*THZ*THZ)                               FF  49
      RRV=-(ROZ-ZRATI*ZRSIN)/(ROZ+ZRATI*ZRSIN)                          FF  50
      RRH=(ZRATI*ROZ-ZRSIN)/(ZRATI*ROZ+ZRSIN)                           FF  51
    2 IF (IFAR.LE.1) GO TO 3                                            FF  52
C                                                                       FF  53
C     FOR THE CLIFF PROBLEM, TWO REFLCTION COEFFICIENTS CALCULATED      FF  54
C                                                                       FF  55
      RRV1=RRV                                                          FF  56
      RRH1=RRH                                                          FF  57
      TTHET=TAN(THET)                                                   FF  58
      IF (IFAR.EQ.4) GO TO 3                                            FF  59
      ZRSIN=CSQRT(1.-ZRATI2*ZRATI2*THZ*THZ)                             FF  60
      RRV2=-(ROZ-ZRATI2*ZRSIN)/(ROZ+ZRATI2*ZRSIN)                       FF  61
      RRH2=(ZRATI2*ROZ-ZRSIN)/(ZRATI2*ROZ+ZRSIN)                        FF  62
      DARG=-TP*2.*CH*ROZ                                                FF  63
    3 ROZ=-ROZ                                                          FF  64
```

```
      CCX=CIX                                                           FF  65
      CCY=CIY                                                           FF  66
      CCZ=CIZ                                                           FF  67
    4 CIX=(0.,0.)                                                       FF  68
      CIY=(0.,0.)                                                       FF  69
      CIZ=(0.,0.)                                                       FF  70
C                                                                       FF  71
C     LOOP OVER STRUCTURE SEGMENTS                                      FF  72
C                                                                       FF  73
      DO 17 I=1,N                                                       FF  74
      OMEGA=-(ROX*CAB(I)+ROY*SAB(I)+ROZ*SALP(I))                        FF  75
      EL=PI*SI(I)                                                       FF  76
      SILL=OMEGA*EL                                                     FF  77
      TOP=EL+SILL                                                       FF  78
      BOT=EL-SILL                                                       FF  79
      IF (ABS(OMEGA).LT.1.E-7) GO TO 5                                  FF  80
      A=2.*SIN(SILL)/OMEGA                                              FF  81
      GO TO 6                                                           FF  82
    5 A=(2.-OMEGA*OMEGA*EL*EL/3.)*EL                                    FF  83
    6 IF (ABS(TOP).LT.1.E-7) GO TO 7                                    FF  84
      TOO=SIN(TOP)/TOP                                                  FF  85
      GO TO 8                                                           FF  86
    7 TOO=1.-TOP*TOP/6.                                                 FF  87
    8 IF (ABS(BOT).LT.1.E-7) GO TO 9                                    FF  88
      BOO=SIN(BOT)/BOT                                                  FF  89
      GO TO 10                                                          FF  90
    9 BOO=1.-BOT*BOT/6.                                                 FF  91
   10 B=EL*(BOO-TOO)                                                    FF  92
      C=EL*(BOO+TOO)                                                    FF  93
      RR=A*AIR(I)+B*BII(I)+C*CIR(I)                                     FF  94
      RI=A*AII(I)-B*BIR(I)+C*CII(I)                                     FF  95
      ARG=TP*(X(I)*ROX+Y(I)*ROY+Z(I)*ROZ)                               FF  96
      IF (K.EQ.2.AND.IFAR.GE.2) GO TO 11                                FF  97
      EXA=CMPLX(COS(ARG),SIN(ARG))*CMPLX(RR,RI)                         FF  98
C                                                                       FF  99
C     SUMMATION FOR FAR FIELD INTEGRAL                                  FF 100
C                                                                       FF 101
      CIX=CIX+EXA*CAB(I)                                                FF 102
      CIY=CIY+EXA*SAB(I)                                                FF 103
      CIZ=CIZ+EXA*SALP(I)                                               FF 104
      GO TO 17                                                          FF 105
C                                                                       FF 106
C     CALCULATION OF IMAGE CONTRIBUTION IN CLIFF AND GROUND SCREEN      FF 107
C     PROBLEMS.                                                         FF 108
C                                                                       FF 109
   11 DR=Z(I)*TTHET                                                     FF 110
C                                                                       FF 111
C     SPECULAR POINT DISTANCE                                           FF 112
C                                                                       FF 113
      D=DR*PHY+X(I)                                                     FF 114
      IF (IFAR.EQ.2) GO TO 13                                           FF 115
      D=SQRT(D*D+(Y(I)-DR*PHX)**2)                                      FF 116
      IF (IFAR.EQ.3) GO TO 13                                           FF 117
      IF ((SCRWL-D).LT.0.) GO TO 12                                     FF 118
C                                                                       FF 119
C     RADIAL WIRE GROUND SCREEN REFLECTION COEFFICIENT                  FF 120
C                                                                       FF 121
      D=D+T2                                                            FF 122
      ZSCRN=T1*D*ALOG(D/T2)                                             FF 123
      ZSCRN=(ZSCRN*ZRATI)/(ETA*ZRATI+ZSCRN)                             FF 124
      ZRSIN=CSQRT(1.-ZSCRN*ZSCRN*THZ*THZ)                               FF 125
      RRV=(ROZ+ZSCRN*ZRSIN)/(-ROZ+ZSCRN*ZRSIN)                          FF 126
      RRH=(ZSCRN*ROZ+ZRSIN)/(ZSCRN*ROZ-ZRSIN)                           FF 127
      GO TO 16                                                          FF 128
```

```
129 12    IF (IFAR.EQ.4) GO TO 14                                          FF 129
130       IF (IFAR.EQ.5) D=DR*PHY+X(I)                                     FF 130
131 13    IF ((CL-D).LE.0.) GO TO 15                                       FF 131
132 14    RRV=RRV1                                                         FF 132
133       RRH=RRH1                                                         FF 133
134       GO TO 16                                                         FF 134
135 15    RRV=RRV2                                                         FF 135
136       RRH=RRH2                                                         FF 136
137       ARG=ARG+DARG                                                     FF 137
138 16    EXA=CMPLX(COS(ARG),SIN(ARG))*CMPLX(RR,RI)                        FF 138
139 C                                                                      FF 139
140 C     CONTRIBUTION OF EACH IMAGE SEGMENT MODIFIED BY REFLECTION COEF.  FF 140
141 C     FOR CLIFF AND GROUND SCREEN PROBLEMS                             FF 141
142 C                                                                      FF 142
143       TIX=EXA*CAB(I)                                                   FF 143
144       TIY=EXA*SAB(I)                                                   FF 144
145       TIZ=EXA*SALP(I)                                                  FF 145
146       CDP=(TIX*PHX+TIY*PHY)*(RRH-RRV)                                  FF 146
147       CIX=CIX+TIX*RRV+CDP*PHX                                          FF 147
148       CIY=CIY+TIY*RRV+CDP*PHY                                          FF 148
149       CIZ=CIZ-TIZ*RRV                                                  FF 149
150 17    CONTINUE                                                         FF 150
151       IF (K.EQ.1) GO TO 19                                             FF 151
152       IF (IFAR.GE.2) GO TO 18                                          FF 152
153 C                                                                      FF 153
154 C     CALCULATION OF CONTRIBUTION OF STRUCTURE IMAGE FOR INFINITE GROUND FF 154
155 C                                                                      FF 155
156       CDP=(CIX*PHX+CIY*PHY)*(RRH-RRV)                                  FF 156
157       CIX=CCX+CIX*RRV+CDP*PHX                                          FF 157
158       CIY=CCY+CIY*RRV+CDP*PHY                                          FF 158
159       CIZ=CCZ-CIZ*RRV                                                  FF 159
160       GO TO 19                                                         FF 160
161 18    CIX=CIX+CCX                                                      FF 161
162       CIY=CIY+CCY                                                      FF 162
163       CIZ=CIZ+CCZ                                                      FF 163
164 19    CONTINUE                                                         FF 164
165       IF (M.GT.0) GO TO 21                                             FF 165
166       ETH=(CIX*THX+CIY*THY+CIZ*THZ)*CONST                              FF 166
167       EPH=(CIX*PHX+CIY*PHY)*CONST                                      FF 167
168       RETURN                                                           FF 168
169 20    CIX=(0.,0.)                                                      FF 169
170       CIY=(0.,0.)                                                      FF 170
171       CIZ=(0.,0.)                                                      FF 171
172 21    ROZ=ROZS                                                         FF 172
173 C                                                                      FF 173
174 C     ELECTRIC FIELD COMPONENTS                                        FF 174
175 C                                                                      FF 175
176       RFL=-1.                                                          FF 176
177       DO 25 IP=1,KSYMP                                                 FF 177
178       RFL=-RFL                                                         FF 178
179       RRZ=ROZ*RFL                                                      FF 179
180       CALL FFLDS (ROX,ROY,RRZ,CUR(N+1),GX,GY,GZ)                       FF 180
181       IF (IP.EQ.2) GO TO 22                                            FF 181
182       EX=GX                                                            FF 182
183       EY=GY                                                            FF 183
184       EZ=GZ                                                            FF 184
185       GO TO 25                                                         FF 185
186 22    IF (IPERF.NE.1) GO TO 23                                         FF 186
187       GX=-GX                                                           FF 187
188       GY=-GY                                                           FF 188
189       GZ=-GZ                                                           FF 189
190       GO TO 24                                                         FF 190
191 23    RRV=CSQRT(1.-ZRATI*ZRATI*THZ*THZ)                                FF 191
192       RRH=ZRATI*ROZ                                                    FF 192
```

```
      RRH=(RRH-RRV)/(RRH+RRV)                                          FF 193
      RRV=ZRATI*RRV                                                    FF 194
      RRV=-(ROZ-RRV)/(ROZ+RRV)                                         FF 195
      ETH=(GX*PHX+GY*PHY)*(RRH-RRV)                                    FF 196
      GX=GX*RRV+ETH*PHX                                                FF 197
      GY=GY*RRV+ETH*PHY                                                FF 198
      GZ=GZ*RRV                                                        FF 199
   24 EX=EX+GX                                                         FF 200
      EY=EY+GY                                                         FF 201
      EZ=EZ-GZ                                                         FF 202
   25 CONTINUE                                                         FF 203
      EX=EX+CIX*CONST                                                  FF 204
      EY=EY+CIY*CONST                                                  FF 205
      EZ=EZ+CIZ*CONST                                                  FF 206
      ETH=EX*THX+EY*THY+EZ*THZ                                         FF 207
      EPH=EX*PHX+EY*PHY                                                FF 208
      RETURN                                                           FF 209
      END                                                              FF 210-
```

FFLDS

PURPOSE

To calculate the x, y, z components of the far electric field due to surface currents. The term $\exp(-jkr_0)/(r_0/\lambda)$ is omitted.

METHOD

The field is computed using the surface portion of equation (126) in Part I. With lengths normalized to the wavelength, the equation is

$$\bar{E}(\bar{r}_0) = \frac{jn}{2}\frac{\exp(-jkr_0)}{r_0/\lambda}(\hat{k}\hat{k} - \bar{\bar{I}}) \cdot \int_S \bar{J}_S(\bar{r})\exp(j\bar{k}\cdot\bar{r})\, dA/\lambda^2 ,$$

where

$r_0 = |\bar{r}_0|$
$\hat{k} = \bar{r}_0/|\bar{r}_0|$
$k = 2\pi/\lambda$
$\bar{k} = k\hat{k}$
$\bar{J}_S$ = surface current on surface S
$\bar{\bar{I}}$ = identity dyad

The dot product with the dyad $\hat{k}\hat{k} - \bar{\bar{I}}$ results in the component of the integral

$$\bar{F}(\bar{r}_0) = \int_S \bar{J}_S(\bar{r})\exp(j\bar{k}\cdot\bar{r})\, dA/\lambda^2$$

transverse to $\hat{k}$. The integral is evaluated by summation over the patches with the current assumed constant over each patch.

SYMBOL DICTIONARY

ARG = $\bar{k}\cdot\bar{r}_i$, $\bar{r}_i$ = center of patch I
CONS = CONSX = $jn/2$
CT = $\exp(j\bar{k}\cdot\bar{r}_i)\, dA/\lambda^2$ at FL18
= $\hat{k}\cdot\bar{F}(\bar{r}_0)$ at FL24
EX, EY, EZ = x, y, z components of $\bar{F}(\bar{r}_0)$ at FL22
= $(r_0/\lambda)\exp(jkr_0)\bar{E}(\bar{r}_0)$ at FL27
I = array location of patch data
J = patch number
K = current array index

ROX, ROY, ROZ = x, y, z components of $\hat{k}$

S(I) = (area of patch I)/λ^2

SCUR = array containing surface current components

TPI = 2π

XS, YS, ZS = arrays containing center point coordinates of patches normalized to wavelength.

CODE LISTING

```
      SUBROUTINE FFLDS (ROX,ROY,ROZ,SCUR,EX,EY,EZ)                      FL   1
C     CALCULATES THE XYZ COMPONENTS OF THE ELECTRIC FIELD DUE TO        FL   2
C     SURFACE CURRENTS                                                  FL   3
      COMPLEX CT,CONS,SCUR,EX,EY,EZ                                     FL   4
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 FL   5
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( FL   6
     2300),WLAM,IPSYM                                                   FL   7
      DIMENSION XS(1), YS(1), ZS(1), S(1), SCUR(1), CONSX(2)            FL   8
      EQUIVALENCE (XS,X), (YS,Y), (ZS,Z), (S,BI), (CONS,CONSX)          FL   9
      DATA TPI/6.283185308/,CONSX/0.,188.365/                           FL  10
      EX=(0.,0.)                                                        FL  11
      EY=(0.,0.)                                                        FL  12
      EZ=(0.,0.)                                                        FL  13
      I=LD+1                                                            FL  14
      DO 1 J=1,M                                                        FL  15
      I=I-1                                                             FL  16
      ARG=TPI*(ROX*XS(I)+ROY*YS(I)+ROZ*ZS(I))                           FL  17
      CT=CMPLX(COS(ARG)*S(I),SIN(ARG)*S(I))                             FL  18
      K=3*J                                                             FL  19
      EX=EX+SCUR(K-2)*CT                                                FL  20
      EY=EY+SCUR(K-1)*CT                                                FL  21
      EZ=EZ+SCUR(K)*CT                                                  FL  22
1     CONTINUE                                                          FL  23
      CT=ROX*EX+ROY*EY+ROZ*EZ                                           FL  24
      EX=CONS*(CT*ROX-EX)                                               FL  25
      EY=CONS*(CT*ROY-EY)                                               FL  26
      EZ=CONS*(CT*ROZ-EZ)                                               FL  27
      RETURN                                                            FL  28
      END                                                               FL  29-
```


GF

PURPOSE

To supply values of the integrated function exp(jkr)/(kr) to the numerical integration routine INTX.

METHOD

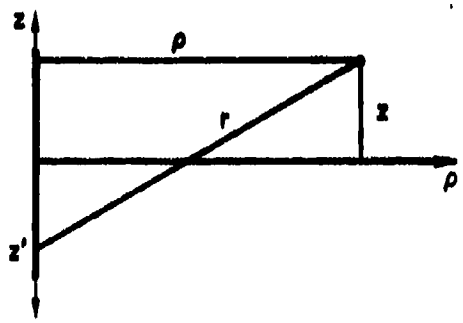The geometry parameters for integration over a segment are shown in the following diagram.



in which

$$r(z') = [\rho^2 + (z' - z)^2]^{1/2} .$$

If the field point (ρ,z) is not on the source segment, the integrand value is

$$G(z') = \frac{\exp[jkr(z')]}{kr(z')} .$$

If the field point is on the source segment (ρ = 0, z = 0), the integrand value is

$$G(z') = \frac{\exp[jkr(z')] - 1}{kr(z')} .$$

In the latter case, if kr is less than 0.2, then (cos kr)/kr is evaluated by the first three terms of its Taylor's series to reduce numerical error.

SYMBOL DICTIONARY

CO = real part of G(z')
COS = external function (cosine)
IJ = flag to indicate when field point is on source segment (by IJ = 0)
RK = kr

RKB2 = $(k\rho)^2$

SI = imaginary part of G(z')

SIN = external function (sine)

SQRT = external function (square root)

ZDK = kz' - kz

ZK = kz'

ZPK = kz

CONSTANTS

-1.38888889E-3
4.16666667E-2
0.5

} = constants in series for (cos kr - 1)/kr

CODE LISTING

```
      SUBROUTINE GF (ZK,CO,SI)                                          GF   1
C                                                                       GF   2
C     GF COMPUTES THE INTEGRAND EXP(JKR)/(KR) FOR NUMERICAL INTEGRATION. GF   3
C                                                                       GF   4
      COMMON /TMI/ ZPK,RKB2,IJ                                          GF   5
      ZDK=ZK-ZPK                                                        GF   6
      RK=SQRT(RKB2+ZDK*ZDK)                                             GF   7
      SI=SIN(RK)/RK                                                     GF   8
      IF (IJ) 1,2,1                                                     GF   9
1     CO=COS(RK)/RK                                                     GF  10
      RETURN                                                            GF  11
2     IF (RK.LT..2) GO TO 3                                             GF  12
      CO=(COS(RK)-1.)/RK                                                GF  13
      RETURN                                                            GF  14
3     RKS=RK*RK                                                         GF  15
      CO=((-1.38888889E-3*RKS+4.16666667E-2)*RKS-.5)*RK                 GF  16
      RETURN                                                            GF  17
      END                                                               GF  18
```

GFIL

PURPOSE

To read the NGF file and store parameters in the proper arrays.

METHOD

GI22	Miscellaneous parameters are read.
GI30 - GI48	Segment coordinates were converted to the form involving the segment center, segment length, and orientation (see Section III, COMMON/DATA/) with dimensions of wavelength. They must be converted back to the coordinates of the segment ends so that subroutine CONNECT can locate connections. Dimensions are converted to meters.
GI52 - GI62	Patch coordinates are converted from units of wavelength to meters since they will be scaled back to wavelengths along with the new segments and patches.
GI63	Matrix blocking parameters are read.
GI64	Interpolation tables for the Sommerfeld integrals are read if the Sommerfeld/Norton ground treatment was used.
GI74	Matrix A_F is read for in-core storage (ICASE = 1 or 2).
GI78 - GI81	A_F is read for ICASE = 4.
GI83 - GI88	A_F is read for ICASE = 3 or 5.
GI92 - GI113	A heading summarizing the NGF file is printed.

SYMBOL DICTIONARY

DX	= half segment length (meters)
IGFL	= file number for NGF file
IOUT	= number of elements in matrix
IPRT	= 1 to print coordinates of ends of segments
NBL2	= two times number of blocks in matrix A_F (since A_F is stored twice, in ascending and descending order)
NEQ	= order of the NGF matrix
NOP	= number of symmetric sections
NPEQ	= number of unknowns for a symmetric section
XI, YI, ZI	= coordinates of the center of a segment or patch

GFIL

```
      SUBROUTINE GFIL (IPRT)                                                GI   1
C                                                                           GI   2
C     GFIL READS THE N.G.F. FILE                                            GI   3
C                                                                           GI   4
      COMPLEX CM,SSX,ZRATI,ZRATI2,T1,ZARRAY,AR1,AR2,AR3,EPSCF,FRATI         GI   5
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300    GI   6
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX(    GI   7
     2300),WLAM,IPSYM                                                       GI   8
      COMMON /CMB/ CM(4000)                                                 GI   9
      COMMON /ANGL/ SALP(300)                                               GI  10
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR,    GI  11
     1IPERF,T1,T2                                                           GI  12
      COMMON /GGRID/ AR1(11,10,4),AR2(17,8,4),AR3(9,8,4),EPSCF,DXA(3),DY    GI  13
     1A(3),XSA(3),YSA(3),NXA(3),NYA(3)                                      GI  14
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I    GI  15
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                    GI  16
      COMMON /SMAT/ SSX(16,16)                                              GI  17
      COMMON /ZLOAD/ ZARRAY(300),NLOAD,NLODF                                GI  18
      COMMON /SAVE/ IP(600),KCOM,COM(13,5),EPSR,SIG,SCRWLT,SCRWRT,FMHZ      GI  19
      DATA IGFL/20/                                                         GI  20
      REWIND IGFL                                                           GI  21
      READ (IGFL) N1,NP,M1,MP,WLAM,FMHZ,IPSYM,KSYMP,IPERF,NRADL,EPSR,SIG    GI  22
     1,SCRWLT,SCRWRT,NLODF,KCOM                                             GI  23
      N=N1                                                                  GI  24
      M=M1                                                                  GI  25
      N2=N1+1                                                               GI  26
      M2=M1+1                                                               GI  27
      IF (N1.EQ.0) GO TO 2                                                  GI  28
C     READ SEG. DATA AND CONVERT BACK TO END COORD. IN UNITS OF METERS      GI  29
      READ (IGFL) (X(I),I=1,N1),(Y(I),I=1,N1),(Z(I),I=1,N1)                 GI  30
      READ (IGFL) (SI(I),I=1,N1),(BI(I),I=1,N1),(ALP(I),I=1,N1)             GI  31
      READ (IGFL) (BET(I),I=1,N1),(SALP(I),I=1,N1)                          GI  32
      READ (IGFL) (ICON1(I),I=1,N1),(ICON2(I),I=1,N1)                       GI  33
      READ (IGFL) (ITAG(I),I=1,N1)                                          GI  34
      IF (NLODF.NE.0) READ (IGFL) (ZARRAY(I),I=1,N1)                        GI  35
      DO 1 I=1,N1                                                           GI  36
      XI=X(I)*WLAM                                                          GI  37
      YI=Y(I)*WLAM                                                          GI  38
      ZI=Z(I)*WLAM                                                          GI  39
      DX=SI(I)*.5*WLAM                                                      GI  40
      X(I)=XI-ALP(I)*DX                                                     GI  41
      Y(I)=YI-BET(I)*DX                                                     GI  42
      Z(I)=ZI-SALP(I)*DX                                                    GI  43
      SI(I)=XI+ALP(I)*DX                                                    GI  44
      ALP(I)=YI+BET(I)*DX                                                   GI  45
      BET(I)=ZI+SALP(I)*DX                                                  GI  46
      BI(I)=BI(I)*WLAM                                                      GI  47
1     CONTINUE                                                              GI  48
2     IF (M1.EQ.0) GO TO 4                                                  GI  49
      J=LD-M1+1                                                             GI  50
C     READ PATCH DATA AND CONVERT TO METERS                                 GI  51
      READ (IGFL) (X(I),I=J,LD),(Y(I),I=J,LD),(Z(I),I=J,LD)                 GI  52
      READ (IGFL) (SI(I),I=J,LD),(BI(I),I=J,LD),(ALP(I),I=J,LD)             GI  53
      READ (IGFL) (BET(I),I=J,LD),(SALP(I),I=J,LD)                          GI  54
      READ (IGFL) (ICON1(I),I=J,LD),(ICON2(I),I=J,LD)                       GI  55
      READ (IGFL) (ITAG(I),I=J,LD)                                          GI  56
      DX=WLAM*WLAM                                                          GI  57
      DO 3 I=J,LD                                                           GI  58
      X(I)=X(I)*WLAM                                                        GI  59
      Y(I)=Y(I)*WLAM                                                        GI  60
      Z(I)=Z(I)*WLAM                                                        GI  61
3     BI(I)=BI(I)*DX                                                        GI  62
4     READ (IGFL) ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT          GI  63
      IF (IPERF.EQ.2) READ (IGFL) AR1,AR2,AR3,EPSCF,DXA,DYA,XSA,YSA,NXA,    GI  64
```

```
      1NYA                                                              GI  65
       NEQ=N1+2*M1                                                      GI  66
       NPEQ=NP+2*MP                                                     GI  67
       NOP=NEQ/NPEQ                                                     GI  68
       IF (NOP.GT.1) READ (IGFL) ((SSX(I,J),I=1,NOP),J=1,NOP)           GI  69
       READ (IGFL) (IP(I),I=1,NEQ),COM                                  GI  70
C      READ MATRIX A AND WRITE TAPE13 FOR OUT OF CORE                   GI  71
       IF (ICASE.GT.2) GO TO 5                                          GI  72
       IOUT=NEQ*NPEQ                                                    GI  73
       READ (IGFL) (CM(I),I=1,IOUT)                                     GI  74
       GO TO 10                                                         GI  75
5      REWIND 13                                                        GI  76
       IF (ICASE.NE.4) GO TO 7                                          GI  77
       IOUT=NPEQ*NPEQ                                                   GI  78
       DO 6 K=1,NOP                                                     GI  79
       READ (IGFL) (CM(J),J=1,IOUT)                                     GI  80
6      WRITE (13) (CM(J),J=1,IOUT)                                      GI  81
       GO TO 9                                                          GI  82
7      IOUT=NPSYM*NPEQ*2                                                GI  83
       NBL2=2*NBLSYM                                                    GI  84
       DO 8 IOP=1,NOP                                                   GI  85
       DO 8 I=1,NBL2                                                    GI  86
       CALL BLCKIN (CM,IGFL,1,IOUT,1,206)                               GI  87
8      CALL BLCKOT (CM,13,1,IOUT,1,205)                                 GI  88
9      REWIND 13                                                        GI  89
10     REWIND IGFL                                                      GI  90
C      PRINT N.G.F. HEADING                                             GI  91
       PRINT 16                                                         GI  92
       PRINT 14                                                         GI  93
       PRINT 14                                                         GI  94
       PRINT 17                                                         GI  95
       PRINT 18, N1,M1                                                  GI  96
       IF (NOP.GT.1) PRINT 19, NOP                                      GI  97
       PRINT 20, IMAT,ICASE                                             GI  98
       IF (ICASE.LT.3) GO TO 11                                         GI  99
       NBL2=NEQ*NPEQ                                                    GI 100
       PRINT 21, NBL2                                                   GI 101
11     PRINT 22, FMHZ                                                   GI 102
       IF (KSYMP.EQ.2.AND.IPERF.EQ.1) PRINT 23                          GI 103
       IF (KSYMP.EQ.2.AND.IPERF.EQ.0) PRINT 27                          GI 104
       IF (KSYMP.EQ.2.AND.IPERF.EQ.2) PRINT 28                          GI 105
       IF (KSYMP.EQ.2.AND.IPERF.NE.1) PRINT 24, EPSR,SIG                GI 106
       PRINT 17                                                         GI 107
       DO 12 J=1,KCOM                                                   GI 108
12     PRINT 15, (COM(I,J),I=1,13)                                      GI 109
       PRINT 17                                                         GI 110
       PRINT 14                                                         GI 111
       PRINT 14                                                         GI 112
       PRINT 16                                                         GI 113
       IF (IPRT.EQ.0) RETURN                                            GI 114
       PRINT 25                                                         GI 115
       DO 13 I=1,N1                                                     GI 116
13     PRINT 26, I,X(I),Y(I),Z(I),SI(I),ALP(I),BET(I)                   GI 117
       RETURN                                                           GI 118
C                                                                       GI 119
14     FORMAT (5X,50H**********************************************,3 GI 120
      14H**********************************)                          GI 121
15     FORMAT (5X,3H** ,13A6,3H **)                                     GI 122
16     FORMAT (////)                                                    GI 123
17     FORMAT (5X,2H**,80X,2H**)                                        GI 124
18     FORMAT (5X,29H** NUMERICAL GREEN'S FUNCTION,53X,2H**,/,5X,17H** NO GI 125
      1. SEGMENTS =,I4,10X,13HNO. PATCHES =,I4,34X,2H**)                GI 126
19     FORMAT (5X,27H** NO. SYMMETRIC SECTIONS =,I4,51X,2H**)           GI 127
20     FORMAT (5X,34H** N.G.F. MATRIX -  CORE STORAGE =,I7,23H COMPLEX NU GI 128
```

GFIL

```
      1MBERS,  CASE,I2,16X,2H**)                                          GI 129
   21  FORMAT (5X,2H**,19X,13HMATRIX SIZE =,I7,16H COMPLEX NUMBERS,25X,2H GI 130
     1**)                                                                 GI 131
   22  FORMAT (5X,14H** FREQUENCY =,E12.5,5H MHZ.,51X,2H**)               GI 132
   23  FORMAT (5X,17H** PERFECT GROUND,65X,2H**)                          GI 133
   24  FORMAT (5X,44H** GROUND PARAMETERS - DIELECTRIC CONSTANT =,E12.5,2 GI 134
     16X,2H**,/,5X,2H**,21X,14HCONDUCTIVITY =,E12.5,6H MHOS/M.,28X,2H**) GI 135
   25  FORMAT (39X,31HNUMERICAL GREEN'S FUNCTION DATA,/,41X,27HCOORDINATE GI 136
     1S OF SEGMENT ENDS,/,51X,8H(METERS),/,5X,4HSEG.,11X,19H- - - END ON GI 137
     2E - - -,26X,19H- - - END TWO - - -,/,6X,3HNO.,6X,1HX,14X,1HY,14X,1 GI 138
     3HZ,14X,1HX,14X,1HY,14X,1HZ)                                         GI 139
   26  FORMAT (1X,I7,6E15.6)                                              GI 140
   27  FORMAT (5X,55H** FINITE GROUND.  REFLECTION COEFFICIENT APPROXIMAT GI 141
     1ION,27X,2H**)                                                       GI 142
   28  FORMAT (5X,38H** FINITE GROUND.  SOMMERFELD SOLUTION,44X,2H**)     GI 143
       END                                                                GI 144-
```

GFLD

PURPOSE

To compute the electric field at intermediate distances from a radiating structure over ground, including the surface-wave field component.

METHOD

Approximate expressions for the field of a horizontal or vertical current element over a ground plane were derived by K. A. Norton (ref. 2). These expressions are used to evaluate the field of each segment in a structure and the components summed for the total field of the structure. To evaluate Norton's expressions for segment i, a local coordinate system (x', y', z') is defined (fig. 6a) with origin on the ground plane and the vertical z axis passing through segment i. In the (x, y, z) coordinate system (fig. 6 b) the location and orientation of segment i are

$$\bar{r}_i = x_i\hat{x} + y_i\hat{y} + z_i\hat{z}$$

$$\hat{i} = \cos\alpha\cos\beta\,\hat{x} + \cos\alpha\sin\beta\,\hat{y} + \sin\alpha\,\hat{z}$$

and the field observation point is at (ρ, ϕ, z). The origin of the primed coordinate system is at $(x_i, y_i, 0)$ in the unprimed coordinates, and the x' axis is along the projection of the segment on the ground plane.


Norton's expressions give the electric field in ρ', ϕ', and z' components for infinitesimal current elements either vertical or horizontal, and directed along the x' axis. To evaluate the field of a segment, the segment current is decomposed into horizontal and vertical components, and the fields of the infinitesimal current elements are integrated over the segment. Each field component for the infinitesimal current element has the form

$$E_\Delta(\rho', \phi', z') = F_1(\rho', \phi', z')\exp(-jkR_1) + F_2(\rho', \phi', z')\exp(-jkR_2)\ ,$$


for

$$R_1 = |\bar{R}_1|$$

$$R_2 = |\bar{R}_2|$$

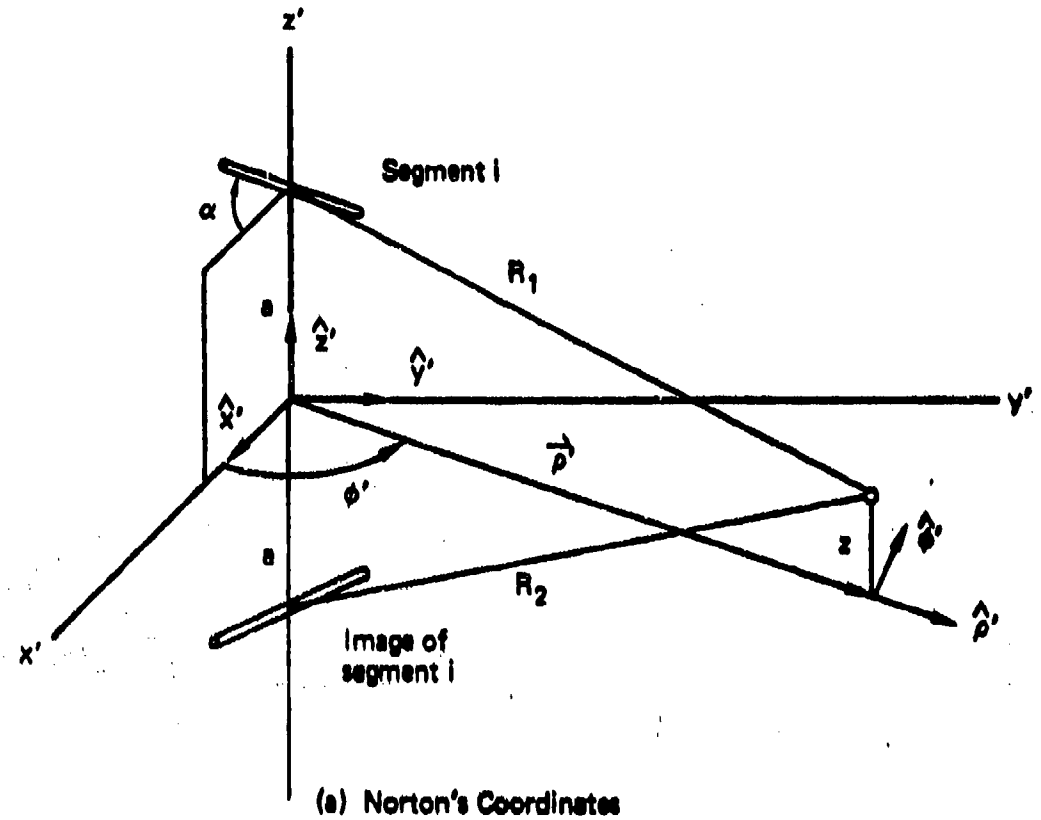

(a) Norton's Coordinates

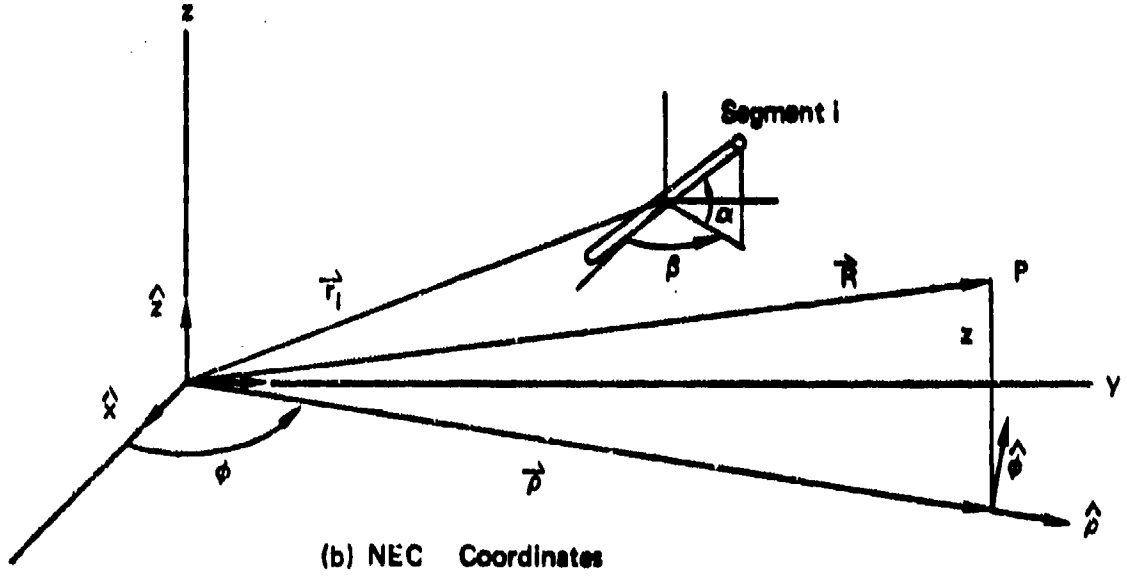

(b) NEC Coordinates

Figure 6. Coordinate Systems Used to Evaluate Norton's Expressions for the Ground Wave Fields in the NEC Program.

where F_1 and F_2 are algebraic functions of R_1 and R_2 and can be considered constant for integration over the segment as long as R_1 and R_2 are much greater than the segment length. To integrate the exponential factors over the segment, R_1 and R_2 are approximated as

$$R_1 \approx R - \hat{R}_1 \cdot (\bar{r}_i + \hat{i}s)$$

$$R_2 \approx R - \hat{R}_2 \cdot (\bar{r}_i' + \hat{i}'s)$$

where $R = |\bar{R}|$, $\hat{R}_1 = \bar{R}_1/|\bar{R}_1|$, $\hat{R}_2 = \bar{R}_2/|\bar{R}_2|$; $\bar{r}_i'$, $\hat{i}'$ = position and orientation of image of segment i, and s = variable of length along the segment (s = 0 at segment center). The current on the segment is

$$I_i(s) = A_i + B_i \sin ks + C_i \cos ks .$$

With F_1 and F_2 considered constant, each vector component of the field produced by segment i involves an integral of the form

$$E = F_1' \int_{-\Delta/2\lambda}^{\Delta/2\lambda} \frac{I_i(s)}{\lambda} \exp(-jks\omega)\, d\frac{s}{\lambda} + F_2' \int_{-\Delta/2\lambda}^{\Delta/2\lambda} \frac{I_i(s)}{\lambda} \exp(-jks\omega')\, d(s/\lambda)$$

where

$$F_1' = \lambda^2 F_1 \exp[-jk(R - \hat{R}_1 \cdot \bar{r}_i)]$$

$$F_2' = \lambda^2 F_2 \exp[-jk(R - \hat{R}_2 \cdot \bar{r}_i')]$$

$$\omega = -\hat{R}_1 \cdot \hat{i}$$

$$\omega' = -\hat{R}_2 \cdot \hat{i}'$$

$$\Delta = \text{segment length}$$

The integrals can be evaluated as

$$G_1 = \int_{-\Delta/2\lambda}^{\Delta/2\lambda} \frac{I_i(s)}{\lambda} \exp(-j2\pi\, \omega\, s/\lambda)\, d\frac{s}{\lambda}$$

$$2\pi G_1 = \frac{A_i}{\lambda} \frac{2 \sin \pi \omega d}{\omega}$$

$$- j \frac{B_i}{\lambda} \left| \frac{\sin [\pi (1 - \omega)d]}{(1 - \omega)} - \frac{\sin [\pi (1 + \omega)d]}{(1 + \omega)} \right|$$

$$+ \frac{C_i}{\lambda} \left| \frac{\sin [\pi (1 - \omega)d]}{(1 - \omega)} + \frac{\sin [\pi (1 + \omega)d]}{(1 + \omega)} \right|$$

where $d = \Delta/\lambda$. The integral for G_2 (the coefficient of F_2') is the same with $\vec{r}_i$ and $\hat{i}$ reflected in the ground plane. The terms G_1 and G_2 and other necessary quantities are passed to subroutine GWAVE through COMMON/GWAV/. GWAVE returns the field components

E_ρ^v = ρ' component of field due to vertical current component

E_z^v = z component of field due to vertical current component

E_ρ^h = ρ' component of field due to horizontal current component

E_ϕ^h = ϕ' component of field due to horizontal current component

E_z^h = z component of field due to horizontal current component

The common factor exp(-jkR) occurring in F_1' and F_2' is omitted from the field components and included in the total field after summation.

These field components are then combined to form the total field in x, y, z components and summed for each segment. The field is finally converted to r, θ, ϕ components in a spherical coordinate system coinciding with the x, y, z coordinate system.

The approximations involved in the calculation of the surface wave are valid to second order in u^2, where

$u = k/k_2$

k = wave number in free space

k_2 = wave number in ground medium

The approximations are valid for practical ground parameters. To ensure that the expressions are not used in an invalid range, however, the surface wave is not computed if $|u|$ is greater than 0.5. Rather, subroutine FFLD is called, and the resulting space wave is multiplied by the range factor exp(-jkR)/(R/λ). The radial field component will be zero in this case. FFLD is also called if R/λ is greater than 10^5, or if there is no ground present.

SYMBOL DICTIONARY

A = coefficient of A_i/λ in $2\pi C_1$ and $2\pi G_2$

ABS = external routine (absolute value)

ARG = argument of exp( ) for phase factor

ATAN = external routine (arctangent)

B = coefficient of B_i/λ in $2\pi G_1$ and $2\pi G_2$

BOO = sin (BOT)/BOT

BOT = $\pi(1 - \omega)d$

C = coefficient of C_i/λ in $2\pi G_1$ and $2\pi G_2$

CAB(I) = cos α cos β for segment I

CABS = external routine (magnitude of complex number)

CALP = cos α

CBET = cos β

CIX, CIY, CIZ = x, y, z components in summation for field

CMPLX = external routine (forms complex number)

COS = external routine (cosine)

CPH = cos ϕ'

DX, DY, DZ = x, y, z components of $\hat{i}$

EL = πd

EPH = E_ϕ^h or E_ϕ^h cos α (ϕ' component of total field of segment i)

EPI = ϕ component of field of structure

ERD = R component of field of structure

ERH = E_ρ^h and ρ' component of total field of segment i

ERV = E_ρ^v

ETH = θ component of field of structure

EX = x component of field for segment i

EXA = phase factor at GD30 and GD130:

$G_1 \exp(jk\hat{R}_1 \cdot \bar{r}_i)$ or $G_2 \exp(jk\hat{R}_2 \cdot \bar{r}_i')$ at GD109

EY = y component of field for segment i

EZH = E_z^h and z component of total field of segment i

EZV = E_z^ϕ

FFLD = external routine (computes space wave)
GWAVE = external routine (computes E_ρ^v, E_ρ^h, ...)
I = DO loop index (i)
K = DO loop index (loop over segment and image)
KSYMP = 1 if ground is present; 0 otherwise
OMEGA = ω
PHI = ϕ
PHX = x component of $\hat{\phi}$
PHY = y component of $\hat{\phi}$
PI = π
R = R/λ
RFL = sign factor to reflect segment coordinates in ground
RHO = ρ/λ
RHP = ρ'/λ
RHS = $(\rho'/\lambda)^2$
RHX = x component of $\hat{\rho}'$
RHY = y component of $\hat{\rho}'$
RI = imaginary part of $2\pi G_1$ or $2\pi G_2$
RIX = x component of $\bar{R}_1/\lambda$ or $\bar{R}_2/\lambda$
RIY = y component of $\bar{R}_1/\lambda$ or $\bar{R}_2/\lambda$
RIZ = z component of $\bar{R}_1/\lambda$ or $\bar{R}_2/\lambda$
RNX, RNY, RNZ = x, y, z components of $\hat{R}_1$ or $\hat{R}_2$ or $\hat{R}$
RR = real part of $2\pi G_1$ or $2\pi G_2$
RX = x component of $\bar{\rho}/\lambda$
RXYZ = R_1/λ or R_2/λ (for s = 0)
RY = y component of $\bar{\rho}/\lambda$
RZ = z/λ
SAB(I) = cos α sin β
SBET = sin β
SILL = $\pi d\omega$
SIN = external routine (sine)
SPH = sin ϕ'

SQRT = external routine (square root)
THET = θ in spherical coordinate system
THX = x component of $\hat{\theta}$
THY = y component of $\hat{\theta}$
THZ = z component of $\hat{\theta}$
TOO = sin (TOP)/TOP
TOP = $\pi(1 + \omega)d$
TP = 2π
U = u
UX = u
U2 = u^2
XX1 = $G_1 \exp(jk\hat{R}_1 \cdot \bar{r}_i)$
XX2 = $G_2 \exp(jk\hat{R}_2 \cdot \bar{r}_i')$

CONSTANTS

1.E-20 = tolerance in test for zero
1.E-7 = tolerance in test for zero
1.E-6 = tolerance in test for zero
0.5 = upper limit for |u|
3.141592654 = π
6.283185308 = 2π
1.E+3 = upper limit for R/λ

```
      SUBROUTINE GFLD (RHO,PHI,RZ,ETH,EPI,ERD,UX,KSYMP)                  GD   1
C                                                                        GD   2
C     GFLD COMPUTES THE RADIATED FIELD INCLUDING GROUND WAVE.            GD   3
C                                                                        GD   4
      COMPLEX CUR,EPI,CIX,CIY,CIZ,EXA,XX1,XX2,U,U2,ERV,EZV,ERH,EPH       GD   5
      COMPLEX EZH,EX,EY,ETH,UX,ERD                                       GD   6
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 GD   7
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( GD   8
     2300),WLAM,IPSYM                                                    GD   9
      COMMON /ANGL/ SALP(300)                                            GD  10
      COMMON /CRNT/ AIR(300),AII(300),BIR(300),BII(300),CIR(300),CII(300 GD  11
     1),CUR(900)                                                         GD  12
      COMMON /GWAV/ U,U2,XX1,XX2,R1,R2,ZMH,ZPH                           GD  13
      DIMENSION CAB(1), SAB(1)                                           GD  14
      EQUIVALENCE (CAB(1),ALP(1)), (SAB(1),BET(1))                       GD  15
      DATA PI,TP/3.141592654,6.283185308/                                GD  16
      R=SQRT(RHO*RHO+RZ*RZ)                                              GD  17
      IF (KSYMP.EQ.1) GO TO 1                                            GD  18
      IF (CABS(UX).GT..5) GO TO 1                                        GD  19
      IF (R.GT.1.E5) GO TO 1                                             GD  20
      GO TO 4                                                            GD  21
C                                                                        GD  22
C     COMPUTATION OF SPACE WAVE ONLY                                     GD  23
C                                                                        GD  24
1     IF (RZ.LT.1.E-20) GO TO 2                                          GD  25
      THET=ATAN(RHO/RZ)                                                  GD  26
      GO TO 3                                                            GD  27
2     THET=PI*.5                                                         GD  28
3     CALL FFLD (THET,PHI,ETH,EPI)                                       GD  29
      ARG=-TP*R                                                          GD  30
      EXA=CMPLX(COS(ARG),SIN(ARG))/R                                     GD  31
      ETH=ETH*EXA                                                        GD  32
      EPI=EPI*EXA                                                        GD  33
      ERD=(0.,0.)                                                        GD  34
      RETURN                                                             GD  35
C                                                                        GD  36
C     COMPUTATION OF SPACE AND GROUND WAVES.                             GD  37
C                                                                        GD  38
4     U=UX                                                               GD  39
      U2=U*U                                                             GD  40
      PHX=-SIN(PHI)                                                      GD  41
      PHY=COS(PHI)                                                       GD  42
      RX=RHO*PHY                                                         GD  43
      RY=-RHO*PHX                                                        GD  44
      CIX=(0.,0.)                                                        GD  45
      CIY=(0.,0.)                                                        GD  46
      CIZ=(0.,0.)                                                        GD  47
C                                                                        GD  48
C     SUMMATION OF FIELD FROM INDIVIDUAL SEGMENTS                        GD  49
C                                                                        GD  50
      DO 17 I=1,N                                                        GD  51
      DX=CAB(I)                                                          GD  52
      DY=SAB(I)                                                          GD  53
      DZ=SALP(I)                                                         GD  54
      RIX=RX-X(I)                                                        GD  55
      RIY=RY-Y(I)                                                        GD  56
      RHS=RIX*RIX+RIY*RIY                                                GD  57
      RHP=SQRT(RHS)                                                      GD  58
      IF (RHP.LT.1.E-6) GO TO 5                                          GD  59
      RHX=RIX/RHP                                                        GD  60
      RHY=RIY/RHP                                                        GD  61
      GO TO 6                                                            GD  62
5     RHX=1.                                                             GD  63
      RHY=0.                                                             GD  64
```

```
 65 6      CALP=1.-DZ*DZ                                                    GD  65
 66        IF (CALP.LT.1.E-6) GO TO 7                                       GD  66
 67        CALP=SQRT(CALP)                                                  GD  67
 68        CBET=DX/CALP                                                     GD  68
 69        SBET=DY/CALP                                                     GD  69
 70        CPH=RHX*CBET+RHY*SBET                                            GD  70
 71        SPH=RHY*CBET-RHX*SBET                                            GD  71
 72        GO TO 8                                                          GD  72
 73 7      CPH=RHX                                                          GD  73
 74        SPH=RHY                                                          GD  74
 75 8      EL=PI*SI(I)                                                      GD  75
 76        RFL=-1.                                                          GD  76
 77 C                                                                       GD  77
 78 C      INTEGRATION OF (CURRENT)*(PHASE FACTOR) OVER SEGMENT AND IMAGE FOR GD  78
 79 C      CONSTANT, SINE, AND COSINE CURRENT DISTRIBUTIONS                 GD  79
 80 C                                                                       GD  80
 81        DO 16 K=1,2                                                      GD  81
 82        RFL=-RFL                                                         GD  82
 83        RIZ=RZ-Z(I)*RFL                                                  GD  83
 84        RXYZ=SQRT(RIX*RIX+RIY*RIY+RIZ*RIZ)                               GD  84
 85        RNX=RIX/RXYZ                                                     GD  85
 86        RNY=RIY/RXYZ                                                     GD  86
 87        RNZ=RIZ/RXYZ                                                     GD  87
 88        OMEGA=-(RNX*DX+RNY*DY+RNZ*DZ*RFL)                                GD  88
 89        SILL=OMEGA*EL                                                    GD  89
 90        TOP=EL+SILL                                                      GD  90
 91        BOT=EL-SILL                                                      GD  91
 92        IF (ABS(OMEGA).LT.1.E-7) GO TO 9                                 GD  92
 93        A=2.*SIN(SILL)/OMEGA                                             GD  93
 94        GO TO 10                                                         GD  94
 95 9      A=(2.-OMEGA*OMEGA*EL*EL/3.)*EL                                   GD  95
 96 10     IF (ABS(TOP).LT.1.E-7) GO TO 11                                  GD  96
 97        TOO=SIN(TOP)/TOP                                                 GD  97
 98        GO TO 12                                                         GD  98
 99 11     TOO=1.-TOP*TOP/6.                                                GD  99
100 12     IF (ABS(BOT).LT.1.E-7) GO TO 13                                  GD 100
101        BOO=SIN(BOT)/BOT                                                 GD 101
102        GO TO 14                                                         GD 102
103 13     BOO=1.-BOT*BOT/6.                                                GD 103
104 14     B=EL*(BOO-TOO)                                                   GD 104
105        C=EL*(BOO+TOO)                                                   GD 105
106        RR=A*AIR(I)+B*BII(I)+C*CIR(I)                                    GD 106
107        RI=A*AII(I)-B*BIR(I)+C*CII(I)                                    GD 107
108        ARG=TP*(X(I)*RNX+Y(I)*RNY+Z(I)*RNZ*RFL)                          GD 108
109        EXA=CMPLX(COS(ARG),SIN(ARG))*CMPLX(RR,RI)/TP                     GD 109
110        IF (K.EQ.2) GO TO 15                                             GD 110
111        XX1=EXA                                                          GD 111
112        R1=RXYZ                                                          GD 112
113        ZMH=RIZ                                                          GD 113
114        GO TO 16                                                         GD 114
115 15     XX2=EXA                                                          GD 115
116        R2=RXYZ                                                          GD 116
117        ZPH=RIZ                                                          GD 117
118 16     CONTINUE                                                         GD 118
119 C                                                                       GD 119
120 C      CALL SUBROUTINE TO COMPUTE THE FIELD OF SEGMENT INCLUDING GROUND GD 120
121 C      WAVE.                                                            GD 121
122 C                                                                       GD 122
123        CALL GWAVE (ERV,EZV,ERH,EZH,EPH)                                 GD 123
124        ERH=ERH*CPH*CALP+ERV*DZ                                          GD 124
125        EPH=EPH*SPH*CALP                                                 GD 125
126        EZH=EZH*CPH*CALP+EZV*DZ                                          GD 126
127        EX=ERH*RHX-EPH*RHY                                               GD 127
128        EY=ERH*RHY+EPH*RHX                                               GD 128
```

```
      CIX=CIX+EX                                                        GD 129
      CIY=CIY+EY                                                        GD 130
   17 CIZ=CIZ+EZH                                                       GD 131
      ARG=-TP*R                                                         GD 132
      EXA=CMPLX(COS(ARG),SIN(ARG))                                      GD 133
      CIX=CIX*EXA                                                       GD 134
      CIY=CIY*EXA                                                       GD 135
      CIZ=CIZ*EXA                                                       GD 136
      RNX=RX/R                                                          GD 137
      RNY=RY/R                                                          GD 138
      RNZ=RZ/R                                                          GD 139
      THX=RNZ*PHY                                                       GD 140
      THY=-RNZ*PHX                                                      GD 141
      THZ=-RHO/R                                                        GD 142
      ETH=CIX*THX+CIY*THY+CIZ*THZ                                       GD 143
      EPI=CIX*PHX+CIY*PHY                                               GD 144
      ERD=CIX*RNX+CIY*RNY+CIZ*RNZ                                       GD 145
      RETURN                                                            GD 146
      END                                                               GD 147-
```

GFOUT

PURPOSE

To write the NGF file.

METHOD

The contents of the COMMON blocks in GFOUT are written to file 20. If ICASE is 3 or 5 the blocks of the LU decomposition of matrix A are on file 13 in ascending order and on file 14 in descending order. Both files are written to file 20.

SYMBOL DICTIONARY

ICFL = NGF file number
IOUT = number of elements in matrix
NEQ = order of matrix A
NOP = number of symmetric sections
NPEQ = number of unknowns for a symmetric section

```
      SUBROUTINE GFOUT                                                  GO   1
C                                                                       GO   2
C     WRITE N.G.F. FILE                                                 GO   3
C                                                                       GO   4
      COMPLEX CM,SSX,ZRATI,ZRATI2,T1,ZARRAY,AR1,AR2,AR3,EPSCF,FRATI     GO   5
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 GO   6
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( GO   7
     2300),WLAM,IPSYM                                                   GO   8
      COMMON /CMB/ CM(4000)                                             GO   9
      COMMON /ANGL/ SALP(300)                                           GO  10
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR, GO  11
     1IPERF,T1,T2                                                       GO  12
      COMMON /GGRID/ AR1(11,10,4),AR2(17,6,4),AR3(9,8,4),EPSCF,DXA(3),DY GO  13
     1A(3),XSA(3),YSA(3),NXA(3),NYA(3)                                  GO  14
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I GO  15
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                GO  16
      COMMON /SMAT/ SSX(16,16)                                          GO  17
      COMMON /ZLOAD/ ZARRAY(300),NLOAD,NLODF                            GO  18
      COMMON /SAVE/ IP(600),KCOM,COM(13,5),EPSR,SIG,SCRWLT,SCRWRT,FMHZ  GO  19
      DATA IGFL/20/                                                     GO  20
      NEQ=N+2*M                                                         GO  21
      NPEQ=NP+2*MP                                                      GO  22
      NOP=NEQ/NPEQ                                                      GO  23
      WRITE (IGFL) N,NP,M,MP,WLAM,FMHZ,IPSYM,KSYMP,IPERF,NRADL,EPSR,SIG, GO  24
     1SCRWLT,SCRWRT,NLOAD,KCOM                                          GO  25
      IF (N.EQ.0) GO TO 1                                               GO  26
      WRITE (IGFL) (X(I),I=1,N),(Y(I),I=1,N),(Z(I),I=1,N)               GO  27
      WRITE (IGFL) (SI(I),I=1,N),(BI(I),I=1,N),(ALP(I),I=1,N)           GO  28
      WRITE (IGFL) (BET(I),I=1,N),(SALP(I),I=1,N)                       GO  29
      WRITE (IGFL) (ICON1(I),I=1,N),(ICON2(I),I=1,N)                    GO  30
      WRITE (IGFL) (ITAG(I),I=1,N)                                      GO  31
      IF (NLOAD.GT.0) WRITE (IGFL) (ZARRAY(I),I=1,N)                    GO  32
1     IF (M.EQ.0) GO TO 2                                               GO  33
      J=LD-M+1                                                          GO  34
      WRITE (IGFL) (X(I),I=J,LD),(Y(I),I=J,LD),(Z(I),I=J,LD)            GO  35
      WRITE (IGFL) (SI(I),I=J,LD),(BI(I),I=J,LD),(ALP(I),I=J,LD)        GO  36
      WRITE (IGFL) (BET(I),I=J,LD),(SALP(I),I=J,LD)                     GO  37
      WRITE (IGFL) (ICON1(I),I=J,LD),(ICON2(I),I=J,LD)                  GO  38
      WRITE (IGFL) (ITAG(I),I=J,LD)                                     GO  39
2     WRITE (IGFL) ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT     GO  40
      IF (IPERF.EQ.2) WRITE (IGFL) AR1,AR2,AR3,EPSCF,DXA,DYA,XSA,YSA,NXA GO  41
     1,NYA                                                              GO  42
      IF (NOP.GT.1) WRITE (IGFL) ((SSX(I,J),I=1,NOP),J=1,NOP)           GO  43
      WRITE (IGFL) (IP(I),I=1,NEQ),COM                                  GO  44
      IF (ICASE.GT.2) GO TO 3                                           GO  45
      IOUT=NEQ*NPEQ                                                     GO  46
      WRITE (IGFL) (CM(I),I=1,IOUT)                                     GO  47
      GO TO 12                                                          GO  48
3     IF (ICASE.NE.4) GO TO 5                                           GO  49
      REWIND 13                                                         GO  50
      I=NPEQ*NPEQ                                                       GO  51
      DO 4 K=1,NOP                                                      GO  52
      READ (13) (CM(J),J=1,I)                                           GO  53
4     WRITE (IGFL) (CM(J),J=1,I)                                        GO  54
      REWIND 13                                                         GO  55
      GO TO 12                                                          GO  56
5     REWIND 13                                                         GO  57
      REWIND 14                                                         GO  58
      IF (ICASE.EQ.5) GO TO 8                                           GO  59
      IOUT=NPBLK*NEQ*2                                                  GO  60
      DO 6 I=1,NBLOKS                                                   GO  61
      CALL BLCKIN (CM,13,1,IOUT,1,201)                                  GO  62
6     CALL BLCKOT (CM,IGFL,1,IOUT,1,202)                                GO  63
      DO 7 I=1,NBLOKS                                                   GO  64
```

```
      CALL BLCKIN (CM,14,1,IOUT,1,203)                                  GO  65
    7 CALL BLCKOT (CM,IGFL,1,IOUT,1,204)                                GO  66
      GO TO 12                                                          GO  67
    8 IOUT=NPSYM*NPEQ*2                                                 GO  68
      DO 11 IOP=1,NOP                                                   GO  69
      DO 9 I=1,NBLSYM                                                   GO  70
      CALL BLCKIN (CM,13,1,IOUT,1,205)                                  GO  71
    9 CALL BLCKOT (CM,IGFL,1,IOUT,1,206)                                GO  72
      DO 10 I=1,NBLSYM                                                  GO  73
      CALL BLCKIN (CM,14,1,IOUT,1,207)                                  GO  74
   10 CALL BLCKOT (CM,IGFL,1,IOUT,1,208)                                GO  75
   11 CONTINUE                                                          GO  76
      REWIND 13                                                         GO  77
      REWIND 14                                                         GO  78
   12 REWIND IGFL                                                       GO  79
      PRINT 13, IGFL,IMAT                                               GO  80
      RETURN                                                            GO  81
    C                                                                   GO  82
   13 FORMAT (///,44H ****NUMERICAL GREEN'S FUNCTION FILE ON TAPE,I3,8H  GO  83
     1****,/,8X,16HMATRIX STORAGE -,I7,16H COMPLEX NUMBERS,///)         GO  84
      END                                                               GO  85-
```

GH

PURPOSE

To compute the function that is numerically integrated for the near H field of a segment.

METHOD

The value returned by GH is

$$G = \left[\frac{1}{(kr)^3} + \frac{j}{(kr)^2}\right] \exp(-jkr) ,$$

where

$r = \left[\rho'^2 + (z - z')^2\right]^{1/2}$

ρ' = ρ coordinate of the field observation point in a cylindrical coordinate system with origin at the center of the source segment and z axis oriented along the source segment

z' = z coordinate of the field observation point in the cylindrical coordinate system

z = z coordinate of the integration point on the source segment

$k = 2\pi/\lambda$

SYMBOL DICTIONARY

CKR = cos kr

HR = real part of G

HI = imaginary part of G

R = kr

RHKS = $(k\rho')^2$

RR2 = $1/(kr)^2$

RR3 = $1/(kr)^3$

RS = $(kr)^2$

SKR = sin kr

ZK = kz

ZPK = kz'

```
      SUBROUTINE GH (ZK,HR,HI)                                          GH    1
C     INTEGRAND FOR H FIELD OF A WIRE                                   GH    2
      COMMON /TMH/ ZPK,RHKS                                             GH    3
      RS=ZK-ZPK                                                         GH    4
      RS=RHKS+RS*RS                                                     GH    5
      R=SQRT(RS)                                                        GH    6
      CKR=COS(R)                                                        GH    7
      SKR=SIN(R)                                                        GH    8
      RR2=1./RS                                                         GH    9
      RR3=RR2/R                                                         GH   10
      HR=SKR*RR2+CKR*RR3                                                GH   11
      HI=CKR*RR2-SKR*RR3                                                GH   12
      RETURN                                                            GH   13
      END                                                               GH   14
```

GWAVE

PURPOSE

To compute the components of electric field due to an electric current element over a ground plane at intermediate distances, including the surface wave field.

METHOD

Approximate expressions for the electric field of a vertical or horizontal infinitesimal current element above a ground plane, including surface wave, were derived by K. A. Norton (ref. 2). The geometry is shown in figure 6a for a current element at height a above the ground plane and field observation point at p. The current element is located on the z' axis, and the horizontal current element is directed along the x' axis. The vertical current element produces z' and ρ' field components given by

$$E_z^v = -\frac{j\eta I d\ell}{2\lambda}\left\{\cos^2\psi' \frac{\exp(-jkR_1)}{R_1} + R_v \cos^2\psi \frac{\exp(-jkR_2)}{R_2}\right.$$

$$+ (1 - R_v)\cos^2\psi \; F \frac{\exp(-jkR_2)}{R_2}$$

$$+ u\sqrt{1 - u^2\cos^2\psi}\,\sin\psi\; 2\frac{\exp(-jkR_2)}{jkR_2^2}$$

$$+ \frac{\exp(-jkR_1)}{R_1}\left(\frac{1}{jkR_1} + \frac{1}{(jkR_1)^2}\right)(1 - 3\sin^2\psi')$$

$$\left. + \frac{\exp(-jkR_2)}{R_2}\left(\frac{1}{jkR_2} + \frac{1}{(jkR_2)^2}\right)(1 - 3\sin^2\psi)\right\},$$

$$E_\rho^v = \frac{j\eta I d\ell}{2\lambda} \left\{ \sin\psi' \cos\psi' \frac{\exp(-jkR_1)}{R_1} + R_v \sin\psi \cos\psi \frac{\exp(-jkR_2)}{R_2} \right.$$

$$- \cos\psi(1 - R_v)\, u \sqrt{1 - u^2 \cos^2\psi}\, F \frac{\exp(-jkR_2)}{R_2}$$

$$- \sin\psi \cos\psi\, (1 - R_v) \frac{\exp(-jkR_2)}{jkR_2^2}$$

$$+ 3 \sin\psi' \cos\psi' \left(\frac{1}{jkR_1} + \frac{1}{(jkR_1)^2} \right) \frac{\exp(-jkR_1)}{R_1}$$

$$- \cos\psi\, u \sqrt{1 - u^2 \cos^2\psi}\, (1 - R_v) \frac{\exp(-jkR_2)}{2jkR_2^2}$$

$$\left. + 3 \sin\psi \cos\psi \left(\frac{1}{jkR_2} + \frac{1}{(jkR_2)^2} \right) \frac{\exp(-jkR_2)}{R_2} \right\},$$

where

$F = 1 - j\sqrt{\pi w}\, \exp(-w)\, \mathrm{erfc}(j\sqrt{w})$

$\mathrm{erfc}(z) = 1 - \mathrm{erf}(z)$

$\mathrm{erf}(z) = 2/\sqrt{\pi} \int_0^z \exp(-t^2)\, dt$ (error function)

$w = 4p_1/(1 - R_v)^2$

$p_1 = -jkR_2 u^2 (1 - u^2 \cos^2\psi)/(2\cos^2\psi)$

$R_v = \dfrac{\sin\psi - u\sqrt{1 - u^2\cos^2\psi}}{\sin\psi + u\sqrt{1 - u^2\cos^2\psi}}$

$u = k/k_2$

k = wave number in free space

k_2 = wave number in lower medium

$\sin\psi = (z + a)/R_2$

$\sin\psi' = (z - a)/R_1$

The horizontal current element directed along the x' axis produces ρ', φ', and z' field components given by

$$E_z^h = \frac{j\eta I d\ell}{2\lambda} \cos\phi' \left\{ \sin\psi' \cos\psi' \frac{\exp(-jkR_1)}{R_1} \right.$$

$$- R_v \sin\psi \cos\psi \cdot \frac{\exp(-jkR_2)}{R_2}$$

$$+ \cos\psi (1 - R_v)\, u\sqrt{1 - u^2\cos^2\psi}\, F \frac{\exp(-jkR_2)}{R_2}$$

$$+ \sin\psi \cos\psi (1 - R_v) \frac{\exp(-jkR_2)}{jkR_2^2}$$

$$+ 3 \sin\psi' \cos\psi' \left(\frac{1}{jkR_1} + \frac{1}{(jkR_1)^2}\right) \frac{\exp(-jkR_1)}{R_1}$$

$$+ \cos\psi (1 - R_v)\, u\sqrt{1 - u^2\cos^2\psi} \frac{\exp(-jkR_2)}{2jkR_2^2}$$

$$\left. - 3 \sin\psi \cos\psi \left(\frac{1}{jkR_2} + \frac{1}{(jkR_2)^2}\right) \frac{\exp(-jkR_2)}{R_2} \right\},$$

$$E_\rho^h = \frac{-j\eta I d\ell}{2\lambda} \cos\phi' \left\{ \sin^2\psi' \frac{\exp(-jkR_1)}{R_1} - R_v \sin^2\psi \frac{\exp(-jkR_2)}{R_2} \right.$$

$$- (1 - u^2\cos^2\psi)\, u^2\, (1 - R_v)\, F \frac{\exp(-jkR_2)}{R_2}$$

$$+ \left(\frac{1}{jkR_1} + \frac{1}{(jkR_1)^2}\right) (1 - 3\cos^2\psi') \frac{\exp(-jkR_1)}{R_1}$$

$$- \left(\frac{1}{jkR_2} + \frac{1}{(jkR_2)^2}\right) (1 - 3\cos^2\psi) \left[1 - u^2\,(1 + R_v) - u^2(1 - R_v)F\right]$$

$$\times \frac{\exp(-jkR_2)}{R_2} + u^2\cos^2\psi\,(1 - R_v)\left(1 + \frac{1}{jkR_2}\right)$$

$$\left. \times \left[F\left(u^2(1 - u^2\cos^2\psi) - \sin^2\psi + \frac{1}{jkR_2}\right) - \frac{1}{jkR_2}\right] \frac{\exp(-jkR_2)}{R_2} \right\},$$

$$E_\phi^h = \frac{j\eta I d\ell}{2\lambda} \sin\phi' \left\{ \frac{\exp(-jkR_1)}{R_1} - R_h \frac{\exp(-jkR_2)}{R_2} \right.$$

$$+ (R_h + 1)\, G \frac{\exp(-jkR_2)}{R_2} + \left(1 + \frac{1}{jkR_1}\right) \frac{\exp(-jkR_1)}{jkR_1^2}$$

$$- \left(1 + \frac{1}{jkR_2}\right)[1 - u^2\,(1 + R_v) - u^2\,(1 - R_v)F] \frac{\exp(-jkR_2)}{jkR_2^2}$$

$$- \frac{u^2(1 - R_v)}{2} \left[F\left(u^2\,(1 - u^2\cos^2\psi) - \sin^2\psi + \frac{1}{jkR_2}\right) - \frac{1}{jkR_2}\right]$$

$$\left. \times \frac{\exp(-jkR_2)}{jkR_2^2} \right\},$$

where

$$G = [1 - j\sqrt{\pi v}\,\exp(-v)\,\mathrm{erfc}\,(j\sqrt{v})],$$

$$v = 4q_1/(1 + R_h)^2$$

$$q_1 = -jkR_2\,(1 - u^2\cos^2\psi)/(2u^2\cos^2\psi)$$

$$R_h = \frac{\sqrt{1 - u^2\cos^2\psi} - u\sin\psi}{\sqrt{1 - u^2\cos^2\psi} + u\sin\psi}$$

The approximations in these expressions are valid for R_1 and R_2 greater than about a wavelength and to second order in u^2. In each equation, the first term represents the direct space wave field of the current element, the second term is the space wave field reflected from the ground, and the following higher order terms involving F and G represent the ground wave. It may be noted that the coefficients R_v and R_h are the Fresnel reflection coefficients for vertical and horizontal polarization, respectively.

To obtain the field due to a structure, these expressions are integrated over each segment and the fields of the segments are summed in subroutine GFLD. For integration, R_1 and R_2 are the distances from the integration point ℓ on the segment to point p. Since R_1 and R_2 are assumed large compared to the segment length, R_1, R_2, ψ, and ψ' are considered constant during integration over the segment except where jkR_1 and jkR_2 occur in exponential functions. Thus, if s represents distance along the segment, the integral of each expression over the segment is obtained by replacing $(Id\ell/\lambda^2)\exp(-jkR_1)$ and $(Id\ell/\lambda^2)\exp(-jkR_2)$ by XX1 and XX2 from subroutine GFLD. A factor of $\exp(-jkR)$ is omitted from the fields and is included after summation in GFLD. Including a factor of $1/\lambda^2$ in XX1 and XX2 makes a factor of λ available to normalize R_1 and R_2 in the denominators of the field expressions. The factors $\sin\phi'$ or $\cos\phi'$ are omitted from the fields due to a horizontal current element in GWAVE and are supplied later.

SYMBOL DICTIONARY

CPP = $\cos \psi$

CPPP = $\cos \psi'$

CPPP2 = $\cos^2 \psi'$

CPP2 = $\cos^2 \psi$

ECON = $-j\eta/2$ (η = impedance of free space)

EPH = $E_\phi^h / \sin \phi'$

ERH = $E_\rho^h / \cos \phi'$

ERV = E_ρ^v

EZH = $E_z^h / \cos \phi'$

EZV = E_z^v

F = F

FJ = $j = \sqrt{-1}$

G = G

OMR = $1 - R_v$

PI = π

P1 = p_1

Q1 = q_1

RH = R_h

RK1 = $-jkR_1$

RK2 = $-jkR_2$

RV = R_v

R1 = R_1/λ

R2 = R_2/λ

SPP = $\sin \psi$

SPPP = $\sin \psi'$

SPPP2 = $\sin^2 \psi'$

SPP2 = $\sin^2 \psi$

TPJ = $2\pi j$

T1 = $1 - u^2 \cos^2 \psi$

T2 = $\sqrt{T1}$

T3 = $-[1/(jkR_1) + 1/(jkR_1)^2]$

GWAVE

T4 = $-[1/(jkR_2) + 1/(jkR_2)^2]$

U = u

U2 = u^2

V = v

W = w

XR1 = XX1/(R/λ)

XR2 = XX2/(R/λ)

XX1 = $G_1 \exp(jk\hat{R}_1 \cdot \bar{r}_i)$

XX2 = $G_2 \exp(jk\hat{R}_2 \cdot \bar{r}_i')$

X1, X2, X3, X4, X5, X6, X7 = first, second, ..., seventh term in each field expression

ZMH = z - a

ZPH = z + a

CONSTANTS

(0., 1.) = $j = \sqrt{-1}$

(0., 6.2831853) = $2\pi j$

(0., -188.363) = $-j\eta/2$

3.1415926 = π

```
      SUBROUTINE GWAVE (ERV,EZV,ERH,EZH,EPH)                            GW   1
C                                                                       GW   2
C     GWAVE COMPUTES THE ELECTRIC FIELD, INCLUDING GROUND WAVE, OF A    GW   3
C     CURRENT ELEMENT OVER A GROUND PLANE USING FORMULAS OF K.A. NORTON  GW   4
C     (PROC. IRE, SEPT., 1937, PP.1203,1236.)                           GW   5
C                                                                       GW   6
      COMPLEX FJ,TPJ,U2,U,RK1,RK2,T1,T2,T3,T4,P1,RV,OMR,W,F,Q1,RH,V,G,XR GW   7
     11,XR2,X1,X2,X3,X4,X5,X6,X7,EZV,ERV,EZH,ERH,EPH,XX1,XX2,ECON,FBAR  GW   8
      COMMON /GWAV/ U,U2,XX1,XX2,R1,R2,ZMH,ZPH                          GW   9
      DIMENSION FJX(2), TPJX(2), ECONX(2)                               GW  10
      EQUIVALENCE (FJ,FJX), (TPJ,TPJX), (ECON,ECONX)                    GW  11
      DATA PI/3.141592654/,FJX/0.,1./,TPJX/0.,6.283185308/              GW  12
      DATA ECONX/0.,-188.367/                                           GW  13
      SPPP=ZMH/R1                                                       GW  14
      SPPP2=SPPP*SPPP                                                   GW  15
      CPPP2=1.-SPPP2                                                    GW  16
      IF (CPPP2.LT.1.E-20) CPPP2=1.E-20                                 GW  17
      CPPP=SQRT(CPPP2)                                                  GW  18
      SPP=ZPH/R2                                                        GW  19
      SPP2=SPP*SPP                                                      GW  20
      CPP2=1.-SPP2                                                      GW  21
      IF (CPP2.LT.1.E-20) CPP2=1.E-20                                   GW  22
      CPP=SQRT(CPP2)                                                    GW  23
      RK1=-TPJ*R1                                                       GW  24
      RK2=-TPJ*R2                                                       GW  25
      T1=1.-U2*CPP2                                                     GW  26
      T2=CSQRT(T1)                                                      GW  27
      T3=(1.-1./RK1)/RK1                                                GW  28
      T4=(1.-1./RK2)/RK2                                                GW  29
      P1=RK2*U2*T1/(2.*CPP2)                                            GW  30
      RV=(SPP-U*T2)/(SPP+U*T2)                                          GW  31
      OMR=1.-RV                                                         GW  32
      W=1./OMR                                                          GW  33
      W=(4.,0.)*P1*W*W                                                  GW  34
      F=FBAR(W)                                                         GW  35
      Q1=RK2*T1/(2.*U2*CPP2)                                            GW  36
      RH=(T2-U*SPP)/(T2+U*SPP)                                          GW  37
      V=1./(1.+RH)                                                      GW  38
      V=(4.,0.)*Q1*V*V                                                  GW  39
      G=FBAR(V)                                                         GW  40
      XR1=XX1/R1                                                        GW  41
      XR2=XX2/R2                                                        GW  42
      X1=CPPP2*XR1                                                      GW  43
      X2=RV*CPP2*XR2                                                    GW  44
      X3=OMR*CPP2*F*XR2                                                 GW  45
      X4=U*T2*SPP*2.*XR2/RK2                                            GW  46
      X5=XR1*T3*(1.-3.*SPPP2)                                           GW  47
      X6=XR2*T4*(1.-3.*SPP2)                                            GW  48
      EZV=(X1+X2+X3-X4-X5-X6)*ECON                                      GW  49
      X1=SPPP*CPPP*XR1                                                  GW  50
      X2=RV*SPP*CPP*XR2                                                 GW  51
      X3=CPP*OMR*U*T2*F*XR2                                             GW  52
      X4=SPP*CPP*OMR*XR2/RK2                                            GW  53
      X5=3.*SPPP*CPPP*T3*XR1                                            GW  54
      X6=CPP*U*T2*OMR*XR2/RK2*.5                                        GW  55
      X7=3.*SPP*CPP*T4*XR2                                              GW  56
      ERV=-(X1+X2-X3+X4-X5+X6-X7)*ECON                                  GW  57
      EZH=-(X1-X2+X3-X4-X5-X6+X7)*ECON                                  GW  58
      X1=SPPP2*XR1                                                      GW  59
      X2=RV*SPP2*XR2                                                    GW  60
      X4=U2*T1*OMR*F*XR2                                                GW  61
      X5=T3*(1.-3.*CPPP2)*XR1                                           GW  62
      X6=T4*(1.-3.*CPP2)*(1.-U2*(1.+RV)-U2*OMR*F)*XR2                   GW  63
      X7=U2*CPP2*OMR*(1.-1./RK2)*(F*(U2*T1-SPP2-1./RK2)+1./RK2)*XR2     GW  64
```

```
      ERH=(X1-X2-X4-X5+X6+X7)*ECON                                      GW  65
      X1=XR1                                                            GW  66
      X2=RH*XR2                                                         GW  67
      X3=(RH+1.)*G*XR2                                                  GW  68
      X4=T3*XR1                                                         GW  69
      X5=T4*(1.-U2*(1.+RV)-U2*OMR*F)*XR2                                GW  70
      X6=.5*U2*OMR*(F*(U2*T1-SPP2-1./RK2)+1./RK2)*XR2/RK2               GW  71
      EPH=-(X1-X2+X3-X4+X5+X6)*ECON                                     GW  72
      RETURN                                                            GW  73
      END                                                               GW  74-
```

GX

PURPOSE

To evaluate terms for the field contribution due to segment ends in the thin wire kernel.

SYMBOL DICTIONARY

GZ = $\exp(-jkr)/r = G_0$

GZP = $-(1 + jkr)\exp(-jkr)/r^3$

R = r

R2 = $r^2 = \rho^2 + z^2$

RH = ρ

RK = kR

XK = $2\pi/\lambda$

ZZ = z

CODE LISTING

```
      SUBROUTINE GX (ZZ,RH,XK,GZ,GZP)                                   GX   1
C     SEGMENT END CONTRIBUTIONS FOR THIN WIRE APPROX.                   GX   2
      COMPLEX GZ,GZP                                                    GX   3
      R2=ZZ*ZZ+RH*RH                                                    GX   4
      R=SQRT(R2)                                                        GX   5
      RK=XK*R                                                           GX   6
      GZ=CMPLX(COS(RK),-SIN(RK))/R                                      GX   7
      GZP=-CMPLX(1.,RK)*GZ/R2                                           GX   8
      RETURN                                                            GX   9
      END                                                               GX  10-
```

GXX

PURPOSE

To evaluate terms for the field contribution due to segment ends in the extended thin wire kernel.

METHOD

Equations 89 through 94 in Part I are evaluated for $\rho > a$, and equations 99 through 103 for $\rho < a$. Several variables are used for storage of intermediate results before being set to their final values.

SYMBOL DICTIONARY

A = radius of source segment, a
A2 = a^2
C1 = $1 + jkr_0$
C2 = $3(1 + jkr_0) - k^2r_0^2$
C3 = $(6 + jkr_0)k^2r_0^2 - 15(1 + jkr_0)$
G1 = G_1
G1P = $\partial G_1/\partial z'$
G2 = G_2
G2P = $\partial G_2/\partial z'$
G3 = $\partial G_1/\partial \rho$
GZ = G_0
GZP = $\partial G_0/\partial z'$
IRA = 1 to indicate $\rho < a$
R = r_0
R2 = r_0^2
R4 = r_0^4
RH = ρ
RH2 = ρ^2
RK = kr_0
RK2 = $k^2r_0^2$
T1 = $a^2\rho^2/4r^4$
T2 = $a^2/2r^2$
XK = $k = 2\pi/\lambda$
ZZ = $z' - z$

```
      SUBROUTINE GXX (ZZ,RH,A,A2,XK,IRA,G1,G1P,G2,G2P,G3,GZP)                GY   1
C     SEGMENT END CONTRIBUTIONS FOR EXT. THIN WIRE APPROX.                  GY   2
      COMPLEX GZ,C1,C2,C3,G1,G1P,G2,G2P,G3,GZP                              GY   3
      R2=ZZ*ZZ+RH*RH                                                        GY   4
      R=SQRT(R2)                                                            GY   5
      R4=R2**2                                                              GY   6
      RK=XK*R                                                               GY   7
      RK2=RK*RK                                                             GY   8
      RH2=RH*RH                                                             GY   9
      T1=.25*A2*RH2/R4                                                      GY  10
      T2=.5*A2/R2                                                           GY  11
      C1=CMPLX(1.,RK)                                                       GY  12
      C2=3.*C1-RK2                                                          GY  13
      C3=CMPLX(6.,RK)*RK2-15.*C1                                            GY  14
      GZ=CMPLX(COS(RK),-SIN(RK))/R                                          GY  15
      G2=GZ*(1.+T1*C2)                                                      GY  16
      G1=G2-T2*C1*GZ                                                        GY  17
      GZ=GZ/R2                                                              GY  18
      G2P=GZ*(T1*C3-C1)                                                     GY  19
      GZP=T2*C2*GZ                                                          GY  20
      G3=G2P+GZP                                                            GY  21
      G1P=G3*ZZ                                                             GY  22
      IF (IRA.EQ.1) GO TO 2                                                 GY  23
      G3=(G3+GZP)*RH                                                        GY  24
      GZP=-ZZ*C1*GZ                                                         GY  25
      IF (RH.GT.1.E-10) GO TO 1                                             GY  26
      G2=0.                                                                 GY  27
      G2P=0.                                                                GY  28
      RETURN                                                                GY  29
1     G2=G2/RH                                                              GY  30
      G2P=G2P*ZZ/RH                                                         GY  31
      RETURN                                                                GY  32
2     T2=.5*A                                                               GY  33
      G2=-T2*C1*GZ                                                          GY  34
      G2P=T2*GZ*C2/R2                                                       GY  35
      G3=RH2*G2P-A*GZ*C1                                                    GY  36
      G2P=G2P*ZZ                                                            GY  37
      GZP=-ZZ*C1*GZ                                                         GY  38
      RETURN                                                                GY  39
      END                                                                   GY  40-
```

HFK

PURPOSE

To compute the near H field of a uniform current filament by numerical integration.

METHOD

The H field of a current filament of length Δ with uniform current distribution of magnitude $I = \lambda$ is

$$H_\phi = \frac{k\rho'}{2} \int_{-k\Delta/2}^{k\Delta/2} \left[\frac{1}{(kr)^3} + \frac{1}{(kr)^2} \right] \exp(-jkr)\, d(kz) ,$$

where r, ρ', z' and z are defined in the description of subroutine GH. The numerical integration is performed by the method of Romberg quadrature with variable interval width, which is described in the discussion of subroutine INTX. The integral is multiplied by $k\rho'/2$ at HF79 and HF80 in the code.

SYMBOL DICTIONARY

This listing excludes those variables used in the numerical quadrature algorithm, which are defined under subroutine INTX.

RHK = $k\rho'$

RHKS = $(k\rho')^2$

SGI = imaginary part of H_ϕ

SGR = real part of H_ϕ

ZPK = kz' (z' = z coordinate of observation point)

ZPKX = ZPK

```
      SUBROUTINE HFK (EL1,EL2,RHK,ZPKX,SGR,SGI)                          HF    1
C     HFK COMPUTES THE H FIELD OF A UNIFORM CURRINT FILAMENT BY          HF    2
C     NUMERICAL INTEGRATION                                              HF    3
      COMMON /TMH/ ZPK,RHKS                                              HF    4
      DATA NX,NM,NTS,RX/1,65536,4,1.E-4/                                 HF    5
      ZPK=ZPKX                                                           HF    6
      RHKS=RHK*RHK                                                       HF    7
      Z=EL1                                                              HF    8
      ZE=EL2                                                             HF    9
      S=ZE-Z                                                             HF   10
      EP=S/(10.*NM)                                                      HF   11
      ZEND=ZE-EP                                                         HF   12
      SGR=0.0                                                            HF   13
      SGI=0.0                                                            HF   14
      NS=NX                                                              HF   15
      NT=0                                                               HF   16
      CALL GH (Z,G1R,G1I)                                                HF   17
1     DZ=S/NS                                                            HF   18
      ZP=Z+DZ                                                            HF   19
      IF (ZP-ZE) 3,3,2                                                   HF   20
2     DZ=ZE-Z                                                            HF   21
      IF (ABS(DZ)-EP) 17,17,3                                            HF   22
3     DZOT=DZ*.5                                                         HF   23
      ZP=Z+DZOT                                                          HF   24
      CALL GH (ZP,G3R,G3I)                                               HF   25
      ZP=Z+DZ                                                            HF   26
      CALL GH (ZP,G5R,G5I)                                               HF   27
4     T00R=(G1R+G5R)*DZOT                                                HF   28
      T00I=(G1I+G5I)*DZOT                                                HF   29
      T01R=(T00R+DZ*G3R)*0.5                                             HF   30
      T01I=(T00I+DZ*G3I)*0.5                                             HF   31
      T10R=(4.0*T01R-T00R)/3.0                                           HF   32
      T10I=(4.0*T01I-T00I)/3.0                                           HF   33
      CALL TEST (T01R,T10R,TE1R,T01I,T10I,TE1I,0.)                       HF   34
      IF (TE1I-RX) 5,5,6                                                 HF   35
5     IF (TE1R-RX) 8,8,6                                                 HF   36
6     ZP=Z+DZ*0.25                                                       HF   37
      CALL GH (ZP,G2R,G2I)                                               HF   38
      ZP=Z+DZ*0.75                                                       HF   39
      CALL GH (ZP,G4R,G4I)                                               HF   40
      T02R=(T01R+DZOT*(G2R+G4R))*0.5                                     HF   41
      T02I=(T01I+DZOT*(G2I+G4I))*0.5                                     HF   42
      T11R=(4.0*T02R-T01R)/3.0                                           HF   43
      T11I=(4.0*T02I-T01I)/3.0                                           HF   44
      T20R=(16.0*T11R-T10R)/15.0                                         HF   45
      T20I=(16.0*T11I-T10I)/15.0                                         HF   46
      CALL TEST (T11R,T20R,TE2R,T11I,T20I,TE2I,0.)                       HF   47
      IF (TE2I-RX) 7,7,14                                                HF   48
7     IF (TE2R-RX) 9,9,14                                                HF   49
8     SGR=SGR+T10R                                                       HF   50
      SGI=SGI+T10I                                                       HF   51
      NT=NT+2                                                            HF   52
      GO TO 10                                                           HF   53
9     SGR=SGR+T20R                                                       HF   54
      SGI=SGI+T20I                                                       HF   55
      NT=NT+1                                                            HF   56
10    Z=Z+DZ                                                             HF   57
      IF (Z-ZEND) 11,17,17                                               HF   58
11    G1R=G5R                                                            HF   59
      G1I=G5I                                                            HF   60
      IF (NT-NTS) 1,12,12                                                HF   61
12    IF (NS-NX) 1,1,13                                                  HF   62
13    NS=NS/2                                                            HF   63
      NT=1                                                               HF   64
```

```
      GO TO 1                                                          HF  65
14    NT=0                                                             HF  66
      IF (NS-NM) 16,15,15                                              HF  67
15    PRINT 18, Z                                                      HF  68
      GO TO 9                                                          HF  69
16    NS=NS*2                                                          HF  70
      DZ=S/NS                                                          HF  71
      DZOT=DZ*0.5                                                      HF  72
      G5R=G3R                                                          HF  73
      G5I=G3I                                                          HF  74
      G3R=G2R                                                          HF  75
      G3I=G2I                                                          HF  76
      GO TO 4                                                          HF  77
17    CONTINUE                                                         HF  78
      SGR=SGR*RHK**.5                                                  HF  79
      SGI=SGI*RHK**.5                                                  HF  80
      RETURN                                                           HF  81
C                                                                      HF  82
18    FORMAT (24H STEP SIZE LIMITED AT Z=,F10.8)                       HF  83
      END                                                              HF  84-
```

HINTG

PURPOSE

To compute the near magnetic field due to a single patch in free space or over ground.

METHOD

The magnetic field is computed at the point, XI, YI, ZI due to the patch defined by parameters in COMMON/DATAJ/. The H field at $\bar{r} = (XI)\hat{x} + (YI)\hat{y} + (ZI)\hat{z}$ due to patch i, centered at $\bar{r}_i$, is approximated as:

$$\bar{H}(\bar{r}) = -\frac{1}{4\pi}\left[(1 + jkR)\frac{\exp(-jkR)}{(R/\lambda)^3}\right]\left[(\bar{R}/\lambda) \times \bar{J}_i\right] A_i/\lambda^2$$

where $\bar{R} = \bar{r} - \bar{r}_i$, and A_i is the area of patch i. This expression treats the surface currents as lumped at the center of the patch. $\bar{H}$ is computed for unit currents along the surface vectors $\hat{t}_{1i}$ and $\hat{t}_{2i}$.

When a ground is present, the code is executed twice in a loop. In the second pass, the field of the image of the patch is computed, multiplied by the reflection coefficients, and added to the direct field.

SYMBOL DICTIONARY

CR = cos (kR)

CTH = cos θ, θ = angle between the reflected ray and the normal to the ground

EXC, EYC, EZC = x, y, and z components of $\bar{H}$ excluding ($\times \bar{J}_i$) term

EXK, EYK, EZK = $\bar{H}$ for $\bar{J}_i = \hat{t}_{1i}$

EXS, EYS, EZS = $\bar{H}$ for $\bar{J}_i = \hat{t}_{2i}$

F1X, F1Y, F1Z = $\bar{H}$ for $\bar{J}_i = \hat{t}_{1i}$; direct or reflected field contribution

F2X, F2Y, F2Z = $\bar{H}$ for $\bar{J}_i = \hat{t}_{2i}$; direct or reflected field contribution

FPI = 4π

GAM = $\bar{H}$ excluding the term $(\bar{R}/\lambda) \times \bar{J}_i$

IP = 1 for direct field, 2 for reflected field

IPERF = 1 for perfect ground, 0 otherwise

KSYMP = 1 for free space, 2 for ground

PX, PY = unit vector normal to plane of incidence for reflected ray $\hat{\rho}$

R = R/λ

RFL = +1 for direct field, -1 for reflected field

RK = kR; $k = 2\pi/\lambda$

RRH = R_H

RRV = R_V

RSQ = R^2/λ^2

RX, RY, RZ = $\bar{R}/\lambda$

S = A_i/λ^2

SR = sin (kR)

T1XJ, T1YJ, T1ZJ = $\hat{t}_{1i}$

T2XJ, T2YJ, T2ZJ = $\hat{t}_{2i}$

T1ZR = z component of $\hat{t}_{1i}$ for patch i or for the image of patch i reflected in the ground

T2ZR = same as T1ZR for the $\hat{t}_{2i}$

TP = 2π

XI, YI, ZI = field evaluation point $\bar{r}/\lambda$

XJ
YJ } = position of center of patch $\bar{r}_1/\lambda$
ZJ

XYMAG = magnitude of $\bar{R}/\lambda$ projected on the x-y plane

CONSTANTS

12.56637062 = 4π

6.283185308 = 2π

```
      SUBROUTINE HINTG (XI,YI,ZI)                                          HI   1
C     HINTG COMPUTES THE H FIELD OF A PATCH CURRENT                        HI   2
      COMPLEX EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC,ZRATI,ZRATI2,GAM,F1X,F   HI   3
     11Y,F1Z,F2X,F2Y,F2Z,RRV,RRH,T1,FRATI                                  HI   4
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ   HI   5
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                              HI   6
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR,   HI   7
     1IPERF,T1,T2                                                         HI   8
      EQUIVALENCE (T1XJ,CABJ), (T1YJ,SABJ), (T1ZJ,SALPJ), (T2XJ,B), (T2Y   HI   9
     1J,IND1), (T2ZJ,IND2)                                                HI  10
      DATA FPI/12.56637062/,TP/6.283185308/                                HI  11
      RX=XI-XJ                                                             HI  12
      RY=YI-YJ                                                             HI  13
      RFL=-1.                                                              HI  14
      EXK=(0.,0.)                                                          HI  15
      EYK=(0.,0.)                                                          HI  16
      EZK=(0.,0.)                                                          HI  17
      EXS=(0.,0.)                                                          HI  18
      EYS=(0.,0.)                                                          HI  19
      EZS=(0.,0.)                                                          HI  20
      DO 5 IP=1,KSYMP                                                      HI  21
      RFL=-RFL                                                             HI  22
      RZ=ZI-ZJ*RFL                                                         HI  23
      RSQ=RX*RX+RY*RY+RZ*RZ                                                HI  24
      IF (RSQ.LT.1.E-20) GO TO 5                                           HI  25
      R=SQRT(RSQ)                                                          HI  26
      RK=TP*R                                                              HI  27
      CR=COS(RK)                                                           HI  28
      SR=SIN(RK)                                                           HI  29
      GAM=-(CMPLX(CR,-SR)+RK*CMPLX(SR,CR))/(FPI*RSQ*R)*S                   HI  30
      EXC=GAM*RX                                                           HI  31
      EYC=GAM*RY                                                           HI  32
      EZC=GAM*RZ                                                           HI  33
      T1ZR=T1ZJ*RFL                                                        HI  34
      T2ZR=T2ZJ*RFL                                                        HI  35
      F1X=EYC*T1ZR-EZC*T1YJ                                                HI  36
      F1Y=EZC*T1XJ-EXC*T1ZR                                                HI  37
      F1Z=EXC*T1YJ-EYC*T1XJ                                                HI  38
      F2X=EYC*T2ZR-EZC*T2YJ                                                HI  39
      F2Y=EZC*T2XJ-EXC*T2ZR                                                HI  40
      F2Z=EXC*T2YJ-EYC*T2XJ                                                HI  41
      IF (IP.EQ.1) GO TO 4                                                 HI  42
      IF (IPERF.NE.1) GO TO 1                                              HI  43
      F1X=-F1X                                                             HI  44
      F1Y=-F1Y                                                             HI  45
      F1Z=-F1Z                                                             HI  46
      F2X=-F2X                                                             HI  47
      F2Y=-F2Y                                                             HI  48
      F2Z=-F2Z                                                             HI  49
      GO TO 4                                                              HI  50
1     XYMAG=SQRT(RX*RX+RY*RY)                                              HI  51
      IF (XYMAG.GT.1.E-6) GO TO 2                                          HI  52
      PX=0.                                                                HI  53
      PY=0.                                                                HI  54
      CTH=1.                                                               HI  55
      RRV=(1.,0.)                                                          HI  56
      GO TO 3                                                              HI  57
2     PX=-RY/XYMAG                                                         HI  58
      PY=RX/XYMAG                                                          HI  59
      CTH=RZ/R                                                             HI  60
      RRV=CSQRT(1.-ZRATI*ZRATI*(1.-CTH*CTH))                               HI  61
3     RRH=ZRATI*CTH                                                        HI  62
      RRH=(RRH-RRV)/(RRH+RRV)                                              HI  63
      RRV=ZRATI*RRV                                                        HI  64
```

```
      RRV=-(CTH-RRV)/(CTH+RRV)                                    HI  65
      GAM=(F1X*PX+F1Y*PY)*(RRV-RRH)                               HI  66
      F1X=F1X*RRH+GAM*PX                                          HI  67
      F1Y=F1Y*RRH+GAM*PY                                          HI  68
      F1Z=F1Z*RRH                                                 HI  69
      GAM=(F2X*PX+F2Y*PY)*(RRV-RRH)                               HI  70
      F2X=F2X*RRH+GAM*PX                                          HI  71
      F2Y=F2Y*RRH+GAM*PY                                          HI  72
      F2Z=F2Z*RRH                                                 HI  73
4     EXK=EXK+F1X                                                 HI  74
      EYK=EYK+F1Y                                                 HI  75
      EZK=EZK+F1Z                                                 HI  76
      EXS=EXS+F2X                                                 HI  77
      EYS=EYS+F2Y                                                 HI  78
      EZS=EZS+F2Z                                                 HI  79
5     CONTINUE                                                    HI  80
      RETURN                                                      HI  81
      END                                                         HI  82-
```

HSFLD

PURPOSE

To compute the near magnetic field due to constant, sine, and cosine current distributions on a segment in free space or over ground.

METHOD

The magnetic field is computed at the point XI, YI, ZI due to the segment defined by parameters in COMMON/DATAJ/. The fields computed by routine HSFLX are stored in /DATAJ/. When a ground is present, the code is executed twice in a loop. In the second pass, the field of the image of the segment is computed, multiplied by the reflection coefficients, and added to the direct field.

The field is evaluated in a cylindrical coordinate system with the source segment at the origin. The radius of a segment on which the field is evaluated is treated in the same way as for the electric field in subroutine EFLD. When the field evaluation point is not on a segment, the observation segment radius is set to zero in the call to HSFLD. Thus, as for the electric field, the ρ coordinate of the field evaluation point is computed for the surface of the observation segment as $\rho' = (\rho^2 + a^2)^{1/2}$, where ρ is the distance from the axis of the source segment to (XI, YI, ZI) and a is the radius of the observation segment. The resulting H field is multiplied by ρ/ρ'.

SYMBOL DICTIONARY

AI = radius of observation segment, if any

CTH = cos θ, θ = angle between the ray reflected from the ground and vertical

ETA = $\eta = \sqrt{\mu/\epsilon}$

HPC, HPK, HPS = H_ϕ due to cosine, constant, and sine current, respectively

PHX, PHY, PHZ = $(\rho/\rho')\hat{\phi}$ in the cylindrical coordinates of the source segment or its image

PX, PY = unit vector normal to the plane of incidence of the reflected ray, $\hat{p}$

QX, QY, QZ = $\rho/\rho'\ [R_H\hat{\phi} + (R_V - R_H)(\hat{\phi} \cdot \hat{p})\hat{p}]$ for reflected ray

RFL = +1 for direct field, -1 for reflected field

RH = ρ'

RHOSPC = distance from coordinate origin to the point where the ray from the source to (XI, YI, ZI) reflects from the ground

RHOX, RHOY, RHOZ = $\overline{\rho}$ or $\overline{\rho}/\rho'$

RMAG = distance from the field evaluation point to the center of the source segment

RRH = R_H

RRV = R_V

SALPR = z component of unit vector in the direction of the source segment or its image

XI, YI, ZI = x, y, z coordinates of the field evaluation point

XIJ, YIJ, ZIJ = x, y, z components of distance from center of source segment to field observation point

XSPEC, YSPEC = x, y coordinates of the ground plane reflection point

XYMAG = horizontal distance from the source segment to the field observation point

ZP = projection of the vector (XIJ, YIJ, ZIJ) on the axis of the source segment

ZRATX = temporary storage for ZRATI

```
      SUBROUTINE HSFLD (XI,YI,ZI,AI)                                    HS    1
C     HSFLD COMPUTES THE H FIELD FOR CONSTANT, SINE, AND COSINE CURRENT  HS    2
C     ON A SEGMENT INCLUDING GROUND EFFECTS.                            HS    3
      COMPLEX EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC,ZRATI,ZRATI2,T1,HPK,HP HS    4
     1S,HPC,QX,QY,QZ,RRV,RRH,ZRATX,FRATI                               HS    5
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ HS    6
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                           HS    7
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR, HS    8
     1IPERF,T1,T2                                                       HS    9
      DATA ETA/376.73/                                                  HS   10
      XIJ=XI-XJ                                                         HS   11
      YIJ=YI-YJ                                                         HS   12
      RFL=-1.                                                           HS   13
      DO 7 IP=1,KSYMP                                                   HS   14
      RFL=-RFL                                                          HS   15
      SALPR=SALPJ*RFL                                                   HS   16
      ZIJ=ZI-RFL*ZJ                                                     HS   17
      ZP=XIJ*CABJ+YIJ*SABJ+ZIJ*SALPR                                    HS   18
      RHOX=XIJ-CABJ*ZP                                                  HS   19
      RHOY=YIJ-SABJ*ZP                                                  HS   20
      RHOZ=ZIJ-SALPR*ZP                                                 HS   21
      RH=SQRT(RHOX*RHOX+RHOY*RHOY+RHOZ*RHOZ+AI*AI)                      HS   22
      IF (RH.GT.1.E-10) GO TO 1                                         HS   23
      EXK=0.                                                            HS   24
      EYK=0.                                                            HS   25
      EZK=0.                                                            HS   26
      EXS=0.                                                            HS   27
      EYS=0.                                                            HS   28
      EZS=0.                                                            HS   29
      EXC=0.                                                            HS   30
      EYC=0.                                                            HS   31
      EZC=0.                                                            HS   32
      GO TO 7                                                           HS   33
1     RHOX=RHOX/RH                                                      HS   34
      RHOY=RHOY/RH                                                      HS   35
      RHOZ=RHOZ/RH                                                      HS   36
      PHX=SABJ*RHOZ-SALPR*RHOY                                          HS   37
      PHY=SALPR*RHOX-CABJ*RHOZ                                          HS   38
      PHZ=CABJ*RHOY-SABJ*RHOX                                           HS   39
      CALL HSFLX (S,RH,ZP,HPK,HPS,HPC)                                  HS   40
      IF (IP.NE.2) GO TO 6                                              HS   41
      IF (IPERF.EQ.1) GO TO 5                                           HS   42
      ZRATX=ZRATI                                                       HS   43
      RMAG=SQRT(ZP*ZP+RH*RH)                                            HS   44
      XYMAG=SQRT(XIJ*XIJ+YIJ*YIJ)                                       HS   45
C                                                                       HS   46
C     SET PARAMETERS FOR RADIAL WIRE GROUND SCREEN.                     HS   47
C                                                                       HS   48
      IF (NRADL.EQ.0) GO TO 2                                           HS   49
      XSPEC=(XI*ZJ+ZI*XJ)/(ZI+ZJ)                                       HS   50
      YSPEC=(YI*ZJ+ZI*YJ)/(ZI+ZJ)                                       HS   51
      RHOSPC=SQRT(XSPEC*XSPEC+YSPEC*YSPEC+T2*T2)                        HS   52
      IF (RHOSPC.GT.SCRWL) GO TO 2                                      HS   53
      RRV=T1*RHOSPC*ALOG(RHOSPC/T2)                                     HS   54
      ZRATX=(RRV*ZRATI)/(ETA*ZRATI+RRV)                                 HS   55
2     IF (XYMAG.GT.1.E-6) GO TO 3                                       HS   56
C                                                                       HS   57
C     CALCULATION OF REFLECTION COEFFICIENTS WHEN GROUND IS SPECIFIED.  HS   58
C                                                                       HS   59
      PX=0.                                                             HS   60
      PY=0.                                                             HS   61
      CTH=1.                                                            HS   62
      RRV=(1.,0.)                                                       HS   63
      GO TO 4                                                           HS   64
```

```
      3     PX=-YIJ/XYMAG                                                  HS  65
            PY=XIJ/XYMAG                                                   HS  66
            CTH=ZIJ/RMAG                                                   HS  67
            RRV=CSQRT(1.-ZRATX*ZRATX*(1.-CTH*CTH))                         HS  68
      4     RRH=ZRATX*CTH                                                  HS  69
            RRH=-(RRH-RRV)/(RRH+RRV)                                       HS  70
            RRV=ZRATX*RRV                                                  HS  71
            RRV=(CTH-RRV)/(CTH+RRV)                                        HS  72
            QY=(PHX*PX+PHY*PY)*(RRV-RRH)                                   HS  73
            QX=QY*PX+PHX*RRH                                               HS  74
            QY=QY*PY+PHY*RRH                                               HS  75
            QZ=PHZ*RRH                                                     HS  76
            EXK=EXK-HPK*QX                                                 HS  77
            EYK=EYK-HPK*QY                                                 HS  78
            EZK=EZK-HPK*QZ                                                 HS  79
            EXS=EXS-HPS*QX                                                 HS  80
            EYS=EYS-HPS*QY                                                 HS  81
            EZS=EZS-HPS*QZ                                                 HS  82
            EXC=EXC-HPC*QX                                                 HS  83
            EYC=EYC-HPC*QY                                                 HS  84
            EZC=EZC-HPC*QZ                                                 HS  85
            GO TO 7                                                        HS  86
      5     EXK=EXK-HPK*PHX                                                HS  87
            EYK=EYK-HPK*PHY                                                HS  88
            EZK=EZK-HPK*PHZ                                                HS  89
            EXS=EXS-HPS*PHX                                                HS  90
            EYS=EYS-HPS*PHY                                                HS  91
            EZS=EZS-HPS*PHZ                                                HS  92
            EXC=EXC-HPC*PHX                                                HS  93
            EYC=EYC-HPC*PHY                                                HS  94
            EZC=EZC-HPC*PHZ                                                HS  95
            GO TO 7                                                        HS  96
      6     EXK=HPK*PHX                                                    HS  97
            EYK=HPK*PHY                                                    HS  98
            EZK=HPK*PHZ                                                    HS  99
            EXS=HPS*PHX                                                    HS 100
            EYS=HPS*PHY                                                    HS 101
            EZS=HPS*PHZ                                                    HS 102
            EXC=HPC*PHX                                                    HS 103
            EYC=HPC*PHY                                                    HS 104
            EZC=HPC*PHZ                                                    HS 105
      7     CONTINUE                                                       HS 106
            RETURN                                                         HS 107
            END                                                            HS 108-
```

HSFLX

PURPOSE

To compute the near H field of filamentary currents of sine, cosine, and constant distribution on a segment.

METHOD

The wire segment is considered to be located at the origin of a local cylindrical coordinate system with the point at which the H field is computed being (ρ, ϕ, z). The coordinate geometry for a filament of current of length Δ is shown in figure 7. For a sine or cosine current distribution, the field can be written in closed form. For a current

$$I_0 \begin{bmatrix} \sin kz' \\ \cos kz' \end{bmatrix},$$

the field is

$$H_\phi(\rho, z) = \frac{-jI_0/\lambda}{2k\rho} \left\{ \exp(-jkr_2) \begin{bmatrix} \cos(k\Delta/2) \\ -\sin(k\Delta/2) \end{bmatrix} - \exp(-jkr_1) \begin{bmatrix} \cos(k\Delta/2) \\ \sin(k\Delta/2) \end{bmatrix} \right.$$

$$- j(kz - k\Delta/2) \frac{\exp(-jkr_2)}{kr_2} \begin{bmatrix} \sin(k\Delta/2) \\ \cos(k\Delta/2) \end{bmatrix}$$

$$\left. + j(kz + k\Delta/2) \frac{\exp(-jkr_1)}{kr_1} \begin{bmatrix} -\sin(k\Delta/2) \\ \cos(k\Delta/2) \end{bmatrix} \right\}.$$

$I_0/\lambda = 1$ is assumed in this routine.

For small values of ρ with $|z| > \Delta/2$, this equation may produce large numerical errors due to cancellation of large terms. Hence, for $z > 0$ and $\rho/(z - \Delta/2) < 10^{-3}$, a more stable approximation for small $\rho/(z \pm \Delta/2)$ is used:

$$H_\phi(\rho, z) = \frac{(\rho/\lambda)(Io/\lambda)}{8\pi} \exp(-jkz) \left\{ \left[\frac{2\pi}{(z + \Delta/2)/\lambda} - \frac{2\pi}{(z - \Delta/2)/\lambda} \right] \begin{bmatrix} 1 \\ -j \end{bmatrix} \right.$$

$$\left. + \left[\frac{\exp(jk\Delta/2)}{(z - \Delta/2)^2/\lambda^2} \begin{pmatrix} \sin(k\Delta/2) \\ \cos(k\Delta/2) \end{pmatrix} - \frac{\exp(-jk\Delta/2)}{(z + \Delta/2)^2/\lambda^2} \begin{pmatrix} -\sin(k\Delta/2) \\ \cos(k\Delta/2) \end{pmatrix} \right] \right\}.$$

For $z < 0$, the above equation is evaluated for $H_\phi(\rho, -z)$. The field of a sin kz' current is multiplied by -1 in this case, since it is an odd function of z.

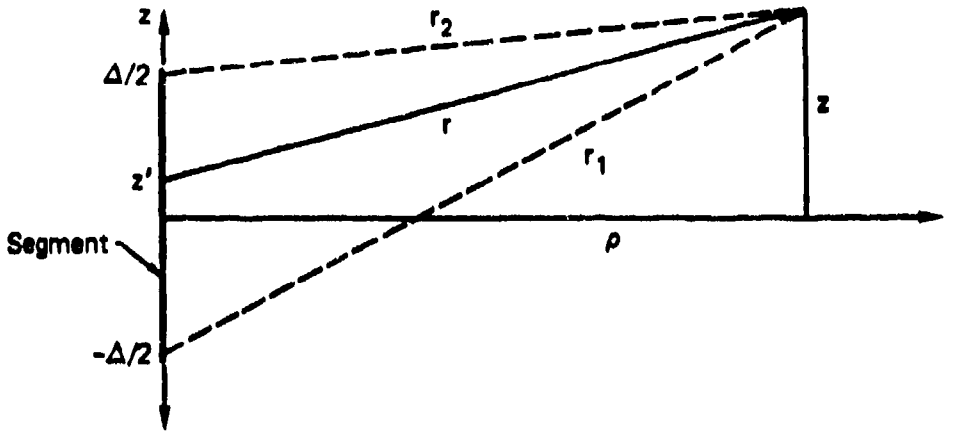


Figure 7. Coordinates for Evaluating H Field of a Segment.

The field due to a constant current is obtained by numerical integration, which is performed by subroutine HFK. If ρ is zero, all field quantities are set to zero, since H_ϕ is undefined.

SYMBOL DICTIONARY

CDK = cos(kΔ/2)
CONS = -j/(2kρ)
DH = Δ/2
DK = kΔ/2
EKR1 = exp(-jkr$_1$)
EKR2 = exp(-jkr$_2$)
FJ = j
FJK = -j2π
HKR, HKI = real and imaginary parts of H_ϕ due to a constant current
HPC, HPK, HPS = H_ϕ due to cosine, constant, and sine currents, respectively
HSS = sign of z
PI8 = 8π
R1 = r$_1$
R2 = r$_2$
RH = ρ
RH2 = ρ^2
RHZ = ρ/(z - Δ/2)

S = Δ

SDK = $\sin(k\Delta/2)$

TP = 2π

Z1 = $z + \Delta/2$

Z2 = $z - \Delta/2$

ZP = z

```
      SUBROUTINE HSFLX (S,RH,ZPX,HPK,HPS,HPC)                          HX   1
C     CALCULATES H FIELD OF SINE COSINE, AND CONSTANT CURRENT OF SEGMENT HX   2
      COMPLEX FJ,FJK,EKR1,EKR2,T1,T2,CONS,HPS,HPC,HPK                  HX   3
      DIMENSION FJX(2), FJKX(2)                                        HX   4
      EQUIVALENCE (FJ,FJX), (FJK,FJKX)                                 HX   5
      DATA TP/6.283185308/,FJX/0.,1./,FJKX/0.,-6.283185308/            HX   6
      DATA PI8/25.13274123/                                            HX   7
      IF (RH.LT.1.E-10) GO TO 6                                        HX   8
      IF (ZPX.LT.0.) GO TO 1                                           HX   9
      ZP=ZPX                                                           HX  10
      HSS=1.                                                           HX  11
      GO TO 2                                                          HX  12
1     ZP=-ZPX                                                          HX  13
      HSS=-1.                                                          HX  14
2     DH=.5*S                                                          HX  15
      Z1=ZP+DH                                                         HX  16
      Z2=ZP-DH                                                         HX  17
      IF (Z2.LT.1.E-7) GO TO 3                                         HX  18
      RHZ=RH/Z2                                                        HX  19
      GO TO 4                                                          HX  20
3     RHZ=1.                                                           HX  21
4     DK=TP*DH                                                         HX  22
      CDK=COS(DK)                                                      HX  23
      SDK=SIN(DK)                                                      HX  24
      CALL HFK (-DK,DK,RH*TP,ZP*TP,HKR,HKI)                            HX  25
      HPK=CMPLX(HKR,HKI)                                               HX  26
      IF (RHZ.LT.1.E-3) GO TO 5                                        HX  27
      RH2=RH*RH                                                        HX  28
      R1=SQRT(RH2+Z1*Z1)                                               HX  29
      R2=SQRT(RH2+Z2*Z2)                                               HX  30
      EKR1=CEXP(FJK*R1)                                                HX  31
      EKR2=CEXP(FJK*R2)                                                HX  32
      T1=Z1*EKR1/R1                                                    HX  33
      T2=Z2*EKR2/R2                                                    HX  34
      HPS=(CDK*(EKR2-EKR1)-FJ*SDK*(T2+T1))*HSS                         HX  35
      HPC=-SDK*(EKR2+EKR1)-FJ*CDK*(T2-T1)                              HX  36
      CONS=-FJ/(2.*TP*RH)                                              HX  37
      HPS=CONS*HPS                                                     HX  38
      HPC=CONS*HPC                                                     HX  39
      RETURN                                                           HX  40
5     EKR1=CMPLX(CDK,SDK)/(Z2*Z2)                                      HX  41
      EKR2=CMPLX(CDK,-SDK)/(Z1*Z1)                                     HX  42
      T1=TP*(1./Z1-1./Z2)                                              HX  43
      T2=CEXP(FJK*ZP)*RH/PI8                                           HX  44
      HPS=T2*(T1+(EKR1+EKR2)*SDK)*HSS                                  HX  45
      HPC=T2*(-FJ*T1+(EKR1-EKR2)*CDK)                                  HX  46
      RETURN                                                           HX  47
6     HPS=(0.,0.)                                                      HX  48
      HPC=(0.,0.)                                                      HX  49
      HPK=(0.,0.)                                                      HX  50
      RETURN                                                           HX  51
      END                                                              HX  52-
```

INTRP

PURPOSE

To evaluate the Sommerfeld integral contributions to the field of a source over ground by interpolation in precomputed tables.

METHOD

The interpolation region in R_1 and θ is covered by three grids as shown in Figure 12 of Part I. The interpolation tables and the number of data points and the boundaries of each grid are read from file 21 and stored in COMMON/GGRID/ by the main program. In subroutine INTRP the variable x corresponds to R_1 and y to θ.

The three interpolation tables are stored in the arrays AR1, AR2 and AR3 in COMMON/GGRID/. For grid i, ARi(I,J,K) is the value at

$$x_I = s_i + (I - 1)\,\Delta x_i\,, \qquad I = 1, \ldots N_i$$
$$y_J = t_i + (J - 1)\,\Delta y_i\,, \qquad J = 1, \ldots M_i$$

where s_i = XSA(i) , Δx_i = DXA(i) , N_i = NXA(i)

t_i = YSA(i) , Δy_i = DYA(i) , M_i = NYA(i)

Each array contains values for I_ρ^V, I_z^V, I_ρ^H and I_ϕ^H from equations 156 through 159 of Part I for K equal to 1 through 4, respectively. The grid boundaries and density of points can be varied but the relative positions of the three grids must be as shown in Figure 12 of Part I for the logic for choosing the correct grid to work correctly. In particular, XSA(1), YSA(1) and YSA(2) must be zero; and XSA(2) and XSA(3) must be equal.

For a given x and y the values of I_ρ^V, I_z^V, I_ρ^H and I_ϕ^H are found by bivariate cubic interpolation and returned in the variables F1, F2, F3 and F4. The grid containing (x,y) is determined and a four by four point region containing (x,y) is selected. If x_i and y_k are the minimum values of x and y in the four by four point region then four interpolation polynomials in x are computed for $y = y_j$ with $j = k, k + 1, k + 2, k + 3$. These are

$$f_{ij}(x) = a_{ij}\xi_i^3 + b_{ij}\xi_i^2 + c_{ij}\xi_i + d_{ij}$$

where $\xi_i = (x - x_{i+1})/\Delta x$

$$a_{ij} = \frac{1}{6}\left[F_{i+3,j} - F_{i,j} + 3(F_{i+1,j} - F_{i+2,j})\right]$$

$$b_{ij} = \frac{1}{2}\left[F_{i,j} - 2F_{i+1,j} + F_{i+2,j}\right]$$

$$c_{ij} = F_{i+2,j} - \frac{1}{6}\left[2F_{i,j} + 3F_{i+1,j} + F_{i+3,j}\right]$$

$$d_{ij} = F_{i+1,j}$$

$$F_{i,j} = F(x_i, y_j)$$

A cubic polynomial in y, fit to the points $f_{ij}(x)$ for $j = k, \ldots k + 3$ is then evaluated for the given y to obtain the interpolated value $\hat{F}(x,y)$

$$\hat{F}(x,y) = \frac{1}{6}(p_1\eta_k^3 + p_2\eta_k^2 + p_3\eta_k) + p_4$$

$$\eta_k = (y - y_{k+1})/\Delta y$$

$$p_1 = f_{i,k+3}(x) - f_{ik}(x) + 3\left[f_{i,k+1}(x) - f_{i,k+2}(x)\right]$$

$$p_2 = 3[f_{i,k}(x) - 2f_{i,k+1}(x) + f_{i,k+2}(x)]$$

$$p_3 = 6f_{i,k+2}(x) - 2f_{i,k}(x) - 3f_{i,k+1}(x) - f_{i,k+3}(x)$$

$$p_4 = f_{i,k+1}$$

To reduce computation time the coefficients a_{ij}, b_{ij}, c_{ij} and d_{ij} are saved as long as successive points (x,y) fall in the same four by four point region of a grid. In addition the four by four point interpolation regions are restricted to starting indices i and k with values $3n + 1$, $n = 0, 1 \ldots$. Thus the regions do not overlap. This is less accurate than centering the region on each x,y point but requires less frequent computation of the coefficients. At the outer edges of a grid the regions are chosen to extend to the edge but not beyond. If x,y is out of the entire three grid region the nearest four by four point region is used for extrapolation.

The coefficients a_{ij}, b_{ij}, c_{ij} and d_{ij} are stored in two dimensional arrays from IT 106 to IT 109. When they are used, from IT 118 to

IT 149 they are used as simple variables (A(1,1) ≡ A11) to save time. Also the three dimensional arrays AR1, AR2, and AR3 are used as linear arrays from IT 92 to IT 105. The equivalent three subscripts are shown in the comment at IT 91.

SYMBOL DICTIONARY

Aij	= A(i,j) = a_{ij}
AR1	= ARL1 = grid 1
AR2	= ARL2 = grid 2
AR3	= ARL3 = grid 3
Bij	= B(i,j) = b_{ij}
Cij	= C(i,j) = c_{ij}
Dij	= D(i,j) = d_{ij}
DX	= Δx for grid being used
DXA	= array of Δx values for the three grids
DY	= Δy for grid being used
DYA	= array of Δy values
EPSCF	= $\epsilon_1 - j\sigma/\omega\epsilon_0$
F1	= I_ρ^V
F2	= I_Z^V
F3	= I_ρ^H
F4	= I_ϕ^H
FX1	= $f_{i,j}(x)$
FX2	= $f_{i,j+1}(x)$
FX3	= $f_{i,j+2}(x)$
FX4	= $f_{i,j+3}(x)$
IADD	= index for linear arrays ARL1, etc.
IADZ	= initial value for IADD
IGR	= grid number for present x,y
IGRS	= grid number for last x,y
IX	= x index of the grid coordinate just less than x
IXEG	= x index of the upper edge of the last normally located interpolation patch when a patch out of the

	normal locations is used at the outer edge of a grid, -10000 otherwise
IXS	= 1 plus the x index of the lower edge of 4 by 4 point interpolation patch
IY, IYEG, IYS	= same for y as IX, IXEG and IXS
K	= 1, 2, 3, 4 for I_ρ^V, I_z^V, I_ρ^H, I_ϕ^H
ND	= NDA for the particular grid
NDA	= array containing the first dimensions of AR1, AR2 and AR3
NDP	= NDPA for a particular grid
NDPA	= array containing the product of the first two dimensions in AR1, AR2 and AR3
NXA	= number of x values in each grid
NXM2	= NXA - 2 for a particular grid
NXMS	= upper x index of the last normally located patch at the edge of a grid
NYA, NYM2, NYMS	= same for y as NXA, NXM2 and NXMS
P1, P2, P3, P4	= P_1, P_2, P_3, P_4
X	= x
XS	= XSA for the present grid
XS2	= XSA(2) through equivalence
XSA	= array of values of x at lower edge of each grid (s_i)
XX	= ξ_i
XZ	= x_{i+1} for computing ξ_i
Y	= y
YS	= YSA for present grid
YS3	= YSA(3) through equivalence
YSA	= array of values of y at lower edge of each grid (t_i)
YY	= η_k
YZ	= y_{k+1} for computing η_k

```
      SUBROUTINE INTRP (X,Y,F1,F2,F3,F4)                                IT   1
C                                                                       IT   2
C     INTRP USES BIVARIATE CUBIC INTERPOLATION TO OBTAIN THE VALUES OF  IT   3
C     4 FUNCTIONS AT THE POINT (X,Y).                                   IT   4
C                                                                       IT   5
      COMPLEX F1,F2,F3,F4,A,B,C,D,FX1,FX2,FX3,FX4,P1,P2,P3,P4,A11,A12,A1 IT   6
     13,A14,A21,A22,A23,A24,A31,A32,A33,A34,A41,A42,A43,A44,B11,B12,B13, IT   7
     2B14,B21,B22,B23,B24,B31,B32,B33,B34,B41,B42,B43,B44,C11,C12,C13,C1 IT   8
     34,C21,C22,C23,C24,C31,C32,C33,C34,C41,C42,C43,C44,D11,D12,D13,D14, IT   9
     4D21,D22,D23,D24,D31,D32,D33,D34,D41,D42,D43,D44                   IT  10
      COMPLEX AR1,AR2,AR3,ARL1,ARL2,ARL3,EPSCF                          IT  11
      COMMON /GGRID/ AR1(11,10,4),AR2(17,5,4),AR3(9,8,4),EPSCF,DXA(3),DY IT  12
     1A(3),XSA(3),YSA(3),NXA(3),NYA(3)                                  IT  13
      DIMENSION NDA(3), NDPA(3)                                         IT  14
      DIMENSION A(4,4), B(4,4), C(4,4), D(4,4), ARL1(1), ARL2(1), ARL3(1 IT  15
     1)                                                                 IT  16
      EQUIVALENCE (A(1,1),A11), (A(1,2),A12), (A(1,3),A13), (A(1,4),A14) IT  17
      EQUIVALENCE (A(2,1),A21), (A(2,2),A22), (A(2,3),A23), (A(2,4),A24) IT  18
      EQUIVALENCE (A(3,1),A31), (A(3,2),A32), (A(3,3),A33), (A(3,4),A34) IT  19
      EQUIVALENCE (A(4,1),A41), (A(4,2),A42), (A(4,3),A43), (A(4,4),A44) IT  20
      EQUIVALENCE (B(1,1),B11), (B(1,2),B12), (B(1,3),B13), (B(1,4),B14) IT  21
      EQUIVALENCE (B(2,1),B21), (B(2,2),B22), (B(2,3),B23), (B(2,4),B24) IT  22
      EQUIVALENCE (B(3,1),B31), (B(3,2),B32), (B(3,3),B33), (B(3,4),B34) IT  23
      EQUIVALENCE (B(4,1),B41), (B(4,2),B42), (B(4,3),B43), (B(4,4),B44) IT  24
      EQUIVALENCE (C(1,1),C11), (C(1,2),C12), (C(1,3),C13), (C(1,4),C14) IT  25
      EQUIVALENCE (C(2,1),C21), (C(2,2),C22), (C(2,3),C23), (C(2,4),C24) IT  26
      EQUIVALENCE (C(3,1),C31), (C(3,2),C32), (C(3,3),C33), (C(3,4),C34) IT  27
      EQUIVALENCE (C(4,1),C41), (C(4,2),C42), (C(4,3),C43), (C(4,4),C44) IT  28
      EQUIVALENCE (D(1,1),D11), (D(1,2),D12), (D(1,3),D13), (D(1,4),D14) IT  29
      EQUIVALENCE (D(2,1),D21), (D(2,2),D22), (D(2,3),D23), (D(2,4),D24) IT  30
      EQUIVALENCE (D(3,1),D31), (D(3,2),D32), (D(3,3),D33), (D(3,4),D34) IT  31
      EQUIVALENCE (D(4,1),D41), (D(4,2),D42), (D(4,3),D43), (D(4,4),D44) IT  32
      EQUIVALENCE (ARL1,AR1), (ARL2,AR2), (ARL3,AR3), (XS2,XSA(2)), (YS3 IT  33
     1,YSA(3))                                                          IT  34
      DATA IXS,IYS,IGRS/-10,-10,-10/,DX,DY,XS,YS/1.,1.,0.,0./           IT  35
      DATA NDA/11,17,9/,NDPA/110,85,72/,IXEG,IYEG/0,0/                  IT  36
      IF (X.LT.XS.OR.Y.LT.YS) GO TO 1                                   IT  37
      IX=INT((X-XS)/DX)+1                                               IT  38
      IY=INT((Y-YS)/DY)+1                                               IT  39
C                                                                       IT  40
C     IF POINT LIES IN SAME 4 BY 4 POINT REGION AS PREVIOUS POINT, OLD  IT  41
C     VALUES ARE REUSED                                                 IT  42
C                                                                       IT  43
      IF (IX.LT.IXEG.OR.IY.LT.IYEG) GO TO 1                             IT  44
      IF (IABS(IX-IXS).LT.2.AND.IABS(IY-IYS).LT.2) GO TO 12             IT  45
C                                                                       IT  46
C     DETERMINE CORRECT GRID AND GRID REGION                            IT  47
C                                                                       IT  48
1     IF (X.GT.XS2) GO TO 2                                             IT  49
      IGR=1                                                             IT  50
      GO TO 3                                                           IT  51
2     IGR=2                                                             IT  52
      IF (Y.GT.YS3) IGR=3                                               IT  53
3     IF (IGR.EQ.IGRS) GO TO 4                                          IT  54
      IGRS=IGR                                                          IT  55
      DX=DXA(IGRS)                                                      IT  56
      DY=DYA(IGRS)                                                      IT  57
      XS=XSA(IGRS)                                                      IT  58
      YS=YSA(IGRS)                                                      IT  59
      NXM2=NXA(IGRS)-2                                                  IT  60
      NYM2=NYA(IGRS)-2                                                  IT  61
      NXMS=((NXM2+1)/3)*3+1                                             IT  62
      NYMS=((NYM2+1)/3)*3+1                                             IT  63
      ND=NDA(IGRS)                                                      IT  64
```

```
      NDP=NDPA(IGRS)                                                    IT  65
      IX=INT((X-XS)/DX)+1                                               IT  66
      IY=INT((Y-YS)/DY)+1                                               IT  67
 4    IXS=((IX-1)/3)*3+2                                                IT  68
      IF (IXS.LT.2) IXS=2                                               IT  69
      IXEG=-10000                                                       IT  70
      IF (IXS.LE.NXM2) GO TO 5                                          IT  71
      IXS=NXM2                                                          IT  72
      IXEG=NXMS                                                         IT  73
 5    IYS=((IY-1)/3)*3+2                                                IT  74
      IF (IYS.LT.2) IYS=2                                               IT  75
      IYEG=-10000                                                       IT  76
      IF (IYS.LE.NYM2) GO TO 6                                          IT  77
      IYS=NYM2                                                          IT  78
      IYEG=NYMS                                                         IT  79
C                                                                       IT  80
C     COMPUTE COEFFICIENTS OF 4 CUBIC POLYNOMIALS IN X FOR THE 4 GRID   IT  81
C     VALUES OF Y FOR EACH OF THE 4 FUNCTIONS                           IT  82
C                                                                       IT  83
 6    IADZ=IXS+(IYS-3)*ND-NDP                                           IT  84
      DO 11 K=1,4                                                       IT  85
      IADZ=IADZ+NDP                                                     IT  86
      IADD=IADZ                                                         IT  87
      DO 11 I=1,4                                                       IT  88
      IADD=IADD+ND                                                      IT  89
      GO TO (7,8,9), IGRS                                               IT  90
C     P1=AR1(IXS-1,IYS-2+I,K)                                           IT  91
 7    P1=ARL1(IADD-1)                                                   IT  92
      P2=ARL1(IADD)                                                     IT  93
      P3=ARL1(IADD+1)                                                   IT  94
      P4=ARL1(IADD+2)                                                   IT  95
      GO TO 10                                                          IT  96
 8    P1=ARL2(IADD-1)                                                   IT  97
      P2=ARL2(IADD)                                                     IT  98
      P3=ARL2(IADD+1)                                                   IT  99
      P4=ARL2(IADD+2)                                                   IT 100
      GO TO 10                                                          IT 101
 9    P1=ARL3(IADD-1)                                                   IT 102
      P2=ARL3(IADD)                                                     IT 103
      P3=ARL3(IADD+1)                                                   IT 104
      P4=ARL3(IADD+2)                                                   IT 105
10    A(I,K)=(P4-P1+3.*(P2-P3))*.1666666667                             IT 106
      B(I,K)=(P1-2.*P2+P3)*.5                                           IT 107
      C(I,K)=P3-(2.*P1+3.*P2+P4)*.1666666667                            IT 108
11    D(I,K)=P2                                                         IT 109
      XZ=(IXS-1)*DX+XS                                                  IT 110
      YZ=(IYS-1)*DY+YS                                                  IT 111
C                                                                       IT 112
C     EVALUATE POLYNOMIALS IN X AND THEN USE CUBIC INTERPOLATION IN Y   IT 113
C     FOR EACH OF THE 4 FUNCTIONS.                                      IT 114
C                                                                       IT 115
12    XX=(X-XZ)/DX                                                      IT 116
      YY=(Y-YZ)/DY                                                      IT 117
      FX1=((A11*XX+B11)*XX+C11)*XX+D11                                  IT 118
      FX2=((A21*XX+B21)*XX+C21)*XX+D21                                  IT 119
      FX3=((A31*XX+B31)*XX+C31)*XX+D31                                  IT 120
      FX4=((A41*XX+B41)*XX+C41)*XX+D41                                  IT 121
      P1=FX4-FX1+3.*(FX2-FX3)                                           IT 122
      P2=3.*(FX1-2.*FX2+FX3)                                            IT 123
      P3=6.*FX3-2.*FX1-3.*FX2-FX4                                       IT 124
      F1=((P1*YY+P2)*YY+P3)*YY*.1666666667+FX2                          IT 125
      FX1=((A12*XX+B12)*XX+C12)*XX+D12                                  IT 126
      FX2=((A22*XX+B22)*XX+C22)*XX+D22                                  IT 127
      FX3=((A32*XX+B32)*XX+C32)*XX+D32                                  IT 128
```

```
      FX4=((A42*XX+B42)*XX+C42)*XX+D42                                  IT 129
      P1=FX4-FX1+3.*(FX2-FX3)                                           IT 130
      P2=3.*(FX1-2.*FX2+FX3)                                            IT 131
      P3=6.*FX3-2.*FX1-3.*FX2-FX4                                       IT 132
      F2=((P1*YY+P2)*YY+P3)*YY*.1666666667+FX2                          IT 133
      FX1=((A13*XX+B13)*XX+C13)*XX+D13                                  IT 134
      FX2=((A23*XX+B23)*XX+C23)*XX+D23                                  IT 135
      FX3=((A33*XX+B33)*XX+C33)*XX+D33                                  IT 136
      FX4=((A43*XX+B43)*XX+C43)*XX+D43                                  IT 137
      P1=FX4-FX1+3.*(FX2-FX3)                                           IT 138
      P2=3.*(FX1-2.*FX2+FX3)                                            IT 139
      P3=6.*FX3-2.*FX1-3.*FX2-FX4                                       IT 140
      F3=((P1*YY+P2)*YY+P3)*YY*.1666666667+FX2                          IT 141
      FX1=((A14*XX+B14)*XX+C14)*XX+D14                                  IT 142
      FX2=((A24*XX+B24)*XX+C24)*XX+D24                                  IT 143
      FX3=((A34*XX+B34)*XX+C34)*XX+D34                                  IT 144
      FX4=((A44*XX+B44)*XX+C44)*XX+D44                                  IT 145
      P1=FX4-FX1+3.*(FX2-FX3)                                           IT 146
      P2=3.*(FX1-2.*FX2+FX3)                                            IT 147
      P3=6.*FX3-2.*FX1-3.*FX2-FX4                                       IT 148
      F4=((P1*YY+P2)*YY+P3)*YY*.1666666667+FX2                          IT 149
      RETURN                                                            IT 150
      END                                                               IT 151-
```

INTX

PURPOSE

To numerically compute the integral of the function exp(jkr)/kr.

METHOD

For evaluation of the field due to a segment, a local cylindrical coordinate system is defined with origin at the center of the segment and z axis in the segment direction. This geometry is illustrated in the discussion of subroutine GF. Subroutine INTX is called by subroutine EFLD to evaluate the integral

$$G = \int_{-k\Delta/2}^{k\Delta/2} \frac{\exp(-jkr)}{kr}\, d(kz) ,$$

where

$$r = [\rho'^2 + (z - z')^2]^{1/2} ,$$

and other symbols are defined in the discussion of subroutine GF.

The numerical integration technique of Romberg integration with variable interval width is used (refs. 3 and 4). The Romberg integration formula is obtained from the trapezoidal formula by an iterative procedure (ref. 1). The trapezoidal rule for integration of the function f(x) over an interval (a, b) using 2^k subintervals is

$$T_{0k} = [(b - a)/N][(1/2)\, f_0 + f_1 + \ldots + f_{N-1} + (1/2) f_N] ,$$

where

$$N = 2^k$$
$$f_i = f(x_i)$$
$$x_i = a + i(b - a)/N$$

These trapezoidal-rule answers are then used in the iterative formula

$$T_{m,n} = \left(4^m T_{m-1,n+1} - T_{m-1,n}\right)/(4^m - 1) .$$

The results $T_{m,n}$ may be arranged in a triangular matrix of the form

$$\begin{array}{lll} T_{0,0} & & \\ T_{0,1} & T_{1,0} & \\ T_{0,2} & T_{1,1} & T_{2,0} \\ \vdots & \vdots & \vdots \end{array}$$

where the elements in the first column, T_{0k}, represent the trapezoidal rule results, and the elements in the diagonal, T_{k0}, are the Romberg integration results for 2^k subintervals.

Convergence to increasingly more accurate answers takes place down the first column and the diagonal, as well as towards the right along the rows. The row convergence generally provides a more realistic indication of error magnitude than two successive trapezoidal-rule or Romberg answers.

This convergence along the rows is used to determine the interval width in the variable interval-width scheme. The complete integration interval is first divided into a minimum number of subintervals (presently set to 1) and T_{00}, T_{01}, and T_{10} are computed on the first subinterval. The relative difference of T_{01} and T_{10} is then computed, and if less than the error criterion, R_x, T_{10} is accepted as the integral over that interval, and integration proceeds to the next interval. If the difference of T_{01} and T_{10} is too great, T_{02}, T_{11} and T_{20} are computed. The relative difference of T_{11} and T_{20} is then computed, and if less than R_x, T_{20} is accepted as the integral over the subinterval. If the difference of T_{11} and T_{20} is too great, the subinterval is divided in half and the process repeated starting with T_{00} for the left hand, new subinterval. The subinterval is repeatedly halved until convergence to less than R_x is found. The process is repeated for successive subintervals until the right-hand side of the integration interval is reached. When convergence has been obtained with a given subinterval size for a few times, the routine attempts doubling the subinterval size to maintain the largest subinterval size that will give the required accuracy. Thus, the routine will use many points in a rapidly changing region of a function and fewer points where the function is smoothly varying.

Since the function to be integrated is complex, the convergence of both real and imaginary parts is tested and both must be less than R_x. The same subinterval sizes are used for real and imaginary parts.

When the field of a segment is being computed at the segment's own center, the length r becomes

$$r = [b^2 + (z - z')^2]^{1/2} ,$$

where b is the wire radius. For small values of b, the real part of the integrand is sharply peaked and, hence, difficult to integrate numerically. Hence, the integral is divided into the components

$$G' = \int_{-k\Delta/2}^{k\Delta/2} \frac{\exp(-jkr) - 1}{kr} \, d(kz)$$

$$G'' = \int_{-k\Delta/2}^{k\Delta/2} \frac{1}{kr} \, d(kz)$$

$$G = G' + G''$$

G' must be computed numerically; however, the integrand is no longer peaked. G'', which contains the sharp peak, can be computed as

$$G'' = 2 \log \left(\frac{\sqrt{b^2 + \Delta^2} + \Delta}{b} \right)$$

To further reduce integration time for the self term, the integral of G' is computed from $-k\Delta/2$ to 0, and the result doubled to obtain G'.

SYMBOL DICTIONARY

ABS = external routine (absolute value)
ALOG = external routine (natural log)
B = wire radius, b/λ
DZ = subinterval size on which T_{00}, T_{01}, ... are computed
DZOT = 0.5 DZ
EL1 = $-k\Delta/2$
EL2 = $k\Delta/2$
EP = tolerance for ending the integration interval
FNM = real number equivalent of NM
FNS = real number equivalent of NS
GF = external routine (integrand)
G1I = imaginary part of f_1
G1R = real part of f_1

G2I = imaginary part of f_2
G2R = real part of f_2
G3I = imaginary part of f_3
G3R = real part of f_3
G4I = imaginary part of f_4
G4R = real part of f_4
G5I = imaginary part of f_5
G5R = real part of f_5
IJ = indication of self term integration when equal to zero
NM = minimum allowed subinterval size is $k\Delta/NM$
NS = present subinterval size is $k\Delta/NS$
NT = counter to control increasing of subinterval size
NTS = larger values retard increasing of subinterval size
NX = maximum allowed subinterval size is $k\Delta/NX$
RX = R_x
S = Δ/λ
SGI = imaginary part of G
SGR = real part of G
SQRT = external routine (square root)
TEST = external routine (computes relative convergence)
TE1I = relative difference of T_{01} and T_{10} for imaginary part
TE1R = relative difference of T_{01} and T_{10} for real part
TE2I = relative difference of T_{11} and T_{20} for imaginary part
TE2R = relative difference of T_{11} and T_{20} for real part
T00I = imaginary part T_{00}
T00R = real part T_{00}
T01I = imaginary part T_{01}
T01R = real part T_{01}
T02I = imaginary part T_{02}
T02R = real part T_{02}
T10I = imaginary part T_{10}
T10R = real part of T_{10}
T11I = imaginary part of T_{11}
T11R = real part of T_{11}
T20I = imaginary part of T_{20}
T20R = real part of T_{20}

Z = integration variable at left-hand side of subinterval

ZE = $k\Delta/2$

ZEND = $k\Delta/2$ - EP; EP = tolerance term

ZP = integration variable

CONSTANTS

65536 = 2^{16} = limit of minimum subinterval size (NM)

1.E-4 = error criterion, R_x

```
      SUBROUTINE INTX (EL1,EL2,B,IJ,SGR,SGI)                            IN   1
C                                                                       IN   2
C     INTX PERFORMS NUMERICAL INTEGRATION OF EXP(JKR)/R BY THE METHOD OF IN   3
C     VARIABLE INTERVAL WIDTH ROMBERG INTEGRATION.  THE INTEGRAND VALUE IN   4
C     IS SUPPLIED BY SUBROUTINE GF.                                     IN   5
C                                                                       IN   6
      DATA NX,NM,NTS,RX/1,65536,4,1.E-4/                                IN   7
      Z=EL1                                                             IN   8
      ZE=EL2                                                            IN   9
      IF (IJ.EQ.0) ZE=0.                                                IN  10
      S=ZE-Z                                                            IN  11
      FNM=NM                                                            IN  12
      EP=S/(10.*FNM)                                                    IN  13
      ZEND=ZE-EP                                                        IN  14
      SGR=0.                                                            IN  15
      SGI=0.                                                            IN  16
      NS=NX                                                             IN  17
      NT=0                                                              IN  18
      CALL GF (Z,G1R,G1I)                                               IN  19
1     FNS=NS                                                            IN  20
      DZ=S/FNS                                                          IN  21
      ZP=Z+DZ                                                           IN  22
      IF (ZP-ZE) 3,3,2                                                  IN  23
2     DZ=ZE-Z                                                           IN  24
      IF (ABS(DZ)-EP) 17,17,3                                           IN  25
3     DZOT=DZ*.5                                                        IN  26
      ZP=Z+DZOT                                                         IN  27
      CALL GF (ZP,G3R,G3I)                                              IN  28
      ZP=Z+DZ                                                           IN  29
      CALL GF (ZP,G5R,G5I)                                              IN  30
4     T00R=(G1R+G5R)*DZOT                                               IN  31
      T00I=(G1I+G5I)*DZOT                                               IN  32
      T01R=(T00R+DZ*G3R)*0.5                                            IN  33
      T01I=(T00I+DZ*G3I)*0.5                                            IN  34
      T10R=(4.0*T01R-T00R)/3.0                                          IN  35
      T10I=(4.0*T01I-T00I)/3.0                                          IN  36
C                                                                       IN  37
C     TEST CONVERGENCE OF 3 POINT ROMBERG RESULT.                       IN  38
C                                                                       IN  39
      CALL TEST (T01R,T10R,TE1R,T01I,T10I,TE1I,0.)                      IN  40
      IF (TE1I-RX) 5,5,6                                                IN  41
5     IF (TE1R-RX) 8,8,6                                                IN  42
6     ZP=Z+DZ*0.25                                                      IN  43
      CALL GF (ZP,G2R,G2I)                                              IN  44
      ZP=Z+DZ*0.75                                                      IN  45
      CALL GF (ZP,G4R,G4I)                                              IN  46
      T02R=(T01R+DZOT*(G2R+G4R))*0.5                                    IN  47
      T02I=(T01I+DZOT*(G2I+G4I))*0.5                                    IN  48
      T11R=(4.0*T02R-T01R)/3.0                                          IN  49
      T11I=(4.0*T02I-T01I)/3.0                                          IN  50
      T20R=(16.0*T11R-T10R)/15.0                                        IN  51
      T20I=(16.0*T11I-T10I)/15.0                                        IN  52
C                                                                       IN  53
C     TEST CONVERGENCE OF 5 POINT ROMBERG RESULT.                       IN  54
C                                                                       IN  55
      CALL TEST (T11R,T20R,TE2R,T11I,T20I,TE2I,0.)                      IN  56
      IF (TE2I-RX) 7,7,14                                               IN  57
7     IF (TE2R-RX) 9,9,14                                               IN  58
8     SGR=SGR+T10R                                                      IN  59
      SGI=SGI+T10I                                                      IN  60
      NT=NT+2                                                           IN  61
      GO TO 10                                                          IN  62
9     SGR=SGR+T20R                                                      IN  63
      SGI=SGI+T20I                                                      IN  64
```

```
      NT=NT+1                                                          IN  65
   10 Z=Z+DZ                                                           IN  66
      IF (Z-ZEND) 11,17,17                                             IN  67
   11 G1R=G5R                                                          IN  68
      G1I=G5I                                                          IN  69
      IF (NT-NTS) 1,12,12                                              IN  70
   12 IF (NS-NX) 1,1,13                                                IN  71
C                                                                      IN  72
C     DOUBLE STEP SIZE                                                 IN  73
C                                                                      IN  74
   13 NS=NS/2                                                          IN  75
      NT=1                                                             IN  76
      GO TO 1                                                          IN  77
   14 NT=0                                                             IN  78
      IF (NS-NM) 16,15,15                                              IN  79
   15 PRINT 20, Z                                                      IN  80
      GO TO 9                                                          IN  81
C                                                                      IN  82
C     HALVE STEP SIZE                                                  IN  83
C                                                                      IN  84
   16 NS=NS*2                                                          IN  85
      FNS=NS                                                           IN  86
      DZ=S/FNS                                                         IN  87
      DZOT=DZ*0.5                                                      IN  88
      G5R=G3R                                                          IN  89
      G5I=G3I                                                          IN  90
      G3R=G2R                                                          IN  91
      G3I=G2I                                                          IN  92
      GO TO 4                                                          IN  93
   17 CONTINUE                                                         IN  94
      IF (IJ) 19,18,19                                                 IN  95
C                                                                      IN  96
C     ADD CONTRIBUTION OF NEAR SINGULARITY FOR DIAGONAL TERM           IN  97
C                                                                      IN  98
   18 SGR=2.*(SGR+ALOG((SQRT(B*B+S*S)+S)/B))                           IN  99
      SGI=2.*SGI                                                       IN 100
   19 CONTINUE                                                         IN 101
      RETURN                                                           IN 102
C                                                                      IN 103
   20 FORMAT (24H STEP SIZE LIMITED AT Z=,F10.5)                       IN 104
      END                                                              IN 105-
```

ISEGNO

PURPOSE

To determine the segment number of the m^{th} segment ordered by increasing segment numbers in the set of segments with tag numbers equal to the given tag number. With a given tag of zero, segment number m is returned.

METHOD

Search segments consecutively and check their tag numbers against a given tag.

SYMBOL DICTIONARY

I = DO loop index

ICNT = counter

ITAGI = input tag number (given tag)

M = input quantity specifying the position in the set of segments with the given tag

CODE LISTING

```
 1       FUNCTION ISEGNO (ITAGI,MX)                                      IS   1
 2 C                                                                     IS   2
 3 C     ISEGNO RETURNS THE SEGMENT NUMBER OF THE MTH SEGMENT HAVING THE IS   3
 4 C     TAG NUMBER ITAGI.  IF ITAGI=0 SEGMENT NUMBER M IS RETURNED.     IS   4
 5 C                                                                     IS   5
 6       COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 IS   6
 7      1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( IS   7
 8      2300),WLAM,IPSYM                                                 IS   8
 9       IF (MX.GT.0) GO TO 1                                            IS   9
10       PRINT 6                                                         IS  10
11       STOP                                                            IS  11
12 1     ICNT=0                                                          IS  12
13       IF (ITAGI.NE.0) GO TO 2                                         IS  13
14       ISEGNO=MX                                                       IS  14
15       RETURN                                                          IS  15
16 2     IF (N.LT.1) GO TO 4                                             IS  16
17       DO 3 I=1,N                                                      IS  17
18       IF (ITAG(I).NE.ITAGI) GO TO 3                                   IS  18
19       ICNT=ICNT+1                                                     IS  19
20       IF (ICNT.EQ.MX) GO TO 5                                         IS  20
21 3     CONTINUE                                                        IS  21
22 4     PRINT 7, ITAGI                                                  IS  22
23       STOP                                                            IS  23
24 5     ISEGNO=I                                                        IS  24
25       RETURN                                                          IS  25
26 C                                                                     IS  26
27 6     FORMAT (4X,91HCHECK DATA, PARAMETER SPECIFYING SEGMENT POSITION IN IS  27
28      1 A GROUP OF EQUAL TAGS MUST NOT BE ZERO)                        IS  28
29 7     FORMAT (///,10X,26HNO SEGMENT HAS AN ITAG OF ,I5)               IS  29
30       END                                                             IS  30-
```

LFACTR

PURPOSE

To perform the Gauss-Doolittle factorization calculations on two blocks of the matrix in core storage. This routine in conjunction with FACIO factors a matrix that is too large for core storage into an upper and lower triangular matrix using the Gauss-Doolittle technique. The factored matrix is used by LUNSCR and LTSOLV to determine the solution of the transposed matrix equation $x^T A^T = B^T$.

METHOD

The basic algorithm used in this routine is presented by Ralston in ref. 1 on pages 411-416. A brief discussion is also given under FACTR in this manual. The main difference between LFACTR and FACTR is that LFACTR is set up to perform the calculations on two blocks of columns of the transposed matrix that reside in core storage. This situation arises when the matrix is too large to fit in core at one time; thus, the matrix is divided into blocks of columns and stored on files. This matrix is then factored into a lower triangular matrix and an upper triangular matrix by the subroutines FACIO and LFACTR. The function of these two subroutines is closely tied together: LFACTR performs the mathematical computations involved in the factorization, while FACIO controls the input and output of matrix blocks in core storage, and, thus, controls the necessary block ordering input to LFACTR. For clarification of the ordering of matrix blocks during factorization, refer to FACIO.

The computations performed in LFACTR are slightly different for three matrix block conditions: (1) block numbers 1 and 2, (2) adjacent matrix blocks, and (3) non-adjacent matrix blocks. If the blocks are numbers 1 and 2, both blocks are factored, and the computations proceed exactly as in FACTR. The only difference between LFACTR and FACTR here is that the two blocks do not form a square matrix, and the row and column indices in LFACTR have not been interchanged as in FACTR. At the end of this stage, both blocks 1 and 2 are completely factored. For case 2, where the blocks are adjacent in the matrix and other than 1 and 2, the first block is assumed factored and is used to complete the factorization of the partially factored second block. The computations start with the first column of the second block and proceed as in FACTR (with the exceptions noted above). If the blocks are not adjacent (case 3), the first block is assumed factored and is used to partially

factor the second block. Computations start with the first column of the second block. Factorization cannot be completed, since values from the intervening columns are necessary.

CODING

LF20 - LF39 Initialization of loop parameters for the various matrix block conditions.

LF40 - LF99 Loop over columns to be factored or partially factored.

LF44 - LF46 Write column of A in scratch vector D.

LF49 - LF62 Computations for u_{ir} (see FACTR), where positioning for size is taken into account. The range of i is determined by the matrix blocks used.

LF69 - LF71 For case 3, the partially factored column is stored in A, and a jump to LF100 is made.

LF73 - LF87 For cases 1 and 2, the maximum value in the column is found for positioning.

LF92 - LF94 For cases 1 and 2, ℓ_{ir} (see FACTR) is calculated; limits on i are dependent on blocks.

SYMBOL DICTIONARY

A = array which contains the two blocks of columns of the transposed matrix in some state of factorization

CONJG = external routine (conjugate of complex numbers)

D = scratch vector, temporary storage of one column

DMAX = maximum value in column

ELMAG = intermediate variable

I = DO loop index

IFLG = small pivot value flag

IP = array containing positioning information

IXJ = index

IX1 = first block number, input

IX2 = second block number, input

J = DO loop index

JP1 = J + 1

J1, J2 = DO loop limits

J2P1 = J2 + 1

J2P2 = J2 + 2

K = DO loop index

L1, L2, L3 = logical variables for testing

NCOL = number of columns

NROW = number of rows

PJ, PR = intermediate variables

R = DO loop index

REAL = external routine (real part of a complex number)

R1, R2 = DO loop limits, relative column number limits for calculations

In programs using double precision accumulation in the matrix solution, the following double precision variables are used in LFACTR.

DAR1, DAI1, DAR2, DAI2 = real and imaginary parts of a number for temporary storage

DR, DI = real and imaginary vectors replacing the complex vector D in single precision programs

CONSTANT

1.E-10 = small value test

```
      SUBROUTINE LFACTR (A,NROW,IX1,IX2,IP)                              LF   1
C                                                                        LF   2
C     LFACTR PERFORMS GAUSS-DOOLITTLE MANIPULATIONS ON THE TWO BLOCKS OF LF   3
C     THE TRANSPOSED MATRIX IN CORE STORAGE.  THE GAUSS-DOOLITTLE        LF   4
C     ALGORITHM IS PRESENTED ON PAGES 411-418 OF A. RALSTON — A FIRST    LF   5
C     COURSE IN NUMERICAL ANALYSIS.  COMMENTS BELOW REFER TO COMMENTS IN LF   6
C     RALSTONS TEXT.                                                     LF   7
C                                                                        LF   8
      COMPLEX A,D,AJR                                                    LF   9
      INTEGER R,R1,R2,PJ,PR                                              LF  10
      LOGICAL L1,L2,L3                                                   LF  11
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I LF  12
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                 LF  13
      COMMON /SCRATM/ D(600)                                             LF  14
      DIMENSION A(NROW,1), IP(NROW)                                      LF  15
      IFLG=0                                                             LF  16
C                                                                        LF  17
C     INITIALIZE R1,R2,J1,J2                                             LF  18
C                                                                        LF  19
      L1=IX1.EQ.1.AND.IX2.EQ.2                                           LF  20
      L2=(IX2-1).EQ.IX1                                                  LF  21
      L3=IX2.EQ.NBLSYM                                                   LF  22
      IF (L1) GO TO 1                                                    LF  23
      GO TO 2                                                            LF  24
1     R1=1                                                               LF  25
      R2=2*NPSYM                                                         LF  26
      J1=1                                                               LF  27
      J2=-1                                                              LF  28
      GO TO 5                                                            LF  29
2     R1=NPSYM+1                                                         LF  30
      R2=2*NPSYM                                                         LF  31
      J1=(IX1-1)*NPSYM+1                                                 LF  32
      IF (L2) GO TO 3                                                    LF  33
      GO TO 4                                                            LF  34
3     J2=J1+NPSYM-2                                                      LF  35
      GO TO 5                                                            LF  36
4     J2=J1+NPSYM-1                                                      LF  37
5     IF (L3) R2=NPSYM+NLSYM                                             LF  38
      DO 16 R=R1,R2                                                      LF  39
C                                                                        LF  40
C     STEP 1                                                             LF  41
C                                                                        LF  42
      DO 6 K=J1,NROW                                                     LF  43
      D(K)=A(K,R)                                                        LF  44
6     CONTINUE                                                           LF  45
C                                                                        LF  46
C     STEPS 2 AND 3                                                      LF  47
C                                                                        LF  48
      IF (L1.OR.L2) J2=J2+1                                              LF  49
      IF (J1.GT.J2) GO TO 9                                              LF  50
      IXJ=0                                                              LF  51
      DO 8 J=J1,J2                                                       LF  52
      IXJ=IXJ+1                                                          LF  53
      PJ=IP(J)                                                           LF  54
      AJR=D(PJ)                                                          LF  55
      A(J,R)=AJR                                                         LF  56
      D(PJ)=D(J)                                                         LF  57
      JP1=J+1                                                            LF  58
      DO 7 I=JP1,NROW                                                    LF  59
      D(I)=D(I)-A(I,IXJ)*AJR                                             LF  60
7     CONTINUE                                                           LF  61
8     CONTINUE                                                           LF  62
9     CONTINUE                                                           LF  63
C                                                                        LF  64
```

```
      C     STEP 4                                                      LF  65
      C                                                                 LF  66
            J2P1=J2+1                                                   LF  67
            IF (L1.OR.L2) GO TO 11                                      LF  68
            IF (NROW.LT.J2P1) GO TO 16                                  LF  69
            DO 10 I=J2P1,NROW                                           LF  70
            A(I,R)=D(I)                                                 LF  71
   10       CONTINUE                                                    LF  72
            GO TO 16                                                    LF  73
   11       DMAX=REAL(D(J2P1)*CONJG(D(J2P1)))                           LF  74
            IP(J2P1)=J2P1                                               LF  75
            J2P2=J2+2                                                   LF  76
            IF (J2P2.GT.NROW) GO TO 13                                  LF  77
            DO 12 I=J2P2,NROW                                           LF  78
            ELMAG=REAL(D(I)*CONJG(D(I)))                                LF  79
            IF (ELMAG.LT.DMAX) GO TO 12                                 LF  80
            DMAX=ELMAG                                                  LF  81
            IP(J2P1)=I                                                  LF  82
   12       CONTINUE                                                    LF  83
   13       CONTINUE                                                    LF  84
            IF (DMAX.LT.1.E-10) IFLG=1                                  LF  85
            PR=IP(J2P1)                                                 LF  86
            A(J2P1,R)=D(PR)                                             LF  87
            D(PR)=D(J2P1)                                               LF  88
      C                                                                 LF  89
      C     STEP 5                                                      LF  90
      C                                                                 LF  91
            IF (J2P2.GT.NROW) GO TO 15                                  LF  92
            AJR=1./A(J2P1,R)                                            LF  93
            DO 14 I=J2P2,NROW                                           LF  94
            A(I,R)=D(I)*AJR                                             LF  95
   14       CONTINUE                                                    LF  96
   15       CONTINUE                                                    LF  97
            IF (IFLG.EQ.0) GO TO 16                                     LF  98
            PRINT 17, J2,DMAX                                           LF  99
            IFLG=0                                                      LF 100
   16       CONTINUE                                                    LF 101
            RETURN                                                      LF 102
      C                                                                 LF 103
   17       FORMAT (1H ,6HPIVOT(,I3,2H)=,E16.8)                         LF 104
            END                                                         LF 105-
```

LOAD

PURPOSE

To compute the impedances at a given frequency for the loading specified by LD cards.

METHOD

The value of $\lambda Z/\Delta$, where Z is the total impedance on a segment and Δ is the length of the segment, is computed for each loaded segment and stored in the array ZARRAY. The proper impedance formula is chosen by the value of the input quantity LDTYP. These computations are performed from the sequence LO74 to LO96 of the program, and the formulas are:

LDTYP = 0 (series R, L, and C):

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$Z' = \frac{\lambda Z}{\Delta} = \frac{R}{\frac{\Delta}{\lambda}} + j2\pi c \left(\frac{L}{\Delta}\right) + \frac{1}{j2\pi c \left(\frac{\Delta}{\lambda}\right)^2 \left(\frac{C}{\Delta}\right)}$$

where c is the speed of light and R, L, and C are input.

LDTYP = 1 (parallel R, L, and C; R, L, and C input):

$$Z' = \frac{1}{\left(\frac{\Delta}{\lambda}\right)\frac{1}{R} + \frac{\Delta}{j2\pi cL} + j2\pi c \left(\frac{\Delta}{\lambda}\right)^2 \left(\frac{C}{\Delta}\right)}$$

LDTYP = 2 and 3 (same as above, but R/Δ, L/Δ, C/Δ are input)

LDTYP = 4 (resistance and reactance input):

$$Z' = \frac{\text{resistance} + j\ \text{reactance}}{\frac{\Delta}{\lambda}}$$

LDTYP = 5 (call another subroutine for wire conductivity calculation)

SYMBOL DICTIONARY

ABS = external routine (absolute value of a real number)
AIMAG = external routine (imaginary part of a complex number)
CMPLX = external routine (forms a complex number)
ICHK = check flag in diagnosing data errors
ISTEP = loading card subscript
IWARN = flag checking for multiply loaded segments
JUMP = LDTYP + 1
LDTAG = tag number, input quantity
LDTAGF = input quantity
LDTAGS = LDTAG(ISTEP)
LDTAGT = input quantity
LDTYP = input quantity specifying loading type
NLOAD = number of input loading data cards
PRNT = external routine (prints the impedance data in a table)
REAL = external routine (takes the real part of a complex number)
TPCJ = $j2\pi c$, where c is the speed of light
ZARRAY = array containing $\lambda Z/\Delta$ for each segment, dimensioned to the maximum number of segments
ZINT = external routine (calculates the internal impedance of a finitely conducting wire)
ZLC, ZLI, ZLR = input quantities, the definitions are a function of the type of loading specified. For the case of series RLC (LDTYP = 0): ZLC = capacitance (farads), ZLI = inductance (henrys), and ZLR = resistance (ohms). For the remaining cases, see Part III.
ZT = $Z' = \lambda Z/\Delta$ for one segment; however, variable name is used during the calculation of this quantity

CONSTANTS

1.E-20 = floating point zero test
(0., 1.88365371E+9) = $j2\pi c$, where c is the velocity of light

```
      SUBROUTINE LOAD (LDTYP,LDTAG,LDTAGF,LDTAGT,ZLR,ZLI,ZLC)                LO   1
C                                                                            LO   2
C     LOAD CALCULATES THE IMPEDANCE OF SPECIFIED SEGMENTS FOR VARIOUS        LO   3
C     TYPES OF LOADING                                                       LO   4
C                                                                            LO   5
      COMPLEX ZARRAY,ZT,TPCJ,ZINT                                            LO   6
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300     LO   7
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX(     LO   8
     2300),WLAM,IPSYM                                                        LO   9
      COMMON /ZLOAD/ ZARRAY(300),NLOAD,NLODF                                 LO  10
      DIMENSION LDTYP(1), LDTAG(1), LDTAGF(1), LDTAGT(1), ZLR(1), ZLI(1)     LO  11
     1, ZLC(1), TPCJX(2)                                                     LO  12
      EQUIVALENCE (TPCJ,TPCJX)                                               LO  13
      DATA TPCJX/0.,1.883689855E+9/                                          LO  14
C                                                                            LO  15
C     PRINT HEADING                                                          LO  16
C                                                                            LO  17
      PRINT 25                                                               LO  18
C                                                                            LO  19
C     INITIALIZE D ARRAY, USED FOR TEMPORARY STORAGE OF LOADING              LO  20
C     INFORMATION.                                                           LO  21
C                                                                            LO  22
      DO 1 I=N2,N                                                            LO  23
    1 ZARRAY(I)=(0.,0.)                                                      LO  24
      IWARN=0                                                                LO  25
C                                                                            LO  26
C     CYCLE OVER LOADING CARDS                                               LO  27
C                                                                            LO  28
      ISTEP=0                                                                LO  29
    2 ISTEP=ISTEP+1                                                          LO  30
      IF (ISTEP.LE.NLOAD) GO TO 5                                            LO  31
      IF (IWARN.EQ.1) PRINT 26                                               LO  32
      IF (N1+2*M1.GT.0) GO TO 4                                              LO  33
      NOP=N/NP                                                               LO  34
      IF (NOP.EQ.1) GO TO 4                                                  LO  35
      DO 3 I=1,NP                                                            LO  36
      ZT=ZARRAY(I)                                                           LO  37
      L1=I                                                                   LO  38
      DO 3 L2=2,NOP                                                          LO  39
      L1=L1+NP                                                               LO  40
    3 ZARRAY(L1)=ZT                                                          LO  41
    4 RETURN                                                                 LO  42
    5 IF (LDTYP(ISTEP).LE.5) GO TO 6                                         LO  43
      PRINT 27, LDTYP(ISTEP)                                                 LO  44
      STOP                                                                   LO  45
    6 LDTAGS=LDTAG(ISTEP)                                                    LO  46
      JUMP=LDTYP(ISTEP)+1                                                    LO  47
      ICHK=0                                                                 LO  48
C                                                                            LO  49
C     SEARCH SEGMENTS FOR PROPER ITAGS                                       LO  50
C                                                                            LO  51
      L1=N2                                                                  LO  52
      L2=N                                                                   LO  53
      IF (LDTAGS.NE.0) GO TO 7                                               LO  54
      IF (LDTAGF(ISTEP).EQ.0.AND.LDTAGT(ISTEP).EQ.0) GO TO 7                 LO  55
      L1=LDTAGF(ISTEP)                                                       LO  56
      L2=LDTAGT(ISTEP)                                                       LO  57
      IF (L1.GT.N1) GO TO 7                                                  LO  58
      PRINT 28                                                               LO  59
      STOP                                                                   LO  60
    7 DO 17 I=L1,L2                                                          LO  61
      IF (LDTAGS.EQ.0) GO TO 8                                               LO  62
      IF (LDTAGS.NE.ITAG(I)) GO TO 17                                        LO  63
```

```
      IF (LDTAGF(ISTEP).EQ.0) GO TO 8                                   LO  64
      ICHK=ICHK+1                                                       LO  65
      IF (ICHK.GE.LDTAGF(ISTEP).AND.ICHK.LE.LDTAGT(ISTEP)) GO TO 9      LO  66
      GO TO 17                                                          LO  67
    8 ICHK=1                                                            LO  68
C                                                                       LO  69
C     CALCULATION OF LAMDA*IMPED. PER UNIT LENGTH, JUMP TO APPROPRIATE  LO  70
C     SECTION FOR LOADING TYPE                                          LO  71
C                                                                       LO  72
    9 GO TO (10,11,12,13,14,15), JUMP                                   LO  73
   10 ZT=ZLR(ISTEP)/SI(I)+TPCJ*ZLI(ISTEP)/(SI(I)*WLAM)                  LO  74
      IF (ABS(ZLC(ISTEP)).GT.1.E-20) ZT=ZT+WLAM/(TPCJ*SI(I)*ZLC(ISTEP)) LO  75
      GO TO 16                                                          LO  76
   11 ZT=TPCJ*SI(I)*ZLC(ISTEP)/WLAM                                     LO  77
      IF (ABS(ZLI(ISTEP)).GT.1.E-20) ZT=ZT+SI(I)*WLAM/(TPCJ*ZLI(ISTEP)) LO  78
      IF (ABS(ZLR(ISTEP)).GT.1.E-20) ZT=ZT+SI(I)/ZLR(ISTEP)             LO  79
      ZT=1./ZT                                                          LO  80
      GO TO 16                                                          LO  81
   12 ZT=ZLR(ISTEP)*WLAM+TPCJ*ZLI(ISTEP)                                LO  82
      IF (ABS(ZLC(ISTEP)).GT.1.E-20) ZT=ZT+1./(TPCJ*SI(I)*SI(I)*ZLC(ISTE LO  83
     1P))                                                               LO  84
      GO TO 16                                                          LO  85
   13 ZT=TPCJ*SI(I)*SI(I)*ZLC(ISTEP)                                    LO  86
      IF (ABS(ZLI(ISTEP)).GT.1.E-20) ZT=ZT+1./(TPCJ*ZLI(ISTEP))         LO  87
      IF (ABS(ZLR(ISTEP)).GT.1.E-20) ZT=ZT+1./(ZLR(ISTEP)*WLAM)         LO  88
      ZT=1./ZT                                                          LO  89
      GO TO 16                                                          LO  90
   14 ZT=CMPLX(ZLR(ISTEP),ZLI(ISTEP))/SI(I)                             LO  91
      GO TO 16                                                          LO  92
   15 ZT=ZINT(ZLR(ISTEP)*WLAM,BI(I))                                    LO  93
   16 IF ((ABS(REAL(ZARRAY(I)))+ABS(AIMAG(ZARRAY(I)))).GT.1.E-20) IWARN= LO  94
     1 1                                                                LO  95
      ZARRAY(I)=ZARRAY(I)+ZT                                            LO  96
   17 CONTINUE                                                          LO  97
      IF (ICHK.NE.0) GO TO 18                                           LO  98
      PRINT 28, LDTAGS                                                  LO  99
      STOP                                                              LO 100
C                                                                       LO 101
C     PRINTING THE SEGMENT LOADING DATA, JUMP TO PROPER PRINT           LO 102
C                                                                       LO 103
   18 GO TO (19,20,21,22,23,24), JUMP                                   LO 104
   19 CALL PRNT (LDTAGS,LDTAGF(ISTEP),LDTAGT(ISTEP),ZLR(ISTEP),ZLI(ISTEP LO 105
     1),ZLC(ISTEP),0.,0.,0.,7H SERIES,7)                                LO 106
      GO TO 2                                                           LO 107
   20 CALL PRNT (LDTAGS,LDTAGF(ISTEP),LDTAGT(ISTEP),ZLR(ISTEP),ZLI(ISTEP LO 108
     1),ZLC(ISTEP),0.,0.,0.,8HPARALLEL,8)                               LO 109
      GO TO 2                                                           LO 110
   21 CALL PRNT (LDTAGS,LDTAGF(ISTEP),LDTAGT(ISTEP),ZLR(ISTEP),ZLI(ISTEP LO 111
     1),ZLC(ISTEP),0.,0.,0.,18HSERIES (PER METER),18)                   LO 112
      GO TO 2                                                           LO 113
   22 CALL PRNT (LDTAGS,LDTAGF(ISTEP),LDTAGT(ISTEP),ZLR(ISTEP),ZLI(ISTEP LO 114
     1),ZLC(ISTEP),0.,0.,0.,20HPARALLEL (PER METER),20)                 LO 115
      GO TO 2                                                           LO 116
   23 CALL PRNT (LDTAGS,LDTAGF(ISTEP),LDTAGT(ISTEP),0.,0.,0.,ZLR(ISTEP), LO 117
     1ZLI(ISTEP),0.,15HFIXED IMPEDANCE,15)                              LO 118
      GO TO 2                                                           LO 119
   24 CALL PRNT (LDTAGS,LDTAGF(ISTEP),LDTAGT(ISTEP),0.,0.,0.,0.,0.,ZLR(I LO 120
     1STEP),6H  WIRE,6)                                                 LO 121
      GO TO 2                                                           LO 122
C                                                                       LO 123
   25 FORMAT (//,7X,8HLOCATION,10X,10HRESISTANCE,3X,10HINDUCTANCE,2X,11H LO 124
     1CAPACITANCE,7X,18HIMPEDANCE (OHMS),5X,12HCONDUCTIVITY,4X,4HTYPE,/, LO 125
     24X,4HTAG,10H FROM THRU,10X,4HOHMS,8X,6HHENRYS,7X,6HFARADS,8X,4HRE LO 126
     3AL,6X,9HIMAGINARY,4X,10HMHOS/METER)                               LO 127
```

```
128   26    FORMAT (/,10X,74HNOTE, SOME OF THE ABOVE SEGMENTS HAVE BEEN LOADED LO 128
129        1 TWICE - IMPEDANCES ADDED)                                        LO 129
130   27    FORMAT (/,10X,46HIMPROPER LOAD TYPE CHOOSEN, REQUESTED TYPE IS ,I3 LO 130
131        1)                                                                 LO 131
132   28    FORMAT (/,10X,50HLOADING DATA CARD ERROR, NO SEGMENT HAS AN ITAG = LO 132
133        1 ,I5)                                                             LO 133
134   29    FORMAT (63H ERROR - LOADING MAY NOT BE ADDED TO SEGMENTS IN N.G.F. LO 134
135        1 SECTION)                                                         LO 135
136         END                                                               LO 136-
```

LTSOLV

PURPOSE

To solve the matrix equation $X^R LU = B^R$, where R denotes a row vector and L and U are the lower and upper triangular matrices stored as blocks on files.

METHOD

The L and U triangular matrices are written in a square array, where the 1's on the diagonal of the L matrix are suppressed. The array is stored by blocks of columns in ascending order on file IFL1 and descending order on file IFL2. The solution procedure is as follows. First solve the equation

$$Y^R U = B^R \tag{1}$$

then

$$X^R L = Y^R , \tag{2}$$

since $X^R LU = B^R$. The solutions of equations (1) and (2) are straightforward, since both matrices are triangular. In particular for equation (1),

$$y_j^R = \frac{1}{u_{jj}} \left(b_j^R - \sum_{i=1}^{j-1} y_i^R u_{ij} \right) \qquad j = 1, \ldots, n$$

and similarly for equation (2).

Several right-hand side vectors may be stored in the two dimensional array B. The forward and backward substitution is then done on each vector in the loops from LT 23 to LT 34 and LT 43 to LT 56. This can be much faster than calling LTSOLV for each vector since the files IFL1 and IFL2 are read only once. This feature is used in computing $A^{-1}B$ for the NGF solution. It is not used with the multiple excitations for a receiving pattern or to compute the driving point interaction matrix in NETWK but could reduce the out-of-core solution time in these cases.

Row interchanges were used to position elements for size in factoring the transposed structure matrix; therefore, the elements in the solution vector X^R are not in the original locations. Using the IX array (filled by LUNSCR), the vector can be put back into the original order. The integer contained in IX(J) is the index of the original location of the parameter now in the j^{th} location. The solution vector is overwritten on the input right-hand side vector B^R.

SYMBOL DICTIONARY

A	= array for matrix blocks
B	= B^R, right-hand side and solution
I2	= number of words in a block
IFL1	= file with blocks in normal order
IFL2	= file with blocks in reversed order
IX	= solution unscramble vector
IXBLK1	= block number
J	= row index
JST	= initial value for J
K2	= number of columns in a block
KP	= column index
NEQ	= total number of equations
NRH	= number of right-hand side vectors in B
NROW	= row dimension of A (number of equations in a symmetric section)
SUM	= summation result

```
      SUBROUTINE LTSOLV (A,NROW,IX,B,NEQ,NRH,IFL1,IFL2)                  LT    1
C                                                                        LT    2
C     LTSOLV SOLVES THE MATRIX EQ. Y(R)*LU(T)=B(R) WHERE (R) DENOTES ROW LT    3
C     VECTOR AND LU(T) DENOTES THE LU DECOMPOSITION OF THE TRANSPOSE OF  LT    4
C     THE ORIGINAL COEFFICIENT MATRIX.  THE LU(T) DECOMPOSITION IS       LT    5
C     STORED ON TAPE 5 IN BLOCKS IN ASCENDING ORDER AND ON FILE 3 IN     LT    6
C     BLOCKS OF DESCENDING ORDER.                                        LT    7
C                                                                        LT    8
      COMPLEX A,B,Y,SUM                                                  LT    9
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I LT   10
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                 LT   11
      COMMON /SCRATM/ Y(600)                                             LT   12
      DIMENSION A(NROW,NROW), B(NEQ,NRH), IX(NEQ)                        LT   13
C                                                                        LT   14
C     FORWARD SUBSTITUTION                                               LT   15
C                                                                        LT   16
      I2=2*NPSYM*NROW                                                    LT   17
      DO 4 IXBLK1=1,NBLSYM                                               LT   18
      CALL BLCKIN (A,IFL1,1,I2,1,121)                                    LT   19
      K2=NPSYM                                                           LT   20
      IF (IXBLK1.EQ.NBLSYM) K2=NLSYM                                     LT   21
      JST=(IXBLK1-1)*NPSYM                                               LT   22
      DO 4 IC=1,NRH                                                      LT   23
      J=JST                                                              LT   24
      DO 3 K=1,K2                                                        LT   25
      JM1=J                                                              LT   26
      J=J+1                                                              LT   27
      SUM=(0.,0.)                                                        LT   28
      IF (JM1.LT.1) GO TO 2                                              LT   29
      DO 1 I=1,JM1                                                       LT   30
1     SUM=SUM+A(I,K)*B(I,IC)                                             LT   31
2     B(J,IC)=(B(J,IC)-SUM)/A(J,K)                                       LT   32
3     CONTINUE                                                           LT   33
4     CONTINUE                                                           LT   34
C                                                                        LT   35
C     BACKWARD SUBSTITUTION                                              LT   36
C                                                                        LT   37
      JST=NROW+1                                                         LT   38
      DO 8 IXBLK1=1,NBLSYM                                               LT   39
      CALL BLCKIN (A,IFL2,1,I2,1,122)                                    LT   40
      K2=NPSYM                                                           LT   41
      IF (IXBLK1.EQ.1) K2=NLSYM                                          LT   42
      DO 7 IC=1,NRH                                                      LT   43
      KP=K2+1                                                            LT   44
      J=JST                                                              LT   45
      DO 6 K=1,K2                                                        LT   46
      KP=KP-1                                                            LT   47
      JP1=J                                                              LT   48
      J=J-1                                                              LT   49
      SUM=(0.,0.)                                                        LT   50
      IF (NROW.LT.JP1) GO TO 6                                           LT   51
      DO 5 I=JP1,NROW                                                    LT   52
5     SUM=SUM+A(I,KP)*B(I,IC)                                            LT   53
      B(J,IC)=B(J,IC)-SUM                                                LT   54
6     CONTINUE                                                           LT   55
7     CONTINUE                                                           LT   56
8     JST=JST-K2                                                         LT   57
C                                                                        LT   58
C     UNSCRAMBLE SOLUTION                                                LT   59
C                                                                        LT   60
      DO 10 IC=1,NRH                                                     LT   61
      DO 9 I=1,NROW                                                      LT   62
      IXI=IX(I)                                                          LT   63
9     Y(IXI)=B(I,IC)                                                     LT   64
```

```
      DO 10 I=1,NROW
10    B(I,IC)=Y(I)
      RETURN
      END
```

```
LT   65
LT   66
LT   67
LT   68-
```

LUNSCR

PURPOSE

To unscramble the lower triangular matrix of the factored out-of-core matrix and to determine the appropriate ordering of the unknowns. The unscrambled factored matrix is written in blocks on file IU3 in ascending order and on file IU4 in descending order.

METHOD

During factorization by LFACTR, the elements in the lower triangular matrix L were not explicitly arranged in accordance with the row interchanges used in positioning for size during the calculations. Specifically, as the factorization proceeds by columns from left to right in the matrix, row rearrangements in the r^{th} column are not explicitly performed in the left r - 1 columns; rather, positioning information is stored in the IP array. For the in-core calculations, these rearrangements are included during the final solution (subroutine SOLVE). For the out-of-core case, rearrangement during the solution (subroutine LTSOLV) is inconvenient, since the transposed system $x^r A^t = B^r$ is being solved, where r signifies a row vector.

The procedure for unscrambling the L matrix is as follows. p_k is the positioning information contained in IP(K). Then for the r^{th} column, let t be a temporary variable:

$$t = \ell_{k,r}$$

$$\ell_{p_k,r} \text{ overwrites } \ell_{k,r}$$

$$t \text{ overwrites } \ell_{p_k,r} \quad \text{for } k = r + 1, \ldots, n - 1$$

Since row interchanges were used on the transposed matrix, the positions of the unknowns in the equations have changed. The final arrangement is determined by performing interchanges on a vector of integers. Specifically, let

$$x_i = i \quad i = 1, \ldots, n$$

then set

$$t = x_k$$

x_{p_k} overwrites x_k

t overwrites x_{p_k} for k = 1, ..., n

The integer now contained in x_i specifies the original placement of the i^{th} unknown.

SYMBOL DICTIONARY

A	= array for matrix blocks
I1	= first word of matrix block
I2	= last word of matrix block
IP	= array of pivot index data
IU2	= input file
IU3	= output file, blocks in normal order
IU4	= output file, blocks in reversed order
IX	= array x_i
IXBLK1	= block number
KA	= increment to locate the KK^{th} submatrix in case of symmetry
NOP	= number of symmetric sections
NROW	= row dimension of A

```
      SUBROUTINE LUNSCR (A,NROW,NOP,IX,IP,IU2,IU3,IU4)                  LU    1
C                                                                       LU    2
C     S/R WHICH UNSCRAMBLES, SCRAMBLED FACTORED MATRIX                  LU    3
C                                                                       LU    4
      COMPLEX A,TEMP                                                    LU    5
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I LU    6
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                LU    7
      DIMENSION A(NROW,1), IP(NROW), IX(NROW)                           LU    8
      I1=1                                                              LU    9
      I2=2*NPSYM*NROW                                                   LU   10
      NM1=NROW-1                                                        LU   11
      REWIND IU2                                                        LU   12
      REWIND IU3                                                        LU   13
      REWIND IU4                                                        LU   14
      DO 9 KK=1,NOP                                                     LU   15
      KA=(KK-1)*NROW                                                    LU   16
      DO 4 IXBLK1=1,NBLSYM                                              LU   17
      CALL BLCKIN (A,IU2,I1,I2,1,121)                                   LU   18
      K1=(IXBLK1-1)*NPSYM+2                                             LU   19
      IF (NM1.LT.K1) GO TO 3                                            LU   20
      J2=0                                                              LU   21
      DO 2 K=K1,NM1                                                     LU   22
      IF (J2.LT.NPSYM) J2=J2+1                                          LU   23
      IPK=IP(K+KA)                                                      LU   24
      DO 1 J=1,J2                                                       LU   25
      TEMP=A(K,J)                                                       LU   26
      A(K,J)=A(IPK,J)                                                   LU   27
      A(IPK,J)=TEMP                                                     LU   28
    1 CONTINUE                                                          LU   29
    2 CONTINUE                                                          LU   30
    3 CONTINUE                                                          LU   31
      CALL BLCKOT (A,IU3,I1,I2,1,122)                                   LU   32
    4 CONTINUE                                                          LU   33
      DO 5 IXBLK1=1,NBLSYM                                              LU   34
      BACKSPACE IU3                                                     LU   35
      IF (IXBLK1.NE.1) BACKSPACE IU3                                    LU   36
      CALL BLCKIN (A,IU3,I1,I2,1,123)                                   LU   37
      CALL BLCKOT (A,IU4,I1,I2,1,124)                                   LU   38
    5 CONTINUE                                                          LU   39
      DO 6 I=1,NROW                                                     LU   40
      IX(I+KA)=I                                                        LU   41
    6 CONTINUE                                                          LU   42
      DO 7 I=1,NROW                                                     LU   43
      IPI=IP(I+KA)                                                      LU   44
      IXT=IX(I+KA)                                                      LU   45
      IX(I+KA)=IX(IPI+KA)                                               LU   46
      IX(IPI+KA)=IXT                                                    LU   47
    7 CONTINUE                                                          LU   48
      IF (NOP.EQ.1) GO TO 9                                             LU   49
      NB1=NBLSYM-1                                                      LU   50
C     SKIP NB1 LOGICAL RECORDS FORWARD                                  LU   51
      DO 8 IXBLK1=1,NB1                                                 LU   52
      CALL BLCKIN (A,IU3,I1,I2,1,125)                                   LU   53
    8 CONTINUE                                                          LU   54
    9 CONTINUE                                                          LU   55
      REWIND IU2                                                        LU   56
      REWIND IU3                                                        LU   57
      REWIND IU4                                                        LU   58
      RETURN                                                            LU   59
      END                                                               LU   60-
```

MOVE

PURPOSE

To rotate and translate a previously defined structure, either moving original segments and patches or leaving the original fixed and producing new segments and patches.

METHOD

The formal parameters ROX, ROY, ROZ are the angles of rotation about the x, y, and z axes, respectively, and XS, YS, ZS are the translation distances in the x, y, and z directions. Angles are in radians, and a positive angle represents a right-hand rotation. The structure is first rotated about the x axis by ROX, then about the y axis by ROY, then about the z axis by ROZ, and finally translated by XS, YS, ZS. These operations transform a point with coordinates x, y, z to x', y', z', where

$$\begin{pmatrix} x' \\ y' \\ z' \end{pmatrix} = \begin{pmatrix} T_{11} & T_{12} & T_{13} \\ T_{21} & T_{22} & T_{23} \\ T_{31} & T_{32} & T_{33} \end{pmatrix} \begin{pmatrix} x \\ y \\ z \end{pmatrix} + \begin{pmatrix} x_s \\ y_s \\ z_s \end{pmatrix}$$

where

$T_{11} = \cos\phi \cos\theta$

$T_{12} = \cos\phi \sin\theta \sin\psi - \sin\phi \cos\psi$

$T_{13} = \cos\phi \sin\theta \cos\psi + \sin\phi \sin\psi$

$T_{21} = \sin\phi \cos\theta$

$T_{22} = \sin\phi \sin\theta \sin\psi + \cos\phi \cos\psi$

$T_{23} = \sin\phi \sin\theta \cos\psi - \cos\phi \sin\psi$

$T_{31} = -\sin\theta$

$T_{32} = \cos\theta \sin\psi$

$T_{33} = \cos\theta \cos\psi$

with

ψ = ROX

θ = ROY

ϕ = ROZ

X_s = XS

Y_s = YS

Z_s = ZS

This transformation is applied to those wire segments from segment number i_s to the last defined segment in COMMON/DATA/. Thus, if i_s is greater than 1, the segments from 1 to $i_s - 1$ are unaffected. All patches are transformed.

NRPT is the structure repetition factor. If NRPT is zero, the transformed segment and patch coordinates overwrite the original coordinates so that the structure is moved with nothing left in the original location. If NRPT is greater than zero, the transformed coordinates are written on the ends of the arrays in COMMON/DATA/ and the process repeated NRPT times so that NRPT new structures are formed, each shifted from the previous one by the specified transformation, while the original structure is unchanged.

CODING

MO18 Adjust symmetry flag if structure is rotated about the x or y axis. If the ground plane flag is also set on the GE card, symmetry will not be used in the solution.

MO19 - MO33 Compute transformation matrix.

MO37 - MO61 Transform segment coordinates.

MO63 - MO93 Transform patch coordinates.

MO94 - MO97 Set parameters to no-symmetry condition if NRPT > 0 or IX > 1.

SYMBOL DICTIONARY

ABS = external routine (absolute value)

COS = external routine (cosine)

CPH = cos ϕ

CPS = cos Ψ

CTH = cos θ

IR = DO loop index, array index for original patch

ISEGNO = external routine (searches segment tag numbers)

ITGI = increment applied to segment tag numbers as segments are transformed

ITS = i_s is the first occurring segment in COMMON/DATA/ with tag ITS

IX = i_s

I1 = lower DO loop limit for I (initially I1 = i_s)

[illegible] = increment to segment number for transformed segment

[illegible] = array index for new patch

LDI = LD + 1

NRP = upper DO loop limit for IR

NRPT = repetition factor

ROX = Ψ (radians)

ROY = θ

ROZ = ϕ

SIN = external routine (sine)

SPH = sin ϕ

SPS = sin Ψ

STH = sin θ

T1X, T1Y, T1Z = arrays containing components of $\hat{t}_1$ for patches

T2X, T2Y, T2Z = arrays containing components of $\hat{t}_2$ for patches

XI = old x coordinate

XS = x_s

XX = T_{11}

XY = T_{12}

XZ = T_{13}

X2(I) = x coordinate of end 2 of segment I

YI = old y coordinate

YS = y_s

YX = T_{21}

YY = T_{22}

YZ = T_{23}

Y2(I) = y coordinate of end 2 of segment I

ZI = old Z coordinate

ZS = Z_s

ZX = T_{31}

ZY = T_{32}

ZZ = T_{33}

Z2(I) = Z coordinate of end 2 of segment I

```
      SUBROUTINE MOVE (ROX,ROY,ROZ,XS,YS,ZS,ITS,NRPT,ITGI)                    MO   1
C                                                                             MO   2
C     SUBROUTINE MOVE MOVES THE STRUCTURE WITH RESPECT TO ITS                 MO   3
C     COORDINATE SYSTEM OR REPRODUCES STRUCTURE IN NEW POSITIONS.             MO   4
C     STRUCTURE IS ROTATED ABOUT X,Y,Z AXES BY ROX,ROY,ROZ                    MO   5
C     RESPECTIVELY, THEN SHIFTED BY XS,YS,ZS                                  MO   6
C                                                                             MO   7
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300      MO   8
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX(     MO   9
     2300),WLAM,IPSYM                                                         MO  10
      COMMON /ANGL/ SALP(300)                                                 MO  11
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1), X2(1), Y      MO  12
     12(1), Z2(1)                                                             MO  13
      EQUIVALENCE (X2(1),SI(1)), (Y2(1),ALP(1)), (Z2(1),BET(1))               MO  14
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON      MO  15
     12), (T2Z,ITAG)                                                          MO  16
      IF (ABS(ROX)+ABS(ROY).GT.1.E-10) IPSYM=IPSYM*3                          MO  17
      SPS=SIN(ROX)                                                            MO  18
      CPS=COS(ROX)                                                            MO  19
      STH=SIN(ROY)                                                            MO  20
      CTH=COS(ROY)                                                            MO  21
      SPH=SIN(ROZ)                                                            MO  22
      CPH=COS(ROZ)                                                            MO  23
      XX=CPH*CTH                                                              MO  24
      XY=CPH*STH*SPS-SPH*CPS                                                  MO  25
      XZ=CPH*STH*CPS+SPH*SPS                                                  MO  26
      YX=SPH*CTH                                                              MO  27
      YY=SPH*STH*SPS+CPH*CPS                                                  MO  28
      YZ=SPH*STH*CPS-CPH*SPS                                                  MO  29
      ZX=-STH                                                                 MO  30
      ZY=CTH*SPS                                                              MO  31
      ZZ=CTH*CPS                                                              MO  32
      NRP=NRPT                                                                MO  33
      IF (NRPT.EQ.0) NRP=1                                                    MO  34
      IF (N.LT.N2) GO TO 3                                                    MO  35
      I1=ISEGNO(ITS,1)                                                        MO  36
      IF (I1.LT.N2) I1=N2                                                     MO  37
      IX=I1                                                                   MO  38
      K=N                                                                     MO  39
      IF (NRPT.EQ.0) K=I1-1                                                   MO  40
      DO 2 IR=1,NRP                                                           MO  41
      DO 1 I=I1,N                                                             MO  42
      K=K+1                                                                   MO  43
      XI=X(I)                                                                 MO  44
      YI=Y(I)                                                                 MO  45
      ZI=Z(I)                                                                 MO  46
      X(K)=XI*XX+YI*XY+ZI*XZ+XS                                               MO  47
      Y(K)=XI*YX+YI*YY+ZI*YZ+YS                                               MO  48
      Z(K)=XI*ZX+YI*ZY+ZI*ZZ+ZS                                               MO  49
      XI=X2(I)                                                                MO  50
      YI=Y2(I)                                                                MO  51
      ZI=Z2(I)                                                                MO  52
      X2(K)=XI*XX+YI*XY+ZI*XZ+XS                                              MO  53
      Y2(K)=XI*YX+YI*YY+ZI*YZ+YS                                              MO  54
      Z2(K)=XI*ZX+YI*ZY+ZI*ZZ+ZS                                              MO  55
      BI(K)=BI(I)                                                             MO  56
      ITAG(K)=ITAG(I)+ITGI                                                    MO  57
    1 CONTINUE                                                                MO  58
      I1=N+1                                                                  MO  59
      N=K                                                                     MO  60
    2 CONTINUE                                                                MO  61
    3 IF (M.LT.M2) GO TO 6                                                    MO  62
      I1=M2                                                                   MO  63
      K=M                                                                     MO  64
```

```
      LDI=LD+1                                                          MO  65
      IF (NRPT.EQ.0) K=M1                                               MO  66
      DO 5 II=1,NRP                                                     MO  67
      DO 4 I=I1,M                                                       MO  68
      K=K+1                                                             MO  69
      IR=LDI-I                                                          MO  70
      KR=LDI-K                                                          MO  71
      XI=X(IR)                                                          MO  72
      YI=Y(IR)                                                          MO  73
      ZI=Z(IR)                                                          MO  74
      X(KR)=XI*XX+YI*XY+ZI*XZ+XS                                        MO  75
      Y(KR)=XI*YX+YI*YY+ZI*YZ+YS                                        MO  76
      Z(KR)=XI*ZX+YI*ZY+ZI*ZZ+ZS                                        MO  77
      XI=T1X(IR)                                                        MO  78
      YI=T1Y(IR)                                                        MO  79
      ZI=T1Z(IR)                                                        MO  80
      T1X(KR)=XI*XX+YI*XY+ZI*XZ                                         MO  81
      T1Y(KR)=XI*YX+YI*YY+ZI*YZ                                         MO  82
      T1Z(KR)=XI*ZX+YI*ZY+ZI*ZZ                                         MO  83
      XI=T2X(IR)                                                        MO  84
      YI=T2Y(IR)                                                        MO  85
      ZI=T2Z(IR)                                                        MO  86
      T2X(KR)=XI*XX+YI*XY+ZI*XZ                                         MO  87
      T2Y(KR)=XI*YX+YI*YY+ZI*YZ                                         MO  88
      T2Z(KR)=XI*ZX+YI*ZY+ZI*ZZ                                         MO  89
      SALP(KR)=SALP(IR)                                                 MO  90
    4 BI(KR)=BI(IR)                                                     MO  91
      I1=M+1                                                            MO  92
    5 M=K                                                               MO  93
    6 IF ((NRPT.EQ.0).AND.(IX.EQ.1)) RETURN                             MO  94
      NP=N                                                              MO  95
      MP=M                                                              MO  96
      IPSYM=0                                                           MO  97
      RETURN                                                            MO  98
      END                                                               MO  99-
```

NEFLD

PURPOSE

To compute the near electric field due to currents induced on a structure.

CODING

NE30 - NE93 Near E field due to currents on segments is computed.

NE30 - NE41 Each segment is checked to determine whether the field observation point (XOB, YOB, ZOB) falls within the segment volume. If it does, AX is set to the radius of that segment. AX is then sent to routine EFLD as the radius of the observation segment. If (XOB, YOB, ZOB) is on the axis of a segment at its center, the field calculation with AX set to the segment radius is the same as that used in filling the matrix.

NE42 - NE93 Loop computing the field contribution of each segment.

NE43 - NE50 Parameters of source segment are stored in COMMON/DATAJ/.

NE51 - NE85 When the extended thin wire approximation is used, IND1 is set to 0 if end 1 of segment I is connected to a single parallel segment of the same radius, 1 if it is a free end, and 2 if it connects to a multiple junction, a bend, or a segment of different radius. IND2 is the same for end 2. If IND1 or IND2 is 2, the extended thin wire approximation will not be used for that end.

NE87 EFLD stores the electric fields due to constant, sin ks, and cos ks currents in COMMON/DATAJ/.

NE88 - NE93 The field components are multiplied by the coefficients of the constant, sin ks, and cos ks components of the total segment current, and the field is summed.

NE95 - NE117 Near field due to patch currents is computed.

SYMBOL DICTIONARY

ACX = constant component of segment current at NE88; $\hat{t}_1$ component of patch current at NE110

AX = segment radius when the field evaluation point falls within a segment volume

B = source segment radius

BCX = sin ks component of segment current at NE89; $\hat{t}_2$ component of patch current at NE111

CCX = cos ks component of segment current at NE90

EX, EY, EZ = x, y, and z components of total electric field

EXC, EYC, EZC = E field due to a cos ks current on a segment

EXK, EYK, EZK = E field due to a constant current at NE87; E field due to the $\hat{t}_1$ component of patch current at NE114

EXS, EYX, EZS = E field due to a sin ks current at NE87; E field due to the $\hat{t}_2$ component of patch current at NE114

IP = loop index for direct and reflected field (1, 2, respectively)

T1X, T1Y, T1Z = arrays for $\hat{t}_1$

T1XJ, T1YJ, T1ZJ = $\hat{t}_1$ for source patch

T2X, T2Y, T2Z = arrays for $\hat{t}_2$

T2XJ, T2YJ, T2ZJ = $\hat{t}_2$ for source path

XI = cosine of the angle between segment I and the segment connected to its end

XOB, YOB, ZOB = field evaluation point

ZP = coordinates of the field evaluation point, z or ρ^2, in a cylindrical coordinate system centered on the source segment

CONSTANTS

0.5001 = fraction of segment length used to test whether the field evaluation point falls within a segment

0.9 = fraction of segment radius used to test whether the field evaluation point falls within a segment

0.999999 = minimum XI for extended thin wire kernel (maximum angle = 0.08 degree)

```
      SUBROUTINE NEFLD (XOB,YOB,ZOB,EX,EY,EZ)                                NE   1
C                                                                            NE   2
C     NEFLD COMPUTES THE NEAR FIELD AT SPECIFIED POINTS IN SPACE AFTER       NE   3
C     THE STRUCTURE CURRENTS HAVE BEEN COMPUTED.                             NE   4
C                                                                            NE   5
      COMPLEX EX,EY,EZ,CUR,ACX,BCX,CCX,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,E     NE   6
     1ZC,ZRATI,ZRATI2,T1,FRATI                                               NE   7
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300     NE   8
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX(     NE   9
     2300),WLAM,IPSYM                                                        NE  10
      COMMON /ANGL/ SALP(300)                                                NE  11
      COMMON /CRNT/ AIR(300),AII(300),BIR(300),BII(300),CIR(300),CII(300     NE  12
     1),CUR(900)                                                             NE  13
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ     NE  14
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                                 NE  15
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR,     NE  16
     1IPERF,T1,T2                                                            NE  17
      DIMENSION CAB(1), SAB(1), T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1),      NE  18
     1T2Z(1)                                                                 NE  19
      EQUIVALENCE (CAB,ALP), (SAB,BET)                                       NE  20
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON     NE  21
     12), (T2Z,ITAG)                                                         NE  22
      EQUIVALENCE (T1XJ,CABJ), (T1YJ,SABJ), (T1ZJ,SALPJ), (T2XJ,B), (T2Y     NE  23
     1J,IND1), (T2ZJ,IND2)                                                   NE  24
      EX=(0.,0.)                                                             NE  25
      EY=(0.,0.)                                                             NE  26
      EZ=(0.,0.)                                                             NE  27
      AX=0.                                                                  NE  28
      IF (N.EQ.0) GO TO 20                                                   NE  29
      DO 1 I=1,N                                                             NE  30
      XJ=XOB-X(I)                                                            NE  31
      YJ=YOB-Y(I)                                                            NE  32
      ZJ=ZOB-Z(I)                                                            NE  33
      ZP=CAB(I)*XJ+SAB(I)*YJ+SALP(I)*ZJ                                      NE  34
      IF (ABS(ZP).GT.0.5001*SI(I)) GO TO 1                                   NE  35
      ZP=XJ*XJ+YJ*YJ+ZJ*ZJ-ZP*ZP                                             NE  36
      XJ=BI(I)                                                               NE  37
      IF (ZP.GT.0.9*XJ*XJ) GO TO 1                                           NE  38
      AX=XJ                                                                  NE  39
      GO TO 2                                                                NE  40
1     CONTINUE                                                               NE  41
2     DO 19 I=1,N                                                            NE  42
      S=SI(I)                                                                NE  43
      B=BI(I)                                                                NE  44
      XJ=X(I)                                                                NE  45
      YJ=Y(I)                                                                NE  46
      ZJ=Z(I)                                                                NE  47
      CABJ=CAB(I)                                                            NE  48
      SABJ=SAB(I)                                                            NE  49
      SALPJ=SALP(I)                                                          NE  50
      IF (IEXK.EQ.0) GO TO 18                                                NE  51
      IPR=ICON1(I)                                                           NE  52
      IF (IPR) 3,8,4                                                         NE  53
3     IPR=-IPR                                                               NE  54
      IF (-ICON1(IPR).NE.I) GO TO 9                                          NE  55
      GO TO 6                                                                NE  56
4     IF (IPR.NE.I) GO TO 5                                                  NE  57
      IF (CABJ*CABJ+SABJ*SABJ.GT.1.E-6) GO TO 9                              NE  58
      GO TO 7                                                                NE  59
5     IF (ICON2(IPR).NE.I) GO TO 9                                           NE  60
6     XI=ABS(CABJ*CAB(IPR)+SABJ*SAB(IPR)+SALPJ*SALP(IPR))                    NE  61
      IF (XI.LT.0.999999) GO TO 9                                            NE  62
      IF (ABS(BI(IPR)/B-1.).GT.1.E-6) GO TO 9                                NE  63
7     IND1=0                                                                 NE  64
```

```
      GO TO 10                                                          NE  65
    8 IND1=1                                                            NE  66
      GO TO 10                                                          NE  67
    9 IND1=2                                                            NE  68
   10 IPR=ICON2(I)                                                      NE  69
      IF (IPR) 11,16,12                                                 NE  70
   11 IPR=-IPR                                                          NE  71
      IF (-ICON2(IPR).NE.I) GO TO 17                                    NE  72
      GO TO 14                                                          NE  73
   12 IF (IPR.NE.I) GO TO 13                                            NE  74
      IF (CABJ*CABJ+SABJ*SABJ.GT.1.E-8) GO TO 17                        NE  75
      GO TO 15                                                          NE  76
   13 IF (ICON1(IPR).NE.I) GO TO 17                                     NE  77
   14 XI=ABS(CABJ*CAB(IPR)+SABJ*SAB(IPR)+SALPJ*SALP(IPR))               NE  78
      IF (XI.LT.0.999999) GO TO 17                                      NE  79
      IF (ABS(BI(IPR)/B-1.).GT.1.E-6) GO TO 17                          NE  80
   15 IND2=0                                                            NE  81
      GO TO 18                                                          NE  82
   16 IND2=1                                                            NE  83
      GO TO 18                                                          NE  84
   17 IND2=2                                                            NE  85
   18 CONTINUE                                                          NE  86
      CALL EFLD (XOB,YOB,ZOB,AX,1)                                      NE  87
      ACX=CMPLX(AIR(I),AII(I))                                          NE  88
      BCX=CMPLX(BIR(I),BII(I))                                          NE  89
      CCX=CMPLX(CIR(I),CII(I))                                          NE  90
      EX=EX+EXK*ACX+EXS*BCX+EXC*CCX                                     NE  91
      EY=EY+EYK*ACX+EYS*BCX+EYC*CCX                                     NE  92
   19 EZ=EZ+EZK*ACX+EZS*BCX+EZC*CCX                                     NE  93
      IF (M.EQ.0) RETURN                                                NE  94
   20 JC=N                                                              NE  95
      JL=LD+1                                                           NE  96
      DO 21 I=1,M                                                       NE  97
      JL=JL-1                                                           NE  98
      S=BI(JL)                                                          NE  99
      XJ=X(JL)                                                          NE 100
      YJ=Y(JL)                                                          NE 101
      ZJ=Z(JL)                                                          NE 102
      T1XJ=T1X(JL)                                                      NE 103
      T1YJ=T1Y(JL)                                                      NE 104
      T1ZJ=T1Z(JL)                                                      NE 105
      T2XJ=T2X(JL)                                                      NE 106
      T2YJ=T2Y(JL)                                                      NE 107
      T2ZJ=T2Z(JL)                                                      NE 108
      JC=JC+3                                                           NE 109
      ACX=T1XJ*CUR(JC-2)+T1YJ*CUR(JC-1)+T1ZJ*CUR(JC)                    NE 110
      BCX=T2XJ*CUR(JC-2)+T2YJ*CUR(JC-1)+T2ZJ*CUR(JC)                    NE 111
      DO 21 IP=1,KSYMP                                                  NE 112
      IPGND=IP                                                          NE 113
      CALL UNERE (XOB,YOB,ZOB)                                          NE 114
      EX=EX+ACX*EXK+BCX*EXS                                             NE 115
      EY=EY+ACX*EYK+BCX*EYS                                             NE 116
   21 EZ=EZ+ACX*EZK+BCX*EZS                                             NE 117
      RETURN                                                            NE 118
      END                                                               NE 119-
```

NETWK

PURPOSE

To solve for the voltages and currents at the ports of non-radiating networks that are part of the antenna. This routine also is involved in the solution for current when there are no non-radiating networks, and computes the relative driving point matrix asymmetry when this option is requested.

METHOD

Driving Point Matrix Asymmetry (NT32 to NT84):

To satisfy physical reciprocity, the elements of the inverse of the interaction matrix should satisfy the condition

$$G_{ij}^{-1}/\Delta_j = G_{ji}^{-1}/\Delta_i \quad i, j = 1, \ldots, n ,$$

where Δ_i = length of segment i. This condition is not satisfied exactly, except on special structures, since the terms computed are not true reactions. The relative asymmetry of a matrix element is defined as

$$A = \left| \frac{\left(G_{ij}^{-1}/\Delta_j - G_{ji}^{-1}/\Delta_i\right)}{(G_{ij}^{-1}/\Delta_j)} \right| .$$

The code from NT32 to NT84 computes the relative asymmetries of matrix elements for i and j of all driving point segments: either voltage source driving points or network connection points. The maximum relative asymmetry is located, and the rms relative asymmetry of all elements used is computed.

LOCAL CODING STRUCTURE

NT32 - NT44 Determine numbers of segments that are network connection points.

NT46 - NT54 Determine numbers of segments that are voltage source driving points. Indices of segments with network connections or voltage sources are stored in array IPNT with no duplication of numbers.

NT59 - NT69 Compute $G_{k\ell}^{-1}/\Delta_\ell$ for k,ℓ = all segment numbers in IPNT.

NT70 - NT84 Compute relative asymmetries of elements computed above, search for maximum and compute rms asymmetry.

LOCAL SYMBOL DICTIONARY

ASA = sum of squares of relative asymmetries and rms value

ASM = Δ_{ISC1} before NT70; maximum relative asymmetry after NT69

CMN(J,I) = $G^{-1}_{k\ell}/\Delta_{\ell}$; k = IPNT(J), ℓ = IPNT(I)

CUR = temporary storage of $G^{-1}_{\ell k}/\Delta_{k}$

IPNT = array of driving point segment indices

IROW1 = number of entries in IPNT

ISC1 = temporary storage of segment index

MASYM = flag; if non-zero, matrix asymmetry is computed

NTEQ = row index of element having maximum asymmetry

NTSC = column index of element having maximum asymmetry

PWR = relative matrix asymmetry

RHS = vector for matrix solution used in obtaining $G^{-1}_{k\ell}$

Non-radiating Network Solution (NT89 to NT262):

The solution method when non-radiating networks are present is discussed in Part I.

Data for non-radiating networks is passed through the COMMON/NETCX/ where

ISEG1(I) = number of the segment to which end 1 of I^{th} two-port network is connected

ISEG2(I) = number of segment to which end 2 of I^{th} two-port network is connected

NONET = number of two-port networks for which data is given

Network parameters are contained in the arrays X11R, X11I, X12R, X12I, X22R, and X22I, and the type of network is determined by NTYP:

If NTYP is 1 -- the network parameters are the short-circuit admittance parameters of the network:

X11R, X11I = real and imaginary parts of Y_{11}

X12R, X12I = real and imaginary parts of $Y_{12} = Y_{21}$

X22R, X22I = real and imaginary parts of Y_{22}

If NTYP is 2 or 3 -- the network is a transmission line:

X11R = characteristic impedance of transmission line

X11I = length of transmission line in meters

X12R = real part of shunt admittance on end 1 of line

X12I = imaginary part of shunt admittance on end 1 of line
X22R = real part of shunt admittance on end 2 of line
X22I = imaginary part of shunt admittance on end 2 of line

If NTYP is 2 -- the transmission line runs straight between the segments with respect to the segment reference directions.

If NTYP is 3 -- the transmission line is twisted as shown in figure 8.

The short circuit admittance parameters of the transmission line, Y_{11}, Y_{12}, and Y_{22}, are computed from NT110 to NT120 in the code. When NTYP is 3, the sign of Y_{12} is reversed.

The code from NT99 to NT194 forms a loop that for each network: computes the network parameters Y_{11}, Y_{12} and Y_{22}; sorts the segment indices involved; and adds the parameters Y_{11}, Y_{12}, and Y_{22} to the appropriate network equations. The sorting procedure for the connection of end 1 of the network is described in figure 9. Decision 1 is made in the code from NT121 to NT126, decision 2 from NT128 to NT133, and decision 3 from NT138 to NT143. Segments having network connections only are assigned equation rows in the array CMN starting from the top in the order that the segments are encountered. Segments with both network and voltage source connections are assigned equation rows in CMN starting at the bottom and proceeding up. The former are eventually solved for the unknown gap voltages, while the latter are used to obtain source input admittances after the structure currents have been computed. The code from NT148 to NT174 assigns equation numbers for the connection of end 2 of the networks and sets IROW2 and ISC2.

The network short circuit parameters are added to the network equations from NT182 to NT193. The coefficient matrix is transposed in filling the CMN array, since the matrix solution routines operate on a transposed system. Hence, the first index should be considered the column number and the second index the row number. If a segment NSEG1 does not have a voltage source connected, the parameters Y_{11} and Y_{12} are added to column IROW1 at rows IROW1 and IROW2, respectively. IROW2 may be either (1) in the upper rows as part of the equations for the unknown gap voltages, or (2) if a voltage source is connected to segment NSEG2, in the lower rows for later determination of the source current. If a voltage source is connected to segment NSEG1, the

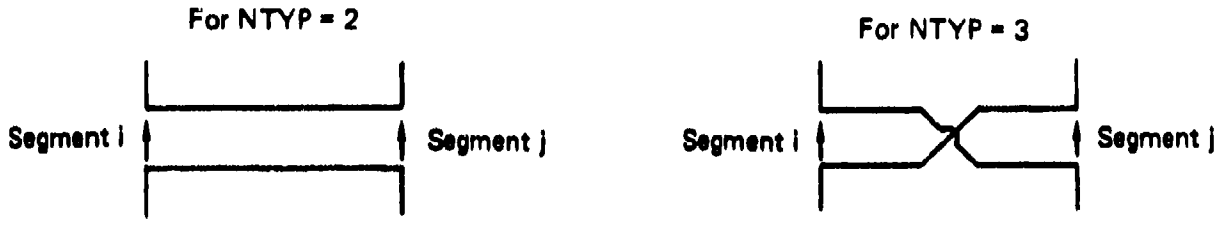


Figure 8. Options for Transmission Line Connection.

coefficients Y_{11} and Y_{12} are multiplied by the known source voltage and added to the right-hand side of the network equation in the rows IROW1 and IROW2. The parameters Y_{12} and Y_{22} are added to the equations in a similar manner.

The loop from NT199 to NT208 computes the elements of the inverse matrix G_{mn}^{-1} and adds them to the network equations. The network matrix is then factored at NT213. The code from NT218 to NT225 computes B_i = RHS(I), where

$$B_i = \sum_{j=1}^{N} G_{ij}^{-1} E_j' \qquad i = 1, \ldots N ,$$

with $(-E_j')$ being the known applied field on segment j, not including unknown voltage drops at network ports. Those elements B_i for segments in the network equations are then added to the right-hand side of the network equations. At NT229 the network equations are solved for the excitation fields due to voltage drops at the network ports. The negatives of these fields are added to the excitation vector at NT234 to NT236, completing the definition of the excitation vector E_j. The structure equations are then solved for the induced currents.

$$I_j = \sum_{j=1}^{N} G_{ij}^{-1} E_j .$$

From NT241 to NT261, the voltage, current, admittance, and power seen looking into the structure at each network port are printed. This current does not include current through any voltage sources that are connected to the port.

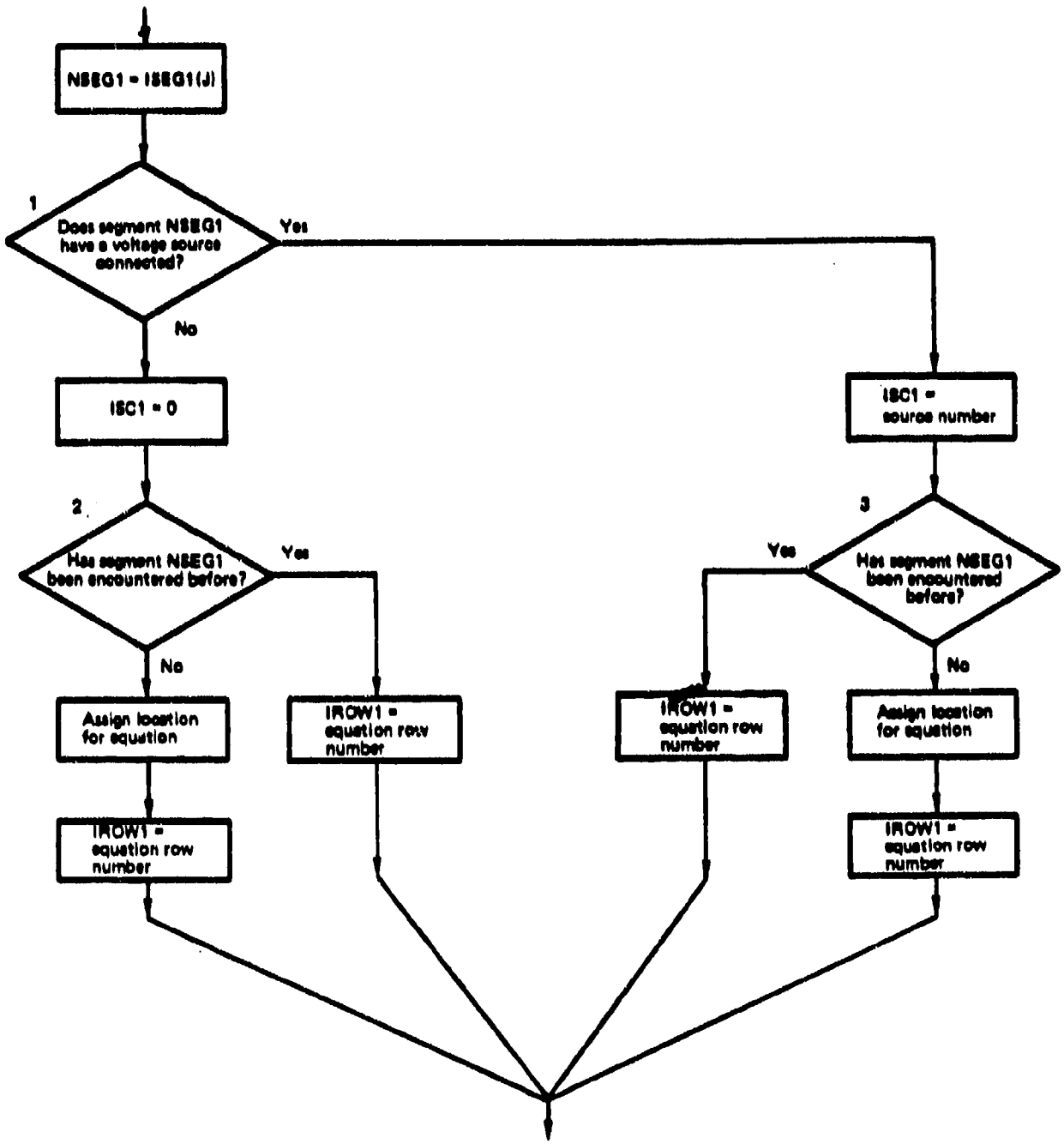


Figure 9. Sorting Procedure for Segments Having Network Connections.

The code from NT269 to NT294 computes and prints the voltage, current, admittance, and power seen by each voltage source looking into the structure and parallel connected network port, if a network is present.

After the network equations have once been set up, they can be solved for various incident fields by entering the code at NT218. If the location of voltage sources is changed, however, the equations must be recomputed.

If a structure has no non-radiating networks, the currents are computed at NT266.

SYMBOL DICTIONARY

ASA	= sum of squares of relative matrix asymmetries and rms value
ASM	= segment length and maximum relative matrix asymmetry
CABS	= external routine (magnitude of complex number)
CM	= array of matrix elements G_{ij}
CMN	= array for network equation coefficients
CMPLX	= external routine (forms complex number)
CONJG	= external routine (conjugate)
COS	= external routine (cosine)
CUR	= current
EINC	= excitation vector
FACTR	= external routine (Gauss-Doolittle matrix factoring)
FLOAT	= external routine (integer to real conversion)
I	= DO loop index
IP	= array of positioning data from factoring of CM
IPNT	= array of positioning data from factoring of CMN
IROW1	= matrix element index
IROW2	= matrix element index
ISANT	= array of segment numbers for voltage source connection
ISC1	= segment location in array ISANT
ISC2	= segment location in array ISANT
ISEG1	= number of segment to which port 1 of network is connected
ISEG2	= number of segment to which port 2 is connected
IX	= array of positioning data from factoring of CM
J	= DO loop index
MASYM	= flag to request matrix asymmetry calculation
NCOL	= number of columns in CM
NDIMN	= array dimension of CMN

NDIMNP = NDIMN + 1
NONET = number of networks
NOP = N/NP
NPRINT = flag to control printing
NROW = number of rows in CM
NSANT = number of voltage sources
NSEG1 = array of segments to which port 1 of a network connects
NSEG2 = array of segments to which port 2 of a network connects
NTEQA(I) = segment number associated with I^{th} network equation
NTSC = number of network-voltage source equations
NTSCA(I) = segment number associated with I^{th} network-voltage source equation
NTSOL = flag to indicate network equations do not need to be recomputed
NTYP(I) = type of I^{th} network
PIN = total input power from sources
PNLS = power lost in networks
PWR = power
REAL = external routine (real part of complex number)
RHNT = vector for right-hand side of network equations
RHNX = component of RHNT due to Y_{11}, Y_{12}, Y_{22} terms
RHS = vector for right-hand side of structure interaction equation
SIN = external routine (sine)
SOLVE = external routine (Gauss-Doolittle solution)
SOLVES = external routine (Gauss-Doolittle solution of CM matrix)
SQRT = external routine (square root)
TP = 2π
VLT = voltage
VSANT(I) = voltage of source on segment NSANT(I)
VSRC(I) = voltage of source on I^{th} segment in network-voltage source equations
X11I, X11R, X12I, X12R, X22I, X22R = network or transmission line specification parameters

YM1T = admittance
Y11I = imaginary part of Y_{11}
Y11R = real part of Y_{11}
Y12I = imaginary part of Y_{12}
Y12R = real part of Y_{12}
Y22I = imaginary part of Y_{22}
Y22R = real part of Y_{22}
ZPED = impedance

CONSTANTS

6.283185308 = 2π
30 = row and column dimensions of CMN
31 = (row and column dimensions of CMN) + 1

```
      SUBROUTINE NETWK (CM,CMB,CMC,CMD,IP,EINC)                          NT   1
C                                                                        NT   2
C     SUBROUTINE NETWK SOLVES FOR STRUCTURE CURRENTS FOR A GIVEN         NT   3
C     EXCITATION INCLUDING THE EFFECT OF NON-RADIATING NETWORKS IF       NT   4
C     PRESENT.                                                           NT   5
C                                                                        NT   6
      COMPLEX CMN,RHNT,YMIT,RHS,ZPED,EINC,VSANT,VLT,CUR,VSRC,RHNX,VQD,VQ NT   7
     1DS,CUX,CM,CMB,CMC,CMD                                              NT   8
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 NT   9
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( NT  10
     2300),WLAM,IPSYM                                                    NT  11
      COMMON /CRNT/ AIR(300),AII(300),BIR(300),BII(300),CIR(300),CII(300 NT  12
     1),CUR(900)                                                         NT  13
      COMMON /VSORC/ VQD(30),VSANT(30),VQDS(30),IVQD(30),ISANT(30),IQDS( NT  14
     130),NVQD,NSANT,NQDS                                                NT  15
      COMMON /NETCX/ ZPED,PIN,PNLS,NEQ,NPEQ,NEQ2,NONET,NTSOL,NPRINT,MASY NT  16
     1M,ISEG1(30),ISEG2(30),X11R(30),X11I(30),X12R(30),X12I(30),X22R(30) NT  17
     2,X22I(30),NTYP(30)                                                 NT  18
      DIMENSION EINC(1), IP(1)                                           NT  19
      DIMENSION CMN(30,30), RHNT(30), IPNT(30), NTEQA(30), NTSCA(30), RH NT  20
     1S(900), VSRC(10), RHNX(30)                                         NT  21
      DATA NDIMN,NDIMNP/30,31/,TP/6.283185308/                           NT  22
      PIN=0.                                                             NT  23
      PNLS=0.                                                            NT  24
      NEQT=NEQ+NEQ2                                                      NT  25
      IF (NTSOL.NE.0) GO TO 42                                           NT  26
      NOP=NEQ/NPEQ                                                       NT  27
      IF (MASYM.EQ.0) GO TO 14                                           NT  28
C                                                                        NT  29
C     COMPUTE RELATIVE MATRIX ASYMMETRY                                  NT  30
C                                                                        NT  31
      IROW1=0                                                            NT  32
      IF (NONET.EQ.0) GO TO 5                                            NT  33
      DO 4 I=1,NONET                                                     NT  34
      NSEG1=ISEG1(I)                                                     NT  35
      DO 3 ISC1=1,2                                                      NT  36
      IF (IROW1.EQ.0) GO TO 2                                            NT  37
      DO 1 J=1,IROW1                                                     NT  38
      IF (NSEG1.EQ.IPNT(J)) GO TO 3                                      NT  39
1     CONTINUE                                                           NT  40
2     IROW1=IROW1+1                                                      NT  41
      IPNT(IROW1)=NSEG1                                                  NT  42
3     NSEG1=ISEG2(I)                                                     NT  43
4     CONTINUE                                                           NT  44
5     IF (NSANT.EQ.0) GO TO 9                                            NT  45
      DO 8 I=1,NSANT                                                     NT  46
      NSEG1=ISANT(I)                                                     NT  47
      IF (IROW1.EQ.0) GO TO 7                                            NT  48
      DO 6 J=1,IROW1                                                     NT  49
      IF (NSEG1.EQ.IPNT(J)) GO TO 8                                      NT  50
6     CONTINUE                                                           NT  51
7     IROW1=IROW1+1                                                      NT  52
      IPNT(IROW1)=NSEG1                                                  NT  53
8     CONTINUE                                                           NT  54
9     IF (IROW1.LT.NDIMNP) GO TO 10                                      NT  55
      PRINT 59                                                           NT  56
      STOP                                                               NT  57
10    IF (IROW1.LT.2) GO TO 14                                           NT  58
      DO 12 I=1,IROW1                                                    NT  59
      ISC1=IPNT(I)                                                       NT  60
      ASM=SI(ISC1)                                                       NT  61
      DO 11 J=1,NEQT                                                     NT  62
11    RHS(J)=(0.,0.)                                                     NT  63
      RHS(ISC1)=(1.,0.)                                                  NT  64
```

```
      CALL SOLGF (CM,CMB,CMC,CMD,RHS,IP,NP,N1,N,MP,M1,M,NEQ,NEQ2)      NT  65
      CALL CABC (RHS)                                                  NT  66
      DO 12 J=1,IROW1                                                  NT  67
      ISC1=IPNT(J)                                                     NT  68
12    CMN(J,I)=RHS(ISC1)/ASM                                           NT  69
      ASM=0.                                                           NT  70
      ASA=0.                                                           NT  71
      DO 13 I=2,IROW1                                                  NT  72
      ISC1=I-1                                                         NT  73
      DO 13 J=1,ISC1                                                   NT  74
      CUX=CMN(I,J)                                                     NT  75
      PWR=CABS((CUX-CMN(J,I))/CUX)                                     NT  76
      ASA=ASA+PWR*PWR                                                  NT  77
      IF (PWR.LT.ASM) GO TO 13                                         NT  78
      ASM=PWR                                                          NT  79
      NTEQ=IPNT(I)                                                     NT  80
      NTSC=IPNT(J)                                                     NT  81
13    CONTINUE                                                         NT  82
      ASA=SQRT(ASA*2./FLOAT(IROW1*(IROW1-1)))                          NT  83
      PRINT 58, ASM,NTEQ,NTSC,ASA                                      NT  84
14    IF (NONET.EQ.0) GO TO 48                                         NT  85
C                                                                      NT  86
C     SOLUTION OF NETWORK EQUATIONS                                    NT  87
C                                                                      NT  88
      DO 15 I=1,NDIMN                                                  NT  89
      RHNX(I)=(0.,0.)                                                  NT  90
      DO 15 J=1,NDIMN                                                  NT  91
15    CMN(I,J)=(0.,0.)                                                 NT  92
      NTEQ=0                                                           NT  93
      NTSC=0                                                           NT  94
C                                                                      NT  95
C     SORT NETWORK AND SOURCE DATA AND ASSIGN EQUATION NUMBERS TO      NT  96
C     SEGMENTS.                                                        NT  97
C                                                                      NT  98
      DO 38 J=1,NONET                                                  NT  99
      NSEG1=ISEG1(J)                                                   NT 100
      NSEG2=ISEG2(J)                                                   NT 101
      IF (NTYP(J).GT.1) GO TO 16                                       NT 102
      Y11R=X11R(J)                                                     NT 103
      Y11I=X11I(J)                                                     NT 104
      Y12R=X12R(J)                                                     NT 105
      Y12I=X12I(J)                                                     NT 106
      Y22R=X22R(J)                                                     NT 107
      Y22I=X22I(J)                                                     NT 108
      GO TO 17                                                         NT 109
16    Y22R=TP*X11I(J)/WLAM                                             NT 110
      Y12R=0.                                                          NT 111
      Y12I=1./(X11R(J)*SIN(Y22R))                                      NT 112
      Y11R=X12R(J)                                                     NT 113
      Y11I=-Y12I*COS(Y22R)                                             NT 114
      Y22R=X22R(J)                                                     NT 115
      Y22I=Y11I+X22I(J)                                                NT 116
      Y11I=Y11I+X12I(J)                                                NT 117
      IF (NTYP(J).EQ.2) GO TO 17                                       NT 118
      Y12R=-Y12R                                                       NT 119
      Y12I=-Y12I                                                       NT 120
17    IF (NSANT.EQ.0) GO TO 19                                         NT 121
      DO 18 I=1,NSANT                                                  NT 122
      IF (NSEG1.NE.ISANT(I)) GO TO 18                                  NT 123
      ISC1=I                                                           NT 124
      GO TO 22                                                         NT 125
18    CONTINUE                                                         NT 126
19    ISC1=0                                                           NT 127
      IF (NTEQ.EQ.0) GO TO 21                                          NT 128
```

```
      DO 20 I=1,NTEQ                                                    NT 129
      IF (NSEG1.NE.NTEQA(I)) GO TO 20                                   NT 130
      IROW1=I                                                           NT 131
      GO TO 25                                                          NT 132
20    CONTINUE                                                          NT 133
21    NTEQ=NTEQ+1                                                       NT 134
      IROW1=NTEQ                                                        NT 135
      NTEQA(NTEQ)=NSEG1                                                 NT 136
      GO TO 25                                                          NT 137
22    IF (NTSC.EQ.0) GO TO 24                                           NT 138
      DO 23 I=1,NTSC                                                    NT 139
      IF (NSEG1.NE.NTSCA(I)) GO TO 23                                   NT 140
      IROW1=NDIMNP-I                                                    NT 141
      GO TO 25                                                          NT 142
23    CONTINUE                                                          NT 143
24    NTSC=NTSC+1                                                       NT 144
      IROW1=NDIMNP-NTSC                                                 NT 145
      NTSCA(NTSC)=NSEG1                                                 NT 146
      VSRC(NTSC)=VSANT(ISC1)                                            NT 147
25    IF (NSANT.EQ.0) GO TO 27                                          NT 148
      DO 26 I=1,NSANT                                                   NT 149
      IF (NSEG2.NE.ISANT(I)) GO TO 26                                   NT 150
      ISC2=I                                                            NT 151
      GO TO 30                                                          NT 152
26    CONTINUE                                                          NT 153
27    ISC2=0                                                            NT 154
      IF (NTEQ.EQ.0) GO TO 29                                           NT 155
      DO 28 I=1,NTEQ                                                    NT 156
      IF (NSEG2.NE.NTEQA(I)) GO TO 28                                   NT 157
      IROW2=I                                                           NT 158
      GO TO 33                                                          NT 159
28    CONTINUE                                                          NT 160
29    NTEQ=NTEQ+1                                                       NT 161
      IROW2=NTEQ                                                        NT 162
      NTEQA(NTEQ)=NSEG2                                                 NT 163
      GO TO 33                                                          NT 164
30    IF (NTSC.EQ.0) GO TO 32                                           NT 165
      DO 31 I=1,NTSC                                                    NT 166
      IF (NSEG2.NE.NTSCA(I)) GO TO 31                                   NT 167
      IROW2=NDIMNP-I                                                    NT 168
      GO TO 33                                                          NT 169
31    CONTINUE                                                          NT 170
32    NTSC=NTSC+1                                                       NT 171
      IROW2=NDIMNP-NTSC                                                 NT 172
      NTSCA(NTSC)=NSEG2                                                 NT 173
      VSRC(NTSC)=VSANT(ISC2)                                            NT 174
33    IF (NTSC+NTEQ.LT.NDIMNP) GO TO 34                                 NT 175
      PRINT 59                                                          NT 176
      STOP                                                              NT 177
C                                                                       NT 178
C     FILL NETWORK EQUATION MATRIX AND RIGHT HAND SIDE VECTOR WITH      NT 179
C     NETWORK SHORT-CIRCUIT ADMITTANCE MATRIX COEFFICIENTS.             NT 180
C                                                                       NT 181
34    IF (ISC1.NE.0) GO TO 35                                           NT 182
      CMN(IROW1,IROW1)=CMN(IROW1,IROW1)-CMPLX(Y11R,Y11I)*SI(NSEG1)      NT 183
      CMN(IROW1,IROW2)=CMN(IROW1,IROW2)-CMPLX(Y12R,Y12I)*SI(NSEG1)      NT 184
      GO TO 36                                                          NT 185
35    RHNX(IROW1)=RHNX(IROW1)+CMPLX(Y11R,Y11I)*VSANT(ISC1)/WLAM         NT 186
      RHNX(IROW2)=RHNX(IROW2)+CMPLX(Y12R,Y12I)*VSANT(ISC1)/WLAM         NT 187
36    IF (ISC2.NE.0) GO TO 37    *                                      NT 188
      CMN(IROW2,IROW2)=CMN(IROW2,IROW2)-CMPLX(Y22R,Y22I)*SI(NSEG2)      NT 189
      CMN(IROW2,IROW1)=CMN(IROW2,IROW1)-CMPLX(Y12R,Y12I)*SI(NSEG2)      NT 190
      GO TO 38                                                          NT 191
37    RHNX(IROW1)=RHNX(IROW1)+CMPLX(Y12R,Y12I)*VSANT(ISC2)/WLAM         NT 192
```

```
      RHNX(IROW2)=RHNX(IROW2)+CMPLX(Y22R,Y22I)*VSANT(ISC2)/WLAM          NT 193
38    CONTINUE                                                          NT 194
C                                                                       NT 195
C     ADD INTERACTION MATRIX ADMITTANCE ELEMENTS TO NETWORK EQUATION    NT 196
C     MATRIX                                                            NT 197
C                                                                       NT 198
      DO 41 I=1,NTEQ                                                    NT 199
      DO 39 J=1,NEQT                                                    NT 200
39    RHS(J)=(0.,0.)                                                    NT 201
      IROW1=NTEQA(I)                                                    NT 202
      RHS(IROW1)=(1.,0.)                                                NT 203
      CALL SOLGF (CM,CMB,CMC,CMD,RHS,IP,NP,N1,N,MP,M1,M,NEQ,NEQ2)       NT 204
      CALL CABC (RHS)                                                   NT 205
      DO 40 J=1,NTEQ                                                    NT 206
      IROW1=NTEQA(J)                                                    NT 207
40    CMN(I,J)=CMN(I,J)+RHS(IROW1)                                      NT 208
41    CONTINUE                                                          NT 209
C                                                                       NT 210
C     FACTOR NETWORK EQUATION MATRIX                                    NT 211
C                                                                       NT 212
      CALL FACTR (NTEQ,CMN,IPNT,NDIMN)                                  NT 213
C                                                                       NT 214
C     ADD TO NETWORK EQUATION RIGHT HAND SIDE THE TERMS DUE TO ELEMENT  NT 215
C     INTERACTIONS                                                      NT 216
C                                                                       NT 217
42    IF (NONET.EQ.0) GO TO 48                                          NT 218
      DO 43 I=1,NEQT                                                    NT 219
43    RHS(I)=EINC(I)                                                    NT 220
      CALL SOLGF (CM,CMB,CMC,CMD,RHS,IP,NP,N1,N,MP,M1,M,NEQ,NEQ2)       NT 221
      CALL CABC (RHS)                                                   NT 222
      DO 44 I=1,NTEQ                                                    NT 223
      IROW1=NTEQA(I)                                                    NT 224
44    RHNT(I)=RHNX(I)+RHS(IROW1)                                        NT 225
C                                                                       NT 226
C     SOLVE NETWORK EQUATIONS                                           NT 227
C                                                                       NT 228
      CALL SOLVE (NTEQ,CMN,IPNT,RHNT,NDIMN)                             NT 229
C                                                                       NT 230
C     ADD FIELDS DUE TO NETWORK VOLTAGES TO ELECTRIC FIELDS APPLIED TO  NT 231
C     STRUCTURE AND SOLVE FOR INDUCED CURRENT                           NT 232
C                                                                       NT 233
      DO 45 I=1,NTEQ                                                    NT 234
      IROW1=NTEQA(I)                                                    NT 235
45    EINC(IROW1)=EINC(IROW1)-RHNT(I)                                   NT 236
      CALL SOLGF (CM,CMB,CMC,CMD,EINC,IP,NP,N1,N,MP,M1,M,NEQ,NEQ2)      NT 237
      CALL CABC (EINC)                                                  NT 238
      IF (NPRINT.EQ.0) PRINT 61                                         NT 239
      IF (NPRINT.EQ.0) PRINT 60                                         NT 240
      DO 46 I=1,NTEQ                                                    NT 241
      IROW1=NTEQA(I)                                                    NT 242
      VLT=RHNT(I)*SI(IROW1)*WLAM                                        NT 243
      CUX=EINC(IROW1)*WLAM                                              NT 244
      YMIT=CUX/VLT                                                      NT 245
      ZPED=VLT/CUX                                                      NT 246
      IROW2=ITAG(IROW1)                                                 NT 247
      PWR=.5*REAL(VLT*CONJG(CUX))                                       NT 248
      PNLS=PNLS-PWR                                                     NT 249
46    IF (NPRINT.EQ.0) PRINT 62, IROW2,IROW1,VLT,CUX,ZPED,YMIT,PWR      NT 250
      IF (NTSC.EQ.0) GO TO 49                                           NT 251
      DO 47 I=1,NTSC                                                    NT 252
      IROW1=NTSCA(I)                                                    NT 253
      VLT=VSRC(I)                                                       NT 254
      CUX=EINC(IROW1)*WLAM                                              NT 255
      YMIT=CUX/VLT                                                      NT 256
```

```
      ZPED=VLT/CUX                                                          NT 257
      IROW2=ITAG(IROW1)                                                     NT 258
      PWR=.5*REAL(VLT*CONJG(CUX))                                           NT 259
      PNLS=PNLS-PWR                                                         NT 260
47    IF (NPRINT.EQ.0) PRINT 62, IROW2,IROW1,VLT,CUX,ZPED,YMIT,PWR          NT 261
      GO TO 49                                                              NT 262
C                                                                           NT 263
C     SOLVE FOR CURRENTS WHEN NO NETWORKS ARE PRESENT                       NT 264
C                                                                           NT 265
48    CALL SOLGF (CM,CMB,CMC,CMD,EINC,IP,NP,N1,N,MP,M1,M,NEQ,NEQ2)          NT 266
      CALL CABC (EINC)                                                      NT 267
      NTSC=0                                                                NT 268
49    IF (NSANT+NVQD.EQ.0) RETURN                                           NT 269
      PRINT 63                                                              NT 270
      PRINT 60                                                              NT 271
      IF (NSANT.EQ.0) GO TO 56                                              NT 272
      DO 55 I=1,NSANT                                                       NT 273
      ISC1=ISANT(I)                                                         NT 274
      VLT=VSANT(I)                                                          NT 275
      IF (NTSC.EQ.0) GO TO 51                                               NT 276
      DO 50 J=1,NTSC                                                        NT 277
      IF (NTSCA(J).EQ.ISC1) GO TO 52                                        NT 278
50    CONTINUE                                                              NT 279
51    CUX=EINC(ISC1)*WLAM                                                   NT 280
      IROW1=0                                                               NT 281
      GO TO 54                                                              NT 282
52    IROW1=NDIMNP-J                                                        NT 283
      CUX=RHNX(IROW1)                                                       NT 284
      DO 53 J=1,NTEQ                                                        NT 285
53    CUX=CUX-CMN(J,IROW1)*RHNT(J)                                          NT 286
      CUX=(EINC(ISC1)+CUX)*WLAM                                             NT 287
54    YMIT=CUX/VLT                                                          NT 288
      ZPED=VLT/CUX                                                          NT 289
      PWR=.5*REAL(VLT*CONJG(CUX))                                           NT 290
      PIN=PIN+PWR                                                           NT 291
      IF (IROW1.NE.0) PNLS=PNLS+PWR                                         NT 292
      IROW2=ITAG(ISC1)                                                      NT 293
55    PRINT 62, IROW2,ISC1,VLT,CUX,ZPED,YMIT,PWR                            NT 294
56    IF (NVQD.EQ.0) RETURN                                                 NT 295
      DO 57 I=1,NVQD                                                        NT 296
      ISC1=IVQD(I)                                                          NT 297
      VLT=VQD(I)                                                            NT 298
      CUX=CMPLX(AIR(ISC1),AII(ISC1))                                        NT 299
      YMIT=CMPLX(BIR(ISC1),BII(ISC1))                                       NT 300
      ZPED=CMPLX(CIR(ISC1),CII(ISC1))                                       NT 301
      PWR=SI(ISC1)*TP*.5                                                    NT 302
      CUX=(CUX-YMIT*SIN(PWR)+ZPED*COS(PWR))*WLAM                            NT 303
      YMIT=CUX/VLT                                                          NT 304
      ZPED=VLT/CUX                                                          NT 305
      PWR=.5*REAL(VLT*CONJG(CUX))                                           NT 306
      PIN=PIN+PWR                                                           NT 307
      IROW2=ITAG(ISC1)                                                      NT 308
57    PRINT 64, IROW2,ISC1,VLT,CUX,ZPED,YMIT,PWR                            NT 309
      RETURN                                                                NT 310
C                                                                           NT 311
58    FORMAT (///,3X,47HMAXIMUM RELATIVE ASYMMETRY OF THE DRIVING POINT,    NT 312
     121H ADMITTANCE MATRIX IS,E10.3,13H FOR SEGMENTS,I5,4H AND,I5,/,3X,    NT 313
     225HRMS RELATIVE ASYMMETRY IS,E10.3)                                   NT 314
59    FORMAT (1X,44HERROR - - NETWORK ARRAY DIMENSIONS TOO SMALL)           NT 315
60    FORMAT (/,3X,3HTAG,3X,4HSEG.,4X,15HVOLTAGE (VOLTS),9X,14HCURRENT (    NT 316
     1AMPS),9X,16HIMPEDANCE (OHMS),8X,17HADMITTANCE (MHOS),8X,5HPOWER,/,    NT 317
     223X,3HNO.,3X,3HNO.,4X,4HREAL,8X,5HIMAG.,3(7X,4HREAL,8X,5HIMAG.),5X,   NT 318
     337H(WATTS))                                                           NT 319
61    FORMAT (///,27X,66H- - - STRUCTURE EXCITATION DATA AT NETWORK CONN    NT 320
```

```
      1ECTION POINTS - - -)                                                  NT 321
62     FORMAT (2(1X,I5),9E12.5)                                              NT 322
63     FORMAT (///,42X,36H- - - ANTENNA INPUT PARAMETERS - - -)              NT 323
64     FORMAT (1X,I5,2H *,I4,9E12.5)                                         NT 324
       END                                                                   NT 325-
```

NFFAT

PURPOSE

To compute and print the near E or H field over a range of points.

METHOD

The range of points in rectangular or spherical coordinates is obtained from parameters in COMMON/FPAT/. Subroutine NEFLD is called for near E field and NHFLD is called for near H field.

SYMBOL DICTIONARY

CPH	= cos ϕ
CTH	= cos θ
DXNR	= increment for x in rectangular coordinates or R in spherical coordinates
DYNR	= increment for y in rectangular coordinates or ϕ in spherical coordinates
DZNR	= increment for z in rectangular coordinates or θ in spherical coordinates
EX, EY, EZ	= x, y and z components of E or H
NEAR	= 0 for rectangular coordinates 1 for spherical coordinates
NFEH	= 0 for near E field 1 for near H field
NRX, NRY, NRZ	= number of values for x, y and z or R, ϕ, θ
SPH	= sin ϕ
STH	= sin θ
TA	= $\pi/180$
XNR	= initial x or R
XNRT	= x or R
XOB	= x
YNR	= initial y or ϕ
YNRT	= y or ϕ
YOB	= y
ZNR	= initial z or θ
ZNRT	= z or θ
ZOB	= z

```
      SUBROUTINE NFPAT                                                  NP   1
C     COMPUTE NEAR E OR H FIELDS OVER A RANGE OF POINTS                 NP   2
      COMPLEX EX,EY,EZ                                                  NP   3
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 NP   4
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( NP   5
     2300),WLAM,IPSYM                                                   NP   6
      COMMON /FPAT/ NTH,NPH,IPD,IAVP,INOR,IAX,THETS,PHIS,DTH,DPH,RFLD,GN NP   7
     1OR,CLT,CHT,EPSR2,SIG2,IXTYP,XPR6,PINR,PNLR,PLOSS,NEAR,NFEH,NRX,NRY NP   8
     2,NRZ,XNR,YNR,ZNR,DXNR,DYNR,DZNR                                   NP   9
      DATA TA/1.745329252E-02/                                          NP  10
      IF (NFEH.EQ.1) GO TO 1                                            NP  11
      PRINT 10                                                          NP  12
      GO TO 2                                                           NP  13
    1 PRINT 12                                                          NP  14
    2 ZNRT=ZNR-DZNR                                                     NP  15
      DO 9 I=1,NRZ                                                      NP  16
      ZNRT=ZNRT+DZNR                                                    NP  17
      IF (NEAR.EQ.0) GO TO 3                                            NP  18
      CTH=COS(TA*ZNRT)                                                  NP  19
      STH=SIN(TA*ZNRT)                                                  NP  20
    3 YNRT=YNR-DYNR                                                     NP  21
      DO 9 J=1,NRY                                                      NP  22
      YNRT=YNRT+DYNR                                                    NP  23
      IF (NEAR.EQ.0) GO TO 4                                            NP  24
      CPH=COS(TA*YNRT)                                                  NP  25
      SPH=SIN(TA*YNRT)                                                  NP  26
    4 XNRT=XNR-DXNR                                                     NP  27
      DO 9 KK=1,NRX                                                     NP  28
      XNRT=XNRT+DXNR                                                    NP  29
      IF (NEAR.EQ.0) GO TO 5                                            NP  30
      XOB=XNRT*STH*CPH                                                  NP  31
      YOB=XNRT*STH*SPH                                                  NP  32
      ZOB=XNRT*CTH                                                      NP  33
      GO TO 6                                                           NP  34
    5 XOB=XNRT                                                          NP  35
      YOB=YNRT                                                          NP  36
      ZOB=ZNRT                                                          NP  37
    6 TMP1=XOB/WLAM                                                     NP  38
      TMP2=YOB/WLAM                                                     NP  39
      TMP3=ZOB/WLAM                                                     NP  40
      IF (NFEH.EQ.1) GO TO 7                                            NP  41
      CALL NEFLD (TMP1,TMP2,TMP3,EX,EY,EZ)                              NP  42
      GO TO 8                                                           NP  43
    7 CALL NHFLD (TMP1,TMP2,TMP3,EX,EY,EZ)                              NP  44
    8 TMP1=CABS(EX)                                                     NP  45
      TMP2=CANG(EX)                                                     NP  46
      TMP3=CABS(EY)                                                     NP  47
      TMP4=CANG(EY)                                                     NP  48
      TMP5=CABS(EZ)                                                     NP  49
      TMP6=CANG(EZ)                                                     NP  50
      PRINT 11, XOB,YOB,ZOB,TMP1,TMP2,TMP3,TMP4,TMP5,TMP6               NP  51
    9 CONTINUE                                                          NP  52
      RETURN                                                            NP  53
C                                                                       NP  54
   10 FORMAT (///,35X,32H- - - NEAR ELECTRIC FIELDS - - -,//,12X,14H- L NP  55
     1OCATION -,21X,8H- EX -,15X,8H- EY -,15X,8H- EZ -,/,8X,1HX,1 NP  56
     20X,1HY,10X,1HZ,10X,9HMAGNITUDE,3X,5HPHASE,6X,9HMAGNITUDE,3X,5HPHAS NP  57
     3E,6X,9HMAGNITUDE,3X,5HPHASE,/,6X,6HMETERS,5X,6HMETERS,5X,6HMETERS, NP  58
     48X,7HVOLTS/M,3X,7HDEGREES,6X,7HVOLTS/M,3X,7HDEGREES,6X,7HVOLTS/M,3 NP  59
     5X,7HDEGREES)                                                      NP  60
   11 FORMAT (2X,3(2X,F9.4),1X,3(3X,E11.4,2X,F7.2))                     NP  61
   12 FORMAT (///,35X,32H- - - NEAR MAGNETIC FIELDS - - -,//,12X,14H- L NP  62
     1OCATION -,21X,8H- HX -,15X,8H- HY -,15X,8H- HZ -,/,8X,1HX,1 NP  63
     20X,1HY,10X,1HZ,10X,9HMAGNITUDE,3X,5HPHASE,6X,9HMAGNITUDE,3X,5HPHAS NP  64
```

```
      3E.6X,9HMAGNITUDE,3X,5HPHASE,/,6X,6HMETERS,5X,6HMETERS,5X,6HMETERS,  NP  65
      49X,6HAMPS/M,3X,7HDEGREES,7X,6HAMPS/M,3X,7HDEGREES,7X,6HAMPS/M,3X,7  NP  66
      5HDEGREES)                                                           NP  67
       END                                                                 NP  68
```

NHFLD

PURPOSE

To compute the near magnetic field due to currents induced on a structure.

CODING

NH28 - NH56 Near H field due to currents on segments is computed.

NH29 - NH40 Each segment is checked to determine whether the field observation point (XOB, YOB, ZOB) falls within the segment volume. If it does, AX is set to the radius of that segment. AX is then sent to routine HSFLD as the radius of the observation segment to avoid a singularity in the field.

NH41 - NH56 Loop computing the field contribution of each segment.

NH42 - NH49 Parameters of source segment are stored in COMMON/DATAJ/.

NH50 HSFLD stores the magnetic field due to constant, sin ks, and cos ks currents in COMMON/DATAJ/.

NH54 - NH56 The field components are multiplied by the coefficients of the constant, sin ks, and cos ks components of the total segment current, and the field is summed.

NH58 - NH78 Near H fields due to patch currents are computed.

NH62 - NH71 Parameters of source patch are set in COMMON/DATAJ/.

NH72 H field is computed by HINTG.

NH76 - NH78 H fields due to $\hat{t}_1$ and $\hat{t}_2$ current components are multiplied by the current strengths and summed.

SYMBOL DICTIONARY

ACX = constant component of the segment current at NH51; $\hat{t}_1$ component of patch current at NH74

AX = segment radius when the field evaluation point falls within a segment volume

BCX = sin ks component of segment current at NH52; $\hat{t}_2$ component of patch current at NH75

CCX = cos ks component of segment current at NH53

HX, HY, HZ = total H field

T1X, T1Y, T1Z = arrays for $\hat{t}_1$

T1XJ, T1YJ, T1ZJ = $\hat{t}_1$ for patch I

T2X, T2Y, T2Z = arrays for $\hat{t}_2$

T2XJ, T2YJ, T2ZJ = $\hat{t}_2$ for patch I

XOB, YOB, ZOB = field evaluation point

ZP = coordinates of the field evaluation point, z or ρ^2, in a cylindrical coordinate system centered on the source segment.

CONSTANTS

0.5001 = fraction of segment length used to test whether the field evaluation point falls within a segment

0.9 = fraction of segment radius used to test whether the field evaluation point falls within a segment

```
      SUBROUTINE NHFLD (XOB,YOB,ZOB,HX,HY,HZ)                           NH   1
C                                                                       NH   2
C     NHFLD COMPUTES THE NEAR FIELD AT SPECIFIED POINTS IN SPACE AFTER  NH   3
C     THE STRUCTURE CURRENTS HAVE BEEN COMPUTED.                        NH   4
C                                                                       NH   5
      COMPLEX HX,HY,HZ,CUR,ACX,BCX,CCX,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,E NH   6
     12C                                                                NH   7
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 NH   8
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( NH   9
     2300),WLAM,IPSYM                                                   NH  10
      COMMON /ANGL/ SALP(300)                                           NH  11
      COMMON /CRNT/ AIR(300),AII(300),BIR(300),BII(300),CIR(300),CII(300 NH  12
     1),CUR(900)                                                        NH  13
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ NH  14
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                           NH  15
      DIMENSION CAB(1), SAB(1)                                          NH  16
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1), XS(1), Y NH  17
     1S(1), ZS(1)                                                       NH  18
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON NH  19
     12), (T2Z,ITAG), (XS,X), (YS,Y), (ZS,Z)                           NH  20
      EQUIVALENCE (T1XJ,CABJ), (T1YJ,SABJ), (T1ZJ,SALPJ), (T2XJ,B), (T2Y NH  21
     1J,IND1), (T2ZJ,IND2)                                             NH  22
      EQUIVALENCE (CAB,ALP), (SAB,BET)                                  NH  23
      HX=(0.,0.)                                                        NH  24
      HY=(0.,0.)                                                        NH  25
      HZ=(0.,0.)                                                        NH  26
      AX=0.                                                             NH  27
      IF (N.EQ.0) GO TO 4                                               NH  28
      DO 1 I=1,N                                                        NH  29
      XJ=XOB-X(I)                                                       NH  30
      YJ=YOB-Y(I)                                                       NH  31
      ZJ=ZOB-Z(I)                                                       NH  32
      ZP=CAB(I)*XJ+SAB(I)*YJ+SALP(I)*ZJ                                 NH  33
      IF (ABS(ZP).GT.0.5001*SI(I)) GO TO 1                              NH  34
      ZP=XJ*XJ+YJ*YJ+ZJ*ZJ-ZP*ZP                                        NH  35
      XJ=BI(I)                                                          NH  36
      IF (ZP.GT.0.9*XJ*XJ) GO TO 1                                      NH  37
      AX=XJ                                                             NH  38
      GO TO 2                                                           NH  39
1     CONTINUE                                                          NH  40
2     DO 3 I=1,N                                                        NH  41
      S=SI(I)                                                           NH  42
      B=BI(I)                                                           NH  43
      XJ=X(I)                                                           NH  44
      YJ=Y(I)                                                           NH  45
      ZJ=Z(I)                                                           NH  46
      CABJ=CAB(I)                                                       NH  47
      SABJ=SAB(I)                                                       NH  48
      SALPJ=SALP(I)                                                     NH  49
      CALL HSFLD (XOB,YOB,ZOB,AX)                                       NH  50
      ACX=CMPLX(AIR(I),AII(I))                                          NH  51
      BCX=CMPLX(BIR(I),BII(I))                                          NH  52
      CCX=CMPLX(CIR(I),CII(I))                                          NH  53
      HX=HX+EXK*ACX+EXS*BCX+EXC*CCX                                     NH  54
      HY=HY+EYK*ACX+EYS*BCX+EYC*CCX                                     NH  55
3     HZ=HZ+EZK*ACX+EZS*BCX+EZC*CCX                                     NH  56
      IF (M.EQ.0) RETURN                                                NH  57
4     JC=N                                                              NH  58
      JL=LD+1                                                           NH  59
      DO 5 I=1,M                                                        NH  60
      JL=JL-1                                                           NH  61
      S=BI(JL)                                                          NH  62
      XJ=X(JL)                                                          NH  63
      YJ=Y(JL)                                                          NH  64
```

```
      ZJ=Z(JL)                                                          NH  65
      T1XJ=T1X(JL)                                                      NH  66
      T1YJ=T1Y(JL)                                                      NH  67
      T1ZJ=T1Z(JL)                                                      NH  68
      T2XJ=T2X(JL)                                                      NH  69
      T2YJ=T2Y(JL)                                                      NH  70
      T2ZJ=T2Z(JL)                                                      NH  71
      CALL HINTG (XOB,YOB,ZOB)                                          NH  72
      JC=JC+3                                                           NH  73
      ACX=T1XJ*CUR(JC-2)+T1YJ*CUR(JC-1)+T1ZJ*CUR(JC)                    NH  74
      BCX=T2XJ*CUR(JC-2)+T2YJ*CUR(JC-1)+T2ZJ*CUR(JC)                    NH  75
      HX=HX+ACX*EXK+BCX*EXS                                             NH  76
      HY=HY+ACX*EYK+BCX*EYS                                             NH  77
    5 HZ=HZ+ACX*EZK+BCX*EZS                                             NH  78
      RETURN                                                            NH  79
      END                                                               NH  80-
```

PATCH (entry SUBPH)

PURPOSE

To generate patch data for surfaces.

METHOD

The code from PA14 to PA129 generates data for a single new patch or multiple patches. There are four options for defining a single patch, as illustrated in Figure 5 of Part III. For a single patch, NX is zero and NY is NS + 1 where NS is the parameter from the SP input card and is shown on Figure 5. Rectangular, triangular or quadrilateral patches are defined by the coordinates of three or four corners in the parameters X1 though Z4. In the arbitrary shape option (Figure 5A in Part III) the center of the patch is X1, Y1, Z1; α is X2; β is Y2; and the area is Z2. The patch data is stored in COMMON/DATA/ from the top of the arrays downward (see Section III).

The code from PA131 to PA190 divides a patch into four patches and is used when a wire connects to a patch. If NY is equal to zero the patch NX is divided into four patches that become patches NX through NX + 3. Patches following NX are shifted in the arrays in COMMON/DATA/ to leave space for the three additional patches. If NY is greater than zero, patch NX is left in the arrays but four new patches to replace it are added to the end of the arrays. The z coordinate of patch NX is then changed to 10,000 at PA189.

SYMBOL DICTIONARY

MI	= array index for patch data
MIA	= array index for patch data
NTP	= patch type (NY for a single patch)
NX	= zero for a single patch. For multiple patches NX is defined in Figure 6 of Part III. After ENTRY SUBPH, NX is the number of the patch to be divided
S1X, S1Y, S1Z	= vector from corner 1 to corner 2
S2X, S2Y, S2Z	= vector from corner 2 to corner 3
SALN	= $\pm$1 from array SALP
SALPN	= factor in computing center of mass of quadrilateral

XA = $|\bar{S}_1 \times \bar{S}_2|$ = area of rectangle or twice area of triangle (PA53)

XN2, YN2, ZN2 = $\bar{S}_3 \times \bar{S}_4$ at PA79 to PA81. Line PA89 checks that the four corners are coplanar by the test

$(\bar{S}_1 \times \bar{S}_2).(\bar{S}_3 \times \bar{S}_4)/|\bar{S}_1 \times \bar{S}_2||\bar{S}_3 \times \bar{S}_4| > 0.9998$

XNV, YNV, ZNV = unit vector normal to the patch at PA54 to PA56

XS, YS, ZS = patch center at PA151 to PA153

XST = $|\bar{S}_1 \times \bar{S}_2|$ at PA57

CONSTANTS

0.9998 ≈ cos(1.°) in test for planar patch

```
      SUBROUTINE PATCH (NX,NY,X1,Y1,Z1,X2,Y2,Z2,X3,Y3,Z3,X4,Y4,Z4)
C     PATCH GENERATES AND MODIFIES PATCH GEOMETRY DATA
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX(
     2300),WLAM,IPSYM
      COMMON /ANGL/ SALP(300)
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1)
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON
     12), (T2Z,ITAG)
C     NEW PATCHES.  FOR NX=0, NY=1,2,3,4 PATCH IS (RESPECTIVELY)
C     ARBITRARY, RECTAGULAR, TRIANGULAR, OR QUADRILATERAL.
C     FOR NX AND NY .GT. 0 A RECTANGULAR SURFACE IS PRODUCED WITH
C     NX BY NY RECTANGULAR PATCHES.
      M=M+1
      MI=LD+1-M
      NTP=NY
      IF (NX.GT.0) NTP=2
      IF (NTP.GT.1) GO TO 2
      X(MI)=X1
      Y(MI)=Y1
      Z(MI)=Z1
      BI(MI)=Z2
      ZNV=COS(X2)
      XNV=ZNV*COS(Y2)
      YNV=ZNV*SIN(Y2)
      ZNV=SIN(X2)
      XA=SQRT(XNV*XNV+YNV*YNV)
      IF (XA.LT.1.E-6) GO TO 1
      T1X(MI)=-YNV/XA
      T1Y(MI)=XNV/XA
      T1Z(MI)=0.
      GO TO 6
1     T1X(MI)=1.
      T1Y(MI)=0.
      T1Z(MI)=0.
      GO TO 6
2     S1X=X2-X1
      S1Y=Y2-Y1
      S1Z=Z2-Z1
      S2X=X3-X2
      S2Y=Y3-Y2
      S2Z=Z3-Z2
      IF (NX.EQ.0) GO TO 3
      S1X=S1X/NX
      S1Y=S1Y/NX
      S1Z=S1Z/NX
      S2X=S2X/NY
      S2Y=S2Y/NY
      S2Z=S2Z/NY
3     XNV=S1Y*S2Z-S1Z*S2Y
      YNV=S1Z*S2X-S1X*S2Z
      ZNV=S1X*S2Y-S1Y*S2X
      XA=SQRT(XNV*XNV+YNV*YNV+ZNV*ZNV)
      XNV=XNV/XA
      YNV=YNV/XA
      ZNV=ZNV/XA
      XST=SQRT(S1X*S1X+S1Y*S1Y+S1Z*S1Z)
      T1X(MI)=S1X/XST
      T1Y(MI)=S1Y/XST
      T1Z(MI)=S1Z/XST
      IF (NTP.GT.2) GO TO 4
      X(MI)=X1+.5*(S1X+S2X)
      Y(MI)=Y1+.5*(S1Y+S2Y)
      Z(MI)=Z1+.5*(S1Z+S2Z)
```

```
      BI(MI)=XA                                                          PA  65
      GO TO 6                                                            PA  66
 4    IF (NTP.EQ.4) GO TO 5                                              PA  67
      X(MI)=(X1+X2+X3)/3.                                                PA  68
      Y(MI)=(Y1+Y2+Y3)/3.                                                PA  69
      Z(MI)=(Z1+Z2+Z3)/3.                                                PA  70
      BI(MI)=.5*XA                                                       PA  71
      GO TO 6                                                            PA  72
 5    S1X=X3-X1                                                          PA  73
      S1Y=Y3-Y1                                                          PA  74
      S1Z=Z3-Z1                                                          PA  75
      S2X=X4-X1                                                          PA  76
      S2Y=Y4-Y1                                                          PA  77
      S2Z=Z4-Z1                                                          PA  78
      XN2=S1Y*S2Z-S1Z*S2Y                                                PA  79
      YN2=S1Z*S2X-S1X*S2Z                                                PA  80
      ZN2=S1X*S2Y-S1Y*S2X                                                PA  81
      XST=SQRT(XN2*XN2+YN2*YN2+ZN2*ZN2)                                  PA  82
      SALPN=1./(3.*(XA+XST))                                             PA  83
      X(MI)=(XA*(X1+X2+X3)+XST*(X1+X3+X4))*SALPN                         PA  84
      Y(MI)=(XA*(Y1+Y2+Y3)+XST*(Y1+Y3+Y4))*SALPN                         PA  85
      Z(MI)=(XA*(Z1+Z2+Z3)+XST*(Z1+Z3+Z4))*SALPN                         PA  86
      BI(MI)=.5*(XA+XST)                                                 PA  87
      S1X=(XNV*XN2+YNV*YN2+ZNV*ZN2)/XST                                  PA  88
      IF (S1X.GT.0.9998) GO TO 6                                         PA  89
      PRINT 14                                                           PA  90
      STOP                                                               PA  91
 6    T2X(MI)=YNV*T1Z(MI)-ZNV*T1Y(MI)                                    PA  92
      T2Y(MI)=ZNV*T1X(MI)-XNV*T1Z(MI)                                    PA  93
      T2Z(MI)=XNV*T1Y(MI)-YNV*T1X(MI)                                    PA  94
      SALP(MI)=1.                                                        PA  95
      IF (NX.EQ.0) GO TO 8                                               PA  96
      M=M+NX*NY-1                                                        PA  97
      XN2=X(MI)-S1X-S2X                                                  PA  98
      YN2=Y(MI)-S1Y-S2Y                                                  PA  99
      ZN2=Z(MI)-S1Z-S2Z                                                  PA 100
      XS=T1X(MI)                                                         PA 101
      YS=T1Y(MI)                                                         PA 102
      ZS=T1Z(MI)                                                         PA 103
      XT=T2X(MI)                                                         PA 104
      YT=T2Y(MI)                                                         PA 105
      ZT=T2Z(MI)                                                         PA 106
      MI=MI+1                                                            PA 107
      DO 7 IY=1,NY                                                       PA 108
      XN2=XN2+S2X                                                        PA 109
      YN2=YN2+S2Y                                                        PA 110
      ZN2=ZN2+S2Z                                                        PA 111
      DO 7 IX=1,NX                                                       PA 112
      XST=IX                                                             PA 113
      MI=MI-1                                                            PA 114
      X(MI)=XN2+XST*S1X                                                  PA 115
      Y(MI)=YN2+XST*S1Y                                                  PA 116
      Z(MI)=ZN2+XST*S1Z                                                  PA 117
      BI(MI)=XA                                                          PA 118
      SALP(MI)=1                                                         PA 119
      T1X(MI)=XS                                                         PA 120
      T1Y(MI)=YS                                                         PA 121
      T1Z(MI)=ZS                                                         PA 122
      T2X(MI)=XT                                                         PA 123
      T2Y(MI)=YT                                                         PA 124
 7    T2Z(MI)=ZT                                                         PA 125
 8    IPSYM=0                                                            PA 126
      NP=N                                                               PA 127
      MP=M                                                               PA 128
```

```
      RETURN                                                            PA 129
C     DIVIDE PATCH FOR WIRE CONNECTION                                  PA 130
      ENTRY SUBPH(NX,NY,X1,Y1,Z1,X2,Y2,Z2,X3,Y3,Z3,X4,Y4,Z4)            PA 131
      IF (NY.GT.0) GO TO 10                                             PA 132
      IF (NX.EQ.M) GO TO 10                                             PA 133
      NXP=NX+1                                                          PA 134
      IX=LD-M                                                           PA 135
      DO 9 IY=NXP,M                                                     PA 136
      IX=IX+1                                                           PA 137
      NYP=IX-3                                                          PA 138
      X(NYP)=X(IX)                                                      PA 139
      Y(NYP)=Y(IX)                                                      PA 140
      Z(NYP)=Z(IX)                                                      PA 141
      BI(NYP)=BI(IX)                                                    PA 142
      SALP(NYP)=SALP(IX)                                                PA 143
      T1X(NYP)=T1X(IX)                                                  PA 144
      T1Y(NYP)=T1Y(IX)                                                  PA 145
      T1Z(NYP)=T1Z(IX)                                                  PA 146
      T2X(NYP)=T2X(IX)                                                  PA 147
      T2Y(NYP)=T2Y(IX)                                                  PA 148
9     T2Z(NYP)=T2Z(IX)                                                  PA 149
10    MI=LD+1-NX                                                        PA 150
      XS=X(MI)                                                          PA 151
      YS=Y(MI)                                                          PA 152
      ZS=Z(MI)                                                          PA 153
      XA=BI(MI)*.25                                                     PA 154
      XST=SQRT(XA)*.5                                                   PA 155
      S1X=T1X(MI)                                                       PA 156
      S1Y=T1Y(MI)                                                       PA 157
      S1Z=T1Z(MI)                                                       PA 158
      S2X=T2X(MI)                                                       PA 159
      S2Y=T2Y(MI)                                                       PA 160
      S2Z=T2Z(MI)                                                       PA 161
      SALN=SALP(MI)                                                     PA 162
      XT=XST                                                            PA 163
      YT=XST                                                            PA 164
      IF (NY.GT.0) GO TO 11                                             PA 165
      MIA=MI                                                            PA 166
      GO TO 12                                                          PA 167
11    M=M+1                                                             PA 168
      MP=MP+1                                                           PA 169
      MIA=LD+1-M                                                        PA 170
12    DO 13 IX=1,4                                                      PA 171
      X(MIA)=XS+XT*S1X+YT*S2X                                           PA 172
      Y(MIA)=YS+XT*S1Y+YT*S2Y                                           PA 173
      Z(MIA)=ZS+XT*S1Z+YT*S2Z                                           PA 174
      BI(MIA)=XA                                                        PA 175
      T1X(MIA)=S1X                                                      PA 176
      T1Y(MIA)=S1Y                                                      PA 177
      T1Z(MIA)=S1Z                                                      PA 178
      T2X(MIA)=S2X                                                      PA 179
      T2Y(MIA)=S2Y                                                      PA 180
      T2Z(MIA)=S2Z                                                      PA 181
      SALP(MIA)=SALN                                                    PA 182
      IF (IX.EQ.2) YT=-YT                                               PA 183
      IF (IX.EQ.1.OR.IX.EQ.3) XT=-XT                                    PA 184
      MIA=MIA-1                                                         PA 185
13    CONTINUE                                                          PA 186
      M=M+3                                                             PA 187
      IF (NX.LE.MP) MP=MP+3                                             PA 188
      IF (NY.GT.0) Z(MI)=10000.                                         PA 189
      RETURN                                                            PA 190
C                                                                       PA 191
14    FORMAT (62H ERROR -- CORNERS OF QUADRILATERAL PATCH DO NOT LIE IN  PA 192
```

```
193       1A PLANE)                                    PA 193
194        END                                         PA 194-
```

PCINT

PURPOSE

To compute the interaction matrix elements representing the electric field, tangent to a segment connected to a surface, due to the current on the four patches around the connection point.

METHOD

The four patches at the base of a connected wire are located as shown in figure 10 with respect to the vectors $\hat{t}_1$ and $\hat{t}_2$, where patch numbers indicate the order of the patches in the data arrays. The position of a point on the surface is defined by $\bar{\rho}\ (S_1,S_2) = \bar{\rho}_0 + S_1\hat{t}_1 + S_2\hat{t}_2$, where $\bar{\rho}_0$ is the position of the center of the four patches where the wire connects, and S_1 and S_2 are coordinates measured from the center. The current over the surface is represented by $\bar{J}(S_1,S_2)$, the currents at the centers of the four patches are

$$\bar{J}_1 = \bar{J}(d,d)$$
$$\bar{J}_2 = \bar{J}(-d,d)$$
$$\bar{J}_3 = \bar{J}(-d,-d)$$
$$\bar{J}_4 = \bar{J}(d,-d)$$

and the current at the base of the segment, flowing onto the surface, is I_0. The current interpolation function is then

$$\bar{J}(S_1,S_2) = \left[\bar{f}(S_1,S_2) - \sum_{i=1}^{4} g_i(S_1,S_2)\,\bar{f}_i\right] I_0 + \sum_{i=1}^{4} g_i(S_1,S_2)\bar{J}_i \ ,$$

where

$$\bar{f}(S_1,S_2) = \frac{S_1\hat{t}_1 + S_2\hat{t}_2}{2\pi(S_1^2 + S_2^2)}$$

$$\bar{f}_1 = \bar{f}(d,d) = (\hat{t}_1 + \hat{t}_2)/(4\pi d)$$
$$\bar{f}_2 = \bar{f}(-d,d) = (-\hat{t}_1 + \hat{t}_2)/(4\pi d)$$
$$\bar{f}_3 = \bar{f}(-d,-d) = (-\hat{t}_1 - \hat{t}_2)/(4\pi d)$$
$$\bar{f}_4 = \bar{f}(d,-d) = (\hat{t}_1 - \hat{t}_2)/(4\pi d)$$

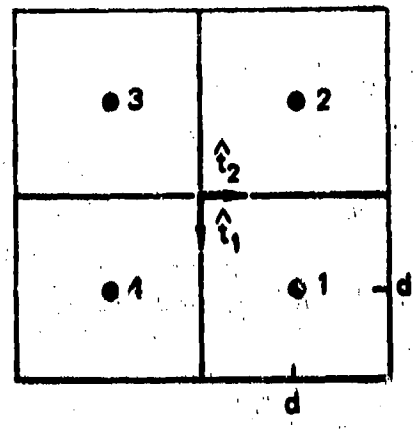


Figure 10. Patches at a Wire Connection Point.

$$g_1(S_1,S_2) = (d + S_1)(d + S_2)/(4d^2)$$
$$g_2(S_1,S_2) = (d - S_1)(d + S_2)/(4d^2)$$
$$g_3(S_1,S_2) = (d - S_1)(d - S_2)/(4d^2)$$
$$g_4(S_1,S_2) = (d + S_1)(d - S_2)/(4d^2)$$

If $\overline{\Gamma}_1(\overline{\rho})dA$ and $\overline{\Gamma}_2(\overline{\rho})dA$ are the electric fields at the center of the connected segment due to unit currents at $\overline{\rho}$ on the surface dA, flowing in the directions $\hat{t}_1$ and $\hat{t}_2$, respectively, the nine matrix elements to be computed are

$$E_1 = \int_S g_1(S_1,S_2)\ \hat{i} \cdot \overline{\Gamma}_1(\overline{\rho})dA$$

$$E_2 = \int_S g_2(S_1,S_2)\ \hat{i} \cdot \overline{\Gamma}_1(\overline{\rho})dA$$

$$E_3 = \int_S g_3(S_1,S_2)\ \hat{i} \cdot \overline{\Gamma}_1(\overline{\rho})dA$$

$$E_4 = \int_S g_4(S_1,S_2)\ \hat{i} \cdot \overline{\Gamma}_1(\overline{\rho})dA$$

$$E_5 = \int_S g_1(S_1,S_2)\ \hat{i} \cdot \overline{\Gamma}_2(\overline{\rho})dA$$

$$E_6 = \int_S g_2(S_1,S_2)\ \hat{i} \cdot \bar{\Gamma}_2(\bar{\rho})dA$$

$$E_7 = \int_S g_3(S_1,S_2)\ \hat{i} \cdot \bar{\Gamma}_2(\bar{\rho})dA$$

$$E_8 = \int_S g_4(S_1,S_2)\ \hat{i} \cdot \bar{\Gamma}_2(\bar{\rho})dA$$

$$E_9 = \int_S \left\{ \left[\bar{h}(S_1,S_2) \cdot \hat{t}_1\right] \left[\hat{i} \cdot \bar{\Gamma}_1(\bar{\rho})\right] + \left[\bar{h}(S_1,S_2) \cdot \hat{t}_2\right] \left[\hat{i} \cdot \bar{\Gamma}_2(\bar{\rho})\right] \right\} dA$$

where

$$\bar{h}(S_1,S_2) = \bar{f}(S_1,S_2) - \sum_{i=1}^{4} g_i(S_1,S_2)\bar{f}_i\ ,$$

and where $\hat{i}$ = the unit vector in the direction of the connected segment.

The integration is over the total area of the four patches and is performed by numerical quadrature. The number of increments in S_1 and S_2 used in integration is set by the variable NINT. When PCINT is called, the parameters in COMMON/DATAJ/ have the values for the first connected patch. During integration, these parameters are set for each integration patch. At the end of PCINT, they are reset to their original values.

SYMBOL DICTIONARY

CABI = x component of $\hat{i}$

D = d

DA = area of the surface element used in integration

DS = width of the surface element of area DA

E = array used to return the values E_1, E_2, ..., E_9

EXK, EYK, EZK = x, y, and z components of $\bar{\Gamma}_1(\bar{\rho})$DA at PC50; at PC51, EXK is set to $\hat{i} \cdot \bar{\Gamma}_1(\bar{\rho})$DA

EXS, EYS, EZS = x, y, and z components of $\bar{\Gamma}_2(\bar{\rho})$DA at PC50; at PC52, EXS is set to $\hat{i} \cdot \bar{\Gamma}_2(\bar{\rho})$DA

E1 = E_1

E2 = E_2

E3 = E_3

E4 = E_4

E5 = E_5

E6 = E_6

E7 = E_7

E8 = E_8

E9 = E_9

FCON = $1/(4\pi d)$ factor in $\bar{f}_1$, $\bar{f}_2$, ...

F1 = $\bar{h}(S_1,S_2) \cdot \hat{t}_1$

F2 = $\bar{h}(S_1,S_2) \cdot \hat{t}_2$

GCON = $1/(4d^2)$ factor in $g_1(S_1,S_2)$, ...

G1 = $g_1(S_1,S_2)$

G2 = $g_2(S_1,S_2)$

G3 = $g_3(S_1,S_2)$

G4 = $g_4(S_1,S_2)$

I1 = DO loop index

I2 = DO loop index

NINT = number of steps in S_1 and S_3 used in approximating the integrals for E_1, E_2, ..., E_9

S = area of each of the four patches at PC11; area of the surface element used in integration at PC20

SABI = y component of $\hat{i}$

SALPI = z component of $\hat{i}$

S1 = S_1

S2 = S_2

S2X = initial value of S_2

TPI = 2π

T1XJ, T1YJ, T1ZJ = x, y, and z components of $\hat{t}_1$

T2XJ, T2YJ, T2ZJ = x, y, and z components of $\hat{t}_2$

XI = x coordinate of the center of the connected segment

XJ, YJ, ZJ = center of first patch above PC41; center of integration element below PC41

XS = x component of $\bar{\rho}(S_1,S_2)$

XSS = initial x coordinate of $\bar{\rho}(S_1,S_2)$

XXJ, XYJ, XZJ = initial value of XJ, YJ, ZJ saved

X1 = x component of $\bar{\rho}(d,d)$ used as reference for computing $\bar{\rho}(S_1,S_2)$

YI = y coordinate of the center of the connected segment

YS = y component of $\bar{\rho}(S_1,S_2)$

YSS = initial y component of $\bar{\rho}(S_1,S_2)$

Y1 = y component of $\bar{\rho}(d,d)$

ZI = z coordinate of the center of the connected segment

ZS = z component of $\bar{\rho}(S_1,S_2)$

ZSS = initial z component of $\bar{\rho}(S_1,S_2)$

Z1 = z component of $\bar{\rho}(d,d)$

```
      SUBROUTINE PCINT (XI,YI,ZI,CABI,SABI,SALPI,E)                     PC    1
C     INTEGRATE OVER PATCHES AT WIRE CONNECTION POINT                   PC    2
      COMPLEX EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC,E,E1,E2,E3,E4,E5,E6,E7 PC    3
     1,E8,E9                                                            PC    4
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ PC    5
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                           PC    6
      DIMENSION E(9)                                                    PC    7
      EQUIVALENCE (T1XJ,CABJ), (T1YJ,SABJ), (T1ZJ,SALPJ), (T2XJ,B), (T2Y PC    8
     1J,IND1), (T2ZJ,IND2)                                              PC    9
      DATA TPI/6.283185308/,NINT/10/                                    PC   10
      D=SQRT(S)*.5                                                      PC   11
      DS=4.*D/FLOAT(NINT)                                               PC   12
      DA=DS*DS                                                          PC   13
      GCON=1./S                                                         PC   14
      FCON=1./(2.*TPI*D)                                                PC   15
      XXJ=XJ                                                            PC   16
      XYJ=YJ                                                            PC   17
      XZJ=ZJ                                                            PC   18
      XS=S                                                              PC   19
      S=DA                                                              PC   20
      S1=D+DS*.5                                                        PC   21
      XSS=XJ+S1*(T1XJ+T2XJ)                                             PC   22
      YSS=YJ+S1*(T1YJ+T2YJ)                                             PC   23
      ZSS=ZJ+S1*(T1ZJ+T2ZJ)                                             PC   24
      S1=S1+D                                                           PC   25
      S2X=S1                                                            PC   26
      E1=(0.,0.)                                                        PC   27
      E2=(0.,0.)                                                        PC   28
      E3=(0.,0.)                                                        PC   29
      E4=(0.,0.)                                                        PC   30
      E5=(0.,0.)                                                        PC   31
      E6=(0.,0.)                                                        PC   32
      E7=(0.,0.)                                                        PC   33
      E8=(0.,0.)                                                        PC   34
      E9=(0.,0.)                                                        PC   35
      DO 1 I1=1,NINT                                                    PC   36
      S1=S1-DS                                                          PC   37
      S2=S2X                                                            PC   38
      XSS=XSS-DS*T1XJ                                                   PC   39
      YSS=YSS-DS*T1YJ                                                   PC   40
      ZSS=ZSS-DS*T1ZJ                                                   PC   41
      XJ=XSS                                                            PC   42
      YJ=YSS                                                            PC   43
      ZJ=ZSS                                                            PC   44
      DO 1 I2=1,NINT                                                    PC   45
      S2=S2-DS                                                          PC   46
      XJ=XJ-DS*T2XJ                                                     PC   47
      YJ=YJ-DS*T2YJ                                                     PC   48
      ZJ=ZJ-DS*T2ZJ                                                     PC   49
      CALL UNERE (XI,YI,ZI)                                             PC   50
      EXK=EXK*CABI+EYK*SABI+EZK*SALPI                                   PC   51
      EXS=EXS*CABI+EYS*SABI+EZS*SALPI                                   PC   52
      G1=(D+S1)*(D+S2)*GCON                                             PC   53
      G2=(D-S1)*(D+S2)*GCON                                             PC   54
      G3=(D-S1)*(D-S2)*GCON                                             PC   55
      G4=(D+S1)*(D-S2)*GCON                                             PC   56
      F2=(S1*S1+S2*S2)*TPI                                              PC   57
      F1=S1/F2-(G1-G2-G3+G4)*FCON                                       PC   58
      F2=S2/F2-(G1+G2-G3-G4)*FCON                                       PC   59
      E1=E1+EXK*G1                                                      PC   60
      E2=E2+EXK*G2                                                      PC   61
      E3=E3+EXK*G3                                                      PC   62
      E4=E4+EXK*G4                                                      PC   63
      E5=E5+EXS*G1                                                      PC   64
```

```
65          E6=E6+EXS*G2                                        PC  65
66          E7=E7+EXS*G3                                        PC  66
67          E8=E8+EXS*G4                                        PC  67
68  1       E9=E9+EXK*F1+EXS*F2                                 PC  68
69          E(1)=E1                                             PC  69
70          E(2)=E2                                             PC  70
71          E(3)=E3                                             PC  71
72          E(4)=E4                                             PC  72
73          E(5)=E5                                             PC  73
74          E(6)=E6                                             PC  74
75          E(7)=E7                                             PC  75
76          E(8)=E8                                             PC  76
77          E(9)=E9                                             PC  77
78          XJ=XXJ                                              PC  78
79          YJ=XYJ                                              PC  79
80          ZJ=XZJ                                              PC  80
81          S=XS                                                PC  81
82          RETURN                                              PC  82
83          END                                                 PC  83-
```

PRNT

PURPOSE

To set up the formats for printing a record of three integers, six floating point numbers, and a Hollerith string, where the variables equal to zero are replaced by blanks. This routine is used by LOAD in printing the impedance data table.

METHOD

A variable format is used to generate the record with arbitrary blank fill. Elements of the format are picked from the array IFORM in the DATA statement. Through IF statements operating on the subroutine input quantities, this routine chooses the desired format elements and builds the format in the array IVAR. The program is divided into two sections: the first builds the integer part of the format and the second the floating point part.

SYMBOL DICTIONARY

ABS = external routine (absolute value)
FL = elements of this array are set equal to the floating point input quantities FL1 - FL6
FLT = array of non-zero floating point input quantities to be printed
FL1, FL2, FL3, FL4, FL5, FL6 = input floating point quantities
HALL = 4H ALL (Hollerith ALL)
I = DO loop index
IA = input Hollerith string (array)
ICHAR = number of characters in the input Hollerith string
IFORM = array containing format elements
IN = array set equal to input integer quantities (IN1 - IN3)
INT = non-zero integer quantities to be printed
IN1, IN2, IN3 = input integer quantities
IVAR = variable format array

I1 = DO loop limit
J = implied DO loop index
K = index parameter
L = implied DO loop index
NCPW = number of Hollerith characters per computer word
NFLT = floating point print index, number of non-zero reals
NINT = integer print index; number of non-zero integers
NWORDS = number of computer words in the input Hollerith string

```
      SUBROUTINE PRNT (IN1,IN2,IN3,FL1,FL2,FL3,FL4,FL5,FL6,IA,ICHAR)     PR   1
C                                                                        PR   2
C     PRNT SETS UP THE PRINT FORMATS FOR IMPEDANCE LOADING               PR   3
C                                                                        PR   4
      DIMENSION IVAR(13), IA(1), IFORM(8), IN(3), INT(3), FL(6), FLT(6)  PR   5
      INTEGER HALL                                                       PR   6
      DATA IFORM/5H(/3X,,3HI5,,3H5X,,3HA5,,6HE13.4,,4H13X,,3H3X,,5H2A10) PR   7
     1/                                                                  PR   8
C                                                                        PR   9
C     NUMBER OF CHARACTERS PER COMPUTER WORD IS NCPW                     PR  10
C                                                                        PR  11
      DATA NCPW/10/,HALL/4H ALL/                                         PR  12
      NWORDS=(ICHAR-1)/NCPW+1                                            PR  13
      IN(1)=IN1                                                          PR  14
      IN(2)=IN2                                                          PR  15
      IN(3)=IN3                                                          PR  16
      FL(1)=FL1                                                          PR  17
      FL(2)=FL2                                                          PR  18
      FL(3)=FL3                                                          PR  19
      FL(4)=FL4                                                          PR  20
      FL(5)=FL5                                                          PR  21
      FL(6)=FL6                                                          PR  22
C                                                                        PR  23
C     INTEGER FORMAT                                                     PR  24
C                                                                        PR  25
      NINT=0                                                             PR  26
      IVAR(1)=IFORM(1)                                                   PR  27
      K=1                                                                PR  28
      I1=1                                                               PR  29
      IF (.NOT.(IN1.EQ.0.AND.IN2.EQ.0.AND.IN3.EQ.0)) GO TO 1             PR  30
      INT(1)=HALL                                                        PR  31
      NINT=1                                                             PR  32
      I1=2                                                               PR  33
      K=K+1                                                              PR  34
      IVAR(K)=IFORM(4)                                                   PR  35
    1 DO 3 I=I1,3                                                        PR  36
      K=K+1                                                              PR  37
      IF (IN(I).EQ.0) GO TO 2                                            PR  38
      NINT=NINT+1                                                        PR  39
      INT(NINT)=IN(I)                                                    PR  40
      IVAR(K)=IFORM(2)                                                   PR  41
      GO TO 3                                                            PR  42
    2 IVAR(K)=IFORM(3)                                                   PR  43
    3 CONTINUE                                                           PR  44
      K=K+1                                                              PR  45
      IVAR(K)=IFORM(7)                                                   PR  46
C                                                                        PR  47
C     FLOATING POINT FORMAT                                              PR  48
C                                                                        PR  49
      NFLT=0                                                             PR  50
      DO 5 I=1,6                                                         PR  51
      K=K+1                                                              PR  52
      IF (ABS(FL(I)).LT.1.E-20) GO TO 4                                  PR  53
      NFLT=NFLT+1                                                        PR  54
      FLT(NFLT)=FL(I)                                                    PR  55
      IVAR(K)=IFORM(5)                                                   PR  56
      GO TO 5                                                            PR  57
    4 IVAR(K)=IFORM(6)                                                   PR  58
    5 CONTINUE                                                           PR  59
      K=K+1                                                              PP  60
      IVAR(K)=IFORM(7)                                                   PR  61
      K=K+1                                                              PP  62
      IVAR(K)=IFORM(8)                                                   PP  63
      PRINT IVAR, (INT(I),I=1,NINT),(FLT(J),J=1,NFLT),(IA(L),L=1,NWORDS) PR  64
```

```
65        RETURN                                        PR  65
66        END                                           PR  66-
```

QDSRC

PURPOSE

To fill the excitation array for a current slope discontinuity voltage source.

METHOD

The current slope discontinuity voltage source is described in section IV-1 of Part I.

CODING

QD22 - QD25 The connection number for end 1 of segment IS is temporarily set to 0, and TBF is called to generate the function $f^*_\ell(s)$ for ℓ = IS. The zero in the second argument of TBF causes f^*_ℓ to go to zero at the first end of segment IS rather than the usual non-zero value that allows for current flowing onto the wire end cap.

QD26 - QD31 β_ℓ is computed and other quantities set.

QD32 - QD119 This loop computes the fields due to each segment on which f^*_ℓ is non-zero.

QD33 - QD77 Parameters of the source segment are stored in COMMON/DATAJ/. Flags for the extended thin wire approximation are set as in routine CMSET.

QD78 - QD91 This loop evaluates the electric field on each segment.

QD95 - QD116 This loop evaluates the magnetic field at each patch.

SYMBOL DICTIONARY

AI = radius of segment on which field is evaluated.

CABI = x component of unit vector in the direction of segment I

CCJ = CCJX = -j/60

CURD = β_ℓ

E = array of segment and patch excitation fields

ETC, ETK, ETS = E field tangent to a segment or H field components on a patch due to cosine, constant, and sine current components, respectively, on a segment

I1 = array index for patch excitation

IJ = flag which, if zero, indicates that the field is being evaluated on the source segment

IPR = temporary storage of connection number

IS = segment which has the source location on end 1

J = source segment number

SABI = y component of unit vector in the direction of segment I

T1X, T1Y, T1Z, T2X, T2Y, T2Z = arrays of components of $\hat{t}_1$ and $\hat{t}_2$ for patches

TP = 2π

TX, TY, TZ = components of $\hat{t}_1$ or $\hat{t}_2$ for patches

V = source voltage

XI, YI, ZI = coordinates of point where field is evaluated; XI is also used in the test for the extended thin wire approximation for the electric field

CONSTANTS

0.01666666667 = 1/60

0.999999 = minimum XI for the extended thin wire approximation (maximum angle = 0.08 degrees)

6.283185308 = 2π

```
      SUBROUTINE QDSRC (IS,V,E)                                          QD   1
C     FILL INCIDENT FIELD ARRAY FOR CHARGE DISCONTINUITY VOLTAGE SOURCE  QD   2
      COMPLEX VQDS,CURD,CCJ,V,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC,ETK,ET QD   3
     1S,ETC,VSANT,VQD,E,ZARRAY                                           QD   4
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 QD   5
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( QD   6
     2300),WLAM,IPSYM                                                    QD   7
      COMMON /VSORC/ VQD(30),VSANT(30),VQDS(30),IVQD(30),ISANT(30),IQDS( QD   8
     130),NVQD,NSANT,NQDS                                                QD   9
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(50),NSCON,IP QD  10
     1CON(10),NPCON                                                      QD  11
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ QD  12
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                             QD  13
      COMMON /ANGL/ SALP(300)                                            QD  14
      COMMON /ZLOAD/ ZARRAY(300),NLOAD,NLODF                             QD  15
      DIMENSION CCJX(2), E(1), CAB(1), SAB(1)                            QD  16
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1)           QD  17
      EQUIVALENCE (CCJ,CCJX), (CAB,ALP), (SAB,BET)                       QD  18
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON QD  19
     12), (T2Z,ITAG)                                                     QD  20
      DATA TP/6.283185308/,CCJX/0.,-.01666666667/                        QD  21
      I=ICON1(IS)                                                        QD  22
      ICON1(IS)=0                                                        QD  23
      CALL TBF (IS,0)                                                    QD  24
      ICON1(IS)=I                                                        QD  25
      S=SI(IS)*.5                                                        QD  26
      CURD=CCJ*V/((ALOG(2.*S/BI(IS))-1.)*(BX(JSNO)*COS(TP*S)+CX(JSNO)*SI QD  27
     1N(TP*S))*WLAM)                                                     QD  28
      NQDS=NQDS+1                                                        QD  29
      VQDS(NQDS)=V                                                       QD  30
      IQDS(NQDS)=IS                                                      QD  31
      DO 20 JX=1,JSNO                                                    QD  32
      J=JCO(JX)                                                          QD  33
      S=SI(J)                                                            QD  34
      B=BI(J)                                                            QD  35
      XJ=X(J)                                                            QD  36
      YJ=Y(J)                                                            QD  37
      ZJ=Z(J)                                                            QD  38
      CABJ=CAB(J)                                                        QD  39
      SABJ=SAB(J)                                                        QD  40
      SALPJ=SALP(J)                                                      QD  41
      IF (IEXK.EQ.0) GO TO 16                                            QD  42
      IPR=ICON1(J)                                                       QD  43
      IF (IPR) 1,6,2                                                     QD  44
1     IPR=-IPR                                                           QD  45
      IF (-ICON1(IPR).NE.J) GO TO 7                                      QD  46
      GO TO 4                                                            QD  47
2     IF (IPR.NE.J) GO TO 3                                              QD  48
      IF (CABJ*CABJ+SABJ*SABJ.GT.1.E-8) GO TO 7                          QD  49
      GO TO 5                                                            QD  50
3     IF (ICON2(IPR).NE.J) GO TO 7                                       QD  51
4     XI=ABS(CABJ*CAB(IPR)+SABJ*SAB(IPR)+SALPJ*SALP(IPR))                QD  52
      IF (XI.LT.0.999999) GO TO 7                                        QD  53
      IF (ABS(BI(IPR)/B-1.).GT.1.E-6) GO TO 7                            QD  54
5     IND1=0                                                             QD  55
      GO TO 8                                                            QD  56
6     IND1=1                                                             QD  57
      GO TO 8                                                            QD  58
7     IND1=2                                                             QD  59
8     IPR=ICON2(J)                                                       QD  60
      IF (IPR) 9,14,10                                                   QD  61
9     IPR=-IPR                                                           QD  62
      IF (-ICON2(IPR).NE.J) GO TO 15                                     QD  63
      GO TO 12                                                           QD  64
```

```
      IF (IPR.NE.J) GO TO 11                                                    QD  65
      IF (CABJ*CABJ+SABJ*SABJ.GT.1.E-8) GO TO 15                                QD  66
      GO TO 13                                                                  QD  67
11    IF (ICON1(IPR).NE.J) GO TO 15                                             QD  68
12    XI=ABS(CABJ*CAB(IPR)+SABJ*SAB(IPR)+SALPJ*SALP(IPR))                       QD  69
      IF (XI.LT.0.999999) GO TO 15                                              QD  70
      IF (ABS(BI(IPR)/B-1.).GT.1.E-6) GO TO 15                                  QD  71
13    IND2=0                                                                    QD  72
      GO TO 16                                                                  QD  73
14    IND2=1                                                                    QD  74
      GO TO 16                                                                  QD  75
15    IND2=2                                                                    QD  76
16    CONTINUE                                                                  QD  77
      DO 17 I=1,N                                                               QD  78
      IJ=I-J                                                                    QD  79
      XI=X(I)                                                                   QD  80
      YI=Y(I)                                                                   QD  81
      ZI=Z(I)                                                                   QD  82
      AI=BI(I)                                                                  QD  83
      CALL EFLD (XI,YI,ZI,AI,IJ)                                                QD  84
      CABI=CAB(I)                                                               QD  85
      SABI=SAB(I)                                                               QD  86
      SALPI=SALP(I)                                                             QD  87
      ETK=EXK*CABI+EYK*SABI+EZK*SALPI                                           QD  88
      ETS=EXS*CABI+EYS*SABI+EZS*SALPI                                           QD  89
      ETC=EXC*CABI+EYC*SABI+EZC*SALPI                                           QD  90
17    E(I)=E(I)-(ETK*AX(JX)+ETS*BX(JX)+ETC*CX(JX))*CURD                         QD  91
      IF (M.EQ.0) GO TO 19                                                      QD  92
      IJ=LD+1                                                                   QD  93
      I1=N                                                                      QD  94
      DO 18 I=1,M                                                               QD  95
      IJ=IJ-1                                                                   QD  96
      XI=X(IJ)                                                                  QD  97
      YI=Y(IJ)                                                                  QD  98
      ZI=Z(IJ)                                                                  QD  99
      CALL HSFLD (XI,YI,ZI,0.)                                                  QD 100
      I1=I1+1                                                                   QD 101
      TX=T2X(IJ)                                                                QD 102
      TY=T2Y(IJ)                                                                QD 103
      TZ=T2Z(IJ)                                                                QD 104
      ETK=EXK*TX+EYK*TY+EZK*TZ                                                  QD 105
      ETS=EXS*TX+EYS*TY+EZS*TZ                                                  QD 106
      ETC=EXC*TX+EYC*TY+EZC*TZ                                                  QD 107
      E(I1)=E(I1)+(ETK*AX(JX)+ETS*BX(JX)+ETC*CX(JX))*CURD*SALP(IJ)              QD 108
      I1=I1+1                                                                   QD 109
      TX=T1X(IJ)                                                                QD 110
      TY=T1Y(IJ)                                                                QD 111
      TZ=T1Z(IJ)                                                                QD 112
      ETK=EXK*TX+EYK*TY+EZK*TZ                                                  QD 113
      ETS=EXS*TX+EYS*TY+EZS*TZ                                                  QD 114
      ETC=EXC*TX+EYC*TY+EZC*TZ                                                  QD 115
18    E(I1)=E(I1)+(ETK*AX(JX)+ETS*BX(JX)+ETC*CX(JX))*CURD*SALP(IJ)              QD 116
19    IF (NLOAD.GT.0.OR.NLODF.GT.0) E(J)=E(J)+ZARRAY(J)*CURD*(AX(JX)+CX(        QD 117
     1JX))                                                                      QD 118
20    CONTINUE                                                                  QD 119
      RETURN                                                                    QD 120
      END                                                                       QD 121-
```

RDPAT

PURPOSE

To compute and print radiated field quantities.

METHOD

The quantities computed and the output formats depend on the options selected by the first integer (IFAR) and fourth integer (IPD, IAVP, INOR, IAX) on the RP card (see Part III). These quantities are defined as follows:

(1) Power Gain

In the direction (θ,ϕ)

$$G_p(\theta,\phi) = 4\pi \frac{P_{\Omega}(\theta,\phi)}{P_{in}},$$

where $P_{\Omega}(\theta,\phi)$ is the power radiated per unit solid angle in the given direction, and P_{in} is the total power accepted by the antenna. Therefore, $P_{in} = (1/2)\mathrm{Re}(VI^*)$, where V is the applied source voltage, and

$$P_{\Omega}(\theta,\phi) = (1/2)\, R^2 \mathrm{Re}(\bar{E} \times \bar{H}^*) = \frac{R^2}{2\eta} \bar{E} \cdot \bar{E}^*,$$

where R is the observation sphere radius. Since the electric field calculated by FFLD (call it $\bar{E}'$) does not include $\exp(-jkR)/(R/\lambda)$,

$$\bar{E} = \frac{\exp(-jkR)}{R/\lambda} \bar{E}'$$

and

$$P_{\Omega} = \frac{\lambda^2}{2\eta} (\bar{E}' \cdot \bar{E}'^*) \quad .$$

Thus,

$$G_p(\theta,\phi) = \frac{2\pi\lambda^2}{\eta P_{in}} (\bar{E}' \cdot \bar{E}'^*)$$

in terms of the program variables.

(2) Directive Gain

In the direction (θ,ϕ),

$$G_d(\theta,\phi) = 4\pi \frac{P_\Omega(\theta,\phi)}{P_{rad}}$$

where P_{rad} is the total power radiated by the antenna. The only difference from power gain is that P_{in} is replaced by P_{rad}, and $P_{rad} = P_{in} - P_{loss}$, where P_{loss} is calculated as the power lost in distributed and lumped loads on the structure and in the networks loads.

(3) Component Gain

The gains are also calculated for separate, orthogonal field components (u, v). In this case, $\bar{E}' \cdot \bar{E}'^*$ is replaced by $E'_u E'^*_u$ or $E'_v E'^*_v$, and the total gain is the sum of the two components.

(4) Average Gain

The user specifies a range and number of points in theta and phi that in turn specify the total solid angle covered, Ω, and the sampling density for the integral in the expression for average gain:

$$G_{av} = \frac{\int_\Omega G_p \, d\Omega}{\Omega}$$

The trapezoidal rule is used in evaluating the integral.

(5) Normalized Gain

Normalized gain is simply the gain divided by its maximum value or some value specified by the user.

The discussion of gains applies only to the case of a structure used as a radiating antenna. For the case of an incident plane wave, the program constants are defined such that the value of σ/λ^2 is printed under the heading "GAIN." The calculation is

$$\frac{\sigma}{\lambda^2} = \frac{4\pi R^2}{\lambda^2} \frac{W_{scat}}{W_{inc}} = \frac{4\pi}{\vec{E}_{inc} \cdot \vec{E}^*_{inc}} (\vec{E}'_{scat} \cdot \vec{E}'^*_{scat}) \quad ,$$


where W_{scat} is the scattered power per unit area at distance R in a given direction, W_{inc} is the power per unit area of the incident plane wave, and the primes on the electric fields specify the fields used in the program as defined above. For the case of a Hertzian dipole used as a source, the gain equations are used; however, P_{in} is equal to the total power radiated by the Hertzian source. That is

$$P_{in} = \frac{\pi\eta}{3} \left| \frac{I\ell}{\lambda} \right|^2 \quad ,$$

where the quantity $I\ell$ is an input quantity.

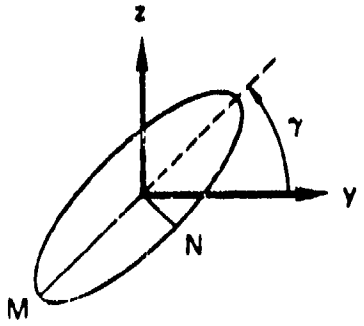(6) Elliptic Polarization

Elliptic polarization parameters are calculated as follows:



$$M = [(E_{ym} \cos\gamma + E_{zm} \cos\xi \sin\gamma)^2 + E_{zm}^2 \sin^2\xi \sin^2\gamma]^{1/2} ,$$

$$N = [E_{ym} \sin\gamma - E_{zm} \cos\xi \cos\gamma)^2 + E_{zm}^2 \sin^2\xi \cos^2\gamma]^{1/2} ,$$

where

$$E_y = E_{ym} \exp[j(\omega t - kx)] ,$$

$$E_z = E_{zm} \exp[j(\omega t - kx + \xi)] ,$$

and γ is given by

$$\tan 2y = \frac{2E_{ym}E_{zm}\cos\xi}{E_{ym}^2 - E_{zm}^2}$$

In this routine, the coordinates y and z above are replaced by θ and ϕ, respectively.

The field is computed by FFLD at RD74 for space wave or by GFLD at RD76 for space and ground wave. Elliptic polarization parameters are computed from RD87 to RD118. RD127 to RD137 stores gain in the array GAIN for normalization. The integral of radiated power for the average gain calculation is summed at RD140 to RD147. Fields and gain are printed at RD162 for space wave or RD165 for ground wave. Average gain is computed and printed from RD168 to RD173. Normalized gain is printed from RD174 to RD208.

SYMBOL DICTIONARY

AXRAT	= N/M (elliptic axial ratio)
CHT	= height of cliff in meters
CLT	= distance in meters of cliff edge from origin
DA	= element of solid angle for average gain summation
DFAZ	= phase difference between E_θ and E_ϕ for elliptic polarization

DPH	= increment for ϕ
DTH	= increment for θ
EMAJR2	= M^2 (M = major axis)
EMINR2	= N^2
EPH	= E_ϕ (phi component of electric field, with or without the term exp(-jkR)/(R/λ) depending on return from GFLD or FFLD)
EPHA	= phase angle of EPH
EPHM	= |EPH|
EPHM2	= $\|EPH\|^2$
EPSR	= relative dielectric constant
EPSR2	= relative dielectric constant of second medium
ERD	= radial electric field for ground wave
ERDA	= phase of ERD
ERDM	= |ERD|
ETH	= E_θ
ETHA	= phase of E_θ
ETHM	= $\|E_\theta\|$
ETHM2	= $\|E_\theta\|^2$
EXRA	= phase of exp(-jkR)
EXRM	= 1/R
GCON	= factor multiplying $\|E\|^2$ to yield gain or σ/λ^2
GCOP	= GCON except when GCON yields directive gain; then GCOP remains power gain
GMAX	= value used for normalized gain
GNH	= horizontal gain in decibels, ϕ component
GNMJ	= major axis gain in decibels
GNMN	= minor axis gain in decibels
GNOR	= if non-zero, equals input gain quantity
GNV	= vertical gain (θ)
GTOT	= total gain
IAVP	= flag for average gain
IAX	= flag for gain type
IFAR	= first integer from RP card

INOR	= integer to select normalized gain
IPD	= flag to select power or directive gain
IXTYP	= excitation type
NORMAX	= dimension of FNORM (maximum number of gain values that will be stored for normalization)
NPH	= number of ϕ values
NTH	= number of θ values
PHA	= ϕ in radians
PHI	= ϕ in degrees
PHIS	= initial ϕ
PI	= π
PINR	= input power for current element source
PINT	= summation variable for average gain
PLOSS	= power dissipated in structure loads
PNLR	= power dissipated in networks and transmission lines
PRAD	= power radiated by the antenna
RFLD	= if non-zero, equal to the observation distance in meters
SIG	= conductivity of ground (mhos/m)
SIG2	= conductivity of second medium (mhos/m)
STILTA	= sin γ; γ is tilt angle of the polarization ellipse
TA	= $\pi/180$
TD	= $180/\pi$
THA	= θ in radians
THET	= θ in degrees
THETS	= initial θ
TILTA	= γ (tilt angle of ellipse)
XPR6	= minor axis of polarization ellipse or strength of current element source

CONSTANTS

1.745329252E-2	= $\pi/180$
1.E-20	= small value test

1.E-5	= small value test
-1.E10	= near minus infinity
3.141592654	= π
376.73	= $\eta_0 = \sqrt{\mu_0/\varepsilon_0}$
394.51	= $\pi\eta_0/3$
57.2957795	= $180/\pi$
59.96	= $\eta_0/(2\pi)$
90.01	= test value for angle exceeding 90 degrees

```
      SUBROUTINE RDPAT                                                  RD   1
C     COMPUTE RADIATION PATTERN, GAIN, NORMALIZED GAIN                  RD   2
      INTEGER HPOL,HBLK,HCIR,HCLIF                                      RD   3
      COMPLEX ETH,EPH,ERD,ZRATI,ZRATI2,T1,FRATI                         RD   4
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 RD   5
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( RD   6
     2300),WLAM,IPSYM                                                   RD   7
      COMMON /SAVE/ IP(600),KCOM,COM(13,5),EPSR,SIG,SCRWLT,SCRWRT,FMHZ  RD   8
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR, RD   9
     1IPERF,T1,T2                                                       RD  10
      COMMON /FPAT/ NTH,NPH,IPD,IAVP,INOR,IAX,THETS,PHIS,DTH,DPH,RFLD,GN RD  11
     1OR,CLT,CHT,EPSR2,SIG2,IXTYP,XPR6,PINR,PNLR,PLOSS,NEAR,NFEH,NRX,NRY RD  12
     2,NRZ,XNR,YNR,ZNR,DXNR,DYNR,DZNR                                   RD  13
      COMMON /SCRATM/ GAIN(1200)                                        RD  14
      DIMENSION IGTP(4), IGAX(4), IGNTP(10), HPOL(3)                    RD  15
      DATA HPOL/6HLINEAR,5HRIGHT,4HLEFT/,HBLK,HCIR/1H ,6HCIRCLE/        RD  16
      DATA IGTP/6H     = ,6HPOWER ,6H- DIRE,6HCTIVE /                   RD  17
      DATA IGAX/6H MAJOR,6H MINOR,6H VERT.,6H HOR. /                    RD  18
      DATA IGNTP/6H MAJOR,6H AXIS ,6H MINOR,6H AXIS ,6H   VER,6HTICAL ,6 RD  19
     1H HORIZ,6HONTAL ,6H       ,6HTOTAL /                              RD  20
      DATA PI,TA,TD/3.141592654,1.745329252E-02,57.29577951/            RD  21
      DATA NORMAX/1200/                                                 RD  22
      IF (IFAR.LT.2) GO TO 2                                            RD  23
      PRINT 35                                                          RD  24
      IF (IFAR.LE.3) GO TO 1                                            RD  25
      PRINT 36, NRADL,SCRWLT,SCRWRT                                     RD  26
      IF (IFAR.EQ.4) GO TO 2                                            RD  27
1     IF (IFAR.EQ.2.OR.IFAR.EQ.5) HCLIF=HPOL(1)                         RD  28
      IF (IFAR.EQ.3.OR.IFAR.EQ.6) HCLIF=HCIR                            RD  29
      CL=CLT/WLAM                                                       RD  30
      CH=CHT/WLAM                                                       RD  31
      ZRATI2=CSQRT(1./CMPLX(EPSR2,-SIG2*WLAM*59.96))                    RD  32
      PRINT 37, HCLIF,CLT,CHT,EPSR2,SIG2                                RD  33
2     IF (IFAR.NE.1) GO TO 3                                            RD  34
      PRINT 41                                                          RD  35
      GO TO 5                                                           RD  36
3     I=2*IPD+1                                                         RD  37
      J=I+1                                                             RD  38
      ITMP1=2*IAX+1                                                     RD  39
      ITMP2=ITMP1+1                                                     RD  40
      PRINT 38                                                          RD  41
      IF (RFLD.LT.1.E-20) GO TO 4                                       RD  42
      EXRM=1./RFLD                                                      RD  43
      EXRA=RFLD/WLAM                                                    RD  44
      EXRA=-360.*(EXRA-AINT(EXRA))                                      RD  45
      PRINT 39, RFLD,EXRM,EXRA                                          RD  46
4     PRINT 40, IGTP(I),IGTP(J),IGAX(ITMP1),IGAX(ITMP2)                 RD  47
5     IF (IXTYP.EQ.0.OR.IXTYP.EQ.5) GO TO 7                             RD  48
      IF (IXTYP.EQ.4) GO TO 6                                           RD  49
      PRAD=0.                                                           RD  50
      GCON=4.*PI/(1.+XPR6*XPR6)                                         RD  51
      GCOP=GCON                                                         RD  52
      GO TO 8                                                           RD  53
6     PINR=394.51*XPR6*XPR6*WLAM*WLAM                                   RD  54
7     GCOP=WLAM*WLAM*2.*PI/(376.73*PINR)                                RD  55
      PRAD=PINR-PLOSS-PNLR                                              RD  56
      GCON=GCOP                                                         RD  57
      IF (IPD.NE.0) GCON=GCON*PINR/PRAD                                 RD  58
8     I=0                                                               RD  59
      GMAX=-1.E10                                                       RD  60
      PINT=0.                                                           RD  61
      TMP1=DPH*TA                                                       RD  62
      TMP2=.5*DTH*TA                                                    RD  63
      PHI=PHIS-DPH                                                      RD  64
```

```
      DO 29 KPH=1,NPH                                                    RD  65
      PHI=PHI+DPH                                                        RD  66
      PHA=PHI*TA                                                         RD  67
      THET=THETS-DTH                                                     RD  68
      DO 29 KTH=1,NTH                                                    RD  69
      THET=THET+DTH                                                      RD  70
      IF (KSYMP.EQ.2.AND.THET.GT.90.01.AND.IFAR.NE.1) GO TO 29           RD  71
      THA=THET*TA                                                        RD  72
      IF (IFAR.EQ.1) GO TO 9                                             RD  73
      CALL FFLD (THA,PHA,ETH,EPH)                                        RD  74
      GO TO 10                                                           RD  75
    9 CALL GFLD (RFLD/WLAM,PHA,THET/WLAM,ETH,EPH,ERD,ZRATI,KSYMP)        RD  76
      ERDM=CABS(ERD)                                                     RD  77
      ERDA=CANG(ERD)                                                     RD  78
   10 ETHM2=REAL(ETH*CONJG(ETH))                                         RD  79
      ETHM=SQRT(ETHM2)                                                   RD  80
      ETHA=CANG(ETH)                                                     RD  81
      EPHM2=REAL(EPH*CONJG(EPH))                                         RD  82
      EPHM=SQRT(EPHM2)                                                   RD  83
      EPHA=CANG(EPH)                                                     RD  84
      IF (IFAR.EQ.1) GO TO 28                                            RD  85
C     ELLIPTICAL POLARIZATION CALC.                                      RD  86
      IF (ETHM2.GT.1.E-20.OR.EPHM2.GT.1.E-20) GO TO 11                   RD  87
      TILTA=0.                                                           RD  88
      EMAJR2=0.                                                          RD  89
      EMINR2=0.                                                          RD  90
      AXRAT=0.                                                           RD  91
      ISENS=HBLK                                                         RD  92
      GO TO 16                                                           RD  93
   11 DFAZ=EPHA-ETHA                                                     RD  94
      IF (EPHA.LT.0.) GO TO 12                                           RD  95
      DFAZ2=DFAZ-360.                                                    RD  96
      GO TO 13                                                           RD  97
   12 DFAZ2=DFAZ+360.                                                    RD  98
   13 IF (ABS(DFAZ).GT.ABS(DFAZ2)) DFAZ=DFAZ2                            RD  99
      CDFAZ=COS(DFAZ*TA)                                                 RD 100
      TSTOR1=ETHM2-EPHM2                                                 RD 101
      TSTOR2=2.*EPHM*ETHM*CDFAZ                                          RD 102
      TILTA=.5*ATGN2(TSTOR2,TSTOR1)                                      RD 103
      STILTA=SIN(TILTA)                                                  RD 104
      TSTOR1=TSTOR1*STILTA*STILTA                                        RD 105
      TSTOR2=TSTOR2*STILTA*COS(TILTA)                                    RD 106
      EMAJR2=-TSTOR1+TSTOR2+ETHM2                                        RD 107
      EMINR2=TSTOR1-TSTOR2+EPHM2                                         RD 108
      IF (EMINR2.LT.0.) EMINR2=0.                                        RD 109
      AXRAT=SQRT(EMINR2/EMAJR2)                                          RD 110
      TILTA=TILTA*TD                                                     RD 111
      IF (AXRAT.GT.1.E-5) GO TO 14                                       RD 112
      ISENS=HPOL(1)                                                      RD 113
      GO TO 16                                                           RD 114
   15 IF (DFAZ.GT.0.) GO TO 15                                           RD 115
      ISENS=HPOL(2)                                                      RD 116
      GO TO 16                                                           RD 117
   15 ISENS=HPOL(3)                                                      RD 118
   16 GNMJ=DB10(GCON*EMAJR2)                                             RD 119
      GNMN=DB10(GCON*EMINR2)                                             RD 120
      GNV=DB10(GCON*ETHM2)                                               RD 121
      GNH=DB10(GCON*EPHM2)                                               RD 122
      GTOT=DB10(GCON*(ETHM2+EPHM2))                                      RD 123
      IF (INOR.LT.1) GO TO 23                                            RD 124
      I=I+1                                                              RD 125
      IF (I.GT.NORMAX) GO TO 23                                          RD 126
      GO TO (17,18,19,20,21), INOR                                       RD 127
   17 TSTOR1=GNMJ                                                        RD 128
```

```
      GO TO 22                                                                  RD 129
18    TSTOR1=GNMN                                                               RD 130
      GO TO 22                                                                  RD 131
19    TSTOR1=GNV                                                                RD 132
      GO TO 22                                                                  RD 133
20    TSTOR1=GNH                                                                RD 134
      GO TO 22                                                                  RD 135
21    TSTOR1=GTOT                                                               RD 136
22    GAIN(I)=TSTOR1                                                            RD 137
      IF (TSTOR1.GT.GMAX) GMAX=TSTOR1                                           RD 138
23    IF (IAVP.EQ.0) GO TO 24                                                   RD 139
      TSTOR1=GCOP*(ETHM2+EPHM2)                                                 RD 140
      TMP3=THA-TMP2                                                             RD 141
      TMP4=THA+TMP2                                                             RD 142
      IF (KTH.EQ.1) TMP3=THA                                                    RD 143
      IF (KTH.EQ.NTH) TMP4=THA                                                  RD 144
      DA=ABS(TMP1*(COS(TMP3)-COS(TMP4)))                                        RD 145
      IF (KPH.EQ.1.OR.KPH.EQ.NPH) DA=.5*DA                                      RD 146
      PINT=PINT+TSTOR1*DA                                                       RD 147
      IF (IAVP.EQ.2) GO TO 29                                                   RD 148
24    IF (IAX.EQ.1) GO TO 25                                                    RD 149
      TMP5=GNMJ                                                                 RD 150
      TMP6=GNMN                                                                 RD 151
      GO TO 26                                                                  RD 152
25    TMP5=GNV                                                                  RD 153
      TMP6=GNH                                                                  RD 154
26    ETHM=ETHM*WLAM                                                            RD 155
      EPHM=EPHM*WLAM                                                            RD 156
      IF (RFLD.LT.1.E-20) GO TO 27                                              RD 157
      ETHM=ETHM*EXRM                                                            RD 158
      ETHA=ETHA+EXRA                                                            RD 159
      EPHM=EPHM*EXRM                                                            RD 160
      EPHA=EPHA+EXRA                                                            RD 161
27    PRINT 42, THET,PHI,TMP5,TMP6,GTOT,AXRAT,TILTA,ISENS,ETHM,ETHA,EPHM RD 162
     1,EPHA                                                                     RD 163
      GO TO 29                                                                  RD 164
28    PRINT 43, RFLD,PHI,THET,ETHM,ETHA,EPHM,EPHA,ERDM,ERDA                     RD 165
29    CONTINUE                                                                  RD 166
      IF (IAVP.EQ.0) GO TO 30                                                   RD 167
      TMP3=THETS*TA                                                             RD 168
      TMP4=TMP3+DTH*TA*FLOAT(NTH-1)                                             RD 169
      TMP3=ABS(DPH*TA*FLOAT(NPH-1)*(COS(TMP3)-COS(TMP4)))                       RD 170
      PINT=PINT/TMP3                                                            RD 171
      TMP3=TMP3/PI                                                              RD 172
      PRINT 44, PINT,TMP3                                                       RD 173
30    IF (INOR.EQ.0) GO TO 34                                                   RD 174
      IF (ABS(GNOR).GT.1.E-20) GMAX=GNOR                                        RD 175
      ITMP1=(INOR-1)*2+1                                                        RD 176
      ITMP2=ITMP1+1                                                             RD 177
      PRINT 45, IGNTP(ITMP1),IGNTP(ITMP2),GMAX                                  RD 178
      ITMP2=NPH*NTH                                                             RD 179
      IF (ITMP2.GT.NORMAX) ITMP2=NORMAX                                         RD 180
      ITMP1=(ITMP2+2)/3                                                         RD 181
      ITMP2=ITMP1*3-ITMP2                                                       RD 182
      ITMP3=ITMP1                                                               RD 183
      ITMP4=2*ITMP1                                                             RD 184
      IF (ITMP2.EQ.2) ITMP4=ITMP4-1                                             RD 185
      DO 31 I=1,ITMP1                                                           RD 186
      ITMP3=ITMP3+1                                                             RD 187
      ITMP4=ITMP4+1                                                             RD 188
      J=(I-1)/NTH                                                               RD 189
      TMP1=THETS+FLOAT(I-J*NTH-1)*DTH                                           RD 190
      TMP2=PHIS+FLOAT(J)*DPH                                                    RD 191
      J=(ITMP3-1)/NTH                                                           RD 192
```

```
      TMP3=THETS+FLOAT(ITMP3-J*NTH-1)*DTH                                RD 193
      TMP4=PHIS+FLOAT(J)*DPH                                             RD 194
      J=(ITMP4-1)/NTH                                                    RD 195
      TMP5=THETS+FLOAT(ITMP4-J*NTH-1)*DTH                                RD 196
      TMP6=PHIS+FLOAT(J)*DPH                                             RD 197
      TSTOR1=GAIN(I)-GMAX                                                RD 198
      IF (I.EQ.ITMP1.AND.ITMP2.NE.0) GO TO 32                            RD 199
      TSTOR2=GAIN(ITMP3)-GMAX                                            RD 200
      PINT=GAIN(ITMP4)-GMAX                                              RD 201
31    PRINT 46, TMP1,TMP2,TSTOR1,TMP3,TMP4,TSTOR2,TMP5,TMP6,PINT         RD 202
      GO TO 34                                                           RD 203
32    IF (ITMP2.EQ.2) GO TO 33                                           RD 204
      TSTOR2=GAIN(ITMP3)-GMAX                                            RD 205
      PRINT 46, TMP1,TMP2,TSTOR1,TMP3,TMP4,TSTOR2                        RD 206
      GO TO 34                                                           RD 207
33    PRINT 46, TMP1,TMP2,TSTOR1                                         RD 208
34    RETURN                                                             RD 209
C                                                                        RD 210
35    FORMAT (///,31X,39H- - - FAR FIELD GROUND PARAMETERS - - -,//)     RD 211
36    FORMAT (40X,25HRADIAL WIRE GROUND SCREEN,/,40X,I5,6H WIRES,/,40X,1 RD 212
     12HWIRE LENGTH=,F8.2,7H METERS,/,40X,12HWIRE RADIUS=,E10.3,7H METER RD 213
     2S)                                                                RD 214
37    FORMAT (40X,A6,6H CLIFF,/,40X,14HEDGE DISTANCE=,F9.2,7H METERS,/,4 RD 215
     10X,7HHEIGHT=,F8.2,7H METERS,/,40X,15HSECOND MEDIUM -,/,40X,27HRELA RD 216
     2TIVE DIELECTRIC CONST.=,F7.3,/,40X,13HCONDUCTIVITY=,E10.3,5H MHOS) RD 217
38    FORMAT (///,48X,30H- - - RADIATION PATTERNS - - -)                 RD 218
39    FORMAT (54X,6HRANGE=,E13.6,7H METERS,/,54X,12HEXP(-JKR)/R=,E12.5,9 RD 219
     1H AT PHASE,F7.2,8H DEGREES,/)                                     RD 220
40    FORMAT (/,2X,14H- - ANGLES - -,7X,2A6,7HGAINS -,7X,24H- - - POLARI RD 221
     1ZATION - - -,4X,20H- - - E(THETA) - - -,4X,16H- - - E(PHI) - -,2H  RD 222
     2-,/,2X,5HTHETA,5X,3HPHI,7X,A6,2X,A6,3X,5HTOTAL,6X,5HAXIAL,5X,4HTIL RD 223
     3T,3X,5HSENSE,2(5X,9HMAGNITUDE,4X,6HPHASE ),/,2(1X,7HDEGREES,1X),3( RD 224
     46X,2HDB),8X,5HRATIO,5X,4HDEG.,8X,2(6X,7HVOLTS/M,4X,7HDEGREES))    RD 225
41    FORMAT (///,28X,40H - - - RADIATED FIELDS NEAR GROUND - - -,//,6X, RD 226
     120H- - - LOCATION - - -,10X,16H- - E(THETA) - -,8X,14H- - E(PHI) - RD 227
     2 -,8X,17H- - E(RADIAL) - -,/,7X,3HRHO,6X,3HPHI,9X,1HZ,12X,3HMAG,6X RD 228
     3,5HPHASE,9X,3HMAG,6X,5HPHASE,9X,3HMAG,6X,5HPHASE,/,5X,6HMETERS,3X, RD 229
     47HDEGREES,4X,6HMETERS,8X,7HVOLTS/M,3X,7HDEGREES,6X,7HVOLTS/M,3X,7H RD 230
     5DEGREES,6X,7HVOLTS/M,3X,7HDEGREES,/)                              RD 231
42    FORMAT (1X,F7.2,F9.2,3X,3F8.2,F11.5,F9.2,2X,A6,2(E15.5,F9.2))      RD 232
43    FORMAT (3X,F9.2,2X,F7.2,2X,F9.2,1X,3(3X,E11.4,2X,F7.2))            RD 233
44    FORMAT (//,3X,19HAVERAGE POWER GAIN=,E12.5,7X, 31HSOLID ANGLE USED RD 234
     1 IN AVERAGING=(,F7.4,16H)*PI STERADIANS.,//)                       RD 235
45    FORMAT (//,37X,31H- - - - NORMALIZED GAIN - - - -,//,37X,2A6,4HGAI RD 236
     1N,/,38X,22HNORMALIZATION FACTOR =,F9.2,3H DB,//,3(4X,14H- - ANGLES RD 237
     2 - -,6X,4HGAIN,7X),/,3(4X,5HTHETA,5X,3HPHI,8X,2HDB,8X),/,3(3X,7HDE RD 238
     3GREES,2X,7HDEGREES,16X))                                          RD 239
46    FORMAT (3(1X,2F9.2,1X,F9.2,6X))                                    RD 240
      END                                                                RD 241-
```

REBLK

PURPOSE

To read the matrix B by blocks of rows and write it by blocks of columns.

METHOD

When ICASX is 3 or 4 subroutine CMNGF writes B to file 14 by blocks of rows. Filling B by rows is convenient since the field of a single segment may contribute to several columns. However, blocks of columns are needed when $A^{-1}B$ is computed. Hence the format is converted.

NBBX is the number of block of B stored by rows and NBBL is the number of blocks stored by columns. The loop from RB16 to RB23 reads file 14 and stores the elements for block NPB of columns. This process is repeated for each of the NBBL blocks of columns.

SYMBOL DICTIONARY

- B = array for blocks of columns of B
- BX = array for blocks of rows of B
- N2C = number of columns in B
- NB = number of rows in B
- NBX = number of rows in blocks of rows of B (NPBX)
- NPB = number of columns in blocks of columns (NPBL or NLBL for last block)
- NPX = NPBX or NLBX for last block of rows

```
      SUBROUTINE REBLK (B,BX,NB,NBX,N2C)                                RB   1
C     REBLOCK ARRAY B IN N.G.F  SOLUTION FROM BLOCKS OF ROWS ON TAPE14  RB   2
C     TO BLOCKS OF COLUMNS ON TAPE16                                    RB   3
      COMPLEX B,BX                                                      RB   4
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I RB   5
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                RB   6
      DIMENSION B(NB,1), BX(NBX,1)                                      RB   7
      REWIND 16                                                         RB   8
      NIB=0                                                             RB   9
      NPB=NPBL                                                          RB  10
      DO 3 IB=1,NBBL                                                    RB  11
      IF (IB.EQ.NBBL) NPB=NLBL                                          RB  12
      REWIND 14                                                         RB  13
      NIX=0                                                             RB  14
      NPX=NPBX                                                          RB  15
      DO 2 IBX=1,NBBX                                                   RB  16
      IF (IBX.EQ.NBBX) NPX=NLBX                                         RB  17
      READ (14) ((BX(I,J),I=1,NPX),J=1,N2C)                             RB  18
      DO 1 I=1,NPX                                                      RB  19
      IX=I+NIX                                                          RB  20
      DO 1 J=1,NPB                                                      RB  21
    1 B(IX,J)=BX(I,J+NIB)                                               RB  22
    2 NIX=NIX+NPBX                                                      RB  23
      WRITE (16) ((B(I,J),I=1,NB),J=1,NPB)                              RB  24
    3 NIB=NIB+NPBL                                                      RB  25
      REWIND 14                                                         RB  26
      REWIND 16                                                         RB  27
      RETURN                                                            RB  28
      END                                                               RB  29-
```

REFLC

PURPOSE

To generate geometry data for structures having plane or cylindrical symmetry by forming symmetric images of a previously defined structure unit.

METHOD

The first part of the code, from statement RE20 to RE153, forms plane symmetric structures by reflecting segments and patches in the coordinate planes. The reflection planes are selected by the formal parameters IX, IY, and IZ. If IZ is greater than zero, an image of the existing segments and patches is formed by reflection in the x-y plane, which will be called reflection along the z axis. Next, if IY is greater than zero, an image of the existing segments and patches, including those generated in the previous step by reflection along the z axis, is formed by reflection along the y axis. Finally, if IX is greater than zero, an image of all segments and patches, including any previously formed by reflection along the z and y axes, is formed by reflection along the x axis. Any combination of zero and non-zero values of IX, IY, and IZ may be used to generate structures with one, two, or three planes of symmetry. Tag numbers of image segments are incremented by ITX from tags of the original segments, except that tags of zero are not incremented. After each reflection in a coordinate plane, ITX is doubled. Thus, if ITX is initially greater than the largest tag of the existing segments, no duplicate tags will be formed by reflection in one, two, or three planes.

The code from RE157 to RE204 forms cylindrically symmetric structures by forming images of previously defined segments and patches rotated about the z axis. The number of images, including the original structure, is selected by NOP in the formal parameters. The angle by which each image is rotated about the z axis from the previous image is computed as $2\pi/NOP$, so that the images are uniformly distributed about the z axis. Tag numbers of segments are incremented by ITX, except that tags of zero are not incremented.

When REFLC is used to form structures with either plane or cylindrical symmetry, the data in COMMON/DATA/ is set so that the program will take advantage of symmetry in filling and factoring the matrix. This is done by setting N equal to the total number of segments but leaving NP equal to the number of segments in the original structure unit that was reflected or

rotated. The symmetry flag IPSYM is also set to indicate the type of symmetry: positive values indicating plane symmetry and negative values cylindrical symmetry. These symmetry conditions may later be changed if the structure is modified in such a way that symmetry is destroyed.

SYMBOL DICTIONARY

ABS = external routine (absolute value)
COS = external routine (cosine)
CS = cos (2π/NOP)
E1 = segment coordinate (temporary storage)
E2 = segment coordinate (temporary storage)
FNOP = NOP
I = DO loop index
ITAGI = segment tag (temporary storage)
ITI = segment tag increment
ITX = segment tag increment
IX = flag for reflection along x axis
IY = flag for reflection along y axis
IZ = flag for reflection along z axis
J = array location for new patch data
K = segment index and array location for old patch data
NOP = number of sections in cylindrically symmetric structure
NX = segment index and array location for new patch data
NNX = array location for old patch
SAM = 2π/NOP
SIN = external routine (sine)
SS = sin (2π/NOP)
T1X, T1Y, T1Z, T2X, T2Y, T2Z = x, y, z components of $\hat{t}_1$ and $\hat{t}_2$
XK = x coordinate of segment
X2(I) = x coordinate of end two of segment I
YK = y coordinate of segment

Y2(I) = y coordinate of end two of segment I

Z2(I) = z coordinate of end two of segment I

CONSTANTS

1.E-6 = tolerance in test for zero

1.E-5 = tolerance in test for zero

6.283185308 = 2π

```
      SUBROUTINE REFLC (IX,IY,IZ,ITX,NOP)                                RE   1
C                                                                        RE   2
C     REFLC REFLECTS PARTIAL STRUCTURE ALONG X,Y, OR Z AXES OR ROTATES   RE   3
C     STRUCTURE TO COMPLETE A SYMMETRIC STRUCTURE.                       RE   4
C                                                                        RE   5
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 RE   6
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( RE   7
     2300),WLAM,IPSYM                                                    RE   8
      COMMON /ANGL/ SALP(300)                                            RE   9
      DIMENSION T1X(1), T1Y(1), T1Z(1), T2X(1), T2Y(1), T2Z(1), X2(1), Y RE  10
     12(1), Z2(1)                                                        RE  11
      EQUIVALENCE (T1X,SI), (T1Y,ALP), (T1Z,BET), (T2X,ICON1), (T2Y,ICON RE  12
     12), (T2Z,ITAG), (X2,SI), (Y2,ALP), (Z2,BET)                        RE  13
      NP=N                                                               RE  14
      MP=M                                                               RE  15
      IPSYM=0                                                            RE  16
      ITI=ITX                                                            RE  17
      IF (IX.LT.0) GO TO 19                                              RE  18
      IF (NOP.EQ.0) RETURN                                               RE  19
      IPSYM=1                                                            RE  20
      IF (IZ.EQ.0) GO TO 6                                               RE  21
C                                                                        RE  22
C     REFLECT ALONG Z AXIS                                               RE  23
C                                                                        RE  24
      IPSYM=2                                                            RE  25
      IF (N.LT.N2) GO TO 3                                               RE  26
      DO 2 I=N2,N                                                        RE  27
      NX=I+N-N1                                                          RE  28
      E1=Z(I)                                                            RE  29
      E2=Z2(I)                                                           RE  30
      IF (ABS(E1)+ABS(E2).GT.1.E-5.AND.E1*E2.GE.-1.E-6) GO TO 1          RE  31
      PRINT 24, I                                                        RE  32
      STOP                                                               RE  33
1     X(NX)=X(I)                                                         RE  34
      Y(NX)=Y(I)                                                         RE  35
      Z(NX)=-E1                                                          RE  36
      X2(NX)=X2(I)                                                       RE  37
      Y2(NX)=Y2(I)                                                       RE  38
      Z2(NX)=-E2                                                         RE  39
      ITAGI=ITAG(I)                                                      RE  40
      IF (ITAGI.EQ.0) ITAG(NX)=0                                         RE  41
      IF (ITAGI.NE.0) ITAG(NX)=ITAGI+ITI                                 RE  42
2     BI(NX)=BI(I)                                                       RE  43
      N=N*2-N1                                                           RE  44
      ITI=ITI*2                                                          RE  45
3     IF (M.LT.M2) GO TO 6                                               RE  46
      NXX=LD+1-M1                                                        RE  47
      DO 5 I=M2,M                                                        RE  48
      NXX=NXX-1                                                          RE  49
      NX=NXX-M+M1                                                        RE  50
      IF (ABS(Z(NXX)).GT.1.E-10) GO TO 4                                 RE  51
      PRINT 25, I                                                        RE  52
      STOP                                                               RE  53
4     X(NX)=X(NXX)                                                       RE  54
      Y(NX)=Y(NXX)                                                       RE  55
      Z(NX)=-Z(NXX)                                                      RE  56
      T1X(NX)=T1X(NXX)                                                   RE  57
      T1Y(NX)=T1Y(NXX)                                                   RE  58
      T1Z(NX)=-T1Z(NXX)                                                  RE  59
      T2X(NX)=-T2X(NXX)                                                  RE  60
      T2Y(NX)=T2Y(NXX)                                                   RE  61
      T2Z(NX)=-T2Z(NXX)                                                  RE  62
      SALP(NX)=-SALP(NXX)                                                RE  63
5     BI(NX)=BI(NXX)                                                     RE  64
```

```
      M=M*2-M1                                                          RE  65
    6 IF (IY.EQ.0) GO TO 12                                             RE  66
C                                                                       RE  67
C     REFLECT ALONG Y AXIS                                              RE  68
C                                                                       RE  69
      IF (N.LT.N2) GO TO 9                                              RE  70
      DO 8 I=N2,N                                                       RE  71
      NX=I+N-N1                                                         RE  72
      E1=Y(I)                                                           RE  73
      E2=Y2(I)                                                          RE  74
      IF (ABS(E1)+ABS(E2).GT.1.E-5.AND.E1*E2.GE.-1.E-6) GO TO 7          RE  75
      PRINT 24, I                                                       RE  76
      STOP                                                              RE  77
    7 X(NX)=X(I)                                                        RE  78
      Y(NX)=-E1                                                         RE  79
      Z(NX)=Z(I)                                                        RE  80
      X2(NX)=X2(I)                                                      RE  81
      Y2(NX)=-E2                                                        RE  82
      Z2(NX)=Z2(I)                                                      RE  83
      ITAGI=ITAG(I)                                                     RE  84
      IF (ITAGI.EQ.0) ITAG(NX)=0                                        RE  85
      IF (ITAGI.NE.0) ITAG(NX)=ITAGI+ITI                                RE  86
    8 BI(NX)=BI(I)                                                      RE  87
      N=N*2-N1                                                          RE  88
      ITI=ITI*2                                                         RE  89
    9 IF (M.LT.M2) GO TO 12                                             RE  90
      NXX=LD+1-M1                                                       RE  91
      DO 11 I=M2,M                                                      RE  92
      NXX=NXX-1                                                         RE  93
      NX=NXX-M+M1                                                       RE  94
      IF (ABS(Y(NXX)).GT.1.E-10) GO TO 10                               RE  95
      PRINT 25, I                                                       RE  96
      STOP                                                              RE  97
   10 X(NX)=X(NXX)                                                      RE  98
      Y(NX)=-Y(NXX)                                                     RE  99
      Z(NX)=Z(NXX)                                                      RE 100
      T1X(NX)=T1X(NXX)                                                  RE 101
      T1Y(NX)=-T1Y(NXX)                                                 RE 102
      T1Z(NX)=T1Z(NXX)                                                  RE 103
      T2X(NX)=T2X(NXX)                                                  RE 104
      T2Y(NX)=-T2Y(NXX)                                                 RE 105
      T2Z(NX)=T2Z(NXX)                                                  RE 106
      SALP(NX)=-SALP(NXX)                                               RE 107
   11 BI(NX)=BI(NXX)                                                    RE 108
      M=M*2-M1                                                          RE 109
   12 IF (IX.EQ.0) GO TO 18                                             RE 110
C                                                                       RE 111
C     REFLECT ALONG X AXIS                                              RE 112
C                                                                       RE 113
      IF (N.LT.N2) GO TO 15                                             RE 114
      DO 14 I=N2,N                                                      RE 115
      NX=I+N-N1                                                         RE 116
      E1=X(I)                                                           RE 117
      E2=X2(I)                                                          RE 118
      IF (ABS(E1)+ABS(E2).GT.1.E-5.AND.E1*E2.GE.-1.E-6) GO TO 13         RE 119
      PRINT 24, I                                                       RE 120
      STOP                                                              RE 121
   13 X(NX)=-E1                                                         RE 122
      Y(NX)=Y(I)                                                        RE 123
      Z(NX)=Z(I)                                                        RE 124
      X2(NX)=-E2                                                        RE 125
      Y2(NX)=Y2(I)                                                      RE 126
      Z2(NX)=Z2(I)                                                      RE 127
      ITAGI=ITAG(I)                                                     RE 128
```

```
      IF (ITAGI.EQ.0) ITAG(NX)=0                                        RE 129
      IF (ITAGI.NE.0) ITAG(NX)=ITAGI+ITI                                RE 130
14    BI(NX)=BI(I)                                                      RE 131
      N=N*2-N1                                                          RE 132
15    IF (M.LT.M2) GO TO 18                                             RE 133
      NXX=LD+1-M1                                                       RE 134
      DO 17 I=M2,M                                                      RE 135
      NXX=NXX-1                                                         RE 136
      NX=NXX-M+M1                                                       RE 137
      IF (ABS(X(NXX)).GT.1.E-10) GO TO 16                               RE 138
      PRINT 25, I                                                       RE 139
      STOP                                                              RE 140
16    X(NX)=-X(NXX)                                                     RE 141
      Y(NX)=Y(NXX)                                                      RE 142
      Z(NX)=Z(NXX)                                                      RE 143
      T1X(NX)=-T1X(NXX)                                                 RE 144
      T1Y(NX)=T1Y(NXX)                                                  RE 145
      T1Z(NX)=T1Z(NXX)                                                  RE 146
      T2X(NX)=-T2X(NXX)                                                 RE 147
      T2Y(NX)=T2Y(NXX)                                                  RE 148
      T2Z(NX)=T2Z(NXX)                                                  RE 149
      SALP(NX)=-SALP(NXX)                                               RE 150
17    BI(NX)=BI(NXX)                                                    RE 151
      M=M*2-M1                                                          RE 152
18    RETURN                                                            RE 153
C                                                                       RE 154
C     REPRODUCE STRUCTURE WITH ROTATION TO FORM CYLINDRICAL STRUCTURE   RE 155
C                                                                       RE 156
19    FNOP=NOP                                                          RE 157
      IPSYM=-1                                                          RE 158
      SAM=6.283185308/FNOP                                              RE 159
      CS=COS(SAM)                                                       RE 160
      SS=SIN(SAM)                                                       RE 161
      IF (N.LT.N2) GO TO 21                                             RE 162
      N=N1+(N-N1)*NOP                                                   RE 163
      NX=NP+1                                                           RE 164
      DO 20 I=NX,N                                                      RE 165
      K=I-NP+N1                                                         RE 166
      XK=X(K)                                                           RE 167
      YK=Y(K)                                                           RE 168
      X(I)=XK*CS-YK*SS                                                  RE 169
      Y(I)=XK*SS+YK*CS                                                  RE 170
      Z(I)=Z(K)                                                         RE 171
      XK=X2(K)                                                          RE 172
      YK=Y2(K)                                                          RE 173
      X2(I)=XK*CS-YK*SS                                                 RE 174
      Y2(I)=XK*SS+YK*CS                                                 RE 175
      Z2(I)=Z2(K)                                                       RE 176
      ITAGI=ITAG(K)                                                     RE 177
      IF (ITAGI.EQ.0) ITAG(I)=0                                         RE 178
      IF (ITAGI.NE.0) ITAG(I)=ITAGI+ITI                                 RE 179
20    BI(I)=BI(K)                                                       RE 180
21    IF (M.LT.M2) GO TO 23                                             RE 181
      M=M1+(M-M1)*NOP                                                   RE 182
      NX=MP+1                                                           RE 183
      K=LD+1-M1                                                         RE 184
      DO 22 I=NX,M                                                      RE 185
      K=K-1                                                             RE 186
      J=K-MP+M1                                                         RE 187
      XK=X(K)                                                           RE 188
      YK=Y(K)                                                           RE 189
      X(J)=XK*CS-YK*SS                                                  RE 190
      Y(J)=XK*SS+YK*CS                                                  RE 191
      Z(J)=Z(K)                                                         RE 192
```

```
      XK=T1X(K)                                                         RE 193
      YK=T1Y(K)                                                         RE 194
      T1X(J)=XK*CS-YK*SS                                                RE 195
      T1Y(J)=XK*SS+YK*CS                                                RE 196
      T1Z(J)=T1Z(K)                                                     RE 197
      XK=T2X(K)                                                         RE 198
      YK=T2Y(K)                                                         RE 199
      T2X(J)=XK*CS-YK*SS                                                RE 200
      T2Y(J)=XK*SS+YK*CS                                                RE 201
      T2Z(J)=T2Z(K)                                                     RE 202
      SALP(J)=SALP(K)                                                   RE 203
   22 BI(J)=BI(K)                                                       RE 204
   23 RETURN                                                            RE 205
    C                                                                   RE 206
   24 FORMAT (29H GEOMETRY DATA ERROR--SEGMENT,I5,26H LIES IN PLANE OF S RE 207
     1YMMETRY)                                                          RE 208
   25 FORMAT (27H GEOMETRY DATA ERROR--PATCH,I4,26H LIES IN PLANE OF SYM RE 209
     1METRY)                                                            RE 210
      END                                                               RE 211-
```

ROM2

PURPOSE

To numerically integrate over the current distribution on a segment to obtain the field due to the Sommerfeld integral term.

METHOD

ROM2 integrates the product of $\bar{E}_s(\bar{r})$ (see discussion of EFLD) and the current over a segment. Separate integrals are evaluated for current distributions of constant, sin $k(s - s_0)$ and cos $k(s - s_0)$. With three vector components of the field, there are nine integrals evaluated simultaneously and stored in the array SUM. The integration method is the same as that described for subroutine INTX, but loops from one through nine are used at each step.

The parameter DMIN is set in EFLD to

$$DMIN = 0.01 \left[|E_x'|^2 + |E_y'|^2 + |E_z'|^2\right]^{1/2}$$

where $\bar{E}' = \int_{\text{segment}} \left[\bar{E}_D(\bar{r}) + \frac{k_1^2 - k_2^2}{k_1^2 + k_2^2} \bar{E}_I(\bar{r})\right] ds$.

DMIN is passed to TEST as the lower limit for the denominator in the relative error evaluation to avoid trying to maintain relative accuracy in integrating the Sommerfeld integral when it is much smaller than the other terms.

SYMBOL DICTIONARY

A	= lower limit of integral
B	= upper limit of integral
DMIN	= minimum for denominator in relative error test
DZ	= subinterval size
DZOT	= 0.5 DZ
EP	= tolerance for hitting upper limit

G1, G2, G3, G4, G5	= integrand values at points within the subinterval
N	= number of functions (9)
NM	= minimum subinterval size is (B - A)/NM
NS	= present subinterval size is (B - A)/NS
NT	= counter to control increasing subinterval size
NTS	= larger values retard increasing subinterval size
NX	= maximum subinterval size is (B - A)/NX
RX	= relative error limit
S	= B - A
SUM	= array for integral values
T00, T01, T02, T10, T11, T20	= (see subroutine INTX)
TMAG1, TMAG2	= sum of the magnitudes of the integral contributions for the constant current distribution
Z	= integration variable at left side of subinterval
ZE	= B
ZEND	= upper limit

CONSTANTS

1.E-4 = relative error criterion

65536 = limit for cutting subinterval size

```
      SUBROUTINE ROM2 (A,B,SUM,DMIN)                                    RO   1
C                                                                       RO   2
C     FOR THE SOMMERFELD GROUND OPTION, ROM2 INTEGRATES OVER THE SOURCE RO   3
C     SEGMENT TO OBTAIN THE TOTAL FIELD DUE TO GROUND.  THE METHOD OF   RO   4
C     VARIABLE INTERVAL WIDTH ROMBERG INTEGRATION IS USED.  THERE ARE 9 RO   5
C     FIELD COMPONENTS - THE X, Y, AND Z COMPONENTS DUE TO CONSTANT,    RO   6
C     SINE, AND COSINE CURRENT DISTRIBUTIONS.                           RO   7
C                                                                       RO   8
      COMPLEX SUM,G1,G2,G3,G4,G5,T00,T01,T10,T02,T11,T20                RO   9
      DIMENSION SUM(9), G1(9), G2(9), G3(9), G4(9), G5(9), T01(9), T10(9 RO  10
     1), T20(9)                                                         RO  11
      DATA NM,NTS,NX,N/65536,4,1,9/,RX/1.E-4/                           RO  12
      Z=A                                                               RO  13
      ZE=B                                                              RO  14
      S=B-A                                                             RO  15
      IF (S.GE.0.) GO TO 1                                              RO  16
      PRINT 18                                                          RO  17
      STOP                                                              RO  18
1     EP=S/(1.E4*NM)                                                    RO  19
      ZEND=ZE-EP                                                        RO  20
      DO 2 I=1,N                                                        RO  21
2     SUM(I)=(0.,0.)                                                    RO  22
      NS=NX                                                             RO  23
      NT=0                                                              RO  24
      CALL SFLDS (Z,G1)                                                 RO  25
3     DZ=S/NS                                                           RO  26
      IF (Z+DZ.LE.ZE) GO TO 4                                           RO  27
      DZ=ZE-Z                                                           RO  28
      IF (DZ.LE.EP) GO TO 17                                            RO  29
4     DZOT=DZ*.5                                                        RO  30
      CALL SFLDS (Z+DZOT,G3)                                            RO  31
      CALL SFLDS (Z+DZ,G5)                                              RO  32
5     TMAG1=0.                                                          RO  33
      TMAG2=0.                                                          RO  34
C                                                                       RO  35
C     EVALUATE 3 POINT ROMBERG RESULT AND TEST CONVERGENCE.             RO  36
C                                                                       RO  37
      DO 6 I=1,N                                                        RO  38
      T00=(G1(I)+G5(I))*DZOT                                            RO  39
      T01(I)=(T00+DZ*G3(I))*.5                                          RO  40
      T10(I)=(4.*T01(I)-T00)/3.                                         RO  41
      IF (I.GT.3) GO TO 6                                               RO  42
      TR=REAL(T01(I))                                                   RO  43
      TI=AIMAG(T01(I))                                                  RO  44
      TMAG1=TMAG1+TR*TR+TI*TI                                           RO  45
      TR=REAL(T10(I))                                                   RO  46
      TI=AIMAG(T10(I))                                                  RO  47
      TMAG2=TMAG2+TR*TR+TI*TI                                           RO  48
6     CONTINUE                                                          RO  49
      TMAG1=SQRT(TMAG1)                                                 RO  50
      TMAG2=SQRT(TMAG2)                                                 RO  51
      CALL TEST(TMAG1,TMAG2,TR,0.,0.,TI,DMIN)                           RO  52
      IF(TR.GT.RX)GO TO 8                                               RO  53
      DO 7 I=1,N                                                        RO  54
7     SUM(I)=SUM(I)+T10(I)                                              RO  55
      NT=NT+2                                                           RO  56
      GO TO 12                                                          RO  57
8     CALL SFLDS (Z+DZ*.25,G2)                                          RO  58
      CALL SFLDS (Z+DZ*.75,G4)                                          RO  59
      TMAG1=0.                                                          RO  60
      TMAG2=0.                                                          RO  61
C                                                                       RO  62
C     EVALUATE 5 POINT ROMBERG RESULT AND TEST CONVERGENCE.             RO  63
C                                                                       RO  64
```

```
      DO 9 I=1,N                                                        RO  65
      T02=(T01(I)+DZOT*(G2(I)+G4(I)))*.5                                RO  66
      T11=(4.*T02-T01(I))/3.                                            RO  67
      T20(I)=(16.*T11-T10(I))/15.                                       RO  68
      IF (I.GT.3) GO TO 9                                               RO  69
      TR=REAL(T11)                                                      RO  70
      TI=AIMAG(T11)                                                     RO  71
      TMAG1=TMAG1+TR*TR+TI*TI                                           RO  72
      TR=REAL(T20(I))                                                   RO  73
      TI=AIMAG(T20(I))                                                  RO  74
      TMAG2=TMAG2+TR*TR+TI*TI                                           RO  75
 9    CONTINUE                                                          RO  76
      TMAG1=SQRT(TMAG1)                                                 RO  77
      TMAG2=SQRT(TMAG2)                                                 RO  78
      CALL TEST(TMAG1,TMAG2,TR,0.,0.,TI,DMIN)                           RO  79
      IF(TR.GT.RX)GO TO 14                                              RO  80
 10   DO 11 I=1,N                                                       RO  81
 11   SUM(I)=SUM(I)+T20(I)                                              RO  82
      NT=NT+1                                                           RO  83
 12   Z=Z+DZ                                                            RO  84
      IF (Z.GT.ZEND) GO TO 17                                           RO  85
      DO 13 I=1,N                                                       RO  86
 13   G1(I)=G5(I)                                                       RO  87
      IF (NT.LT.NTS.OR.NS.LE.NX) GO TO 3                                RO  88
      NS=NS/2                                                           RO  89
      NT=1                                                              RO  90
      GO TO 3                                                           RO  91
 14   NT=0                                                              RO  92
      IF (NS.LT.NM) GO TO 15                                            RO  93
      PRINT 18, Z                                                       RO  94
      GO TO 10                                                          RO  95
 15   NS=NS*2                                                           RO  96
      DZ=S/NS                                                           RO  97
      DZOT=DZ*.5                                                        RO  98
      DO 16 I=1,N                                                       RO  99
      G5(I)=G3(I)                                                       RO 100
 16   G3(I)=G2(I)                                                       RO 101
      GO TO 5                                                           RO 102
 17   CONTINUE                                                          RO 103
      RETURN                                                            RO 104
C                                                                       RO 105
 18   FORMAT (30H ERROR - B LESS THAN A IN ROM2)                        RO 106
 19   FORMAT (33H ROM2 -- STEP SIZE LIMITED AT Z =,E12.5)               RO 107
      END                                                               RO 108-
```

SBF

PURPOSE

To evaluate the current expansion function associated with a given segment, returning only that portion on a particular segment.

METHOD

SBF is very similar to routine TBF. Both routines evaluate the current expansion functions. However, while TBF stores the coefficients for each segment on which a given expansion function is non-zero, SBF returns the coefficients for only a single specified segment.

In the call to SBF, I is the segment on which the expansion function is centered. IS is the segment for which the function coefficients A_j, B_j and C_j are requested. These coefficients are returned in AA, BB, CC, respectively.

Refer to TBF for a discussion of the coding and variables. One additional variable in SBF -- JUNE -- is set to -1 or +1 if segment IS is found connected to end 1 or end 2, respectively, of segment I. If I = IS and segment I is not connected to a surface or ground plane, then JUNE is set to 0.

```
      SUBROUTINE SBF (I,IS,AA,BB,CC)                                    SB   1
C     COMPUTE COMPONENT OF BASIS FUNCTION I ON SEGMENT IS.              SB   2
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 SB   3
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( SB   4
     2300),WLAM,IPSYM                                                   SB   5
      DATA PI/3.141592654/,JMAX/30/                                     SB   6
      AA=0.                                                             SB   7
      BB=0.                                                             SB   8
      CC=0.                                                             SB   9
      JUNE=0                                                            SB  10
      JSNO=0                                                            SB  11
      PP=0.                                                             SB  12
      JCOX=ICON1(I)                                                     SB  13
      IF (JCOX.GT.10000) JCOX=I                                         SB  14
      JEND=-1                                                           SB  15
      IEND=-1                                                           SB  16
      SIG=-1.                                                           SB  17
      IF (JCOX) 1,11,2                                                  SB  18
1     JCOX=-JCOX                                                        SB  19
      GO TO 3                                                           SB  20
2     SIG=-SIG                                                          SB  21
      JEND=-JEND                                                        SB  22
3     JSNO=JSNO+1                                                       SB  23
      IF (JSNO.GE.JMAX) GO TO 24                                        SB  24
      D=PI*SI(JCOX)                                                     SB  25
      SDH=SIN(D)                                                        SB  26
      CDH=COS(D)                                                        SB  27
      SD=2.*SDH*CDH                                                     SB  28
      IF (D.GT.0.015) GO TO 4                                           SB  29
      OMC=4.*D*D                                                        SB  30
      OMC=((1.3888889E-3*OMC-4.1666666667E-2)*OMC+.5)*OMC               SB  31
      GO TO 5                                                           SB  32
4     OMC=1.-CDH*CDH+SDH*SDH                                            SB  33
5     AJ=1./(ALOG(1./(PI*BI(JCOX)))-.577215664)                         SB  34
      PP=PP-OMC/SD*AJ                                                   SB  35
      IF (JCOX.NE.IS) GO TO 6                                           SB  36
      AA=AJ/SD*SIG                                                      SB  37
      BB=AJ/(2.*CDH)                                                    SB  38
      CC=-AJ/(2.*SDH)*SIG                                               SB  39
      JUNE=IEND                                                         SB  40
6     IF (JCOX.EQ.I) GO TO 9                                            SB  41
      IF (JEND.EQ.1) GO TO 7                                            SB  42
      JCOX=ICON1(JCOX)                                                  SB  43
      GO TO 8                                                           SB  44
7     JCOX=ICON2(JCOX)                                                  SB  45
8     IF (IABS(JCOX).EQ.I) GO TO 10                                     SB  46
      IF (JCOX) 1,24,2                                                  SB  47
9     IF (JCOX.EQ.IS) BB=-BB                                            SB  48
10    IF (IEND.EQ.1) GO TO 12                                           SB  49
11    PM=-PP                                                            SB  50
      PP=0.                                                             SB  51
      NJUN1=JSNO                                                        SB  52
      JCOX=ICON2(I)                                                     SB  53
      IF (JCOX.GT.10000) JCOX=I                                         SB  54
      JEND=1                                                            SB  55
      IEND=1                                                            SB  56
      SIG=-1.                                                           SB  57
      IF (JCOX) 1,12,2                                                  SB  58
12    NJUN2=JSNO-NJUN1                                                  SB  59
      D=PI*SI(I)                                                        SB  60
      SDH=SIN(D)                                                        SB  61
      CDH=COS(D)                                                        SB  62
      SD=2.*SDH*CDH                                                     SB  63
      CD=CDH*CDH-SDH*SDH                                                SB  64
```

```
      IF (D.GT.0.015) GO TO 13                                          SB  65
      OMC=4.*D*D                                                        SB  66
      OMC=((1.3888889E-3*OMC-4.1666666667E-2)*OMC+.5)*OMC               SB  67
      GO TO 14                                                          SB  68
13    OMC=1.-CD                                                         SB  69
14    AP=1./(ALOG(1./(PI*BI(I)))-.577215664)                            SB  70
      AJ=AP                                                             SB  71
      IF (NJUN1.EQ.0) GO TO 19                                          SB  72
      IF (NJUN2.EQ.0) GO TO 21                                          SB  73
      QP=SD*(PM*PP+AJ*AP)+CD*(PM*AP-PP*AJ)                              SB  74
      QM=(AP*OMC-PP*SD)/QP                                              SB  75
      QP=-(AJ*OMC+PM*SD)/QP                                             SB  76
      IF (JUNE) 15,16,16                                                SB  77
15    AA=AA*QM                                                          SB  78
      BB=BB*QM                                                          SB  79
      CC=CC*QM                                                          SB  80
      GO TO 17                                                          SB  81
16    AA=-AA*QP                                                         SB  82
      BB=BB*QP                                                          SB  83
      CC=-CC*QP                                                         SB  84
17    IF (I.NE.IS) RETURN                                               SB  85
18    AA=AA-1.                                                          SB  86
      BB=BB+(AJ*QM+AP*QP)*SDH/SD                                        SB  87
      CC=CC+(AJ*QM-AP*QP)*CDH/SD                                        SB  88
      RETURN                                                            SB  89
19    IF (NJUN2.EQ.0) GO TO 23                                          SB  90
      QP=PI*BI(I)                                                       SB  91
      XXI=QP*QP                                                         SB  92
      XXI=QP*(1.-.5*XXI)/(1.-XXI)                                       SB  93
      QP=-(OMC+XXI*SD)/(SD*(AP+XXI*PP)+CD*(XXI*AP-PP))                  SB  94
      IF (JUNE.NE.1) GO TO 20                                           SB  95
      AA=-AA*QP                                                         SB  96
      BB=BB*QP                                                          SB  97
      CC=-CC*QP                                                         SB  98
      IF (I.NE.IS) RETURN                                               SB  99
20    AA=AA-1.                                                          SB 100
      D=CD-XXI*SD                                                       SB 101
      BB=BB+(SDH+AP*QP*(CDH-XXI*SDH))/D                                 SB 102
      CC=CC+(CDH+AP*QP*(SDH+XXI*CDH))/D                                 SB 103
      RETURN                                                            SB 104
21    QM=PI*BI(I)                                                       SB 105
      XXI=QM*QM                                                         SB 106
      XXI=QM*(1.-.5*XXI)/(1.-XXI)                                       SB 107
      QM=(OMC+XXI*SD)/(SD*(AJ-XXI*PM)+CD*(PM+XXI*AJ))                   SB 108
      IF (JUNE.NE.-1) GO TO 22                                          SB 109
      AA=AA*QM                                                          SB 110
      BB=BB*QM                                                          SB 111
      CC=CC*QM                                                          SB 112
      IF (I.NE.IS) RETURN                                               SB 113
22    AA=AA-1.                                                          SB 114
      D=CD-XXI*SD                                                       SB 115
      BB=BB+(AJ*QM*(CDH-XXI*SDH)-SDH)/D                                 SB 116
      CC=CC+(CDH-AJ*QM*(SDH+XXI*CDH))/D                                 SB 117
      RETURN                                                            SB 118
23    AA=-1.                                                            SB 119
      QP=PI*BI(I)                                                       SB 120
      XXI=QP*QP                                                         SD 121
      XXI=QP*(1.-.5*XXI)/(1.-XXI)                                       SB 122
      CC=1./(CDH-XXI*SDH)                                               SB 123
      RETURN                                                            SB 124
24    PRINT 25, I                                                       SB 125
      STOP                                                              SB 126
C                                                                       SB 127
25    FORMAT (43H SBF - SEGMENT CONNECTION ERROR FOR SEGMENT,I5)        SB 128
```

129 END

SECOND

PURPOSE

To obtain the time in seconds

METHOD

This subroutine acts as an interface of the computer system's time function and the NEC program. The system time function is called, the number is converted to seconds, and returned to the NEC program through the argument of subroutine SECOND. On CDC 6000 series computers, the system time function is SECOND and is called by the NEC program. This subroutine is, therefore, omitted on CDC 6000 computers.

CODE LISTING

```
      1     SUBROUTINE SECOND (T)                                    SE   1

            Call system time function and set T equal to time in seconds.

      9     RETURN                                                   SE   9
     10     END                                                      SE  10-
```

SFLDS

PURPOSE

To evaluate the Sommerfeld-integral field components due to an infinitesimal current element on a segment.

METHOD

The coordinates of the segment are stored in COMMON/DATAJ/. The current element, at a distance T from the center of the segment is located at (XT, YT, ZT). From SL16 to SL42 the ρ, ϕ and z coordinates of the field evaluation point (X0, Y0, Z0) are computed in a coordinate system with the z axis passing through the current element and $\phi = 0$ in the direction of the segment reference direction projected on the x,y plane. R2 is as shown in Figure 6 (page 160) and is the same as R1 in Section IV of Part I.

The Sommerfeld-integral field is computed from SL85 to SL111 by giving R2 and θ', with

$$\theta' = \tan^{-1}\left(\frac{z + z'}{\rho}\right),$$

to subroutine INTRP. INTRP returns the quantities in equations 156 through 159 of Part I as

$$ERV = I_{\rho}^{V}$$

$$EZV = I_{z}^{V}$$

$$ERH = I_{\rho}^{H}$$

$$EPH = I_{\phi}^{H}$$

These quantities are then multiplied by $\exp(-jkR_2)/R_2$. The components for a horizontal current element are multiplied by the appropriate factors of $\sin\phi$ or $\cos\phi$ and combined with the components for a vertical current element according to the elevation angle of the segment. Thus lines SL94 to SL96 are the ρ, z and ϕ components of the field of the current element. These are converted to x, y and z components and stored in E(1), E(2) and

E(3). They are also multiplied by sin(kT) and cos(kT) for the sine and cosine current distributions and stored in other elements of E.

When the separation of the source segment and observation point is large enough that the Norton approximation is used for the field, the code from SL49 to SL80 is executed. In this case SFLDS is called directly by EFLD, with T equal to zero, and returns an approximation to the field of the whole segment. The current is lumped at the center for a point source approximation.

GWAVE computes the total field including direct field and the asymptotic approximation of the field due to ground. Since EFLD has already computed

$$\bar{E}_D(\bar{r}) + \frac{k_1^2 - k_2^2}{k_1^2 + k_2^2} \bar{E}_I(\bar{r})$$

these terms must be removed from the field computed by GWAVE. The direct field $\bar{E}_D$ is set to zero by setting XX1 to zero before calling GWAVE. The second term is substracted from the field returned by GWAVE from SL59 to SL63. The field components of a vertical (V) and horizontal (H) current element in the direction $\phi = 0$ at the image point are

$$E_\rho^V = (E_R + E_T) \sin\theta \cos\theta$$

$$E_Z^V = E_R \cos^2\theta - E_T \sin^2\theta$$

$$E_\rho^H = (E_R \sin^2\theta - E_T \cos^2\theta) \cos\phi$$

$$E_Z^H = (E_R + E_T) \sin\theta \cos\theta \cos\phi$$

$$E_\phi^H = E_T \sin\phi$$

where

$$E_R = \frac{-j\eta}{4\pi^2} \frac{\exp(-jkR_2)}{(R_2/\lambda)^3} (1 + jkR_2)$$

$$E_T = \frac{-j\eta}{8\pi^2} \frac{\exp(-jkR_2)}{(R_2/\lambda)^3} (1 - k^2R_2^2 + jkR_2)$$

$$\cos\theta = (z + z')/R_2$$

$$\sin\theta = \rho/R_2$$

and current moment, $I\ell/\lambda^2 = 1$.

The sin ϕ and cos ϕ factors are omitted to match the quantities returned by GWAVE. Also, the fields of the horizontal current are reversed since the image of the source is in the direction $\phi = 180$ degrees. These quantities are multiplied by FRATI and subtracted from the fields returned by GWAVE.

The total field, in x, y and z components, is stored from SL70 to SL72. S is the length of the segment in wavelengths. Hence it is $I\ell/\lambda^2$ when $I/\lambda = 1$. The current moment for a sine distribution is zero and for a cosine distribution is $\sin(\pi S)/\pi$.

SYMBOL DICTIONARY

CPH	= cos ϕ
E	= array for returning field components
EPH	= E_ϕ^H or I_ϕ^H
ER	= E_R
ERH	= E_ρ^H or I_ρ^H
ERV	= E_ρ^V or I_ρ^V
ET	= E_T
EZH	= E_Z^H or I_Z^H
EZV	= E_Z^V or I_Z^V
FRATI	= $(k_1^2 - k_2^2)/(k_1^2 + k_2^2)$
IRH	= E_ρ^H for image of source current element

HRV = E_ρ^V

HZV = H_Z^V

PHX = x component of $\hat{\phi}$

PHY = y component of ϕ

PI = π

POT = $\pi/2$

R1 = direct distance to source (set to arbitrary value)

R2 = distance to image

R2S = $(R2)^2$

RHØ = ρ

RHS = ρ^2

RHX = x component of ρ

RHY = y component of ρ

RK = kR_2

SFAC = value of current or current moment

SPH = sin ϕ

T = distance from center of segment to current element

THET = θ'

TP = 2π

XT, YT, ZT = coordinates of current element

ZPHS = $(z + z')^2$

CONSTANTS

1.570796327 = $\pi/2$

3.141592654 = π

6.283185308 = 2π

```
      SUBROUTINE SFLDS (T,E)                                            SL   1
C                                                                       SL   2
C     SFLDX RETURNS THE FIELD DUE TO GROUND FOR A CURRENT ELEMENT ON    SL   3
C     THE SOURCE SEGMENT AT T RELATIVE TO THE SEGMENT CENTER.           SL   4
C                                                                       SL   5
      COMPLEX E,ERV,EZV,ERH,EZH,EPH,T1,EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,E SL   6
     1ZC,XX1,XX2,U,U2,ZRATI,ZRATI2,FRATI,ER,ET,HRV,HZV,HRH              SL   7
      COMMON /DATAJ/ S,H,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ SL   8
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                           SL   9
      COMMON /INCOM/ XO,YO,ZO,SN,XSN,YSN,ISNOR                          SL  10
      COMMON /GWAV/ U,U2,XX1,XX2,R1,R2,ZMH,ZPH                          SL  11
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR, SL  12
     1IPERF,T1,T2                                                       SL  13
      DIMENSION E(9)                                                    SL  14
      DATA PI/3.141592654/,TP/6.283185308/,POT/1.570796327/             SL  15
      XT=XJ+T*CABJ                                                      SL  16
      YT=YJ+T*SABJ                                                      SL  17
      ZT=ZJ+T*SALPJ                                                     SL  18
      RHX=XO-XT                                                         SL  19
      RHY=YO-YT                                                         SL  20
      RHS=RHX*RHX+RHY*RHY                                               SL  21
      RHO=SQRT(RHS)                                                     SL  22
      IF (RHO.GT.0.) GO TO 1                                            SL  23
      RHX=1.                                                            SL  24
      RHY=0.                                                            SL  25
      PHX=0.                                                            SL  26
      PHY=1.                                                            SL  27
      GO TO 2                                                           SL  28
1     RHX=RHX/RHO                                                       SL  29
      RHY=RHY/RHO                                                       SL  30
      PHX=-RHY                                                          SL  31
      PHY=RHX                                                           SL  32
2     CPH=RHX*XSN+RHY*YSN                                               SL  33
      SPH=RHY*XSN-RHX*YSN                                               SL  34
      IF (ABS(CPH).LT.1.E-10) CPH=0.                                    SL  35
      IF (ABS(SPH).LT.1.E-10) SPH=0.                                    SL  36
      ZPH=ZO+ZT                                                         SL  37
      ZPHS=ZPH*ZPH                                                      SL  38
      R2S=RHS+ZPHS                                                      SL  39
      R2=SQRT(R2S)                                                      SL  40
      RK=R2*TP                                                          SL  41
      XX2=CMPLX(COS(RK),-SIN(RK))                                       SL  42
      IF (ISNOR.EQ.1) GO TO 3                                           SL  43
C                                                                       SL  44
C     USE NORTON APPROXIMATION FOR FIELD DUE TO GROUND.  CURRENT IS     SL  45
C     LUMPED AT SEGMENT CENTER WITH CURRENT MOMENT FOR CONSTANT, SINE,  SL  46
C     OR COSINE DISTRIBUTION.                                           SL  47
C                                                                       SL  48
      ZMH=1.                                                            SL  49
      R1=1.                                                             SL  50
      XX1=0.                                                            SL  51
      CALL GWAVE (ERV,EZV,ERH,EZH,EPH)                                  SL  52
      ET=-(0.,4.77134)*FRATI*XX2/(R2S*R2)                               SL  53
      ER=2.*ET*CMPLX(1.,RK)                                             SL  54
      ET=ET*CMPLX(1.-RK*RK,RK)                                          SL  55
      HRV=(ER+ET)*RHO*ZPH/R2S                                           SL  56
      HZV=(ZPHS*ER-RHS*ET)/R2S                                          SL  57
      HRH=(RHS*ER-ZPHS*ET)/R2S                                          SL  58
      ERV=ERV-HRV                                                       SL  59
      EZV=EZV-HZV                                                       SL  60
      ERH=ERH+HRH                                                       SL  61
      EZH=EZH+HRV                                                       SL  62
      EPH=EPH+ET                                                        SL  63
      ERV=ERV*SALPJ                                                     SL  64
```

```
      EZV=EZV*SALPJ                                                     SL  65
      ERH=ERH*SN*CPH                                                    SL  66
      EZH=EZH*SN*CPH                                                    SL  67
      EPH=EPH*SN*SPH                                                    SL  68
      ERH=ERV+ERH                                                       SL  69
      E(1)=(ERH*RHX+EPH*PHX)*S                                          SL  70
      E(2)=(ERH*RHY+EPH*PHY)*S                                          SL  71
      E(3)=(EZV+EZH)*S                                                  SL  72
      E(4)=0.                                                           SL  73
      E(5)=0.                                                           SL  74
      E(6)=0.                                                           SL  75
      SFAC=PI*S                                                         SL  76
      SFAC=SIN(SFAC)/SFAC                                               SL  77
      E(7)=E(1)*SFAC                                                    SL  78
      E(8)=E(2)*SFAC                                                    SL  79
      E(9)=E(3)*SFAC                                                    SL  80
      RETURN                                                            SL  81
C                                                                       SL  82
C     INTERPOLATE IN SOMMERFELD FIELD TABLES                            SL  83
C                                                                       SL  84
3     IF (RHO.LT.1.E-12) GO TO 4                                        SL  85
      THET=ATAN(ZPH/RHO)                                                SL  86
      GO TO 5                                                           SL  87
4     THET=POT                                                          SL  88
5     CALL INTRP (R2,THET,ERV,EZV,ERH,EPH)                              SL  89
C     COMBINE VERTICAL AND HORIZONTAL COMPONENTS AND CONVERT TO X,Y,Z   SL  90
C     COMPONENTS.  MULTIPLY BY EXP(-JKR)/R.                             SL  91
      XX2=XX2/R2                                                        SL  92
      SFAC=SN*CPH                                                       SL  93
      ERH=XX2*(SALPJ*ERV+SFAC*ERH)                                      SL  94
      EZH=XX2*(SALPJ*EZV-SFAC*ERV)                                      SL  95
      EPH=SN*SPH*XX2*EPH                                                SL  96
C     X,Y,Z FIELDS FOR CONSTANT CURRENT                                 SL  97
      E(1)=ERH*RHX+EPH*PHX                                              SL  98
      E(2)=ERH*RHY+EPH*PHY                                              SL  99
      E(3)=EZH                                                          SL 100
      RK=TP*T                                                           SL 101
C     X,Y,Z FIELDS FOR SINE CURRENT                                     SL 102
      SFAC=SIN(RK)                                                      SL 103
      E(4)=E(1)*SFAC                                                    SL 104
      E(5)=E(2)*SFAC                                                    SL 105
      E(6)=E(3)*SFAC                                                    SL 106
C     X,Y,Z FIELDS FOR COSINE CURRENT                                   SL 107
      SFAC=COS(RK)                                                      SL 108
      E(7)=E(1)*SFAC                                                    SL 109
      E(8)=E(2)*SFAC                                                    SL 110
      E(9)=E(3)*SFAC                                                    SL 111
      RETURN                                                            SL 112
      END                                                               SL 113-
```

SOLGF

PURPOSE

To solve for the basis function amplitudes in the NGF procedure.

METHOD

The operations performed here are described in the NGF overview in Section VI. SOLGF is called for either a NGF solution or a normal solution. For the normal solution, or for a NGF solution when no new segments or patches have been added, the solution is obtained by calling SOLVES at SF14. Otherwise, the rest of the code is executed.

The excitation vector XY is filled in the subroutine ETMNS in the order

1. E on NGF segments (N1 elements)
2. E on new segments (N - N1 elements)
3. H on NGF patches (2M1 elements)
4. H on new patches (2M - 2M1 elements)

From SF18 to SF29 this vector is put in the order

1. E on NGF segments
2. H on NGF patches

} E_1

3. E on new segments
4. H on new patches

} E_2

to conform to the matrix structure. From SF30 to SF36, zeros are stored in XY in the locations opposite the rows of the C' matrix. Line SF37 then computes $A^{-1}E_1$ storing it in place of E_1.

SF41 to SF52 computes $E_2 - C\,A^{-1}E_1$ and stores it in palce of E_2. Matrix C is read from file 15 if necessary to form the product with $A^{-1}E_1$. From SF55 to SF80

$$I_2 = [D - CA^{-1}B]^{-1}[E_2 - CA^{-1}E_1]$$

is computed in the original location of E_2. If ICASX is 4 the block parameters for the primary matrix are temporarily changed to those of $D - CA^{-1}B$ so that LTSOLV, which uses the primary block parameters, can perform the solution procedure. From SF84 to SF95

$$I_1 = A^{-1}E_1 - (A^{-1}B)I_2$$

is computed. The reordering step at the beginning of SOLGF is then reversed from SF98 to SF107 to put the solution vector in the order

1. amplitudes of NGF basis functions
2. amplitudes of new basis functions
3. NGF patch currents
4. new patch currents
5. amplitudes of modified basis functions for NGF segments that connect to new segments
6. meaningless values associated with B'_{ss}

Finally, from SF109 to SF113 the amplitudes of the modified basis functions are stored in place of the NGF basis functions that were set to zero.

SYMBOL DICTIONARY

A	= array for matrix A_F
B	= array starting just after A in CM (used for factoring $D - CA^{-1}B$ for ICASX = 2, 3 or 4)
C	= array for matrix C
D	= array used for factoring $D - CA^{-1}B$ when ICASX = 1
ICASS	= saved value of ICASE
IFL	= file in which blocks of A_F are stored in descending order (ascending order is always on 13)
IP	= array of pivot element indices
M	= number of patches

M1	= number of patches in NGF
MP	= number of patches in one symmetric section of the NGF structure
N	= number of segments
N1	= number of segments in NGF
N1C	= number of unknowns in NGF (N1 + 2M1)
N2	= N1 + 1
N2C	= number of new unknowns (order of D)
NBLSYS	= saved value of NBLSYM
NEQ	= total number of unknowns (NGF and new)
NEQS	= number of columns in B'_{sw} and B'_{ss}
NLSYS	= saved value of NLSYM
NP	= number of segments in a symmetric section of the NGF structure
NPSYS	= saved value of NPSYM
SUM	= summation variable for matrix products
XY	= excitation and solution vector

```
      SUBROUTINE SOLGF (A,B,C,D,XY,IP,NP,N1,N,MP,M1,M,N1C,N2C)                SF    1
C     SOLVE FOR CURRENT IN N.G.F. PROCEDURE                                   SF    2
      COMPLEX A,B,C,D,SUM,XY,Y                                                SF    3
      COMMON /SCRATM/ Y(600)                                                  SF    4
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(50),NSCON,IP      SF    5
     1CON(10),NPCON                                                           SF    6
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I      SF    7
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                      SF    8
      DIMENSION B(N1C,1), C(N1C,1), D(N2C,1), IP(1), XY(1)                    SF    9
      IFL=14                                                                  SF   10
      IF (ICASX.GT.0) IFL=13                                                  SF   11
      IF (N2C.GT.0) GO TO 1                                                   SF   12
C     NORMAL SOLUTION.  NOT N.G.F.                                            SF   13
      CALL SOLVES (A,IP,XY,N1C,1,NP,N,MP,M,13,IFL)                            SF   14
      GO TO 22                                                                SF   15
1     IF (N1.EQ.N.OR.M1.EQ.0) GO TO 5                                         SF   16
C     REORDER EXCITATION ARRAY                                                SF   17
      N2=N1+1                                                                 SF   18
      JJ=N+1                                                                  SF   19
      NPM=N+2*M1                                                              SF   20
      DO 2 I=N2,NPM                                                           SF   21
2     Y(I)=XY(I)                                                              SF   22
      J=N1                                                                    SF   23
      DO 3 I=JJ,NPM                                                           SF   24
      J=J+1                                                                   SF   25
3     XY(J)=Y(I)                                                              SF   26
      DO 4 I=N2,N                                                             SF   27
      J=J+1                                                                   SF   28
4     XY(J)=Y(I)                                                              SF   29
5     NEQS=NSCON+2*NPCON                                                      SF   30
      IF (NEQS.EQ.0) GO TO 7                                                  SF   31
      NEQ=N1C+N2C                                                             SF   32
      NEQS=NEQ-NEQS+1                                                         SF   33
C     COMPUTE INV(A)E1                                                        SF   34
      DO 6 I=NEQS,NEQ                                                         SF   35
6     XY(I)=(0.,0.)                                                           SF   36
7     CALL SOLVES (A,IP,XY,N1C,1,NP,N1,MP,M1,13,IFL)                          SF   37
      NI=0                                                                    SF   38
      NPB=NPBL                                                                SF   39
C     COMPUTE E2-C(INV(A)E1)                                                  SF   40
      DO 10 JJ=1,NBBL                                                         SF   41
      IF (JJ.EQ.NBBL) NPB=NLBL                                                SF   42
      IF (ICASX.GT.1) READ (15) ((C(I,J),I=1,N1C),J=1,NPB)                    SF   43
      II=N1C+NI                                                               SF   44
      DO 9 I=1,NPB                                                            SF   45
      SUM=(0.,0.)                                                             SF   46
      DO 8 J=1,N1C                                                            SF   47
8     SUM=SUM+C(J,I)*XY(J)                                                    SF   48
      J=II+I                                                                  SF   49
9     XY(J)=XY(J)-SUM                                                         SF   50
10    NI=NI+NPBL                                                              SF   51
      REWIND 15                                                               SF   52
      JJ=N1C+1                                                                SF   53
C     COMPUTE INV(D)(E2-C(INV(A)E1)) = I2                                     SF   54
      IF (ICASX.GT.1) GO TO 11                                                SF   55
      CALL SOLVE (N2C,D,IP(JJ),XY(JJ),N2C)                                    SF   56
      GO TO 13                                                                SF   57
11    IF (ICASX.EQ.4) GO TO 12                                                SF   58
      NI=N2C*N2C                                                              SF   59
      READ (11) (B(J,1),J=1,NI)                                               SF   60
      REWIND 11                                                               SF   61
      CALL SOLVE (N2C,B,IP(JJ),XY(JJ),N2C)                                    SF   62
      GO TO 13                                                                SF   63
12    NBLSYS=NBLSYM                                                           SF   64
```

```
      NPSYS=NPSYM                                                       SF  65
      NLSYS=NLSYM                                                       SF  66
      ICASS=ICASE                                                       SF  67
      NBLSYM=NBBL                                                       SF  68
      NPSYM=NPBL                                                        SF  69
      NLSYM=NLBL                                                        SF  70
      ICASE=3                                                           SF  71
      REWIND 11                                                         SF  72
      REWIND 16                                                         SF  73
      CALL LTSOLV (B,N2C,IP(JJ),XY(JJ),N2C,1,11,16)                     SF  74
      REWIND 11                                                         SF  75
      REWIND 16                                                         SF  76
      NBLSYM=NBLSYS                                                     SF  77
      NPSYM=NPSYS                                                       SF  78
      NLSYM=NLSYS                                                       SF  79
      ICASE=ICASS                                                       SF  80
13    NI=0                                                              SF  81
      NPB=NPBL                                                          SF  82
C     COMPUTE INV(A)[1-(INV(A)B)I2 = I1                                 SF  83
      DO 16 JJ=1,NBBL                                                   SF  84
      IF (JJ.EQ.NBBL) NPB=NLBL                                          SF  85
      IF (ICASX.GT.1) READ (14) ((B(I,J),I=1,N1C),J=1,NPB)              SF  86
      II=N1C+NI                                                         SF  87
      DO 15 I=1,N1C                                                     SF  88
      SUM=(0.,0.)                                                       SF  89
      DO 14 J=1,NPB                                                     SF  90
      JP=II+J                                                           SF  91
14    SUM=SUM+B(I,J)*XY(JP)                                             SF  92
15    XY(I)=XY(I)-SUM                                                   SF  93
16    NI=NI+NPBL                                                        SF  94
      REWIND 14                                                         SF  95
      IF (N1.EQ.N.OR.M1.EQ.0) GO TO 20                                  SF  96
C     REORDER CURRENT ARRAY                                             SF  97
      DO 17 I=N2,NPM                                                    SF  98
17    Y(I)=XY(I)                                                        SF  99
      JJ=N1C+1                                                          SF 100
      J=N1                                                              SF 101
      DO 18 I=JJ,NPM                                                    SF 102
      J=J+1                                                             SF 103
18    XY(J)=Y(I)                                                        SF 104
      DO 19 I=N2,N1C                                                    SF 105
      J=J+1                                                             SF 106
19    XY(J)=Y(I)                                                        SF 107
20    IF (NSCON.EQ.0) GO TO 22                                          SF 108
      J=NEQS-1                                                          SF 109
      DO 21 I=1,NSCON                                                   SF 110
      J=J+1                                                             SF 111
      JJ=ISCON(I)                                                       SF 112
21    XY(JJ)=XY(J)                                                      SF 113
22    RETURN                                                            SF 114
      END                                                               SF 115-
```

SOLVE

PURPOSE

To solve the system LUx = B, where L is a lower triangular matrix with ones on the diagonal, U is an upper triangular matrix, and B is the right-hand side vector (RHS).

METHOD

The algorithm used is described on pages 409-415 of ref. 1. The solution of the matrix equation LUx = B is found by first solving

$$Ly = B, \tag{3}$$

and then

$$Ux = y, \tag{4}$$

since

$$LUx = Ly = B .$$

The solution of equations (3) and (4) is straightforward since the matrices are both triangular. The solution of equation (3) can be written

$$y_i = \frac{1}{\ell_{ii}} \left(b_i - \sum_{j=1}^{i-1} \ell_{ij} y_j \right) \quad i = 1, \ldots, n .$$

Equation (4) can be written similarly.

The L and U matrices are both supplied by the subroutine FACTR and are stored in the matrix A; the 1's on the diagonal of L are suppressed. Care must be exercised in the solution, since rows were interchanged during factorization, and this necessitates rearranging the RHS vector; furthermore, the L matrix itself is not completely rearranged. The information pertinent to the row rearrangements has been stored by FACTR in an integer array (IP), and it is used in the computations. The final solution of the equations is overwritten on the input RHS vector B.

The only differences between the coding in SOLVE and the coding suggested in ref. 1 are: (1) double precision variables are not used for the accumulation of sums, since, for the size of matrices anticipated in core, the computer word length is sufficient, and (2) the transposes of the L and U matrices are supplied in A by FACTR. Thus, the row and column indices used in the routine are reversed to account for this transposition.

CODING

S015 - S025 The solution for y in equation (3).

S029 - S039 The solution for x in equation (4) and the storage of the solution in B.

SYMBOL DICTIONARY

A = array contains the input L and U matrices

B = array contains the input RHS and is overwritten with the solution

I = DO loop index

IP = array contains row positioning information

IP1 = I + 1

J = DO loop index

K = DO loop index

N = order of the matrix being solved

NDIM = dimension of the array where the matrix is stored NDIM $\geq$ N

PI = intermediate integer

SUM = intermediate variable

Y = scratch vector

```
      SUBROUTINE SOLVE (N,A,IP,B,NDIM)                                  SO   1
C                                                                       SO   2
C     SUBROUTINE TO SOLVE THE MATRIX EQUATION LU*X=B WHERE L IS A UNIT  SO   3
C     LOWER TRIANGULAR MATRIX AND U IS AN UPPER TRIANGULAR MATRIX BOTH  SO   4
C     OF WHICH ARE STORED IN A.  THE RHS VECTOR B IS INPUT AND THE      SO   5
C     SOLUTION IS RETURNED THROUGH VECTOR B.    (MATRIX TRANSPOSED.     SO   6
C                                                                       SO   7
      COMPLEX A,B,Y,SUM                                                 SO   8
      INTEGER PI                                                        SO   9
      COMMON /SCRATM/ Y(600)                                            SO  10
      DIMENSION A(NDIM,NDIM), IP(NDIM), B(NDIM)                         SO  11
C                                                                       SO  12
C     FORWARD SUBSTITUTION                                              SO  13
C                                                                       SO  14
      DO 3 I=1,N                                                        SO  15
      PI=IP(I)                                                          SO  16
      Y(I)=B(PI)                                                        SO  17
      B(PI)=B(I)                                                        SO  18
      IP1=I+1                                                           SO  19
      IF (IP1.GT.N) GO TO 2                                             SO  20
      DO 1 J=IP1,N                                                      SO  21
      B(J)=B(J)-A(I,J)*Y(I)                                             SO  22
1     CONTINUE                                                          SO  23
2     CONTINUE                                                          SO  24
3     CONTINUE                                                          SO  25
C                                                                       SO  26
C     BACKWARD SUBSTITUTION                                             SO  27
C                                                                       SO  28
      DO 6 K=1,N                                                        SO  29
      I=N-K+1                                                           SO  30
      SUM=(0.,0.)                                                       SO  31
      IP1=I+1                                                           SO  32
      IF (IP1.GT.N) GO TO 5                                             SO  33
      DO 4 J=IP1,N                                                      SO  34
      SUM=SUM+A(J,I)*B(J)                                               SO  35
4     CONTINUE                                                          SO  36
5     CONTINUE                                                          SO  37
      B(I)=(Y(I)-SUM)/A(I,I)                                            SO  38
6     CONTINUE                                                          SO  39
      RETURN                                                            SO  40
      END                                                               SO  41
```

SOLVES

PURPOSE

To control solution of the matrix equation, including transforming and reordering the solution vector.

METHOD

When SOLVES is called, the array B contains the excitation computed by subroutines ETMNS or NETWK. The exciting electric field on all segments is stored first in B, followed by the magnetic fields on all patches. In the case of a symmetric structure, however, the matrix is filled with the coefficients of all segment and patch equations in the first symmetric sector occurring first. These are followed by the coefficients for successive sectors in the same order. This order is required for the solution procedure for symmetric structures described in section III-3 of Part I. For the case of a symmetric structure with both segments and patches, SOLVES first rearranges the excitation coefficients in array B to correspond to the order of the matrix coefficients.

For symmetric structures, SOLVES then computes the transforms of the subvectors in B according to equation (88) of Part I. Subroutine SOLVE or LTSOLV is then called to compute the solution or solution subvectors. The procedure is selected by the parameter ICASE as follows.

1. No symmetry, matrix in core. SOLVE is called for the solution.
2. Symmetry, matrix in core. SOLVE is called for each subvector.
3. No symmetry, matrix out of core. LTSOLV is called for the solution.
4. Symmetry, complete matrix does not fit in core but submatrices do. SOLVE is called for each subvector after first reading the appropriate submatrix from file IFL1.
5. Symmetry, submatrices do not fit in core. LTSOLV is called for each subvector.

SOLVES then computes the total current by inverse transforming the subvectors by equation (115) of Part I. For a symmetric structure with segments and patches, SOLVES then rearranges the solution in array B to put all segment currents first, followed by all patch currents, which is the order of the original excitation coefficients.

SOLVES

Multiple right-hand-side vectors (NRH) may be processed simultaneously at each step in SOLVES. This reduces the time spent reading files when LTSOLV is called, and is used in computing $A^{-1}B$ in the NGF procedure.

CODING

SS22 - SS39 Rearrange excitation coefficients.
SS43 - SS56 Transform subvectors.
SS63 - SS75 Solve for each subvector.
SS81 - SS94 Inverse transform subvectors.
SS96 - SS113 Rearrange solution coefficients.

SYMBOL DICTIONARY

A = array set aside for in-core matrix storage, i.e., factored matrices
B = right-hand side; the solution is overwritten on this array also
FNOP = decimal form of NOP
FNORM = 1/FNOP
IFL1 = file with matrix blocks in normal order
IFL2 = file with matrix blocks in reversed order
IP = array containing positioning data used in SOLVE
M = number of patches
MP = number of patches in a symmetric sector
N = number of segments
NCOL = number of columns in array A
NEQ = order of complete matrix
NOP = number of symmetric sectors
NP = number of segments in a symmetric sector
NPEQ = order of a submatrix
NRH = number of right-hand-side vectors in B
NROW = number of rows in A
SSX = array containing the coefficients S_{ik} in equation (89) of Part I
SUM = summation variable
Y = scratch vector

```
      SUBROUTINE SOLVES (A,IP,B,NEQ,NRH,NP,N,MP,M,IFL1,IFL2)                SS   1
C                                                                           SS   2
C     SUBROUTINE SOLVES, FOR SYMMETRIC STRUCTURES, HANDLES THE              SS   3
C     TRANSFORMATION OF THE RIGHT HAND SIDE VECTOR AND SOLUTION OF THE      SS   4
C     MATRIX EQ.                                                            SS   5
C                                                                           SS   6
      COMPLEX A,B,Y,SUM,SSX                                                 SS   7
      COMMON /SMAT/ SSX(16,16)                                              SS   8
      COMMON /SCRATM/ Y(600)                                                SS   9
      COMMON /MATPAR/ ICASE,NBLOKS,NPBLK,NLAST,NBLSYM,NPSYM,NLSYM,IMAT,I    SS  10
     1CASX,NBBX,NPBX,NLBX,NBBL,NPBL,NLBL                                    SS  11
      DIMENSION A(1), IP(1), B(NEQ,NRH)                                     SS  12
      NPEQ=NP+2*MP                                                          SS  13
      NOP=NEQ/NPEQ                                                          SS  14
      FNOP=NOP                                                              SS  15
      FNORM=1./FNOP                                                         SS  16
      NROW=NEQ                                                              SS  17
      IF (ICASE.GT.3) NROW=NPEQ                                             SS  18
      IF (NOP.EQ.1) GO TO 11                                                SS  19
      DO 10 IC=1,NRH                                                        SS  20
      IF (N.EQ.0.OR.M.EQ.0) GO TO 6                                         SS  21
      DO 1 I=1,NEQ                                                          SS  22
    1 Y(I)=B(I,IC)                                                          SS  23
      KK=2*MP                                                               SS  24
      IA=NP                                                                 SS  25
      IB=N                                                                  SS  26
      J=NP                                                                  SS  27
      DO 5 K=1,NOP                                                          SS  28
      IF (K.EQ.1) GO TO 3                                                   SS  29
      DO 2 I=1,NP                                                           SS  30
      IA=IA+1                                                               SS  31
      J=J+1                                                                 SS  32
    2 B(J,IC)=Y(IA)                                                         SS  33
      IF (K.EQ.NOP) GO TO 5                                                 SS  34
    3 DO 4 I=1,KK                                                           SS  35
      IB=IB+1                                                               SS  36
      J=J+1                                                                 SS  37
    4 B(J,IC)=Y(IB)                                                         SS  38
    5 CONTINUE                                                              SS  39
C                                                                           SS  40
C     TRANSFORM MATRIX EQ. RHS VECTOR ACCORDING TO SYMMETRY MODES           SS  41
C                                                                           SS  42
    6 DO 10 I=1,NPEQ                                                        SS  43
      DO 7 K=1,NOP                                                          SS  44
      IA=I+(K-1)*NPEQ                                                       SS  45
    7 Y(K)=B(IA,IC)                                                         SS  46
      SUM=Y(1)                                                              SS  47
      DO 8 K=2,NOP                                                          SS  48
    8 SUM=SUM+Y(K)                                                          SS  49
      B(I,IC)=SUM*FNORM                                                     SS  50
      DO 10 K=2,NOP                                                         SS  51
      IA=I+(K-1)*NPEQ                                                       SS  52
      SUM=Y(1)                                                              SS  53
      DO 9 J=2,NOP                                                          SS  54
    9 SUM=SUM+Y(J)*CONJG(SSX(K,J))                                          SS  55
   10 B(IA,IC)=SUM*FNORM                                                    SS  56
   11 IF (ICASE.LT.3) GO TO 12                                              SS  57
      REWIND IFL1                                                           SS  58
      REWIND IFL2                                                           SS  59
C                                                                           SS  60
C     SOLVE EACH MODE EQUATION                                              SS  61
C                                                                           SS  62
   12 DO 16 K=1,NOP                                                         SS  63
      I=(K-1)*NPEQ+1                                                        SS  64
```

```
      IB=IA                                                              SS  65
      IF (ICASE.NE.4) GO TO 13                                           SS  66
      I=NPEQ*NPEQ                                                        SS  67
      READ (IFL1) (A(J),J=1,I)                                           SS  68
      IB=1                                                               SS  69
13    IF (ICASE.EQ.3.OR.ICASE.EQ.5) GO TO 15                             SS  70
      DO 14 IC=1,NRH                                                     SS  71
14    CALL SOLVE (NPEQ,A(IB),IP(IA),B(IA,IC),NROW)                       SS  72
      GO TO 16                                                           SS  73
15    CALL LTSOLV (A,NPEQ,IP(IA),B(IA,1),NEQ,NRH,IFL1,IFL2)              SS  74
16    CONTINUE                                                           SS  75
      IF (NOP.EQ.1) RETURN                                               SS  76
C                                                                        SS  77
C     INVERSE TRANSFORM THE MODE SOLUTIONS                               SS  78
C                                                                        SS  79
      DO 26 IC=1,NRH                                                     SS  80
      DO 20 I=1,NPEQ                                                     SS  81
      DO 17 K=1,NOP                                                      SS  82
      IA=I+(K-1)*NPEQ                                                    SS  83
17    Y(K)=B(IA,IC)                                                      SS  84
      SUM=Y(1)                                                           SS  85
      DO 18 K=2,NOP                                                      SS  86
18    SUM=SUM+Y(K)                                                       SS  87
      B(I,IC)=SUM                                                        SS  88
      DO 20 K=2,NOP                                                      SS  89
      IA=I+(K-1)*NPEQ                                                    SS  90
      SUM=Y(1)                                                           SS  91
      DO 19 J=2,NOP                                                      SS  92
19    SUM=SUM+Y(J)*SSX(K,J)                                              SS  93
20    B(IA,IC)=SUM                                                       SS  94
      IF (N.EQ.0.OR.M.EQ.0) GO TO 26                                     SS  95
      DO 21 I=1,NEQ                                                      SS  96
21    Y(I)=B(I,IC)                                                       SS  97
      KK=2*MP                                                            SS  98
      IA=NP                                                              SS  99
      IB=N                                                               SS 100
      J=NP                                                               SS 101
      DO 25 K=1,NOP                                                      SS 102
      IF (K.EQ.1) GO TO 23                                               SS 103
      DO 22 I=1,NP                                                       SS 104
      IA=IA+1                                                            SS 105
      J=J+1                                                              SS 106
22    B(IA,IC)=Y(J)                                                      SS 107
      IF (K.EQ.NOP) GO TO 25                                             SS 108
23    DO 24 I=1,KK                                                       SS 109
      IB=IB+1                                                            SS 110
      J=J+1                                                              SS 111
24    B(IB,IC)=Y(J)                                                      SS 112
25    CONTINUE                                                           SS 113
26    CONTINUE                                                           SS 114
      RETURN                                                             SS 115
      END                                                                SS 116-
```

TBF

PURPOSE

To evaluate the current expansion function associated with a given segment.

METHOD

The current expansion function is described in section III-1 of Part I. The parameter I is the number of the segment on which the function is centered. On segment I and on all segments connected to either end of segment I, the function has the form

$$f_j(s) = A_j + B_j \sin [k(s - s_j)] + C_j \cos [k(s - s_j)] ,$$

where j is the segment number. TBF locates all connected segments and stores the segment numbers, j, in JCO in COMMON/SEGJ/. It computes A_j, B_j, and C_j and stores them in AX, BX, and CX, respectively, in the same location as was used in JCO. A_j, B_j, and C_j for j = I are stored last in the arrays.

If ICAP = 0, the function goes to zero at an end of segment I to which no other segment or surface is connected. If ICAP ≠ 0, the function has a non-zero value at a free end, allowing for the current onto the wire end cap.

CODING

Equations and symbols refer to Part I.

TB9 - TB55 This code forms a loop that locates all segments connected to the ends of segment I, first for end 1 (IEND = -1) and then for end 2 (IEND = 1).

TB9 - TB16 Parameters are initialized to start search for segments connected to end 1 of segment I.

TB34 PP = P_i^- for end 1 of segment I or P_i^+ for end 2 of segment I.

TB35 - TB37 Equations (43) to (48) of Part I evaluated except for $Q_i^\pm$:

AX(JSNO) = $A_j^\pm/Q_i^\pm$

BX(JSNO) = $B_j^\pm/Q_i^\pm$

CX(JSNO) = $C_j^\pm/Q_i^\pm$

JCO(JSNO) = j

TB38 Exit from loop if segment I is connected to a surface or ground plane. Segment I will occur in COMMON/SEGJ/ twice

in this case, once for the center of the expansion function on segment I and once for the part of the function extending onto the image of segment I in the surface. Line TB45 changes the sign of $B_j^{\pm}$ for the image term. The sum of the two parts of the function on segment I then has zero derivative at the end connected to the surface.

TB39 - TB42 Check appropriate end of segment j to determine whether it shows a connection to segment I (end of search) or connection to another segment (multiple junction).

TB44 Continue search for connected segments (multiple junction).

TB46 Exit from loop after finishing search for both ends of segment I.

TB47 - TB55 Store values for end 1 of segment I and initialize for end 2. Then return to previous loop.

TB59 - TB70 Evaluate functions of segment length and radius for segment I. For $k\Delta < 0.03$, a series is used for $1 - \cos k\Delta$, where Δ = segment length.

TB73 - TB86 Final calculations if neither end of segment I is a free end.

TB89 - TB102 Final calculations for free end on end 1 of segment I.

TB104 - TB117 Final calculations for free end on end 2 of segment I.

TB119 - TB126 Final calculations for free ends on both ends of segment I.

TB128 $A_j = -1$ for $j = I$ in all cases.

SYMBOL DICTIONARY

AJ = a_j^-

AP = a_j^+

CD = $\cos k\Delta_j$

CDH = $\cos(k\Delta_j/2)$

D = $k\Delta_j/2$ or $\cos k\Delta_i - X_i \sin k\Delta_i$

ICAP = flag to determine whether the function goes to zero at a free end

IEND = -1 during calculations for end 1 of segment I and +1 for end 2.

JCON = connection index

JEND = -1 if end 1 of a segment is connected to segment I, +1 if end 2 is connected to segment I

JMAX = maximum number of segments allowed in the expansion function. This includes segment I and all segments connected to either end.

JSNOP = JSN + I

NJUN1 = N^-

NJUN2 = N^+

OMC = $1 - \cos k\Delta_j$

PI = π

PM = P_i^-

PP = P_i^+

QM = Q_i^-

QP = Q_i^+

SD = $\sin k\Delta_j$

SDH = $\sin (k\Delta_j/2)$

SIG = sign for calculation of A_j and C_j

XXI = $J_1(ka_i)/J_0(ka_i)$ (small argument series used for Bessel functions)

CONSTANTS

0.577215664 = Eulers constant

0.015 = 0.03/2

1.3888889E-3 = 1/720

3.141592654 = π

4.1666666667E-2 = 1/24

```
      SUBROUTINE TBF (I,ICAP)                                                TB   1
C     COMPUTE BASIS FUNCTION I                                               TB   2
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300     TB   3
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX(     TB   4
     2300),WLAM,IPSYM                                                        TB   5
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(50),NSCON,IP     TB   6
     1CON(10),NPCON                                                          TB   7
      DATA PI/3.141592654/,JMAX/30/                                          TB   8
      JSNO=0                                                                 TB   9
      PP=0.                                                                  TB  10
      JCOX=ICON1(I)                                                          TB  11
      IF (JCOX.GT.10000) JCOX=I                                              TB  12
      JEND=-1                                                                TB  13
      IEND=-1                                                                TB  14
      SIG=-1.                                                                TB  15
      IF (JCOX) 1,10,2                                                       TB  16
1     JCOX=-JCOX                                                             TB  17
      GO TO 3                                                                TB  18
2     SIG=-SIG                                                               TB  19
      JEND=-JEND                                                             TB  20
3     JSNO=JSNO+1                                                            TB  21
      IF (JSNO.GE.JMAX) GO TO 28                                             TB  22
      JCO(JSNO)=JCOX                                                         TB  23
      D=PI*SI(JCOX)                                                          TB  24
      SDH=SIN(D)                                                             TB  25
      CDH=COS(D)                                                             TB  26
      SD=2.*SDH*CDH                                                          TB  27
      IF (D.GT.0.015) GO TO 4                                                TB  28
      OMC=4.*D*D                                                             TB  29
      OMC=((1.3888889E-3*OMC-4.1666666667E-2)*OMC+.5)*OMC                    TB  30
      GO TO 5                                                                TB  31
4     OMC=1.-CDH*CDH+SDH*SDH                                                 TB  32
5     AJ=1./(ALOG(1./(PI*BI(JCOX)))-.577215664)                              TB  33
      PP=PP-OMC/SD*AJ                                                        TB  34
      AX(JSNO)=AJ/SD*SIG                                                     TB  35
      BX(JSNO)=AJ/(2.*CDH)                                                   TB  36
      CX(JSNO)=-AJ/(2.*SDH)*SIG                                              TB  37
      IF (JCOX.EQ.I) GO TO 8                                                 TB  38
      IF (JEND.EQ.1) GO TO 6                                                 TB  39
      JCOX=ICON1(JCOX)                                                       TB  40
      GO TO 7                                                                TB  41
6     JCOX=ICON2(JCOX)                                                       TB  42
7     IF (IABS(JCOX).EQ.I) GO TO 9                                           TB  43
      IF (JCOX) 1,28,2                                                       TB  44
8     BX(JSNO)=-BX(JSNO)                                                     TB  45
9     IF (IEND.EQ.1) GO TO 11                                                TB  46
10    PM=-PP                                                                 TB  47
      PP=0.                                                                  TB  48
      NJUN1=JSNO                                                             TB  49
      JCOX=ICON2(I)                                                          TB  50
      IF (JCOX.GT.10000) JCOX=I                                              TB  51
      JEND=1                                                                 TB  52
      IEND=1                                                                 TB  53
      SIG=-1.                                                                TB  54
      IF (JCOX) 1,11,2                                                       TB  55
11    NJUN2=JSNO-NJUN1                                                       TB  56
      JSNOP=JSNO+1                                                           TB  57
      JCO(JSNOP)=I                                                           TB  58
      D=PI*SI(I)                                                             TB  59
      SDH=SIN(D)                                                             TB  60
      CDH=COS(D)                                                             TB  61
      SD=2.*SDH*CDH                                                          TB  62
      CD=CDH*CDH-SDH*SDH                                                     TB  63
      IF (D.GT.0.015) GO TO 12                                               TB  64
```

```
      OMC=4.*D*D                                                        TB  65
      OMC=((1.3888889E-3*OMC-4.1666666667E-2)*OMC+.5)*OMC               TB  66
      GO TO 13                                                          TB  67
12    OMC=1.-CD                                                         TB  68
13    AP=1./(ALOG(1./(PI*BI(I)))-.577215664)                            TB  69
      AJ=AP                                                             TB  70
      IF (NJUN1.EQ.0) GO TO 16                                          TB  71
      IF (NJUN2.EQ.0) GO TO 20                                          TB  72
      QP=SD*(PM*PP+AJ*AP)+CD*(PM*AP-PP*AJ)                              TB  73
      QM=(AP*OMC-PP*SD)/QP                                              TB  74
      QP=-(AJ*OMC+PM*SD)/QP                                             TB  75
      BX(JSNOP)=(AJ*QM+AP*QP)*SDH/SD                                    TB  76
      CX(JSNOP)=(AJ*QM-AP*QP)*CDH/SD                                    TB  77
      DO 14 IEND=1,NJUN1                                                TB  78
      AX(IEND)=AX(IEND)*QM                                              TB  79
      BX(IEND)=BX(IEND)*QM                                              TB  80
14    CX(IEND)=CX(IEND)*QM                                              TB  81
      JEND=NJUN1+1                                                      TB  82
      DO 15 IEND=JEND,JSNO                                              TB  83
      AX(IEND)=-AX(IEND)*QP                                             TB  84
      BX(IEND)=BX(IEND)*QP                                              TB  85
15    CX(IEND)=-CX(IEND)*QP                                             TB  86
      GO TO 27                                                          TB  87
16    IF (NJUN2.EQ.0) GO TO 24                                          TB  88
      IF (ICAP.NE.0) GO TO 17                                           TB  89
      XXI=0.                                                            TB  90
      GO TO 18                                                          TB  91
17    QP=PI*BI(I)                                                       TB  92
      XXI=QP*QP                                                         TB  93
      XXI=QP*(1.-.5*XXI)/(1.-XXI)                                       TB  94
18    QP=-(OMC+XXI*SD)/(SD*(AP+XXI*PP)+CD*(XXI*AP-PP))                  TB  95
      D=CD-XXI*SD                                                       TB  96
      BX(JSNOP)=(SDH+AP*QP*(CDH-XXI*SDH))/D                             TB  97
      CX(JSNOP)=(CDH+AP*QP*(SDH+XXI*CDH))/D                             TB  98
      DO 19 IEND=1,NJUN2                                                TB  99
      AX(IEND)=-AX(IEND)*QP                                             TB 100
      BX(IEND)=BX(IEND)*QP                                              TB 101
19    CX(IEND)=-CX(IEND)*QP                                             TB 102
      GO TO 27                                                          TB 103
20    IF (ICAP.NE.0) GO TO 21                                           TB 104
      XXI=0.                                                            TB 105
      GO TO 22                                                          TB 106
21    QM=PI*BI(I)                                                       TB 107
      XXI=QM*QM                                                         TB 108
      XXI=QM*(1.-.5*XXI)/(1.-XXI)                                       TB 109
22    QM=(OMC+XXI*SD)/(SD*(AJ-XXI*PM)+CD*(PM+XXI*AJ))                   TB 110
      D=CD-XXI*SD                                                       TB 111
      BX(JSNOP)=(AJ*QM*(CDH+XXI*SDH)-SDH)/D                             TB 112
      CX(JSNOP)=(CDH-AJ*QM*(SDH+XXI*CDH))/D                             TB 113
      DO 23 IEND=1,NJUN1                                                TB 114
      AX(IEND)=AX(IEND)*QM                                              TB 115
      BX(IEND)=BX(IEND)*QM                                              TB 116
23    CX(IEND)=CX(IEND)*QM                                              TB 117
      GO TO 27                                                          TB 118
24    BX(JSNOP)=0.                                                      TB 119
      IF (ICAP.NE.0) GO TO 25                                           TB 120
      XXI=0.                                                            TB 121
      GO TO 26                                                          TB 122
25    QP=PI*BI(I)                                                       TB 123
      XXI=QP*QP                                                         TB 124
      XXI=QP*(1.-.5*XXI)/(1.-XXI)                                       TB 125
26    CX(JSNOP)=1./(CDH-XXI*SDH)                                        TB 126
27    JSNO=JSNOP                                                        TB 127
      AX(JSNO)=-1.                                                      TB 128
```

```
129         RETURN                                                    TB 129
130 28      PRINT 29, I                                               TB 130
131         STOP                                                      TB 131
132 C                                                                 TB 132
133 29      FORMAT (43H TBI - SEGMENT CONNECTION ERROR FOR SEGMENT,I5)  TB 133
134         END                                                       TB 134-
```

TEST

PURPOSE

To compute the relative difference of two numerical integration results for the Romberg variable-interval-width integration routines.

METHOD

The first numerical integration result is the complex number (F1R, F1I) and the second is (F2R, F2I). The real and imaginary parts of the two results are subtracted and the differences are divided by the largest of F2R, F2I, DMIN or 10^{-37}. The denominator is chosen to avoid trying to maintain a small relative error for a quantity that is insignificantly small.

SYMBOL DICTIONARY

ABS = external routine (absolute value)
DEN = largest of |F2R| and |F2I|
DMIN = minimum denominator
F1I = imaginary part of first integration result
F1R = real part of first integration result
F2I = imaginary part of second integration result
F2R = real part of second integration result
TI = relative difference of imaginary parts
TR = relative difference of real parts

CONSTANT

1.E-37 = tolerance in test for zero

```
      SUBROUTINE TEST (F1R,F2R,TR,F1I,F2I,TI,DMIN)                      TE   1
C                                                                       TE   2
C     TEST FOR CONVERGENCE IN NUMERICAL INTEGRATION                     TE   3
C                                                                       TE   4
      DEN=ABS(F2R)                                                      TE   5
      TR=ABS(F21)                                                       TE   6
      IF (DEN.LT.TR) DEN=TR                                             TE   7
      IF (DEN.LT.DMIN) DEN=DMIN                                         TE   8
      IF (DEN.LT.1.E-37) GO TO 1                                        TE   9
      TR=ABS((F1R-F2R)/DEN)                                             TE  10
      TI=ABS((F1I-F2I)/DEN)                                             TE  11
      RETURN                                                            TE  12
1     TR=0.                                                             TE  13
      TI=0.                                                             TE  14
      RETURN                                                            TE  15
      END                                                               TE  16-
```

TRIO

PURPOSE

To evaluate each of the parts of current expansion functions on a single segment due to each of the segments connected to the given segment.

METHOD

TRIO consists of a loop that uses the connection data in arrays ICON1 and ICON2 to locate all segments connected to segment J. Subroutine SBF is called to evaluate the current expansion function centered on each connected segment and on segment J. Only the function coefficients for that part of each expansion function on segment J are returned and are stored in arrays AX, BX, and CX. The number of the segment with which each expansion function part is associated is stored in array JCO and the total number of expansion functions involved is stored as JSNO.

SYMBOL DICTIONARY

IEND = -1 during calculations for end 1 of segment J, and +1 for end 2

JCOX = number of a segment connected to segment J

JEND = -1 if end 1 of segment JCOX is connected to segment J; +1 if end 2 of segment JCOX is connected to segment J

JMAX = dimension of the arrays in COMMON/SEGJ/

```
      SUBROUTINE TRIO (J)                                                TR   1
C     COMPUTE THE COMPONENTS OF ALL BASIS FUNCTIONS ON SEGMENT J         TR   2
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 TR   3
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( TR   4
     2300),WLAM,IPSYM                                                   TR   5
      COMMON /SEGJ/ AX(30),BX(30),CX(30),JCO(30),JSNO,ISCON(50),NSCON,IP TR   6
     1CON(10),NPCON                                                     TR   7
      DATA JMAX/30/                                                     TR   8
      JSNO=0                                                            TR   9
      JCOX=ICON1(J)                                                     TR  10
      IF (JCOX.GT.10000) GO TO 7                                        TR  11
      JEND=-1                                                           TR  12
      IEND=-1                                                           TR  13
      IF (JCOX) 1,7,2                                                   TR  14
1     JCOX=-JCOX                                                        TR  15
      GO TO 3                                                           TR  16
2     JEND=-JEND                                                        TR  17
3     IF (JCOX.EQ.J) GO TO 6                                            TR  18
      JSNO=JSNO+1                                                       TR  19
      IF (JSNO.GE.JMAX) GO TO 9                                         TR  20
      CALL SBF (JCOX,J,AX(JSNO),BX(JSNO),CX(JSNO))                      TR  21
      JCO(JSNO)=JCOX                                                    TR  22
      IF (JEND.EQ.1) GO TO 4                                            TR  23
      JCOX=ICON1(JCOX)                                                  TR  24
      GO TO 5                                                           TR  25
4     JCOX=ICON2(JCOX)                                                  TR  26
5     IF (JCOX) 1,8,2                                                   TR  27
6     IF (IEND.EQ.1) GO TO 8                                            TR  28
7     JCOX=ICON2(J)                                                     TR  29
      IF (JCOX.GT.10000) GO TO 8                                        TR  30
      JEND=1                                                            TR  31
      IEND=1                                                            TR  32
      IF (JCOX) 1,8,2                                                   TR  33
8     JSNO=JSNO+1                                                       TR  34
      CALL SBF (J,J,AX(JSNO),BX(JSNO),CX(JSNO))                         TR  35
      JCO(JSNO)=J                                                       TR  36
      RETURN                                                            TR  37
9     PRINT 10, J                                                       TR  38
      STOP                                                              TR  39
C                                                                       TR  40
10    FORMAT (44H TRIO - SEGMENT CONNENTION ERROR FOR SEGMENT,I5)       TR  41
      END                                                               TR  42
```

UNERE

PURPOSE

To calculate the electric field due to unit currents in the $\hat{t}_1$ and $\hat{t}_2$ directions on a surface patch.

METHOD

The electric field due to a patch j is calculated by the expression

$$\bar{E}(\bar{r}_0) = \frac{\eta_0}{8\pi^2}\left[\left(\frac{-1 - i2\pi R/\lambda + 4\pi^2 (R/\lambda)^2}{(R/\lambda)^3}\right)\bar{J}_j + \left(\frac{3 + i6\pi R/\lambda - 4\pi^2 (R/\lambda)^2}{(R/\lambda)^5}\right)\bar{J}_j \cdot (\bar{R}/\lambda)(\bar{R}/\lambda)\right]\exp(-i2\pi R/\lambda)\frac{\Delta A_j}{\lambda^2},$$

where $i = \sqrt{-1}$, $\bar{J}_j = J_{1j}\hat{t}_{1j} + J_{2j}\hat{t}_{2j}$, $\bar{R}$ is the vector from the source to the observation point, and ΔA_j is the area of the patch. For UNERE, J_{1j} and J_{2j} are unity. The expression above for a single patch is obtained from the surface integral in equation (3) in Part I where constant current and one step integration are used for the patch.

CODING

UE14 - UE20 z components of patch parameters are adjusted for direct or reflected fields.

UE25 - UE32 For $R < 10^{-10}$, the fields are set to zero.

UE34 - UE47 Expression for $\bar{E}$ is evaluated for $\bar{J}_j$ equal to $\hat{t}_1$ and $\hat{t}_2$.

UE50 - UE55 For reflection in a perfect ground, $\bar{E}$ is reversed in sign.

UE57 - UE79 For reflection in an imperfect ground, $\bar{E}$ is multiplied by the reflection coefficients.

SYMBOL DICTIONARY

CONST = $\frac{\eta_0}{8\pi^2}$

CTH = cos θ; θ is the angle between the reflected ray and the normal to the surface

EDP = $(\bar{E} \cdot \hat{p})(R_{\parallel} - R_{\perp})$

ER = $\frac{\eta_0}{i8\pi^2} \exp(-i\ 2\pi\ R/\lambda)\ \Delta A_j/\lambda^2$ at UE37

= Q2 $(\hat{t}_{1j} \cdot \bar{R}/\lambda)$ at UE40

= Q2 $(\hat{t}_{2j} \cdot \bar{R}/\lambda)$ at UE44

EXK, EYK, EZK = $\bar{E}$ due to current $\hat{t}_{1j}$

EXS, EYS, EZS = $\bar{E}$ due to current $\hat{t}_{2j}$

IPGND = flag to cause computation of reflected field when equal to 2

PX, PY = $\hat{p}$; unit vector normal to the plane of incidence of the reflected ray

Q1 = $\left[\frac{-1 - i2\pi R/\lambda + 4\pi^2(R/\lambda)^2}{(R/\lambda)^3}\right]$ (ER)

Q2 = $\left[\frac{3 + i6\pi R/\lambda - 4\pi^2(R/\lambda)^2}{(R/\lambda)^5}\right]$ (ER)

R = R/λ

RRH = R_H

RRV = R_V

RT = $(R/\lambda)^3$

RX, RY, RZ = $\bar{R}/\lambda$

R2 = $(R/\lambda)^2$

S = $\Delta A_j/\lambda^2$

T1XJ, T1YJ, T1ZJ = $\hat{t}_{1j}$

T2XJ, T2YJ, T2ZJ = $\hat{t}_{2j}$

TPI = 2π

TT1 = $-2\pi R/\lambda$

TT2 = $4\pi 2(R/\lambda)^2$

XOB
YOB } = field evaluation point
ZOB

XYMAG = magnitude of the projection of $\bar{R}/\lambda$ onto the x-y plane

ZR = z component of $\bar{R}/\lambda$ after reflection

CONSTANTS

4.771341188 = $\frac{\eta_0}{8\pi^2}$

6.283185308 = 2π

```
      SUBROUTINE UNERE (XOB,YOB,ZOB)                                    UN    1
C     CALCULATES THE ELECTRIC FIELD DUE TO UNIT CURRENT IN THE T1 AND T2 UN    2
C     DIRECTIONS ON A PATCH                                             UN    3
      COMPLEX EXK,EYK,EZK,EXS,EYS,EZS,EXC,EYC,EZC,ZRATI,ZRATI2,T1,ER,Q1, UN    4
     1Q2,RRV,RRH,EDP,FRATI                                              UN    5
      COMMON /DATAJ/ S,B,XJ,YJ,ZJ,CABJ,SABJ,SALPJ,EXK,EYK,EZK,EXS,EYS,EZ UN    6
     1S,EXC,EYC,EZC,RKH,IEXK,IND1,IND2,IPGND                           UN    7
      COMMON /GND/ZRATI,ZRATI2,FRATI,CL,CH,SCRWL,SCRWR,NRADL,KSYMP,IFAR, UN    8
     1IPERF,T1,T2                                                       UN    9
      EQUIVALENCE (T1XJ,CABJ), (T1YJ,SABJ), (T1ZJ,SALPJ), (T2XJ,B), (T2Y UN   10
     1J,IND1), (T2ZJ,IND2)                                              UN   11
      DATA TPI,CONST/6.283185308,4.771341188/                           UN   12
C     CONST=ETA/(8.*PI**2)                                              UN   13
      ZR=ZJ                                                             UN   14
      T1ZR=T1ZJ                                                         UN   15
      T2ZR=T2ZJ                                                         UN   16
      IF (IPGND.NE.2) GO TO 1                                           UN   17
      ZR=-ZR                                                            UN   18
      T1ZR=-T1ZR                                                        UN   19
      T2ZR=-T2ZR                                                        UN   20
1     RX=XOB-XJ                                                         UN   21
      RY=YOB-YJ                                                         UN   22
      RZ=ZOB-ZR                                                         UN   23
      R2=RX*RX+RY*RY+RZ*RZ                                              UN   24
      IF (R2.GT.1.E-20) GO TO 2                                         UN   25
      EXK=(0.,0.)                                                       UN   26
      EYK=(0.,0.)                                                       UN   27
      EZK=(0.,0.)                                                       UN   28
      EXS=(0.,0.)                                                       UN   29
      EYS=(0.,0.)                                                       UN   30
      EZS=(0.,0.)                                                       UN   31
      RETURN                                                            UN   32
2     R=SQRT(R2)                                                        UN   33
      TT1=-TPI*R                                                        UN   34
      TT2=TT1*TT1                                                       UN   35
      RT=R2*R                                                           UN   36
      ER=CMPLX(SIN(TT1),-COS(TT1))*(CONST*S)                            UN   37
      Q1=CMPLX(TT2-1.,TT1)*ER/RT                                        UN   38
      Q2=CMPLX(3.-TT2,-3.*TT1)*ER/(RT*R2)                               UN   39
      ER=Q2*(T1XJ*RX+T1YJ*RY+T1ZR*RZ)                                   UN   40
      EXK=Q1*T1XJ+ER*RX                                                 UN   41
      EYK=Q1*T1YJ+ER*RY                                                 UN   42
      EZK=Q1*T1ZR+ER*RZ                                                 UN   43
      ER=Q2*(T2XJ*RX+T2YJ*RY+T2ZR*RZ)                                   UN   44
      EXS=Q1*T2XJ+ER*RX                                                 UN   45
      EYS=Q1*T2YJ+ER*RY                                                 UN   46
      EZS=Q1*T2ZR+ER*RZ                                                 UN   47
      IF (IPGND.EQ.1) GO TO 6                                           UN   48
      IF (IPERF.NE.1) GO TO 3                                           UN   49
      EXK=-EXK                                                          UN   50
      EYK=-EYK                                                          UN   51
      EZK=-EZK                                                          UN   52
      EXS=-EXS                                                          UN   53
      EYS=-EYS                                                          UN   54
      EZS=-EZS                                                          UN   55
      GO TO 6                                                           UN   56
3     XYMAG=SQRT(RX*RX+RY*RY)                                           UN   57
      IF (XYMAG.GT.1.E-6) GO TO 4                                       UN   58
      PX=0.                                                             UN   59
      PY=0.                                                             UN   60
      CTH=1.                                                            UN   61
      RRV=(1.,0.)                                                       UN   62
      GO TO 5                                                           UN   63
4     PX=-RY/XYMAG                                                      UN   64
```

```
      PY=RX/XYMAG                                                       UN  65
      CTH=RZ/SQRT(XYMAG*XYMAG+RZ*RZ)                                    UN  66
      RRV=CSQRT(1.-ZRATI*ZRATI*(1.-CTH*CTH))                            UN  67
    5 RRH=ZRATI*CTH                                                     UN  68
      RRH=(RRH-RRV)/(RRH+RRV)                                           UN  69
      RRV=ZRATI*RRV                                                     UN  70
      RRV=-(CTH-RRV)/(CTH+RRV)                                          UN  71
      EDP=(EXK*PX+EYK*PY)*(RRH-RRV)                                     UN  72
      EXK=EXK*RRV+EDP*PX                                                UN  73
      EYK=EYK*RRV+EDP*PY                                                UN  74
      EZK=EZK*RRV                                                       UN  75
      EDP=(EXS*PX+EYS*PY)*(RRH-RRV)                                     UN  76
      EXS=EXS*RRV+EDP*PX                                                UN  77
      EYS=EYS*RRV+EDP*PY                                                UN  78
      EZS=EZS*RRV                                                       UN  79
    6 RETURN                                                            UN  80
      END                                                               UN  81
```

WIRE

PURPOSE

To compute segment coordinates to fill COMMON/DATA/ for a straight line of segments.

METHOD

The formal parameters specify the beginning and ending points of the line and the number of segments into which it is to be divided. The code computes the coordinates of the end points of each segment. The lengths of successive segments are scaled by the factor RDEL if this factor is not one. For NS segments, the length of the first segment is

$$S_1 = \frac{L(1 - RDEL)}{1 - (RDEL)^{NS}}$$

or $S_1 = L/NS$ if RDEL = 1

where L is the total length of wire.

The radius is RAD for the first segment and is scaled by RRAD.

SYMBOL DICTIONARY

DELZ	= segment length
FNS	= real number equivalent of NS
IST	= initial segment number
ITG	= tag number assigned to all segments of the line
NS	= number of segments into which line is divided
RAD	= radius of first segment
RADZ	= segment radius
RD, RDEL	= scaling factor for segment length
RRAD	= scaling factor for segment radius
XD	= increment to x coordinates
XS1	= x coordinate of first end of segment
XS2	= x coordinate of second end of segment
XW1	= x coordinate of first end of line
XW2	= x coordinate of second end of line

X2(I) = x coordinate of end 2 of segment I
YD = increment to y coordinates
YS1 = y coordinate of first end of segment
YS2 = y coordinate of second end of segment
YW1 = y coordinate of first end of wire
YW2 = y coordinate of second end of wire
Y2(I) = y coordinate of end 2 of segment I
ZD = increment to z coordinates
ZS1 = z coordinate of first end of segment
ZS2 = z coordinate of second end of segment
ZW1 = z coordinate of first end of line
ZW2 = z coordinate of second end of line
Z2(I) = z coordinate of second end of segment I

```
      SUBROUTINE WIRE (XW1,YW1,ZW1,XW2,YW2,ZW2,RAD,RDEL,RRAD,NS,ITG)     WI   1
C                                                                        WI   2
C     SUBROUTINE WIRE GENERATES SEGMENT GEOMETRY DATA FOR A STRAIGHT     WI   3
C     WIRE OF NS SEGMENTS.                                               WI   4
C                                                                        WI   5
      COMMON /DATA/ LD,N1,N2,N,NP,M1,M2,M,MP,X(300),Y(300),Z(300),SI(300 WI   6
     1),BI(300),ALP(300),BET(300),ICON1(300),ICON2(300),ITAG(300),ICONX( WI   7
     2300),WLAM,IPSYM                                                   WI   8
      DIMENSION X2(1), Y2(1), Z2(1)                                      WI   9
      EQUIVALENCE (X2(1),SI(1)), (Y2(1),ALP(1)), (Z2(1),BET(1))          WI  10
      IST=N+1                                                            WI  11
      N=N+NS                                                             WI  12
      NP=N                                                               WI  13
      MP=M                                                               WI  14
      IPSYM=0                                                            WI  15
      IF (NS.LT.1) RETURN                                                WI  16
      XD=XW2-XW1                                                         WI  17
      YD=YW2-YW1                                                         WI  18
      ZD=ZW2-ZW1                                                         WI  19
      IF (ABS(RDEL-1.).LT.1.E-6) GO TO 1                                 WI  20
      DELZ=SQRT(XD*XD+YD*YD+ZD*ZD)                                       WI  21
      XD=XD/DELZ                                                         WI  22
      YD=YD/DELZ                                                         WI  23
      ZD=ZD/DELZ                                                         WI  24
      DELZ=DELZ*(1.-RDEL)/(1.-RDEL**NS)                                  WI  25
      RD=RDEL                                                            WI  26
      GO TO 2                                                            WI  27
    1 FNS=NS                                                             WI  28
      XD=XD/FNS                                                          WI  29
      YD=YD/FNS                                                          WI  30
      ZD=ZD/FNS                                                          WI  31
      DELZ=1.                                                            WI  32
      RD=1.                                                              WI  33
    2 RADZ=RAD                                                           WI  34
      XS1=XW1                                                            WI  35
      YS1=YW1                                                            WI  36
      ZS1=ZW1                                                            WI  37
      DO 3 I=IST,N                                                       WI  38
      ITAG(I)=ITG                                                        WI  39
      XS2=XS1+XD*DELZ                                                    WI  40
      YS2=YS1+YD*DELZ                                                    WI  41
      ZS2=ZS1+ZD*DELZ                                                    WI  42
      X(I)=XS1                                                           WI  43
      Y(I)=YS1                                                           WI  44
      Z(I)=ZS1                                                           WI  45
      X2(I)=XS2                                                          WI  46
      Y2(I)=YS2                                                          WI  47
      Z2(I)=ZS2                                                          WI  48
      BI(I)=RADZ                                                         WI  49
      DELZ=DELZ*RD                                                       WI  50
      RADZ=RADZ*RRAD                                                     WI  51
      XS1=XS2                                                            WI  52
      YS1=YS2                                                            WI  53
    3 ZS1=ZS2                                                            WI  54
      X2(N)=XW2                                                          WI  55
      Y2(N)=YW2                                                          WI  56
      Z2(N)=ZW2                                                          WI  57
      RETURN                                                             WI  58
      END                                                                WI  59
```

ZINT

PURPOSE

To compute the internal impedance of a circular wire with finite conductivity.

METHOD

The internal impedance per unit length of a circular wire is given by

$$Z = \frac{j}{b}\sqrt{\frac{f\mu}{2\pi\sigma}}\left[\frac{Ber(q) + jBei(q)}{Ber'(q) + jBei'(q)}\right],$$

where

$q = b\sqrt{2\pi f\mu\sigma}$

σ = wire conductivity

μ = permeability of free space

b = wire radius

f = frequency

Ber, Bei = Kelvin functions

The term that modifies the diagonal matrix element G_{ii} in the interaction matrix is the total impedance of segment i divided by Δ_i/λ, where Δ_i = segment length. Thus, if G_{ii} is the diagonal matrix element without loading, the new element is

$$G_{ii} - Z\Delta_i/(\Delta_i/\lambda) = G_{ii} - Z\lambda .$$

Normalized to wavelength, this term is

$$Z_i = Z\lambda = \frac{j}{(b/\lambda)}\sqrt{\frac{c\mu}{2\pi(\sigma\lambda)}}\left[\frac{Ber(q) + jBei(q)}{Ber'(q) + jBei'(q)}\right],$$

where

$q = (b/\lambda)\sqrt{2\pi c\mu(\sigma\lambda)}$

c = velocity of light

The Kelvin functions and derivatives of Kelvin functions are computed from their polynomial approximations.

CODING

ZI8 - ZI15 Functions θ, ϕ, f, and g for large argument polynomial approximations (see ref. 5).

ZI19 - ZI26 Compute Ber(q) + jBei(q) for $q \leq 8$.

ZI27 - ZI31 Compute Ber'(q) + jBei'(q) for $q \leq 8$.

ZI32 [Ber(q) + jBei(q)]/[Ber'(q) + jBei'(q)].

ZI34 Ber(q) + jBei(q) for $8 < q \leq 110$.

ZI35 Ber'(q) + jBei'(q) for $8 < q \leq 110$.

ZI36 [Ber(q) + jBei(q)]/[Ber'(q) + jBei'(q)].

ZI38 [Ber(q) + jBei(q)]/[Ber'(q) + jBei'(q)] for $110 < q < \infty$.

ZI39 Computation of Z_1.

SYMBOL DICTIONARY

BEI = Bei(q) or Bei'(q)

BER = Ber(q) or Ber'(q)

BR1 = Ber(q) + jBei(q) or [Ber(q) + jBei(q)]/[Ber'(q) + Bei'(q)]

BR2 = Ber'(q) + jBei'(q)

CEXP = external routine [exp(complex argument)]

CMOTP = $c\mu/(2\pi)$

CMPLX = external routine (forms complex number)

CN = $(1 + j)/\sqrt{2}$

D = function argument

F(D) = f(D) (see ref. 5)

FJ = j

G(D) = g(D) (see ref. 5)

PH(D) = $\phi(X)$, D = 8/X (see ref. 5)

PI = π

POT = $\pi/2$

ROLAM = b/λ

S = $(X/8)^4$

SIGL = $\sigma\lambda$

SQRT = external routine (square root)

TH(D) = $\theta(X)$, D = 8/X (see ref. 5)

TP = 2π

TPCMU = $2\pi c\mu$; c = velocity of light

X = q

Y = $(X/8)^2$

ZINT = Z_i

CONSTANTS

1.5707963	= $\pi/2$
3.141592654	= π
6.283185308	= 2π
60.	= $c\mu/2\pi$
2.368705E+3	= $2\pi c\mu$
(0., 1.)	= j
(0.70710678, 0.70710678)	= $(1 + j)/\sqrt{2}$
(0.70710678, -0.70710678)	= limit for $q \to \infty$ of [Ber(q) + jBei(q)]/[Ber'(q) + jBei'(q)]

Other constants are factors in the polynomial approximations.

```
      COMPLEX FUNCTION ZINT(SIGL,ROLAM)                                 ZI   1
C                                                                       ZI   2
C     ZINT COMPUTES THE INTERNAL IMPEDANCE OF A CIRCULAR WIRE           ZI   3
C                                                                       ZI   4
C                                                                       ZI   5
      COMPLEX TH,PH,F,G,FJ,CN,BR1,BR2                                   ZI   6
      COMPLEX CC1,CC2,CC3,CC4,CC5,CC6,CC7,CC8,CC9,CC10,CC11,CC12,CC13,CC ZI   7
     114                                                                ZI   8
      DIMENSION FJX(2), CNX(2), CCN(28)                                 ZI   9
      EQUIVALENCE (FJ,FJX), (CN,CNX), (CC1,CCN(1)), (CC2,CCN(3)), (CC3,C ZI  10
     1CN(5)), (CC4,CCN(7)), (CC5,CCN(9)), (CC6,CCN(11)), (CC7,CCN(13)),  ZI  11
     2(CC8,CCN(15)), (CC9,CCN(17)), (CC10,CCN(19)), (CC11,CCN(21)), (CC1 ZI  12
     32,CCN(23)), (CC13,CCN(25)), (CC14,CCN(27))                        ZI  13
      DATA PI,POT,TP,TPCMU/3.1415926,1.5707963,6.2831853,2.368705E+3/    ZI  14
      DATA CMOTP/60.00/,FJX/0.,1./,CNX/.70710678,.70710678/             ZI  15
      DATA CCN/6.E-7,1.9E-6,-3.4E-6,5.1E-6,-2.52E-5,0.,-9.06E-5,-9.01E-5 ZI  16
     1,0.,-9.765E-4,.0110486,-.0110485,0.,-.3926991,1.6E-6,-3.2E-6,1.17E ZI  17
     2-5,-2.4E-6,3.46E-5,3.38E-5,5.E-7,2.452E-4,-1.3813E-3,1.3811E-3,-6. ZI  18
     325001E-2,-1.E-7,.7071068,.7071068/                                ZI  19
      TH(D)=(((((CC1*D+CC2)*D+CC3)*D+CC4)*D+CC5)*D+CC6)*D+CC7           ZI  20
      PH(D)=(((((CC8*D+CC9)*D+CC10)*D+CC11)*D+CC12)*D+CC13)*D+CC14      ZI  21
      F(D)=SQRT(POT/D)*CEXP(-CN*D+TH(-8./X))                            ZI  22
      G(D)=CEXP(CN*D+TH(8./X))/SQRT(TP*D)                               ZI  23
      X=SQRT(TPCMU*SIGL)*ROLAM                                          ZI  24
      IF (X.GT.110.) GO TO 2                                            ZI  25
      IF (X.GT.8.) GO TO 1                                              ZI  26
      Y=X/8.                                                            ZI  27
      Y=Y*Y                                                             ZI  28
      S=Y*Y                                                             ZI  29
      BER=((((((-9.01E-6*S+1.22552E-3)*S-.08349609)*S+2.6419140)*S-32.36 ZI  30
     13458)*S+113.77778)*S-64.)*S+1.                                    ZI  31
      BEI=((((((1.1346E-4*S-.01103667)*S+.52185615)*S-10.567658)*S+72.81 ZI  32
     17777)*S-113.77778)*S+16.)*Y                                       ZI  33
      BR1=CMPLX(BER,BEI)                                                ZI  34
      BER=(((((((-3.94E-6*S+4.5957E-4)*S-.02609253)*S+.66047849)*S-6.068 ZI  35
     11481)*S+14.222222)*S-4.)*Y)*X                                     ZI  36
      BEI=((((((4.609E-5*S-3.79386E-3)*S+.14677204)*S-2.3116751)*S+11.37 ZI  37
     17778)*S-10.666667)*S+.5)*X                                        ZI  38
      BR2=CMPLX(BER,BEI)                                                ZI  39
      BR1=BR1/BR2                                                       ZI  40
      GO TO 3                                                           ZI  41
1     BR2=FJ*F(X)/PI                                                    ZI  42
      BR1=G(X)+BR2                                                      ZI  43
      BR2=G(X)*PH(8./X)-BR2*PH(-8./X)                                   ZI  44
      BR1=BR1/BR2                                                       ZI  45
      GO TO 3                                                           ZI  46
2     BR1=CMPLX(.70710678,-.70710678)                                   ZI  47
3     ZINT=FJ*SQRT(CMOTP/SIGL)*BR1/ROLAM                                ZI  48
      RETURN                                                            ZI  49
      END                                                               ZI  50-
```

Section III
Common Blocks

This section discusses each labeled common block which is used in the NEC-2 code. For each common block, a list of the routines in which it is used is given along with a definition of the variables used in conjunction with the common block. The common blocks are presented in alphabetical order.

COMMON/ANGL/ SALP(300)

Routines Using /ANGL/

CABC, CMSS, CMSW, CMWS, CMWW, DATAGN, ETMNS, FFLD, GFIL, GFLD, GFOUT, MOVE, NEFLD, NHFLD, PATCH, QDSRC, REFLC

/ANGL/ Parameters for Wire Segments

SALP(I) = sin (α), where α = elevation angle of segment I (see figure 11)

/ANGL/ Parameters for Surface Patches

SALP(LD - I + 1) = +1 if $\hat{t}_1 \times \hat{t}_2 = \hat{n}$ for patch I, or
-1 if $\hat{t}_1 \times \hat{t}_2 = -\hat{n}$ for patch I

The second case occurs when the patch has been produced by reflection of a patch originally input.

COMMON/CMB/ CM(4000)

Routines Using /CMB/

MAIN, GFIL, GFOUT

The interaction matrix is stored in array CM. If the matrix is too large to fit in CM, then pairs of blocks of the matrix are stored in CM as they are needed.

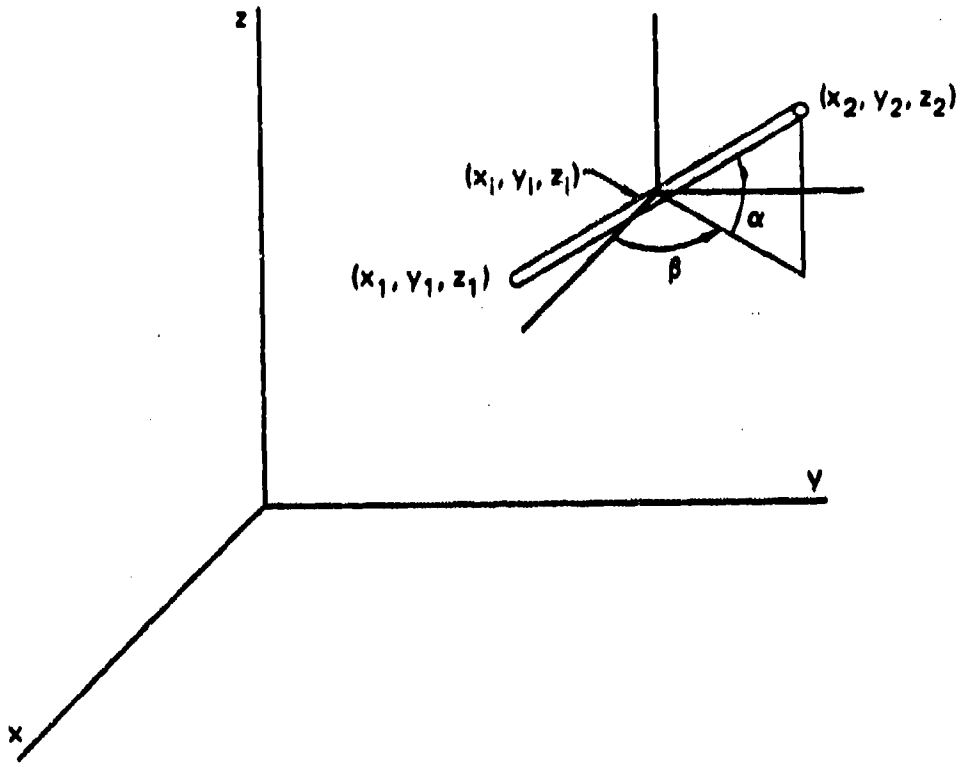


Figure 11. Coordinates of Segment i.

COMMON/CRNT/AIR(300), AII(300), BIR(300), BII(300), CIR(300), CII(300)
CUR(900)

Routines Using /CRNT/

MAIN, CABC, FFLD, GFLD, NEFLD, NETWK, NHFLD

/CRNT/ Parameters for Wire Segments

Subroutine CABC fills the first six arrays in /CRNT/ with the real and imaginary parts of the constants in the current expansion of each segment,

$$I_i(s) = A_i + B_i \sin [k(s - s_i)] + C_i \cos [k(s - s_i)] ,$$

where $s = s_i$ at the center of segment i. Except during intermediate calculations for non-radiating networks, the current basis-function amplitudes are computed and stored in array CUR. CABC replaces the basis function amplitudes in CUR by the current at the center of each segment, $(A_i + C_i)$. For i = 1,

AIR(I)
AII(I) = A_i/λ (real, imaginary)

BIR(I)
BII(I) = B_i/λ

CIR(I)
CII(I) = C_i/λ

CUR(I) = amplitude of i^{th} basis function going into CABC or $(A_i + C_i)/\lambda$ at end of CABC

/CRNT/ Parameters for Surface Patches

Surface current components are stored in CUR. Before CABC is called, the surface current strengths in directions $\hat{t}_1$ and $\hat{t}_2$ on patch i are stored in CUR(N + 2I - 1) and CUR(N + 2I), respectively where N is the number of segments. After CABC, the x, y and z components of surface current are stored in CUR(N + 3I - 2), CUR(N + 3I - 1) and CUR(N + 3I), respectively.

COMMON/DATA/ LD, N1, N2, N, NP, M1, M2, M, MP, X(300), Y(300), Z(300), BI(300), BI(300), ALP(300), BET(300), ICON1(300), ICON2(300), ITAG(300), ICONX(300), WLAM, IPSYM

Routines Using /DATA/

MAIN, ARC, CABC, CMNGF, CMSET, CMSS, CMSW, CMWS, CMWW, CONECT, DATAGN, ETMNS, FFLD, FFLDS, GFIL, GFLD, GFOUT, ISEGNO, LOAD, MOVE, NEFLD, NETWK, NFPAT, NHFLD, PATCH, QDSRC, RDPAT, REFLC, SBF, TBF, TRIO, WIRE

/DATA/ Parameters for Wire Segments

The arrays in /DATA/ are used to store the parameters defining the segments. Two forms of the segment parameters are used.

During geometry input in routines ARC, CONECT, DATAGN, MOVE, REFLEC and WIRE, the coordinates of the segment ends are stored. The symbol meanings in the geometry routines are:

X(I) = X_1

Y(I) = Y_1

Z(I) = Z_1

SI(I) = X_2 [equivalenced to X2(I)]

ALP(I) = Y_2 [equivalenced to Y2(I)]

BET(I) = Z_2 [equivalenced to Z2(I)]

where X_1, Y_1, Z_1 are the coordinates of the first end of the segment, and X_2, Y_2, Z_2 are the coordinates of the second end, as illustrated in figure 11. Coordinates may have any units but must be scaled to meters before data input is ended, since the main program requires meters.

In the main program, the segment data is converted to: the coordinates of the segment center, components of the unit vector in the direction of the segment, and the segment length. The symbol meanings after the geometry section are:

X(I), Y(I), Z(I) = X_i, Y_i, Z_i (see figure 11.)

SI(I) = segment length

ALP(I) = cos α cos β [equivalenced to CAB(I)]

BET(I) = cos α sin β [equivalenced to SAB(I)]

The z component of the unit vector in the direction of the segment, sin α, is stored in /ANGL/.

The other symbol meanings in /DATA/ for segments are:

BI(I) = radius of segment I

ICON1(I) = connection number for end 1 of segment I. If k is a positive integer less than 10,000, the meaning of ICON1 is as follows.

ICON1(1) = 0: no connection.

ICON1(I) = ±k: end 1 connects to segment k. If more than one segment connects to end 1 of segment I, then k is the number of the next connected segment encountered by starting at I and going through the list of segments in cyclic order. ICON1(I) = +k: parallel reference directions with end 2 of the other segment connecting to end 1 of segment I. ICON1(I) = -k: opposed reference directions.

ICON1(I) = 1: end 1 of segment I connects to a ground plane.

ICON1(I) = 10,000 +k: end 1 of segment I connects to a surface with the 4 patches around the connection point numbered k, k + 1, k + 2 and k + 3.

ICON2(I) = connection number for end 2 of segment I.

ITAG(I) = tag number of segment I. This number is assigned during structure input to permit later reference to the segment without knowing the segment index I in the data arrays.

ICONX(I) = equation number for the new basis function when segment I is in a numerical Green's function file and a new segment connects to segment I modifying the old basis function.

/DATA/ Parameters for Surface Patches

Patch parameters are set in subroutine PATCH. The input parameters for a patch are the coordinates of the patch center, patch area, and orientation of the outward, normal unit vector, $\hat{n}$. The parameters stored in /DATA/ are the center point coordinates, area, and the components of the two surface unit vectors, $\hat{t}_1$ and $\hat{t}_2$. The vector $\hat{t}_1$ is parallel to a side of the triangular, rectangular, or quadrilateral patch. For a patch of arbitrary shape, it is chosen by the following rules:

For a horizontal patch, $\hat{t}_1 = \hat{x}$;
For a nonhorizontal patch, $\hat{t}_1 = (\hat{z} \times \hat{n})/|\hat{z} \times \hat{n}|$;
$\hat{t}_2$ is then chosen as $\hat{t}_2 = \hat{n} \times \hat{t}_1$

With J = LD + 1 - I, the parameters for patch I are stored as follows.

X(J), Y(J), Z(J) = x, y, and z coordinates of the patch center

SI(J), ALP(J), BET(J) = x, y, z components of $\hat{t}_1$ (equivalenced to T1X, T1Y, T1Z)

ICON1(J), ICON2(J), ITAG(J) = x, y, and z components of $\hat{t}_2$ (equivalenced to T2X, T2Y, T2Z)

BI(J) = patch area

Scalar variables in /DATA/ are:

IPSYM = symmetry flag. The meanings of IPSYM are:

IPSYM = 0: no symmetry

IPSYM > 0: plane symmetry

IPSYM < 0: cylindrical symmetry

IPSYM = 2: plane symmetry about Z = 0

|IPSYM| > 2: structure has been rotated about x or y axis. If ground plane is indicated by IGND ≠ 0 in the call to subroutine CONECT and IPSYM = 2, symmetry about a horisontal plane is removed by multiplying NP by 2. If |IPSYM| > 2 and IGND ≠ 0, all symmetry is removed by setting NP = N and IPSYM = 0 in CONECT.

LD = length of arrays in /DATA/

N1 = number of segments in NGF. If NGF is not used N1 = 0

N2 = N1 + 1

N = total number of segments

NP = number of segments in a symmetric cell

M1 = number of patches in NGF. If NGF is not used M1 = 0

M2 = M1 + 1

M = total number of patches

MP = number of patches in a symmetric cell

WLAM = wavelength in meters

COMMON/DATAJ/ S, B, XJ, YJ, ZJ, CABJ, SABJ, SALPJ, EXK, EYK, EZK, EXS, EYS, EZS, EXC, EYC, EZC, RKH, IEXK, IND1, IND2, IPGND

Routines Using /DATAJ/

CMNGF, CMSET, CMSS, CMSW, CMWS, CMWW, EFLD, HINTG, HSFLD, NEFLD, NHFLD, PCINT, QDSRC, SFLDS, UNERE

/DATAJ/ is used to pass the parameters of the source segment or patch to the routines that compute the E or H field and to return the field components.

/DATAJ/ Parameters for Wire Segments

S = segment length

B = segment radius

XJ, YJ, ZJ = coordinates of segment center

CABJ, SABJ, SALPJ = x, y, and z, respectively, of the unit vector in the direction of the segment

EXK, EYK, EZK = x, y, and z components of the E or H field due to a constant current

EXS, EYS, EZS = x, y, and z components of the E or H field due to a sin ks current

EXC, EYC, EZC = x, y, and z components of the E or H field due to cos ks current

RKH = minimum distance for use of the Hertzian dipole approximation for computing the E field of a segment

IEXK = flag to select thin wire approximation or extended thin wire approximation for E field (IEXK = 1 for extended thin wire approximation)

IND1 = flag to inhibit use of the extended thin wire approximation on end 1 of the source segment. This is used when there is a bend or change in radius at end 1. IND1 = 2 inhibits the extended thin wire approximation.

IND2 = flag to inhibit use of the extended thin wire approximation on end 2 of the source segment

IPGND = not used

/DATAJ/ Parameters for Surface Patches

S = patch area in units of wavelength squared

B = x component of $\hat{t}_2$ for the patch

XJ, YJ, ZJ = x, y, and z components of the position of the patch center

CABJ, SABJ, SALPJ = x, y, and z components of $\hat{t}_1$

EXK, EYK, EZK = x, y, and z components of $\bar{E}$ or $\bar{H}$ due to a current with unit magnitude in the direction $\hat{t}_1$ on the patch

EXS, EYS, EZS = $\bar{E}$ or $\bar{H}$ due to a current $\hat{t}_2$ on the patch

EXC, EYC, EZC = not used; may serve as intermediate variables in some routines

IND1 = y component of $\hat{t}_2$

IND2 = z component of $\hat{t}_2$

IPGND = flag to request calculation of the direct field or field reflected from the ground (two for ground)

COMMON/FPAT/ NTH, NPH, IPD, IAVP, INOR, IAX, THETS, PHIS, DTH, DPH, RFLD, GNOR, CLT, CHT, EPSR2, SIG2, IXTYP, XPR6, PINR, PNLR, PLOSS NEAR, NFEH, NRX, NRY, NRZ, XNR, YNR, ZNR, DXNR, DYNR, DZNR

Routines Using /FPAT/

MAIN, NFPAT, RDPAT

Variables are defined in subroutine descriptions.

COMMON/GGRID/ AR1(11, 10, 4), AR2(17, 5, 4), AR3(9, 8, 4), EPSCF, DXA(3), DYA(3), XSA(3), YSA(3), NXA(3), NYA(3)

Routines Using /GGRID/

MAIN, GFIL, GFOUT, INTRP

Variables are defined under subroutine INTRP.

COMMON/GND/ ZRATI, ZRATI2, FRATI, CL, CH, SCRWL, SCRWR, NRADL, KSYMP, IFAR, IPERF, T1, T2

Routines Using /GND/

MAIN, CMSW, EFLD, ETMNS, FFLD, GFIL, GFOUT, HINTG, HSFLD, NEFLD, RDPAT, SFLDS, UNERE

/GND/ contains parameters of the ground including the two-medium ground and radial-wire ground-screen cases. The symbol definitions are as follows.

ZRATI = $[\epsilon_r - j\sigma/\omega\epsilon_0]^{-1/2}$

where σ is ground conductivity (mhos/meter), ϵ_r is the relative dielectric constant, ϵ_0 is the permittivity of free space (farads/meter), and $\omega = 2\pi f$.

ZRATI2 = same as ZRATI, but for a second ground medium

FRATI = $(k_1^2 - k_2^2)/(k_1^2 + k_2^2)$ where $k_2 = \omega\sqrt{\mu_0\epsilon_0}$ and $k_1 = k_2/ZRATI$

CL = distance in wavelengths of cliff edge from origin

CH = cliff height in wavelengths

SCRAWL = length of wires in radial-wire ground screen (normalized to wavelength)

SCRWR = radius of wires in screen in wavelengths

NRADL = number of radials in ground screen; zero implies no screen (input quantity, GN card)

KSYMP = ground flag (=1, no ground; =2, ground present)

IFAR = input integer flag on RP card; specifies type of field computation or type of ground system for far fields

IPERF = flag to select type of ground (see GN card)

T1, T2 = constants for the radial-wire ground-screen impedance

COMMON/GWAV/ U, U2, XX1, XX2, R1, R2, ZMH, ZPH

Routines Using /GWAV/

MAIN, GFLD, GWAVE, SFLDS

Symbol Definitions:

U = $(\epsilon_r - j\sigma/\omega\epsilon_0)^{-1/2}$

ϵ_r = relative dielectric constant; σ = conductivity of ground

U2 = U^2

XX1, XX2 : defined in GFLD and SFLDS

R1 = distance from current element to point at which field is evaluated

R2 = distance from image of current element to point at which field is evaluated

ZMH = Z - Z'

ZPH = Z + Z' where Z is height of the field evaluation point and Z' is the height of the current element

COMMON/INCOM/ XO, YO, ZO, SN XSN, YSN, ISNOR

Routines Using /INCOM/

EFLD, SFLDS

Sympol Definitions:

XO, YO, ZO = point at which field due to ground will be evaluated

SN = cos α (see Figure 11)

XSN = cos ß

YSN = sin ß

ISNOR = 1 to evaluate field due to ground by interpolation
0 to use Norton's approximation

COMMON/MATPAR/ ICASE, NBLOKS, NPBLK, NLAST, NBLSYM, NPSYM, NLSYM, IMAT, ICASX, NDBX, NPBX, NLBX, NBBL NPBL, NLBL

Routines Using /MATPAR/

MAIN, CMNGF, CMSET, FACGF, FACIO, FACTRS, FBLOCK, FBNGF, GFIL, GFOUT, LFACTR, LTSOLV, NUNSCR, REBLK, SOLGF, SOLVES

/MATPAR/ contains matrix blocking parameters for cases requiring file storage of the matrix. Symbol definitions in /MATPAR/ are as follows.

ICASE = storage mode for primary matrix, defined as follows.

1 unsymmetric matrix fits in core

2 symmetric matrix fits in core

3 unsymmetric matrix out of core

4 symmetric matrix out of core, but submatrices fit in core

5 symmetric matrix out of core, submatrices also out of core

NBLOKS = number of blocks of columns of the computed matrix (in core matrix, NBLOKS = 1)

NPBLK = number of columns in the first (NBLOKS - 1) blocks

NLAST = number of columns in the last block

NBLSYM, NPSYM, NLSYM = same function as the preceding three variables; however, in this case the parameters refer to the submatrix in the symmetry case

IMAT = storage reserved in CM for the primary NGF matrix A or a block of A (number of complex numbers)

ICASX = storage mode for NGF solution (see Section VII)

NBBX = number of blocks in matrix B stored by blocks of rows

NPBX = number of rows in a block of B stored by rows

NLBX = number of rows in the last block of B

NBBL = number of blocks in matrix C stored by rows (and number of blocks in B stored by columns)

NPBL = number of rows (columns) in a block of C (B)

NLBL = number of rows (columns) in the last block of C (B)

COMMON/NETCX/ ZPED, PIN, PNLS, NEQ, NPEQ, NEQ2, NONET, NTSOL, NPRINT, MASYM, ISEG1(30), ISEG2(30), X11R(30), X11I(30), X12R(30), X12I(30), X22R(30), X22I(30), NTYP(30)

Routines Using /NETCX/

MAIN, NETWK

Variables are defined under subroutine NETWK.

COMMON/SAVE/ IP(600), KCOM, COM(13,5), EPSR, SIG, SCRWLT, SCRWRT, FMHZ

Routines Using /SAVE/

MAIN, GFIL, GFOUT, RDPAT

Symbol Definitions:

IP = vector of indices of pivot elements used in factoring the matrix

KCOM = number of CM or CE data cards (maximum 5)

COM = array storing the contents of CM or CE cards

EPSR = relative dielectric constant of the ground

SIG = conductivity of the ground

SCRWLT = length of radials in radial wire ground screen approximation (meters)

SCRWRT = radius of wires in radial wire ground screen approximation (meters)

FMHZ = frequency in MHz

COMMON/SCRATM/D(600)

in routines CMSET, FACTR, LFACTR

COMMON/SCRATM/Y(600)

in routines LTSOLV, SOLGF, SOLVE, SOLVES

COMMON/SCRATM/GAIN(1200)

in routine RDPAT

Symbol Definitions:

D and Y = complex vectors used in matrix decomposition and solution

GAIN = array to store antenna gain for subsequent normalization

COMMON/SEGJ/ AX(30), BX(30), CX(30), JCO(30), JSNO, ISCON(50), NSCON, IPCON(10), NPCON

Routines Using /SEGJ/

MAIN, CABC, CMNGF, CMSET, CMSW, CMWS, CMWW, CONECT, QDSRC, SFLDS, TBF, TRIO

/SEGJ/ is used to store the parameters defining current expansion functions. The equations for the current expansion functions are given in Section III-1 of Part I. The i^{th} current expansion function consists of a center section on segment i and branches on each segment connected to segment i. On segment j, where j is i or the number of a segment connected to segment i, the i^{th} expansion function is

$$f_j^i(s) = A_j^i + B_j^i \sin [k(s - s_j)] + C_j^i \cos [k(s - s_j)]$$

with the constants defined in Part I to match conditions on the current. A superscript i has been added to indicate the number of the current expansion function.

When subroutine TBF is called for expansion function i, it locates each segment connected to segment i and stores the segment number, j, in array JCO. TBF also computes the constants A_j^i, B_j^i, and C_j^i for segment j and stores them in AX, BX, and CX, respectively.

After all connected segments have been found, i is stored in the next location in JCO, and A_i^i, B_i^i, and C_i^i are stored in the corresponding locations in AX, BX, and CX.

/SEGJ/ is also used by subroutine TRIO. When TRIO is called for segment j, it locates each segment i connected to segment j and stores i in array JCO. TRIO calls SBF to compute the constants A_j^i, B_j^i, and C_j^i for the branch of expansion function i that extends onto segment j and stores these in AX, BX, and CX. The total number of entries, including i = j, is stored in JSNO. The remaining parameters are used with the NGF solution.

ISCON(I) = number of the segment in the NGF file having equation number I in the set of equations for modified basis functions. This is used when a new segment or patch connects to the NGF segment

NSCON = number of entries in ISCON

IPCON(I) = number of the patch in the NGF file having equation number I in the set of equations for modified patch basis functions. This is used when a new segment connects to the NGF patch

NPCON = number of entries in IPCON

COMMON/SMAT/ SSX(16,16)

Routines Using /SMAT/

CMSET, FBLOCK GFIL, GFOUT, SOLVES

The array SSX is described under subroutine FBLOCK. In some copies of NEC-2 the variable name S is used in FBLOCK rather than SSX.

COMMON/TMH/ ZPK, RHKS

Routines Using /TMH/

GH, HFK

/TMH/ is used to pass values from HFK to GH. The variables ZPK and RHKS are defined in the discussion of subroutine HFK.

COMMON/TMI/ ZPK, RKB2, IJX

Routines Using /TMI/

EKSC, EKSCX, GF

/TMI/ is used to pass values from EKSC or EKSCX to GF. The meanings of the variables are listed in subroutines EKSC and EKSCX.

COMMON/VSORC/ VQD(10), VSANT(10), VQDS(10), IVQD(10), ISANT(10), IQDS(10), NVQD, NSANT, NQDS

Routines Using /VSORC/

MAIN, CABC, COUPLE, ETMNS, NETWK, QDSRC

The arrays in /VSORC/ contain the strengths and locations of voltage sources on wires. Separate arrays are used for applied-field voltage sources and current-derivative discontinuity voltage sources. The variables are defined as follows.

ISANT(I) = number of the segment on which the I^{th} applied-field source is located

IVQD(I) = IQDS(I) = number of the segment on end 1 of which the I^{th} current-slope discontinuity voltage source is located

VQD(I) = VQDS(I) = voltage of the I^{th} current-slope discontinuity source

VSANT(I) = voltage of the I^{th} applied-field voltage source

NSANT = number of applied-field voltage sources

NVQD = NQDS = number of current-slope discontinuity voltage sources

NVQD, IVQD, and VQD are set in MAIN from the input data. NQDS, IQDS, and VQDS are set in subroutine QDSRC. The latter were included to allow for current-slope discontinuities other than voltage sources, such as lumped loads. Loading by this means has not been implemented in NEC-2 however.

COMMON/YPARM/ NCOUP, ICOUP, NCTAG(5), NCSEG(5), Y11A(5), Y12A(20)

Routines Using /YPARM/

MAIN, COUPLE

Symbol Definitions:

NCOUP = number of segments between which coupling will be computed

ICOUP = number of segments in the coupling array that have been excited. When ICOUP = NCOUP subroutine COUPLE completes the coupling calculation

NCTAG(I) = tag number of segment I

NCSEG(I) = number of segment in set of segments having tag NCTAG(I)

Y11A(I) = self admittance of I^{th} segment specified

Y12A(I) = mutual admittances stored in order (1,2), (1,3), ... (2,3), (2,4), ... etc.

COMMON/ZLOAD/ ZARRAY(300)

Routines Using /ZLOAD/

MAIN, CMNGF, CMSET, GFIL, GFOUT, LOAD, QDSRC

ZARRAY(I) = $Z_I/(\Delta_I/\lambda)$, where Z_I is the total impedance on segment I, Δ_I is the length of segment I, and λ is the wavelength.

Section IV
System Library Functions Used by NEC

ABS(X)	= absolute value of X
AIMAG(Z)	= imaginary part of the complex number Z; result is real
AINT(X)	= integer truncation; result is real
ALOG(X)	= natural log of X
ALOG10(X)	= log to the base ten of X
ASIN(X)	= arcsine of X; result in radians
ATAN(X)	= arctangent of X; result in radians
ATAN2(X_1,X_2)	= arctangent of X_1/X_2; result in radians covering all four quadrants
CABS(Z)	= magnitude of the complex number, Z
CEXP(Z)	= complex exponential (e^Z)
CMPLX(X_1,X_2)	= formation of a complex number, $Z = X_1 + jX_2$
CONJG(Z)	= conjugate of the complex number Z
COS(X)	= cosine of X
CSQRT(Z)	= square root of a complex number, $\sqrt{Z}$
FLOAT(K)	= real number equivalent of integer K
IABS(K)	= absolute value of integer K
INT(X)	= X truncated to an integer
REAL(Z)	= real part of the complex number Z
SIN(X)	= sine of X
SQRT(X)	= square root of X
TAN(X)	= tangent of X

Section V
Array Dimension Limitations

Array dimensions in the program limit the structure model in various ways. Any of these limits may be increased if necessary at the expense of core storage capacity, which may require reducing other array dimensions. The limits imposed by array dimensions are described below.

In-Core Matrix Storage, I_r = 4000.

Arrays:

COMMON/CMB/ CM(I_r)

Limit constant:

IRESRV = I_r at MA68 of MAIN

I_r is the number of words of core available for storage of the interaction matrix. The complete matrix will fit in core storage if (N + 2M) × (NP + 2MP) is not greater than I_r. For out-of-core solution, I_r must be at least 2(N + 2M) and should be as large as possible to minimize file manipulation.

Maximum Segments and Patches

Minimum Dimensions for N segments and M patches:

COMMON/DATA/ X(N + M), Y(N + M), Z(N + M), SI(N + M), BI(N + M), ALP(N + M), BET(N + M), ICON1(N + M), ICON2(N + M), ITAG(N + M), ICONX(N + M)

COMMON/CRNT/AIR (N), AII(N), BIR(N), BII(N), CIR(N), CII(N), CUR(N + 3M)

COMMON/ANGL/ SALP(N + M)

COMMON/SAVE/ IP(N + 2M)

COMMON/ZLOAD/ ZARRAY(N)

COMMON/SCRATM/ D(N + 2M) or Y(N + 2M)

MAIN: IX(N + 2M)

SUBROUTINE NETWK: RHS(N + 3M)

Limit Constant:

LD = N + M at MA66 of MAIN

All segments and patches resulting from reflection or rotation of a symmetric structure must be included in determining the limiting structure size.

Maximum Number of Non-radiating Networks, N_n = 30.

Arrays:

COMMON/NETCX/: ISEG1(N_n), ISEG2(N_n), X11R(N_n), X11I(N_n), X12R(N_n), X12I(N_n), X22R(N_n), X22I(N_n), NTYP(N_n)

SUBROUTINE NETWK: RHNT(N_n), IPNT(N_n), NTEQA(N_n), NTSCA(N_n), RHNX(N_n), CMN(N_n,N_n)

Limit Constants:

NETMX = N_n at MA63 of MAIN

NDIMN = N_n at NT22 of NETWK

NDIMNP = N_n + 1 at NT22 of NETWK

N_n is the limit for either the number of networks (including transmission lines) or the number of segments having one or more network ports connected, whichever is greater. When relative driving point matrix asymmetry is computed, N_n must also be greater than or equal to the sum of the number of segments with network ports connected plus the number of segments with voltage sources.

Maximum Number of Degrees of Symmetry, N_p = 16.

Arrays:

COMMON/SMAT/ S(N_p, N_p)

N_p limits the number of symmetric cells in a structure. The number of symmetric cells is equal to the ratio of N to NP in COMMON/DATA/.

Maximum Number of Segments Joined at Junctions, N_j = 30

If N^- and N^+ are the numbers of segments connected to end 1 and end 2 of a segment, respectively, then the dimensions in COMMON/SEGJ/, N_j, must be at least $N^- + N^+ + 1$.

Array:

COMMON/SEGJ/ AX(N_j), BX(N_j), CX(N_j), JCO(N_j), JSNO

Limit Constants:

JMAX = N_j at SB6 in SBF

JMAX = N_j at TB8 in TBF

JMAX = N_j at TR8 in TRIO

Maximum Number of Voltage Sources, N_v = 30.

Arrays:

COMMON/VSORC/ VQD(N_v), VSANT(N_v), VQDS(N_v), IVQD(N_v), ISANT(N_v), IQDS(N_v)

Limit Constant:

NSMAX = N_v at MA63 of MAIN

A model may use up to N_v applied field voltage sources and up to N_v current slope discontinuity voltage sources.

Maximum Number of Loading Cards, N_1 = 30

Arrays:

MAIN: LDTYP(N_1), LDTAG(N_1), LDTAGF(N_1), LDTAGT(N_1), ZLR(N_1), ZLI(N_1), ZLC(N_1)

Limit Constants:

LOADMX = N_1 at MA63 of MAIN

When the NGF option is used only new loading cards are counted, not those used in generating the NGF file.

Number of Comment Cards Saved, N_c = 5

Arrays:

COMMON/SAVE/: COM(13,N_c)

Limit Constant:

Constants at MA71 of MAIN

Any number of comment cards may be placed at the beginning of a data deck and will be printed in the output. Only N_c of the cards will be saved in array COM for later use in labeling plots, however. The first N_c - 1 comment cards and the last comment card will be saved.

Maximum Field Points for Normalized Gain, N_g = 1200.

Arrays:

COMMON/SCRATM/ GAIN(N_g)

Limit Constant:

NORMAX = N_g at RD22 of SUBROUTINE RDPAT

N_g is the maximum number of field points from a single RP data card that can be stored for output in normalized form or for plotting if plotting is

implemented. If an RP card requesting more than N_g points calls for normalized gain, the gain will be computed and printed at all requested angles, but only the first N_g gains will be stored and normalized.

COMMON/SCRATM/ GAIN occurs in SUBROUTINE RDPAT. COMMON/SCRATM/ D and COMMON/SCRATM/ Y occur in certain other routines where D and Y are complex (see "Maximum Segments and Patches"). GAIN, D, and Y should be dimensioned so that each common statement contains the same number of words.

Maximum Number of Frequencies for Normalized Impedance or Maximum Number of Angles for Which Received Signal Strength Is Stored, N_f = 200

Array:

MAIN: FNORM(N_f)

Limit Constant:

NORMF = N_f at MA63 of MAIN

The maximum number of frequencies for which input impedance may be stored and normalized is $N_f/4$, since the real and imaginary impedance and magnitude and phase are each stored. The receiving current can be stored for up to N_f angles.

Maximum Number of Points in Coupling Calculation, N_c = 5.

The maximum number of segments among which coupling can be computed (CP cards) is N_c.

COMMON/YPARM/: NCTAG(N_c), NCSEG(N_c), Y11A(N_c), Y12A($N_c^2 - N_c$)

Limit Constants:

Constants at MA207 and MA212 of MAIN should equal N_c

Maximum Number of NGF Segments to Which New Segments or Patches Connect, N_s = 50

COMMON/SEGJ/: ISCON(N_s)

Limit Constant:

NSMAX = N_s at CN13 of CONECT

Maximum Number of NGF Patches to Which New Segments Connect, N_p = 10.

COMMON/SEGJ/: IPCON(N_p)

Limit Constant:

NPMAX = N_p at CN13 of CONECT

Section VI
Overview of Numerical Green's Function Operation

NEC includes a provision to generate and factor an interaction matrix and save the result on a file. A later run, using the file, may add to the structure and solve the complete model without unnecessary repetition of calculations. This procedure is called the Numerical Green's Function (NGF) option since the effect is as if the free space Green's function in NEC were replaced by the Green's function for the structure on the file. The NGF is particularly useful for a large structure, such as a ship, on which various antennas will be added or modified. It also permits taking advantage of partial symmetry since a NGF file may be written for the symmetric part of a structure, taking advantage of the symmetry to reduce computation time. Unsymmetric parts can then be added in a later run.

For the NGF solution the matrix is partitioned as

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} ,$$

where A is the interaction matrix for the initial structure, D is the matrix for the added structure, and B and C represent mutual interactions. The current is computed as

$$I_2 = \left[D - CA^{-1}B\right]^{-1} \left[E_2 - CA^{-1}E_1\right] ,$$

$$I_1 = A^{-1}E_1 - A^{-1}BI_2 ,$$

after the factored matrix A has been read from the NGF file along with other necessary data. Since the LU decomposition is obtained in NEC rather than the inverse, the multiplication by A^{-1} is accomplished by using the solution procedure in subroutine SOLVE on each column in the matrix to the right of A^{-1}.

To use the NGF option the parameters of the fixed, or NGF, part of the model are defined in the first run. A WG data card causes the matrix A to be computed (CMSET), factored (FACTRS), and written to file TAPE20 by subroutine

GFOUT. Other necessary data, such as segment and patch coordinates, frequency, loading, and ground parameters, are also written to TAPE20.

When the NGF file, TAPE20, is used the data are read into the usual arrays by subroutine GFIL and new segments and patches are added to the arrays in COMMON/DATA/. Subroutine CMNGF is then called to compute the matrix elements in B, C, and D. FACGF computes $A^{-1}B$, storing it in place of B, and computes $(D - CA^{-1}B)$, factors it into L and U parts, and stores the result in place of D. For each excitation E_1 and E_2, SOLGF completes the procedure of solving for I_1 and I_2.

The procedure is complicated by the connection of new segments or patches to NGF segments or patches. A connection to a segment modifies the current basis function (see Section III.1 of Part I). Since the elements in A cannot be changed, a modified basis function must be treated as a new basis function with a new column added to B and D and the new basis function amplitude added to the end of I_2. The amplitude of the original basis function is set to zero by adding a row containing all zeros except for a one in the column of C corresponding to the modified basis function. Since the segment is not modified the boundary condition equation is not altered in this case.

When a new segment connects to a NGF patch the patch must be divided into four new patches, after the user defined patches, requiring eight new rows and columns in B, C, and D. Two additional rows are added to set the two current components on the old patch to zero. Since the old patch is replaced by the four new patches, the condition on the field at the center of the patch should be removed. This is done by adding two new columns each containing all zeros except for a one in the row of the equation to be removed.

The matrix structure is further complicated by the division of each submatrix into sections for segment-to-segment, patch-to-patch, segment-to-patch and patch-to-segment interactions. The matrix structure is shown in Figure 12, where the subscript w denotes wire segments and s denotes surface patches. The elements of B'_{ww} and B'_{sw} are the E fields and H fields due to modified basis functions in the NGF section. Each column of B'_{ss} and row of C'_{ww} and C'_{ss} contains 0's and a single 1.

The subroutine ETMNS fills the excitation array with the E fields illuminating all segments, followed by the H fields on patches. These elements are reordered in SOLGF to correspond to the matrix structure. After

A_{ww}	A_{ws}	B_{ww}	B_{ws}	B'_{ww}	0
A_{sw}	A_{ss}	B_{sw}	B_{ss}	B'_{sw}	B'_{ss}
C_{ww}	C_{ws}	D_{ww}	D_{ws}	D'_{ww}	0
C_{sw}	C_{ss}	D_{sw}	D_{ss}	D'_{sw}	0
C'_{ww}	0	0	0	0	0
0	C'_{ss}	0	0	0	0

Figure 12. Matrix Structure for the NGF Solution

the solution this reordering is reversed in SOLGF to put basis function amplitudes for segments first, followed by those for patches. If symmetry is used in the NGF section the matrix A is structured as submatrices for the symmetric sections. Each submatrix contains elements for segments and patches in that section, with the order as shown for A in Figure 12. In this case the excitation and solution vectors are ordered in SOLVES to correspond to the submatrix structure.

Section VII
Overview of Matrix Operations Using File Storage

File storage is used when the matrix size exceeds the length of the array CM in COMMON/CMB/. For the basic solution (not NGF) there are five matrix storage modes associated with the integer ICASE as follows:

ICASE	Matrix Storage
1	Matrix fits in CM; no structure symmetry
2	Matrix fits in CM; structure symmetry used
3	Matrix stored on file; no symmetry
4	Matrix stored on file; symmetry; each submatrix fits into CM for LU decomposition
5	Matrix stored on file; symmetry; submatrices do not fit into CM.

For case 3 the matrix is initially written on file 11 by blocks of rows. The block size is chosen in subroutine FBLOCK so that two blocks will fit into CM for the Gauss elimination procedure. The block size and number of blocks is set by the parameters NBLOKS, NPBLK, and NLAST in COMMON/MATPAR/.

Subroutine FACIO reads file 11 and writes file 12 using 13 and 14 for scratch storage. LUNSCR then reads 12 and writes the blocks of the factored matrix on file 13 in forward order and on file 14 in reversed order. File 13 is then used for forward substitution in the solution and file 14 is used for backward substitution.

For case 4, FACTRS reads the matrix from file 11, where it was written by blocks of rows (columns of the transposed matrix), and writes it to file 12 by submatrices. The submatrices are then read from 12, factored, and written to 13.

In case 5, FACTRS reads the matrix from file 11 and writes it to file 12 by blocks of rows (columns of the transposed matrix) for each submatrix. File 12 is then copied back to file 11, and the procedure of case 3 is repeated for each submatrix.

When a NGF file is to be written, half of CM is reserved for matrix storage and manipulations of the matrices B, C, and D. Hence for cases 1, 2 or 4 the primary matrix A (or submatrix for case 4) must fit into half of CM.

There is no restriction for cases 3 or 5 since, with two matrix blocks fitting into CM for the LU decomposition, half of CM is available during the solution when blocks are used one at a time.

There are four modes for storing B, C, and D in the NGF solution. These are associated with the integer ICASX as follows:

A_F = matrix A factored into L and U

A_R = A_F for ICASE = 1 or 2
one block of A_F for ICASE = 3
one submatrix for ICASE = 4
one block of submatrix for ICASE = 5

A_X = A_F for ICASE = 1 or 2
nothing otherwise

ICASX	NGF Matrix Storage
1	A_R, B, C, and D fit into CM
2	B, C, and D fit into CM but not with A_R (ICASE = 3, 4, 5) A_R and B must also fit into CM together
3	B, C, and D do not fit into CM, but A_X and $F = D - CA^{-1}B$ fit into CM for the LU decomposition of F
4	Same as 3 but $D - CA^{-1}B$ requires file storage for LU decomposition

When a NGF file (TAPE20) is written with ICASE = 3 or 5, files 13 and 14 are both written to TAPE20. When the NGF file is read these data are written on the single file 13 with the blocks in ascending order first and then in descending order. If A_F is stored on file 13 then space for A_R in CM is needed only when A_R is used in a solution in CM. This accounts for the definition of A_X.

File usage for ICASX = 2, 3, and 4 is outlined in Figures 13 and 14. The value for ICASX is chosen in subroutine FBNGF as the smallest value possible. The number of blocks into which matrices B, C, and D are divided is also chosen in FBNGF.

NGF Procedure for ICASX = 2	Contents of CM	Files 11	12	13	14	15	16
				A_F			
1. (CMNGF) Compute B, C and D in CM. Write to files 12, 14 and 15.	B, C, D		D	A_F	B	C	
2. (FACGF) Read 13 and 14. Compute $A^{-1}B$. Write 14.	A_F, B		D	A_F	$A^{-1}B$	C	
3. Compute $F = D - CA^{-1}B$. Store over D in CM.	$A^{-1}B$, C, D		D	A_F	$A^{-1}B$	C	
4. Factor F. Write on 11.	$A^{-1}B$, C, F	F_F		A_F	$A^{-1}B$	C	
Solution for excitation $(E_1, E_2)^T$ (SOLGF)							
1. Compute $I_1' = A^{-1}E_1$	A_F	F_F		A_F	$A^{-1}B$	C	
2. $I_2' = E_2 - CA^{-1}E_1 = E_2 - CI_1'$	C						
3. $I_2 = F^{-1}I_2'$	F_F						
4. $I_1 = I_1' - (A^{-1}B)I_2$	$A^{-1}B$						

(Subscript F indicates that the matrix has been factored into L and U triangular parts)

Figure 13. NGF File Usage for ICASX = 2.

NGF Procedure for ICASX = 3,4	Contents of CM	11	12	13	14	15	16
				A_F			
1. (CMNGF) Compute B by blocks of rows. Write to file 14.	A_X, B_R			A_F	B_R		
2. Compute C and D by blocks by rows. Write to 15 and 12.	A_X, C_R, D_R		D_R	A_F	B_R	C_R	
3. (REBLK) Read 14. Write B by blocks of columns on file 16.	A_X, B_C, B_R		D_R	A_F	B_R	C_R	B_C
4. (FACGF) Read 16; compute $A^{-1}B$; write 14.	A_F, B_C		D_R	A_F	$A^{-1}B_C$	C_R	
5. Read blocks from 12, 14 and 15 and compute $F = D - C(A^{-1}B)$ by blocks of rows. Write on 11.	A_X, $A_{-1}B_C$ C_R, D_R	F	D_R	A_F	$A^{-1}B_C$	C_R	
6. For ICASX = 4 call FACIO to factor F. FACIO reads 11 and writes 12, using 11 and 16 as scratch storage.	A_X and 2 blocks of F	X	F'_F	A_F	$A^{-1}B_C$	C_R	X
7. LUNSCR reads 12 and writes blocks of FF on 111 in forward order and on 16 in reversed order.	A_X and block of F	F_F		A_F	$A^{-1}B_C$	C_R	F_F
6' For ICASX = 3, read all blocks of F into CM; Factor F; write to 11.	A_X, F	F_F		A_F	$A^{-1}B_C$	C_R	

Figure 14. NGF File Usage for ICASX = 3 or 4.

Section VIII
NEC Subroutine Linkage

Figures 15 and 16 show the organization of subroutines in the NEC-2 program. All possible subroutine calls are traced, although in a particular run only certain of the traces will be followed. Routines that are called at more than one point in the program are shown as separate blocks for each call.

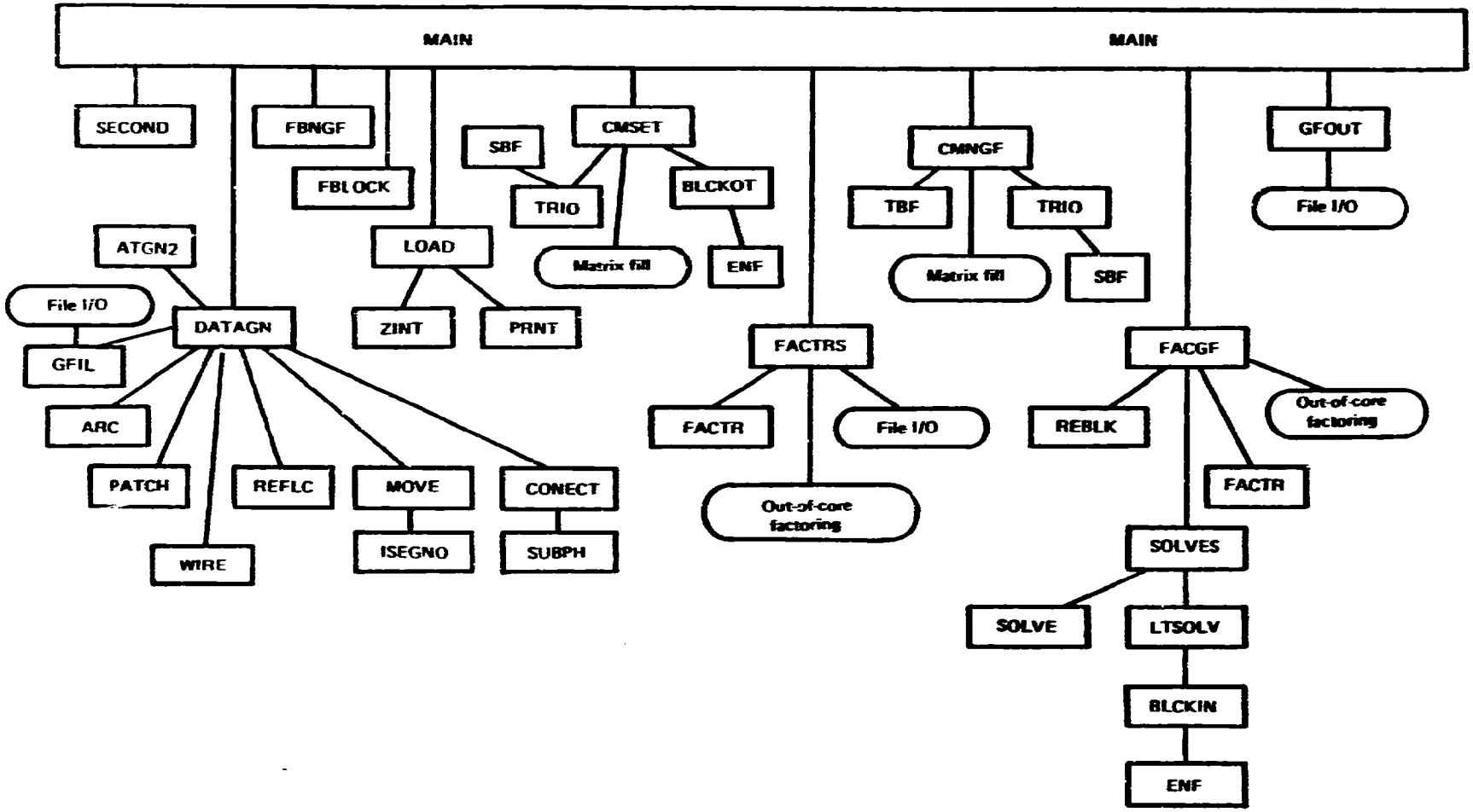


Figure 15. NEC Subroutine Linkage Chart. For Block Definitions, see Figure 16

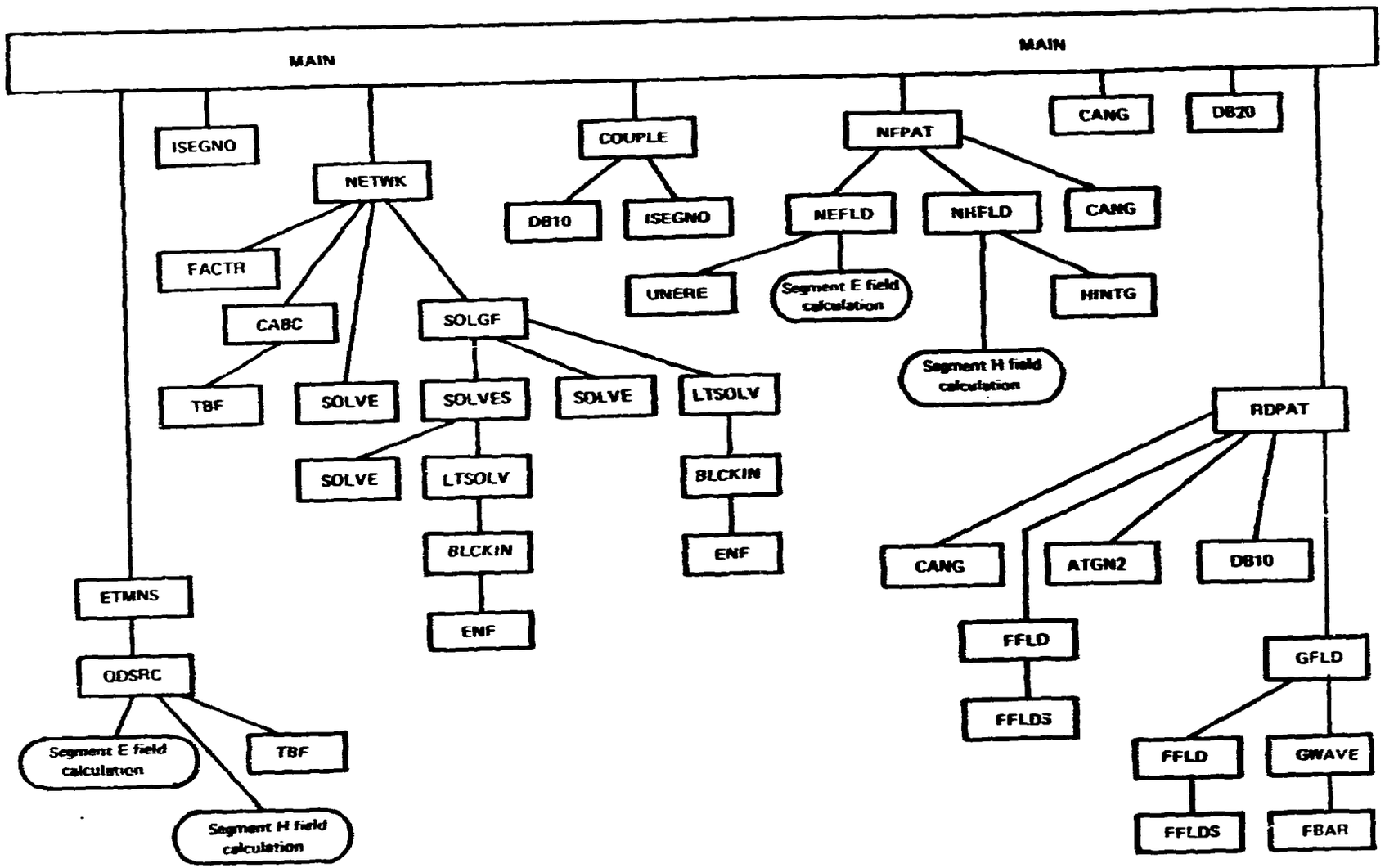


Figure 15 (continued)

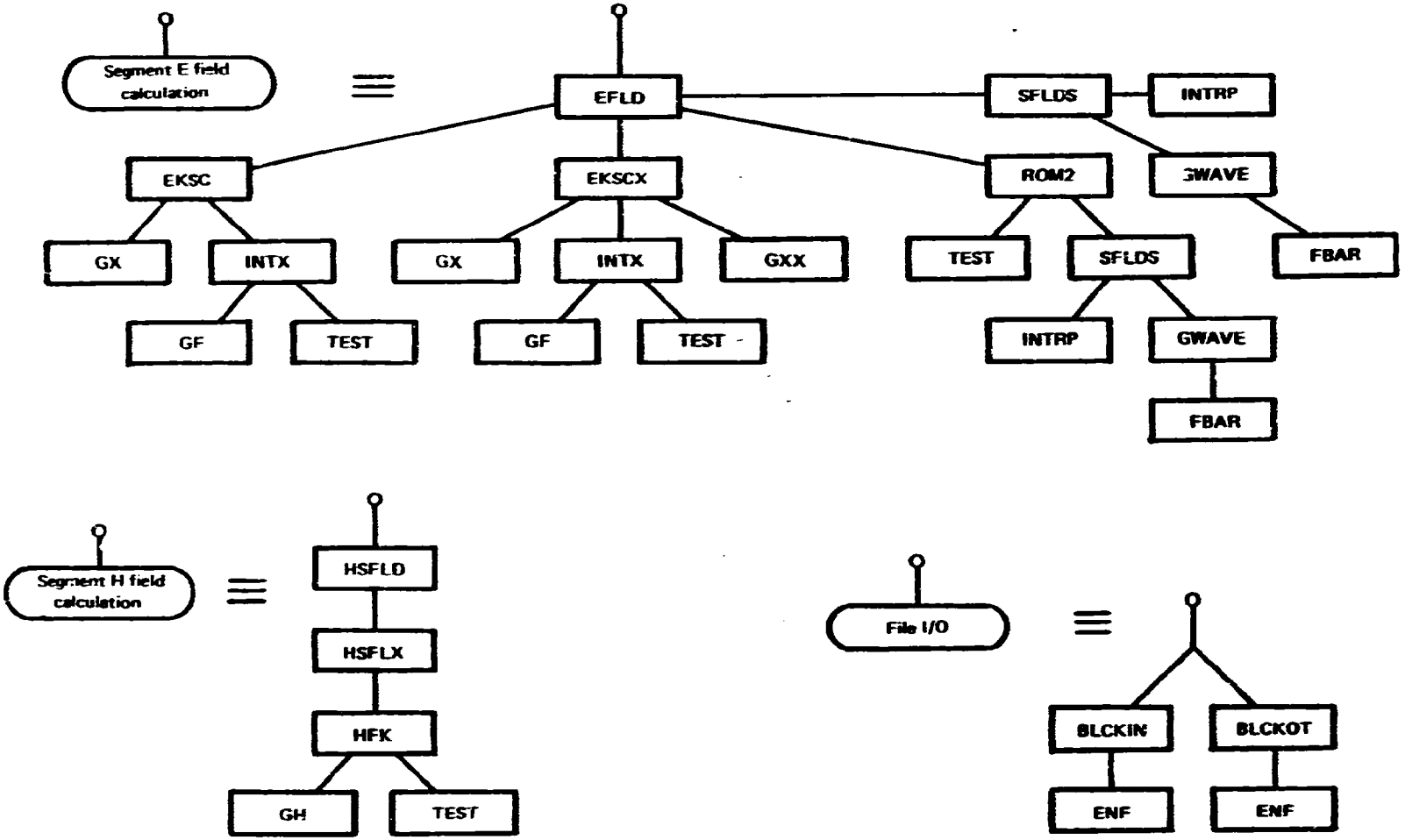


Figure 16. Block Definitions for NEC Subroutine Linkage Chart. See Figure 15

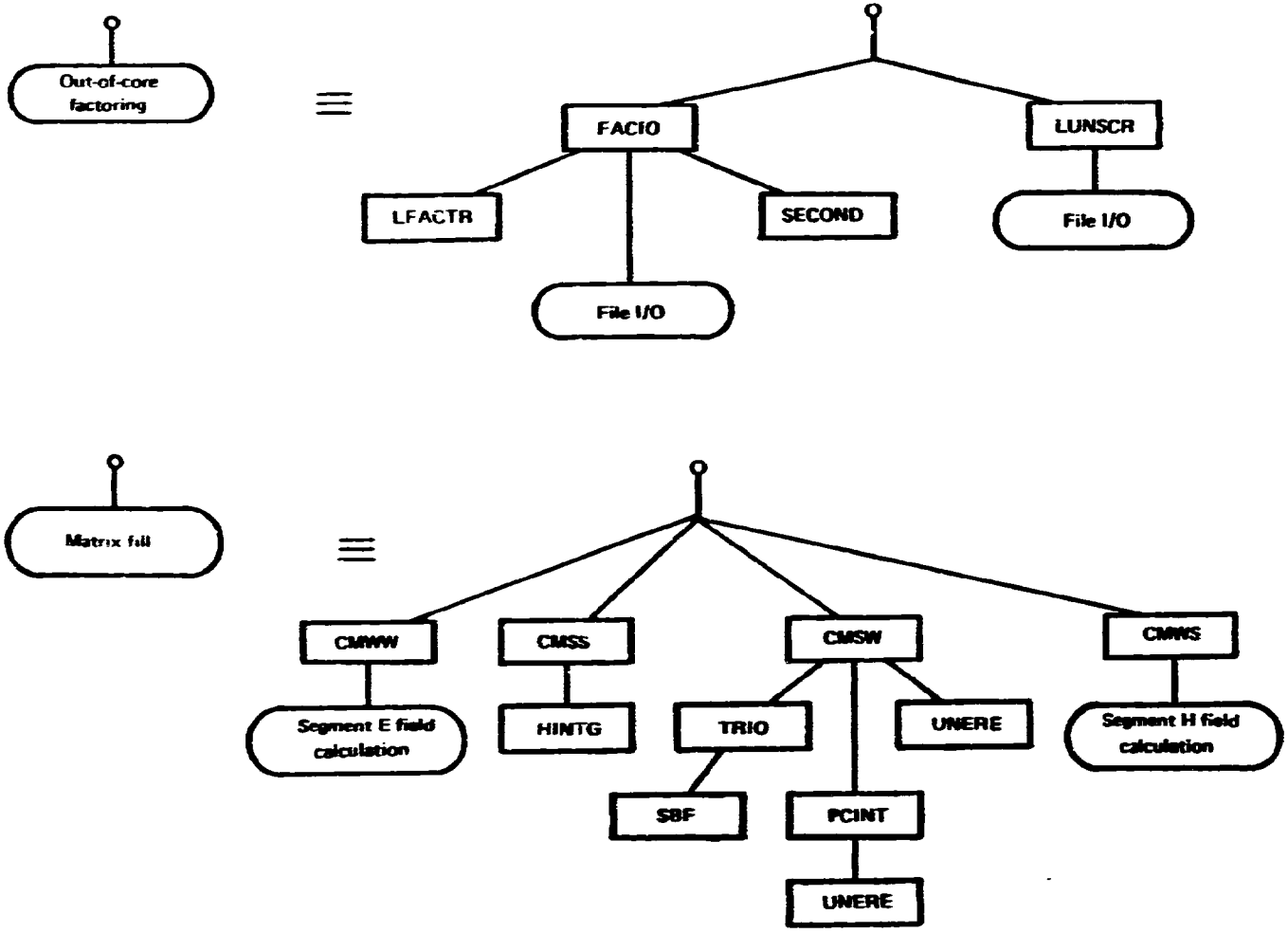


Figure 16 (continued)

Section IX
SOMNEC

1. SOMNEC CODE DESCRIPTION

SOMNEC is an independent code that generates the interpolation tables for the Sommerfeld/Norton ground option for NEC. The tables are written on file TAPE21 which becomes an input file to NEC. Coding of the routines in SOMNEC is described in this section.

SOMNEC (main program)

PURPOSE

To generate interpolation tables for the Sommerfeld/Norton ground option and write them on file TAPE21.

METHOD

The code from SN17 to SN51 reads the input data and sets parameters in COMMON/EVLCOM/. Since all equations are scaled to a free-space wavelength of one meter the results depend only on the complex dielectric constant

$$\epsilon_c = \epsilon_1 - j\sigma_1/(\omega\epsilon_0) .$$

In the routines that evaluate the Sommerfeld integrals the time dependence is exp(-jωt) rather than exp(+jωt) which is used in the remainder of NEC. Hence the conjugate of ϵ_c (EPSCF) is taken before computing the parameters in COMMON/EVLCOM/. The conjugate of the results is taken at the end of EVLUA, so the results returned to SOMNEC and written on TAPE21 are for exp(+jωt).

Three interpolation tables, as shown in Figure 12 of Part I, are generated in the code from SN55 to SN123. For each R_1, θ pair in the tables the values of ρ and z + z' are computed and stored in COMMON/EVLCOM/. Subroutine EVLUA is then called and returns the quantities

$$ERV = \frac{\partial^2}{\partial\rho\partial z} k_1^2 V_{22}'$$

$$EZV = (\frac{\partial^2}{\partial z^2} + k_2^2)\, k_1^2 V_{22}'$$

$$ERH = (\frac{\partial^2}{\partial\rho^2} k_2^2 V_{22}' + k_2^2 U_{22}')$$

$$EPH = -(\frac{1}{\rho}\frac{\partial}{\partial\rho} k_2^2 V_{22}' + k_2^2 U_{22}')$$

These are multiplied by $C_1 R_1 \exp(jkR_1)$ to form the quantities in equation (156) through (159) in Part I. When R_1 is zero the limiting forms in equations (169) through (172) of Part I are used. The expressions from

SN116 to SN118 are obtained by letting θ go to zero in the expressions for $R_1 = 0$.

The data are stored in COMMON/GGRID/ which is identical to the common block in NEC. File 21 is written at SN127 and includes coordinates of the grid boundaries, number of points, and increments for R_1 and θ. Hence those grid parameters can be changed in SOMNEC without changing NEC. If the number of grid points is increased, however, the arrays in COMMON/GGRID/ must be increased in both SOMNEC and NEC. Also, the parameters NDA and NDPA in subroutine INTRP must be changed.

SYMBOL DICTIONARY

AR1 = array for grid 1

AR2 = array for grid 2

AR3 = array for grid 3

CK1 = k_1

CK1R = real part of k_1

CK1SQ = k_1^2

CK2 = k_2 (= 2π since $\lambda = 1$)

CK2SQ = k_2^2

CKSM = $k_2^2/(k_1^2 + k_2^2)$

CL1 = $k_2^2 C_1 C_3$ (see Part 1 for C_1, C_2, and C_3)

CL2 = $k_2^2 C_1 C_2$

CON = $C_1 R_1 \exp(jkR_1)$

CT1 = $(k_1^2 - k_2^2)/2$

CT2 = $(k_1^4 - k_2^4)/8$

CT3 = $(k_1^6 - k_2^6)/16$

DR = ΔR_1

DTH = $\Delta\theta$

DXA = ΔR_1 for each grid

DYA = $\Delta\theta$ for each grid (radians)

EPH = EPH

EPR = ϵ_1

EPSCF = ϵ_c

ERH = ERH

ERV = ERV

EZV = EZV

FMHZ = frequency in MHz

IPT = flag to control printing of grid

IR = index for R_1 values

IRS = starting value for IR

ITH = index for θ values

LCOMP = labels for output

NR = number of R_1 values

NTH = number of θ values

NXA = number of R_1 values for each grid

NYA = number of θ values for each grid

R = R_1

RHO = ρ

RK = $k_2 R$

SIG = σ_1

TFAC1 = $(1 - \sin\theta)/\cos\theta$

TFAC2 = $(1 - \sin\theta)/\cos^2\theta$

THET = θ

TIM = time to fill arrays

TKMAG = $100.|k_1|$

TSMAG = $100.|k_1|^2$

TST = starting time

WLAM = wavelength in free space

XSA = starting value of R_1 in each grid

YSA = starting value of θ in each grid

ZPH = Z + Z'

CONSTANTS

299.8 = 10^{-6} times velocity of light in m/s

59.96 = $1/(2\pi c\epsilon_o)$, c = velocity of light

6.283185308 = 2π

```
      PROGRAM SOMNEC(INPUT,OUTPUT,TAPE21)                                SN    1
C                                                                        SN    2
C     PROGRAM TO GENERATE NEC INTERPOLATION GRIDS FOR FIELDS DUE TO      SN    3
C     GROUND.  FIELD COMPONENTS ARE COMPUTED BY NUMERICAL EVALUATION     SN    4
C     OF MODIFIED SOMMERFELD INTEGRALS.                                  SN    5
C                                                                        SN    6
      COMPLEX CK1,CK1SQ,ERV,EZV,ERH,EPH,AR1,AR2,AR3,EPSCF,CKSM,CT1,CT2,C SN    7
     1T3,CL1,CL2,CON                                                     SN    8
      COMMON /EVLCOM/ CKSM,CT1,CT2,CT3,CK1,CK1SQ,CK2,CK2SQ,TKMAG,TSMAG,C SN    9
     1K1R,ZPH,RHO,JH                                                     SN   10
      COMMON /GGRID/ AR1(11,10,4),AR2(17,5,4),AR3(9,8,4),EPSCF,DXA(3),DY SN   11
     1A(3),XSA(3),YSA(3),NXA(3),NYA(3)                                   SN   12
      DIMENSION LCOMP(4)                                                 SN   13
      DATA NXA/11,17,9/,NYA/10,5,8/,XSA/0.,.2,.2/,YSA/0.,0.,.3490658504/ SN   14
      DATA DXA/.02,.05,.1/,DYA/.1745329252,.0872664626,.1745329252/      SN   15
      DATA LCOMP/3HERV,3HEZV,3HERH,3HEPH/                                SN   16
C                                                                        SN   17
C     READ GROUND PARAMETERS - EPR = RELATIVE DIELECTRIC CONSTANT        SN   18
C                              SIG = CONDUCTIVITY (MHOS/M)               SN   19
C                              FMHZ = FREQUENCY (MHZ)                    SN   20
C                              IPT = 1 TO PRINT GRIDS.  =0 OTHERWISE.    SN   21
C     IF SIG .LT. 0. THEN COMPLEX DIELECTRIC CONSTANT = EPR + J*SIG      SN   22
C     AND FMHZ IS NOT USED                                               SN   23
C                                                                        SN   24
      READ 15, EPR,SIG,FMHZ,IPT                                          SN   25
      IF (SIG.LT.0.) GO TO 1                                             SN   26
      WLAM=299.8/FMHZ                                                    SN   27
      EPSCF=CMPLX(EPR,-SIG*WLAM*59.96)                                   SN   28
      GO TO 2                                                            SN   29
1     EPSCF=CMPLX(EPR,SIG)                                               SN   30
2     CALL SECOND (TST)                                                  SN   31
      CK2=6.283185308                                                    SN   32
      CK2SQ=CK2*CK2                                                      SN   33
C                                                                        SN   34
C     SOMMERFELD INTEGRAL EVALUATION USES EXP(-JWT), NEC USES EXP(+JWT), SN   35
C     HENCE NEED CONJG(EPSCF).  CONJUGATE OF FIELDS OCCURS IN SUBROUTINE SN   36
C     EVLUA.                                                             SN   37
C                                                                        SN   38
      CK1SQ=CK2SQ*CONJG(EPSCF)                                           SN   39
      CK1=CSQRT(CK1SQ)                                                   SN   40
      CK1R=REAL(CK1)                                                     SN   41
      TKMAG=100.*CABS(CK1)                                               SN   42
      TSMAG=100.*CK1*CONJG(CK1)                                          SN   43
      CKSM=CK2SQ/(CK1SQ+CK2SQ)                                           SN   44
      CT1=.5*(CK1SQ-CK2SQ)                                               SN   45
      ERV=CK1SQ*CK1SQ                                                    SN   46
      EZV=CK2SQ*CK2SQ                                                    SN   47
      CT2=.125*(ERV-EZV)                                                 SN   48
      ERV=ERV*CK1SQ                                                      SN   49
      EZV=EZV*CK2SQ                                                      SN   50
      CT3=.0625*(ERV-EZV)                                                SN   51
C                                                                        SN   52
C     LOOP OVER 3 GRID REGIONS                                           SN   53
C                                                                        SN   54
      DO 6 K=1,3                                                         SN   55
      NR=NXA(K)                                                          SN   56
      NTH=NYA(K)                                                         SN   57
      DR=DXA(K)                                                          SN   58
      DTH=DYA(K)                                                         SN   59
      R=XSA(K)-DR                                                        SN   60
      IRS=1                                                              SN   61
      IF (K.EQ.1) R=XSA(K)                                               SN   62
      IF (K.EQ.1) IRS=2                                                  SN   63
```

```
      C                                                                 SN  64
      C     LOOP OVER R.  (R=SQRT(RHO**2 + (Z+H)**2))                   SN  65
      C                                                                 SN  66
            DO 6 IR=IRS,NR                                              SN  67
            R=R+DR                                                      SN  68
            THET=YSA(K)-DTH                                             SN  69
      C                                                                 SN  70
      C     LOOP OVER THETA.  (THETA=ATAN((Z+H)/RHO))                   SN  71
      C                                                                 SN  72
            DO 6 ITH=1,NTH                                              SN  73
            THET=THET+DTH                                               SN  74
            RHO=R*COS(THET)                                             SN  75
            ZPH=R*SIN(THET)                                             SN  76
            IF (RHO.LT.1.E-7) RHO=1.E-6                                 SN  77
            IF (ZPH.LT.1.E-7) ZPH=0.                                    SN  78
            CALL EVLUA (ERV,EZV,ERH,EPH)                                SN  79
            RK=CK2*R                                                    SN  80
            CON=-(0.,.77147)*R/CMPLX(COS(RK),-SIN(RK))                  SN  81
            GO TO (3,4,5), K                                            SN  82
    3       AR1(IR,ITH,1)=ERV*CON                                       SN  83
            AR1(IR,ITH,2)=EZV*CON                                       SN  84
            AR1(IR,ITH,3)=ERH*CON                                       SN  85
            AR1(IR,ITH,4)=EPH*CON                                       SN  86
            GO TO 6                                                     SN  87
    4       AR2(IR,ITH,1)=ERV*CON                                       SN  88
            AR2(IR,ITH,2)=EZV*CON                                       SN  89
            AR2(IR,ITH,3)=ERH*CON                                       SN  90
            AR2(IR,ITH,4)=EPH*CON                                       SN  91
            GO TO 6                                                     SN  92
    5       AR3(IR,ITH,1)=ERV*CON                                       SN  93
            AR3(IR,ITH,2)=EZV*CON                                       SN  94
            AR3(IR,ITH,3)=ERH*CON                                       SN  95
            AR3(IR,ITH,4)=EPH*CON                                       SN  96
    6       CONTINUE                                                    SN  97
      C                                                                 SN  98
      C     FILL GRID 1 FOR R EQUAL TO ZERO.                            SN  99
      C                                                                 SN 100
            CL2=-(0.,188.370)*(EPSCF-1.)/(EPSCF+1.)                     SN 101
            CL1=CL2/(EPSCF+1.)                                          SN 102
            EZV=EPSCF*CL1                                               SN 103
            THET=-DTH                                                   SN 104
            NTH=NYA(1)                                                  SN 105
            DO 9 ITH=1,NTH                                              SN 106
            THET=THET+DTH                                               SN 107
            IF (ITH.EQ.NTH) GO TO 7                                     SN 108
            TFAC2=COS(THET)                                             SN 109
            TFAC1=(1.-SIN(THET))*TFAC2                                  SN 110
            TFAC2=TFAC1/TFAC2                                           SN 111
            ERV=EPSCF*CL1*TFAC1                                         SN 112
            ERH=CL1*(TFAC2-1.)+CL2                                      SN 113
            EPH=CL1*TFAC2-CL2                                           SN 114
            GO TO 8                                                     SN 115
    7       ERV=0.                                                      SN 116
            ERH=CL2-.5*CL1                                              SN 117
            EPH=-ERH                                                    SN 118
    8       AR1(1,ITH,1)=ERV                                            SN 119
            AR1(1,ITH,2)=EZV                                            SN 120
            AR1(1,ITH,3)=ERH                                            SN 121
    9       AR1(1,ITH,4)=EPH                                            SN 122
            CALL SECOND (TIM)                                           SN 123
      C                                                                 SN 124
      C     WRITE GRID ON TAPE21                                        SN 125
      C                                                                 SN 126
            WRITE (21) AR1,AR2,AR3,EPSCF,DXA,DYA,XSA,YSA,NXA,NYA        SN 127
```

```
      REWIND 21                                                          SN 128
      IF (IPT.EQ.0) GO TO 14                                             SN 129
C                                                                        SN 130
C     PRINT GRID                                                         SN 131
C                                                                        SN 132
      PRINT 17, EPSCF                                                    SN 133
      DO 13 K=1,3                                                        SN 134
      NR=NXA(K)                                                          SN 135
      NTH=NYA(K)                                                         SN 136
      PRINT 18, K,XSA(K),DXA(K),NR,YSA(K),DYA(K),NTH                     SN 137
      DO 13 L=1,4                                                        SN 138
      PRINT 19, LCOMP(L)                                                 SN 139
      DO 13 IR=1,NR                                                      SN 140
      GO TO (10,11,12), K                                                SN 141
10    PRINT 20, IR,(AR1(IR,ITH,L),ITH=1,NTH)                             SN 142
      GO TO 13                                                           SN 143
11    PRINT 20, IR,(AR2(IR,ITH,L),ITH=1,NTH)                             SN 144
      GO TO 13                                                           SN 145
12    PRINT 20, IR,(AR3(IR,ITH,L),ITH=1,NTH)                             SN 146
13    CONTINUE                                                           SN 147
14    TIM=TIM-TST                                                        SN 148
      PRINT 16,TIM                                                       SN 149
      STOP                                                               SN 150
C                                                                        SN 151
15    FORMAT (3E10.3,I5)                                                 SN 152
16    FORMAT (6H TIME=,E12.5)                                            SN 153
17    FORMAT (30H1NEC GROUND INTERPOLATION GRID,/,21H DIELECTRIC CONSTAN SN 154
     1T=,2E12.5)                                                         SN 155
18    FORMAT (///,5H GRID,I2,/,4X,5HR(1)=,F7.4,4X,3HDR=,F7.4,4X,3HNR=,I3 SN 156
     1,/,9H THET(1)=,F7.4,3X,4HDTH=,F7.4,3X,4HNTH=,I3,//)               SN 157
19    FORMAT (///,A3)                                                    SN 158
20    FORMAT (4H IR=,I3,/,(10E12.5))                                     SN 159
      END                                                                SN 160-
```

BESSEL

PURPOSE

To compute the Bessel function of order zero and its derivative for a complex argument.

METHOD

For argument magnitudes less than a limit Z_s the functions are evaluated by the ascending series and for larger magnitudes by Hankel's asymptotic expansion (ref. 5). The ascending series are

$$J_0(Z) = \sum_{k=0}^{\infty} \frac{(-Z^2/4)^k}{(k!)^2}$$

$$J_0'(Z) = -J_1(Z) = -\frac{Z}{2} \sum_{k=0}^{\infty} \frac{(-Z^2/4)^k}{k!(k+1)!}$$

The number of terms used with an argument Z is M(IZ) where $IZ = 1. + |Z|^2$. The array M is filled for IZ from 1 to 101 on the first call to BESSEL by determining the value of k at which the term in the series for J_0 is less than 10^{-6}.

When |Z| is greater than Z_s Hankel's asymptotic expansions are used with two or three terms. These are

$$J_\nu(Z) = \sqrt{\frac{2}{\pi Z}} [P(\nu,Z)\cos \chi - Q(\nu,Z)\sin \chi] \qquad (|\arg Z| < \pi)$$

$$\chi = Z - (\tfrac{1}{2}\nu + \tfrac{1}{4})\pi$$

$$P(\nu,Z) = 1 - \frac{(\mu-1)(\mu-9)}{2!(8Z)^2} + \frac{(\mu-1)(\mu-9)(\mu-25)(\mu-49)}{4!(8Z)^4}$$

$$Q(\nu,Z) = \frac{(\mu-1)}{8} - \frac{(\mu-1)(\mu-9)(\mu-25)}{3!(8Z)^3}$$

where $\mu = 4\nu^2$.

When $Z_s < |Z| < Z_s + \Delta$ both the series and asymptotic forms are evaluated and are combined as

$$J(Z) = \frac{1}{2}\left[J_s(Z)(1+C) + J_a(Z)(1-C)\right]$$

where $C = \cos\left(\frac{\pi}{\Delta}(|Z| - Z_s)\right)$

$J_s(Z)$ = result of series evaluation

$J_a(Z)$ = result of asymptotic evaluation

This combination ensures a smooth transition between the two regions. In the code Z_s is 6 and Δ is 0.1.

SYMBOL DICTIONARY

A1 = $-1./(4k^2)$

A2 = $1./(k + 1)$

C3 = $\sqrt{2/\pi} = 0.7978845608$

CZ = $\cos \chi$

FJ = $\sqrt{-1.}$

FJX = FJ

IB = 1 to indicate that both the series and asymptotic forms will be evaluated and combined

INIT = flag to indicate that initialization of constants has been completed

IZ = $1. + |Z|^2$ truncated to an integer

JO = $J_0(Z)$

JOP = $J_0'(Z)$

JOPX = $J_0'(Z)$ from series to be combined with asymptotic result

JOX = $J_0(Z)$, same as JOPX

K = summation index k, summed from 1 to limit

M = array of upper limits for k

MIZ = upper limit for k

POZ = P(0,z)

P10 = coefficient in POZ = $9/(2 \times 8^2)$

P11 = coefficient in P1Z = $-(4 - 1)(4 - 9)/(2 \times 8^2)$

P1Z = P(1,Z)

P20 = coefficient in POZ = $9 \times 25 \times 49/(4!8^4)$

P21 = coefficient in P1Z = $-(4 - 1)(4 - 9)(4 - 25)(4 - 49)/(4!8^4)$

PI = π

POF = $\pi/4$

QOZ = Q(0,Z)

Q10 = coefficient in Q(0,Z) = 1/8

Q11 = coefficient in Q(1,Z) = 3/8

Q1Z = Q(1,Z)

Q20 = coefficient in Q(0,Z) = $9 \times 25/(3!8^3)$

Q21 = coefficient in Q(1,Z) = $(4 - 1)(4 - 9)(4 - 25)/(3!8^3)$

SZ = sin χ

TEST = magnitude of the term in the series

Z = Z

ZI = Z^2 or 1/Z

ZI2 = $1/Z^2$ or $\exp(-j\chi)$

ZK = $(-Z^2/4)^k/(k!)^2$ for series. Also temporary storage for asymptotic method

ZMS = $|Z|^2$ or temporary storage

CONSTANTS

31.41592654 = $10.\pi$

36. = 6^2

37.21 = 6.1^2

```
      SUBROUTINE BESSEL (Z,JO,JOP)                                      BE   1
C                                                                       BE   2
C     BESSEL EVALUATES THE ZERO-ORDER BESSEL FUNCTION AND ITS DERIVATIVE BE   3
C     FOR COMPLEX ARGUMENT Z.                                           BE   4
C                                                                       BE   5
      COMPLEX JO,JOP,P0Z,P1Z,Q0Z,Q1Z,Z,ZI,ZI2,ZK,FJ,CZ,SZ,JOX,JOPX      BE   6
      DIMENSION M(101), A1(25), A2(25), FJX(2)                          BE   7
      EQUIVALENCE (FJ,FJX)                                              BE   8
      DATA PI,C3,P10,P20,Q10,Q20/3.141592654,.7978845608,.0703125,.11215 BE   9
     120998,.125,.0732421875/                                           BE  10
      DATA P11,P21,Q11,Q21/.1171875,.1441955566,.375,.1025390625/       BE  11
      DATA POF,INIT/.7853981635,0/,FJX/0.,1./                           BE  12
      IF (INIT.EQ.0) GO TO 5                                            BE  13
1     ZMS=Z*CONJG(Z)                                                    BE  14
      IF (ZMS.GT.1.E-12) GO TO 2                                        BE  15
      JO=(1.,0.)                                                        BE  16
      JOP=-.5*Z                                                         BE  17
      RETURN                                                            BE  18
2     IB=0                                                              BE  19
      IF (ZMS.GT.37.21) GO TO 4                                         BE  20
      IF (ZMS.GT.36.) IB=1                                              BE  21
C     SERIES EXPANSION                                                  BE  22
      IZ=1.+ZMS                                                         BE  23
      MIZ=M(IZ)                                                         BE  24
      JO=(1.,0.)                                                        BE  25
      JOP=JO                                                            BE  26
      ZK=JO                                                             BE  27
      ZI=Z*Z                                                            BE  28
      DO 3 K=1,MIZ                                                      BE  29
      ZK=ZK*A1(K)*ZI                                                    BE  30
      JO=JO+ZK                                                          BE  31
3     JOP=JOP+A2(K)*ZK                                                  BE  32
      JOP=-.5*Z*JOP                                                     BE  33
      IF (IB.EQ.0) RETURN                                               BE  34
      JOX=JO                                                            BE  35
      JOPX=JOP                                                          BE  36
C     ASYMPTOTIC EXPANSION                                              BE  37
4     ZI=1./Z                                                           BE  38
      ZI2=ZI*ZI                                                         BE  39
      P0Z=1.+(P20*ZI2-P10)*ZI2                                          BE  40
      P1Z=1.+(P11-P21*ZI2)*ZI2                                          BE  41
      Q0Z=(Q20*ZI2-Q10)*ZI                                              BE  42
      Q1Z=(Q11-Q21*ZI2)*ZI                                              BE  43
      ZK=CEXP(FJ*(Z-POF))                                               BE  44
      ZI2=1./ZK                                                         BE  45
      CZ=.5*(ZK+ZI2)                                                    BE  46
      SZ=FJ*.5*(ZI2-ZK)                                                 BE  47
      ZK=C3*CSQRT(ZI)                                                   BE  48
      JO=ZK*(P0Z*CZ-Q0Z*SZ)                                             BE  49
      JOP=-ZK*(P1Z*SZ+Q1Z*CZ)                                           BE  50
      IF (IB.EQ.0) RETURN                                               BE  51
      ZMS=COS((SQRT(ZMS)-6.)*31.41592654)                               BE  52
      JO=.5*(JOX*(1.+ZMS)+JO*(1.-ZMS))                                  BE  53
      JOP=.5*(JOPX*(1.+ZMS)+JOP*(1.-ZMS))                               BE  54
      RETURN                                                            BE  55
C     INITIALIZATION OF CONSTANTS                                       BE  56
5     DO 6 K=1,25                                                       BE  57
      A1(K)=-.25/(K*K)                                                  BE  58
6     A2(K)=1./(K+1.)                                                   BE  59
      DO 8 I=1,101                                                      BE  60
      TEST=1.                                                           BE  61
      DO 7 K=1,24                                                       BE  62
      INIT=K                                                            BE  63
      TEST=-TEST*I*A1(K)                                                BE  64
```

```
65          IF (TEST.LT.1.E-6) GO TO 8                          BE  65
66 7        CONTINUE                                            BE  66
67 8        M(I)=INIT                                           BE  67
68          GO TO 1                                             BE  68
69          END                                                 BE  69-
```

EVLUA

PURPOSE

To control the evaluation of the Sommerfeld integrals.

METHOD

The integration contour of either Figures 13, 14 or 15 of Part I is used depending on the values of ρ, $Z + Z'$ and k_1. Figures 13, 14, and 15 should be inverted, however, since they are for a time dependence of $\exp(j\omega t)$ and the coding for the Sommerfeld integrals is for $\exp(-j\omega t)$. Thus the contours and branch cuts in EVALUA are the conjugate of those shown. The conjugate of the results is taken at the end of EVLUA to conform to the NEC time dependence of $\exp(j\omega t)$.

The code from EV 19 to EV 34 evaluates the Bessel function form of the Sommerfeld integrals using the contour of Figure 13 of Part I. ROM1 is called to integrate from $\lambda = 0$ to $(p - jp)$ and GSHANK is called for the path from $(p - jp)$ to infinity where p^{-1} is the maximum of ρ and $Z + Z'$ (p = DEL). If p is greater than $100.|k_1|$ then ROM1 is called for the interval 0 to $(p_1 - jp_1)$ where $p_1 = 10|k_1|$. This is done to avoid exceeding the limit by which ROM1 can cut the interval width. Larger steps can then be used from $(p_1 - jp_1)$ to $(p - jp)$ since $\gamma_1 \approx \gamma_2 \approx \lambda$.

The code from EV 39 to EV 86 evaluates the Hankel function form of the integrals using either the contour of Figure 14 or 15. At EV 50 SUM is the negative of the integral from a* to c*. GSHANK is then called to integrate from a* to $-\infty$. The decision whether to use the contour of Figures 14 or 15 is made from EV 58 to EV 64. Figure 15 is used if the real part of $\rho(k_1 - k_2)$ exceeds $2k_2$ and

$$\frac{-u}{|v|} > \frac{4\rho}{Z+Z'}$$

where $u + jv = [-(Z + Z') + j\rho][d^* - c^*]$ is the argument of the exponential function approximating the Sommerfeld integrand for large λ with $\lambda = d^* - c^*$. The left side of the inequality is proportional to the decay per cycle along the c to d path and $\rho/(Z + Z')$ is the same for the vertical path. This condition was chosen arbitrarily but gives some indication of when the contour of Figure 16 may be advantageous.

For the contour of Figure 15 GSHANK is called to integrate from e* to infinity. ROM1 is then called from e* to f*. The sign of the contribution from other parts of the path is switched since they were integrated in reverse direction. Finally, GSHANK is called for the paths from c* to infinity and f* to infinity.

For the contour of Figure 14 (GS 79 to GS 86) GSHANK is called to integrate from c* to d* and on to infinity. The increment changes from DELTA to DELTA2 if d* is reached before the integral converges.

From EV 89 to EV 92 the integrals are combined to form the field components and the conjugates are taken.

SYMBOL DICTIONARY

A	= start of integration interval
ANS	= temporary storage
B	= end of integration interval
BK	= break point (d*) in path for GSHANK
CK1	= k_1
CK1SQ	= k_1^2
CK2	= k_2
CK2SQ	= k_2^2
CP1	= a*
CP2	= b*
CP3	= c*
DEL	= p
DELTA	= increment along path
DELTA2	= alternate increment
EPH	= (see SOMNEC)
ERH	= (see SOMNEC)
ERV	= (see SOMNEC)
EZV	= (see SOMNEC)
JH	= 0 for Bessel function form, 1 for Hankel function form
PTP	= 0.2π
RHØ	= ρ

RMIS = temporary storage

SLOPE = slope of paths to infinity

SUM = temporary storage

TKMAG = $100|k_1|$

ZPH = $\angle + \angle'$

```
      SUBROUTINE EVLUA (ERV,EZV,ERH,EPH)                                EV   1
C                                                                       EV   2
C     EVALUA CONTROLS THE INTEGRATION CONTOUR IN THE COMPLEX LAMBDA     EV   3
C     PLANE FOR EVALUATION OF THE SOMMERFELD INTEGRALS.                 EV   4
C                                                                       EV   5
      COMPLEX ERV,EZV,ERH,EPH,A,B,CK1,CK1SQ,BK,SUM,DELTA,ANS,DELTA2,CP1, EV   6
     1CP2,CP3,CKSM,CT1,CT2,CT3                                          EV   7
      COMMON /CNTOUR/ A,B                                               EV   8
      COMMON /EVLCOM/ CKSM,CT1,CT2,CT3,CK1,CK1SQ,CK2,CK2SQ,TKMAG,TSMAG,C EV   9
     1K1R,ZPH,RHO,JH                                                    EV  10
      DIMENSION SUM(6), ANS(6)                                          EV  11
      DATA PTP/.6283185308/                                             EV  12
      DEL=ZPH                                                           EV  13
      IF (RHO.GT.DEL) DEL=RHO                                           EV  14
      IF (ZPH.LT.2.*RHO) GO TO 4                                        EV  15
C                                                                       EV  16
C     BESSEL FUNCTION FORM OF SOMMERFELD INTEGRALS                      EV  17
C                                                                       EV  18
      JH=0                                                              EV  19
      A=(0.,0.)                                                         EV  20
      DEL=1./DEL                                                        EV  21
      IF (DEL.LE.TKMAG) GO TO 2                                         EV  22
      B=CMPLX(.1*TKMAG,-.1*TKMAG)                                       EV  23
      CALL ROM1 (6,SUM,2)                                               EV  24
      A=B                                                               EV  25
      B=CMPLX(DEL,-DEL)                                                 EV  26
      CALL ROM1 (6,ANS,2)                                               EV  27
      DO 1 I=1,6                                                        EV  28
1     SUM(I)=SUM(I)+ANS(I)                                              EV  29
      GO TO 3                                                           EV  30
2     B=CMPLX(DEL,-DEL)                                                 EV  31
      CALL ROM1 (6,SUM,2)                                               EV  32
3     DELTA=PTP*DEL                                                     EV  33
      CALL GSHANK (B,DELTA,ANS,6,SUM,0,B,B)                             EV  34
      GO TO 10                                                          EV  35
C                                                                       EV  36
C     HANKEL FUNCTION FORM OF SOMMERFELD INTEGRALS                      EV  37
C                                                                       EV  38
4     JH=1                                                              EV  39
      CP1=CMPLX(0.,.4*CK2)                                              EV  40
      CP2=CMPLX(.6*CK2,-.2*CK2)                                         EV  41
      CP3=CMPLX(1.02*CK2,-.2*CK2)                                       EV  42
      A=CP1                                                             EV  43
      B=CP2                                                             EV  44
      CALL ROM1 (6,SUM,2)                                               EV  45
      A=CP2                                                             EV  46
      B=CP3                                                             EV  47
      CALL ROM1 (6,ANS,2)                                               EV  48
      DO 5 I=1,6                                                        EV  49
5     SUM(I)=-(SUM(I)+ANS(I))                                           EV  50
C     PATH FROM IMAGINARY AXIS TO -INFINITY                             EV  51
      SLOPE=1000.                                                       EV  52
      IF (ZPH.GT..001*RHO) SLOPE=RHO/ZPH                                EV  53
      DEL=PTP/DEL                                                       EV  54
      DELTA=CMPLX(-1.,SLOPE)*DEL/SQRT(1.+SLOPE*SLOPE)                   EV  55
      DELTA2=-CONJG(DELTA)                                              EV  56
      CALL GSHANK (CP1,DELTA,ANS,6,SUM,0,BK,BK)                         EV  57
      RMIS=RHO*(REAL(CK1)-CK2)                                          EV  58
      IF (RMIS.LT.2.*CK2) GO TO 8                                       EV  59
      IF (RHO.LT.1.E-10) GO TO 8                                        EV  60
      IF (ZPH.LT.1.E-10) GO TO 6                                        EV  61
      BK=CMPLX(-ZPH,RHO)*(CK1-CP3)                                      EV  62
      RMIS=-REAL(BK)/ABS(AIMAG(BK))                                     EV  63
      IF(RMIS.GT.4.*RHO/ZPH)GO TO 8                                     EV  64
```

```
      C     INTEGRATE UP BETWEEN BRANCH CUTS, THEN TO + INFINITY
    6 6     CP1=CK1-(.1,.2)
      7     CP2=CP1+.2
      8     BK=CMPLX(0.,DEL)
      9     CALL GSHANK (CP1,BK,SUM,6,ANS,0,BK,BK)
     10     A=CP1
     11     B=CP2
     12     CALL ROM1 (6,ANS,1)
     13     DO 7 I=1,6
    14 7    ANS(I)=ANS(I)-SUM(I)
     15     CALL GSHANK (CP3,BK,SUM,6,ANS,0,BK,BK)
     16     CALL GSHANK (CP2,DELTA2,ANS,6,SUM,0,BK,BK)
     17     GO TO 10
     18 C   INTEGRATE BELOW BRANCH POINTS, THEN TO + INFINITY
    19 8    DO 9 I=1,6
    20 9    SUM(I)=-ANS(I)
     21     RMIS=REAL(CK1)*1.01
     22     IF (CK2+1..GT.RMIS) RMIS=CK2+1.
     23     BK=CMPLX(RMIS,.99*AIMAG(CK1))
     24     DELTA=BK-CP3
     25     DELTA=DELTA*DEL/CABS(DELTA)
     26     CALL GSHANK (CP3,DELTA,ANS,6,SUM,1,BK,DELTA2)
    27 10   ANS(6)=ANS(6)*CK1
    28 C    CONJUGATE SINCE NEC USES EXP(+JWT)
     29     ERV=CONJG(CK1SQ*ANS(3))
     30     EZV=CONJG(CK1SQ*(ANS(2)+CK2SQ*ANS(5)))
     31     ERH=CONJG(CK2SQ*(ANS(1)+ANS(6)))
     32     EPH=-CONJG(CK2SQ*(ANS(4)+ANS(6)))
     33     RETURN
     34     END
```

EV 65
EV 66
EV 67
EV 68
EV 69
EV 70
EV 71
EV 72
EV 73
EV 74
EV 75
EV 76
EV 77
EV 78
EV 79
EV 80
EV 81
EV 82
EV 83
EV 84
EV 85
EV 86
EV 87
EV 88
EV 89
EV 90
EV 91
EV 92
EV 93
EV 94-

GSHANK

PURPOSE

To apply the Shanks transformation (ref. 6) to accelerate the convergence of a semi-infinite integral.

METHOD

Six integrals (NANS = 6) are evaluated simultaneously in this routine. The integrals over semi-infinite sections of the contours (Figures 13, 14 and 15 of Part I) are evaluated by using the Romberg variable interval width integration method on subsections to obtain a converging sequence of partial sums

$$S_i = S_0 + \int_{A_0}^{A_0+i\Delta} f(\lambda)d\lambda \qquad i = 1, 2, \ldots$$

where A_0 is the start of the semi-infinite path, S_0 is the contribution from other parts of the contour and Δ is a complex increment with

$$|\Delta| = \text{minimum of } \begin{cases} 0.2\pi/\rho \\ 0.2\pi/(Z + Z') \end{cases}$$

$$\arg(\Delta) = \text{direction of integration path in } \lambda\text{-plane}$$

The Shanks interated first order transformation is applied to S_i to accelerate convergence. Starting with the sequence of M elements $Q_{i,0} = S_i$, i = 1, ... M the j^{th} iterated transform is the sequence of M - 2j elements

$$Q_{ij} = \frac{Q_{i-1,j-1}Q_{i+1,j-1} - Q_{i,j-1}^2}{Q_{i-1,j-1} + Q_{i+1,j-1} - 2Q_{i,j-1}}$$

$$= Q_{i-1,j-1} - \frac{(Q_{i,j-1} - Q_{i-1,j-1})^2}{Q_{i-1,j-1} + Q_{i+1,j-1} - 2Q_{i,j-1}}$$

$i = j + 1, \ldots M - j$

$j = 1, \ldots [(M - 1)/2].$

The second form for $Q_{i,j}$ is used since it suffers less numerical error as the sequence converges. Each iteration of the transform should produce a sequence that converges more rapidly to the limit of the original sequence.

In this subroutine the starting value S_0 comes in as SEED. With each pass through the loop over INT, starting at GS 21, two new values are added to the sequence by calling ROM1 to evaluate the integrals

$$S_{2N-1} = S_{2N-2} + \int_{A_0+(2N-2)\Delta}^{A_0+(2N-1)\Delta} f(\lambda)d\lambda$$

$$S_{2N} = S_{2N-1} + \int_{A_0+(2N-1)\Delta}^{A_0+(2N)\Delta} f(\lambda)d\lambda$$

where N = INT. The $(N - 1)^{th}$ interated Shanks transformation, consisting of the two elements $Q_{N,N-1}$ and $Q_{N+1,N-1}$, is then computed. At the end of each pass through the loop over INT the arrays Q1 and Q2 contain the last two elements in each sequence. For function I,

$$Q1(I,J) = Q_{2N-J,J-1}$$

$$Q2(I,J) = Q_{2N-J+1,J-1}, \quad J = 1, \ldots N.$$

For the path from c to infinity in Figure 14 of Part I the point d is a break point at which Δ may change. If d is reached before convergence the Shanks transformation is started over with the final value of S_i becoming S_0 for the new sequence.

Convergence is tested from GS 78 to GS 89 by comparing the last two values in the transformed sequences. Although the last sequence, consisting of two elements, should have the highest convergence the last four sequences are tested to avoid a false indication of convergence. The relative difference is computed for each of the six functions and compared with CRIT. If convergence does not occur by INT = MAXH a message is printed and the average of the two values in the last sequence is used for each integral. In computing the relative difference for each function the denominator is not allowed to be less than 10^{-3} times the magnitude of the largest of the six functions to avoid convergence problems when one function goes to zero.

SYMBOL DICTIONARY

A = beginning of integration subinterval
A1 = new value for Q1 array
A2 = new value for Q2 array
AA = temporary storage
AMG = approximate magnitude of function
ANS1 = S_i for i odd
ANS2 = S_i for i even
AS1 = S_i for i odd
AS2 = S_i for i even
B = end of integration subinterval
BK = break point in integration contour
CRIT = limit for relative error in convergence test
DEL = Δ
DELA = Δ before break point
DELB = Δ after break point
DEN = approximate magnitude of the largest of the six functions (GS 76)
DENM = minimum denominator for relative error test
IBK = 1 if path contains break point
IBX = 0 if path contains break point and it has not been passed
INT = N

INX = INT

JM = J - 1

MAXH = maximum for index J in Q1 and Q2

NANS = number of functions (6)

Q1, Q2 = (see description of method)

RBK = real part of BK

SEED = S_0

START = A_0

SUM = increment to integral

```
      SUBROUTINE GSHANK (START,DELA,SUM,NANS,SEED,IBK,BK,DELB)                GS   1
C                                                                             GS   2
C     GSHANK INTEGRATES THE 6 SOMMERFELD INTEGRALS FROM START TO              GS   3
C     INFINITY (UNTIL CONVERGENCE) IN LAMBDA.  AT THE BREAK POINT, BK,        GS   4
C     THE STEP INCREMENT MAY BE CHANGED FROM DELA TO DELB.  SHANK S           GS   5
C     ALGORITHM TO ACCELERATE CONVERGENCE OF A SLOWLY CONVERGING SERIES        GS   6
C     IS USED                                                                 GS   7
C                                                                             GS   8
      COMPLEX START,DELA,SUM,SEED,BK,DELB,A,B,Q1,Q2,ANS1,ANS2,A1,A2,AS1,      GS   9
     1AS2,DEL,AA                                                              GS  10
      COMMON /CNTOUR/ A,B                                                     GS  11
      DIMENSION Q1(6,20), Q2(6,20), ANS1(6), ANS2(6), SUM(6), SEED(6)         GS  12
      DATA CRIT/1.E-4/,MAXH/20/                                               GS  13
      RBK=REAL(BK)                                                            GS  14
      DEL=DELA                                                                GS  15
      IBX=0                                                                   GS  16
      IF (IBK.EQ.0) IBX=1                                                     GS  17
      DO 1 I=1,NANS                                                           GS  18
    1 ANS2(I)=SEED(I)                                                         GS  19
      B=START                                                                 GS  20
    2 DO 20 INT=1,MAXH                                                        GS  21
      INX=INT                                                                 GS  22
      A=B                                                                     GS  23
      B=B+DEL                                                                 GS  24
      IF (IBX.EQ.0.AND.REAL(B).GE.RBK) GO TO 5                                GS  25
      CALL ROM1 (NANS,SUM,2)                                                  GS  26
      DO 3 I=1,NANS                                                           GS  27
    3 ANS1(I)=ANS2(I)+SUM(I)                                                  GS  28
      A=B                                                                     GS  29
      B=B+DEL                                                                 GS  30
      IF (IBX.EQ.0.AND.REAL(B).GE.RBK) GO TO 6                                GS  31
      CALL ROM1 (NANS,SUM,2)                                                  GS  32
      DO 4 I=1,NANS                                                           GS  33
    4 ANS2(I)=ANS1(I)+SUM(I)                                                  GS  34
      GO TO 11                                                                GS  35
C     HIT BREAK POINT.  RESET SEED AND START OVER.                            GS  36
    5 IBX=1                                                                   GS  37
      GO TO 7                                                                 GS  38
    6 IBX=2                                                                   GS  39
    7 B=BK                                                                    GS  40
      DEL=DELB                                                                GS  41
      CALL ROM1 (NANS,SUM,2)                                                  GS  42
      IF (IBX.EQ.2) GO TO 9                                                   GS  43
      DO 8 I=1,NANS                                                           GS  44
    8 ANS2(I)=ANS2(I)+SUM(I)                                                  GS  45
      GO TO 2                                                                 GS  46
    9 DO 10 I=1,NANS                                                          GS  47
   10 ANS2(I)=ANS1(I)+SUM(I)                                                  GS  48
      GO TO 2                                                                 GS  49
   11 DEN=0.                                                                  GS  50
      DO 18 I=1,NANS                                                          GS  51
      AS1=ANS1(I)                                                             GS  52
      AS2=ANS2(I)                                                             GS  53
      IF (INT.LT.2) GO TO 17                                                  GS  54
      DO 16 J=2,INT                                                           GS  55
      JM=J-1                                                                  GS  56
      AA=Q2(I,JM)                                                             GS  57
      A1=Q1(I,JM)+AS1-2.*AA                                                   GS  58
      IF (REAL(A1).EQ.0..AND.AIMAG(A1).EQ.0.) GO TO 12                        GS  59
      A2=AA-Q1(I,JM)                                                          GS  60
      A1=Q1(I,JM)-A2*A2/A1                                                    GS  61
      GO TO 13                                                                GS  62
   12 A1=Q1(I,JM)                                                             GS  63
   13 A2=AA+AS2-2.*AS1                                                        GS  64
```

```
      IF (REAL(A2).EQ.0..AND.AIMAG(A2).EQ.0.) GO TO 14                  GS  65
      A2=AA-(AS1-AA)*(AS1-AA)/A2                                        GS  66
      GO TO 15                                                          GS  67
14    A2=AA                                                             GS  68
15    Q1(I,JM)=AS1                                                      GS  69
      Q2(I,JM)=AS2                                                      GS  70
      AS1=A1                                                            GS  71
16    AS2=A2                                                            GS  72
17    Q1(I,INT)=AS1                                                     GS  73
      Q2(I,INT)=AS2                                                     GS  74
      AMG=ABS(REAL(AS2))+ABS(AIMAG(AS2))                                GS  75
      IF (AMG.GT.DEN) DEN=AMG                                           GS  76
18    CONTINUE                                                          GS  77
      DENM=1.E-3*DEN*CRIT                                               GS  78
      JM=INT-3                                                          GS  79
      IF (JM.LT.1) JM=1                                                 GS  80
      DO 19 J=JM,INT                                                    GS  81
      DO 19 I=1,NANS                                                    GS  82
      A1=Q2(I,J)                                                        GS  83
      DEN=(ABS(REAL(A1))+ABS(AIMAG(A1)))*CRIT                           GS  84
      IF (DEN.LT.DENM) DEN=DENM                                         GS  85
      A1=Q1(I,J)-A1                                                     GS  86
      AMG=ABS(REAL(A1))+ABS(AIMAG(A1))                                  GS  87
      IF (AMG.GT.DEN) GO TO 20                                          GS  88
19    CONTINUE                                                          GS  89
      GO TO 22                                                          GS  90
20    CONTINUE                                                          GS  91
      PRINT 24                                                          GS  92
      DO 21 I=1,NANS                                                    GS  93
21    PRINT 25, Q1(I,INX),Q2(I,INX)                                     GS  94
22    DO 23 I=1,NANS                                                    GS  95
23    SUM(I)=.5*(Q1(I,INX)+Q2(I,INX))                                   GS  96
      RETURN                                                            GS  97
C                                                                       GS  98
24    FORMAT (46H **** NO CONVERGENCE IN SUBROUTINE GSHANK ****)        GS  99
25    FORMAT (10E12.5)                                                  GS 100
      END                                                               GS 101-
```

HANKEL

PURPOSE

To compute the Hankel function of the first kind, zeroth order, and its derivative for a complex argument.

METHOD

For argument magnitudes less than a limit Z_s the functions are evaluated by the ascending series and for larger magnitudes by Hankel's asymptotic expansion (ref. 5). The series are

$$Y_0(Z) = \frac{2}{\pi} \ln(Z/2) J_0(Z) - \frac{2}{\pi} \sum_{k=0}^{\infty} \psi(k+1) \frac{(-Z^2/4)^k}{(k!)^2}$$

$$Y_0'(Z) = \frac{2}{\pi Z} + \frac{2}{\pi} \ln(Z/2) J_0'(Z) + \frac{Z}{2\pi} \sum_{k=0}^{\infty} [\psi(k+1) + \psi(k+2)] \frac{(-Z^2/4)^k}{k!(k+1)!}$$

where $\psi(k+1) = -\gamma + \sum_{j=1}^{k} j^{-1}$

$\psi(1) = -\gamma$,

γ = Euler's constant = 0.5772156649

The Hankel functions are

$$H_0^{(1)}(Z) = J_0(Z) + j\, Y_0(Z)$$

$$H_0^{(1)'}(Z) = J_0'(Z) + j\, Y_0'(Z)$$

The series for $J_0(Z)$ and $J_0'(Z)$ are given in the description of subroutine BESSEL. The number of terms used with an argument Z is M(IZ) where IZ = 1. + $|Z|^2$.

The array M is filled for IZ from 1 to 101 on the first call to HANKEL by determining the value of k at which the term in the series of Y_0 is less than 10^{-6}.

When $|Z|$ is greater than Z_s Hankel's asymptotic expansions are used with two or three terms. These are

$$H_\nu^{(1)}(Z) = \sqrt{\frac{2}{\pi Z}}\,[P(\nu,Z) + jQ(\nu,Z)]e^{jX}$$

$$X = Z - (\tfrac{1}{2}\nu + \tfrac{1}{4})\pi$$

$P(\nu,Z)$ and $Q(\nu,Z)$ are given in the description of subroutine BESSEL.

When $Z_s < |Z| < Z_s + \Delta$ both the series and asymptotic forms are evaluated and are combined as in BESSEL to eliminate any discontinity. In HANKEL Z_s is 4 and Δ is 0.1.

SYMBOL DICTIONARY

A1 = $-1./(4k^2)$

A2 = $1./(k+1)$

A3 = $2\psi(k+1)$

A4 = $[\psi(k+1) + \psi(k+2)]/(k+1)$

C1 = $[\psi(1) + \psi(2)]/(2\pi)$

C2 = $2\gamma/\pi$

C3 = $\sqrt{2/\pi}$

CLOGZ = $\ln(Z)$

FJ = $\sqrt{-1}$

FJX = FJ

GAMMA = γ

HO = $H_0^{(1)}(Z)$

HOP = $H_0^{(1)'}(Z)$

IB = 1 to indicate that both the series and asymptotic forms will be evaluated and combined

INIT = flag to indicate that initialization of constants has been completed

IZ = $1. + |Z|^2$

JO = $J_0(Z)$

JOP = $J_0'(Z)$

K = summation index k, summed from 1 to limit

M = array of upper limits for k

MIZ = upper limit for k

P0Z, P10, P11, P1Z, P20, P21: see BESSEL

PI = π

POF = $\pi/4$

PSI = ψ

Q0Z, Q10, Q11, Q1Z, Q20, Q21: see BESSEL

TEST = magnitude of term in the series

YO = $Y_0(Z)$

YOP = $Y_0'(Z)$

Z = Z

ZI = Z^2 or $1/Z$

ZI2 = $1/Z^2$

ZK = $(-Z^2/4)^k/(k!)^2$; also temporary storage

ZMS = $|Z^2|$ or temporary storage

CONSTANTS

16.	4^2
16.81	4.1^2
31.41592654	$10.\pi$

HANKEL

```
      SUBROUTINE HANKEL (Z,HO,HOP)                                          HA   1
C                                                                           HA   2
C     HANKEL EVALUATES HANKEL FUNCTION OF THE FIRST KIND, ORDER ZERO,       HA   3
C     AND ITS DERIVATIVE FOR COMPLEX ARGUMENT Z.                            HA   4
C                                                                           HA   5
      COMPLEX CLOGZ,HO,HOP,JO,JOP,POZ,P1Z,QOZ,Q1Z,YO,YOP,Z,ZI,ZI2,ZK,FJ    HA   6
      DIMENSION M(101), A1(25), A2(25), A3(25), A4(25), FJX(2)              HA   7
      EQUIVALENCE (FJ,FJX)                                                  HA   8
      DATA PI,GAMMA,C1,C2,C3,P10,P20/3.141592654,.5772156649,-.024578509    HA   9
     1,.3674669052,.7978845608,.0703125,.1121520996/                        HA  10
      DATA Q10,Q20,P11,P21,Q11,Q21/.125,.0732421875,.1171875,.1441955566    HA  11
     1,.375,.1025390625/                                                    HA  12
      DATA POF,INIT/.7853981635,0/,FJX/0.,1./                               HA  13
      IF (INIT.EQ.0) GO TO 5                                                HA  14
1     ZMS=Z*CONJG(Z)                                                        HA  15
      IF (ZMS.NE.0.) GO TO 2                                                HA  16
      PRINT 9                                                               HA  17
      STOP                                                                  HA  18
2     IB=0                                                                  HA  19
      IF (ZMS.GT.16.81) GO TO 4                                             HA  20
      IF (ZMS.GT.16.) IB=1                                                  HA  21
C     SERIES EXPANSION                                                      HA  22
      IZ=1.+ZMS                                                             HA  23
      MIZ=M(IZ)                                                             HA  24
      JO=(1.,0.)                                                            HA  25
      JOP=JO                                                                HA  26
      YO=(0.,0.)                                                            HA  27
      YOP=YO                                                                HA  28
      ZK=JO                                                                 HA  29
      ZI=Z*Z                                                                HA  30
      DO 3 K=1,MIZ                                                          HA  31
      ZK=ZK*A1(K)*ZI                                                        HA  32
      JO=JO+ZK                                                              HA  33
      JOP=JOP+A2(K)*ZK                                                      HA  34
      YO=YO+A3(K)*ZK                                                        HA  35
3     YOP=YOP+A4(K)*ZK                                                      HA  36
      JOP=-.5*Z*JOP                                                         HA  37
      CLOGZ=CLOG(.5*Z)                                                      HA  38
      YO=(2.*JO*CLOGZ-YO)/PI+C2                                             HA  39
      YOP=(2./Z+2.*JOP*CLOGZ+.5*YOP*Z)/PI+C1*Z                              HA  40
      HO=JO+FJ*YO                                                           HA  41
      HOP=JOP+FJ*YOP                                                        HA  42
      IF (IB.EQ.0) RETURN                                                   HA  43
      YO=HO                                                                 HA  44
      YOP=HOP                                                               HA  45
C     ASYMPTOTIC EXPANSION                                                  HA  46
4     ZI=1./Z                                                               HA  47
      ZI2=ZI*ZI                                                             HA  48
      POZ=1.+(P20*ZI2-P10)*ZI2                                              HA  49
      P1Z=1.+(P11-P21*ZI2)*ZI2                                              HA  50
      QOZ=(Q20*ZI2-Q10)*ZI                                                  HA  51
      Q1Z=(Q11-Q21*ZI2)*ZI                                                  HA  52
      ZK=CEXP(FJ*(Z-POF))*CSQRT(ZI)*C3                                      HA  53
      HO=ZK*(POZ+FJ*QOZ)                                                    HA  54
      HOP=FJ*ZK*(P1Z+FJ*Q1Z)                                                HA  55
      IF (IB.EQ.0) RETURN                                                   HA  56
      ZMS=COS((SQRT(ZMS)-4.)*31.41592654)                                   HA  57
      HO=.5*(YO*(1.+ZMS)+HO*(1.-ZMS))                                       HA  58
      HOP=.5*(YOP*(1.+ZMS)+HOP*(1.-ZMS))                                    HA  59
      RETURN                                                                HA  60
C     INITIALIZATION OF CONSTANTS                                           HA  61
5     PSI=-GAMMA                                                            HA  62
      DO 6 K=1,25                                                           HA  63
      A1(K)=-.25/(K*K)                                                      HA  64
```

```
      A2(K)=1./(K+1.)                                                    HA  65
      PSI=PSI+1./K                                                       HA  66
      A3(K)=PSI+PSI                                                      HA  67
6     A4(K)=(PSI+PSI+1./(K+1.))/(K+1.)                                   HA  68
      DO 8 I=1,101                                                       HA  69
      TEST=1.                                                            HA  70
      DO 7 K=1,24                                                        HA  71
      INIT=K                                                             HA  72
      TEST=-TEST*I*A1(K)                                                 HA  73
      IF (TEST*A3(K).LT.1.E-6) GO TO 8                                   HA  74
7     CONTINUE                                                           HA  75
8     M(I)=INIT                                                          HA  76
      GO TO 1                                                            HA  77
C                                                                        HA  78
9     FORMAT (34H ERROR - HANKEL NOT VALID FOR Z=0.)                     HA  79
      END                                                                HA  80-
```

LAMBDA

PURPOSE

To compute the complex value of λ from the real integration parameter in RUN1.

METHOD

For integration along a straight path between the points a and b in the λ plane, λ and $d\lambda$ are

$$\lambda = a + (b - a)t$$

$$d\lambda = (b - a)dt$$

SYMBOL DICTIONARY

A = a

B = b

DXLAM = b - a

T = t

XLAM = λ

```
      SUBROUTINE LAMBDA (T,XLAM,DXLAM)                                  LA   1
C                                                                       LA   2
C     COMPUTE INTEGRATION PARAMETER XLAM=LAMBDA FROM PARAMETER T.       LA   3
C                                                                       LA   4
      COMPLEX A,B,XLAM,DXLAM                                            LA   5
      COMMON /CNTOUR/ A,B                                               LA   6
      DXLAM=B-A                                                         LA   7
      XLAM=A+DXLAM*T                                                    LA   8
      RETURN                                                            LA   9
      END                                                               LA  10-
```

ROM1

PURPOSE

To integrate the Sommerfeld integrands between two points in λ by the method of variable interval-width Romberg integration.

METHOD

A and B in common block /CNTOUR/ are the ends of the integration path and are set before ROM1 is called. The integration parameter Z in ROM1 starts at zero and ends at one. The corresponding value of λ is determined by subroutine LAMBDA as

$$\lambda = A + (B - A)Z$$

Subroutine SAOA returns six integrand values which are handled simultaneously in loops throughout the code. The Romberg variable interval-width integration method will not be described in detail since it is the same as that used in subroutine INTX in the main NEC program. The convergence test in ROM1 requires that all six components satisfy the relative error tests simultaneously.

```
      SUBROUTINE ROM1 (N,SUM,NX)                                        RO   1
C                                                                       RO   2
C     ROM1 INTEGRATES THE 6 SOMMERFELD INTEGRALS FROM A TO B IN LAMBDA. RO   3
C     THE METHOD OF VARIABLE INTERVAL WIDTH ROMBERG INTEGRATION IS USED. RO   4
C                                                                       RO   5
      COMPLEX A,B,SUM,G1,G2,G3,G4,G5,T00,T01,T10,T02,T11,T20            RO   6
      COMMON /CNTOUR/ A,B                                               RO   7
      DIMENSION SUM(6), G1(6), G2(6), G3(6), G4(6), G5(6), T01(6), T10(6 RO   8
     1), T20(6)                                                         RO   9
      DATA NM,NTS,RX/131072,4,1.E-4/                                    RO  10
      LSTEP=0                                                           RO  11
      Z=0.                                                              RO  12
      ZE=1.                                                             RO  13
      S=1.                                                              RO  14
      EP=S/(1.E4*NM)                                                    RO  15
      ZEND=ZE-EP                                                        RO  16
      DO 1 I=1,N                                                        RO  17
1     SUM(I)=(0.,0.)                                                    RO  18
      NS=NX                                                             RO  19
      NT=0                                                              RO  20
      CALL SAOA (Z,G1)                                                  RO  21
2     DZ=S/NS                                                           RO  22
      IF (Z+DZ.LE.ZE) GO TO 3                                           RO  23
      DZ=ZE-Z                                                           RO  24
      IF (DZ.LE.EP) GO TO 17                                            RO  25
3     DZOT=DZ*.5                                                        RO  26
      CALL SAOA (Z+DZOT,G3)                                             RO  27
      CALL SAOA (Z+DZ,G5)                                               RO  28
4     NOGO=0                                                            RO  29
      DO 5 I=1,N                                                        RO  30
      T00=(G1(I)+G5(I))*DZOT                                            RO  31
      T01(I)=(T00+DZ*G3(I))*.5                                          RO  32
      T10(I)=(4.*T01(I)-T00)/3.                                         RO  33
C     TEST CONVERGENCE OF 3 POINT ROMBERG RESULT                        RO  34
      CALL TEST (REAL(T01(I)),REAL(T10(I)),TR,AIMAG(T01(I)),AIMAG(T10(I) RO  35
     1),TI,0.)                                                          RO  36
      IF (TR.GT.RX.OR.TI.GT.RX) NOGO=1                                  RO  37
5     CONTINUE                                                          RO  38
      IF (NOGO.NE.0) GO TO 7                                            RO  39
      DO 6 I=1,N                                                        RO  40
6     SUM(I)=SUM(I)+T10(I)                                              RO  41
      NT=NT+2                                                           RO  42
      GO TO 11                                                          RO  43
7     CALL SAOA (Z+DZ*.25,G2)                                           RO  44
      CALL SAOA (Z+DZ*.75,G4)                                           RO  45
      NOGO=0                                                            RO  46
      DO 8 I=1,N                                                        RO  47
      T02=(T01(I)+DZOT*(G2(I)+G4(I)))*.5                                RO  48
      T11=(4.*T02-T01(I))/3.                                            RO  49
      T20(I)=(16.*T11-T10(I))/15.                                       RO  50
C     TEST CONVERGENCE OF 5 POINT ROMBERG RESULT                        RO  51
      CALL TEST (REAL(T11),REAL(T20(I)),TR,AIMAG(T11),AIMAG(T20(I)),TI,0 RO  52
     1.)                                                                RO  53
      IF (TR.GT.RX.OR.TI.GT.RX) NOGO=1                                  RO  54
8     CONTINUE                                                          RO  55
      IF (NOGO.NE.0) GO TO 13                                           RO  56
9     DO 10 I=1,N                                                       RO  57
10    SUM(I)=SUM(I)+T20(I)                                              RO  58
      NT=NT+1                                                           RO  59
11    Z=Z+DZ                                                            RO  60
      IF (Z.GT.ZEND) GO TO 17                                           RO  61
      DO 12 I=1,N                                                       RO  62
12    G1(I)=G5(I)                                                       RO  63
      IF (NT.LT.NTS.OR.NS.LE.NX) GO TO 2                                RO  64
```

```
      NS=NS/2                                                          RO  65
      NT=1                                                             RO  66
      GO TO 2                                                          RO  67
13    NT=0                                                             RO  68
      IF (NS.LT.NM) GO TO 15                                           RO  69
      IF (LSTEP.EQ.1) GO TO 9                                          RO  70
      LSTEP=1                                                          RO  71
      CALL LAMBDA (Z,T00,T11)                                          RO  72
      PRINT 18, T00                                                    RO  73
      PRINT 19, Z,DZ,A,B                                               RO  74
      DO 14 I=1,N                                                      RO  75
14    PRINT 19, G1(I),G2(I),G3(I),G4(I),G5(I)                          RO  76
      GO TO 9                                                          RO  77
15    NS=NS*2                                                          RO  78
      DZ=S/NS                                                          RO  79
      DZOT=DZ*.5                                                       RO  80
      DO 16 I=1,N                                                      RO  81
      G5(I)=G3(I)                                                      RO  82
16    G3(I)=G2(I)                                                      RO  83
      GO TO 4                                                          RO  84
17    CONTINUE                                                         RO  85
      RETURN                                                           RO  86
C                                                                      RO  87
18    FORMAT (38H ROM1 -- STEP SIZE LIMITED AT LAMBDA =,2E12.5)        RO  88
19    FORMAT (10E12.5)                                                 RO  89
      END                                                              RO  90
```

SAOA

PURPOSE

To compute the integrands for the Sommerfeld integrals.

METHOD

The input to SAOA is the integration parameter T and constants in common block /EVLCOM/. The integration variable λ corresponding to T is obtained by calling subroutine LAMBDA. The values returned in array ANS are

$$ANS(1) = D_2 H_0^{(1)''}(\lambda\rho) e^{-\gamma_2(z+z')} \lambda^3 d\lambda/dT$$

$$ANS(2) = D_2 \gamma_2^2 H_0^{(1)}(\lambda\rho) e^{-\gamma_2(z+z')} \lambda\, d\lambda/dT$$

$$ANS(3) = -D_2 \gamma_2 H_0^{(1)'}(\lambda\rho) e^{-\gamma_2(z+z')} \lambda^2 d\lambda/dT$$

$$ANS(4) = \rho^{-1} D_2 H_0^{(1)'}(\lambda\rho) e^{-\gamma_2(z+z')} \lambda^2 d\lambda/dT$$

$$ANS(5) = D_2 H_0^{(1)}(\lambda\rho) e^{-\gamma_2(z+z')} \lambda d\lambda/dT$$

$$ANS(6) = k_1^{-1} D_1 H_0^{(1)}(\lambda\rho) e^{-\gamma_2(z+z')} \lambda d\lambda/dT$$

where $D_1 = \dfrac{1}{\gamma_1+\gamma_2} - \dfrac{k_2^2}{\gamma_2(k_1^2+k_2^2)}$

$$D_2 = \frac{1}{k_1^2\gamma_2+k_2^2\gamma_1} - \frac{1}{\gamma_2(k_1^2+k_2^2)} = \frac{k_2^2(\gamma_2-\gamma_1)}{\gamma_2(k_1^2+k_2^2)(k_1^2\gamma_2+k_2^2\gamma_1)}$$

$$\gamma_1 = [\lambda^2 - k_1^2]^{1/2}$$

$$\gamma_2 = [\lambda^2 - k_2^2]^{1/2}$$

$$k_1 = k_2(\epsilon_1 - j\sigma_1/\omega\epsilon_0)^{1/2}$$

$$k_2 = \omega\sqrt{\mu_0\epsilon_0}$$

The integrands given above are computed when JH >0. When JH ≤ 0, $H_0^{(1)}(\lambda\rho)$ is replaced by $2J_0(\lambda\rho)$. The functions γ_1 and γ_2 are computed from SA 24 to SA 29 so that the branch cuts are vertical. This is not necessary from SA 17 to SA 20 since for the Bessel function form the integration contour is confined to a different quadrant than the branch cuts.

To avoid loss of accuracy due to cancellation when λ is large, D_2 is computed from the approximation for $\gamma_2 - \gamma_1$:

$$\gamma_2 - \gamma_1 \approx \pm\left[\frac{1}{2}\frac{k_1^2-k_2^2}{\lambda} + \frac{1}{8}\frac{k_1^4-k_2^4}{\lambda^3} + \frac{1}{16}\frac{k_1^6-k_2^6}{\lambda^5}\right]$$

when $|\lambda|^2 \geq 100.|k_1|^2$.
The sign is:

- for $\lambda_R < k_{2_R}$, $\lambda_I \geq 0$
- for $\lambda_R < -k_{1_R}$, $\lambda_I < 0$
+ for $\lambda_R > k_{1_R}$, $\lambda_I \geq 0$
+ for $\lambda_R > -k_{2_R}$, $\lambda_I < 0$.

There is no cancellation and this approximation is not valid when

$$k_{2_R} \leq \lambda_R \leq k_{1_R}, \quad \lambda_I \geq 0$$
$$\text{or} \quad -k_{1_r} \leq \lambda_R \leq -k_{2_R}, \quad \lambda_I < 0.$$

D_1 and D_2 are computed from SA 30 to SA 44.

SYMBOL DICTIONARY

ANS	= integrand values
BO	= $2J_0(\lambda\rho)$ or $H_0^{(1)}(\lambda\rho)$
BOP	= $2J_0(\lambda\rho)/\rho$ or $H_0^{(1)'}(\lambda\rho)/\rho$
CGAM1	= γ_1
CGAM2	= γ_2
CK1	= k_1
CK1R	= real part of k_1
CK1SQ	= k_1^2
CK2	= k_2
CK2SQ	= k_2^2
CKSM	= $k_2^2/(k_1^2+k_2^2)$
COM	= $\exp[-\gamma_2(z+z')]\lambda d\lambda/dT$ at SA 45
CT1	= $(k_1^2-k_2^2)/2$
CT2	= $(k_1^4-k_2^4)/8$
CT3	= $(k_1^6-k_2^6)/16$
DEN1	= D_1
DEN2	= D_2
DGAM	= $\gamma_2 - \gamma_1$
DXL	= $d\lambda/dT$
JH	= flag to select Bessel or Hankel function form
RHO	= ρ
SIGN	= sign in approximation for $\gamma_2 - \gamma_1$
T	= integration parameter
TKMAG	= $100.\|k_1\|$
TSMAG	= $100.\|k_1\|^2$
XL	= λ
XLR	= real part of λ
ZPH	= $z + z'$

```
      SUBROUTINE SAOA (T,ANS)                                                  SA   1
C                                                                              SA   2
C     SAOA COMPUTES THE INTEGRAND FOR EACH OF THE 6                            SA   3
C     SOMMERFELD INTEGRALS FOR SOURCE AND OBSERVER ABOVE GROUND                SA   4
C                                                                              SA   5
      COMPLEX ANS,XL,DXL,CGAM1,CGAM2,BO,BOP,COM,CK1,CK1SQ,CKSM,CT1,CT2,C       SA   6
     1T3,DGAM,DEN1,DEN2                                                        SA   7
      COMMON /EVLCOM/ CKSM,CT1,CT2,CT3,CK1,CK1SQ,CK2,CK2SQ,TKMAG,TSMAG,C      SA   8
     1K1R,ZPH,RHO,JH                                                           SA   9
      DIMENSION ANS(6)                                                         SA  10
      CALL LAMBDA (T,XL,DXL)                                                   SA  11
      IF (JH.GT.0) GO TO 1                                                     SA  12
C     BESSEL FUNCTION FORM                                                     SA  13
      CALL BESSEL (XL*RHO,BO,BOP)                                              SA  14
      BO=2.*BO                                                                 SA  15
      BOP=2.*BOP                                                               SA  16
      CGAM1=CSQRT(XL*XL-CK1SQ)                                                 SA  17
      CGAM2=CSQRT(XL*XL-CK2SQ)                                                 SA  18
      IF (REAL(CGAM1).EQ.0.) CGAM1=CMPLX(0.,-ABS(AIMAG(CGAM1)))                SA  19
      IF (REAL(CGAM2).EQ.0.) CGAM2=CMPLX(0.,-ABS(AIMAG(CGAM2)))                SA  20
      GO TO 2                                                                  SA  21
C     HANKEL FUNCTION FORM                                                     SA  22
1     CALL HANKEL (XL*RHO,BO,BOP)                                              SA  23
      COM=XL-CK1                                                               SA  24
      CGAM1=CSQRT(XL+CK1)*CSQRT(COM)                                           SA  25
      IF (REAL(COM).LT.0..AND.AIMAG(COM).GE.0.) CGAM1=-CGAM1                   SA  26
      COM=XL-CK2                                                               SA  27
      CGAM2=CSQRT(XL+CK2)*CSQRT(COM)                                           SA  28
      IF (REAL(COM).LT.0..AND.AIMAG(COM).GE.0.) CGAM2=-CGAM2                   SA  29
2     XLR=XL*CONJG(XL)                                                         SA  30
      IF (XLR.LT.TSMAG) GO TO 3                                                SA  31
      IF (AIMAG(XL).LT.0.) GO TO 4                                             SA  32
      XLR=REAL(XL)                                                             SA  33
      IF (XLR.LT.CK2) GO TO 5                                                  SA  34
      IF (XLR.GT.CK1R) GO TO 4                                                 SA  35
3     DGAM=CGAM2-CGAM1                                                         SA  36
      GO TO 7                                                                  SA  37
4     SIGN=1.                                                                  SA  38
      GO TO 6                                                                  SA  39
5     SIGN=-1.                                                                 SA  40
6     DGAM=1./(XL*XL)                                                          SA  41
      DGAM=SIGN*((CT3*DGAM+CT2)*DGAM+CT1)/XL                                   SA  42
7     DEN2=CKSM*DGAM/(CGAM2*(CK1SQ*CGAM2+CK2SQ*CGAM1))                         SA  43
      DEN1=1./(CGAM1+CGAM2)-CKSM/CGAM2                                         SA  44
      COM=DXL*XL*CEXP(-CGAM2*ZPH)                                              SA  45
      ANS(6)=COM*BO*DEN1/CK1                                                   SA  46
      COM=COM*DEN2                                                             SA  47
      IF (RHO.EQ.0.) GO TO 8                                                   SA  48
      BOP=BOP/RHO                                                              SA  49
      ANS(1)=-COM*XL*(BOP+BO*XL)                                               SA  50
      ANS(4)=COM*XL*BOP                                                        SA  51
      GO TO 9                                                                  SA  52
8     ANS(1)=-COM*XL*XL*.5                                                     SA  53
      ANS(4)=ANS(1)                                                            SA  54
9     ANS(2)=COM*CGAM2*CGAM2*BO                                                SA  55
      ANS(3)=-ANS(4)*CGAM2*RHO                                                 SA  56
      ANS(5)=COM*BO                                                            SA  57
      RETURN                                                                   SA  58
      END                                                                      SA  59-
```

SECOND - see SECOND in main NEC program.

TEST - see TEST in main NEC program.

2. COMMON BLOCKS IN SOMNEC

COMMON/CNTOUR/ A, B

Routines Using /CNTOUR/

EVLUA, GSHANK, LAMBDA, ROM1

Parameters

A = start of integration interval

B = end of integration interval

A and B are used by subroutine LAMBDA to compute the complex value of λ from the real parameter supplied by ROM1.

COMMON/EVLCOM/ CKSM, CT1, CT2, CT3, CK1, CK1SQ, CK2, CK2SQ, TKMAG, TSMAG, CK1R, ZPH, RHO, JH

Routines Using /EVLCOM/

SOMNEC, EVLUA, SAOA

Parameters

See symbol dictionaries for subroutines

COMMON/GGRID/ AR1 (11, 10, 4), AR2 (17, 5, 4), AR3 (9, 8, 4), EPSCF, DXA(3), DYA(3), XSA(3), YSA(3), NXA(3), NYA(3)

Routines Using /GGRID/

SOMNEC (main program)

Parameters

AR1 = array for grid 1 (see Figure 12, Part I)

AR2 = array for grid 2

AR3 = array for grid 3

EPSCF = ε_c

For grid i, ARi(j, k, m) is the value of I_ρ^V, I_z^V, I_ρ^H, or I_ϕ^H for M = 1, ... 4 respectively at the point

$$R_1/\lambda = S_i + (j-1)\Delta R_i \qquad j = 1, \ldots N_i$$
$$\theta = T_i + (k-1)\Delta\theta_i \qquad k = 1, \ldots M_i$$

where S_i = XSA(i)
ΔR_i = DXA(i)
N_i = NXA(i)

T_i = YSA(i)
$\Delta\theta_i$ = DYA(i)
M_i = NYA(i)

XSA and DXA are in units of wavelength. YSA and DYA are in units of radians. The upper limit of grid 1 (XSA(2) = XSA(3)) and the upper limit of grid 2 (YSA(3)) may be changed and the densities of points may be changed. Boundaries that are zero should not be changed without modifying subroutine INTRP in NEC. The three grids must cover the region $0 \leq R_1/\lambda \leq 1$ and $0 \leq \theta \leq \pi/2$.

3. ARRAY DIMENSION LIMITATIONS

Number of Points in Interpolation Grids

Arrays:

COMMON/GGRID/AR1 (N_1, M_1, 4), AR2 (N_2, M_2, 4), AR3 (N_3, M_3, 4)

where $N_i \geq$ NXA(i) and $M_i \geq$ NYA(i)

The dimensions in common /GGRID/ in SOMNEC must be the same as the dimension of /GGRID/ in NEC.

Maximum Number of Iterations in GSHANK

Arrays:

Subroutine GSHANK: Q1 (6, MAXH), Q2 (6, MAXH)

where MAXH = maximum value of INT in GSHANK set at GS 13.

4. SOMNEC SUBROUTINE LINKAGE

Figure 17 shows the organization of subroutines in SOMNEC.

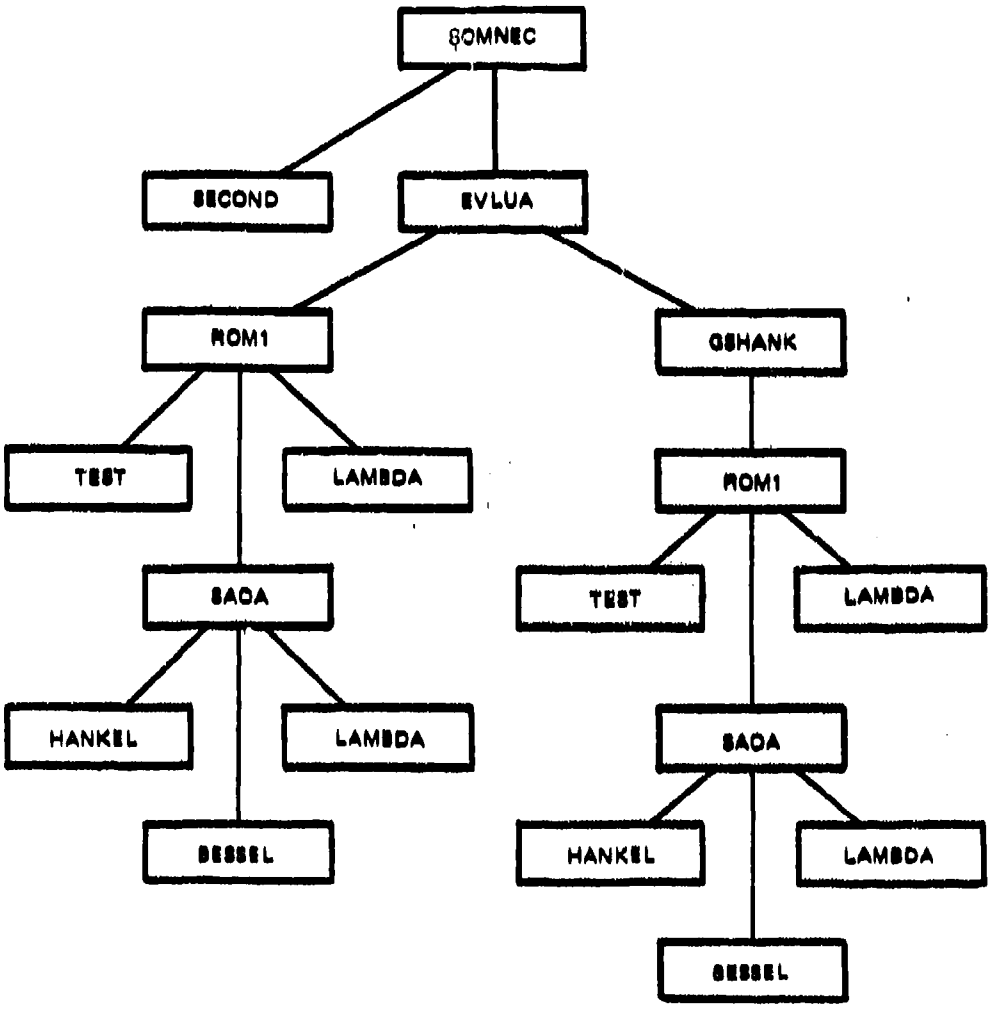


Figure 17. SOMNEC Subroutine Linkage Chart.

References

1. Ralston, A., A First Course in Numerical Analysis, McGraw-Hill, New York, 1965.

2. Norton, K. A., "The Propagation of Radio Waves Over the Surface of the Earth and in the Upper Atmosphere," Proceedings of the Institute of Radio Engineers, Vol. 25, No. 9, Sept. 1937.

3. Miller, E. K., "A Variable Interval Width Quadrature Technique Based on Romberg's Method," Journal of Computational Physics, Vol. 5, No. 2, April 1970.

4. Miller, E. K., and G. J. Burke, "Numerical Integration Methods," IEEE Transactions, Vol. Ap-17, No. 5, Sept. 1969.

5. Handbook of Mathematical Functions, edited by M. Abramowitz, National Bureau of Standards (U.S.), Applied Mathematics Series 55, 1964.

6. Shanks, D., "Non-Linear Transformations of Divergent and Slowly Convergent Sequences," J. Math. Phys. 24, 1, 1955.


UCID-18834

NUMERICAL ELECTROMAGNETICS CODE (NEC) - METHOD OF MOMENTS

PART III: USER'S GUIDE

G. J. Burke
A. J. Poggio

January 1981

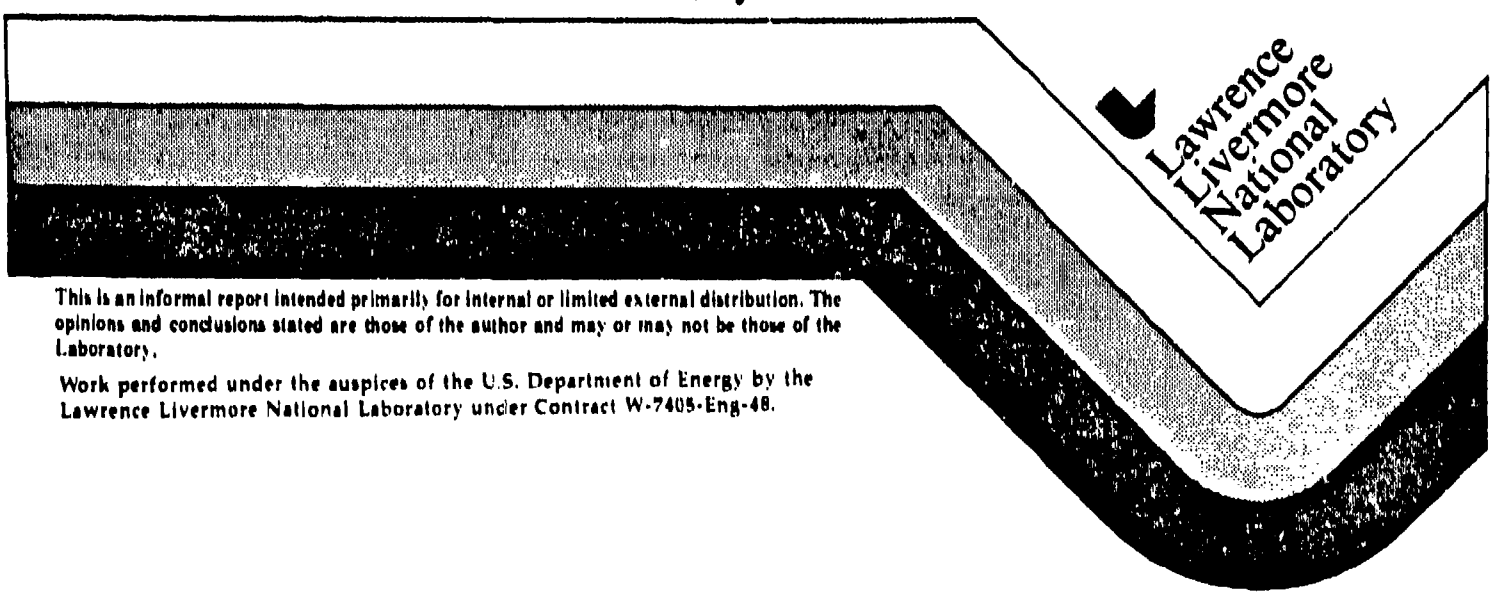

This is an informal report intended primarily for internal or limited external distribution. The opinions and conclusions stated are those of the author and may or may not be those of the Laboratory.

Work performed under the auspices of the U.S. Department of Energy by the Lawrence Livermore National Laboratory under Contract W-7405-Eng-48.

Preface

The Numerical Electromagnetics Code (NEC) has been developed at the Lawrence Livermore Laboratory, Livermore, California, under the sponsorship of the Naval Ocean Systems Center and the Air Force Weapons Laboratory. It is an advanced version of the Antenna Modeling Program (AMP) developed in the early 1970's by MBAssociates for the Naval Research Laboratory, Naval Ship Engineering Center, U.S. Army ECOM/Communications Systems, U.S. Army Strategic Communications Command, and Rome Air Development Center under Office of Naval Research Contract N00014-71-C-0187. The present version of NEC is the result of efforts by G. J. Burke and A. J. Poggio of Lawrence Livermore Laboratory.

The documentation for NEC consists of three volumes:

Part I: NEC Program Description — Theory

Part II: NEC Program Description — Code

Part III: NEC User's Guide

The documentation has been prepared by using the AMP documents as foundations and by modifying those as needed. In some cases this led to minor changes in the original documents while in many cases major modifications were required.

Over the years many individuals have been contributors to AMP and NEC and are acknowledged here as follows:

R. W. Adams	R. J. Lytle
J. N. Brittingham	E. K. Miller
G. J. Burke	J. B. Morton
F. J. Deadrick	G. M. Pjerrou
K. K. Hazard	A. J. Poggio
D. L. Knepp	E. S. Selden
D. L. Lager	

The support for the development of NEC-2 at the Lawrence Livermore Laboratory has been provided by the Naval Ocean Systems Center under MIPR-N0095376MP. Cognizant individuals under whom this project was carried out include: J. Rockway and J. Logan. Previous development of NEC also included the support of the Air Force Weapons Laboratory (Project Order 76-090) and was monitored by J. Castillo and TSgt. H. Goodwin.

Work was performed under the auspices of the U.S. Department of Energy under contract No. W-7405-Eng-48. Reference to a company or product name does not imply approval or recommendation of the product by the University

of California or the U.S. Department of Energy to the exclusion of others that may be suitable.

Contents

Section		Page
	LIST OF ILLUSTRATIONS	v
I.	INTRODUCTION	1
II.	STRUCTURE MODELING GUIDELINES	3
	1. Wire Modeling	3
	2. Surface Modeling	6
	3. Modeling Structures Over Ground	11
III.	PROGRAM INPUT	14
	1. Comment Cards	15
	2. Structure Geometry Input	16
	Wire Arc Specification (GA)	18
	End Geometry Input (GE)	19
	Read NGF File (GF)	21
	Coordinate Transformation (GM)	22
	Generate Cylindrical Structure (GR)	24
	Scale Structure Dimensions (GS)	27
	Wire Specification (GW)	28
	Reflection in Coordinate Planes (GX)	31
	Surface Patch (SP)	34
	Multiple Patch Surface (SM)	38
	Examples of Structure Geometry Data	40
	3. Program Control Cards	47
	Maximum Coupling Calculation (CP)	50
	Extended Thin-Wire Kernel (EK)	51
	End of Run (EN)	52
	Excitation (EX)	53
	Frequency (FR)	58
	Additional Ground Parameters (GD)	60
	Ground Parameters (GN)	62
	Interaction Approximation Range (KH)	65
	Loading (LD)	66
	Near Fields (NE, NH)	69
	Networks (NT)	72
	Next Structure (NX)	75
	Print Control for Charge on Wires (PQ)	76

Section		Page
	Print Control for Current on Wires (PT)	77
	Radiation Pattern (RP)	79
	Transmission Line (TL)	84
	Write NGF File (WG)	86
	Execute (XQ)	87
	4. SOMNEC Input for Sommerfeld/Norton Ground Method	89
	5. The Numerical Green's Function Option	89
IV.	NEC OUTPUT	93
	Examples 1 through 4	95
	Example 5, Log-Periodic Antenna	115
	Example 6, Cylinder with Attached Wires	123
	Examples 7 and 8, Scattering by a Wire and Aircraft	133
	Example 9, Scattering by a Sphere	143
	Example 10, Monopole on Radial Wire Ground Screen	153
V.	EXECUTION TIME	165
VI.	DIFFERENCES BETWEEN NEC-2, NEC-1, AND AMP2	167
VII.	FILE STORAGE REQUIREMENTS	169
VIII.	ERROR MESSAGES	172
	REFERENCES	179

List of Illustrations

Figure		Page
1.	Patch Position and Orientation	7
2.	Connection of a Wire to a Surface Patch	8
3.	Patch Models for a Sphere	9
4.	Bistatic RCS of a Sphere with ka = 5.3	10
5.	Surface Patch Options	36
6.	Rectangular Surface Covered by Multiple Patches	39
7.	Rhombic Antenna — No Symmetry	40
8.	Rhombic Antenna — 2 Planes of Symmetry	41
9.	Rhombic Antenna — 1 Plane of Symmetry	42
10.	Coaxial Rings	42
11.	Wire Grid Plate and Dipole	43
12.	Development of Surface Model for Cylinder with Attached Wires	45
13.	Segmentation of Cylinder for Wires Connected to End and Side	46
14.	Specification of Incident Wave	55
15.	Orientation of Current Element	56
16.	Parameters for a Second Ground Medium	60
17.	Segment Loaded by Means of a 2-Port Network	74
18.	Coordinates for Radiated Field	80
19.	Stick Model of Aircraft	133

Abstract

The Numerical Electromagnetics Code (NEC-2) is a computer code for analyzing the electromagnetic response of an arbitrary structure consisting of wires and surfaces in free space or over a ground plane. The analysis is accomplished by the numerical solution of integral equations for induced currents. The excitation may be an incident plane wave or a voltage source on a wire, while the output may include current and charge density, electric or magnetic field in the vicinity of the structure, and radiated fields. NEC-2 includes several features not contained in NEC-1, including an accurate method for modeling grounds, based on the Sommerfeld integrals, and an option to modify a structure without repeating the complete solution.

This manual contains instruction for use of the Code, including preparation of input data and interpretation of the output. Examples are included that show typical input and output and illustrate many of the special options available in NEC-2. The examples exercise most parts of the Code and, hence, may also be used to check that the Code is operating correctly. Two other manuals for NEC-2, covering the equations and details of the coding, are referenced.

Section I
Introduction

The Numerical Electromagnetics Code (NEC-2) is a user-oriented computer code for analysis of the electromagnetic response of antennas and other metal structures. It is built around the numerical solution of integral equations for the currents induced on the structure by sources or incident fields. This approach avoids many of the simplifying assumptions required by other solution methods and provides a highly accurate and versatile tool for electromagnetic analysis.

The code combines an integral equation for smooth surfaces with one specialized to wires to provide for convenient and accurate modeling of a wide range of structures. A model may include nonradiating networks and transmission lines connecting parts of the structure, perfect or imperfect conductors, and lumped element loading. A structure may also be modeled over a ground plane that may be either a perfect or imperfect conductor.

The excitation may be either voltage sources on the structure or an incident plane wave of linear or elliptic polarization. The output may include induced currents and charges, near electric or magnetic fields, and radiated fields. Hence, the program is suited to either antenna analysis or scattering and EMP studies.

The integral equation approach is best suited to structures with dimensions up to several wavelengths. Although there is no theoretical size limit, the numerical solution requires a matrix equation of increasing order as the structure size is increased relative to wavelength. Hence, modeling very large structures may require more computer time and file storage than is practical on a particular machine. In such cases standard high-frequency approximations such as geometrical optics, physical optics, or geometrical theory of defraction may be more suitable than the integral equation approach used in NEC-2.

NEC-2 retains all features of the earlier version NEC-1 except for a restart option. Major additions in NEC-2 are the Numerical Green's Function for partitioned-matrix solution and a treatment for lossy grounds that is accurate for antennas very close to the ground surface. NEC-2 also includes an option to compute maximum coupling between antennas and new options for structure input.

This manual contains instructions for use of the NEC-2 code and sample runs to illustrate the output. The sample runs may also be used as a standard to check the operation of a newly duplicated or modified deck. There are two other manuals for NEC-2: Part I: NEC Program Description — Theory (ref. 1); and Part II: NEC Program Description — Code (ref. 2). Part I covers the equations and numerical methods, and Part II is a detailed description of the Fortran code.

Section II
Structure Modeling Guidelines

The basic devices for modeling structures with the NEC code are short, straight segments for modeling wires and flat patches for modeling surfaces. An antenna and any other conducting objects in its vicinity that affect its performance must be modeled with strings of segments following the paths of wires and with patches covering surfaces. Propar choice of the segments and patches for a model is the most critical step to obtaining accurate results. The number of segments and patches should be the minimum required for accuracy, however, since the program running time increases rapidly as this number increases. Guidelines for choosing segments and patches are given below and should be followed carefully by anyone using the NEC code. Experience gained by using the code will also aid the user in developing models.

1. WIRE MODELING

A wire segment is defined by the coordinates of its two end points and its radius. Modeling a wire structure with segments involves both geometrical and electrical factors. Geometrically, the segments should follow the paths of conductors as closely as possible, using a piece-wise linear fit on curves.

The main electrical consideration is segment length Δ relative to the wavelength λ. Generally, Δ should be less than about 0.1 λ at the desired frequency. Somewhat longer segments may be acceptable on long wires with no abrupt changes while shorter segments, 0.05 λ or less, may be needed in modeling critical regions of an antenna. The size of the segments determines the resolution in solving for the current on the model since the current is computed at the center of each segment. Extremely short segments, less than about 10^{-3} λ, should also be avoided since the similarity of the constant and cosine components of the current expansion leads to numerical inaccuracy.

The wire radius, a, relative to λ is limited by the approximations used in the kernel of the electric field integral equation. Two approximation options are available in NEC: the thin-wire kernel and the extended thin-wire kernel. These are discussed in reference 1. In the thin-wire kernel, the current on the surface of a segment is reduced to a filament of current on the segment axis. In the extended thin-wire kernel, a current uniformly distributed around the segment surface is assumed. The field of this current is approximated by the first two terms in a series expansion of the exact field

in powers of a^2. The first term in the series, which is independent of a, is identical to the thin-wire kernel while the second term extends the accuracy for larger values of a. Higher order approximations are not used because they would require excessive computation time.

In either of these approximations, only currents in the axial direction on a segment are considered, and there is no allowance for variation of the current around the wire circumference. The acceptability of these approximations depends on both the value of a/λ and the tendency of the excitation to produce circumferential current or current variation. Unless $2\pi a/\lambda$ is much less than 1, the validity of these approximations should be considered.

The accuracy of the numerical solution for the dominant axial current is also dependent on Δ/a. Small values of Δ/a may result in extraneous oscillations in the computed current near free wire ends, voltage sources, or lumped loads. Use of the extended thin-wire kernel will extend the limit on Δ/a to smaller values than are permissible with the normal thin-wire kernel. Studies of the computed field on a segment due to its own current have shown that with the thin-wire kernel, Δ/a must be greater than about 8 for errors of less than 1%. With the extended thin-wire kernel, Δ/a may be as small as 2 for the same accuracy (ref. 3). In the current solution with either of these kernels, the error tends to be less than for a single field evaluation. Reasonable current solutions have been obtained with the thin-wire kernel for Δ/a down to about 2 and with the extended thin-wire kernel for Δ/a down to 0.5. When a model includes segments with Δ/a less than about 2, the extended thin-wire kernel option should be used by inclusion of an EK card in the data deck.

When the extended thin-wire kernel option is selected, it is used at free wire ends and between parallel, connected segments. The normal thin-wire kernel is always used at bends in wires, however. Hence, segments with small Δ/a should be avoided at bends. Use of a small Δ/a at a bend, which results in the center of one segment falling within the radius of the other segment, generally leads to severe errors.

The current expansion used in NEC enforces conditions on the current and charge density along wires, at junctions, and at wire ends. For these conditions to be applied properly, segments that are electrically connected must have coincident end points. If segments intersect other than at their ends, the NEC code will not allow current to flow from one segment to the other. Segments will be treated as connected if the separation of their ends is less

than about 10^{-3} times the length of the shortest segment. When possible, however, identical coordinates should be used for connected segment ends.

The angle of the intersection of wire segments in NEC is not restricted in any manner. In fact, the acute angle may be so small as to place the observation point on one wire segment within the volume of another wire segment. Numerical studies have shown that such overlapping leads to meaningless results; thus, as a minimum, one must ensure that the angle is large enough to prevent overlaps. Even with such care, the details of the current distribution near the intersection may not be reliable even though the results for the current may be accurate at distances from this region.

NEC includes a patch option for modeling surfaces using the magnetic-field integral equation. This formulation is restricted to closed surfaces with nonvanishing enclosed volume. For example, it is not theoretically applicable to a conducting plate of zero thickness and, actually, the numerical algorithm is not practical for thin bodies (such as solar panels). The latter difficulty is due to the possibility of poor conditioning of the matrix equation.

Wire-grid modeling of conducting surfaces has been used with varying success. The earliest applications to the computation of radar cross sections and radiation patterns provided reasonably accurate results. Even computations for the input impedance of antennas driven against grid models of surfaces have oftentimes exhibited good agreement with experiments. However, broad and generalized guidelines for near-field quantities have not been developed, and the use of wire-grid modeling for near-field parameters should be approached with caution. A single wire grid, however, may represent both surfaces of a thin conducting plate. The current on the grid will be the sum of the currents that would flow on opposite sides of the plate. While information on the currents on the individual surfaces is lost, the grid will yield the correct radiated fields.

Other rules for the segment model follow:

- Segments (or patches) may not overlap since the division of current between two overlapping segments is indeterminate. Overlapping segments may result in a singular matrix equation.
- A large radius change between connected segments may decrease accuracy; particularly, with small Δ/a. The problem may be reduced by making the radius change in steps over several segments.

- A segment is required at each point where a network connection or voltage source will be located. This may seem contrary to the idea of an excitation gap as a break in a wire. A continuous wire across the gap is needed, however, so that the required voltage drop can be specified as a boundary condition.
- The two segments on each side of a charge density discontinuity voltage source should be parallel and have the same length and radius. When this source is at the base of a segment connected to a ground plane, the segment should be vertical.
- The number of wires joined at a single junction cannot exceed 30 because of a dimension limitation in the code.
- When wires are parallel and very close together, the segments should be aligned to avoid incorrect current perturbations from offset match points and segment junctions.
- Although extensive tests have not been conducted, it is safe to specify that wires should be several radii apart.

2. SURFACE MODELING

A conducting surface is modeled by means of multiple, small flat surface patches corresponding to the segments used to model wires. The patches are chosen to cover completely the surface to be modeled, conforming as closely as possible to curved surfaces. The parameters defining a surface patch are the Cartesian coordinates of the patch center, the components of the outward-directed, unit normal vector and the patch area. These are illustrated in figure 1 where $\bar{r}_o = x_o \hat{x} + y_o \hat{y} + z_o \hat{z}$ is the position of the segment center; $\hat{n} = n_x \hat{x} + n_y \hat{y} + n_z \hat{z}$ is the unit normal vector and A is the patch area. Although the shape (square, rectangular, etc.) may be used to define a patch on input it does not affect the solution since there is no integration over the patch unless a wire is connected to the patch center. The program computes the surface current on each patch along the orthogonal unit vectors $\hat{t}_1$ and $\hat{t}_2$,

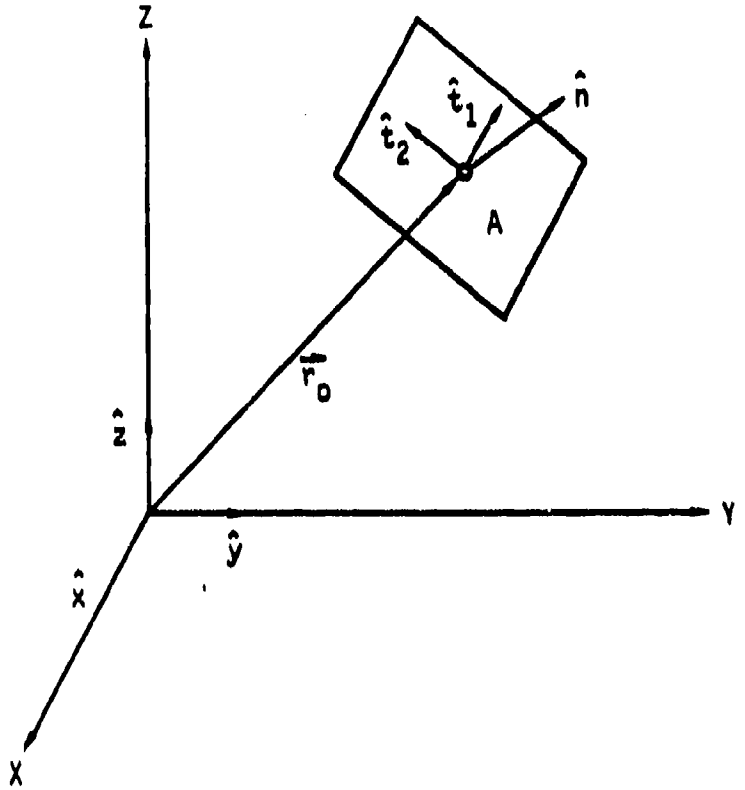


Figure 1. Patch Position and Orientation.

which are tangent to the surface. The vector $\hat{t}_1$ is parallel to a side of the triangular, rectangular, or quadrilateral patch. For a patch of arbitrary shape, it is chosen by the following rules:

For a horizontal patch,

$$\hat{t}_1 = \hat{x} .$$

For a nonhorizontal patch,

$$\hat{t}_1 = (\hat{z} \times \hat{n})/|\hat{z} \times \hat{n}| ,$$

$\hat{t}_2$ is then chosen as $\hat{t}_2 = \hat{n} \times \hat{t}_1$. When a structure having plane symmetry is formed by reflection in a coordinate plane using a GX input card, the vectors $\hat{t}_1$, $\hat{t}_2$ and $\hat{n}$ are also reflected so that the new patches will have $\hat{t}_2 = -\hat{n} \times \hat{t}_1$.

When a wire is connected to a surface, the wire must end at the center of a patch with identical coordinates used for the wire end and the patch center. The program then divides the patch into four equal patches about the wire end as shown in figure 2, where a wire has been connected to the

second of three previously identical patches. The connection patch is divided along lines defined by the vectors $\hat{t}_1$ and $\hat{t}_2$ for that patch, with a square patch assumed. The four new patches are ordinary patches like those input by the user, except when the interactions between these patches and the lowest segment on the connected wire are computed. In this case an interpolation function is applied to the four patches to represent the current from the wire onto the surface, and the function is numerically integrated over the patches. Thus, the shape of the patch is significant in this case. The user should try to choose patches so that those with wires connected are approximately square with sides parallel to $\hat{t}_1$ and $\hat{t}_2$. The connected wire is not required to be normal to the patch but cannot lie in the plane of the patch. Only a single wire may connect to a given patch and a segment may have a patch connection on only one of its ends. Also, a wire may never connect to a patch formed by subdividing another patch for a previous connection.

As with wire modeling, patch size measured in wavelengths is very important for accuracy of the results. A minimum of about 25 patches should be used per square wavelength of surface area, with the maximum size for an individual patch about 0.04 square wavelengths. Large patches may be used on large smooth surfaces while smaller patches are needed in areas of small radius of curvature, both for geometrical modeling accuracy and for accuracy of the integral equation solution. In the case of an edge, a precise local representation cannot be included; however, smaller patches in the vicinity of


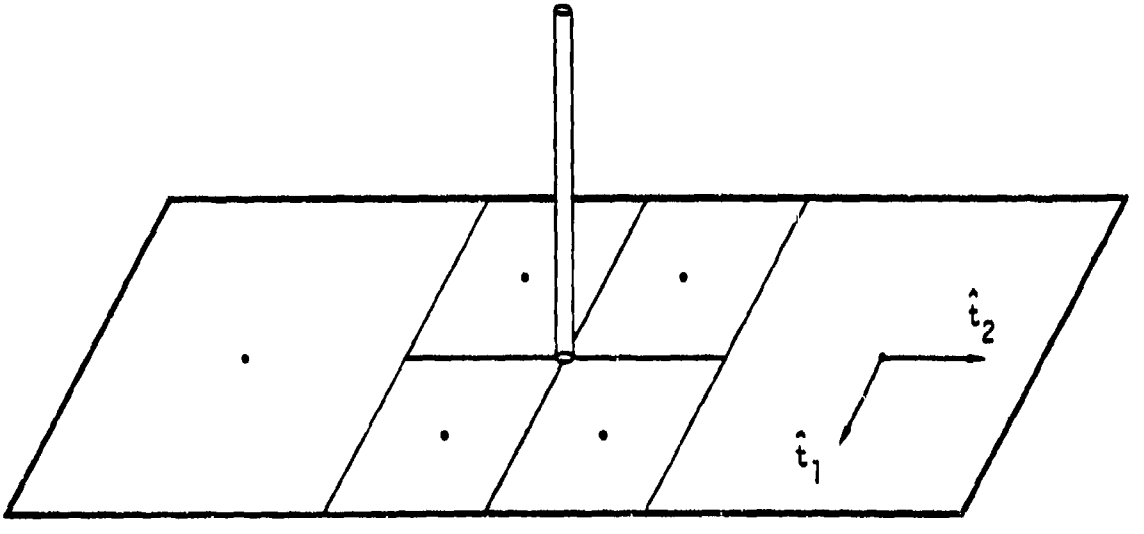


Figure 2. Connection of a Wire to a Surface Patch.

the edge can lead to more accurate results since the current magnitude may vary rapidly in this region. Since connection of a wire to a patch causes the patch to be divided into four smaller patches, a larger patch may be input in anticipation of the subdivision.


While patch shape is not input to the program, very long narrow patches should be avoided when subdividing the surface. This is illustrated by the two methods of modeling a sphere shown in figure 3. The first uses uniform divisions in azimuth and equal cuts along the vertical axis. This results in all patches having equal areas but with long narrow patches near the poles. In the second method, the number of divisions in azimuth is increased toward the equator so that the patch length and width are kept more nearly equal. The areas are again kept approximately equal. The results of the two segmentations are shown in figure 4 for scattering by a sphere of ka (2π • radius/wavelength) equal to 5.3. The uniform segmentation used 14 increments in azimuth and 14 equal bands along the vertical axis. The variable segmentation used 13 equal increments in arc length along the vertical axis, with each band from top to bottom divided into the following number of patches in azimuth: 4, 8, 12, 16, 20, 24, 24, 24, 20, 16, 12, 8, 4. Much better agreement with experiment is obtained with the variable segmentation.

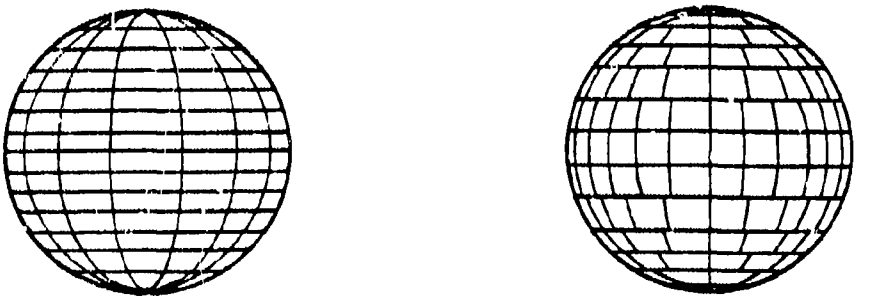In general, the use of surface patches is restricted to modeling voluminous bodies. The surface modeled must be closed since the patches only model the side of the surface from which their normals are directed outward. If a somewhat thin body, such as a box with one narrow dimension, is modeled with patches the narrow sides (edges) must be modeled as well as the broad




Uniform Segmentation Variable Segmentation

Figure 3. Patch Models for a Sphere.

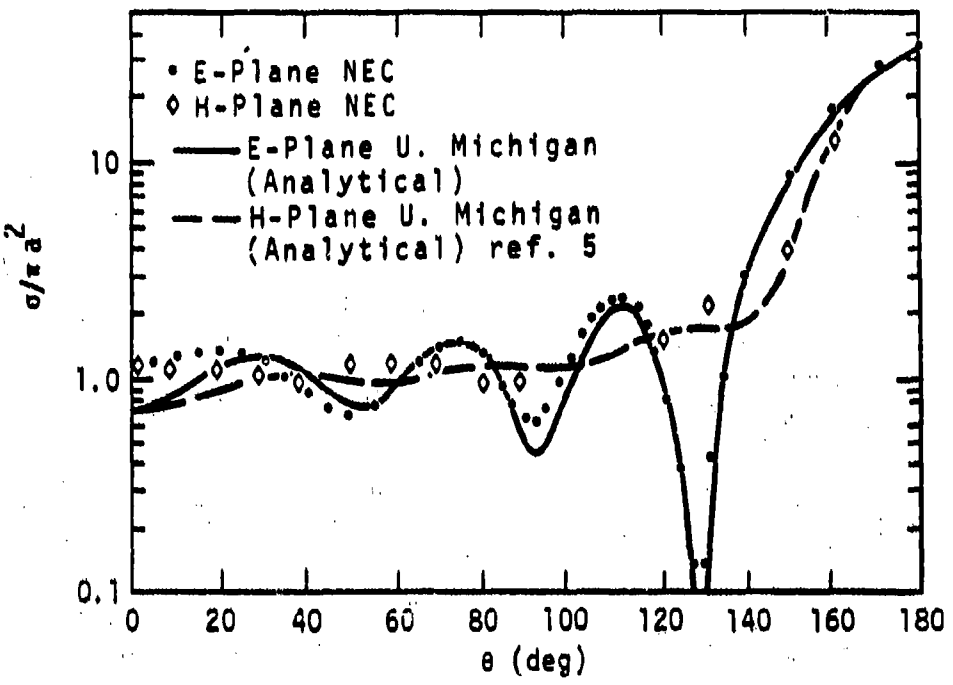

(a) Uniform Segmentation

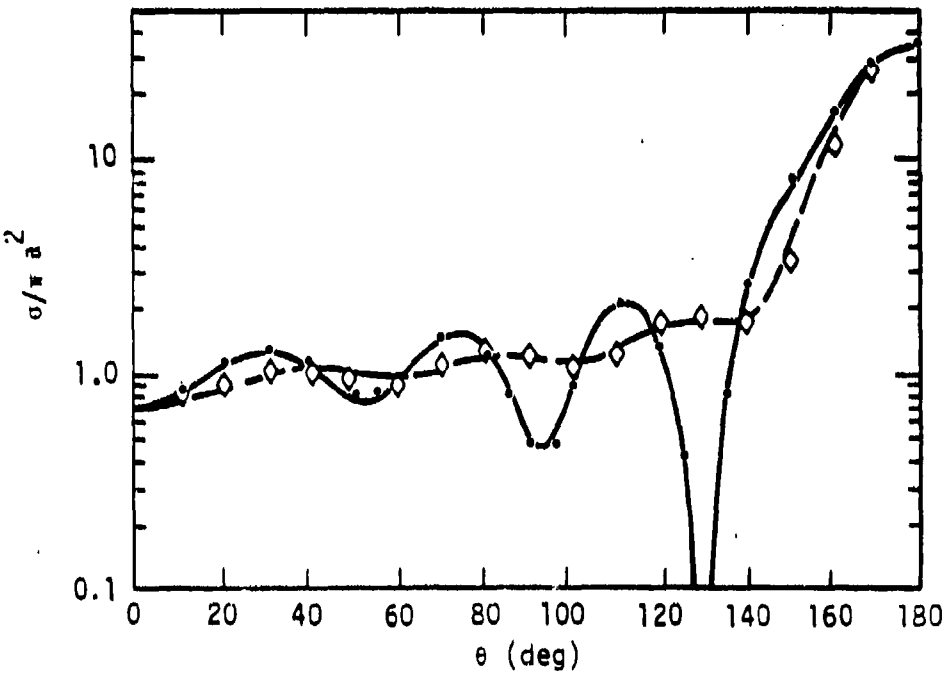

(b) Variable ϕ Segmentation

Figure 4. Bistatic RCS of a Sphere with ka = 5.3.

surfaces. Furthermore, the parallel surfaces on opposite sides cannot be too close together or severe numerical error will occur.

When modeling complex structures with features not previously encountered, accuracy may be checked by comparison with reliable experimental data if available. Alternatively, it may be possible to develop an idealized model for which the correct results can be estimated while retaining the critical features of the desired model. The optimum model for a class of structures can be estimated by varying the segment and patch density and observing the effect on the results. Some dependence of results on segmentation will always be found. A large dependence, however, would indicate that the solution has not converged and more segments or patches should be used. A model will generally be useable over a band of frequencies. For frequencies beyond the upper limit of a particular modal, a new set of geometry cards must be input with a finer segmentation.

3. MODELING STRUCTURES OVER GROUND

Several options are available in NEC for modeling an antenna over a ground plane. For a perfectly conducting ground, the code generates an image of the structure reflected in the ground surface. The image is exactly equivalent to a perfectly conducting ground and results in solution accuracy comparable to that for a free-space model. Structures may be close to the ground or contacting it in this case. However, for a horizontal wire with radius a, and height h, to the wire axis, $[h^2 + a^2]^{1/2}$ should be greater than about 10^{-6} wavelengths. Furthermore, the height should be at least several times the radius for the thin-wire approximation to be valid. This method doubles the time to fill the interaction matrix.

A finitely conducting ground may be modeled by an image modified by the Fresnel plane-wave reflection coefficients. This method is fast but of limited accuracy and should not be used for structures close to the ground. The reflection coefficient approximation for the near fields can yield reasonable accuracy if the structure is at least several tenths of a wavelength above the ground. It should not be used for structures having a large horizontal extent over the ground such as some traveling-wave antennas.

An alternate method (Sommerfeld/Norton), available for wires only, uses the exact solution for the fields in the presence of ground and is accurate close to the ground. For a horizontal wire the height restriction is the same as for a perfect ground. When this method is used NEC requires an input file

(TAPE21) containing field values for the specific ground parameters and frequency. This interpolation table must be generated by running a separate program, SOMNEC, prior to the NEC run. The present NEC code uses the Sommerfeld/Norton method only for wire-to-wire interactions. If Sommerfeld/Norton is requested for a structure that includes surfaces, the reflection coefficient approximation will be used for surface-to-surface and surface-to-wire interactions. Computation of wire-to-wire interactions by the Sommerfeld/Norton method takes about four times longer than for free space. In addition, computation of the interpolation table requires about 15 s on a CDC 7600 computer. However, the file of interpolation tables may be saved and reused for problems having the same ground parameters and frequency. The Sommerfeld/Norton method is not available in the earlier code NEC-1.

A wire ground screen may be modeled with the Sommerfeld/Norton method if it is raised slightly above the ground surface. A ground stake cannot be modeled in NEC since there is presently no provision to compute interactions across the interface. Wires may end on a ground plane with a condition that the charge density (i.e., derivative of current) be zero at the base of the wire, but this is accurate only for a perfectly conducting ground. A wire may end on a finitely conducting ground with the charge set to zero at the connection, but this will not accurately model a ground stake. If a wire is driven against a finitely conducting ground in this way, the input impedance will typically be dependent on length of the source segment.

NEC also includes options for a radial-wire ground-screen approximation and two-medium ground approximation (cliff) based on modified reflection coefficients. These methods are implemented only for wires and not for patches, however, For the radial-wire ground-screen approximation, an approximate surface impedance — based on the wire density and the ground parameters — is computed at specular reflection points. Since the formula for surface impedance yields zero at the center of the screen, the current on a vertical monopole will be the same as over a perfect ground. The ground screen approximation is used in computing both near-field interactions and the radiated field. It should be noted that defraction from the edge of the screen is not included. When limited accuracy can be accepted, the ground screen approximation provides a large time saving over explicit modeling with the Sommerfeld/Norton method since the ground screen does not increase the number of unknowns in the matrix equation.

The two-medium ground approximation permits the user to define a linear or circular cliff with different ground parameters and ground height on opposite sides. This approximation is not used for the near-field interactions affecting the currents but is used in computing the radiated field. The reflection coefficient is based on the ground parameters and height at the specular-reflection point for each ray. This option may also be used to compute the current over a perfect ground and then compute radiated fields for a finitely conducting ground.

Section III
Program Input


Data to describe an antenna and its environment and to request computation of antenna characteristics are input by means of punched cards. The data-card set for a single run consists of three types of data cards. The deck begins with one or more cards containing a description of the run which is printed at the start of the output as a label. These are followed by geometry data cards which specify the geometry of the antenna. Finally, a section of program control cards specifies electrical parameters such as frequency, loading and excitation, and requests calculation of antenna currents and fields.


Every data card has a two-letter alphabetic code in columns one and two to identify the card to the program. All cards having numeric data are punched in a similar format, with integer numbers first followed by real numbers. On antenna geometry data cards, there are two fields for integer numbers (columns 3 through 5 and 6 through 10) followed by real-number fields of ten columns each to the end of the card. The program control cards, following the geometry data, have four integer fields (3 through 5, 6 through 10, 11 through 15, and 16 through 20) followed by real-number fields.

Integer numbers must be punched so that the number ends in the last column of its field. If spaces are left at the end of the field, they will be read as zeros which, in effect, multiplies the desired number by a power of ten. Real numbers are punched as a string of digits containing a decimal, and may be punched anywhere in their field. On the program control cards, following the geometry data, real numbers may also be punched as a string of digits containing a decimal followed by an exponent of ten in the form E ± I, multiplying the number by $10^{\pm I}$. The integer exponent must be between the exponent limits of the computer. When an exponent is used, the integer must end in the last column of the field. Otherwise, spaces will be read as zeros, which is the same as multiplying the exponent by a power of ten. If the field on the card is left blank, the number will be read as zero for either integer or real numbers.

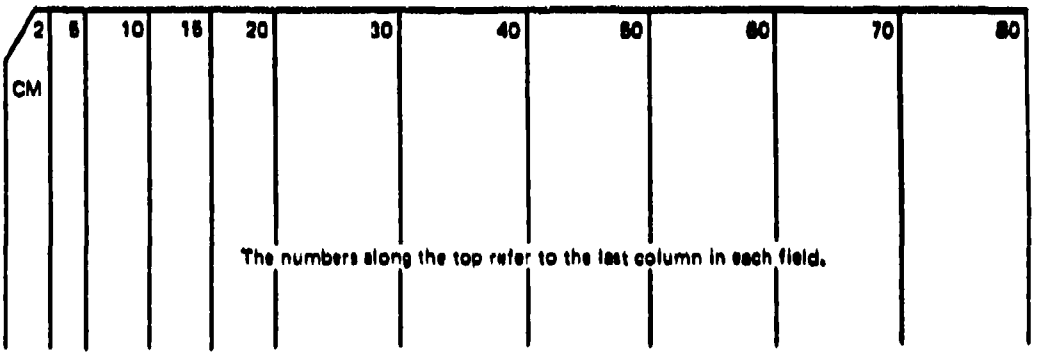1. COMMENT CARDS

The data-card deck for a run must begin with one or more comment cards which can contain a brief description and structure parameters for the run. The cards are printed at the beginning of the output of the run for identification only and have no effect on the computation. Any alphabetic and numeric characters can be punched on these cards. The comment cards, like all other data cards, have a two-letter identifier in columns 1 and 2. The two forms for comment cards are:



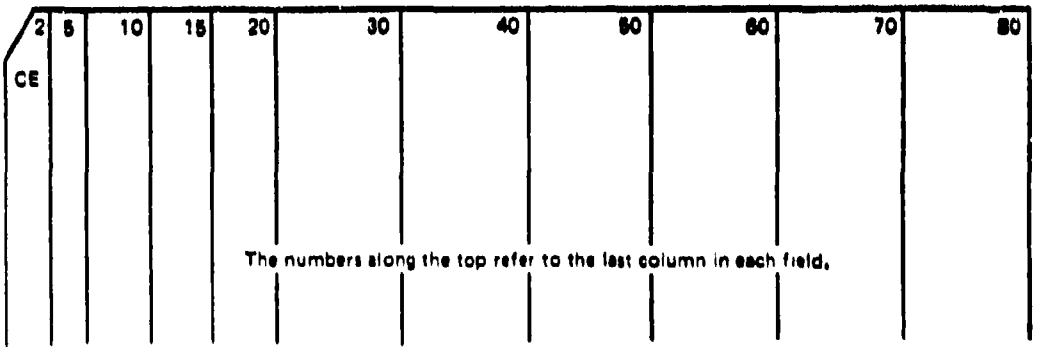

When a CM card is read, the contents of columns 3 through 80 is printed in the output, and the next card is read as a comment card. When a CE card is read, columns 3 through 80 are printed, and reading of comments is terminated. The next card must be a geometry card. Thus, a CE card must always occur in a data deck and may be preceded by as many CM cards as are needed to describe the run.

2. STRUCTURE GEOMETRY INPUT

For convenient input of structure geometry data, several data-card options are provided to generate data for groups of segments or patches. The segment data for a straight wire with an arbitrary number of segments may be generated by a single input card specifying the Cartesian coordinates of each end of the wire and the number of segments. Other input cards can cause a structure to be reflected in a coordinate plane or rotated about an axis to complete the structure.

The geometry input also permits the user to assign tag numbers to the segments for later use in referring to a segment; for example, to specify the location of a voltage source. Each segment has an absolute segment number associated with it which is determined by its location in the sequence of segments specified by the input data. This number can be used to refer to a particular segment. The absolute segment number of the segment in a given location may be difficult to determine in advance, however, when the structure is large and complex. In such cases the segment may be more easily referenced if it is assigned a tag number. The input card for wires includes a provision for specifying a tag number which is assigned to all segments of that wire. A segment can then be identified by its tag number and its number in the set of segments having that same tag number. Thus, if a wire is specified in some part of a structure with 7 segments and a tag of 3, then the center segment of the wire could be referred to as tag 3, segment 4.

The geometry data cards are:

GA — wire arc specification
GE — end geometry data
GF — use Numerical Green's Function
GM — shift and duplicate structure
GR — generate cylindrical structure (symmetry)
GS — scale structure dimensions
GW — specify wire (also GC)
GX — reflect structure (symmetry)
SP — specify surface patch (also SC)
SM — generate multiple surfaces patches (also SC)


The GE card is required to signal the end of the geometry data. The other cards may be used as needed to generate the required structure.

The format for segment geometry data cards begins with a two letter identifier in columns 1 and 2. Two fields for integer numbers follow in columns 3 through 5 and 6 through 10. These are followed by real-number fields in columns 11 through 20, 21 through 30, and continuing in fields of 10 columns to the end of the card. Not all of these number fields are used on most cards, however. In the following descriptions of cards, the integer numbers are referred to as I1 and I2, and the decimal numbers as F1, ..., F7. The Fortran variable names of the parameters on each card are also given in cases where they serve as useful mnemonics.

Wire Arc Specification (GA)

Purpose: To generate a circular arc of wire segments.

Card:

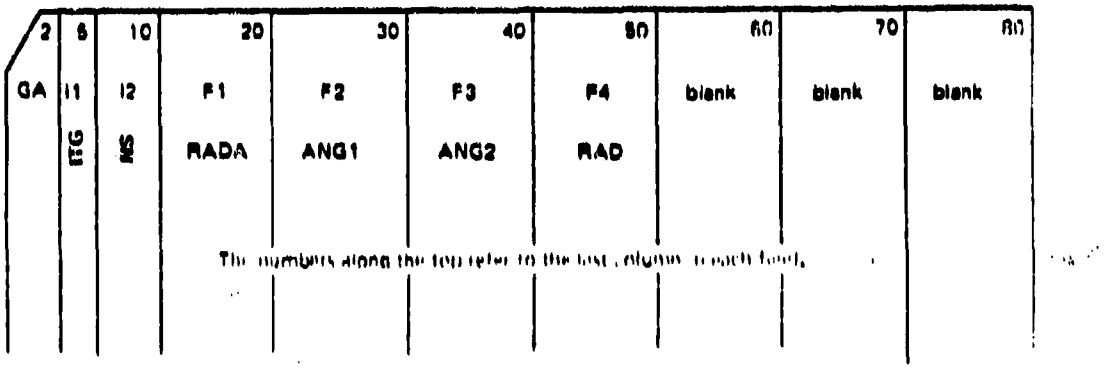

2	5	10	20	30	40	50	60	70	80
GA	I1	I2	F1	F2	F3	F4	blank	blank	blank
	ITG	NS	RADA	ANG1	ANG2	RAD			

The numbers along the top refer to the last column in each field.

Parameters:

Integers

ITG (I-1) — Tag number assigned to all segments of the wire arc.

NS (I-2) — Number of segments into which the arc will be divided.

Decimal Numbers

RADA (F1) — Arc radius (center is the origin and the axis is the y axis).

ANG1 (F2) — Angle of first end of the arc measured from the x axis in a left-hand direction about the y axis (degrees).

ANG2 (F3) — Angle of the second end of the arc.

RAD (F4) — Wire radius.


Notes:

- The segments generated by GA form a section of polygon inscribed within the arc.
- If an arc in a different position or orientation is desired the segments may be moved with a GM card.
- Use of GA to form a circle will not result in symmetry being used in the calculation. It is a good way to form the beginning of the circle, to be completed by GR, however.
- (See notes for GW)

End Geometry Input (GE)

Purpose: To terminate reading of geometry data cards and reset geometry data if a ground plane is used.

Card:

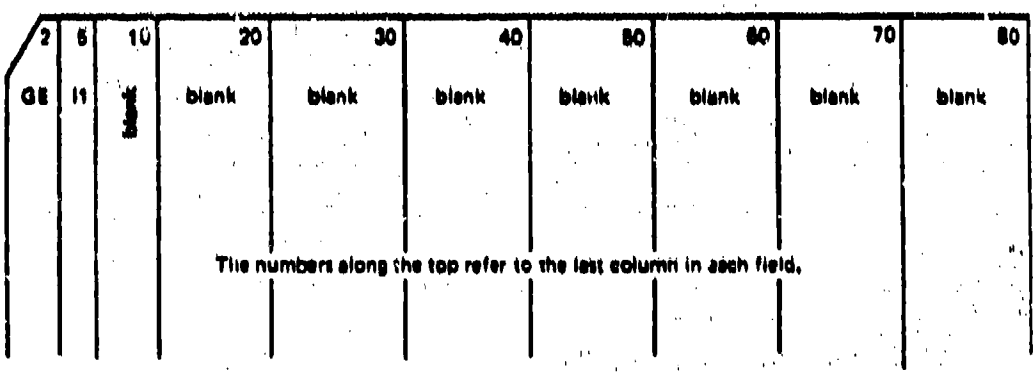

Parameters:

Integers

(I1) — Geometry ground plane flag. The values are:

0 — no ground plane is present.

1 — indicates a ground plane is present. Structure symmetry is modified as required, and the current expansion is modified so that the currents on segments touching the ground (X, Y plane) are interpolated to their images below the ground (charge at base is zero).

-1 — indicates a ground is present. Structure symmetry is modified as required. Current expansion, however, is not modified, Thus, currents on segments touching the ground will go to zero at the ground.

Decimal Numbers

The decimal number fields are not used.

Notes:

- The basic function of the GE card is to terminate reading of geometry data cards. In doing this, it causes the program to search through the segment data that have been generated by the preceding cards to determine which wires are connected for current expansion.
- At the time that the GE card is read, the structure dimensions must be in units of meters.

- A positive or negative value of I1 does not cause a ground to be included in the calculation. It only modifies the geometry data as required when a ground is present. The ground parameters must be specified on a program control card following the geometry cards.

- When I1 is nonzero, no segment may extend below the ground plane (X,Y plane) or lie in this plane. Segments may end on the ground plane, however.


- If the height of a horizontal wire is less than 10^{-3} times the segment length, I1 equal to 1 will connect the end of every segment in the wire to ground. I1 should then be -1 to avoid this disaster.

- As an example of how the symmetry of a structure is affected by the presence of a ground plane (X, Y plane), consider a structure generated with cylindrical symmetry about the Z axis. The presence of a ground does not affect the cylindrical symmetry. If however this same structure is rotated off the vertical, the cylindrical symmetry is lost in the presence of the ground. As a second example, consider a dipole parallel to Z axis which was generated with symmetry about its feed. The presence of a ground plane destroys this symmetry. The program modifies structure symmetries as follows when I1 is nonzero. If the structure was rotated about the X or Y axis by the GM card, all symmetry is lost (i.e., the no-symmetry condition is set). If the structure was not rotated about the X or Y axis, only symmetry about a plane parallel to the X, Y plane is lost. Translation of a structure does not affect symmetries.

Read NGF File (GF)

Purpose: To read a previously written NGF file.

Card:

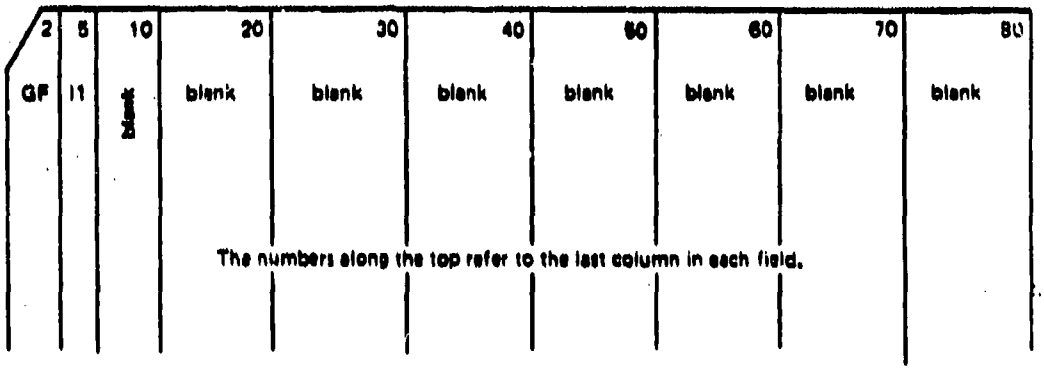

Parameters:

Integers

(I1) – Print a table of the coordinates of the ends of all segments in the NGF if I1 ≠ 0. Normal printing otherwise.


Notes:

- GF must be the first card in the structure geometry section, immediately after CE.
- The effects of some other data cards are altered when a GF card is used. See section III-5.

Coordinate Transformation (GM)

Purpose: To translate or rotate a structure with respect to the coordinate system or to generate new structures translated or rotated from the original.

Card:

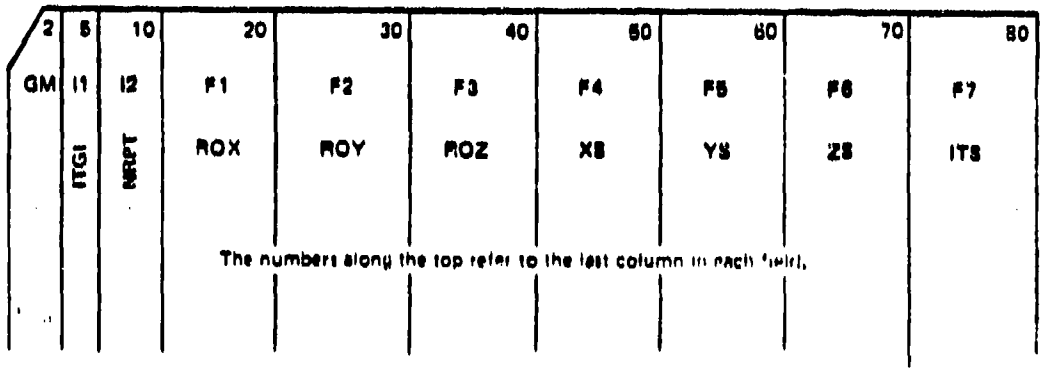

Parameters:

Integers

ITGI (I1) – Tag number increment.

NRPT (I2) – The number of new structures to be generated.

Decimal Numbers

ROX (F1) – Angle in degrees through which the structure is rotated about the X-axis. A positive angle causes a right-hand rotation.

ROY (F2) – Angle of rotation about Y-axis.

ROZ (F3) – Angle of rotation about Z-axis.

XS (F4) – X, Y, Z components of vector by which

YS (F5) – structure is translated with respect to

ZS (F6) – the coordinate system.

ITS (F7) – This number is input as a decimal number but is rounded to an integer before use. Tag numbers are searched sequentially until a segment having a tag of ITS is found. The part of the structure composed of this segment through the end of the sequence of segments is moved by the card. If ITS is blank (usual case) or zero the entire structure is moved.

Notes:

- If NRPT is zero, the structure is moved by the specified rotation and translation leaving nothing in the original location. If NRPT is greater than zero, the original structure remains fixed and NRPT new structures are formed, each shifted from the previous one by the requested transformation.

- The tag increment, ITGI, is used when new structures are generated (NRPT greater than zero) to avoid duplication of tag numbers. Tag numbers of the segments in each new copy of the structure are incremented by ITGI from the tags on the previous copy or original. Tags of segments which are generated from segments having no tags (tag equal to zero) are not incremented. Generally, ITGI will be greater than or equal to the largest tag number used on the original structure to avoid duplication of tags. For example, if tag numbers 1 through 100 have been used before a (GM) card is read having NRPT equal to 2, then ITGI equal to 100 will cause the first copy of the structure to have tags from 101 to 200 and the second copy from 201 to 300. If NRPT is zero, the tags on the original structure will be incremented.

- The result of a transformation depends on the order in which the rotations and translation are applied. The order used is first rotation about X-axis, then rotation about the Y-axis, then rotation about the Z-axis and, finally, translation by (XS, YS, ZS). All operations refer to the fixed coordinate system axes. If a different order is desired, separate GM cards may be used.

Generate Cylindrical Structure (GR)

Purpose: To reproduce a structure while rotating about the Z-axis to form a complete cylindrical array and to set flags so that symmetry is utilized in the solution.

Card:

2	5	10	20	30	40	50	60	70	80
GR	I1	I2	blank	blank	blank	blank	blank	blank	blank

The numbers along the top refer to the last column in each field.

Parameters:

Integers

(I1) – Tag number increment.

(I2) – Total number of times that the structure is to occur in the cylindrical array.

Decimal Numbers

The decimal number fields are not used.

Notes:

- The tag increment (I1) is used to avoid duplication of tag numbers in the reproduced structures. In forming a new structure for the array, all valid tags on the previous copy or original structure are incremented by (I1). Tags equal to zero are not incremented.
- The GR card should never be used when there are segments on the Z-axis or crossing the Z-axis since overlapping segments would result.
- The GR card sets flags so the program makes use of cylindrical symmetry in solving for the currents. If a structure modeled by N segments has M sections in cylindrical symmetry (formed by a GR card with I2 equal to M), the number of complex numbers in matrix storage

and the proportionality factors for matrix fill time and matrix factor time are:

	Matrix Storage	Fill Time	Factor Time
No Symmetry	N^2	N^2	N^3
M Symmetric Sections	N^2/M	N^2/M	N^3/M^2

The matrix factor time represents the optimum for a large matrix factored in core. Generally, somewhat longer times will be observed.

- If the structure is added to or modified after the GR card in such a way that cylindrical symmetry is destroyed, the program must be reset to a no-symmetry condition. In most cases, the program is set by the geometry routines for the existing symmetry. Operations that automatically reset the symmetry conditions are:

  Addition of a wire by a GW card destroys all symmetry.

  Generation of additional structures by a GM card, with NRPT greater than zero, destroys all symmetry.

  A GM card acting on only part of the structure (having ITS greater than zero) destroys all symmetry.

  A GX or GR card will destroy all previously established symmetry.

  If a structure is rotated about either the X or Y axis by use of a GM card and a ground plane is specified on the GE card, all symmetry will be destroyed. Rotation about the Z-axis or translation will not affect symmetry. If a ground is not specified, symmetry will be unaffected by any rotation or translation by a GM card, unless NRPT or ITS on the GM card is greater than zero.

- Symmetry will also be destroyed if lumped loads are placed on the structure in an unsymmetric manner. In this case, the program is not automatically set to a no-symmetry condition but must be set by a data card following the GR card. A GW card with NS blank will set the program to a no-symmetry condition without modifying the structure. The card must specify a nonzero radius, however, to avoid reading a GC card.


- Placement of nonradiating networks or sources does not affect symmetry.

- When symmetry is used in the solution, the number of symmetric sections (I2) is limited by array dimensions. In the demonstration deck, the limit is 16 sections.
- The GR card produces the same effect on the structure as a GM card if I2 on the GR card is equal to (NRPT+1) on the GM card and if ROZ on the GM card is equal to 360/(NRPT+1) degrees. If the GM card is used, however, the program will not be set to take advantage of symmetry.

Scale Structure Dimensions (GS)

Purpose: To scale all dimensions of a structure by a constant.

Card:

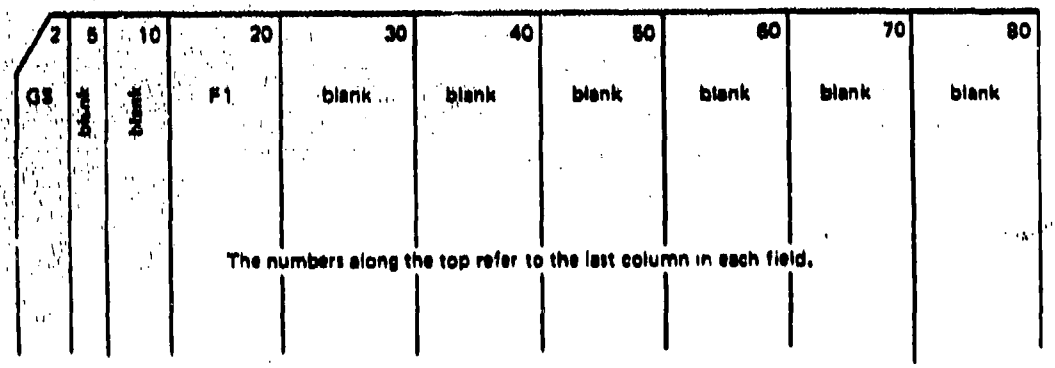

Parameters:

Integers

The integer fields are not used.

Decimal Numbers

(F1) – All structure dimensions, including wire radius, are multiplied by F1.

Notes:

- At the end of geometry input, structure dimensions must be in units of meters. Hence, if the dimensions have been input in other units, a GS card must be used to convert to meters.

Wire Specification (GW)

Purpose: To generate a string of segments to represent a straight wire.

Card:

2	5	10	20	30	40	50	60	70	80
GW	I1	I2	F1	F2	F3	F4	F5	F6	F7
	ITG	NS	XW1	YW1	ZW1	XW2	YW2	ZW2	RAD

The numbers along the top refer to the last column in each field.

The above card defines a string of segments with radius RAD. If RAD is zero or blank, a second card is read to set parameters to taper the segment lengths and radius from one end of the wire to the other. The format for the second card (GC), which is read only when RAD is zero, is:

2	5	10	20	30	40	50	60	70	80
GC	blank	blank	F1	F2	F3	blank	blank	blank	blank
			RDEL	RAD1	RAD2				

The numbers along the top refer to the last column in each field.

Parameters:

Integers

- ITG (I1) – Tag number assigned to all segments of the wire.
- NS (I2) – Number of segments into which the wire will be divided.

Decimal Numbers

- XW1 (F1) – X coordinate
- YW1 (F2) – Y coordinate
- ZW1 (F3) – Z coordinate

} of wire end 1

- XW2 (F4) – X coordinate
- YW2 (F5) – Y coordinate
- ZW2 (F6) – Z coordinate

} of wire end 2

RAD (F7) — Wire radius, or zero for tapered segment option.

Optional GC card parameters

RDEL (F1) — Ratio of the length of a segment to the length of the previous segment in the string.

RAD1 (F2) — Radius of the first segment in the string.

RAD2 (F3) — Radius of the last segment in the string.

The ratio of the radii of adjacent segments is

$$RRAD = \left(\frac{RAD2}{RAD1}\right)^{1/(NS-1)} .$$

If the total wire length is L, the length of the first segment is

$$S_1 = \frac{L(1-RDEL)}{1-(RDEL)^{NS}}$$

or

$$S_1 = L/NS \text{ if } RDEL = 1.$$

Notes:

- The tag number is for later use when a segment must be identified, such as when connecting a voltage source or lumped load to the segment. Any number except zero can be used as a tag. When identifying a segment by its tag, the tag number and the number of the segment in the set of segments having that tag are given. Thus, the tag of a segment does not need to be unique. If no need is anticipated to refer back to any segments on a wire by tag, the tag field may be left blank. This results in a tag of zero which cannot be referenced as a valid tag.

- If two wires are electrically connected at their ends, the identical coordinates should be used for the connected ends to ensure that the wires are treated as connected for current interpolation. If wires intersect away from their ends, the point of intersection must occur at segment ends within each wire for interpolation to occur. Generally, wires should intersect only at their ends unless the location of segment ends is accurately known.

- The only significance of differentiating end one from end two of a wire is that the positive reference direction for current will be in the direction from end one to end two on each segment making up the wire.

- As a rule of thumb, segment lengths should be less than 0.1 wavelength at the desired frequency. Somewhat longer segments may be used on long wires with no abrupt changes, while shorter segments, 0.05 wavelength or less, may be required in modeling critical regions of an antenna.
- If input is in units other than meters, then the units must be scaled to meters through the use of a Scale Structure Dimensions (GS) card.

Reflection in Coordinate Planes (GX)

Purpose: To form structures having planes of symmetry by reflecting part of the structure in the coordinate planes, and to set flags so that symmetry is utilized in the solution.

Card:

2	5	10	20	30	40	50	60	70	80
GX	I1	I2	blank	blank	blank	blank	blank	blank	blank

The numbers along the top refer to the last column in each field.

Parameters:

Integers

(I1) — Tag number increment.

(I2) — This integer is divided into three independent digits, in columns 8, 9, and 10 of the card, which control reflection in the three orthogonal coordinate planes. A one in column 8 causes reflection along the X-axis (reflection in Y, Z plane); a one in column 9 causes reflection along the Y-axis; and a one in column 10 causes reflection along the Z axis. A zero or blank in any of these columns causes the corresponding reflection to be skipped.

Decimal Numbers

The decimal number fields are not used.

Notes:

- Any combination of reflections along the X, Y and Z axes may be used. For example, 101 for (I2) will cause reflection along axes X and Z, and 111 will cause reflection along axes X, Y and Z. When combinations of reflections are requested, the reflections are done in reverse alphabetical order. That is, if a structure is generated in a single octant of space and a GX card is then read with I2 equal to 111, the structure is first reflected along the Z-axis; the structure and its image are then reflected along the Y-axis; and,

finally, these four structures are reflected along the X-axis to fill all octants. This order determines the position of a segment in the sequence and, hence, the absolute segment numbers.

- The tag increment I1 is used to avoid duplication of tag numbers in the image segments. All valid tags on the original structure are incremented by I1 on the image. When combinations of reflections are employed, the tag increment is doubled after each reflection. Thus, a tag increment greater than or equal to the largest tag on the original structure will ensure that no duplicate tags are generated. For example, if tags from 1 to 100 are used on the original structure with I2 equal to 011 and a tag increment of 100, the first reflection, along the Z-axis, will produce tags from 101 to 200; and the second reflection, along the Y-axis, will produce tags from 201 to 400, as a result of the increment being doubled to 200.

- The GX card should never be used when there are segments located in the plane about which reflection would take place or crossing this plane. The image segments would then coincide with or intersect the original segments, and such overlapping segments are not allowed. Segments may end on the image plane, however.

- When a structure having plane symmetry is formed by a GX card, the program will make use of the symmetry to simplify solution for the currents. The number of complex numbers in matrix storage and the proportionality factors for matrix fill time and matrix factor time for a structure modeled by N segments are:

No. of Planes of Symmetry	Matrix Storage	Fill Time	Factor Time
0	N^2	N^2	N^3
1	$\frac{N^2}{2}$	$\frac{N^2}{2}$	$\frac{N^3}{4}$
2	$\frac{N^2}{4}$	$\frac{N^2}{4}$	$\frac{N^3}{16}$
3	$\frac{N^2}{8}$	$\frac{N^2}{8}$	$\frac{N^3}{64}$

The matrix factor time represents the optimum for a large matrix factored in core. Generally, somewhat longer times will be observed.

- If the structure is added to or modified after the GX card in such a way that symmetry is destroyed, the program must be reset to a no-symmetry condition. In most cases, the program is set by the geometry routines for the existing symmetry. Operations that automatically reset the symmetry condition are:

  Addition of a wire by a GW card destroys all symmetry.

  Generation of additional structures by a GM card, with NRPT greater than zero, destroys all symmetry.

  A GM card acting on only part of the structure (having ITS greater than zero) destroys all symmetry.

  A GX card or GR card will destroy all previously established symmetry. For example, two GR cards with I2 equal to 011 and 100, respectively, will produce the same structure as a single GX card with I2 equal to 111; however, the first case will set the program to use symmetry about the Y, Z plane only while the second case will make use of symmetry about all three coordinate planes.

  If a ground plane is specified on the GE card, symmetry about a plane parallel to the X, Y plane will be destroyed. Symmetry about other planes will be used, however.

  If a structure is rotated about either the X or Y axis by use of a GM card and a ground plane is specified on the GE card, all symmetry will be destroyed. Rotation about the Z-axis or translation will not affect symmetry. If a ground is not specified, no rotation or translation will affect symmetry conditions unless NRPT on the GM card is greater than zero.

  Symmetry will also be destroyed if lumped loads are placed on the structure in an unsymmetric manner. In this case, the program is not automatically set to a no-symmetry condition but must be set by a data card following the GX card. A GW card with NS blank will set the program to a no-symmetry condition without modifying the structure. The card must specify a nonzero radius, however, to avoid reading a GC card.

- Placement of sources or nonradiating networks does not affect symmetry.

Surface Patch (SP)

Purpose: To input parameters of a single surface patch.

Card:

2	5	10	20	30	40	50	60	70	80
SP	I1	I2	F1	F2	F3	F4	F5	F6	blank
	blank	NS	X1	Y1	Z1	X2	Y2	Z2	

The numbers along the top refer to the last column in each field.

If NS is 1, 2, or 3, a second card is read in the following format:

2	5	10	20	30	40	50	60	70	80
SC	I1	I2	F1	F2	F3	F4	F5	F6	blank
	blank		X3	Y3	Z3	X4	Y4	Z4	

The numbers along the top refer to the last column in each field.

Parameters:

Integers

(I1) — not used

NS (I2) — Selects patch shape

- 0: (default) arbitrary patch shape
- 1: rectangular patch
- 2: triangular patch
- 3: quadrilateral patch

Decimal Numbers

Arbitrary shape (NS = 0)

X1	(F1) – X coordinate	of patch center
Y1	(F2) – Y coordinate	
Z1	(F3) – Z coordinate	
X2	(F4) – elevation angle above the X-Y plane	of outward normal vector (degrees)
Y2	(F5) – azimuth angle from X-axis	
Z2	(F6) – patch area (square of units used)	

Rectangular, triangular, or quadrilateral patch (NS = 1, 2, or 3)


X1	(F1)	X, Y, Z coordinates of corner 1
Y1	(F2)	
Z1	(F3)	
X2	(F4)	X, Y, Z coordinates of corner 2
Y2	(F5)	
Z2	(F6)	
X3	(F1)	X, Y, Z coordinates of corner 3
Y3	(F2)	
Z3	(F3)	

For the quadrilateral patch only (NS = 3)


X4	(F4)	X, Y, Z coordinates of corner 4
Y4	(F5)	
Z4	(F6)	

Notes:


- The four patch options are shown in figure 5. For the rectangular, triangular, and quadrilateral patches the outward normal vector $\hat{n}$ is specified by the ordering of corners 1, 2, and 3 and the right-hand rule.
- For a rectangular, triangular, or quadrilateral patch, $\hat{\ell}_1$ is parallel to the side from corner 1 to corner 2. For NS = 0, $\hat{\ell}_1$ is chosen as described in section II-2.
- If the sides from corner 1 to corner 2 and from corner 2 to corner 3 of the rectangular patch are not perpendicular, the result will be a parallelogram.

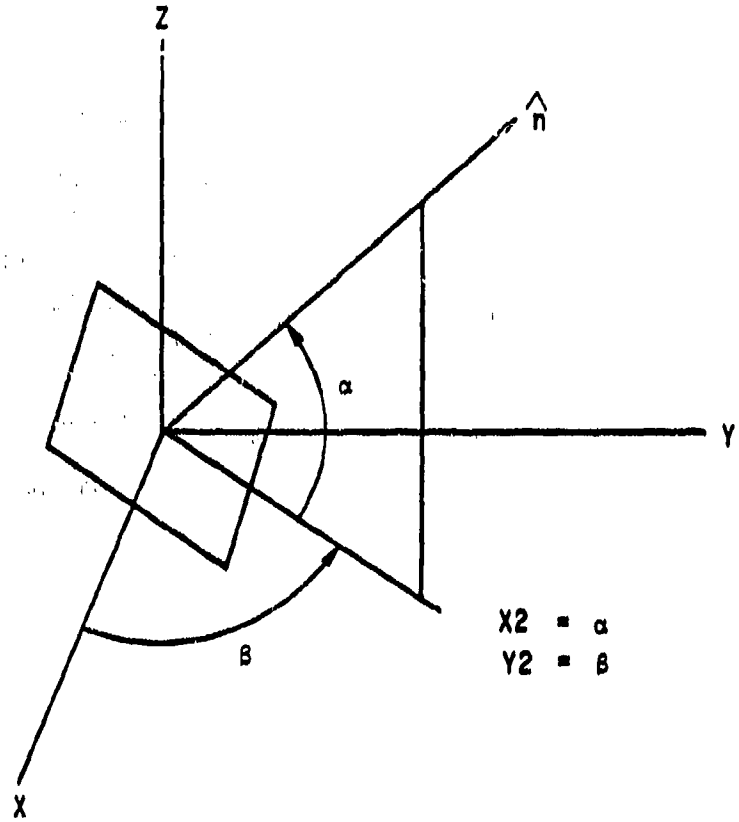


(a) Arbitrary Patch Shape (NS = 0)

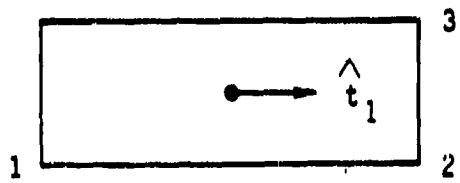

(b) Rectangular Patch (NS = 1)

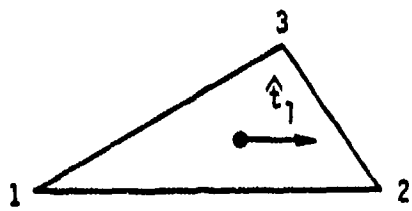

(c) Triangular Patch (NS = 2)

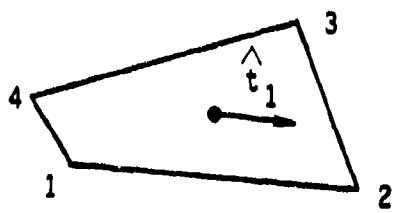

(d) Quadrilateral Patch (NS = 3)

Figure 5. Surface Patch Options.

- If the four corners of the quadrilateral patch do not lie in the same plane, the run will terminate with an error message.
- Since the program does not integrate over patches, except at a wire connection, the patch shape does not affect the results. The only parameters affecting the results are the location of the patch centroid, the patch area, and the outward unit normal vector. For the arbitrary patch shape these are input, while for the other options they are determined from the specified shape. For solution accuracy, however, the distribution of patch centers obtained with generally square patches has been found to be desirable (see section II-2).
- For the rectangular or quadrilateral options, multiple SC cards may follow a SP card to specify a string of patches. The parameters on the second or subsequent SC card specify corner 3 for a rectangle or corners 3 and 4 for a quadrilateral, while corners 3 and 4 of the previous patch become corners 2 and 1, respectively, of the new patch. The integer I2 on the second or subsequent SC card specifies the new patch shape and must be 1 for rectangular shape or 3 for quadrilateral shape. On the first SC card after SP, I2 has no effect. Rectangular or quadrilateral patches may be intermixed, but triangular or arbitrary shapes are not allowed in a string of linked patches.

Multiple Patch Surface (SM)

Purpose: To cover a rectangular region with surface patches.

Card:

2	5	10	20	30	40	50	60	70	80
SM	I1	I2	F1	F2	F3	F4	F5	F6	blank
	NX	NY	X1	Y1	Z1	X2	Y2	Z2	

The numbers along the top refer to the last column in each field.

A second card with the following format must immediately follow a SM card:

2	5	10	20	30	40	50	60	70	80
SC	blank	blank	F1	F2	F3	F4	F5	F6	blank
			X3	Y3	Z3				

The numbers along the top refer to the last column in each field.

Parameters:

Integers

NX	(I1)	The rectangular surface is divided into NX patches from corner 1 to corner 2 and NY patches from corner 2 to corner 3.
NY	(I2)	

Decimal Numbers

X1	(F1)	X, Y, Z coordinates of corner 1
Y1	(F2)	
Z1	(F3)	
X2	(F4)	X, Y, Z coordinates of corner 2
Y2	(F5)	
Z2	(F6)	

X3	(F7)	X, Y, Z coordinates of corner 3
Y3	(F8)	
Z3	(F9)	

Notes:

- The division of the rectangle into patches is as illustrated in figure 6.

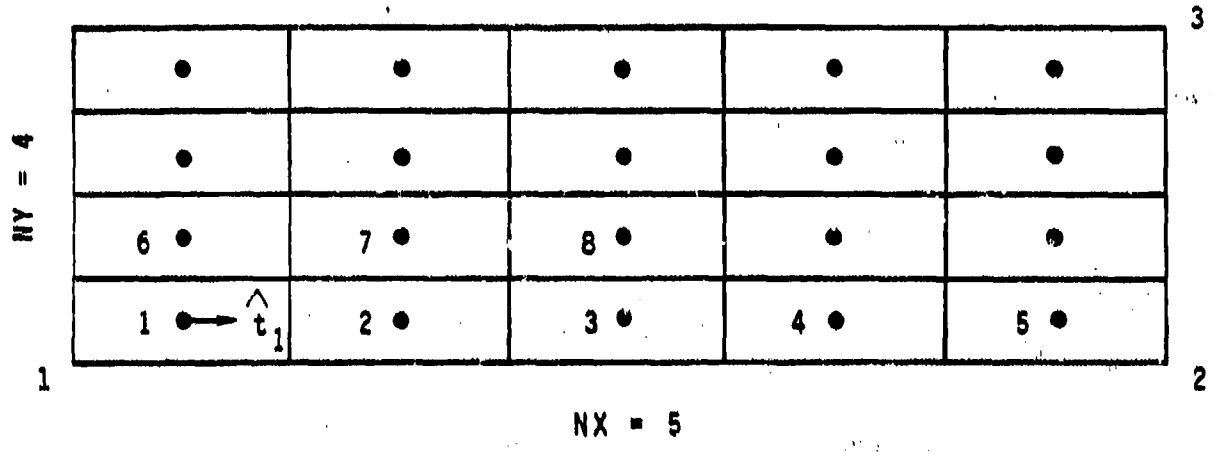


Figure 6. Rectangular Surface Covered by Multiple Patches.

- The direction of the outward normals $\hat{n}$ of the patches is determined by the ordering of corners 1, 2, and 3 and the right-hand rule. The vectors $\hat{t}_1$ are parallel to the side from corner 1 to corner 2 and $\hat{t}_2 = \hat{n} \times \hat{t}_1$. The patch may have arbitrary orientation.
- If the sides between corners 1 and 2 and between corners 2 and 3 are not perpendicular, the complete surface and the individual patches will be parallelograms.
- Multiple SC cards are not allowed with SM.

Examples of Structure Geometry Data

Rhombic Antenna — No Symmetry

Structure: figure 7

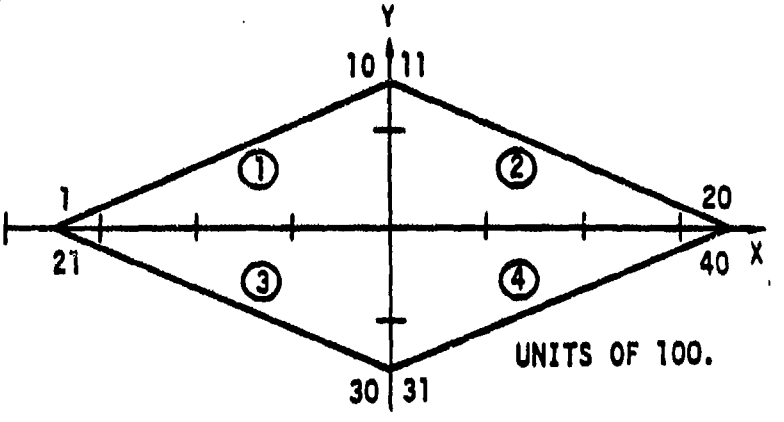


Figure 7. Rhombic Antenna — No Symmetry.

Geometry Data Cards:

```
2 |  5 |  10 |  20 |  30 |  40 |  50 |  60 |  70 |  80
GW |  1 |  10 |  -350.  |  0.  |  150.  |  0.  |  150.  |  150.  |  .1
GW |  2 |  10 |  0.  |  150.  |  150.  |  -350.  |  0.  |  150.  |  .1
GW |  3 |  10 |  350.  |  0.  |  150.  |  0.  |  150.  |  150.  |  .1
GW |  4 |  10 |  0.  |  -150.  |  150.  |  -350.  |  0.  |  150.  |  .1
GE |  0 |  0.80480
```

Number of Segments: 40

Symmetry: None

These cards generate segment data for a rhombic antenna. The data are input in dimensions of feet and scaled to meters. In the figure, numbers near the structure represent segment numbers and circled numbers represent tag numbers.

Rhombic Antenna — Plane Symmetry

Structure: figure 8

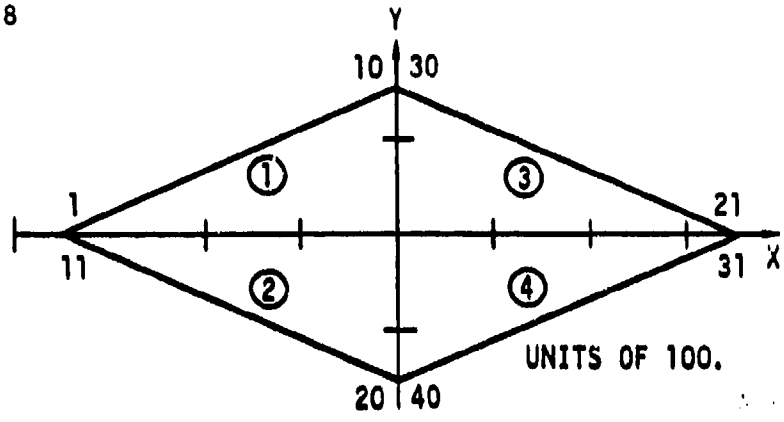


Figure 8. Rhombic Antenna — 2 Planes of Symmetry.

Geometry Data Cards:

```
2 |5 |10 |20 |30 |40 |50 |60 |70 |80
GW | 1 | 10 | .350 | 0. | 150. | 0. | 150. | 150. | .1
GX | 1 | 110 |
GS |  |  | 0.30480 |
GE |  |  |  |  |  |  |  |  |
```

Number of Segments: 40

Symmetry: Two planes

These cards generate the same structure as the previous set although the segment numbering is altered. By making use of two planes of symmetry, these data will require storage of only a 10 by 40 interaction matrix. If segments 21 and 31 are to be loaded as the termination of the antenna, then symmetry about the YZ plane cannot be used. The following cards will result in symmetry about only the XZ plane being used in the solution; thus, allowing segments on one end of the antenna to be loaded.

Structure: figure 9

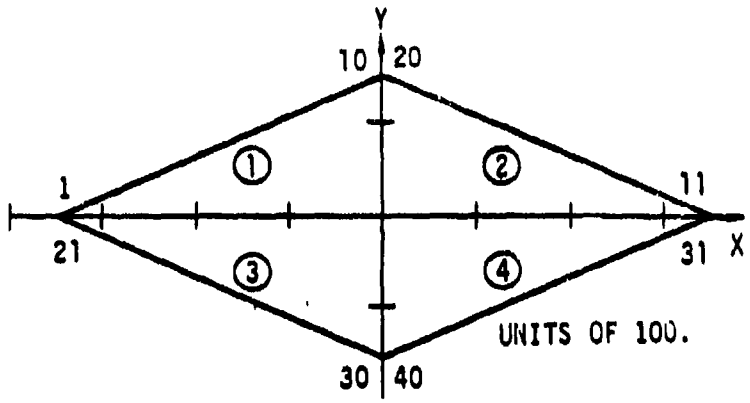


Figure 9. Rhombic Antenna — 1 Plane of Symmetry.

Geometry Data Cards:

```
2    5    10        20        30        40        50        60        70        80
GW   1    10   .350.     0.        150.      0.        150.      150.      1
GX   1   100
GX   2   010
GS        0.50400
GE
```

Number of Segments: 40

Symmetry: One plane

Segments 1 through 20 of this structure are in the first symmetric section. Hence, segments 11 and 31 can be loaded without loading segments 1 and 21 (loading segments in symmetric structures is discussed in the section covering the LD card). These data will cause storage of a 20 by 40 interaction matrix.

Two Coaxial Rings

Structure: figure 10

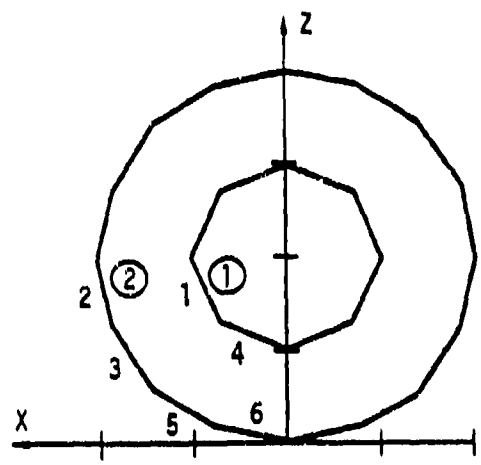


Figure 10. Coaxial Rings.

Geometry Data Cards:

2	5	10	20	30	40	50	60	70	80
GW	1	1	1.0	0.	0.	0.70711	0.70711	0.	.001
GW	2	1	2.0	0.	0.	0.78536	1.84776	0.	.001
GR	8	1	0.78536	1.84776	0.	1.41421	1.41421	0.	.001
GE		0							
GM			90.	0.	0.	0.	0.	2.0	
SP									

Number of Segments: 24

Symmetry: 8 section cylindrical symmetry

The first 45 degree section of the two rings is generated by the first three GW cards. This section is then rotated about the Z-axis to complete the structure. The rings are then rotated about the X-axis and elevated to produce the structure shown. Since no tag increment is specified on the GR card, all segments on the first ring have tags of 1 and all segments on the second ring have tags of 2. Because of symmetry, these data will require storage of only a 3 by 24 interaction matrix. If a 1 were punched in column 5 of the GE card, however, symmetry would be destroyed by the interaction with the ground, requiring storage of a 24 by 24 matrix.

Linear Antenna over a Wire Grid Plate

Structure: figure 11


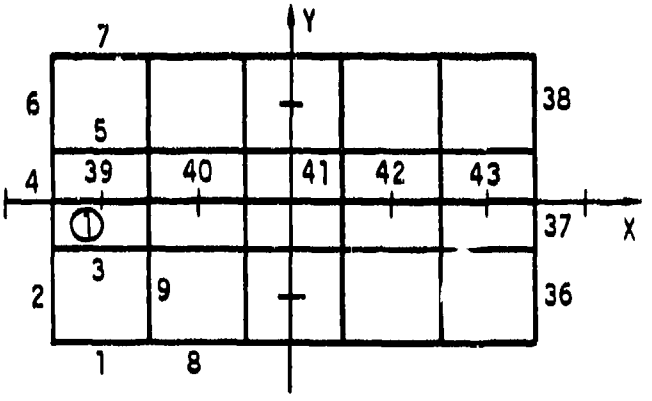


Figure 11. Wire Grid Plate and Dipole.

Geometry Data Cards:

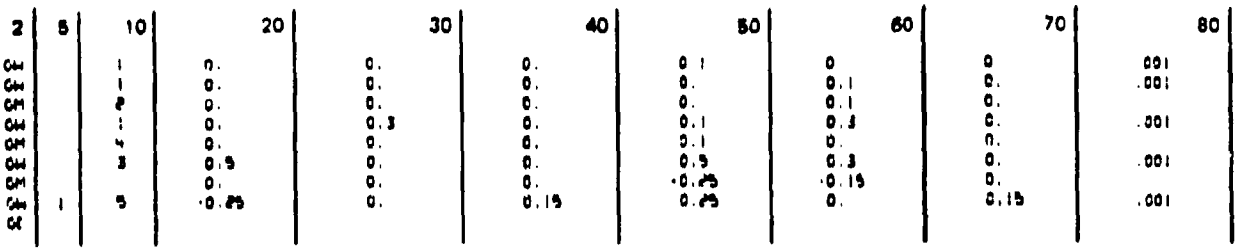

Number of Segments: 43


Symmetry: None

The first 6 cards generate data for the wire grid plate, with the lower left-hand corner at the coordinate origin, by using the GM card to reproduce sections of the structure. The GM card is then used to move the center of the plate to the origin. Finally, a wire is generated 0.15 meters above the plate with a tag of 1.

Cylinder with Attached Wires

Structure: figure 12

Geometry Data Cards:

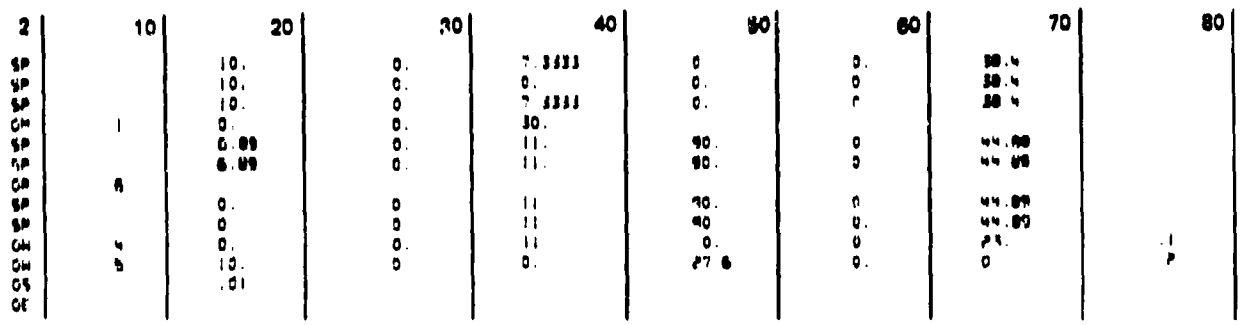

Number of Segments: 9

Number of Patches: 56

Symmetry: None

The cylinder is generated by first specifying three patches in a column centered on the X axis as shown in figure 12(a). A GM card is then used to produce a second column of patches rotated about the Z axis by 30 degrees. A patch is added to the top and another to the bottom to form parts of the end surfaces. The model at this point is shown in figure 12(b). Next a GR card is used to rotate this section of patches about the Z axis to form a total of six similar sections, including the original. A patch is then added to the center of the top and

another to the bottom to form the complete cylinder shown in figure 12(c). Finally, two GW cards are used to add wires connecting to the top and side of the cylinder. The patches to which the wires are connected are divided into four smaller patches as shown in figure 12(d). Although patch shape is not input to the program, square patches are assumed at the base of a connected wire when integrating over the surface current. Hence, a more accurate representation of the model would be as shown in figure 13, where the patches to which wires connect are square with equal areas maintained for all patches (before subdivision).

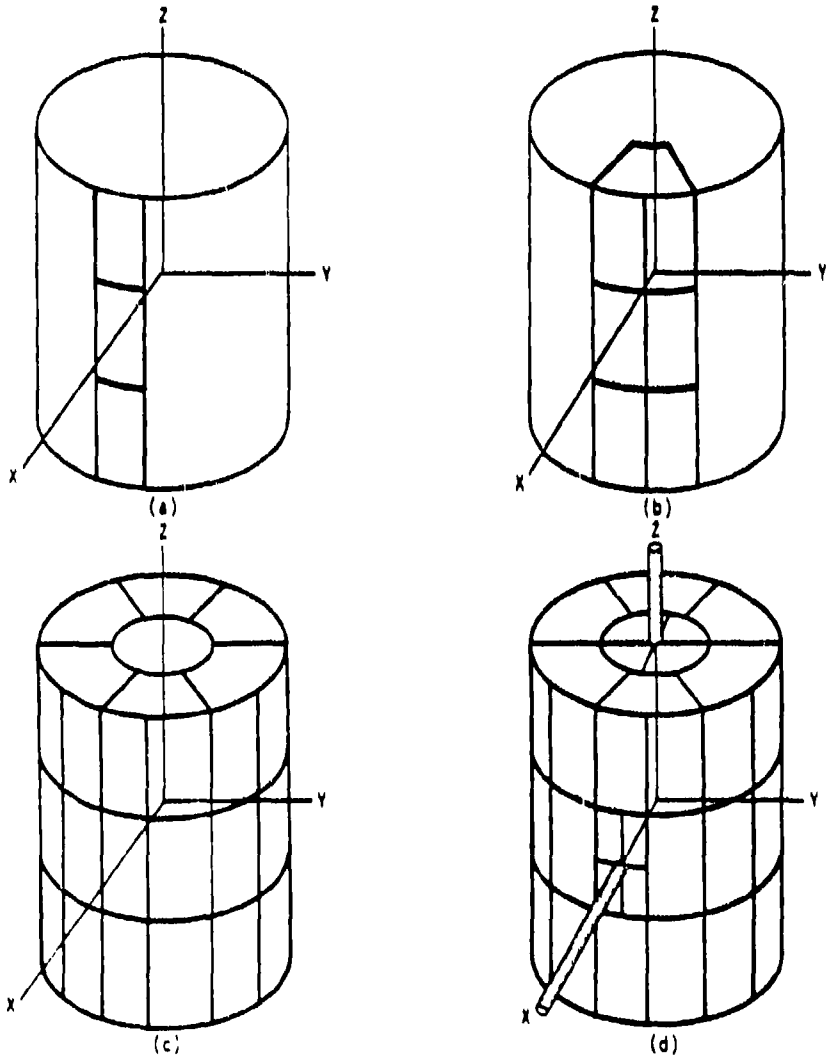


Figure 12. Development of Surface Model for Cylinder with Attached Wires.

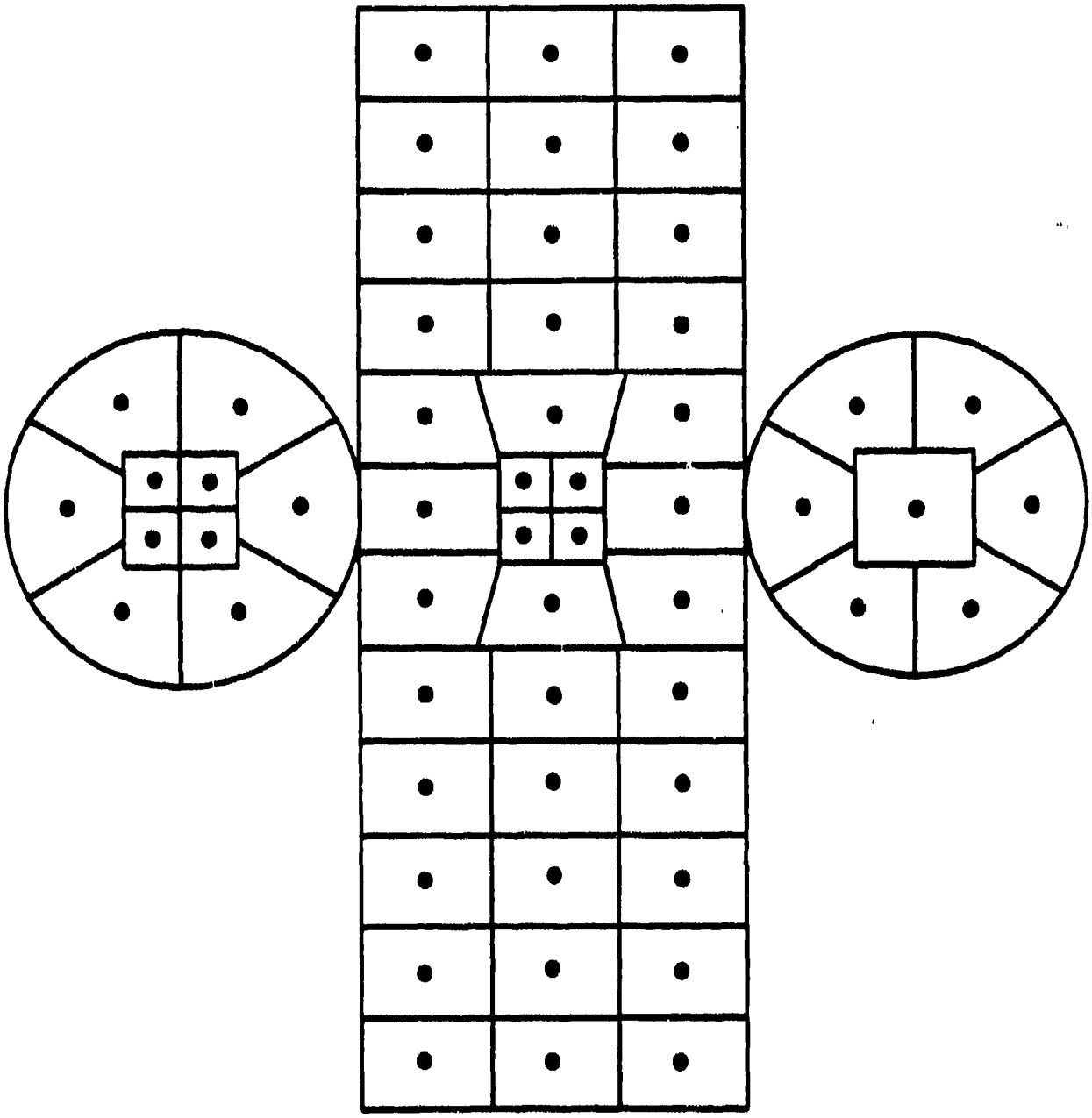


Figure 13. Segmentation of Cylinder for Wires Connected to End and Side.

3. PROGRAM CONTROL CARDS

The program control cards follow the structure geometry cards. They set electrical parameters for the model, select options for the solution procedure, and request data computation. The cards are listed below by their mnemonic identifier with a brief description of their function:

I
- EK — extended thin-wire kernel flag
- FR — frequency specification
- GN — ground parameter specification
- KH — interaction approximation range
- LD — structure impedance loading

II
- EX — structure excitation card
- NT — two-port network specification
- TL — transmission line specification

III
- CP — coupling calculation
- EN — end of data flag
- GD — additional ground parameter specifications
- NE — near electric field request
- NH — near magnetic field request
- NX — next structure flag
- PQ — wire charge density print control
- PT — wire-current print control
- RP — radiation pattern request
- WG — write Numerical Green's Function file
- XQ — execute card

There is no fixed order for the cards. The desired parameters and options are set first followed by requests for calculation of currents, near fields and radiated fields. Parameters that are not set in the input data are given default values. The one exception to this is the excitation (EX) which must be set

Computation of currents may be requested by an XQ card. RP, NE, or NH cards cause calculation of the currents and radiated or near fields on the first occurrence. Subsequent RP, NE, or NH cards cause computation of fields using the previously calculated currents. Any number of near-field and radiation-pattern requests may be grouped together in a data deck. An exception to this occurs when multiple frequencies are requested by a single FR

card. In this case, only a single NE or NH card and a single RP card will remain in effect for all frequencies.

All parameters retain their values until changed by subsequent data cards. Hence, after parameters have been set and currents or fields computed, selected parameters may be changed and the calculations repeated. For example, if a number of different excitations are required at a single frequency, the deck could have the form FR, EX, XQ, EX, XQ, ... If a single excitation is required at a number of frequencies, the cards EX, FR, XQ, FR, XQ, ... could be used.

When the antenna is modified and additional calculations are requested, the order of the cards may, in some cases, affect the solution time since the program will repeat only that part of the solution affected by the changed parameters. For this reason, the user should understand the relation of the data cards to the solution procedure. The first step in the solution is to calculate the interaction matrix, which determines the response of the antenna to an arbitrary excitation, and to factor this matrix in preparation for solution of the matrix equation. This is the most time-consuming single step in the solution procedure. The second step is to solve the matrix equation for the currents due to a specific excitation. Finally, the near fields or radiated fields may be computed from the currents.

The interaction matrix depends only on the structure geometry and the cards in group I of the program control cards. Thus, computation and factorization of the matrix is not repeated if cards beyond group I are changed. On the other hand, antenna currents depend on both the interaction matrix and the cards in group II, so that the currents must be recomputed whenever cards in group I or II are changed. The near fields depend only on the structure currents while the radiated fields depend on the currents and on the GD card, which contains special ground parameters for the radiated-field calculation. An example of the implications of these rules is presented by the following two sets of data cards:

FR, EX, NT_1, LD_1, XQ, LD_2, XQ, NT_2, LD_1, XQ, LD_2, XQ

FR, EX, LD_1, NT_1, XQ, NT_2, XQ, LD_2, NT_1, XQ, NT_2, XQ

Calculation and factoring of the matrix would be required four times by the first set but only twice by the second set in obtaining the same information.

The program control cards are explained on the following pages. The format of all program control cards has four integers and six floating point

numbers. The integers are contained in columns 3 through 5, 6 through 10, 11 through 15, and 16 through 20 (each integer field stops at an integral multiple of 5 columns), and the floating point numbers are contained in fields of 10 for the remainder of the card (i.e., from 21 through 30, 31 through 40, etc.). Integers are right justified in their fields. The floating point numbers can be punched either as a string of digits containing a decimal point, punched anywhere in the field; or as a string of digits containing a decimal point and followed by an exponent of ten in the form E ± I which multiplies the number by $10^{\pm I}$. The integer exponent must be right justified in the field.

Maximum Coupling Calculation (CP)

Purpose: To request calculation of the maximum coupling between segments.

Card:

2	5	10	15	20	30	40	50	60	70	80
CP	I1 TAG1	I2 SEG1	I3 TAG2	I4 SEG2	blank	blank	blank	blank	blank	blank

The numbers along the top refer to the last column in each field.

Parameters:

TAG1	(I1)	Specify segment number SEG1 in the set of segments having tag TAG1. If TAG1 is blank or zero, then SEG1 is the segment number.
SEG1	(I2)	
TAG2	(I3)	Same as above
SEG2	(I4)	


Notes:

- Up to five segments may be specified on 2-1/2 CP cards. Coupling is computed between all pairs of these segments. When more than two segments are specified, the CP cards must be grouped together. A new group of CP cards replaces the old group.
- CP does not cause the program to proceed with the calculation but only sets the segment numbers. The specified segments must then be excited (EX card) one at a time in the specified order and the currents computed (XQ, RP, NE, or NH card). The excitation must use the applied-field voltage-source model. When all of the specified segments have been excited in the proper order, the couplings will be computed and printed. After the coupling calculation the set of CP cards is cancelled.

Extended Thin-Wire Kernel (EK)

Purpose: To control use of the extended thin-wire kernel approximation.

Card:

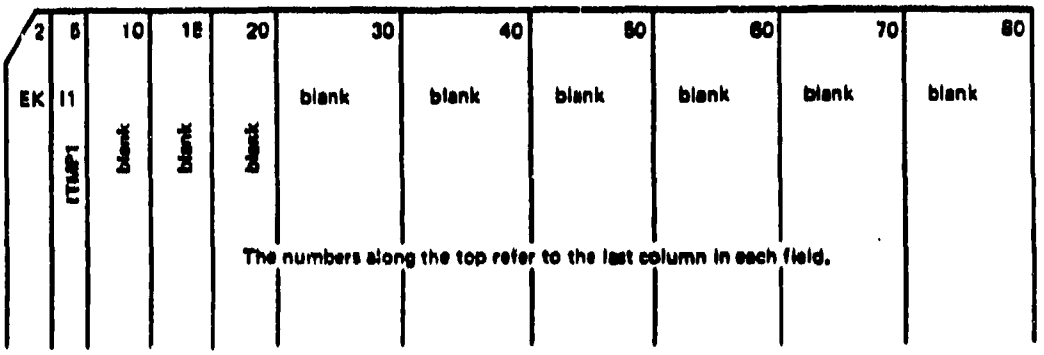

Parameters:

Integers

ITMP1 (I1) – Blank or zero to initiate use of the extended thin-wire kernel, -1 to return to standard thin-wire kernel. Without an EK card, the program will use the standard thin-wire kernel.

End of Run (EN)

Purpose: To indicate to the program the end of all execution.

Card:

2	5	10	15	20	30	40	50	60	70	80
EN	blank	blank	blank	blank	blank	blank	blank	blank	blank	blank


The numbers along the top refer to the last column in each field.

Parameters: None

Excitation (EX)

Purpose: To specify the excitation for the structure. The excitation can be voltage sources on the structure, an elementary current source, or a plane-wave incident on the structure.

Card:

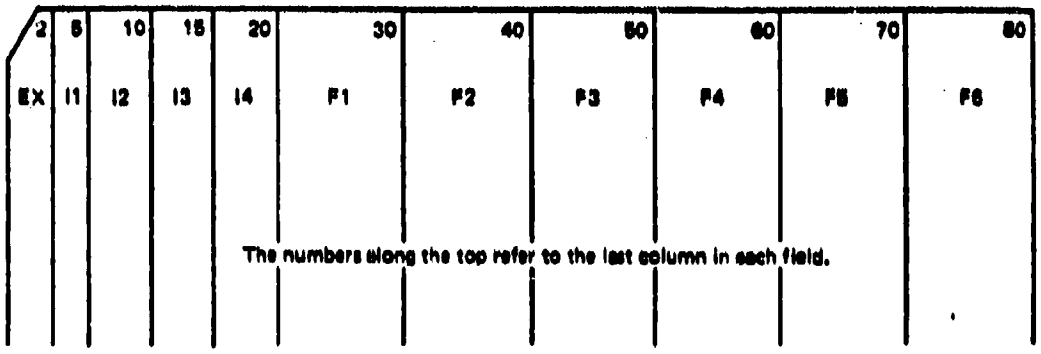

Parameters:

Integers

(I1) — Determines the type of excitation which is used.

0 — voltage source (applied-E-field source).

1 — incident plane wave, linear polarization.

2 — incident plane wave, right-hand (thumb along the incident k vector) elliptic polarization.

3 — incident plane wave, left-hand elliptic polarization.

4 — elementary current source.

5 — voltage source (current-slope-discontinuity).

Remaining Integers Depend on Excitation Type

a. Voltage source ((I1) = 0 or 5)

(I2) — Tag number of the source segment. This tag number along with the number to be given in (I3), which identifies the position of the segment in a set of equal tag numbers, uniquely defines the source segment. Blank or zero in field (I2) implies that the source segment will be identified by using the absolute segment number in the next field.

(I3) — Equal to m, specifies the m^{th} segment of the set of segments whose tag numbers are equal to the number

set by the previous parameter. If the previous parameter is zero, the number in (I3) must be the absolute segment number of the source.

(I4) – Columns 19 and 20 of this field are used separately.

The options for column 19 are:

1 – maximum relative admittance matrix asymmetry for source segments and network connections will be calculated and printed.

0 – no action.

The options for column 20 are:

1 – the input impedance at voltage sources is always printed directly before the segment currents in the output. By setting this flag, the impedances of a single source segment in a frequency loop will be collected and printed in a table (in a normalized and unnormalized form) after the information at all frequencies has been printed. Normalization to the maximum value is a default, but the normalization value can be specified (refer to F3 under voltage source below). When there is more than one source on the structure, only the impedance of the last source specified will be collected.

0 – no action.

b. Incident plane wave ((I1) = 1, 2, or 3)

(I2) – Number of theta angles desired for the incident plane wave.

(I3) – Number of phi angles desired for the incident plane wave.

(I4) – Only column 19 is used. The options are:

1 – maximum relative admittance matrix asymmetry for network connections will be calculated and printed.

0 – no action.

c. Elementary current source ((I1) = 4)

(I2) & (I3) — blank.

(I4) — Only column 19 is used and its function is identical to that listed under b.

Floating Point Options

a. Voltage source ((I1) = 0 or 5)

(F1) — Real part of the voltage in volts.

(F2) — Imaginary part of the voltage in volts.

(F3) — If a one is placed in column 20 (see above), this field can be used to specify a normalization constant for the impedance printed in the optional impedance table. Blank in this field produces normalization to the maximum value.

(F4), (F5), & (F6) — Blank.

b. Incident plane wave ((I1) = 1, 2, or 3). The incident wave is characterized by the direction of incidence $\hat{k}$ and polarization in the plane normal to $\hat{k}$.

(F1) — Theta in degrees. Theta is defined in standard spherical coordinates as illustrated in figure 14.

(F2) — Phi in degrees. Phi is the standard spherical angle defined in the XY plane.

(F3) — Eta in degrees. Eta is the polarization angle defined as the angle between the theta unit vector and the

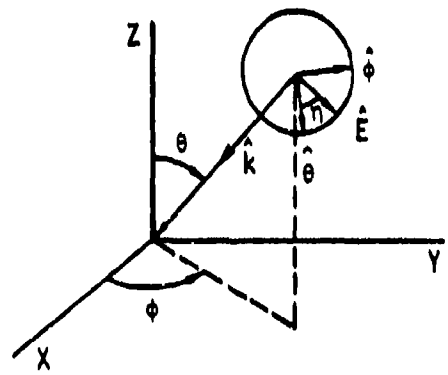


Figure 14. Specification of Incident Wave.

direction of the electric field for linear polarization or the major ellipse axis for elliptical polarization. Refer to figure 14.

(F4) – Theta angle stepping increment in degrees.

(F5) – Phi angle stepping increment in degrees.

(F6) – Ratio of minor axis to major axis for elliptic polarization (major axis field strength = 1 V/m).

c. Elementary current source ((I1) = 4). The current source is characterized by its Cartesian coordinate position, its orientation, and its magnitude.

(F1) – X position in meters.

(F2) – Y position in meters.

(F3) – Z position in meters.

(F4) – α in degrees. α is the angle the current source makes with the XY plane as illustrated in figure 15.

(F5) – β in degrees. β is the angle the projection of the current source on the XY plane makes with the X axis.

(F6) – "Current moment" of the source. This parameter is equal to the product $I\ell$ in amp meters.

Notes:

- In the case of voltage sources, excitation cards can be grouped together in order to specify multiple sources. The maximum number of voltage sources that may be specified is determined by dimension statements in the program. The dimensions are set for 10 applied-E-field voltage sources and 10 current-slope-discontinuity voltage sources.

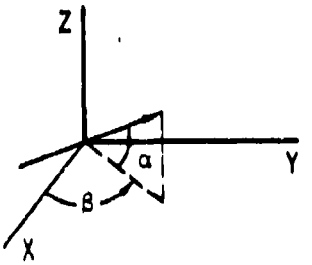



Figure 15. Orientation of Current Element.

- The applied-E-field voltage source is located on the segment specified.
- The current-slope-discontinuity voltage source is located at the first end, relative to the reference direction, of the specified segment, at the junction between the specified segment and the previous segment. This junction must be a simple two-segment junction, and the two segments must be parallel with equal lengths and radii.
- A current-slope-discontinuity voltage source may lie in a symmetry plane. An applied field voltage source may not lie in a symmetry plane since a segment may not lie in a symmetry plane. An applied field voltage source may be used on a wire crossing a symmetry plane by exciting the two segments on opposite sides of the symmetry plane each with half the total voltage, taking account of the reference directions of the two segments.
- An applied field voltage source specified on a segment which has been impedance-loaded, through the use of an LD card, is connected in series with the load. An applied field voltage source specified on the same segment as a network is connected in parallel with the network port. For the specific case of a transmission line, the source is in parallel with both the line and the shunt load. Applied field voltage sources should be used in these cases since loads and network connections are located on, rather than between, segments.
- Only one incident plane wave or one elementary current source is allowed at a time. Also plane-wave or current-source excitation is not allowed with voltage sources. If the excitation types are mixed, the program will use the last excitation type encountered.
- When a number of theta and phi angles are specified for an incident plane-wave excitation, the theta angle changes more rapidly than phi.
- The current element source illuminates the structure with the field of an infinitesimal current element at the specified location. The current element source cannot be used over a ground plane.

Frequency (FR)

Purpose: To specify the frequency(s) in megahertz.

Card:

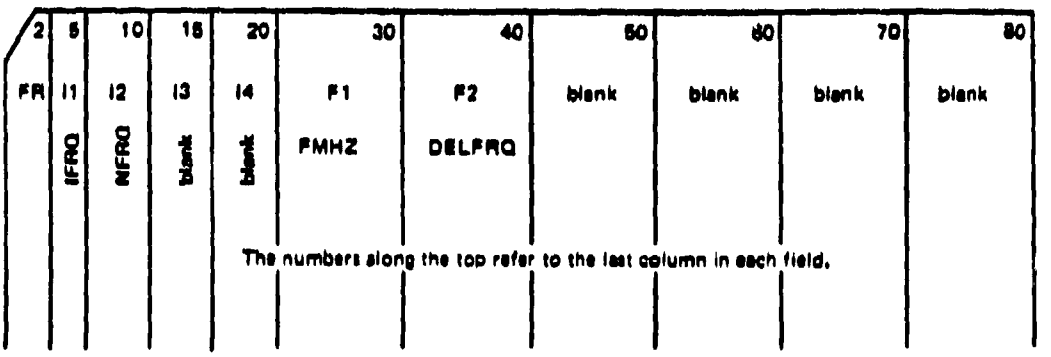

Parameters:

Integers

IFRQ (I1) – Determines the type of frequency stepping which is used.

0 – linear stepping.

1 – multiplicative stepping.

NFRQ (I2) – Number of frequency steps. If this field is blank, one is assumed.

(I3) & (I4) – Blank.

Floating Point

FMHZ (F1) – Frequency in megahertz.

DELFRQ (F2) – Frequency stepping increment. If the frequency stepping is linear, this quantity is added to the frequency each time. If the stepping is multiplicative, this is the multiplication factor.

(F3)---(F6) – Blank.

Notes:

- If a frequency card does not appear in the data deck, a single frequency of 299.8 MHz is assumed. Since the wavelength at 299.8 MHz is one meter, the geometry is in units of wavelengths for this case.
- Frequency cards may not be grouped together. If they are, only the information on the last card in the group will be used.

- After an FR card with NFRQ greater than 1, an NE or NH card will not initiate execution while an RP or XQ card will. In this case, only one NE or NH card and one RP card will be effective for the multiple frequencies.
- After a frequency loop for NFRQ greater than one has been completed, it will not be repeated for a second execution request. The FR card must be repeated in this case.

Additional Ground Parameters (GD)

Purpose: To specify the ground parameters of a second medium which is not in the immediate vicinity of the antenna. This card may only be used if a GN card has also been used. It does not affect the field of surface patches.

Card:

2	5	10	15	20	30	40	50	60	70	80
GD	blank	blank	blank	blank	F1	F2	F3	F4	blank	blank
					EPSR2	SIG2	CLT	CHT		

The numbers along the top refer to the last column in each field.

Parameters:

Integers

All integer fields are blank.

Floating Point

EPSR2 (F1) — Relative dielectric constant of the second medium.

SIG2 (F2) — Conductivity in mhos/meter of the second medium.

CLT (F3) — Distance in meters from the origin of the coordinate system to the join between medium 1 and 2. This distance is either the radius of the circle where the two media join or the distance out the plus X axis to where the two media join in a line parallel to the Y axis. Specification of the circular or linear option is on the RP card. See figure 16.

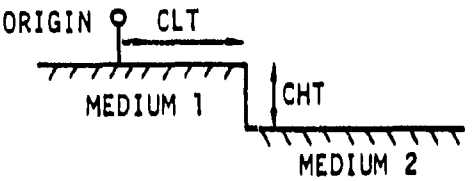


Figure 16. Parameters for a Second Ground Medium.

CHT (F4) — Distance in meters (positive or zero) by which the surface of medium 2 is below medium 1.

(F5) & (F6) — Blank.


Notes:

- The GD card can only be used in a data set where the GN card has been used since the GN card is the only way to specify the ground parameters in the vicinity of the antenna (see GN card write-up). However, a number of GD cards may be used in the same data set with only one GN card.
- GD cards may not be grouped together. If they are, only the information on the last card of the group is retained.
- When a second medium is specified, a flag must also be set on the radiation-pattern (RP) data card in order to calculate the patterns including the effect of the second medium. Refer to the radiation-pattern card write-up for details.
- Use of the GD card does not require recalculation of the matrix or currents.
- The parameters for the second medium are used only in the calculation of the far fields. It is possible then to set the radius of the boundary between the two media equal to zero and thus have the far fields calculated by using only the parameters of medium 2. The currents for this case will still have been calculated by using the parameters of medium 1.
- When a model includes surface patches, the fields due to the patches will be calculated by using only the primary ground parameters. Hence, a second ground medium should not be used with patches.

Ground Parameters (GN)

Purpose: To specify the relative dielectric constant and conductivity of ground in the vicinity of the antenna. In addition, a second set of ground parameters for a second medium can be specified, or a radial wire ground screen can be modeled using a reflection coefficient approximation.

Card:

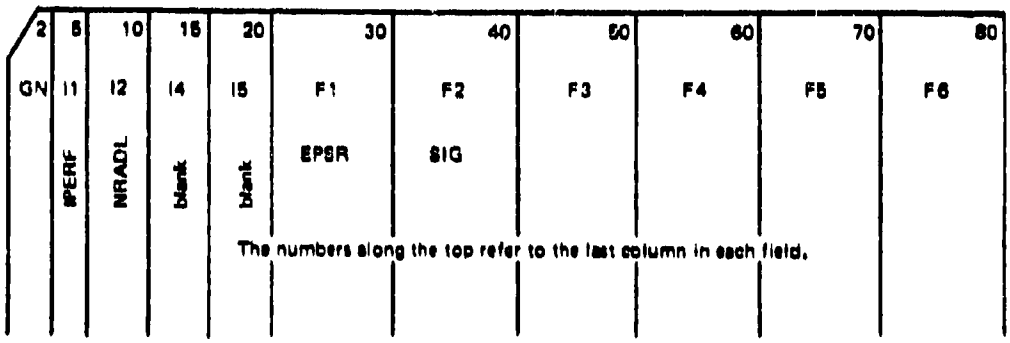

Parameters:

Integers

IPERF (I1) — Ground-type flag. The options are:

-1 — nullifies ground parameters previously used and sets free-space condition. The remainder of the card is left blank in this case.

0 — finite ground, reflection coefficient approximation.

1 — perfectly conducting ground.

2 — finite ground, Sommerfeld/Norton method.

NRADL (I2) — Number of radial wires in the ground screen approximation, blank or 0 implies no ground screen.

(I3) & (I4) — Blank.

Floating Point

EPSR (F1) — Relative dielectric constant for ground in the vicinity of the antenna. Leave blank in case of a perfect ground.

SIG (F2) — Conductivity in mhos/meter of the ground in the vicinity of the antenna. Leave blank in case of a perfect ground. If SIG is input as a negative number, the complex dielectric constant $\varepsilon_c = \varepsilon_r - j\sigma/\omega\varepsilon_o$ is set to EPSR - j|SIG|.

Options for Remaining Floating Point Fields (F3-F6)

a. For the case of an infinite ground plane, F3 through F6 are blank.

b. Radial wire ground screen approximation (NRADL ≠ 0). The ground screen is always centered at the origin, i.e., (0,0,0) and lies in the XY plane.
(F3) — The radius of the screen in meters.
(F4) — Radius of the wires used in the screen in meters.
(F5) & (F6) — Blank.

c. Second medium parameters (NRADL = 0) for medium outside the region of the first medium (cliff problem). These parameters alter the far field patterns but do not affect the antenna impedance or current distribution.
(F3) — Relative dielectric constant of medium 2.
(F4) — Conductivity of medium 2 in mhos/meter.
(F5) — Distance in meters from the origin of the coordinate system to join between medium 1 and 2. This distance is either the radius of the circle where the two media join or the distance out the positive X axis to where the two media join in a line parallel to the Y axis. Specification of the circular or linear option is on the RP card. See figure 16.
(F6) — Distance in meters (positive or zero) by which the surface of medium 2 is below medium 1.

Notes:


- When the Sommerfeld/Norton method is used, NEC requires an input-data file (TAPE21) that is generated by the program SOMNEC for the specific ground parameters and frequency (see section III-4). The file generated by SOMNEC depends only on the complex dielectric constant, $\varepsilon_c = \varepsilon_r - j\sigma/\omega\varepsilon_o$. NEC compares ε_c from the file with that determined by the GN card parameters and frequency. If the relative difference exceeds 10^{-3} an error message is printed. Once TAPE21 has been read for the first use of the Sommerfeld/Norton method the data is retained until the end of the run. Subsequent data, including new data sets following NX cards, may use the TAPE21 data if the ground parameters and frequency (ε_c) remain unchanged. Other ground options may be intermixed with the Sommerfeld/Norton option.

- The parameters of the second medium can also be specified on another data card whose mnemonic is GD. With the GD card, the parameters of the second medium can be varied and only the radiated fields need to be recalculated. Furthermore, if a radial wire ground screen has been specified on the GN card, the GD card is the only way to include a second medium. See the write-up of the GD card for details.
- GN cards may not be grouped together. If they are, only the information on the last card will be retained.
- Use of a GN card after any form of execute dictates structure matrix regeneration.
- Only the parameters of the first medium are used when the antenna currents are calculated; the parameters associated with the second medium are not used until the calculation of the far fields. It is possible then to calculate the currents over one set of ground parameters (medium one), but to calculate the far fields over another set (medium two) by setting the distance to the start of medium two to zero. Medium one can even be a perfectly conducting ground specified by IPERF=1.
- When a radial wire ground screen or a second medium is specified, it is necessary to indicate their presence by the first parameter on the RP card in order to generate the proper radiation patterns.
- When a ground plane is specified, this fact should also be indicated on the GE card. Refer to the GE card for details.
- When a model includes surface patches, the fields due to the patches will be calculated by using only the primary ground parameters. Hence, a second ground medium should not be used with patches. The radial wire ground screen approximation also is not implemented for patches.

Interaction Approximation Range (KH)

Purpose: To set the minimum separation distance for use of a time-saving approximation in filling the interaction matrix.

Card:

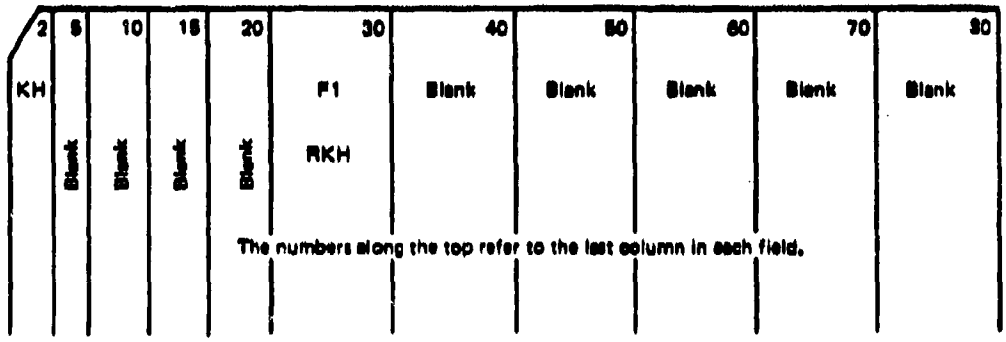

Parameters:

Integers — None

Decimal Numbers

RKH (F1) — The approximation is used for interactions over distances greater than RKH wavelengths.

Notes:

- If two segments or a segment and a patch are separated by more than RKH wavelengths, the interaction field is computed from an impulse approximation to the segment current. The field of a current element located at the segment center is used. No approximation is used for the field due to the surface current on a patch since the time for the standard calculation is very short.
- The KH card can be placed anywhere in the data cards following the geometry cards (with FR, EX, LD, etc.) and affects all calculations requested following its occurrence. The value of RKH may be changed within a data set by use of a new KH card.

Loading (LD)

Purpose: To specify the impedance loading on one segment or a number of segments. Series and parallel RLC circuits can be generated. In addition, a finite conductivity can be specified for segments.

Card:

2	5	10	15	20	30	40	50	60	70	80
LD	I1	I2	I3	I4	F1	F2	F3	blank	blank	blank
	LDTYP	LDTAG	LDTAGF	LDTAGT	ZLR	ZLI	ZLC			

The numbers along the top refer to the last column in each field.

Parameters:

Integers

LDTYP (I1) – Determines the type of loading which is used. The options are:

- -1 – short all loads (used to nullify previous loads). The remainder of the card is left blank.
- 0 – series RLC, input ohms, henries, farads.
- 1 – parallel RLC, input ohms, henries, farads.
- 2 – series RLC, input ohms/meter, henries/meter, farads/meter.
- 3 – parallel RLC, input ohms/meter, henries/meter, farads/meter.
- 4 – impedance, input resistance and reactance in ohms.
- 5 – wire conductivity, mhos/meter.


LDTAG (I2) – Tag number; identifies the wire section(s) to be loaded by its (their) tag numbers. The next two parameters can be used to further specify certain segment(s) on the wire section(s). Blank or zero here implies that absolute segment numbers are being used in the next two parameters to identify segments.

If the next two parameters are blank or zero, all segments with tag LDTAG are loaded.


LDTAGF (I3) — Equal to m specifies the m^{th} segment of the set of segments whose tag numbers equal the tag number specified in the previous parameter. If the previous parameter (LDTAG) is zero, LDTAGF then specifies an absolute segment number. If both LDTAG and LDTAGF are zero, all segments will be loaded.

LDTAGT (I4) — Equal to n specifies the n^{th} segment of the set of segments whose tag numbers equal the tag number specified in the parameter LDTAG. This parameter must be greater than or equal to the previous parameter. The loading specified is applied to each of the m^{th} through n^{th} segments of the set of segments having tags equal to LDTAG. Again if LDTAG is zero, these parameters refer to absolute segment numbers. If LDTAGT is left blank, it is set equal to the previous parameter (LDTAGF).

Floating Point Input for the Various Load Types

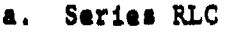a. Series RLC () (LDTYP = 0)

ZLR (F1) — Resistance in ohms, if none, leave blank.
ZLI (F2) — Inductance in henries, if none, leave blank.
ZLC (F3) — Capacitance in farads, if none, leave blank.

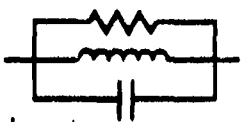b. Parallel RLC () (LDTYP = 1),
floating point input same as a.

c. Series RLC (LDTYP = 2) input, parameters per unit length.
ZLR — Resistance in ohms/meter, if none, leave blank.
ZLI — Inductance in henries/meter, if none, leave blank.
ZLC — Capacitance in farads/meter, if none, leave blank.

d. Parallel RLC (LDTYP = 3), input parameters per unit length, floating point input same as c.

e. Impedance (LDTYP = 4)

ZLR — Resistance in ohms.

ZLI — Reactance in ohms.

f. Wire conductivity (LDTYP = 5)

ZLR — Conductivity in mhos/meter.

Notes:

- Loading cards can be input in groups to achieve a desired structure loading. The maximum number of loading cards in a group is determined by dimensions in the program. The limit is presently 30.
- If a segment is loaded more than once by a group of loading cards, the loads are assumed to be in series (impedances added), and a comment is printed in the output alerting the user to this fact.
- When resistance and reactance are input (LDTYP = 4), the impedance does not automatically scale with frequency.
- Loading cards used after any form of execute, require the regeneration of the structure matrix.
- Since loading modifies the interaction matrix, it will affect the conditions of plane or cylindrical symmetry of a structure. If a structure is geometrically symmetric and each symmetric section is to receive identical loading, then symmetry may be used in the solution. The program is set to utilize symmetry during geometry input by inputting the data for one symmetric section and completing the structure with a GR or GX card. If symmetry is used, the loading on only the first symmetric section is input on LD cards. The same loading will be assumed on the other sections. Loading should not be specified for segments beyond the first section when symmetry is used. If the sections are not identically loaded, then during geometry input the program must be set to a no-symmetry condition to permit independent loading of corresponding segments in different sections.

Near Fields (NE, NH)

Purpose: To request calculation of near electric fields in the vicinity of the antenna (NE) and to request near magnetic fields (NH).

Card:

2	5	10	15	20	30	40	50	60	70	80
NE NH	I1 NEAR	I2 NRX	I3 NRY	I4 NRZ	F1 XNR	F2 YNR	F3 ZNR	F4 DXNR	F5 DYNR	F6 DZNR

The numbers along the top refer to the last column in each field.

Parameters:

Integers

NEAR (I1) — Coordinate system type. The options are:
0 — rectangular coordinates will be used.
1 — spherical coordinates will be used.

Remaining Integers Depend on Coordinate Type

a. Rectangular coordinates (NEAR = 0)

NRX (I2) —
NRY (I3) — } Number of points desired in the X, Y, and Z directions respectively. X changes the most rapidly, then Y, and then Z.
NRZ (I4) —

The value 1 is assumed for any field left blank.

b. Spherical coordinates (NEAR = 1)

(I2) —
(I3) — } Number of points desired in the r, ϕ, and θ directions, respectively. r changes the most rapidly, then ϕ, and then θ. The value 1 is assumed for any field left blank.
(I4) —

Floating Point Fields

Their specification depends on the coordinate system chosen.

a. Rectangular coordinates (NEAR = 0)

XNR (F1) –
YNR (F2) –
ZNR (F3) – } The (X, Y, Z) coordinate position (F1, F2, F3) respectively, in meters of the first field point.

DXNR (F4) –
DYNR (F5) –
DZNR (F6) – } Coordinate stepping increment in meters for the X, Y, and Z coordinates (F4, F5, F6), respectively. In stepping, X changes most rapidly, then Y, and then Z.

b. Spherical coordinates (NEAR = 1)

(F1) –
(F2) –
(F3) – } The (r, ϕ, θ) coordinate position (F1, F2, F3) respectively, of the first field point. r is in meters, and ϕ and θ are in degrees.

(F4) –
(F5) –
(F6) – } Coordinate stepping increments for r, ϕ, and θ (F4, F5, F6), respectively. The stepping increment for r is in meters, and for ϕ and θ is in degrees.

Notes:

- When only one frequency is being used, near-field cards may be grouped together in order to calculate fields at points with various coordinate increments. For this case, each card encountered produces an immediate execution of the near-field routine and the results are printed. When automatic frequency stepping is being used [i.e., when the number of frequency steps (NFRQ) on the FR card is greater than one], only one NE or NH card can be used for program control inside the frequency loop. Furthermore, the NE or NH card does not cause an execution in this case. Execution will begin only after a subsequent radiation-pattern card (RP) or execution card (XQ) is encountered (see respective write-ups on both of these cards).

- The time required to calculate the field at one point is equivalent to filling one row of the matrix. Thus, if there are N segments in the structure, the time required to calculate fields at N points is equivalent to the time required to fill an N × N interaction matrix.

- The near electric field is computed by whichever form of the field equations selected for filling the matrix, either the thin-wire approximation or extended thin-wire approximation. At large distances from the structure, the segment currents are treated as infinitesimal current elements.
- If the field calculation point falls within a wire segment, the point is displaced by the radius of that segment in a direction normal to the plane containing each source segment and the vector from that source segment to the observation segment. When the specified field-calculation point is at the center of a segment, this convention is the same as is used in filling the interaction matrix. If the field point is on a segment axis, that segment produces no contribution to the H-field or the radial component of the E-field. If these components are of interest, the field point should be on or outside of the segment surface.

Networks (NT)

Purpose: To generate a two-port nonradiating network connected between any two segments in the structure. The characteristics of the network are specified by its short-circuit admittance matrix elements. For the special case of a transmission line, a separate card is provided for convenience although the mathematical method is the same as for networks. Refer to the TL card.

Card:

2	5	10	15	20	30	40	50	60	70	80
NT	I1	I2	I3	I4	F1	F2	F3	F4	F5	F6
					Y11R	Y11I	Y12R	Y12I	Y22R	Y22I

The numbers along the top refer to the last column in each field.

Parameters:

Integers

(I1) — Tag number of the segment to which port one of the network is connected. This tag number along with the number to be given in (I2), which identifies the position of the segment in a set of equal tag numbers, uniquely defines the segment for port one. Blank or zero here implies that the segment will be identified, using the absolute segment number in the next location (I2).

(I2) — Equal to m, specifies the m^{th} segment of the set of segments whose tag numbers are equal to the number set by the previous parameter. If the previous parameter is zero, the number in (I2) is the absolute segment number corresponding to end one of the network. A minus one in this field will nullify all previous network and transmission line connections. The rest of the card is left blank in this case.

(I3) & (I4) — Used in exactly the same way as (I1) & (I2) in order to specify the segment corresponding to port two of the network connection.

Floating Point

The six floating-point fields are used to specify the real and imaginary parts of three short circuit admittance matrix elements (1, 1), (1, 2), and (2, 2), respectively. The admittance matrix is symmetric so it is unnecessary to specify element (2, 1).

Y11R (F1) — Real part of element (1, 1) in mhos.
Y11I (F2) — Imaginary part of element (1, 1) in mhos.
Y12R (F3) — Real part of element (1, 2) in mhos.
Y12I (F4) — Imaginary part of element (1, 2) in mhos.
Y22R (F5) — Real part of element (2, 2) in mhos.
Y22I (F6) — Imaginary part of element (2, 2) in mhos.

Notes:

- Network cards may be used in groups to specify several networks on a structure. All network cards for a network configuration must occur together with no other cards (except TL cards) separating them. When the first NT card is read following a card other than an NT or TL card, all previous network and transmission line data are destroyed. Hence, if a set of network data is to be modified, all network data must be input again in the modified form. Dimensions in the program limit the number of networks that may be specified. In the present NEC deck, the number of two-port networks (including transmission lines) is limited to thirty, and the number of different segments having network ports connected to them is limited to thirty.
- One or more network ports can be connected to any given segment. Multiple network ports connected to one segment are connected in parallel.
- If a network is connected to a segment which has been impedance loaded (i.e., through the use of the LD card), the load acts in series with the network port.
- A voltage source specified on the same segment as a network port is connected in parallel with the network port.
- Segments can be impedance-loaded by using network cards. Consider a network connected from the segment to be loaded to some other arbitrary segment as shown in figure 17. The admittance matrix

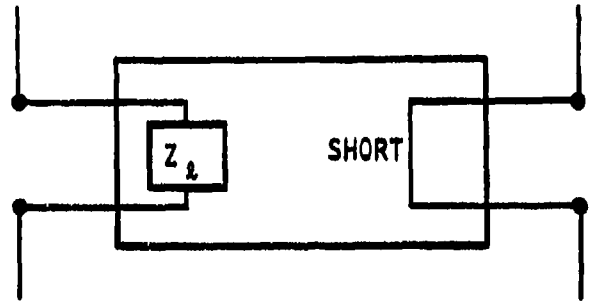


Figure 17. Segment Loaded by Means of a 2-Port Network.


elements are $Y_{11} = 1/Z_\ell$, $Y_{12} = 0$, and Y_{22} = infinity (computationally, a very large number such as 10^{10}). The advantage of using this technique for loading is that the load can be changed without causing a recalculation of the structure matrix as is required when LD cards are used. Furthermore, in some cases a higher degree of structure matrix symmetry can be preserved because the matrix elements are not directly modified by networks as they are when using the LD cards. (Consider for instance a loop with one load where the loop is rotationally symmetric until the load is placed on it.) The disadvantage of the NT card form of loading is that the user must calculate the load admittance, and this value does not automatically scale with frequency. Obviously, in the above schematic, replacing the short with an impedance would load two segments. At a segment at which a voltage source is specified, the effect of loading by the LD and NT cards differs, however, since the network is in parallel with the voltage source while the load specified by an LD card is in series with the source.

- Use of network cards (NT) after any form of execute requires the recalculation of the current only.
- NT and TL cards do not affect structure symmetry.

Next Structure (NX)

Purpose: To signal the end of data for one structure and the beginning of data for the next structure.

Card:

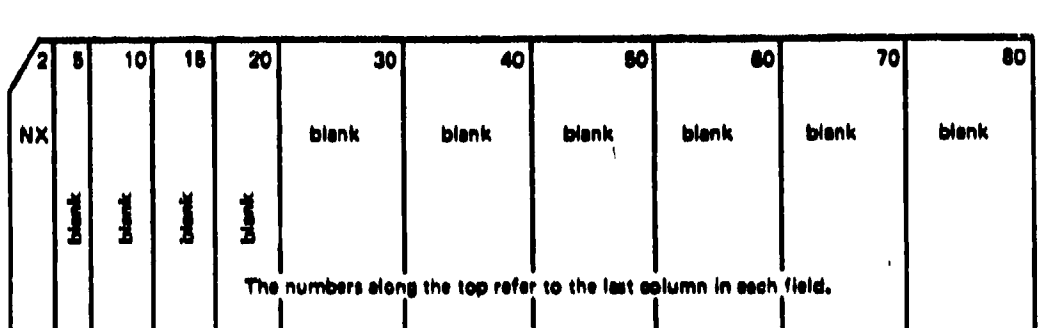

Parameters: NX appears in the first two columns, and the rest of the card is blank.

Notes: The card that directly follows the NX card must be a comment card.

Print Control for Charge on Wires (PQ)

Purpose: To control the printing of charge densities on wire segments.

Card:

2	5	10	15	20	30	40	50	60	70	80
PQ	I1	I2	I3	I4	blank	blank	blank	blank	blank	blank
	IPTFLQ	IPTAQ	IPTAQF	IPTAQT						

The numbers along the top refer to the last column in each field.

Parameters:

Integers

IPTFLQ (I1) – Print control flag:

-1 – suppress printing of charge densities. This is the default condition.

0 – (or blank) print charge densities on segments specified by the following parameters. If the following parameters are blank, charge densities are printed for all segments.

IPTAQ (I2) – Tag number of the segments for which charge densities will be printed.


IPTAQF (I3) – Equal to m specifies the m^{th} segment of the set of segments having tag numbers of IPTAQ. If IPTAQ is zero or blank, then IPTAQF refers to an absolute segment number. If IPTAQF is left blank, then charge density is printed for all segments.

IPTAQT (I4) – Equal to n, specifies the n^{th} segment of the set of segments having tag numbers of IPTAQ. Charge densities are printed for segments having tag number IPTAQ starting at the m^{th} segment in the set and ending at the n^{th} segment. If IPTAQ is zero or blank, then IPTAQF and IPTAQT refer to absolute segment numbers. If IPTAQT is left blank, it is set equal to IPTAQF.

Print Control for Current on Wires (PT)

Purpose: To control the printing of currents on wire segments. Current printing can be suppressed, limited to a few segments, or special formats for receiving patterns can be requested.

Card:

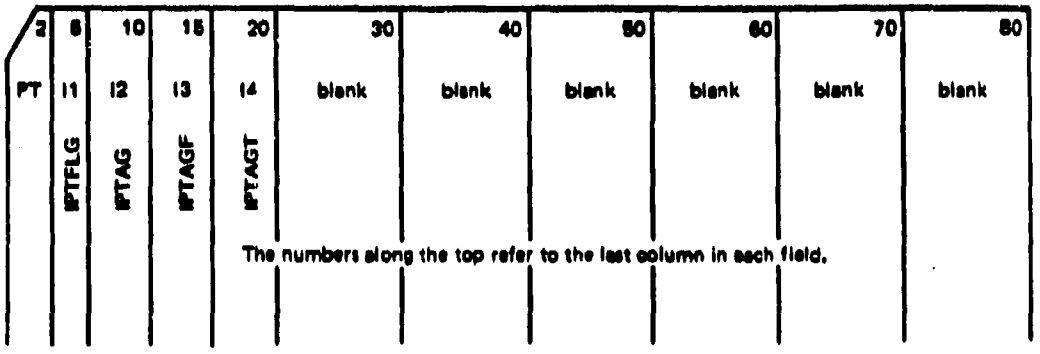

Parameters:

Integers

IPTFLG (I1) — Print control flag, specifies the type of format used in printing segment currents. The options are:

-2 — all currents printed. This is a default value for the program if the card is omitted.

-1 — suppress printing of all wire segment currents.

0 — current printing will be limited to the segments specified by the next three parameters.

1 — currents are printed by using a format designed for a receiving pattern (refer to output section in this manual). Only currents for the segments specified by the next three parameters are printed.

2 — same as for 1 above; in addition, however, the current for one segment will be normalized to its maximum, and the normalized values along with the relative strength in dB will be printed in a table. If the currents for more than one segment are being printed, only currents from the last segment in the group appear in the normalized table.

3 — only normalized currents from one segment are printed for the receiving pattern case.

IPTAG (I2) — Tag number of the segments for which currents will be printed.

IPTAGF (I3) — Equal to m, specifies the m^{th} segment of the set of segments having the tag numbers of IPTAG, at which printing of currents starts. If IPTAG is zero or blank, then IPTAGF refers to an absolute segment number. If IPTAGF is blank, the current is printed for all segments.

IPTAGT (I4) — Equal to n, specifies the n^{th} segment of the set of segments having tag numbers of IPTAG. Currents are printed for segments having tag number IPTAG starting at the m^{th} segment in the set and ending at the n^{th} segment. If IPTAG is zero or blank, then IPTAGF and IPTAGT refer to absolute segment numbers. If IPTAGT is left blank, it is set equal to IPTAGF.

Radiation Pattern (RP)

Purpose: To specify radiation pattern sampling parameters and to cause program execution. Options for a field computation include a radial wire ground screen, a cliff, or surface-wave fields.

Card:

2	5	10	15	20	30	40	50	60	70	80
RP	I1	I2	I3	I4	F1	F2	F3	F4	F5	F6
		NTH	NPH	XNDA	THETS	PHIS	DTH	DPH	RFLD	GNOR

The numbers along the top refer to the last column in each field.

Parameters:

Integers

(I1) — This integer selects the mode of calculation for the radiated field. Some values of (I1) will affect the meaning of the remaining parameters on the card. Options available for I1 are:

0 — normal mode. Space-wave fields are computed. An infinite ground plane is included if it has been specified previously on a GN card; otherwise, antenna is in free space.

1 — surface wave propagating along ground is added to the normal space wave. This option changes the meaning of some of the other parameters on the RP card as explained below, and the results appear in a special output format. Ground parameters must have been input on a GN card.

The following options cause calculation of only the space wave but with special ground conditions. Ground conditions include a two medium ground (cliff) where the media join in a circle or a line, and a radial wire ground screen. Ground parameters and dimensions must be input

on a GN or GD card before the RP card is read. The RP card only selects the option for inclusion in the field calculation. (Refer to the GN and GD cards for further explanation.)

2 — linear cliff with antenna above upper level. Lower medium parameters are as specified for the second medium on the GN card or on the GD card.


3 — circular cliff centered at origin of coordinate system with antenna above upper level. Lower medium parameters are as specified for the second medium on the GN card or on the GD card.

4 — radial wire ground screen centered at origin.

5 — both radial wire ground screen and linear cliff.

6 — both radial wire ground screen and circular cliff.

The field point is specified in spherical coordinates (R, θ, ϕ), illustrated in figure 18, except when the surface wave is computed. For computing the surface-wave field (I1 = 1), cylindrical coordinates (ρ, ϕ, z) are used to accurately define points near the ground plane at large radial distances. The RP card allows automatic stepping of the field point to compute the field over a region about the antenna at uniformly spaced points. The integers I2 and I3 and floating point numbers F1, F2, F3 and F4 control the field-point stepping.

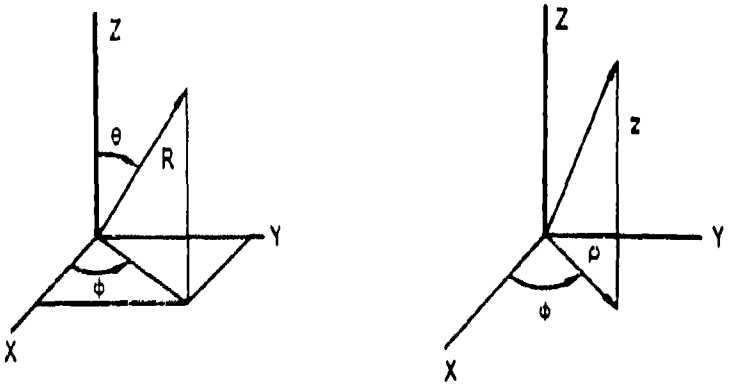

Spherical coordinates Cylindrical coordinates

Figure 18. Coordinates for Radiated Field.

NTH (I2) — Number of values of theta (θ) at which the field is to be computed (number of values of z for I1 = 1).

NPH (I3) — Number of values of phi (φ) at which field is to be computed. The total number of field points requested by the card is NTH × NPH. If I2 or I3 is left blank, a value of one will be assumed.

XNDA (I4) — This optional integer consists of four independent digits in columns 17, 18, 19 and 20, each having a different function. The mnemonic XNDA is not a variable name in the program. Rather, each letter represents a mnemonic for the corresponding digit in I4. If I1 = 1, then I4 has no effect and should be left blank.

X — (column 17) controls output format.
X = 0 major axis, minor axis and total gain printed.
X = 1 vertical, horizontal and total gain printed.

N — (column 18) causes normalized gain for the specified field points to be printed after the standard gain output. The number of field points for which the normalized gain can be printed is limited by an array dimension in the program. In the demonstration program, the limit is 600 points. If the number of field points exceeds this limit, the remaining points will be omitted from the normalized gain. The gain may be normalized to its maximum or to a value input in field F6. The type of gain that is normalized is determined by the value of N as follows:

N = 0 no normalized gain.
= 1 major axis gain normalized.
= 2 minor axis gain normalized.
= 3 vertical axis gain normalized.
= 4 horizontal axis gain normalized.
= 5 total gain normalized.

D — (column 19) selects either power gain or directive gain for both standard printing and normalization. If the structure excitation is an incident plane wave, the quantities printed under the heading "gain" will actually

be the scattering cross section (σ/λ^2) and will not be affected by the value of D. The column heading for the output will still read "power" or "directive gain," however.

D = 0 power gain.

D = 1 directive gain.

A — (column 20) requests calculation of average power gain over the region covered by field points.

A = 0 no averaging.

A = 1 average gain computed.

A = 2 average gain computed, printing of gain at the field points used for averaging is suppressed.

If NTH or NPH is equal to one, average gain will not be computed for any value of A since the area of the region covered by field points vanishes.

Floating Point Numbers

THETS (F1) — Initial theta angle in degrees (initial z coordinate in meters if I1 = 1).

PHIS (F2) — Initial phi angle in degrees.

DTH (F3) — Increment for theta in degrees (increment for z in meters if I1 = 1).

DPH (F4) — Increment for phi in degrees.

RFLD (F5) — Radial distance (R) of field point from the origin in meters. RFLD is optional. If it is blank, the radiated electric field will have the factor exp(-jkR)/R omitted. If a value of R is specified, it should represent a point in the far-field region since near components of the field cannot be obtained with an RP card. (If I1 = 1, then RFLD represents the cylindrical coordinate ρ in meters and is not optional. It must be greater than about one wavelength.)

GNOR (F6) — Determines the gain normalization factor if normalization has been requested in the I4 field. If GNOR is blank or zero, the gain will be normalized to its maximum value. If GNOR is not zero, the gain will be normalized to the value of GNOR.


Notes:

- The RP card will initiate program execution, causing the interaction matrix to be computed and factored and the structure currents to be computed if these operations have not already been performed. Hence, all required input parameters must be set before the RP card is read.
- At a single frequency, any number of RP cards may occur in sequence so that different field-point spacings may be used over different regions of space. If automatic frequency stepping is being used (i.e., NFRQ on the FR card is greater than one), only one RP card will act as data inside the loop. Subsequent cards will calculate patterns at the final frequency.
- When both NTH and NPH are greater than one, the angle theta (or Z) will be stepped faster than phi.
- When a ground plane has been specified, field points should not be requested below the ground (θ greater than 90 degrees or Z less than zero).

Transmission Line (TL)

Purpose: To generate a transmission line between any two points on the structure. Characteristic impedance, length, and shunt admittance are the defining parameters.

Card:

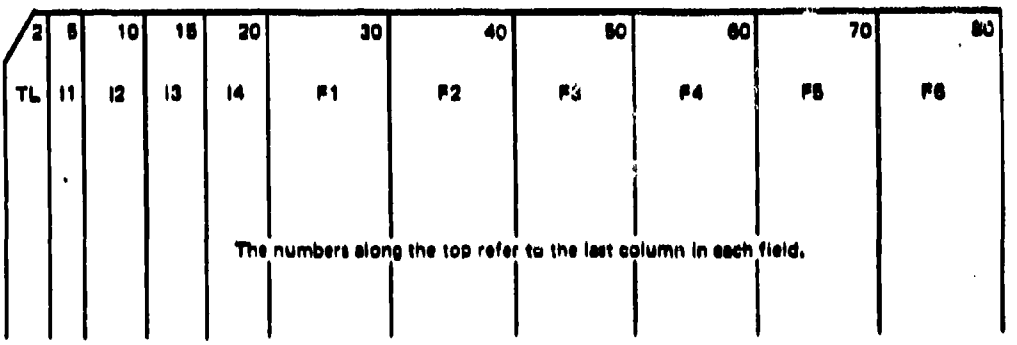

Parameters:

Integers — (the integer specifications are identical to those on the network (NT) card.)

Floating Point

(F1) — The characteristic impedance of the transmission line in ohms. A negative sign in front of the characteristic impedance will act as a flag for generating the transmission line with a 180° phase reversal (crossed line) if this is desired.

(F2) — The length of transmission line in meters. If this field is left blank, the program will use the straight line distance between the specified connection points.

The remaining four floating-point fields are used to specify the real and imaginary parts of the shunt admittances at end one and two, respectively.

(F3) — Real part of the shunt admittance in mhos at end one.

(F4) — Imaginary part of the shunt admittance in mhos at end one.

(F5) — Real part of the shunt admittance in mhos at end two

(F6) — Imaginary part of the shunt admittance in mhos at end two.


Notes:

- The rules for transmission line cards are the same as for network cards. All transmission line cards for a particular transmission line configuration must occur together with no other cards (except NT cards) separating them. When the first TL or NT card is read following a card other than a TL or NT card, all previous network or transmission line data are destroyed. Hence, if a set of TL cards is to be modified, all transmission line and network data must be input again in the modified form. Dimensions in the program limit the number of cards in a group that may be specified. In the NEC demonstration deck, the number of two-port networks (specified by NT cards and TL cards) is limited to thirty, and the number of different segments having network ports connected to them is limited to thirty.
- One or more networks (including transmission lines) may be connected to any given segment. Multiple network ports connected to one segment are connected in parallel.
- If a transmission line is connected to a segment that has been impedance loaded (i.e., through the use of an LD card), the load acts in series with the line.
- Use of transmission line cards (TL) after any form of execute requires the recalculation of the current only, and does not require recalculation of the matrix.
- NT and TL cards do not affect symmetry.

Write NGF File (WG)

Purpose: To write a NGF file for a structure on the file TAPE20.

Card:

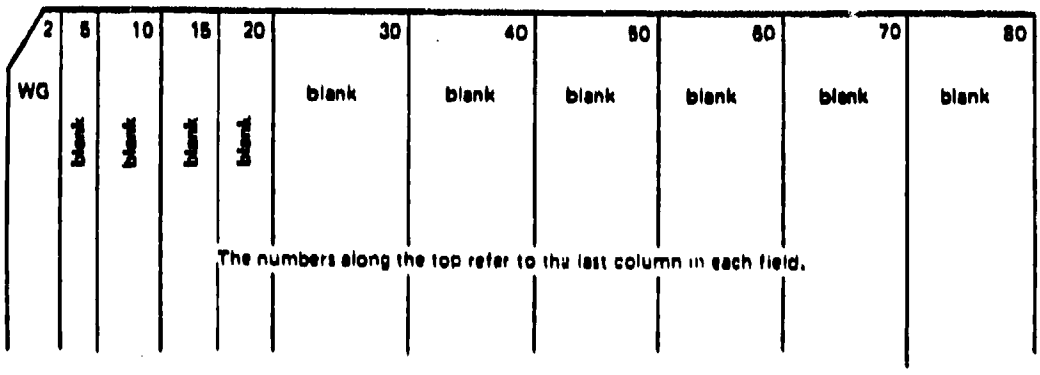

Parameters: None


Notes:

- See section III-5.

Execute (XQ)

Purpose: To cause program execution at points in the data stream where execution is not automatic. Options on the card also allow for automatic generation of radiation patterns in either of two vertical cuts.

Card:

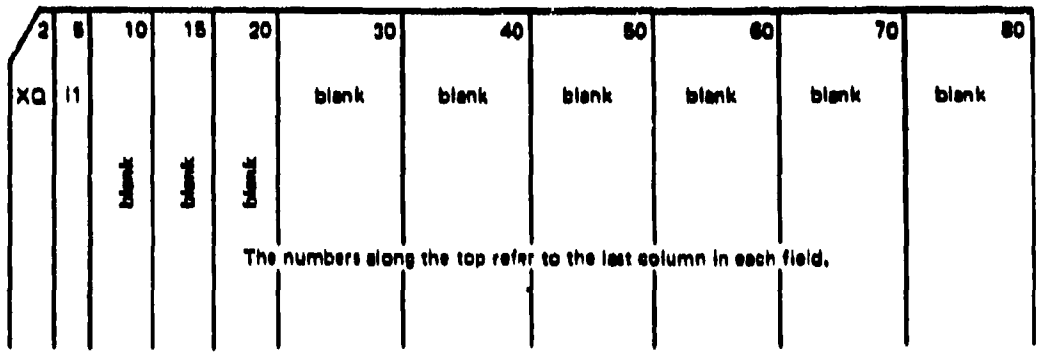

Parameters:

Integers

(I1) — Options controlled by (I1) are:

0 — no patterns requested (normal case).

1 — generates a pattern cut in the XZ plane, i.e., $\phi = 0°$ and θ varies from 0° to 90° in 1° steps.

2 — generates a pattern cut in the YZ plane, i.e., $\phi = 90°$ θ varies from 0° to 90° in 1° steps.

3 — generates both of the cuts described for the values 1 and 2.

The remainder of the card is blank.

Notes:

- For the case of a single frequency step, four cards will automatically produce program execution (i.e., the program stops reading data and proceeds with the calculations requested to that point); the four cards are the execute card (XQ), the near-field cards (NE,NH), and the radiation-pattern card (RP). Thus, the only time the XQ card is mandatory, for the case of one frequency, is when only currents and impedances for the structure are desired. On the other hand, for the case of automatic frequency stepping, only the XQ card and the RP

card cause execution. Thus, if only near-fields or currents are desired, the XQ card is mandatory to cause execution. Furthermore, the XQ card can always be used as a divider in the data after a card which produces an execute. For instance, if the user wished to put a blank XQ card after an RP card to more easily divide the data into execution groups, the XQ card will act as a do-nothing card.

- The radiation-pattern generation option of the XQ card must not be used when a radial wire ground screen or a second medium has been specified. For these cases, the RP card is used where the presence of the additional ground parameters is indicated.

4. SOMNEC INPUT FOR SOMMERFELD/NORTON GROUND METHOD

When the Sommerfeld/Norton ground option is requested on the GN card, NEC reads interpolation tables from the file TAPE21. This file must be created prior to the NEC run by running the separate program SOMNEC. SOMNEC reads a single data card with the parameters:

EPR, SIG, FMHZ, IPT (format 3E10.3, I5)

The three decimal numbers end in columns 10, 20, and 30 and the integer IPT must end in column 35. The parameters are:

EPR = relative dielectric constant of ground (ε_r)
SIG = conductivity of ground in mhos/m (σ)
FMHZ = frequency in MHz
IPT = 1 to print the interpolation tables
= 0 for no printed output.

The interpolation tables depend only on the complex dielectric constant

$$\varepsilon_c = \varepsilon_r - j\frac{\sigma}{\omega\varepsilon_o} ,$$

$$\varepsilon_r = \text{EPR} , \quad \sigma = \text{SIG} .$$

If SIG is input as a negative number, the program sets

$$\varepsilon_c = \text{EPR} - j|\text{SIG}| ,$$

and frequency is not used. The tables are written on the file TAPE21. The central processor time to generate the tables on a CDC 7600 computer is about 15 seconds.

5. THE NUMERICAL GREEN'S FUNCTION OPTION

With the Numerical Green's Function (NGF) option, a fixed structure and its environment may be modeled and the factored interaction matrix saved on a file. New parts may then be added to the model in subsequent computer runs and the complete solution obtained without repeating calculations for the data on the file. The main purpose of the NGF is to avoid unnecessary repetition of calculations when a part of a model, such as a single antenna in a complex environment, will be modified one or more times while the environment remains fixed. For example, when modeling antennas on ships,

several antenna designs or locations may be considered on an otherwise unchanged ship. With the NGF, the self-interaction matrix for the fixed environment may be computed, factored for solution, and saved on a tape or disk file. Solution for a new antenna then requires only the evaluation of the self-interaction matrix for the antenna, the mutual antenna-to-environment interactions, and matrix manipulations for a partitioned-matrix solution. When the previously written NGF file is used, the free space Green's function in the NEC formulation is, in effect, replaced by the Green's function for the environment.

Another reason for using the NGF option is to exploit partial symmetry in a structure. In a single run, a structure must be perfectly symmetric for NEC to use symmetry in the solution. Any unsymmetric segments or patches, or ones that lie in a symmetry plane or on the axis of rotation, will destroy the symmetry. Such partial symmetry may be exploited to reduce solution time by running the symmetric part of the model first and writing a NGF file. The unsymmetric parts may then be added in a second run.

Use of the NGF option may also be warranted for large, time-consuming models to save an expensive result for further use. Without adding new antennas, it may be used with a new excitation or to compute new radiation, near-field, or coupling data not computed in the original run.

To write a NGF file for a structure, the data deck is constructed as for a normal run. After the GE card, the frequency, ground parameters, and loading may be set by FR, GN, and LD cards. EK or KH may also be used. Other cards, such as EX or NT that do not change the matrix, will not affect the NGF and will not be saved on the file. After the model has been defined, a WG card is used to fill and factor the matrix and cause the NGF data to be written to the file TAPE20. TAPE20 should be saved after the run terminates. Other cards may follow the WG card to define an excitation and request field calculations as in a normal run. WG should be the first card to request filling and factoring of the matrix, however, since it reserves array space for the matrix in subsequent runs when the NGF is used. Hence, WG should come before XQ, RP, NE, or NH. The FR card must not specify multiple frequencies when a NGF is written.

To use a previously generated NGF file, the file is made available to the program as TAPE20. The first structure-geometry data card, following the CE card, must be a GF card to cause the program to read TAPE20. Subsequent

structure data cards define the new structure to be added to the NGF structure. All types of structure geometry data cards may be used although GM, GR, GX, and GS will affect new structure but not that from the NGF file. GR and GX will have their usual effect on the new structure but will not result in use of symmetry in the solution. Symmetry may be used in writing the NGF file but not for new structure used with the NGF.

For connections between the new structure and NGF structure, the new segment ends or patch centers are made to coincide with the NGF segment ends or patch centers as in a normal run. The rules still apply that only a single segment may connect to a given patch and a segment may have a patch connection on only one of its ends. Also, a wire may never connect to a patch formed by subdividing another patch for a previous connection.

Following the GE card the program control cards may be used as usual, with the exception that FR and GN cards may not be used. The parameters from these cards are taken from the NGF file and cannot be changed. LD cards may be used to load new segments but not segments in the NGF. If integers I3 and I4 on a LD card are blank, the card will load all new segments (new segments with tag LDTAG if I2 is not zero) but not NGF segments. If I2, I3 and I4 select a specific NGF segment, the run will terminate with an error message. The effect of loading on NGF segments may be obtained with a NT card, since NT (and TL) may connect to either new or NGF segments.

Computation time for a run using a NGF file may be estimated from the formulas in section V by evaluating the time to run the complete structure and subtracting time to fill and factor the matrix for the NGF part of the structure alone (T_1 and T_2). If the new structure connects to the NGF structure, new unknowns — in addition to those for the new segments and patches — are produced and should be included in the time estimate for the complete structure. If a new segment or patch connects to a NGF segment, the current expansion function for the NGF segment is modified. One new unknown is then added to the matrix equation to represent the modified expansion function and suppress the old expansion function. If a new segment connects to a NGF patch, 10 new unknowns are produced in addition to that for the new segment. Four new patches are automatically generated at the connection point accounting for eight unknowns. The remaining two new unknowns are needed to suppress the current on the old patch that has been replaced.

Although connection to a NGF segment modifies the old basis function, the current on the segment will be printed in its normal location in the table of segment currents. When a new wire connects to a NGF patch, the patch is divided into four new patches that will appear after the user-defined patches in the patch data. The original patch will be listed in the tables but with nearly zero current. Also, the Z coordinate of the original patch will be set to 9999.

Section IV
NEC Output

Typical NEC output is illustrated in this section with examples that exercise most of the options available. In addition to demonstrating the use of the code and typical output, the results may be used to check the operation of the code when it is put in use on a new computer system. Most of the output is self-explanatory. The general form is outlined below, the particular points are discussed with the examples in which they occur.

The output follows the form of the input data, starting with the descriptive comments, followed by geometry data and then requested computations. Under the heading "STRUCTURE SPECIFICATION" is a list of the geometry data cards. The heading on the table is for a GW card, giving the X, Y, and Z coordinates of the wire ends, the radius, and the number of segments. Under the heading "WIRE NO." is a count of the number of GW cards. Data from other geometry cards are printed in the table with a label identifying the card. For a patch, the patch number is printed under "WIRE NO." followed by a letter to indicate the shape option — P for arbitrary, R for rectangular, T for triangular, and Q for quadrilateral.

After a GE card is read, a summary of the number of segments and patches is printed. The symmetry flag is zero for no symmetry, positive for planar symmetry, and negative for rotational symmetry. A table of multiple-wire junctions lists all junctions at which three or more wires join. The number of each connected segment is printed preceded by a minus sign if the current reference direction is out of the junction.

Data for individual segments are printed under "SEGMENTATION DATA," including angles, α and β, which are defined the same as for the patch normal vector (see figure 5). The connection data show the connection condition at each segment. "I-" is the number of the segment connected to the first end of segment I. If more than one segment connects to this junction, then I- will be the first connected segment following I in the sequence of segments. The numbers under "I+" give the same information for the second end of segment I. If the connection number is positive, the reference directions of the connected segments are parallel. If the number is negative, they are opposed (first end to first end, or second end to second end). A zero indicates a free wire end, while if it is equal to I, that end of segment I is connected

to a ground plane. If I± is greater than 10,000, the end is connected to a surface and (I±) - 10,000 is the number of the first of the four patches around the connection point.

When patches are used, the next section is "SURFACE PATCH DATA." This includes the coordinates of the patch center, components of the unit normal vector, and patch area. Components of the unit tangent vectors, $\hat{t}_1$ and $\hat{t}_2$, (see Section II) are also printed for use in reading the surface currents printed later.

The data cards following the geometry cards are printed exactly as they are read by the program. When a card requesting computations is encountered, information on ground parameters and loading is printed, followed by currents. The line "APPROXIMATE INTEGRATION..." gives the separation distance, set by a KH card, at which the Hertzian dipole approximation is used for the electric field due to a segment. If the extended thin-wire kernel has been requested by an EK card, this is also noted at this point in the output. Under "MATRIX TIMING" is printed the time to fill and factor the interaction matrix.

If one or more voltage sources have been specified, the voltage, current, impedance, admittance and input power are printed for each driving point. If the voltage source is the current-slope-discontinuity type, this is noted by "*" after the tag number in the input parameters table (see example 2). The antenna input parameters are followed by a table giving the current at the center of each segment. This table includes the coordinates at the segment centers and segment lengths in units of wavelength. If the model includes patches, a table of patch currents is printed giving the surface current in components along the tangent vectors $\hat{t}_1$ and $\hat{t}_2$ and in X, Y, and Z components.

If there are voltage sources on a model, a power budget is printed following the current tables. The input power here is the total power supplied by all voltage sources. The structure loss is ohmic loss in wires, while the network loss is the total power into all network and transmission line ports, assuming no radiation from networks or transmission lines. Finally, the radiated power is computed as input power minus structure and network loss.

Radiated fields or near-fields requested in the input data are printed following the current tables. In the normal radiation-pattern format, transmitting antenna gains are printed in dB in the components requested on

the RP card. If an incident-field excitation is used, rather than a voltage source, the gain columns will contain the bistatic scattering cross section (σ/λ^2). For very small gains, the number -999.99 is printed.

The radiation-pattern format also includes the radiated electric field in θ and ϕ components. These are labeled with the units "volts/m" for $E(R, \theta, \phi)$. Unless the range, R, is specified on the RP card, however, the quantity printed is the limit of $RE(R, \theta, \phi)$ as R approaches infinity, having units of volts. The polarization is printed in a format for general elliptic polarization, including axial ratio (minor axis/major axis), tilt angle of the major axis (η in figure 14), and sense of rotation (right-hand, left-hand, or linear).

In addition to these basic formats, there are a number of special formats for optional calculations. Many of these occur in the following examples.

EXAMPLES 1 THROUGH 4

Examples 1 through 4 are simple cases intended to illustrate the basic formats. Example 1 includes a calculation of near-electric-field along the wire. When the field is computed at the center of a segment without an applied field or loading, the Z-component of electric field is small since the solution procedure enforces the boundary condition at these points. This is a check that the program is operating correctly. The values would be still smaller if the field points were more precisely at the segment centers. The radial, or X, components of the near-field can also be compared with the charge densities at the segment centers ($\rho = 2\pi a\, \varepsilon_o\, E_x$). If the fields were computed along the wire axis, the radial field would be set to zero. For a nonplanar structure, however, computation along the axis is the only way to reproduce the conditions of the current solution and obtain small fields at the match points.

In example 2 the wire has an even number of segments so that a charge-discontinuity voltage source can be used at the center. The symbol "*" in the table of antenna input parameters is a reminder that this type of source has been used. Three frequencies are run for this case and the EX card option is used to collect and normalize the input impedances. At the end of example 2 the wire is given the conductivity of aluminum. This has a significant effect since the wire is relatively thin.

Example 3 is a vertical dipole over ground. Since the wire is thick, the extended thin-wire approximation has been used. Computation of the average power gain is requested on the RP cards. Over a perfectly conducting ground the average power gain should be 2. The computed result differs by about 1.5%, probably due to the 10-degree steps used in integrating the radiated power. For a more complex structure, the average gain can provide a check on the accuracy of the computed input impedance over a perfect ground where it should equal 2 or in free space where it should equal 1. Example 3 also includes a finitely conducting ground where the average gain of 0.72 indicates that only 36% of the power leaving the antenna is going into the space wave. The formats for normalized gain and the combined space-wave and ground-wave fields are illustrated. At the end of example 3, the wire is excited with an incident wave at 10-degree angles and the PT card option is used to print receiving antenna patterns.

Example 4 includes both patches and wires. Although the structure is over a perfect ground, the average power gain is 1.8. This indicates that the input impedance is inaccurate, probably due to the crude patch model used for the box. Since there is no ohmic loss, a more accurate input resistance can be obtained as

$$\text{Radiated power} = 1/2 \text{ (avg. gain)} \times \text{(computed input power)}$$
$$= 1.016\ (10^{-3})\ \text{W}$$
$$\text{Radiation resistance} = 2 \text{ (radiated power)}/|I_{\text{source}}|^2$$
$$= 162.6 \text{ ohms.}$$

Since the input power used in computing the gains in the radiation pattern table is too large by 0.46 dB, the gains can be corrected by adding this factor.

Examples 1 through 4 Input

```
CEEXAMPLE 1.  CENTER FED LINEAR ANTENNA
GW        7   0.        0.        -.25      0.        0.        .25       .001
GE
EX  0     0   4    0    1.
XQ
LD  0     0   4    4    10.       3.000E-09 5.300E-11
FQ
NE  0     1   1   15    .001      0.        0.        0.        0.        .01786
NX
CMEXAMPLE 2.  CENTER FED LINEAR ANTENNA.
CM            CURRENT SLOPE DISCONTINUITY SOURCE.
CM            1. THIN PERFECTLY CONDUCTING WIRE
CE            2. THIN ALUMINUM WIRE
GW  0     8   0.        0.        -.25      0.        0.        .25       .00001
GE
FR  0     3   0    0    200.      90.
EX  5     0   5    1    1.        0.        90.
XQ
LD  5     0   0    0 3.750E+07
FR  0     1   0    0    300.
EX  5     0   5    0    1.
XQ
NX
CMEXAMPLE 3.  VERTICAL HALF WAVELENGTH ANTENNA OVER GROUND
CM            EXTENDED THIN WIRE KERNEL USED
CM            1. PERFECT GROUND
CM            2. IMPERFECT GROUND INCLUDING GROUND WAVE AND RECEIVING
CE               PATTERN CALCULATIONS
GW        9   0.        0.        2.        0.        0.        7.        .3
GE  1
EK
FR        1             30.
EX  0     0   5    0    1.
GN  1
RP  0     10  2 1301    0.        0.        10.       90.
GN                      6.        1.000E-03
RP  0     10  2 1301    0.        0.        10.       90.
RP  1     10  1         1.        0.        2.        0.        1.000E+05
EX  1     10  1         0.        0.        0.        10.
PT  2     0   9    5
XQ
NX
CEEXAMPLE 4.  T ANTENNA ON A BOX OVER PERFECT GROUND
SP            .1        .05       .05       0.        0.        .01
SP            .05       .1        .05       0.        90.       .01
GX      110
SP            0.        0.        1         90.       0.        .04
GW  1     4   0.        0.        1         0         0.        .3        .001
GW  2     2   0.        0.        .3        .15       0.        .3        .001
GW  3     2   0.        0         .3        -.15      0.        .3        .001
GE  1
GN  1
EX        1   1         1.
RP        10  4 1001    0.        0.        10.       30.
EN
```

Examples 1 through 4 Output

```
                    ************************************

                      NUMERICAL ELECTROMAGNETICS CODE

                    ************************************


                            - - - - COMMENTS - - - -

                      EXAMPLE 1.  CENTER FED LINEAR ANTENNA


                          - - - STRUCTURE SPECIFICATION - - -

                              COORDINATES MUST BE INPUT IN
                              METERS OR BE SCALED TO METERS
                              BEFORE STRUCTURE INPUT IS ENDED

 WIRE                                                                  NO. OF   FIRST  LAST   TAG
 NO.        X1          Y1          Z1          X2          Y2          Z2       RADIUS  SEG.    SEG.   SEG.   NO.
    1    0.          0.         -0.25000     0.          0.          0.25000   0.00100     7       1      7     -0

  TOTAL SEGMENTS USED=    7     NO. SEG. IN A SYMMETRIC CELL=    7     SYMMETRY FLAG=  0


        - MULTIPLE WIRE JUNCTIONS -
 JUNCTION    SEGMENTS (- FOR END 1, + FOR END 2)
 NONE


                          - - - - SEGMENTATION DATA - - - -

                              COORDINATES IN METERS

                      (- AND (+ INDICATE THE SEGMENTS BEFORE AND AFTER (

 SEG.    COORDINATES OF SEG. CENTER      SEG.      ORIENTATION ANGLES      WIRE     CONNECTION DATA     TAG
 NO.        X          Y          Z      LENGTH      ALPHA      BETA     RADIUS    (-     (     (+     NO.
    1    0.          0.         -0.21429  0.07143   90.00000    0.      0.00100     0     1     2     -0
    2    0.          0.         -0.14286  0.07143   90.00000    0.      0.00100     1     2     3     -0
    3    0.          0.         -0.07143  0.07143   90.00000    0.      0.00100     2     3     4     -0
    4    0.          0.          0.00000  0.07143   90.00000    0.      0.00100     3     4     5     -0
    5    0.          0.          0.07143  0.07143   90.00000    0.      0.00100     4     5     6     -0
    6    0.          0.          0.14286  0.07143   90.00000    0.      0.00100     5     6     7     -0
    7    0.          0.          0.21429  0.07143   90.00000    0.      0.00100     6     7     0     -0



***** DATA CARD NO.  1  EX  0    0    4    0  1.00000E+00  0.          0          0.          0.          0.
***** DATA CARD NO.  2  XQ  -0   -0   -0   -0  0           0          0.         0.          0.          0.


                            - - - - - - FREQUENCY - - - - - -

                              FREQUENCY= 2.99800+08 MHZ
                              WAVELENGTH= 1.00000+00 METERS


                    APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN  1.000 WAVELENGTHS APART
```

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE

- - - MATRIX TIMING - - -

FILL= 0.021 SEC., FACTOR= 0.001 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG.	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
-0	4	1.000000E+00	0.	9.209695E-03	-9.194742E-03	5.269795E+01	4.630600E+01	9.209695E-03	-9.194742E-03	4.602984E-03

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	CURRENT (AMPS) REAL	IMAG.	MAG.	PHASE
1	-0	0.	0.	-0.2143	0.07143	2.359?E-03	-1.8881E-03	3.0210E-03	-38.684
2	-0	0.	0.	-0.1429	0.07143	5.9999E-03	-4.0463E-03	7.2367E-03	-33.986
3	-0	0.	0.	-0.0714	0.07143	8.3711E-03	-5.1957E-03	9.8472E-03	-31.777
4	-0	0.	0.	0.0000	0.07143	9.2096E-03	-5.1947E-03	1.0571E-02	-29.246
5	-0	0.	0.	0.0714	0.07143	8.3711E-03	-5.1957E-03	9.8472E-03	-31.777
6	-0	0.	0.	0.1429	0.07143	5.9999E-03	-4.0463E-03	7.2367E-03	-33.986
7	-0	0.	0.	0.2143	0.07143	2.3597E-03	-1.8881E-03	3.0210E-03	-38.684

- - - POWER BUDGET - - -

INPUT POWER = 4.602984E-03 WATTS
RADIATED POWER= 4.602984E-03 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

***** DATA CARD NO.	3	LD	0	0	4	4	1.000000E+01	3.000000E-09	5.300000E-11	0.	0.	0.
***** DATA CARD NO.	4	PQ	-0	-0	-0	-0	0.	0.	0.	0.	0.	0.
***** DATA CARD NO.	5	NE	0	1	1	15	1.000000E-03	0.	0.	0.	0.	1.796000E-02

- - - STRUCTURE IMPEDANCE LOADING - - -

LOCATION TAG FROM	LOCATION THRU	RESISTANCE OHMS	INDUCTANCE HENRYS	CAPACITANCE FARADS	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAGINARY	CONDUCTIVITY MHOS/METER	TYPE
4	4	1.0000E+01	3.0000E-09	5.3000E-11				SERIES

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE

- - - MATRIX TIMING - - -

FILL= 0.021 SEC., FACTOR= 0.001 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG.	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
-0	4	0.0000E+00	0.	8.9946E-03	-4.0914E-03	8.2697E+01	4.1940E+01	8.9946E-03	-4.0914E-03	4.4773E-03

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	-0	0.	0.	-0.2143	0.0714	2.3241E-03	-1.3780E-03	2.7024E-03	-30.682
2	-0	0.	0.	-0.1429	0.0714	5.0808E-03	-3.2778E-03	6.7413E-03	-28.083
3	-0	0.	0.	-0.0714	0.0714	8.1824E-03	-4.1467E-03	9.1731E-03	-26.875
4	-0	0.	0.	0.0000	0.0714	8.9947E-03	-4.0819E-03	9.8799E-03	-24.344
5	-0	0.	0.	0.0714	0.0714	8.1824E-03	-4.1467E-03	9.1731E-03	-26.875
6	-0	0.	0.	0.1429	0.0714	5.0808E-03	-3.2778E-03	6.7413E-03	-28.083
7	-0	0.	0.	0.2143	0.0714	2.3241E-03	-1.3780E-03	2.7024E-03	-30.682

- - - CHARGE DENSITIES - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG LENGTH	CHARGE DENSITY (COULOMBS/METER) REAL	IMAG.	MAG.	PHASE
1	-0	0	0.	-0.2143	0.0714	1.0292E-11	3.1761E-11	3.0659E-11	60.061
2	-0	0.	0.	-0.1429	0.0714	1.0429E-11	2.2040E-11	2.4383E-11	64.678
3	-0	0.	0.	-0.0714	0.0714	2.1140E-12	1.1638E-11	1.1829E-11	79.705
4	-0	0.	0.	0.0000	0.0714	5.1804E-19	2.3814E-19	5.8008E-19	24.730
5	-0	0.	0.	0.0714	0.0714	-2.1140E-12	-1.1638E-11	1.1829E-11	-100.295
6	-0	0.	0.	0.1429	0.0714	-1.0429E-11	-2.2040E-11	2.4383E-11	-115.324
7	-0	0.	0.	0.2143	0.0714	-1.0292E-11	-3.1761E-11	3.0659E-11	-110.939

- - - POWER BUDGET - - -

INPUT POWER = 4.4773E-03 WATTS
RADIATED POWER= 3.9943E-03 WATTS
STRUCTURE LOSS= 4.8300E-04 WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 89.21 PERCENT

- - - NEAR ELECTRIC FIELDS - - -

LOCATION X METERS	Y METERS	Z METERS	EX MAGNITUDE VOLTS/M	EX PHASE DEGREES	EY MAGNITUDE VOLTS/M	EY PHASE DEGREES	EZ MAGNITUDE VOLTS/M	EZ PHASE DEGREES
0.0010	0.	0.	1.0228E-05	84.74	0.	0.	1.3042E+01	-179.10
0.0010	0.	0.0179	5.5442E+01	-66.31	0.	0.	1.2837E+01	-179.09
0.0010	0.	0.0357	1.0968E+02	-67.15	0.	0.	8.7271E+00	-179.46
0.0010	0.	0.0536	1.5608E+02	-68.85	0.	0.	8.4338E-01	-179.75
0.0010	0.	0.0714	2.1267E+02	-100.30	0.	0.	4.2135E-04	-8.13
0.0010	0.	0.0893	2.7147E+02	-106.86	0.	0.	3.4497E-01	-8.87
0.0010	0.	0.1072	3.2920E+02	-111.08	0.	0.	8.8000E-01	82.83
0.0010	0.	0.1250	3.8592E+02	-113.51	0.	0.	2.2076E-01	74.41
0.0010	0.	0.1429	4.3835E+02	-115.33	0.	0.	3.0905E-04	-84.14
0.0010	0.	0.1607	4.8563E+02	-116.77	0.	0.	2.1937E-01	-108.41
0.0010	0.	0.1786	5.2800E+02	-117.97	0.	0.	1.9790E+00	97.97
0.0010	0.	0.1965	5.6564E+02	-118.98	0.	0.	3.3113E+00	58.83
0.0010	0.	0.2143	5.9880E+02	-119.84	0.	0.	9.9958E-03	-121.84
0.0010	0.	0.2322	6.2766E+02	-120.57	0.	0.	1.0880E+01	-121.68
0.0010	0.	0.2500	6.5236E+02	-121.19	0.	0.	3.8032E+02	-121.43

***** DATA CARD NO. 6 NX -0 -0 -0 -0 0 0 0. 0. 0 0

```
**********************************

NUMERICAL ELECTROMAGNETICS CODE

**********************************
```

- - - - COMMENTS - - - -

EXAMPLE 2. CENTER FED LINEAR ANTENNA.
CURRENT SLOPE DISCONTINUITY SOURCE.
1. THIN PERFECTLY CONDUCTING WIRE
2. THIN ALUMINUM WIRE

- - - STRUCTURE SPECIFICATION - - -

COORDINATES MUST BE INPUT IN
METERS OR BE SCALED TO METERS
BEFORE STRUCTURE INPUT IS ENDED

WIRE NO.	XI	YI	ZI	XF	YF	ZF	RADIUS	NO. OF SEG.	FIRST SEG.	LAST SEG.	TAG NO.
1	0.	0.	-0.25000	0.	0.	0.25000	0.00001	8	1	8	0

TOTAL SEGMENTS USED= 8 NO. SEG. IN A SYMMETRIC CELL= 0 SYMMETRY FLAG= 0

- MULTIPLE WIRE JUNCTIONS -
JUNCTION SEGMENTS (- FOR END 1, + FOR END #1)
NONE

- - - - SEGMENTATION DATA - - - -

COORDINATES IN METERS

(+ AND (- INDICATE THE SEGMENTS BEFORE AND AFTER (

SEG. NO.	COORDINATES OF SEG. CENTER X	Y	Z	SEG. LENGTH	ORIENTATION ANGLES ALPHA	BETA	WIRE RADIUS	CONNECTION DATA (-	(	(+	TAG NO.
1	0.	0.	-0.21875	0.06250	90.00000	0.	0.00001	0	1	2	0
2	0.	0.	-0.15625	0.06250	90.00000	0.	0.00001	1	2	3	0
3	0.	0.	-0.09375	0.06250	90.00000	0.	0.00001	2	3	4	0
4	0.	0.	-0.03125	0.06250	90.00000	0.	0.00001	3	4	5	0
5	0.	0.	0.03125	0.06250	90.00000	0.	0.00001	4	5	6	0
6	0.	0.	0.09375	0.06250	90.00000	0.	0.00001	5	6	7	0
7	0.	0.	0.15625	0.06250	90.00000	0.	0.00001	6	7	8	0
8	0.	0.	0.21875	0.06250	90.00000	0.	0.00001	7	8	0	0

***** DATA CARD NO. 1	FR	0	3	0	0	2.00000E+02	5.00000E+01	0.	0.	0.	0.
***** DATA CARD NO. 2	EX	5	0	5	1	1.00000E+00	0.	5.00000E+01	0.	0.	0.
***** DATA CARD NO. 3	XQ	-0	-0	-0	-0	0.	0.	0.	0.	0.	0.

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 2.0000E+02 MHZ
WAVELENGTH= 1.4990E+00 METERS

APPROXIMATE INTERPOLATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE

- - - MATRIX TIMING - - -

FILL= 0.027 SEC., FACTOR= 0.002 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	IMAG.	CURRENT (AMPS) REAL	IMAG.	IMPEDANCE (OHMS) REAL	IMAG.	ADMITTANCE (MHOS) REAL	IMAG.	POWER (WATTS)
0	5	1.000000E+00	0.	6.040618E-05	1.979344E-03	2.697682E+01	-8.826806E+02	6.040618E-05	1.979344E-03	3.320318E-05

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	0	0.	0.	-0.1459	0.04168	1.9768E-05	2.9220E-04	2.9267E-04	86.013
2	0	0.	0.	-0.1042	0.04168	3.9866E-05	7.0589E-04	7.0702E-04	86.760
3	0	0.	0.	-0.0625	0.04168	5.6673E-05	1.1008E-03	1.1023E-03	87.093
4	0	0.	0.	-0.0208	0.04168	6.5714E-05	1.4319E-03	1.4334E-03	87.388
5	0	0.	0.	0.0208	0.04168	6.5714E-05	1.4319E-03	1.4334E-03	87.388
6	0	0.	0.	0.0625	0.04168	5.6673E-05	1.1008E-03	1.1023E-03	87.093
7	0	0.	0.	0.1042	0.04168	3.9866E-05	7.0589E-04	7.0702E-04	86.760
8	0	0.	0.	0.1459	0.04168	1.9768E-05	2.9220E-04	2.9267E-04	86.013

- - - POWER BUDGET - - -

INPUT POWER = 3.3203E-05 WATTS
RADIATED POWER= 3.3203E-05 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 2.5000E+02 MHZ
WAVELENGTH= 1.1992E+00 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE

- - - MATRIX TIMING - - -

FILL= 0.027 SEC., FACTOR= 0.002 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG.	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
0	5	1.00000E+00	0.	6.16884E-04	3.96468E-03	4.71431E+01	-2.72372E+02	6.16884E-04	3.96468E-03	3.08492E-04

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	0	0.	0.	-0.1824	0.03212	1.38286E-04	8.4701E-04	8.6120E-04	78.106
2	0	0.	0.	-0.1303	0.03212	3.8168E-04	1.7863E-03	1.8259E-03	78.083
3	0	0.	0.	-0.0782	0.03212	5.2215E-04	2.7057E-03	2.7557E-03	78.077
4	0	0.	0.	-0.0261	0.03212	6.0627E-04	3.3503E-03	3.4047E-03	78.743
5	0	0.	0.	0.0261	0.03212	6.0627E-04	3.3503E-03	3.4047E-03	78.743
6	0	0.	0.	0.0782	0.03212	5.2215E-04	2.7057E-03	2.7557E-03	78.077
7	0	0.	0.	0.1303	0.03212	3.8168E-04	1.7863E-03	1.8259E-03	78.083
8	0	0.	0.	0.1824	0.03212	1.38286E-04	8.4701E-04	8.6120E-04	78.106

- - - POWER BUDGET - - -

INPUT POWER = 3.0849E-04 WATTS
RADIATED POWER= 3.0849E-04 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 3.0000E+02 MHZ
WAVELENGTH= 9.9933E-01 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE

- - - MATRIX TIMING - - -

FILL= 0.027 SEC., FACTOR= 0.002 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO	SEG. NO	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG.	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
0	5	1.00000E+00	0.	9.39012E-03	-5.32909E-03	8.00511E+01	4.57144E+01	9.39012E-03	-5.32909E-03	4.69506E-03

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	0	0.	0.	-0.2189	0.08294	1.9807E-03	-1.2798E-03	2.3419E-03	-33.139
2	0	0.	0.	-0.1564	0.08294	9.3917E-03	-3.4033E-03	8.3422E-03	-32.494
3	0	0.	0.	-0.0938	0.08294	7.8678E-03	-4.8421E-03	9.2384E-03	-31.610
4	0	0.	0.	-0.0313	0.08294	9.2168E-03	-5.4147E-03	1.0690E-02	-30.433
5	0	0.	0.	0.0313	0.08294	9.2168E-03	-5.4147E-03	1.0690E-02	-30.433
6	0	0.	0.	0.0938	0.08294	7.8678E-03	-4.8421E-03	9.2384E-03	-31.610
7	0	0.	0.	0.1564	0.08294	9.3917E-03	-3.4033E-03	8.3422E-03	-32.494
8	0	0.	0.	0.2189	0.08294	1.9807E-03	-1.2798E-03	2.3419E-03	-33.139

- - - POWER BUDGET - - -

INPUT POWER = 4.6981E-03 WATTS
RADIATED POWER= 4.6981E-03 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

- - - INPUT IMPEDANCE DATA - - -
SOURCE SEGMENT NO. 9
NORMALIZATION FACTOR= 5.00000E+01

FREQ. MHZ	UNNORMALIZED IMPEDANCE RESISTANCE OHMS	REACTANCE OHMS	MAGNITUDE OHMS	PHASE DEGREES	NORMALIZED IMPEDANCE RESISTANCE	REACTANCE	MAGNITUDE	PHASE DEGREES
200.000	2.6578E+01	-6.3206E+02	6.3261E+02	-87.59	5.3156E-01	-1.2641E+01	1.2652E+01	-87.59
250.000	4.7143E+01	-2.7237E+02	2.7642E+02	-80.18	9.4286E-01	-5.4474E+00	5.5284E+00	-80.18
300.000	8.0581E+01	4.5714E+01	9.2619E+01	29.59	1.6116E+00	9.1428E-01	1.8524E+00	29.59

***** DATA CARD NO.	4	LD	5	0	0	0	3.72000E+07	0		0.	0.	0.	0.
***** DATA CARD NO.	5	FR	0	1	0	0	3.00000E+02	0.		0.	0.	0.	0.
***** DATA CARD NO.	6	EX	5	0	5	0	1.00000E+00	0.		0.	0.	0.	0.
***** DATA CARD NO	7	XQ	-0	-0	-0	-0	0	0		0.	0.	0.	0.

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 3.0000E+02 MHZ
WAVELENGTH= 9.9933E-01 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

LOCATION ITAG FROM	THRU	RESISTANCE OHMS	INDUCTANCE HENRYS	CAPACITANCE FARADS	IMPEDANCE (OHMS) REAL	IMAGINARY	CONDUCTIVITY MHOS/METER	TYPE
ALL							3.7200E+07	WIRE

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE

- - - MATRIX TIMING - - -

FILL= 0.027 SEC., FACTOR= 0.002 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG NO	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG.	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
0	5	1.00000E+00	0.	6.84431E-03	-3.86630E-03	1.18430E+02	6.69278E+01	6.84431E-03	-3.86630E-03	3.32219E-03

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	0	0.	0.	-0.2188	0.08294	1.3862E-03	-8.6305E-04	1.6879E-03	-34.780
2	0	0.	0.	-0.1564	0.08294	3.7848E-03	-2.3548E-03	4.5863E-03	-34.018
3	0	0.	0.	-0.0938	0.08294	5.9658E-03	-3.6091E-03	6.9736E-03	-32.661
4	0	0.	0.	-0.0313	0.08294	6.9219E-03	-3.8782E-03	7.9368E-03	-31.384
5	0	0.	0.	0.0313	0.08294	6.9219E-03	-3.8782E-03	7.9368E-03	-31.384
6	0	0.	0.	0.0938	0.08294	5.9658E-03	-3.6091E-03	6.9736E-03	-32.661
7	0	0.	0.	0.1564	0.08294	3.7848E-03	-2.3548E-03	4.5863E-03	-34.018
8	0	0.	0.	0.2188	0.08294	1.3862E-03	-8.6305E-04	1.6879E-03	-34.780

- - - POWER BUDGET - - -

INPUT POWER = 3.3222E-03 WATTS
RADIATED POWER= 2.4402E-03 WATTS
STRUCTURE LOSS= 8.8199E-04 WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 73.45 PERCENT

***** DATA CARD NO. 8 NX -0 -0 -0 -0 0. 0. 0. 0. 0. 0

****

NUMERICAL ELECTROMAGNETICS CODE

****

- - - - COMMENTS - - - -

EXAMPLE 3. VERTICAL HALF WAVELENGTH ANTENNA OVER GROUND
EXTENDED THIN WIRE KERNEL USED
1. PERFECT GROUND
2. IMPERFECT GROUND INCLUDING GROUND WAVE AND RECEIVING
PATTERN CALCULATIONS

- - - - STRUCTURE SPECIFICATION - - - -

COORDINATES MUST BE INPUT IN
METERS OR BE SCALED TO METERS
BEFORE STRUCTURE INPUT IS ENDED

WIRE NO.	X1	Y1	Z1	X2	Y2	Z2	RADIUS	NO. OF SEG.	FIRST SEG.	LAST SEG.	TAG NO
1	0.	0.	2.00000	0.	0.	7.00000	0.30000	9	1	9	-0

GROUND PLANE SPECIFIED.

WHERE WIRE ENDS TOUCH GROUND, CURRENT WILL BE INTERPOLATED TO IMAGE IN GROUND PLANE.

TOTAL SEGMENTS USED= 9 NO. SEG IN A SYMMETRIC CELL= 9 SYMMETRY FLAG= 0

- MULTIPLE WIRE JUNCTIONS -
JUNCTION SEGMENTS (- FOR END 1, + FOR END 2)
NONE

- - - - SEGMENTATION DATA - - - -

COORDINATES IN METERS

(+ AND (- INDICATE THE SEGMENTS BEFORE AND AFTER (

SEG. NO	COORDINATES OF SEG. CENTER X	Y	Z	SEG. LENGTH	ORIENTATION ANGLES ALPHA	BETA	WIRE RADIUS	CONNECTION DATA (-	(	(+	TAG NO.
1	0.	0.	2.27778	0.55556	90.00000	0.	0.30000	0	1	2	-0
2	0	0.	2.83333	0.55556	90.00000	0.	0.30000	1	2	3	-0
3	0.	0.	3.38889	0.55556	90.00000	0.	0.30000	2	3	4	-0
4	0	0.	3.94444	0.55556	90.00000	0	0.30000	3	4	5	-0
5	0.	0.	4.50000	0.55556	90.00000	0	0.30000	4	5	6	-0
6	0	0.	5.05556	0.55556	90.00000	0	0.30000	5	6	7	-0
7	0.	0.	5.61111	0.55556	90.00000	0.	0.30000	6	7	8	-0
8	0	0.	6.16667	0.55556	90.00000	0	0.30000	7	8	9	-0
9	0.	0.	6.72222	0.55556	90.00000	0.	0.30000	8	9	0	-0

***** DATA CARD NO. 1	EK	-0	-0	-0	-0	0.	0.	0.	0.	0.	0.
***** DATA CARD NO. 2	FR	-0	1	-0	-0	3.00000E+01	0.	0.	0.	0.	0.
***** DATA CARD NO. 3	EX	0	0	5	0	1.00000E+00	0.	0.	0.	0.	0.
***** DATA CARD NO. 4	GN	1	-0	-0	-0	0.	0.	0.	0.	0.	0.
**** DATA CARD NO. 5	RP	0	10	2	1301	0.	0.	1.00000E+01	9.00000E+01	0.	0.

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 3.0000E+01 MHZ
WAVELENGTH= 9.9933E+00 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

THE EXTENDED THIN WIRE KERNEL WILL BE USED

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
PERFECT GROUND

- - - MATRIX TIMING - - -

FILL= 0.049 SEC., FACTOR= 0.003 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG.	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
-0	9	1.000000E+00	0.	9.314626E-03	-9.668963E-04	1.094386E+02	9.909468E+00	9.314626E-03	-9.668963E-04	4.657312E-03

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	-0	0.	0.	0.2278	0.05556	2.0000E-03	-2.9964E-03	3.6000E-03	-41.673
2	-0	0.	0.	0.2833	0.05556	5.9184E-03	-4.8028E-03	8.0348E-03	-37.304
3	-0	0.	0.	0.3391	0.05556	7.4811E-03	-4.8595E-03	8.9139E-03	-31.908
4	-0	0.	0.	0.3947	0.05556	8.7867E-03	-3.7800E-03	9.5653E-03	-23.277
5	-0	0.	0.	0.4503	0.05556	9.3148E-03	-8.8888E-04	9.3548E-03	-5.317
6	-0	0.	0.	0.5059	0.05556	9.0040E-03	-3.8010E-03	9.7734E-03	-22.997
7	-0	0.	0.	0.5615	0.05556	7.8825E-03	-4.0996E-03	9.1349E-03	-30.814
8	-0	0.	0.	0.6171	0.05556	5.9682E-03	-4.2264E-03	7.3034E-03	-35.389
9	-0	0.	0.	0.6727	0.05556	3.2218E-03	-2.8004E-03	4.1403E-03	-34.908

- - - POWER BUDGET - - -

INPUT POWER = 4.6573E-03 WATTS
RADIATED POWER= 4.6573E-03 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

- - - RADIATION PATTERNS - - -

- - ANGLES - - THETA DEGREES	PHI DEGREES	- POWER GAINS - VERT. DB	HOR. DB	TOTAL DB	- - - POLARIZATION - - - AXIAL RATIO	TILT DEG.	SENSE	- - - E(THETA) - - - MAGNITUDE VOLTS/M	PHASE DEGREES	- - - E(PHI) - - - MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	-999.99	-999.99	-999.99	0.	0.		0.	0.	0.	0.
10.00	0.	-9.87	-999.99	-9.87	0.	0.	LINEAR	1.696406E-01	-114.38	0.	0.
20.00	0.	-4.21	-999.99	-4.21	0.	0.	LINEAR	3.256506E-01	-114.64	0.	0.
30.00	0.	-1.70	-999.99	-1.70	0.	0.	LINEAR	4.343776E-01	-115.01	0.	0.
40.00	0.	-1.74	-999.99	-1.74	0.	0.	LINEAR	4.323946E-01	-115.37	0.	0.
50.00	0.	-6.73	-999.99	-6.73	0.	0.	LINEAR	2.435096E-01	-115.33	0.	0.
60.00	0.	-10.04	-999.99	-10.04	0.	0.	LINEAR	1.663016E-01	81.67	0.	0.
70.00	0.	2.67	-999.99	2.67	0.	0.	LINEAR	7.189536E-01	82.56	0.	0.
80.00	0.	7.20	-999.99	7.20	0.	0	LINEAR	1.211016+00	82.51	0.	0.
90.00	0.	8.52	-999.99	8.52	0.	0.	LINEAR	1.409676+00	82.47	0.	0.
0.	90.00	-999.99	-999.99	-999.99	0.	0.		0.	0.	0.	0.
10.00	90.00	-9.87	-999.99	-9.87	0.	0	LINEAR	1.696406E-01	-114.38	0.	0
20.00	90.00	-4.21	-999.99	-4.21	0.	0.	LINEAR	3.256506E-01	-114.64	0.	0
30.00	90.00	-1.70	-999.99	-1.70	0.	0.	LINEAR	4.343776E-01	-115.01	0.	0
40.00	90.00	-1.74	-999.99	-1.74	0.	0.	LINEAR	4.323946E-01	-115.37	0.	0.
50.00	90.00	-6.73	-999.99	-6.73	0.	0.	LINEAR	2.435096E-01	-115.33	0.	0.

60.00	90.00	-10.04	-999.99	-10.04	0	0.	LINEAR	1.6630IE-01	61.67	0.	0.
70.00	90.00	2.67	-999.99	2.67	0.	0.	LINEAR	7.1899IE-01	62.56	0.	0.
80.00	90.00	7.20	-999.99	7.20	0.	0.	LINEAR	1.2110IE+00	62.51	0.	0.
90.00	90.00	8.52	-999.99	8.52	0	0.	LINEAR	1.4096?E+00	62.47	0	0.

AVERAGE POWER GAIN= 2.0279?E+00 SOLID ANGLE USED IN AVERAGING=(0.9000)(PI) STERADIANS.

- - - - NORMALIZED GAIN - - - -

VERTICAL GAIN
NORMALIZATION FACTOR = -8.92 DB

- - ANGLES - - THETA DEGREES	PHI DEGREES	GAIN DB	- - ANGLES - - THETA DEGREES	PHI DEGREES	GAIN DB	- - ANGLES - - THETA DEGREES	PHI DEGREES	GAIN DB
0.	0.	-1000.91	70.00	0.	-5.89	40.00	90.00	-10.27
10.00	0.	-18.39	80.00	0.	-1.32	50.00	90.00	-15.25
20.00	0.	-12.73	90.00	0.	0.	60.00	90.00	-18.06
30.00	0.	-10.23	0.	90.00	-1000.91	70.00	90.00	-4.89
40.00	0.	-10.27	10.00	90.00	-18.39	80.00	90.00	-1.32
50.00	0.	-15.25	20.00	90.00	-12.73	90.00	90.00	0.
60.00	0.	-18.06	30.00	90.00	-10.23			

***** DATA CARD NO.	6	GN	-0	-0	-0	-0	6.00000E+00	1.00000E-03	0.	0.	0.	0.
***** DATA CARD NO.	7	RP	0	10	2	1301	0.	0.	1.00000E+01	8.00000E+01	0.	0.

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FINITE GROUND, REFLECTION COEFFICIENT APPROXIMATION
RELATIVE DIELECTRIC CONST.= 6.000
CONDUCTIVITY= 1.000E-03 MHOS/METER
COMPLEX DIELECTRIC CONSTANT= 6.00000E+00-6.99200E-01

- - - MATRIX TIMING - - -

FILL= 0.053 SEC , FACTOR= 0.003 SEC

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG NO.	VOLTAGE (VOLTS) REAL	IMAG	CURRENT (AMPS) REAL	IMAG	IMPEDANCE (OHMS) REAL	IMAG	ADMITTANCE (MHOS) REAL	IMAG	POWER (WATTS)
-0	5	1.00000E+00	0	8.91202E-03	-8.82892E-04	1.11117E+02	1.10081E+01	8.91202E-03	-8.82892E-04	4.45801E-03

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG NO.	TAG NO.	COORD. OF SEG CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG	MAG.	PHASE
1	-0	0.	0.	0.2279	0.05559	2.0768E-03	-2.9728E-03	3.6269E-03	-41.807
2	-0	0.	0.	0.2835	0.05559	5.4154E-03	-4.1894E-03	6.8467E-03	-37.726
3	-0	0.	0.	0.3391	0.05559	7.2728E-03	-4.6627E-03	8.6391E-03	-32.686
4	-0	0.	0.	0.3947	0.05559	8.4698E-03	-3.7953E-03	9.2810E-03	-24.137
5	-0	0.	0	0.4503	0.05559	8.9120E-03	-8.8209E-04	8.9557E-03	-5.658
6	-0	0.	0.	0.5059	0.05559	8.5570E-03	-3.8095E-03	9.3668E-03	-23.991
7	-0	0.	0.	0.5615	0.05559	7.4273E-03	-4.6836E-03	8.7807E-03	-32.235
8	-0	0.	0.	0.6171	0.05559	5.5943E-03	-4.2089E-03	7.0005E-03	-36.994
9	-0	0.	0.	0.6727	0.05559	3.0094E-03	-2.5815E-03	3.9649E-03	-40.623

- - - POWER BUDGET - - -

INPUT POWER = 4.4560E-03 WATTS
RADIATED POWER= 4.4560E-03 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

- - - RADIATION PATTERNS - - -

- - ANGLES - - THETA DEGREES	PHI DEGREES	- POWER GAINS - VERT. DB	HOR. DB	TOTAL DB	- - - POLARIZATION - - - AXIAL RATIO	TILT DEG.	SENSE	- - - E(THETA) - - - MAGNITUDE VOLTS/M	PHASE DEGREES	- - - E(PHI) - - - MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	-999.99	-999.99	-999.99	0.	0.		0.	0.	0.	0.
10.00	0.	-12.87	-999.99	-12.87	0.	0.	LINEAR	1.1747E-01	-124.70	0.	0.
20.00	0.	-7.18	-999.99	-7.18	0.	0.	LINEAR	2.2614E-01	-128.91	0.	0.
30.00	0.	-4.47	-999.99	-4.47	0.	0.	LINEAR	3.0887E-01	-137.31	0.	0.
40.00	0.	-3.45	-999.99	-3.45	0.	0.	LINEAR	3.4727E-01	-153.41	0.	0.
50.00	0.	-2.84	-999.99	-2.84	0.	0.	LINEAR	3.6843E-01	177.07	0.	0.
60.00	0.	-0.78	-999.99	-0.78	0.	0.	LINEAR	4.7183E-01	142.08	0.	0.
70.00	0.	1.84	-999.99	1.84	0.	0.	LINEAR	6.1889E-01	120.37	0.	0.
80.00	0.	0.84	-999.99	0.84	0.	0.	LINEAR	5.8647E-01	110.41	0.	0.
90.00	0.	-999.99	-999.99	-999.99	0.	0.		2.8048E-11	-72.99	0.	0.
0.	90.00	-999.99	-999.99	-999.99	0.	0.		0.	0.	0.	0.
10.00	90.00	-12.87	-999.99	-12.87	0.	0.	LINEAR	1.1747E-01	-124.70	0.	0.
20.00	90.00	-7.18	-999.99	-7.18	0.	0.	LINEAR	2.2614E-01	-128.91	0.	0.
30.00	90.00	-4.47	-999.99	-4.47	0.	0.	LINEAR	3.0887E-01	-137.31	0.	0.
40.00	90.00	-3.45	-999.99	-3.45	0.	0.	LINEAR	3.4727E-01	-153.41	0.	0.
50.00	90.00	-2.84	-999.99	-2.84	0.	0.	LINEAR	3.6843E-01	177.07	0.	0.
60.00	90.00	-0.78	-999.99	-0.78	0.	0.	LINEAR	4.7183E-01	142.08	0.	0.
70.00	90.00	1.84	-999.99	1.84	0.	0.	LINEAR	6.1889E-01	120.37	0.	0.
80.00	90.00	0.84	-999.99	0.84	0.	0.	LINEAR	5.8647E-01	110.41	0.	0.
90.00	90.00	-999.99	-999.99	-999.99	0.	0.		2.8048E-11	-72.99	0.	0.

AVERAGE POWER GAIN= 7.2070IE-01 SOLID ANGLE USED IN AVERAGING= (0.9000)*PI STERADIANS.

- - - - NORMALIZED GAIN - - - -

VERTICAL GAIN
NORMALIZATION FACTOR = 1.84 DB

- - ANGLES - - THETA DEGREES	PHI DEGREES	GAIN DB
0	0.	-1001.83
10.00	0.	-14.41
20.00	0.	-9.72
30.00	0.	-6.01
40.00	0.	-4.99
50.00	0.	-4.48
60.00	0.	-2.33
70.00	0.	0.
80.00	0.	-0.90
90.00	0.	-1001.83
0.	90.00	-1001.83
10.00	90.00	-14.41
20.00	90.00	-9.72
30.00	90.00	-6.01
40.00	90.00	-4.99
50.00	90.00	-4.48
60.00	90.00	-2.33
70.00	90.00	0.
80.00	90.00	-0.90
90.00	90.00	-1001.83

***** DATA CARD NO 8 RP 1 10 1 -0 1.000000E+00 0. 2.000000E+00 0. 1.000000E+05 0.

- - - RADIATED FIELDS NEAR GROUND - - -

- - - LOCATION - - - RHO METERS	PHI DEGREES	Z METERS	- - E(THETA) - - MAG VOLTS/M	PHASE DEGREES	- - E(PHI) - - MAG VOLTS/M	PHASE DEGREES	- - E(RADIAL) - - MAG VOLTS/M	PHASE DEGREES
100000.00	0.	1.00	2.3956E-09	142.08	0.	0.	8.5944E-10	-46.48
100000.00	0.	3.00	2.7218E-09	164.43	0.	0.	8.9834E-10	-46.48
100000.00	0.	5.00	3.3943E-09	-179.80	0.	0.	8.5895E-10	-46.48
100000.00	0.	7.00	4.1558E-09	-169.95	0.	0.	8.5915E-10	-46.48
100000.00	0.	9.00	5.0468E-09	-162.74	0.	0.	8.5906E-10	-46.47
100000.00	0.	11.00	5.9459E-09	-158.05	0.	0.	8.5896E-10	-46.47
100000.00	0.	13.00	6.9550E-09	-154.65	0.	0.	8.5877E-10	-46.48
100000.00	0.	15.00	7.9495E-09	-152.09	0.	0.	8.5877E-10	-46.48
100000.00	0.	17.00	8.9495E-09	-150.09	0.	0.	8.5868E-10	-46.50
100000.00	0.	19.00	9.9511E-09	-148.51	0.	0.	8.5850E-10	-46.52

***** DATA CARD NO. 9 EX 1 10 1 -0 0 0. 0. 1.00000E+01 0. 0.
***** DATA CARD NO. 10 PT 2 0 5 5 0. 0. 0. 0. 0. 0.
***** DATA CARD NO. 11 XQ -0 -0 -0 -0 0. 0. 0. 0. 0. 0.

- - - RECEIVING PATTERN PARAMETERS - - -
ETA= 0. DEGREES
TYPE =LINEAR
AXIAL RATIO=-0.

THETA (DEG)	PHI (DEG)	- CURRENT - MAGNITUDE	PHASE	SEG NO.
0.	0.	0.	0.	5
10.00	0.	6.2309E-03	-34.68	5
20.00	0.	1.1997E-02	-38.90	5
30.00	0.	1.6399E-02	-47.38	5
40.00	0.	1.8430E-02	-63.41	5
50.00	0.	1.9958E-02	-82.93	5
60.00	0.	2.5058E-02	-127.84	5
70.00	0.	3.2788E-02	-148.63	5
80.00	0.	2.9955E-02	-168.59	5
90.00	0.	1.4152E-12	17.01	5

- - - NORMALIZED RECEIVING PATTERN - - -
NORMALIZATION FACTOR= 3.2788E-02
ETA= 0. DEGREES
TYPE =LINEAR
AXIAL RATIO=-0.
SEGMENT NO.= 5

THETA (DEG)	PHI (DEG)	- PATTERN - DB	MAGNITUDE
0.	0.	-999.99	0.
10.00	0.	-14.42	1.9018E-01
20.00	0.	-8.73	3.6814E-01
30.00	0.	-6.02	5.0017E-01
40.00	0.	-5.00	5.6248E-01
50.00	0.	-4.48	5.9691E-01
60.00	0.	-2.33	7.6476E-01
70.00	0.	0.00	1.0000E+00
80.00	0.	-0.90	9.0201E-01
90.00	0.	-207.88	4.3191E-11

***** DATA CARD NO. 12 NX -0 -0 -0 -0 0. 0. 0. 0. 0. 0.

```
**********************************

   NUMERICAL ELECTROMAGNETICS CODE

**********************************
```

- - - - COMMENTS - - - -

EXAMPLE 4. T ANTENNA ON A BOX OVER PERFECT GROUND

- - - STRUCTURE SPECIFICATION - - -

COORDINATES MUST BE INPUT IN
METERS OR BE SCALED TO METERS
BEFORE STRUCTURE INPUT IS ENDED

WIRE NO.		X1	Y1	Z1	X2	Y2	Z2	RADIUS	NO. OF SEG.	FIRST SEG.	LAST SEG.	TAG NO.
	IP	0.10000	0.05000	0.05000	0.	0.	0.01000					
	2P	0.05000	0.10000	0.05000	0.	90.00000	0.01000					
	STRUCTURE REFLECTED ALONG THE AXES X Y , TAGS INCREMENTED BY -0											
	BP	0.	0.	0.10000	90.00000	0.	0.04000					
	1	0.	0.	0.10000	0.	0.	0.30000	0.00100	4	1	4	1
	2	0.	0.	0.30000	0.15000	0.	0.30000	0.00100	2	5	6	2
	3	0.	0.	0.30000	-0.15000	0.	0.30000	0.00100	2	7	8	3

GROUND PLANE SPECIFIED.

WHERE WIRE ENDS TOUCH GROUND, CURRENT WILL BE INTERPOLATED TO IMAGE IN GROUND PLANE.

TOTAL SEGMENTS USED= 8 NO. SEG. IN A SYMMETRIC CELL= 8 SYMMETRY FLAG= 0
TOTAL PATCHES USED= 12 NO. PATCHES IN A SYMMETRIC CELL= 12

- MULTIPLE WIRE JUNCTIONS -
(- FOR END 1, + FOR END 2)

JUNCTION	SEGMENTS		
1	4	-5	-7

- - - - SEGMENTATION DATA - - - -

COORDINATES IN METERS

1+ AND 1- INDICATE THE SEGMENTS BEFORE AND AFTER I

SEG. NO.	COORDINATES OF SEG. CENTER X	Y	Z	SEG. LENGTH	ORIENTATION ANGLES ALPHA	BETA	WIRE RADIUS	CONNECTION DATA 1-	I	I+	TAG NO.
1	0.	0.	0.12500	0.05000	90.00000	0.	0.00100	10000	1	2	1
2	0.	0.	0.17500	0.05000	90.00000	0.	0.00100	1	2	3	1
3	0.	0.	0.22500	0.05000	90.00000	0.	0.00100	2	3	4	1
4	0	0.	0.27500	0.05000	90.00000	0.	0.00100	3	4	5	1
5	0.03750	0.	0.30000	0.07500	0.	0.	0.00100	-7	5	6	2
6	0.11250	0.	0.30000	0.07500	0.	0.	0.00100	5	6	0	2
7	-0.03750	0.	0.30000	0.07500	0.	180.00000	0.00100	4	7	8	3
8	-0.11250	0.	0.30000	0.07500	0.	180.00000	0.00100	7	8	0	3

- - - SURFACE PATCH DATA - - -

COORDINATES IN METERS

PATCH NO.	COORD. OF PATCH CENTER X	Y	Z	UNIT NORMAL VECTOR X	Y	Z	PATCH AREA	COMPONENTS OF UNIT TANGENT VECTORS X1	Y1	Z1	X2	Y2	Z2
1	0.10000	0.05000	0.05000	1.0000	0.	0.	0.01000	-0.	1.0000	0.	0.	0.	1.0000
2	0.05000	0.10000	0.05000	-0.0000	1.0000	0.	0.01000	-1.0000	-0.0000	0.	0.	0.	1.0000
3	0.10000	-0.05000	0.05000	1.0000	0.	0.	0.01000	-0.	-1.0000	0.	0.	-0.	1.0000
4	0.05000	-0.10000	0.05000	-0.0000	-1.0000	0.	0.01000	-1.0000	0.0000	0.	0.	-0.	1.0000
5	-0.10000	0.05000	0.05000	-1.0000	0.	0.	0.01000	0.	1.0000	0.	-0.	0.	1.0000
6	-0.05000	0.10000	0.05000	0.0000	1.0000	0.	0.01000	1.0000	-0.0000	0.	-0.	0.	1.0000
7	-0.10000	-0.05000	0.05000	-1.0000	0.	0.	0.01000	0.	-1.0000	0.	-0.	-0.	1.0000
8	-0.05000	-0.10000	0.05000	0.0000	-1.0000	0.	0.01000	1.0000	0.0000	0.	-0.	-0.	1.0000

9	0.05000	0.05000	0.10000	0.	0.	1.0000	0.01000	1.0000	0.	0.	0.	1.0000	0.
10	-0.05000	0.05000	0.10000	0.	0.	1.0000	0.01000	1.0000	0.	0.	0.	1.0000	0.
11	-0.05000	-0.05000	0.10000	0.	0.	1.0000	0.01000	1.0000	0.	0.	0.	1.0000	0.
12	0.05000	-0.05000	0.10000	0.	0.	1.0000	0.01000	1.0000	0.	0.	0.	1.0000	0.

***** DATA CARD NO	1	GN	1	-0	-0	-0	0.	0.	0.	0.	0.	0.	0.
***** DATA CARD NO	2	EX	-0	1	1	-0	1.00000E+00	0.	0.	0.	0.	0.	0.
***** DATA CARD NO.	3	RP	-0	10	4	1001	0.	0.	1.00000E+01	3.00000E+01	0.	0	

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 2.9980E+02 MHZ
WAVELENGTH= 1.0000E+00 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
PERFECT GROUND

- - - MATRIX TIMING - - -

FILL= 0.132 SEC., FACTOR= 0.082 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG.	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
1	1	1.00000E+00	0.	2.25809E-03	-2.71947E-03	1.80787E+02	2.17854E+02	2.25809E-03	-2.71947E-03	1.12904E-03

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	1	0.	0.	0.1250	0.05000	2.2581E-03	-2.7195E-03	3.5346E-03	-50.296
2	1	0.	0.	0.1750	0.05000	2.2309E-03	-3.4898E-03	4.1418E-03	-57.409
3	1	0.	0.	0.2250	0.05000	2.1622E-03	-3.9058E-03	4.4643E-03	-61.032
4	1	0.	0.	0.2750	0.05000	2.0278E-03	-3.8953E-03	4.3918E-03	-62.800
5	2	0.0375	0.	0.3000	0.07500	8.1382E-04	-1.5860E-03	1.7826E-03	-62.836
6	2	0.1125	0.	0.3000	0.07500	3.2208E-04	-6.4890E-04	7.2443E-04	-63.804
7	3	-0.0375	0.	0.3000	0.07500	8.1382E-04	-1.5860E-03	1.7826E-03	-62.836
8	3	-0.1125	0.	0.3000	0.07500	3.2208E-04	-6.4890E-04	7.2443E-04	-63.804

- - - - SURFACE PATCH CURRENTS - - - -

DISTANCE IN WAVELENGTHS
CURRENT IN AMPS/METER

PATCH CENTER			- - SURFACE COMPONENTS - - TANGENT VECTOR 1		TANGENT VECTOR 2		- - - RECTANGULAR COMPONENTS - - - X		Y		Z	
X	Y	Z	MAG.	PHASE	MAG.	PHASE	REAL	IMAG.	REAL	IMAG.	REAL	IMAG
1												
0.100	0.050	0.050	1.2095E-03	111.80	8.4058E-03	-118.75	0.	0.	-4.91E-04	1.12E-03	-3.65E-03	-7.97E-03
2												
0.050	0.100	0.050	1.2018E-03	-68.27	8.2434E-03	-118.57	-4.45E-04	1.12E-03	-8.27E-19	5.71E-19	-3.69E-03	-7.37E-03
3												
0.100	-0.050	0.050	1.2095E-03	111.80	8.4058E-03	-118.75	0.	0.	4.91E-04	-1.12E-03	-3.65E-03	-7.97E-03
4												
0.050	-0.100	0.050	1.2018E-03	-68.27	8.2434E-03	-118.57	-4.45E-04	1.12E-03	8.27E-19	-5.71E-19	-3.69E-03	-7.37E-03
5												
-0.100	0.050	0.050	1.2095E-03	111.80	8.4058E-03	-118.75	0.	0.	-4.91E-04	1.12E-03	-3.65E-03	-7.97E-03
6												
-0.050	0.100	0.050	1.2018E-03	-68.27	8.2434E-03	-118.57	4.45E-04	-1.12E-03	-8.27E-19	5.71E-19	-3.69E-03	-7.37E-03
7												
-0.100	-0.050	0.050	1.2095E-03	111.80	8.4058E-03	-118.75	0.	0.	4.91E-04	-1.12E-03	-3.65E-03	-7.97E-03
8												
-0.050	-0.100	0.050	1.2018E-03	-68.27	8.2434E-03	-118.57	4.45E-04	-1.12E-03	8.27E-19	-5.71E-19	-3.69E-03	-7.37E-03
9												
0.050	0.050	0.100	8.8792E-03	111.78	8.7774E-03	111.82	-2.99E-03	8.48E-03	-2.92E-03	8.29E-03	0.	0.
10												
-0.050	0.050	0.100	8.8792E-03	-68.22	8.7774E-03	111.82	2.99E-03	-8.48E-03	-2.92E-03	8.29E-03	0.	0.
11												
-0.050	-0.050	0.100	8.8792E-03	-68.22	8.7774E-03	-68.18	2.99E-03	-8.48E-03	2.92E-03	-8.29E-03	0.	0.
12												
0.050	-0.050	0.100	8.8792E-03	111.78	8.7774E-03	-68.18	-2.99E-03	8.48E-03	2.92E-03	-8.29E-03	0.	0.

- - - POWER BUDGET - - -

INPUT POWER = 1.1290E-03 WATTS
RADIATED POWER= 1.1290E-03 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

- - - RADIATION PATTERNS - - -

- - ANGLES - - THETA DEGREES	PHI DEGREES	- POWER GAINS - VERT. DB	HOR. DB	TOTAL DB	- - - POLARIZATION - - - AXIAL RATIO	TILT DEG.	SENSE	- - - E(THETA) - - - MAGNITUDE VOLTS/M	PHASE DEGREES	- - - E(PHI) - - - MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	-999.99	-999.99	-999.99	0.	0.		5.78075E-15	-97.74	1.47886E-16	148.31
10.00	0.	-13.76	-999.99	-13.76	0.00000	-0.00	LINEAR	5.33571E-02	-7.95	2.19958E-16	158.20
20.00	0.	-7.53	-999.99	-7.53	0.00000	-0.00	LINEAR	1.08308E-01	-9.63	2.92407E-16	167.91
30.00	0.	-3.71	-999.99	-3.71	0.00000	-0.00	LINEAR	1.69877E-01	-2.91	3.87399E-16	-176.42
40.00	0.	-0.90	-999.99	-0.90	0.00000	-0.00	LINEAR	2.34570E-01	0.05	1.74491E-16	159.44
50.00	0.	1.28	-999.99	1.28	0.00000	-0.00	LINEAR	3.01472E-01	2.82	1.69409E-16	165.96
60.00	0.	2.94	-999.99	2.94	0.00000	-0.00	LINEAR	3.69093E-01	5.11	7.38348E-17	123.69
70.00	0.	4.12	-999.99	4.12	0.00000	-0.00	LINEAR	4.18288E-01	6.79	1.64652E-16	172.88
80.00	0.	4.83	-999.99	4.83	0.00000	-0.00	LINEAR	4.53811E-01	7.80	8.18903E-17	180.00
90.00	0.	5.07	-999.99	5.07	0.	0.	LINEAR	4.66309E-01	8.13	0.	0.
0.	30.00	-999.99	-999.99	-999.99	0.	0.		9.84045E-15	-98.38	3.44809E-15	84.16
10.00	30.00	-14.02	-37.84	-14.00	0.03738	-3.00	RIGHT	5.18086E-02	-8.73	3.33675E-03	-153.15
20.00	30.00	-7.78	-31.80	-7.76	0.03466	-3.07	RIGHT	1.06290E-01	-9.67	6.69076E-03	-153.15
30.00	30.00	-3.93	-28.38	-3.92	0.03042	-2.96	RIGHT	1.65481E-01	-3.79	9.81400E-03	-153.15
40.00	30.00	-1.08	-26.30	-1.07	0.02517	-2.79	RIGHT	2.23787E-01	-0.58	1.29927E-02	-153.15
50.00	30.00	1.15	-25.34	1.16	0.01957	-2.47	RIGHT	2.89983E-01	2.42	1.40768E-02	-153.15
60.00	30.00	2.86	-25.59	2.87	0.01412	-2.01	RIGHT	3.51723E-01	4.89	1.36728E-02	-153.15
70.00	30.00	4.09	-27.50	4.09	0.00907	-1.42	RIGHT	4.18231E-01	6.68	1.08689E-02	-153.15
80.00	30.00	4.83	-32.55	4.83	0.00442	-0.73	RIGHT	4.53467E-01	7.77	6.13133E-03	-153.15
90.00	30.00	5.07	-999.99	5.07	0.00000	0.00	LINEAR	4.66525E-01	8.13	1.86195E-13	26.89
0.	60.00	-999.99	-999.99	-999.99	0.	0.		3.33654E-15	-99.71	5.90489E-15	82.90
10.00	60.00	-14.54	-37.83	-14.52	0.04222	-3.09	RIGHT	4.87719E-02	-11.33	3.34129E-03	-153.16
20.00	60.00	-8.28	-31.75	-8.26	0.03909	-3.12	RIGHT	1.00327E-01	-8.95	6.72504E-03	-153.16
30.00	60.00	-4.37	-28.29	-4.37	0.03409	-3.09	RIGHT	1.57060E-01	-5.69	1.00184E-02	-153.18
40.00	60.00	-1.46	-26.16	-1.44	0.02787	-2.92	RIGHT	2.20029E-01	-1.99	1.29029E-02	-153.19
50.00	60.00	0.87	-25.14	0.88	0.02130	-2.59	RIGHT	2.87605E-01	1.57	1.43868E-02	-153.20
60.00	60.00	2.69	-25.35	2.70	0.01508	-2.10	RIGHT	3.54503E-01	4.41	1.40578E-02	-153.21
70.00	60.00	4.01	-27.23	4.01	0.00952	-1.47	RIGHT	4.12667E-01	6.48	1.13240E-02	-153.21
80.00	60.00	4.81	-32.26	4.81	0.00458	-0.78	RIGHT	4.52518E-01	7.72	6.34618E-03	-153.22
90.00	60.00	5.08	-999.99	5.08	0.00000	0.00	LINEAR	4.66741E-01	8.13	1.93280E-13	26.79

0.	90.00	-999.99	-999.99	-999.99	0.	0.		1.472686E-16	148.31	6.780795E-15	82.26
10.00	90.00	-14.81	-999.99	-14.81	0.00000	0.00	LINEAR	4.729295E-02	-12.75	4.418495E-14	33.97
20.00	90.00	-8.54	-999.99	-8.54	0.00000	0.00	LINEAR	9.738728E-02	-10.21	8.477431E-14	30.77
30.00	90.00	-4.62	-999.99	-4.62	0.00000	0.00	LINEAR	1.529495E-01	-8.60	1.233131E-13	29.46
40.00	90.00	-1.65	-999.99	-1.65	0.00000	0.00	LINEAR	2.150616E-01	-8.62	1.566310E-13	29.07
50.00	90.00	0.72	-999.99	0.72	0.00000	0.00	LINEAR	2.827576E-01	1.11	1.758995E-13	28.71
60.00	90.00	2.60	-999.99	2.60	0.00000	0.00	LINEAR	3.586182E-01	4.17	1.714246E-13	28.99
70.00	90.00	3.96	-999.99	3.96	0.00000	0.00	LINEAR	4.109897E-01	6.38	1.382431E-13	28.32
80.00	90.00	4.80	-999.99	4.80	0.00000	0.00	LINEAR	4.519135E-01	7.70	7.738365E-14	28.15
90.00	90.00	5.08	-999.99	5.08	0.00000	-0.00	LINEAR	4.667411E-01	8.14	6.784725E-17	181.99

AVERAGE POWER GAIN= 1.789986E+00 SOLID ANGLE USED IN AVERAGING=(0.50001)*PI STERADIANS.

***** DATA CARD NO. 4 EN -0 -0 -0 -0 0. 0. 0. 0. 0. 0.

RUN TIME = 1.319

EXAMPLE 5, LOG-PERIODIC ANTENNA

Example 5 is a practical log-periodic antenna with 12 elements. Input data for the transmission line sections is printed in the table "Network Data." The table "Structure Excitation Data at Network Connection Points" contains the voltage, current, impedance, admittance, and power in each segment to which transmission lines or networks connect. This segment current will differ from the current into the connected transmission line if there are other transmission lines, network ports, or a voltage source providing alternate current paths. Thus, the current printed here for segment 3 differs from that in the table antenna "Input Parameters." The latter is the current through the voltage source and includes the current into the segment and into the transmission line. Power listed in the network-connection table is the power being fed into the segment. A negative power indicates that the structure is feeding power into the network or transmission line.

With 78 segments, file storage must be used for the interaction matrix. The line after data card number 14 shows how the matrix has been divided into blocks for transfer between core and the files. The line "CP TIME TAKEN FOR FACTORIZATION," gives the amount of central processor time used to factor the matrix excluding time spent transferring data between core and the files. Hence it is less than the total time for factoring printed below.

The EX card option has been used to print the relative asymmetry of the driving-point admittance matrix. The driving-point admittance matrix is the matrix of self and mutual admittances of segments connected to transmission lines, network ports, or voltage sources and should be symmetric.

Example 5 Input

```
'
CM 12 ELEMENT LOG PERIODIC ANTENNA IN FREE SPACE.
CM   78 SEGMENTS.     SIGMA=D/L       RECEIVING AND TRANS. PATTERNS.
CM DIPOLE LENGTH TO DIAMETER RATIO=150.
CE TAU=0.93,    SIGMA=0.70,     BOOM IMPEDANCE=50. OHMS.
GW  1   5  0.          -1.        0.          0          1.          0.          0.00667
GW  2   5  -.7527      -1.0753    0.          -.7527     1.0753      0.          .00717
GW  3   5  -1.582      -1.1582    0.          -1.582     1.1582      0.          .00771
GW  4   5  -2.4323     -1.2432    0.          -2.4323    1.2432      0.          .00829
GW  5   5  -3.388      -1.3388    0.          -3.388     1.3388      0.          .00891
GW  6   7  -4.3742     -1.4374    0.          -4.3742    1.4374      0.          .00958
GW  7   7  -5.4662     -1.5466    0.          -5.4662    1.5466      0.          .0103
GW  8   7  -6.6195     -1.6619    0.          -6.6195    1.6619      0.          .01108
GW  9   7  -7.8705     -1.787     0.          -7.8705    1.787       0.          .01191
GW 10   7  -9.2196     -1.9219    0.          -9.2196    1.9219      0.          .01281
GW 11   8  -10.6619    -2.0662    0.          -10.6619   2.0662      0.          .01377
GW 12   8  -12.2171    -2.2217    0.          -12.2171   2.2217      0.          .01481
GE
FR                      46.2%
TL  1   3   2   3      -50.
TL  2   3   3   3      -50.
TL  3   3   4   3      -50.
TL  4   3   5   3      -50.
TL  5   3   6   4      -50.
TL  6   4   7   4      -50.
TL  7   4   8   4      -50.
TL  8   4   9   4      -50
TL  9   4  10   4      -50.
TL 10   4  11   5      -50.
TL 11   5  12   5      -50.                                        .02
EX      1   3  10      1.
RP     37   1 1110     90.         0.          -5.         0.
EN
```

Example 5 Output

```
**********************************

  NUMERICAL ELECTROMAGNETICS CODE

**********************************


- - - - COMMENTS - - - -

 12 ELEMENT LOG PERIODIC ANTENNA IN FREE SPACE.
   78 SEGMENTS.     SIGMA=D/L       RECEIVING AND TRANS. PATTERNS.
 DIPOLE LENGTH TO DIAMETER RATIO=150.
 TAU=0.93,    SIGMA=0.70,     BOOM IMPEDANCE=50. OHMS.


- - - STRUCTURE SPECIFICATION - - -

     COORDINATES MUST BE INPUT IN
     METERS OR BE SCALED TO METERS
     BEFORE STRUCTURE INPUT IS ENDED

 WIRE                                                          NO. OF   FIRST   LAST    TAG
 NO.       X1          Y1          Z1          X2          Y2          Z2       RADIUS   SEG.    SEG.    SEG.    NO.
    1      0.       -1.00000       0.          0.        1.00000       0.      0.00667     6       1       6       1
    2   -0.75270    -1.07530       0.       -0.75270     1.07530       0.      0.00717     5       6      10       2
    3   -1.56200    -1.15620       0.       -1.56200     1.15620       0.      0.00771     5      11      15       3
    4   -2.43230    -1.24320       0.       -2.43230     1.24320       0.      0.00829     5      16      20       4
    5   -3.36800    -1.33680       0.       -3.36800     1.33680       0.      0.00891     5      21      25       5
    6   -4.37420    -1.43740       0.       -4.37420     1.43740       0.      0.00958     7      26      32       6
    7   -5.45620    -1.54560       0.       -5.45620     1.54560       0.      0.01030     7      33      39       7
    8   -6.61950    -1.66190       0.       -6.61950     1.66190       0.      0.01108     7      40      46       8
    9   -7.87050    -1.78700       0.       -7.87050     1.78700       0.      0.01181     7      47      53       9
   10   -9.21560    -1.92150       0.       -9.21560     1.92150       0.      0.01281     7      54      60      10
   11   -10.66190   -2.06620       0.       -10.66190    2.06620       0.      0.01377     9      61      69      11
   12   -12.21710   -2.22170       0.       -12.21710    2.22170       0.      0.01481     9      70      78      12

  TOTAL SEGMENTS USED=   78     NO. SEG. IN A SYMMETRIC CELL=   78     SYMMETRY FLAG=  0


       - MULTIPLE WIRE JUNCTIONS -
 JUNCTION     SEGMENTS (- FOR END 1, + FOR END 2)
 NONE


- - - - SEGMENTATION DATA - - - -

     COORDINATES IN METERS

     (+ AND (- INDICATE THE SEGMENTS BEFORE AND AFTER )

 SEG.    COORDINATES OF SEG. CENTER      SEG.      ORIENTATION ANGLES      WIRE      CONNECTION DATA      TAG
 NO.        X          Y          Z      LENGTH      ALPHA       BETA     RADIUS     (-     |     (+     NO.
    1      0.       -0.80000      0.     0.40000      0.       90.00000   0.00667     0     1     2       1
    2      0.       -0.40000      0.     0.40000      0.       90.00000   0.00667     1     2     3       1
    3      0.        0.00000      0.     0.40000      0.       90.00000   0.00667     2     3     4       1
    4      0.        0.40000      0.     0.40000      0.       90.00000   0.00667     3     4     5       1
    5      0.        0.80000      0.     0.40000      0.       90.00000   0.00667     4     5     0       1
    6   -0.75270    -0.86024      0.     0.43012      0.       90.00000   0.00717     0     6     7       2
    7   -0.75270    -0.43012      0.     0.43012      0.       90.00000   0.00717     6     7     8       2
    8   -0.75270     0.00000      0.     0.43012      0.       90.00000   0.00717     7     8     9       2
    9   -0.75270     0.43012      0.     0.43012      0.       90.00000   0.00717     8     9    10       2
   10   -0.75270     0.86024      0      0.43012      0.       90.00000   0.00717     9    10     0       2
   11   -1.56200    -0.82496      0.     0.46248      0.       90.00000   0.00771     0    11    12       3
   12   -1.56200    -0.46248      0.     0.46248      0.       90.00000   0.00771    11    12    13       3
   13   -1.56200     0.           0.     0.46248      0.       90.00000   0.00771    12    13    14       3
   14   -1.56200     0.46248      0.     0.46248      0.       90.00000   0.00771    13    14    15       3
   15   -1.56200     0.82496      0.     0.46248      0.       90.00000   0.00771    14    15     0       3
   16   -2.43230    -0.89456      0.     0.49728      0.       90.00000   0.00829     0    16    17       4
   17   -2.43230    -0.49728      0.     0.49728      0        90.00000   0.00829    16    17    18       4
```

18	-2.43230	0.00000	0.	0.49728	0.	90.00000	0.00829	17	18	19	4
19	-2.43230	0.49728	0.	0.49728	0.	90.00000	0.00829	18	19	20	4
20	-2.43230	0.99456	0.	0.49728	0.	90.00000	0.00829	19	20	0	4
21	-3.38800	-1.08944	0.	0.53472	0.	90.00000	0.00891	0	21	22	5
22	-3.38800	-0.53472	0.	0.53472	0.	90.00000	0.00891	21	22	23	5
23	-3.38800	-0.00000	0.	0.53472	0.	90.00000	0.00891	22	23	24	5
24	-3.38800	0.53472	0.	0.53472	0.	90.00000	0.00891	23	24	25	5
25	-3.38800	1.08944	0.	0.53472	0.	90.00000	0.00891	24	25	0	5
26	-4.37420	-1.23206	0.	0.41089	0.	90.00000	0.00958	0	26	27	6
27	-4.37420	-0.82137	0.	0.41089	0.	90.00000	0.00958	26	27	28	6
28	-4.37420	-0.41089	0.	0.41089	0.	90.00000	0.00958	27	28	29	6
29	-4.37420	0.00000	0.	0.41089	0.	90.00000	0.00958	28	29	30	6
30	-4.37420	0.41089	0.	0.41089	0	90.00000	0.00958	29	30	31	6
31	-4.37420	0.82137	0.	0.41089	0.	90.00000	0.00958	30	31	32	6
32	-4.37420	1.23206	0.	0.41089	0.	90.00000	0.00958	31	32	0	6
33	-5.45620	-1.32480	0.	0.44160	0.	90.00000	0.01030	0	33	34	7
34	-5.45620	-0.88320	0.	0.44160	0.	90.00000	0.01030	33	34	35	7
35	-5.45620	-0.44160	0.	0.44160	0.	90.00000	0.01030	34	35	36	7
36	-5.45620	0.00000	0.	0.44160	0.	90.00000	0.01030	35	36	37	7
37	-5.45620	0.44160	0.	0.44160	0.	90.00000	0.01030	36	37	38	7
38	-5.45620	0.88320	0.	0.44160	0.	90.00000	0.01030	37	38	39	7
39	-5.45620	1.32480	0.	0.44160	0.	90.00000	0.01030	38	39	0	7
40	-6.61950	-1.42449	0.	0.47483	0.	90.00000	0.01108	0	40	41	8
41	-6.61950	-0.94966	0.	0.47483	0.	90.00000	0.01108	40	41	42	8
42	-6.61950	-0.47483	0	0.47483	0.	90.00000	0.01108	41	42	43	8
43	-6.61950	0.00000	0.	0.47483	0.	90.00000	0.01108	42	43	44	8
44	-6.61950	0.47483	0.	0.47483	0.	90.00000	0.01108	43	44	45	0
45	-6.61950	0.94966	0.	0.47483	0.	90.00000	0.01108	44	45	46	8
46	-6.61950	1.42449	0.	0.47483	0.	90.00000	0.01108	45	46	0	8
47	-7.87050	-1.53171	0.	0.51057	0.	90.00000	0.01191	0	47	48	9
48	-7.87050	-1.02114	0.	0.51057	0.	90.00000	0.01191	47	48	49	9
49	-7.87050	-0.51057	0.	0.51057	0.	90.00000	0.01191	48	49	50	9
50	-7.87050	0.00000	0.	0.51057	0.	90.00000	0.01191	49	50	51	9
51	-7.87050	0.51057	0.	0.51057	0.	90.00000	0.01191	50	51	52	9
52	-7.87050	1.02114	0.	0.51057	0.	90.00000	0.01191	51	52	53	9
53	-7.87050	1.53171	0.	0.51057	0.	90.00000	0.01191	52	53	0	9
54	-9.21960	-1.64700	0.	0.54900	0.	90.00000	0.01281	0	54	55	10
55	-9.21960	-1.09800	0.	0.54900	0.	90.00000	0.01281	54	55	56	10
56	-9.21960	-0.54900	0.	0.54900	0.	90.00000	0.01281	55	56	57	10
57	-9.21960	-0.00000	0.	0.54900	0.	90.00000	0.01281	56	57	58	10
58	-9.21960	0.54900	0.	0.54900	0.	90.00000	0.01281	57	58	59	10
59	-9.21960	1.09800	0.	0.54900	0	90.00000	0.01281	58	59	60	10
60	-9.21960	1.64700	0.	0.54900	0.	90.00000	0.01281	59	60	0	10
61	-10.66190	-1.83662	0.	0.45916	0.	90.00000	0.01377	0	61	62	11
62	-10.66190	-1.37747	0.	0.45916	0.	90.00000	0.01377	61	62	63	11
63	-10.66190	-0.91831	0.	0.45916	0.	90.00000	0.01377	62	63	64	11
64	-10.66190	-0.45916	0.	0.45916	0.	90.00000	0.01377	63	64	65	11
65	-10.66190	0.	0.	0.45916	0.	90.00000	0.01377	64	65	66	11
66	-10.66190	0.45916	0.	0.45916	0	90.00000	0.01377	65	66	67	11
67	-10.66190	0.91831	0.	0.45916	0.	90.00000	0.01377	66	67	68	11
68	-10.66190	1.37747	0.	0.45916	0.	90.00000	0.01377	67	68	69	11
69	-10.66190	1.83662	0.	0.45916	0.	90.00000	0.01377	68	69	0	11
70	-12.21710	-1.97484	0	0.49371	0.	90.00000	0.01481	0	70	71	12
71	-12.21710	-1.48113	0	0.49371	0.	90.00000	0.01481	70	71	72	12
72	-12.21710	-0.98742	0	0.49371	0	90.00000	0.01481	71	72	73	12
73	-12.21710	-0.49371	0	0.49371	0	90.00000	0.01481	72	73	74	12
74	-12.21710	0.	0	0.49371	0	90.00000	0.01481	73	74	75	12
75	-12.21710	0.49371	0	0.49371	0	90.00000	0.01481	74	75	76	12
76	-12.21710	0.98742	0	0.49371	0.	90.00000	0.01481	75	76	77	12
77	-12.21710	1.48113	0.	0.49371	0	90.00000	0.01481	76	77	78	12
78	-12.21710	1.97484	0.	0.49371	0.	90.00000	0.01481	77	78	0	12

*****	DATA CARD NO.	1	FR	-0	-0	-0	4	8.29000E+01	0	0.	0.	0.	0
*****	DATA CARD NO.	2	TL	1	3	2	3	-5.00000E+01	0	0	0.	0.	0
*****	DATA CARD NO.	3	TL	2	3	3	3	-5.00000E+01	0.	0.	0	0	0.
*****	DATA CARD NO.	4	TL	3	3	4	3	-5.00000E+01	0.	0.	0.	0	0
*****	DATA CARD NO	5	TL	4	3	5	3	-5.00000E+01	0	0	0.	0.	0.
*****	DATA CARD NO	6	TL	5	3	6	4	-5.00000E+01	0	0.	0.	0.	0
*****	DATA CARD NO	7	TL	6	4	7	4	-5.00000E+01	0	0	0.	0	0
*****	DATA CARD NO	8	TL	7	4	8	4	-5.00000E+01	0	0.	0.	0.	0
*****	DATA CARD NO.	9	TL	8	4	9	4	-5.00000E+01	0	0	0.	0.	0
*****	DATA CARD NO.	10	TL	9	4	10	4	-5.00000E+01	0	0.	0.	0.	0
*****	DATA CARD NO	11	TL	10	4	11	5	-5.00000E+01	0	0.	0.	0.	0
*****	DATA CARD NO.	12	TL	11	5	12	5	-5.00000E+01	0	0.	0.	2.00000E-02	0
*****	DATA CARD NO.	13	EX	-0	1	3	10	1.00000E+00	0	0	0.	0	0
*****	DATA CARD NO	14	RP	-0	37	1	1110	9.00000E+01	0	-5.00000E+00	0.	0.	0.

MATRIX FILE STORAGE - NO BLOCKS= 4 COLUMNS PER BLOCK= 25 COLUMNS IN LAST BLOCK= 3

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 4.6250E+01 MHZ
WAVELENGTH= 6.4768E+00 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE
CP TIME TAKEN FOR FACTORIZATION = 5.7411E-01

- - - MATRIX TIMING - - -

FILL= 1.045 SEC., FACTOR= 2.861 SEC.

- - - NETWORK DATA - - -

- FROM -		- TO -		TRANSMISSION LINE		- - SHUNT ADMITTANCES (MHOS) - -				LINE
						- END ONE -		- END TWO -		
TAG NO.	SEG. NO.	TAG NO.	SEG. NO.	IMPEDANCE OHMS	LENGTH METERS	REAL	IMAG.	REAL	IMAG.	TYPE
1	3	2	8	5.0000E+01	7.5270E-01	0.	0.	0.	0.	CROSSED
2	8	3	13	5.0000E+01	8.0930E-01	0.	0.	0.	0.	CROSSED
3	13	4	18	5.0000E+01	8.7030E-01	0.	0.	0.	0	CROSSED
4	18	5	23	5.0000E+01	9.3570E-01	0.	0.	0.	0.	CROSSED
5	23	6	29	5.0000E+01	1.0062E+00	0.	0.	0.	0.	CROSSED
6	29	7	38	5.0000E+01	1.0820E+00	0.	0.	0.	0.	CROSSED
7	38	8	43	5.0000E+01	1.1635E+00	0	0.	0.	0.	CROSSED
8	43	9	50	5.0000E+01	1.2510E+00	0.	0.	0.	0.	CROSSED
9	50	10	57	5.0000E+01	1.3451E+00	0.	0.	0.	0.	CROSSED
10	57	11	65	5.0000E+01	1.4463E+00	0.	0.	0.	0.	CROSSED
11	65	12	74	5.0000E+01	1.5552E+00	0.	0.	2.0000E-02	0.	CROSSED

MAXIMUM RELATIVE ASYMMETRY OF THE DRIVING POINT ADMITTANCE MATRIX IS 1.073E-02 FOR SEGMENTS 65 AND 23
RMS RELATIVE ASYMMETRY IS 5.722E-03

- - - STRUCTURE EXCITATION DATA AT NETWORK CONNECTION POINTS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	IMAG.	CURRENT (AMPS) REAL	IMAG.	IMPEDANCE (OHMS) REAL	IMAG.	ADMITTANCE (MHOS) REAL	IMAG.	POWER (WATTS)
2	8-6	7.6815E-01	7.2710E-01	-1.8744E-04	1.9008E-03	3.4408E+02	-3.8987E+02	1.2725E-03	1.4418E-03	6.2785E-04
3	13-11	4.1418E-01	-1.0817E+00	8.8383E-05	2.2868E-03	-8.2567E+01	-1.3785E+02	-2.7506E-03	6.0328E-03	-1.6273E-03
4	18 9	8.6218E-01	5.0314E-01	-4.5805E-04	1.0883E 02	7.1634E+00	-9.3136E+01	8.2095E-04	1.0673E-02	4.8393E-04
5	23-17	2.7116E-01	6.5896E-01	-1.3712E-03	-3.4000E-03	3.8190E+01	5.7736E+01	7.8695E-03	1.2048E-02	3.8231E-03
6	29-2	8.8058E-01	-7.5623E-01	1.8911E-04	1.2747E-02	5.5429E+01	-2.9364E+01	1.4068E-02	7.4832E-03	4.5826E-03
7	38 5	1.1027E+01	5.6778E-02	9.6248E-03	-1.2011TE-03	5.1458E+01	1.2316E+01	1.8380E-02	-4.3992E-03	2.4225E-03
8	43-2	4.4958E-01	2.9921E-01	1.3787E-03	5.0479E-03	4.2825E+01	8.0230E+01	7.0411E-03	-1.1027TE-02	5.0626E-04
9	50-9	8.8180E-02	-3.6[illegible]E-01	-2.3070E-03	5.5275E-04	4.8124E+00	1.8753E+02	1.9371E-04	-6.3417E-03	1.3542E-05
10	57 3	4.0099E-01	2.7850E+02	3.6382E-04	-9.0906E-04	1.0265E+02	3.3303TE+02	8.4520TE-04	-2.7421E-03	4.9209E-05
11	65-9	9.2552E-02	3.3862E-01	5.7264E-04	9.6606E-04	2.1389E+02	3.7989E+02	1.1253E-03	-1.9986E-03	6.9340E-05
12	74-2	2.9465E-01	3.4969E-01	-7.2481E-04	4.7875E-04	1.9740E+02	3.1659E+02	1.4180E-03	-2.2744E-03	7.4475E-05
1	3 1	.0000E+00	0	1.0230E-03	2.3014E-03	2.1148TE+02	-2.6898E+02	1.0230E-03	2.3014E-03	9.1150E-04

- - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
1	3	1.00000E+00	0.	2.3824OE-02	2.90304E-04	4.2325IE+01	-4.4044OE-01	2.3624OE-02	2.9030HE-04	1.1812OE-02

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	1	0.	-0.1235	0.	0.05176	6.9701E-04	5.6831E-04	8.9833E-04	39.182
2	1	0.	-0.0618	0.	0.05176	1.5440E-03	1.5719E-03	2.2031E-03	45.565
3	1	0.	0.0000	0.	0.05176	1.8230E-03	2.3014E-03	2.9360E-03	51.616
4	1	0.	0.0618	0.	0.05176	1.5440E-03	1.5719E-03	2.2031E-03	45.565
5	1	0.	0.1235	0.	0.05176	6.9701E-04	5.6831E-04	8.9833E-04	39.182
6	2	-0.1162	-0.1328	0.	0.06841	1.9927E-04	-4.7369E-04	5.1390E-04	-67.163
7	2	-0.1162	-0.0664	0.	0.06841	1.5391E-04	-1.3187E-03	1.3277E-03	-83.343
8	2	-0.1162	0.0000	0.	0.06841	-1.8744E-04	-1.8009E-03	1.8101E-03	-95.638
9	2	-0.1162	0.0664	0.	0.06841	1.5391E-04	-1.3187E-03	1.3277E-03	-83.343
10	2	-0.1162	0.1328	0.	0.06841	1.9927E-04	-4.7369E-04	5.1390E-04	-67.163
11	3	-0.2412	-0.1428	0.	0.07141	2.1584E-03	9.8295E-04	2.3496E-03	23.162
12	3	-0.2412	-0.0714	0.	0.07141	5.2787E-03	1.9820E-03	5.6420E-03	20.575
13	3	-0.2412	0.	0.	0.07141	6.8384E-03	2.8868E-03	7.2108E-03	10.491
14	3	-0.2412	0.0714	0.	0.07141	5.2787E-03	1.9820E-03	5.6420E-03	20.575
15	3	-0.2412	0.1428	0.	0.07141	2.1584E-03	9.8295E-04	2.3496E-03	23.162
16	4	-0.3756	-0.1536	0.	0.07678	-1.5100E-03	3.9736E-03	3.8079E-03	112.906
17	4	-0.3756	-0.0768	0.	0.07678	-3.6153E-03	8.5186E-03	9.2528E-03	113.001
18	4	-0.3756	0.0000	0.	0.07678	-4.5806E-03	1.0883E-02	1.1844E-02	113.208
19	4	-0.3756	0.0768	0.	0.07678	-3.6153E-03	8.5186E-03	9.2528E-03	113.001
20	4	-0.3756	0.1536	0.	0.07678	-1.5100E-03	3.9736E-03	3.8079E-03	112.906
21	5	-0.5200	-0.1651	0.	0.08256	-4.7273E-03	-9.5637E-04	4.8231E-03	-168.563
22	5	-0.5200	-0.0826	0.	0.08256	-1.1146E-02	-2.5350E-03	1.1431E-02	-167.187
23	5	-0.5200	-0.0000	0.	0.08256	-1.3719E-02	-3.4800E-03	1.4150E-02	-165.762
24	5	-0.5200	0.0826	0.	0.08256	-1.1146E-02	-2.5350E-03	1.1431E-02	-167.187
25	5	-0.5200	0.1651	0.	0.08256	-4.7273E-03	-9.5637E-04	4.8231E-03	-168.563
26	6	-0.6754	-0.1902	0.	0.06341	1.3729E-04	-3.3822E-03	3.3850E-03	-87.675
27	6	-0.6754	-0.1268	0.	0.06341	5.5794E-04	-8.3198E-03	8.3385E-03	-86.183
28	6	-0.6754	-0.0634	0.	0.06341	1.1472E-03	-1.1518E-02	1.1573E-02	-84.311
29	6	-0.6754	0.0000	0.	0.06341	1.6918E-03	-1.2747E-02	1.2858E-02	-82.443
30	6	-0.6754	0.0634	0.	0.06341	1.1472E-03	-1.1518E-02	1.1573E-02	-84.311
31	6	-0.6754	0.1268	0.	0.06341	5.5794E-04	-8.3198E-03	8.3385E-03	-86.183
32	6	-0.6754	0.1902	0	0.06341	1.3729E-04	-3.3822E-03	3.3850E-03	-87.675
33	7	-0.8425	-0.2046	0.	0.08018	2.5954E-03	-5.7118E-04	2.6579E-03	-12.412
34	7	-0.8425	-0.1364	0.	0.08018	6.4087E-03	-1.2269E-03	6.5231E-03	-10.841
35	7	-0.8425	-0.0682	0.	0.08018	8.8142E-03	-1.3926E-03	8.9236E-03	-8.970
36	7	-0.8425	0.0000	0.	0.08018	9.6287E-03	-1.2012E-03	9.7033E-03	-7.111
37	7	-0.8425	0.0682	0.	0.08018	8.8142E-03	-1.3926E-03	8.9236E-03	-8.970
38	7	-0.8425	0.1364	0.	0.08018	6.4087E-03	-1.2269E-03	6.5231E-03	-10.841
39	7	-0.8425	0.2046	0.	0.08018	2.5954E-03	-5.7118E-04	2.6579E-03	-12.412
40	8	-1.0221	-0.2199	0.	0.07331	5.2465E-04	1.4101E-03	1.5049E-03	69.591
41	8	-1.0221	-0.1466	0	0.07331	1.1847E-03	3.4847E-03	3.6806E-03	71.223
42	8	-1.0221	-0.0733	0.	0.07331	1.4458E-03	4.7328E-03	4.9481E-03	73.011
43	8	-1.0221	0.0000	0.	0.07331	1.3788E-03	5.0476E-03	5.2329E-03	74.722
44	8	-1.0221	0.0733	0	0.07331	1.4458E-03	4.7328E-03	4.9481E-03	73.011
45	8	-1.0221	0.1466	0	0.07331	1.1847E-03	3.4847E-03	3.6806E-03	71.223
46	8	-1.0221	0.2199	0	0.07331	5.2465E-04	1.4101E-03	1.5049E-03	69.591
47	9	-1.2152	-0.2365	0	0.07883	-7.4266E-04	2.0199E-04	7.6984E-04	164.785
48	9	-1.2152	-0.1577	0.	0.07883	-1.7935E-03	4.8188E-04	1.8521E-03	165.959
49	9	-1.2152	-0.0788	0.	0.07883	-2.8192E-03	5.7091E-04	2.3884E-03	168.170
50	9	-1.2152	0.0000	0.	0.07883	-2.3071E-03	5.5279E-04	2.3724E-03	166.526
51	9	-1.2152	0.0788	0	0.07883	-2.8192E-03	5.7091E-04	2.3884E-03	168.170
52	9	-1.2152	0.1577	0.	0.07883	-1.7935E-03	4.8188E-04	1.8521E-03	165.959
53	9	-1.2152	0.2365	0	0.07883	-7.4266E-04	2.0199E-04	7.6984E-04	164.785
54	10	-1.4229	-0.2543	0.	0.08477	9.5745E-05	-3.9087E-04	4.0242E-04	-76.236
55	10	-1.4229	-0.1695	0.	0.08477	2.4939E-04	-8.9773E-04	9.3172E-04	-74.476
56	10	-1.4229	-0.0848	0.	0.08477	3.4519E-04	-1.0863E-03	1.1111E-03	-71.906
57	10	-1.4229	-0.0000	0	0.08477	3.6382E-04	-9.0907E-04	9.7917E-04	-68.188
58	10	-1.4229	0.0848	0.	0.08477	3.4519E-04	-1.0863E-03	1.1111E-03	-71.906
59	10	-1.4229	0.1695	0.	0.08477	2.4939E-04	-8.9773E-04	9.3172E-04	-74.476
60	10	-1.4229	0.2543	0.	0.08477	9.5745E-05	-3.9087E-04	4.0242E-04	-76.236
61	11	-1.6462	-0.2836	0.	0.07089	2.7079E-04	1.5010E-04	3.0961E-04	29.000
62	11	-1.6462	-0.2127	0.	0.07089	6.3252E-04	3.7763E-04	7.3667E-04	30.838
63	11	-1.6462	-0.1418	0.	0.07089	8.0838E-04	5.3277E-04	9.6816E-04	33.387
64	11	-1.6462	-0.0709	0.	0.07089	7.6873E-04	5.3417E-04	9.7158E-04	37.701
65	11	-1.6462	0.	0.	0.07089	5.7265E-04	5.6808E-04	8.0520E-04	44.889

66	11	-1.0462	0.0709	0.	0.07089	7.6873E-04	5.9117E-04	9.7159E-04	37.701
67	11	-1.0462	0.1418	0.	0.07089	8.0836E-04	5.3277E-04	9.6816E-04	33.387
68	11	-1.0462	0.2127	0.	0.07089	6.3258E-04	3.7783E-04	7.3667E-04	30.838
69	11	-1.0462	0.2836	0.	0.07089	2.7079E-04	1.5010E-04	3.0961E-04	29.000
70	12	-1.0864	-0.3049	0.	0.07623	-1.9982E-04	2.4071E-04	3.1204E-04	129.690
71	12	-1.0864	-0.2287	0.	0.07623	-5.0501E-04	5.6309E-04	7.5635E-04	131.889
72	12	-1.0864	-0.1525	0.	0.07623	-7.0816E-04	7.1495E-04	1.0070E-03	134.787
73	12	-1.0864	-0.0762	0.	0.07623	-7.7880E-04	6.6718E-04	1.0258E-03	139.414
74	12	-1.0864	0.	0.	0.07623	-7.2458E-04	4.7878E-04	8.6868E-04	146.894
75	12	-1.0864	0.0762	0.	0.07623	-7.7880E-04	6.6718E-04	1.0258E-03	139.414
76	12	-1.0864	0.1525	0.	0.07623	-7.0816E-04	7.1495E-04	1.0070E-03	134.787
77	12	-1.0864	0.2287	0.	0.07623	-5.0501E-04	5.6309E-04	7.5635E-04	131.889
78	12	-1.0864	0.3049	0.	0.07623	-1.9982E-04	2.4071E-04	3.1204E-04	129.690

- - - POWER BUDGET - - -

INPUT POWER = 1.1818E-02 WATTS
RADIATED POWER= 1.0762E-02 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 1.0504E-03 WATTS
EFFICIENCY = 91.11 PERCENT

- - - RADIATION PATTERNS - - -

- - ANGLES - -		- DIRECTIVE GAINS -			- - - POLARIZATION - - -			- - - E(THETA) - - -		- - - E(PHI) - - -	
THETA DEGREES	PHI DEGREES	VERT. DB	HOR. DB	TOTAL DB	AXIAL RATIO	TILT DEG.	SENSE	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES
90.00	0.	-999.99	9.75	9.75	0.00000	90.00	LINEAR	0.	0.	2.48928E+00	-66.00
85.00	0.	-999.99	9.70	9.70	0.00000	90.00	LINEAR	0.	0.	2.45352E+00	-65.20
80.00	0.	-999.99	9.53	9.53	0.00000	90.00	LINEAR	0.	0.	2.40688E+00	-62.83
75.00	0.	-999.99	9.25	9.25	0.00000	90.00	LINEAR	0.	0.	2.33093E+00	-58.97
70.00	0.	-999.99	8.86	8.86	0.00000	90.00	LINEAR	0.	0.	2.22888E+00	-53.74
65.00	0.	-999.99	8.37	8.37	0.00000	90.00	LINEAR	0.	0.	2.10818E+00	-47.30
60.00	0.	-999.99	7.78	7.78	0.00000	90.00	LINEAR	0.	0.	1.97023E+00	-39.77
55.00	0.	-999.99	7.15	7.15	0.00000	90.00	LINEAR	0.	0.	1.82918E+00	-31.17
50.00	0.	-999.99	6.45	6.45	0.00000	90.00	LINEAR	0.	0.	1.68049E+00	-21.34
45.00	0.	-999.99	5.70	5.70	0.00000	90.00	LINEAR	0.	0.	1.54747E+00	-9.81
40.00	0.	-999.99	4.81	4.81	0.00000	90.00	LINEAR	0.	0.	1.39759E+00	3.57
35.00	0.	-999.99	3.87	3.87	0.00000	90.00	LINEAR	0.	0.	1.22600E+00	18.48
30.00	0.	-999.99	2.10	2.10	0.00000	90.00	LINEAR	0.	0.	1.02313E+00	38.02
25.00	0.	-999.99	-0.14	-0.14	0.00000	90.00	LINEAR	0.	0.	7.90310E-01	59.26
20.00	0.	-999.99	-3.40	-3.40	0.00000	90.00	LINEAR	0.	0.	5.43329E-01	83.42
15.00	0.	-999.99	-8.27	-8.27	0.00000	90.00	LINEAR	0.	0.	3.10020E-01	111.77
10.00	0.	-999.99	-16.15	-16.15	0.00000	90.00	LINEAR	0.	0.	1.25192E-01	152.57
5.00	0.	-999.99	-23.15	-23.15	0.00000	90.00	LINEAR	0.	0.	5.58644E-02	-103.82
0.	0.	-999.99	-19.63	-19.63	0.00000	90.00	LINEAR	0.	0.	8.17061E-02	-41.89
-5.00	0.	-999.99	-20.86	-20.86	0.00000	90.00	LINEAR	0.	0.	7.44408E-02	-24.87
-10.00	0.	-999.99	-22.14	-22.14	0.00000	90.00	LINEAR	0.	0.	6.27600E-02	-47.83
-15.00	0.	-999.99	-17.70	-17.70	0.00000	90.00	LINEAR	0.	0.	1.04853E-01	-62.63
-20.00	0.	-999.99	-14.43	-14.43	0.00000	90.00	LINEAR	0.	0.	1.52513E-01	-60.23
-25.00	0.	-999.99	-13.31	-13.31	0.00000	90.00	LINEAR	0.	0.	1.73572E-01	-30.90
-30.00	0.	-999.99	-13.96	-13.96	0.00000	90.00	LINEAR	0.	0.	1.61084E-01	-10.69
-35.00	0.	-999.99	-16.41	-16.41	0.00000	90.00	LINEAR	0.	0.	1.21492E-01	7.49
-40.00	0.	-999.99	-21.41	-21.41	0.00000	90.00	LINEAR	0.	0.	6.83281E-02	18.32
-45.00	0.	-999.99	-29.95	-29.95	0.00000	90.00	LINEAR	0.	0.	2.95839E-02	-16.51
-50.00	0.	-999.99	-24.33	-24.33	0.00000	90.00	LINEAR	0.	0.	4.87767E-02	-74.32
-55.00	0.	-999.99	-19.91	-19.91	0.00000	90.00	LINEAR	0.	0.	8.11489E-02	-72.25
-60.00	0.	-999.99	-17.99	-17.99	0.00000	90.00	LINEAR	0.	0.	1.01231E-01	-63.59
-65.00	0.	-999.99	-17.28	-17.28	0.00000	90.00	LINEAR	0.	0.	1.09815E-01	-55.16
-70.00	0.	-999.99	-17.24	-17.24	0.00000	90.00	LINEAR	0.	0.	1.10368E-01	-48.42
-75.00	0.	-999.99	-17.53	-17.53	0.00000	90.00	LINEAR	0.	0.	1.06716E-01	-43.73
-80.00	0.	-999.99	-17.92	-17.92	0.00000	90.00	LINEAR	0.	0.	1.02037E-01	-40.94
-85.00	0.	-999.99	-18.23	-18.23	0.00000	90.00	LINEAR	0.	0.	9.84778E-02	-39.60
-90.00	0.	-999.99	-18.35	-18.35	0.00000	90.00	LINEAR	0.	0.	9.71778E-02	-39.22

- - - - NORMALIZED GAIN - - - -

MAJOR AXIS GAIN
NORMALIZATION FACTOR = 9.79 DB

- - ANGLES - - THETA DEGREES	PHI DEGREES	GAIN DB	- - ANGLES - - THETA DEGREES	PHI DEGREES	GAIN DB	- - ANGLES - - THETA DEGREES	PHI DEGREES	GAIN DB
90.00	0.	0.	25.00	0.	-9.90	-35.00	0.	-26.16
85.00	0.	-0.06	20.00	0.	-13.16	-40.00	0.	-31.16
80.00	0.	-0.22	15.00	0.	-18.02	-45.00	0.	-35.70
75.00	0.	-0.50	10.00	0.	-25.90	-50.00	0.	-34.09
70.00	0.	-0.89	5.00	0.	-32.91	-55.00	0.	-29.67
65.00	0.	-1.38	0.	0.	-29.38	-60.00	0.	-27.75
60.00	0.	-1.96	-5.00	0.	-30.42	-65.00	0.	-27.04
55.00	0.	-2.61	-10.00	0.	-31.90	-70.00	0.	-26.99
50.00	0.	-3.30	-15.00	0.	-27.46	-75.00	0.	-27.69
45.00	0.	-4.06	-20.00	0.	-24.19	-80.00	0.	-27.60
40.00	0.	-4.94	-25.00	0.	-23.06	-85.00	0.	-27.98
35.00	0.	-6.06	-30.00	0.	-23.71	-90.00	0.	-28.10
30.00	0.	-7.65						

***** DATA CARD NO. 15 EN -0 -0 -0 -0 0. 0. 0. 0. 0. 0.

RUN TIME = 17.907

EXAMPLE 6, CYLINDER WITH ATTACHED WIRES

The geometry data for the cylinder with attached wires was discussed in section III-2. The wire on the end of the cylinder is excited first and a radiation pattern is computed. The CP card requests the coupling between the base segments of the two wires. Hence after the second wire has been excited, the table "ISOLATION DATA" is printed. The coupling printed is the maximum that would occur when the source and load are simultaneously matched to their antennas. The table includes the matched load impedance for the second segment and the corresponding input impedance at the first segment. The source impedance would be the conjugate of this input impedance for maximum coupling.

Example 6 Input

```
CECYLINDER WITH ATTACHED WIRES.
SC          10.         0.          7.3333      0.          0.          38.4
SC          10.         0.          0.          0.          0.          38.4
SC          10.         0.          -7.3333     0.          0.          38.4
GH      1   0.          0.          30.
SF          6.86        0.          11.         90.         0.          44.00
SF          6.88        0.          -11.        -90.        0.          44.00
GS      4
SF          0.          0.          11.         90.         0.          44.00
SF          0.          0.          -11.        -90.        0.          44.00
GH  1   4   0.          0.          11.         0.          0.          23.         .1
GH  2   5   10.         0.          0.          27.6        0.          0.          .2
GS          .01
GE
TR      1               469.84
CP  1   1   2   1
CX      1   1           1.
TP      73  1   1000    0.          0.          5.          0.
CX      2   1           1.
XQ
EN
```

Example 6 Output

```
**************************************

NUMERICAL ELECTROMAGNETICS CODE

**************************************


- - - - COMMENTS - - - -

CYLINDER WITH ATTACHED WIRES.


- - - STRUCTURE SPECIFICATION - - -

COORDINATES MUST BE INPUT IN
METERS OR BE SCALED TO METERS
BEFORE STRUCTURE INPUT IS ENDED

WIRE                                                                    NO. OF   FIRST  LAST   TAG
NO.        X1          Y1          Z1          X2          Y2          Z2          RADIUS   SEG.    SEG.   SEG.   NO.
   1P  10.00000    0.          7.33330     0.          0.          30.40000
   2P  10.00000    0.          0.          0.          0.          30.40000
   3P  10.00000    0.         -7.33330     0.          0.          30.40000
    THE STRUCTURE HAS BEEN MOVED. MOVE DATA CARD IS -
     -0     1    0.          0.          30.00000   -0.         -0.         -0.         -0.
   7P   5.99000    0.         11.00000    90.00000    0.          44.99000
   8P   5.99000    0.        -11.00000   -90.00000    0.          44.99000
    STRUCTURE ROTATED ABOUT Z-AXIS  6 TIMES.  LABLES INCREMENTED BY   -0
  49P   0.          0          11.00000    90.00000    0.          44.99000
  50P   0.          0.         -11.00000   -90.00000    0.          44.99000
   1    0.          0.         11.00000    0.          0.          23.00000    0.10000      4       1      4      1
   2   10.00000    0.          0.          27.80000    0.          0.          0.20000      5       5      9      2
    STRUCTURE SCALED BY FACTOR   0.01000

 TOTAL SEGMENTS USED=   9     NO. SEG. IN A SYMMETRIC CELL=   9     SYMMETRY FLAG=  0
 TOTAL PATCHES USED=   56     NO. PATCHES IN A SYMMETRIC CELL=   56


      - MULTIPLE WIRE JUNCTIONS -
JUNCTION    SEGMENTS  (- FOR END 1, + FOR END 2)
NONE


- - - - SEGMENTATION DATA - - - -

COORDINATES IN METERS

(+ AND (- INDICATE THE SEGMENTS BEFORE AND AFTER (

SEG.    COORDINATES OF SEG. CENTER      SEG.      ORIENTATION ANGLES      WIRE     CONNECTION DATA    TAG
NO.        X          Y          Z      LENGTH      ALPHA      BETA     RADIUS     (-     (     (+    NO.
   1   0.          0.         0.12500   0.03000   90.00000    0.       0.00100  10052    1     2      1
   2   0.          0.         0.15500   0.03000   90.00000    0.       0.00100      1    2     3      1
   3   0.          0.         0.18500   0.03000   90.00000    0.       0.00100      2    3     4      1
   4   0.          0.         0.21500   0.03000   90.00000    0.       0.00100      3    4     0      1
   5   0.11780     0.         0.        0.03520    0.         0.       0.00200  10002    5     5      2
   6   0.15280     0.         0.        0.03520    0.         0.       0.00200      5    6     7      2
   7   0.18800     0.         0.        0.03520    0.         0.       0.00200      6    7     8      2
   8   0.22320     0.         0.        0.03520    0.         0.       0.00200      7    8     9      2
   9   0.25840     0.         0.        0.03520    0.         0.       0.00200      8    9     0      2
```

- - - SURFACE PATCH DATA - - -

COORDINATES IN METERS

PATCH NO	COORD OF PATCH CENTER X	Y	Z	UNIT NORMAL VECTOR X	Y	Z	PATCH AREA	COMPONENTS OF UNIT TANGENT VECTORS X1	Y1	Z1	X2	Y2	Z2
1	0.10000	0.	0.07333	1.0000	0.	0.	0.00384	-0.	1.0000	0.	0.	0.	1.0000
2	0.10000	0.01548	0.01548	1.0000	0	0.	0.00098	-0.	1.0000	0.	0.	0.	1.0000
3	0.10000	-0.01548	0.01548	1.0000	0.	0.	0.00098	-0.	1.0000	0.	0.	0.	1.0000
4	0.10000	-0.01548	-0.01548	1.0000	0.	0.	0.00098	-0.	1.0000	0.	0.	0.	1.0000
5	0.10000	0.01548	-0.01548	1.0000	0.	0.	0.00098	-0.	1.0000	0.	0.	0.	1.0000
6	0.10000	0.	-0.07333	1.0000	0.	0.	0.00384	-0.	1.0000	0.	0.	0.	1.0000
7	0.09660	0.05000	0.07333	0.8660	0.5000	0.	0.00384	-0.5000	0.8660	0.	0.	0.	1.0000
8	0.09660	0.05000	0.	0.8660	0.5000	0.	0.00384	-0.5000	0.8660	0.	0.	0.	1.0000
9	0.09660	0.05000	-0.07333	0.8660	0.5000	0.	0.00384	-0.5000	0.8660	0.	0.	0.	1.0000
10	0.06890	0.	0.11000	0.	0.	1.0000	0.00449	1.0000	0.	0.	0.	1.0000	0.
11	0.06890	0.	-0.11000	0.	0.	-1.0000	0.00449	1.0000	0.	0.	0.	-1.0000	0.
12	0.05000	0.09660	0.07333	0.5000	0.8660	0.	0.00384	-0.8660	0.5000	0.	0.	0.	1.0000
13	0.05000	0.09660	0.	0.5000	0.8660	0.	0.00384	-0.8660	0.5000	0.	0.	0.	1.0000
14	0.05000	0.09660	-0.07333	0.5000	0.8660	0.	0.00384	-0.8660	0.5000	0.	0.	0.	1.0000
15	-0.00000	0.10000	0.07333	-0.0000	1.0000	0.	0.00384	-1.0000	-0.0000	0.	0.	0.	1.0000
16	-0.00000	0.10000	0.	-0.0000	1.0000	0.	0.00384	-1.0000	-0.0000	0.	0.	0.	1.0000
17	-0.00000	0.10000	-0.07333	-0.0000	1.0000	0.	0.00384	-1.0000	-0.0000	0.	0.	0.	1.0000
18	0.03445	0.09967	0.11000	0.	0.	1.0000	0.00449	0.5000	0.8660	0.	-0.8660	0.5000	0.
19	0.03445	0.09967	-0.11000	0.	0.	-1.0000	0.00449	0.5000	0.8660	0.	0.8660	-0.5000	0.
20	-0.05000	0.08660	0.07333	-0.5000	0.8660	0.	0.00384	-0.8660	-0.5000	0.	0.	0.	1.0000
21	-0.05000	0.08660	0.	-0.5000	0.8660	0.	0.00384	-0.8660	-0.5000	0.	0.	0.	1.0000
22	-0.05000	0.08660	-0.07333	-0.5000	0.8660	0.	0.00384	-0.8660	-0.5000	0.	0.	0.	1.0000
23	-0.08660	0.05000	0.07333	-0.8660	0.5000	0.	0.00384	-0.5000	-0.8660	0.	0.	0.	1.0000
24	-0.08660	0.05000	0.	-0.8660	0.5000	0.	0.00384	-0.5000	-0.8660	0.	0.	0.	1.0000
25	-0.08660	0.05000	-0.07333	-0.8660	0.5000	0.	0.00384	-0.5000	-0.8660	0.	0.	0.	1.0000
26	-0.03445	0.05967	0.11000	0.	0.	1.0000	0.00449	-0.5000	0.8660	0.	-0.8660	-0.5000	0.
27	-0.03445	0.05967	-0.11000	0.	0.	-1.0000	0.00449	-0.5000	0.8660	0.	0.8660	0.5000	0.
28	-0.10000	-0.00000	0.07333	-1.0000	-0.0000	0.	0.00384	0.0000	-1.0000	0.	0.	0.	1.0000
29	-0.10000	-0.00000	0.	-1.0000	-0.0000	0.	0.00384	0.0000	-1.0000	0.	0.	0.	1.0000
30	-0.10000	-0.00000	-0.07333	-1.0000	-0.0000	0.	0.00384	0.0000	-1.0000	0.	0.	0.	1.0000
31	-0.08660	-0.05000	0.07333	-0.8660	-0.5000	0.	0.00384	0.5000	-0.8660	0.	0.	0.	1.0000
32	-0.08660	-0.05000	0.	-0.8660	-0.5000	0.	0.00384	0.5000	-0.8660	0.	0.	0.	1.0000
33	-0.08660	-0.05000	-0.07333	-0.8660	-0.5000	0.	0.00384	0.5000	-0.8660	0.	0.	0.	1.0000
34	-0.06890	-0.00000	0.11000	0.	0.	1.0000	0.00449	-1.0000	-0.0000	0.	0.0000	-1.0000	0.
35	-0.06890	-0.00000	-0.11000	0.	0.	-1.0000	0.00449	-1.0000	-0.0000	0.	-0.0000	1.0000	0.
36	-0.05000	-0.08660	0.07333	-0.5000	-0.8660	0.	0.00384	0.8660	-0.5000	0.	0.	0.	1.0000
37	-0.05000	-0.08660	0.	-0.5000	-0.8660	0.	0.00384	0.8660	-0.5000	0.	0.	0.	1.0000
38	-0.05000	-0.08660	-0.07333	-0.5000	-0.8660	0.	0.00384	0.8660	-0.5000	0.	0.	0.	1.0000
39	0.00000	-0.10000	0.07333	0.0000	-1.0000	0.	0.00384	1.0000	0.0000	0.	0.	0.	1.0000
40	0.00000	-0.10000	0.	0.0000	-1.0000	0.	0.00384	1.0000	0.0000	0.	0.	0.	1.0000
41	0.00000	-0.10000	-0.07333	0.0000	-1.0000	0.	0.00384	1.0000	0.0000	0.	0.	0.	1.0000
42	-0.03445	-0.09967	0.11000	0.	0.	1.0000	0.00449	-0.5000	-0.8660	0.	0.8660	-0.5000	0.
43	-0.03445	-0.09967	-0.11000	0.	0.	-1.0000	0.00449	-0.5000	-0.8660	0.	-0.8660	0.5000	0.
44	0.05000	-0.08660	0.07333	0.5000	-0.8660	0.	0.00384	0.8660	0.5000	0.	0.	0.	1.0000
45	0.05000	-0.08660	0.	0.5000	-0.8660	0.	0.00384	0.8660	0.5000	0.	0.	0.	1.0000
46	0.05000	-0.08660	-0.07333	0.5000	-0.8660	0.	0.00384	0.8660	0.5000	0.	0.	0.	1.0000
47	0.08660	-0.05000	0.07333	0.8660	-0.5000	0.	0.00384	0.5000	0.8660	0.	0.	0.	1.0000
48	0.08660	-0.05000	0.	0.8660	-0.5000	0.	0.00384	0.5000	0.8660	0.	0.	0.	1.0000
49	0.08660	-0.05000	-0.07333	0.8660	-0.5000	0.	0.00384	0.5000	0.8660	0.	0.	0.	1.0000
50	0.03445	-0.05967	0.11000	0.	0.	1.0000	0.00449	0.5000	-0.8660	0.	0.8660	0.5000	0.
51	0.03445	-0.05967	-0.11000	0.	0.	-1.0000	0.00449	0.5000	-0.8660	0.	-0.8660	-0.5000	0.
52	0.01875	0.01875	0.11000	0.	0.	1.0000	0.00112	1.0000	0.	0.	0.	1.0000	0.
53	-0.01875	0.01875	0.11000	0.	0.	1.0000	0.00112	1.0000	0.	0.	0.	1.0000	0.
54	-0.01875	-0.01875	0.11000	0.	0.	1.0000	0.00112	1.0000	0.	0.	0.	1.0000	0.
55	0.01875	-0.01875	0.11000	0.	0	1.0000	0.00112	1.0000	0.	0.	0.	1.0000	0.
56	0.	0.	-0.11000	0.	0.	-1.0000	0.00449	1.0000	0.	0.	0.	-1.0000	0.

***** DATA CARD NO.	1	FR	-0	1	-0	-0	4.65840E+02	0	0.	0.	0.	0.
*** * DATA CARD NO.	2	CP	1	1	2	1	0	0.	0.	0.	0.	0.
***** DATA CARD NO.	3	EX	-0	1	1	-0	1.00000E+00	0	0.	0.	0.	0.
*** * ... CARD NO.	4	RP	-0	73	1	1000	0.	0	5.00000E+00	0.	0.	0.

M * FILE STORAGE - NO BLOCKS= 0 COLUMNS PER BLOCK= 16 COLUMNS IN LAST BLOCK= 9

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 4.6584E+02 MHZ
WAVELENGTH= 6.4357E-01 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -

FREE SPACE

CP TIME TAKEN FOR FACTORIZATION = 2.1950E+00

- - - MATRIX TIMING - - -

FILL= 0.967 SEC., FACTOR= 0.886 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG.	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
1	1	1.00000E+00	0.	1.25133E-03	8.29229E-03	1.77929E+01	-1.17908E+02	1.25133E-03	8.29229E-03	6.25663E-04

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	1	0.	0.	0.1942	0.04662	1.25133E-03	8.29229E-03	8.38626E-03	81.419
2	1	0.	0.	0.2408	0.04662	1.09756E-03	8.58000E-03	8.67008E-03	80.531
3	1	0.	0.	0.2875	0.04662	7.91877E-04	4.37586E-03	4.44686E-03	79.749
4	1	0.	0.	0.3341	0.04662	3.30766E-04	1.78506E-03	1.78986E-03	79.146
5	2	0.1827	0.	0.	0.05470	-7.68076E-04	1.86346E-03	1.72896E-03	116.042
6	2	0.2374	0.	0.	0.05470	-7.01476E-04	1.43076E-03	1.99346E-03	116.119
7	2	0.2921	0.	0.	0.05470	-6.04376E-04	1.19016E-03	1.32986E-03	116.193
8	2	0.3468	0.	0.	0.05470	-4.08016E-04	8.31736E-04	9.26426E-04	116.131
9	2	0.4015	0.	0.	0.05470	-1.89986E-04	3.47476E-04	3.86826E-04	116.060

- - - - SURFACE PATCH CURRENTS - - - -

DISTANCE IN WAVELENGTHS
CURRENT IN AMPS/METER

PATCH CENTER X	Y	Z	- - SURFACE COMPONENTS - - TANGENT VECTOR 1 MAG.	PHASE	TANGENT VECTOR 2 MAG.	PHASE	- - - RECTANGULAR COMPONENTS - - - X REAL	X IMAG.	Y REAL	Y IMAG.	Z REAL	Z IMAG.
1												
0.155	0	0.114	2.4110E-12	68.37	7.1982E-03	-35.22	0.	0.	8.89E-13	2.24E-12	5.88E-03	-4.15E-03
2												
0.155	0.024	0.024	8.0012E-03	-65.46	1.4820E-02	-51.34	0.	0.	3.74E-03	-8.19E-03	8.88E-03	-1.11E-02
3												
0.155	-0.024	0.024	8.0012E-03	114.54	1.4820E-02	-51.34	0.	0.	-3.74E-03	8.19E-03	8.88E-03	-1.11E-02
4												
0.155	-0.024	-0.024	8.0081E-03	114.49	5.0968E-03	84.31	0.	0.	-3.73E-03	8.20E-03	5.05E-04	5.07E-03
5												
0.155	0.024	-0.024	8.0081E-03	-65.51	5.0968E-03	84.31	0.	0.	3.73E-03	-8.20E-03	5.05E-04	5.07E-03
6												
0.155	0.	-0.114	8.8399E-13	-4.52	1.8972E-03	12.63	0.	0.	8.82E-13	-5.39E-14	1.86E-03	3.46E-04
7												
0.135	0.070	0.114	1.8793E-03	-94.87	5.5429E-03	-11.30	7.97E-05	9.36E-04	-1.19E-04	-1.82E-03	5.44E-03	-1.09E-03
8												
0.135	0.070	0.	3.9149E-03	-75.49	5.3139E-03	-33.00	-4.90E-04	1.09E-03	8.49E-04	-3.28E-03	4.46E-03	-2.09E-03
9												
0.139	0.070	-0.114	1.8133E-03	-94.60	2.9183E-03	-33.42	7.27E-05	9.04E-04	-1.28E-04	-1.57E-03	2.44E-03	-1.61E-03
10												
0.107	0.	0.171	1.3691E-02	-104.81	2.5901E-12	102.37	-3.50E-03	-1.32E-02	-5.55E-13	2.53E-12	0	0.
11												
0.107	0	-0.171	1.5187E-03	-10.62	1.2045E-12	-163.58	1.49E-03	-2.80E-04	1.18E-12	3.41E-13	0.	0.

12
0.078 0.135 0.114 1.6705E-03 -129.81 4.7414E-03 -8.86 9.25E-04 1.11E-03 -5.35E-04 -8.42E-04 4.68E-03 -7.30E-04
13
0.078 0.135 0. 1.6295E-03 -112.84 5.3699E-03 -33.12 5.48E-04 1.30E-03 -3.18E-04 -7.51E-04 4.50E-03 -2.93E-03
14
0.078 0.135 -0.114 1.7228E-03 -128.58 4.1908E-03 -48.62 9.30E-04 1.17E-03 -9.37E-04 -6.73E-04 2.74E-03 -3.11E-03
15
0.000 0.195 0.114 1.4450E-03 160.34 5.3232E-03 11.87 1.38E-03 4.08E-04 1.08E-13 8.73E-14 5.21E-03 1.08E-03
16
0.000 0.195 0. 1.2074E-03 -155.48 5.3890E-03 -32.95 1.10E-03 5.01E-04 1.52E-13 6.94E-14 4.51E-03 -2.92E-03
17
0.000 0.195 -0.114 1.4418E-03 -160.26 4.6031E-03 -94.81 1.38E-03 4.87E-04 1.08E-13 8.74E-14 2.67E-03 -3.75E-03
18
0.094 0.093 0.171 1.4845E-02 -109.23 1.6078E-03 -149.84 -8.01E-04 -6.38E-03 -4.04E-03 -1.28E-02 0. 0.
19
0.094 0.093 -0.171 1.7548E-03 -90.91 1.6063E-03 35.02 1.88E-03 1.17E-04 3.00E-04 -1.84E-03 0. 0.
20
-0.078 0.135 0.114 1.3168E-03 -178.68 5.0409E-03 -2.54 1.14E-03 2.63E-05 6.98E-04 1.82E-05 5.04E-03 -2.84E-04
21
-0.078 0.135 0. 9.9498E-04 178.84 5.3744E-03 -33.13 8.61E-04 -2.05E-05 4.87E-04 -1.18E-05 4.50E-03 -2.94E-03
22
-0.078 0.135 -0.114 1.3019E-03 178.62 4.3371E-03 -56.63 1.13E-03 -2.72E-05 6.91E-04 -1.57E-05 2.39E-03 -3.62E-03
23
-0.135 0.078 0.114 7.0537E-04 161.19 5.7478E-03 9.56 3.34E-04 -1.14E-04 5.78E-04 -1.97E-04 5.67E-03 9.54E-04
24
-0.135 0.078 0. 5.8001E-04 165.30 5.3716E-03 -33.03 2.81E-04 -7.36E-06 4.86E-04 -1.27E-04 4.50E-03 -2.93E-03
25
-0.135 0.078 -0.114 6.9541E-04 166.60 4.2602E-03 -56.97 3.38E-04 -8.08E-05 5.86E-04 -1.40E-04 2.20E-03 -3.65E-03
26
-0.094 0.093 0.171 1.5570E-02 -109.02 1.4143E-03 -178.69 3.78E-03 7.43E-03 -3.69E-03 -1.27E-02 0. 0.
27
-0.094 0.093 -0.171 1.7609E-03 -92.00 1.4055E-03 2.99 1.25E-03 9.44E-04 6.48E-04 -1.49E-03 0. 0.
28
-0.195 -0.000 0.114 5.3312E-13 -103.74 5.2708E-03 -3.82 -5.19E-23 -2.12E-22 1.27E-13 5.18E-13 5.26E-03 -3.91E-04
29
-0.195 -0.000 0. 4.1841E-13 -125.09 5.3701E-03 -33.05 -8.67E-23 -1.40E-22 2.41E-13 3.42E-13 4.50E-03 -2.93E-03
30
-0.195 -0.000 -0.114 1.1981E-13 -153.34 4.0753E-03 -57.89 -4.25E-23 -2.13E-23 1.03E-13 5.20E-14 2.17E-03 -3.45E-03
31
-0.135 -0.078 0.114 7.0537E-04 -18.81 5.7478E-03 9.56 3.34E-04 -1.14E-04 -5.78E-04 1.97E-04 5.67E-03 9.54E-04
32
-0.135 -0.078 0. 5.8001E-04 -14.70 5.3716E-03 -33.03 2.81E-04 -7.36E-06 -4.86E-04 1.27E-04 4.50E-03 -2.93E-03
33
-0.135 -0.078 -0.114 6.9541E-04 -13.40 4.2602E-03 -56.97 3.38E-04 -8.08E-05 -5.86E-04 1.40E-04 2.20E-03 -3.65E-03
34
-0.107 -0.000 0.171 1.5557E-02 -111.31 3.9138E-13 -73.43 5.65E-03 1.45E-02 2.21E-12 6.32E-12 0. 0.
35
-0.107 -0.000 -0.171 1.6720E-03 -112.54 2.2817E-13 -54.54 6.41E-04 1.54E-03 3.95E-13 4.48E-13 0. 0.
36
-0.078 -0.135 0.114 1.3168E-03 1.32 5.0409E-03 -2.54 1.14E-03 2.63E-05 -6.98E-04 1.82E-05 5.04E-03 -2.84E-04
37
-0.078 -0.135 0. 9.9498E-04 -1.36 5.3744E-03 -33.13 8.61E-04 -2.05E-05 -4.87E-04 1.18E-05 4.50E-03 -2.94E-03
38
-0.078 -0.135 -0.114 1.3019E-03 -1.38 4.3371E-03 -56.63 1.13E-03 -2.72E-05 -6.91E-04 1.57E-05 2.39E-03 -3.62E-03
39
0.000 -0.195 0.114 1.4450E-03 19.66 5.3232E-03 11.87 1.38E-03 4.08E-04 7.47E-13 2.67E-13 5.21E-03 1.08E-03
40
0.000 -0.195 0. 1.2074E-03 24.52 5.3890E-03 -32.95 1.10E-03 5.01E-04 8.03E-13 2.75E-13 4.51E-03 -2.92E-03
41
0.000 -0.195 -0.114 1.4418E-03 19.74 4.6031E-03 -94.81 1.38E-03 4.87E-04 7.44E-13 2.67E-13 2.67E-03 -3.75E-03
42
-0.094 -0.093 0.171 1.5570E-02 -109.02 1.4143E-03 3.31 3.78E-03 7.43E-03 3.69E-03 1.27E-02 0. 0.
43
-0.094 -0.093 -0.171 1.7609E-03 -92.00 1.4055E-03 -177.01 1.25E-03 9.44E-04 -6.48E-04 1.49E-03 0. 0.
44
0.078 -0.135 0.114 1.6705E-03 50.19 4.7414E-03 -8.86 9.25E-04 1.11E-03 5.35E-04 8.42E-04 4.68E-03 -7.30E-04
45
0.078 -0.135 0. 1.6295E-03 67.16 5.3699E-03 -33.12 5.48E-04 1.30E-03 3.18E-04 7.51E-04 4.50E-03 -2.93E-03
46
0.078 -0.135 -0.114 1.7228E-03 91.42 4.1908E-03 -48.62 9.30E-04 1.17E-03 9.37E-04 6.73E-04 2.74E-03 -3.11E-03
47
0.078 0.078 0.114 1.8793E-03 85.13 5.5420E-03 -11.30 7.87E-05 9.38E-04 1.38E-04 1.82E-03 5.44E-03 -1.09E-03
48
0.135 -0.078 0. 3.9149E-03 104.91 5.3139E-03 -33.00 -4.80E-04 1.89E-03 -8.49E-04 3.28E-03 4.46E-03 -2.89E-03
49
0.135 -0.078 -0.114 1.8133E-03 85.40 2.9183E-03 -33.42 7.87E-05 9.04E-04 1.28E-04 1.97E-03 2.44E-03 -1.61E-03
50
0.094 0.093 0.171 1.4845E-02 -109.23 1.6078E-03 34.16 -8.01E-04 -6.38E-03 4.04E-03 1.28E-02 0. 0.
51
0.094 0.093 -0.171 1.7548E-03 -90.91 1.6063E-03 -144.98 1.89E-03 1.17E-04 -3.00E-04 1.84E-03 0. 0.

82												
0.026	0.026	0.171	3.7707E-02	-97.61	3.8523E-02	-99.40	-4.99E-03	-3.74E-02	-8.29E-03	-3.80E-02	0.	0.
83												
-0.026	0.026	0.171	3.8971E-02	78.78	3.9497E-02	-99.34	7.58E-03	3.88E-02	-8.25E-03	-3.60E-02	0.	0.
84												
-0.026	-0.026	0.171	3.8971E-02	78.78	3.9497E-02	80.66	7.58E-03	3.88E-02	8.25E-03	3.80E-02	0.	0.
85												
0.026	-0.026	0.171	3.7707E-02	-97.61	3.8523E-02	80.60	-4.99E-03	-3.74E-02	8.29E-03	3.80E-02	0.	0.
86												
0.	0.	-0.171	1.3523E-03	10.00	6.8843E-13	177.14	1.29E-03	4.18E-04	8.66E-13	-3.33E-14	0.	0.

- - - POWER BUDGET - - -

INPUT POWER = 6.2566E-04 WATTS
RADIATED POWER= 6.2566E-04 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

- - - RADIATION PATTERNS - - -

- - ANGLES - -		- POWER GAINS -			- - - POLARIZATION - - -			- - - E(THETA) - - -		- - - E(PHI) - - -	
THETA DEGREES	PHI DEGREES	VERT. DB	HOR. DB	TOTAL DB	AXIAL RATIO	TILT DEG.	SENSE	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	-8.11	-199.81	-8.11	0.00000	0.00	LINEAR	7.81678E-02	-2.26	2.02584E-11	2.66
5.00	0.	-8.34	-199.81	-8.34	0.00000	0.00	LINEAR	7.41609E-02	-2.08	1.95604E-11	6.76
10.00	0.	-8.85	-999.99	-8.85	0.00000	0.00	LINEAR	6.99504E-02	-2.76	1.89803E-11	10.56
15.00	0.	-9.70	-999.99	-9.70	0.00000	0.00	LINEAR	6.33762E-02	-4.63	1.85045E-11	14.02
20.00	0.	-11.02	-999.99	-11.02	0.00000	0.00	LINEAR	5.44956E-02	-8.24	1.81244E-11	17.07
25.00	0.	-12.94	-999.99	-12.94	0.00000	0.00	LINEAR	4.38412E-02	-14.78	1.78878E-11	19.67
30.00	0.	-15.74	-999.99	-15.74	0.00000	0.00	LINEAR	3.18460E-02	-27.33	1.78075E-11	21.78
35.00	0.	-19.30	-999.99	-19.30	0.00000	0.00	LINEAR	2.08971E-02	-55.34	1.74563E-11	23.39
40.00	0.	-19.97	-999.99	-19.97	0.00000	-0.00	LINEAR	1.94296E-02	-107.78	1.73695E-11	24.47
45.00	0.	-16.08	-999.99	-16.08	0.00000	-0.00	LINEAR	3.04209E-02	-149.20	1.73420E-11	25.02
50.00	0.	-12.40	-999.99	-12.40	0.00000	-0.00	LINEAR	4.84484E-02	-163.87	1.73715E-11	25.02
55.00	0.	-9.60	-999.99	-9.60	0.00000	-0.00	LINEAR	6.41585E-02	-175.93	1.74554E-11	24.47
60.00	0.	-7.40	-999.99	-7.40	0.00000	-0.00	LINEAR	8.26336E-02	174.32	1.75942E-11	23.39
65.00	0.	-5.61	-999.99	-5.61	0.00000	-0.00	LINEAR	1.01578E-01	168.52	1.77895E-11	21.78
70.00	0.	-4.10	-999.99	-4.10	0.00000	-0.00	LINEAR	1.20891E-01	157.18	1.80437E-11	19.68
75.00	0.	-2.80	-999.99	-2.80	0.00000	-0.00	LINEAR	1.40313E-01	149.15	1.83599E-11	17.11
80.00	0.	-1.67	-999.99	-1.67	0.00000	-0.00	LINEAR	1.58736E-01	141.42	1.87420E-11	14.13
85.00	0.	-0.70	-999.99	-0.70	0.00000	-0.00	LINEAR	1.78758E-01	133.99	1.91975E-11	10.77
90.00	0.	0.14	-199.84	0.14	0.00000	-0.00	LINEAR	1.98871E-01	126.82	1.97270E-11	7.12
95.00	0.	0.84	-199.58	0.84	0.00000	-0.00	LINEAR	2.13447E-01	120.23	2.03358E-11	3.25
100.00	0.	1.41	-199.29	1.41	0.00000	-0.00	LINEAR	2.27708E-01	113.95	2.10224E-11	-0.78
105.00	0.	1.83	-199.00	1.83	0.00000	-0.00	LINEAR	2.38180E-01	108.08	2.17895E-11	-4.86
110.00	0.	2.11	-198.86	2.11	0.00000	-0.00	LINEAR	2.46998E-01	102.85	2.26093E-11	-8.99
115.00	0	2.24	-198.32	2.24	0.00000	-0.00	LINEAR	2.50861E-01	97.66	2.34913E-11	-13.03
120.00	0.	2.20	-197.99	2.20	0.00000	-0.00	LINEAR	2.49579E-01	93.15	2.44145E-11	-16.97
125.00	0.	2.00	-197.68	2.00	0.00000	-0.00	LINEAR	2.43788E-01	89.16	2.53657E-11	-20.77
130.00	0.	1.61	-197.33	1.61	0.00000	-0.00	LINEAR	2.33171E-01	85.74	2.63268E-11	-24.41
135.00	0.	1.02	-197.02	1.02	0.00000	-0.00	LINEAR	2.17834E-01	82.99	2.72867E-11	-27.86
140.00	0.	0.21	-196.73	0.21	0.00000	-0.00	LINEAR	1.99504E-01	81.07	2.82341E-11	-31.12
145.00	0.	-0.85	-196.45	-0.85	0.00000	-0.00	LINEAR	1.79591E-01	80.23	2.91618E-11	-34.20
150.00	0.	-2.22	-196.18	-2.22	0.00000	-0.00	LINEAR	1.60002E-01	80.93	3.00638E-11	-37.08
155.00	0	-3.93	-195.93	-3.93	0.00000	-0.00	LINEAR	1.43133E-01	83.98	3.09412E-11	-39.79
160.00	0.	-6.02	-195.69	-6.02	0.00000	-0.00	LINEAR	1.28249E-01	90.96	3.17973E-11	-42.31
165.00	0.	-8.33	-195.47	-8.33	0.00000	-0.00	LINEAR	1.42595E-01	104.77	3.26370E-11	-44.67
170.00	0.	-10.04	-195.25	-10.04	0.00000	-0.00	LINEAR	6.09913E-02	128.40	3.34676E-11	-46.87
175.00	0.	-9.83	-195.04	-9.83	0.00000	-0.00	LINEAR	5.24519E-02	156.53	3.42962E-11	-48.91
180.00	0.	-8.13	-194.83	-8.13	0.00000	-0.00	LINEAR	7.98944E-02	177.76	3.51282E-11	-50.81
185.00	0.	-6.24	-194.62	-6.24	0.00000	-0.00	LINEAR	9.43853E-02	-168.88	3.59723E-11	-52.55
190.00	0.	-4.65	-194.42	-4.65	0.00000	-0.00	LINEAR	1.13349E-01	-159.93	3.68277E-11	-54.15
195.00	0.	-3.40	-194.22	-3.40	0.00000	-0.00	LINEAR	1.30589E-01	-152.98	3.76951E-11	-55.60
200.00	0.	-2.43	-194.02	-2.43	0.00000	0.00	LINEAR	1.46407E-01	-146.80	3.85703E-11	-56.91
205.00	0.	-1.68	-193.82	-1.68	0.00000	0.00	LINEAR	1.59877E-01	-140.77	3.94479E-11	-58.08
210.00	0.	-1.08	-193.63	-1.08	0.00000	0.00	LINEAR	1.70894E-01	-134.57	4.03148E-11	-59.10
215.00	0.	-0.61	-193.45	-0.61	0.00000	0.00	LINEAR	1.80813E-01	-128.05	4.11592E-11	-59.96
220.00	0.	-0.21	-193.28	-0.21	0.00000	0.00	LINEAR	1.89045E-01	-121.22	4.19843E-11	-60.67
225.00	0.	0.13	-193.13	0.13	0.00000	0.00	LINEAR	1.96540E-01	-114.15	4.27120E-11	-61.21
230.00	0.	0.42	-193.00	0.42	0.00000	0.00	LINEAR	2.03207E-01	-106.82	4.33430E-11	-61.58
235.00	0.	0.66	-192.88	0.66	0.00000	0.00	LINEAR	2.08956E-01	-99.67	4.39580E-11	-61.77
240.00	0.	0.85	-192.78	0.85	0.00000	0.00	LINEAR	2.13503E-01	-92.48	4.44184E-11	-61.77
245.00	0.	0.97	-192.73	0.97	0.00000	0.00	LINEAR	2.16480E-01	-85.42	4.47386E-11	-61.59
250.00	0.	1.01	-192.70	1.01	0.00000	0.00	LINEAR	2.17478E-01	-78.56	4.48108E-11	-61.20
255.00	0.	0.95	-192.69	0.95	0.00000	0.00	LINEAR	2.16147E-01	-71.88	4.48195E-11	-60.61
260.00	0	0.80	-192.73	0.80	0.00000	0.00	LINEAR	2.12257E-01	-65.42	4.47415E-11	-59.80

265.00	0.	0.52	-192.00	0.52	0.00000	0.00	LINEAR	2.087368E-01	-59.17	4.438058E-11	-58.77
270.00	0.	0.13	-192.91	0.13	0.00000	0.00	LINEAR	1.966908E-01	-63.13	4.382918E-11	-57.52
275.00	0.	-0.38	-193.06	-0.38	0.00000	0.00	LINEAR	1.853958E-01	-67.32	4.308844E-11	-56.04
280.00	0.	-1.02	-193.24	-1.02	0.00000	0.00	LINEAR	1.728268E-01	-71.75	4.216298E-11	-54.32
285.00	0.	-1.77	-193.47	-1.77	0.00000	0.00	LINEAR	1.579185E-01	-76.46	4.106377E-11	-52.37
290.00	0.	-2.64	-193.74	-2.64	0.00000	0.00	LINEAR	1.429868E-01	-81.49	3.980084E-11	-50.17
295.00	0.	-3.60	-194.05	-3.60	0.00000	0.00	LINEAR	1.279965E-01	-86.81	3.841136E-11	-47.74
300.00	0.	-4.62	-194.40	-4.62	0.00000	0.00	LINEAR	1.137935E-01	-92.79	3.690295E-11	-45.05
305.00	0.	-5.66	-194.78	-5.66	0.00000	0.00	LINEAR	1.008936E-01	-98.23	3.530886E-11	-42.12
310.00	0.	-6.66	-195.20	-6.66	0.00000	0.00	LINEAR	8.994341E-02	-104.30	3.365895E-11	-38.93
315.00	0.	-7.55	-195.64	-7.55	0.00000	0.00	LINEAR	8.111962E-02	-110.02	3.196078E-11	-35.50
320.00	0.	-8.25	-196.11	-8.25	0.00000	0.00	LINEAR	7.408981E-02	-116.38	3.023945E-11	-31.83
325.00	0.	-8.71	-196.58	-8.71	0.00000	0.00	LINEAR	7.105908E-02	-121.81	2.870331E-11	-27.92
330.00	0.	-8.91	-197.07	-8.91	0.00000	0.00	LINEAR	6.943298E-02	-126.94	2.714986E-11	-23.81
335.00	0.	-8.89	-197.55	-8.89	0.00000	0.00	LINEAR	6.883308E-02	-131.80	2.568977E-11	-19.53
340.00	0.	-8.71	-198.02	-8.71	0.00000	0.00	LINEAR	7.108298E-02	-137.21	2.434917E-11	-15.11
345.00	0.	-8.46	-198.46	-8.46	0.00000	0.00	LINEAR	7.313998E-02	-145.72	2.311988E-11	-10.61
350.00	0.	-8.23	-198.88	-8.23	0.00000	0.00	LINEAR	7.510377E-02	-154.27	2.203168E-11	-6.10
355.00	0.	-8.09	-199.27	-8.09	0.00000	0.00	LINEAR	7.631668E-02	-163.08	2.107818E-11	-1.65
360.00	0.	-8.11	-199.61	-8.11	0.00000	0.00	LINEAR	7.618798E-02	-172.26	2.025868E-11	2.80

***** DATA CARD NO. 5 EX -0 2 1 -0 1.000000E+00 0. 0. 0. 0. 0.
***** DATA CARD NO. 6 XQ -0 -0 -0 -0 0. 0. 0. 0. 0. 0.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO.	VOLTAGE (VOLTS) REAL	VOLTAGE (VOLTS) IMAG.	CURRENT (AMPS) REAL	CURRENT (AMPS) IMAG.	IMPEDANCE (OHMS) REAL	IMPEDANCE (OHMS) IMAG.	ADMITTANCE (MHOS) REAL	ADMITTANCE (MHOS) IMAG.	POWER (WATTS)
2	5	1.000000E+00	0.	1.502998E-02	-6.913228E-03	5.498528E+01	2.527038E+01	1.502998E-02	-6.913228E-03	7.512998E-03

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	1	0.	0.	0.1942	0.04662	-8.0950E-04	1.7194E-03	1.9387E-03	117.629
2	1	0.	0.	0.2408	0.04662	-7.8758E-04	1.5063E-03	1.6999E-03	117.605
3	1	0.	0.	0.2875	0.04662	-5.5897E-04	1.0990E-03	1.2341E-03	117.170
4	1	0.	0.	0.3341	0.04662	-2.2527E-04	4.5625E-04	5.1017E-04	116.580
5	2	0.1827	0.	0.	0.05470	1.5029E-02	-6.9132E-03	1.6540E-02	-24.707
6	2	0.2374	0.	0.	0.05470	1.3800E-02	-7.4043E-03	1.5661E-02	-28.216
7	2	0.2921	0.	0.	0.05470	1.1401E-02	-6.7808E-03	1.3268E-02	-30.740
8	2	0.3468	0.	0.	0.05470	7.8887E-03	-5.0218E-03	9.3518E-03	-32.477
9	2	0.4015	0.	0.	0.05470	3.2560E-03	-2.1818E-03	3.9193E-03	-33.821

- - - - SURFACE PATCH CURRENTS - - - -

DISTANCE IN WAVELENGTHS
CURRENT IN AMPS/METER

PATCH CENTER X	Y	Z	- - SURFACE COMPONENTS - - TANGENT VECTOR 1 MAG.	PHASE	TANGENT VECTOR 2 MAG.	PHASE	- - - RECTANGULAR COMPONENTS - - - X REAL	X IMAG.	Y REAL	Y IMAG.	Z REAL	Z IMAG.
1												
0.155	0	0.114	2.5768E-12	-142.35	4.0390E-02	140.22	0.	0.	-2.04E-12	-1.57E-12	-3.10E-02	2.58E-02
2												
0.155	0.024	0.024	8.6315E-02	153.29	8.8950E-02	152.98	0.	0.	-7.71E-02	3.08E-02	-7.92E-02	4.04E-02
3												
0.155	-0.024	0.024	8.6315E-02	-26.71	8.8950E-02	152.98	0.	0.	7.71E-02	-3.08E-02	-7.92E-02	4.04E-02
4												
0.155	-0.024	-0.024	8.6312E-02	-26.71	8.1286E-02	-26.18	0.	0.	7.71E-02	-3.08E-02	8.19E-02	-4.02E-02
5												
0.155	0.024	-0.024	8.6312E-02	153.29	8.1286E-02	-26.18	0.	0.	-7.71E-02	3.08E-02	8.19E-02	-4.02E-02
6												
0.155	0.	-0.114	2.6984E-12	-130.94	4.1814E-02	-37.70	0	0.	-1.77E-12	-2.04E-12	3.31E-02	-2.56E-02
7												
0.135	0.078	0.114	1.7533E-02	121.83	2.2201E-02	129.65	4.62E-03	-7.45E-03	-8.01E-03	1.29E-02	-1.42E-02	1.71E-02

```
 8
 0.135  0.078  0.     3.7641E-02  141.92  1.3236E-03    2.35  1.48E-02 -1.18E-02 -2.57E-02  2.01E-02  1.32E-03  5.43E-05
 9
 0.135  0.078 -0.114  1.7516E-02  121.84  2.3097E-02  -45.71  4.62E-03 -7.44E-03 -8.00E-03  1.29E-02  1.61E-02 -1.65E-02
10
 0.107  0.      0.171  2.0213E-02  -99.04  1.3922E-11  -60.82  1.75E-03 -2.01E-02  6.83E-12 -1.21E-11  0.         0.
11
 0.107  0.     -0.171  1.6874E-02  -97.11  1.4404E-11  121.30  8.52E-04 -1.69E-02  7.48E-12 -1.23E-11  0.         0.
12
 0.078  0.135  0.114  1.6710E-02   87.52  6.2225E-03  106.04 -6.27E-04 -1.49E-02  3.82E-04  8.35E-03 -1.72E-03  9.99E-03
13
 0.078  0.135  0.     1.5787E-02  103.80  1.3328E-03    2.80  3.19E-03 -1.33E-02 -1.84E-03  7.67E-03  1.33E-03  8.52E-05
14
 0.078  0.135 -0.114  1.6854E-02   87.45  6.8118E-03  -58.50 -6.43E-04 -1.44E-02  3.71E-04  8.32E-03  3.76E-03 -5.68E-03
15
-0.000  0.155  0.114  1.3965E-02   98.84  1.7990E-03   99.81 -7.88E-03 -1.15E-02 -1.09E-12 -1.60E-12  5.84E-06  1.80E-03
16
-0.000  0.155  0.     1.1870E-02   80.49  1.3310E-03    3.41 -5.75E-03 -1.02E-02 -7.98E-13 -1.41E-12  1.33E-03  7.93E-05
17
-0.000  0.155 -0.114  1.3951E-02   55.62  2.2807E-03  -31.00 -7.88E-03 -1.15E-02 -1.09E-12 -1.59E-12  1.95E-03 -1.17E-03
18
 0.094  0.093  0.171  9.8477E-03  -98.11  1.6574E-02   70.79 -5.11E-03 -1.79E-02  1.40E-03 -8.33E-04  0.         0.
19
 0.094  0.093 -0.171  6.8731E-03 -109.90  1.5942E-02 -109.84 -8.59E-03 -1.98E-02  6.24E-04  1.98E-03  0.         0.
20
-0.078  0.135  0.114  1.2623E-02   34.29  1.5699E-03  179.32 -8.03E-03 -8.18E-03 -5.22E-03 -3.95E-03 -1.57E-03  1.86E-05
21
-0.078  0.135  0.     9.6163E-03   34.25  1.3372E-03    3.20 -6.88E-03 -4.69E-03 -3.97E-03 -2.71E-03  1.33E-03  7.65E-05
22
-0.078  0.135 -0.114  1.2602E-02   34.42  3.6442E-03    5.05 -8.00E-03 -8.17E-03 -5.20E-03 -3.96E-03  3.63E-03  3.21E-04
23
-0.135  0.078  0.114  6.7433E-03   22.42  4.2068E-03 -179.29 -3.18E-03 -1.29E-03 -9.40E-03 -2.23E-03 -4.21E-03 -5.18E-05
24
-0.135  0.078  0.     5.6061E-03   21.56  1.3441E-03    3.20 -2.61E-03 -1.03E-03 -4.52E-03 -1.78E-03  1.34E-03  7.61E-05
25
-0.135  0.078 -0.114  6.7309E-03   22.44  6.2418E-03    5.87 -3.11E-03 -1.29E-03 -5.39E-03 -2.22E-03  6.20E-03  6.81E-04
26
-0.094  0.093  0.171  5.5923E-03    3.15  1.3634E-02   38.74 -1.20E-02 -7.84E-03 -4.82E-04 -4.00E-03  0.         0.
27
-0.094  0.093 -0.171  5.8822E-03   37.27  1.3609E-02 -141.24 -1.15E-02 -9.18E-03 -1.25E-03 -1.18E-03  0.         0.
28
-0.155 -0.000  0.114  3.2230E-12  143.29  4.2242E-03  178.48 -1.08E-21  7.90E-22  8.58E-12 -1.83E-12 -4.28E-03  1.12E-04
29
-0.155 -0.000  0.     4.1149E-12  115.22  1.3471E-03    3.05 -7.19E-22  1.53E-21  1.75E-12 -3.72E-12  1.35E-03  7.18E-05
30
-0.155 -0.000 -0.114  3.3315E-12  142.78  6.3084E-03    2.13 -1.09E-21  8.27E-22  2.65E-12 -2.02E-12  6.30E-03  2.34E-04
31
-0.135 -0.078  0.114  6.7433E-03 -157.58  4.2068E-03 -179.29 -3.18E-03 -1.29E-03  5.40E-03  2.23E-03 -4.21E-03 -5.18E-05
32
-0.135 -0.078  0.     5.6061E-03 -158.44  1.3441E-03    3.20 -2.61E-03 -1.03E-03  4.52E-03  1.78E-03  1.34E-03  7.61E-05
33
-0.135 -0.078 -0.114  6.7305E-03 -157.56  6.2419E-03    5.87 -3.11E-03 -1.29E-03  5.39E-03  2.22E-03  6.20E-03  6.81E-04
34
-0.107 -0.000  0.171  1.1520E-02    9.48  3.0306E-12  159.12 -1.14E-02 -1.90E-03 -1.83E-12 -1.06E-12  0.         0.
35
-0.107 -0.000 -0.171  1.1848E-02   26.24  3.1761E-12  -21.29 -1.04E-02 -5.15E-03 -1.33E-12 -3.27E-12  0.         0.
36
-0.078 -0.135  0.114  1.2623E-02 -145.72  1.5699E-03  179.32 -8.03E-03 -8.18E-03  5.22E-03  3.95E-03 -1.57E-03  1.86E-05
37
-0.078 -0.135  0.     9.6163E-03 -145.75  1.3372E-03    3.20 -6.88E-03 -4.69E-03  3.97E-03  2.71E-03  1.33E-03  7.65E-05
38
-0.078 -0.135 -0.114  1.2602E-02 -145.58  3.6442E-03    5.05 -8.00E-03 -8.17E-03  5.20E-03  3.96E-03  3.63E-03  3.21E-04
39
 0.000 -0.155  0.114  1.3965E-02 -124.36  1.7990E-03   99.81 -7.88E-03 -1.15E-02 -4.32E-12 -6.32E-12  5.84E-06  1.80E-03
40
 0.000 -0.155  0.     1.1870E-02 -119.52  1.3310E-03    3.41 -5.75E-03 -1.02E-02 -3.15E-12 -5.57E-12  1.33E-03  7.93E-05
41
 0.000 -0.155 -0.114  1.3951E-02 -124.38  2.2807E-03  -31.00 -7.88E-03 -1.15E-02 -4.32E-12 -6.32E-12  1.95E-03 -1.17E-03
42
-0.094 -0.093  0.171  5.5923E-03    3.15  1.3634E-02 -141.26 -1.20E-02 -7.84E-03  4.82E-04  4.00E-03  0.         0.
43
-0.094 -0.093 -0.171  5.8822E-03   37.27  1.3609E-02   38.76 -1.15E-02 -9.18E-03  1.25E-03  1.18E-03  0.         0.
44
 0.078 -0.135  0.114  1.6710E-02  -92.48  6.2225E-03  106.04 -6.27E-04 -1.49E-02 -3.82E-04 -8.35E-03 -1.72E-03  9.99E-03
45
 0.078 -0.135  0.     1.5787E-02  -76.80  1.3328E-03    2.80  3.18E-03 -1.33E-02  1.84E-03 -7.67E-03  1.33E-03  8.52E-05
46
 0.078 -0.135 -0.114  1.6854E-02  -92.55  6.8118E-03  -58.50 -6.43E-04 -1.44E-02 -3.71E-04 -8.32E-03  3.76E-03 -5.68E-03
47
 0.135 -0.078  0.114  1.7533E-02  -58.17  2.2201E-02  129.65  4.62E-03 -7.49E-03  8.01E-03 -1.29E-02 -1.49E-02  1.71E-02
48
 0.135 -0.078  0      3.7641E-02  -38.08  1.3236E-03    2.35  1.48E-02 -1.18E-02  2.57E-02 -2.01E-02  1.32E-03  5.43E-05
```

```
48
0.136 -0.079 -0.114 1.7516E-02  -58.17 2.3097E-02  -45.71  4.62E-03 -7.44E-03  9.00E-03 -1.29E-02  1.61E-02 -1.65E-02
50
0.054 -0.093  0.171 9.5477E-03  -98.11 1.9574E-02 -109.22 -5.11E-03 -1.79E-02 -1.40E-03  8.33E-04  0.        0.
51
0.054 -0.093 -0.171 8.5731E-03 -109.90 1.9842E-02   70.78 -8.98E-03 -1.88E-02 -8.24E-04 -1.88E-03  0.        0.
52
0.026  0.026  0.171 2.0111E-02  -97.14 8.8900E-03  -62.33 -2.90E-03 -2.00E-02  4.04E-03 -7.70E-03  0.        0.
53
-0.026  0.026  0.171 1.2874E-02 -174.09 8.9442E-03  -64.91 -1.29E-02 -1.38E-03  3.08E-03 -8.07E-03  0.        0.
54
-0.026 -0.026  0.171 1.2874E-02 -174.09 8.9442E-03  115.49 -1.29E-02 -1.38E-03 -3.08E-03  8.07E-03  0.        0.
55
0.026 -0.026  0.171 2.0111E-02  -97.14 8.8900E-03  117.87 -2.90E-03 -2.00E-02 -4.04E-03  7.70E-03  0.        0.
56
0.     0.    -0.171 1.3088E-02 -126.31 4.7378E-12   89.35 -7.79E-03 -1.08E-02 -3.84E-13 -4.78E-12  0.        0.
```

- - - POWER BUDGET - - -

INPUT POWER = 7.5130E-03 WATTS
RADIATED POWER= 7.5130E-03 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

- - - ISOLATION DATA - - -

- - COUPLING BETWEEN - -				MAXIMUM	- - - FOR MAXIMUM COUPLING - - -			
	SEG.		SEG.	COUPLING	LOAD IMPEDANCE (2ND SEG.)		INPUT IMPEDANCE	
TAG/SEG.	NO.	TAG/SEG.	NO.	(DB)	REAL	IMAG.	REAL	IMAG.
1 1	1	2 1	5	-13.708	5.5824E+01	-2.0638E+01	1.8229E+01	-1.1843E+02

```
***** DATA CARD NO.  7   EN  -0    -0    -0    -0  0.          0.          0.          0.          0.          0.
```

RUN TIME = 12.698

EXAMPLES 7 AND 8, SCATTERING BY A WIRE AND AIRCRAFT

Examples 7 and 8 demonstrate the use of NEC for scattering. The columns labeled "gain" are, in this case, scattering cross section in square wavelengths (σ/λ^2). Example 8 is a stick model of an aircraft as shown in figure 19.

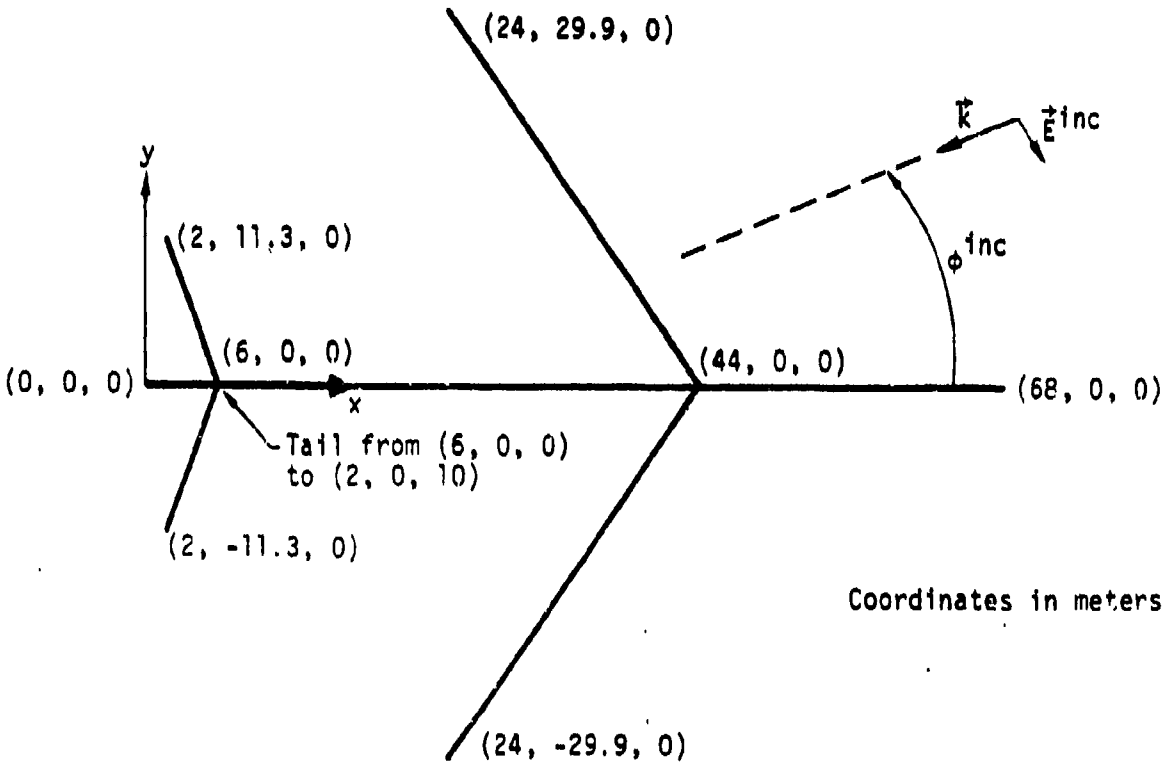


Figure 19. Stick model of aircraft.

Examples 7 and 8 Input

```
'
CMSAMPLE PROBLEMS FOR NEC -  SCATTERING BY A WIRE
CM    1. STRAIGHT WIRE - FREE SPACE
CM    2. STRAIGHT WIRE - PERFECT GROUND
CM    3. STRAIGHT WIRE - FINITELY CONDUCTING GROUND
CE                       (SIG.=1.E-4 MHOS/M., EPS.=6.)
GW  0   15   -99.      0.        10.       99.       0.        10.       .01
GE  1
FR  0    1    0    0   3.
EX  1    2    1    0   0.        0.        0.        45.       0.
RP  0    2    1 1000   0.        0.        45.       0.
GN  1
EX  1    1    1    0   45.       0.        0.
RP  0   19    1 1000   90.       0.        -10.      0.
GN                     6.     1.000E-04
RP  0   19    1 1000   90.       0.        -10.      0.
NX
CMSAMPLE PROBLEM FOR NEC
CESTICK MODEL OF AIRCRAFT - FREE SPACE
GW  1    1   0.        0.        0.        6.        0.        0.        1.
GW  2    6   6.        0.        0.        44.       0.        0.        1.
GW  3    4   44.       0.        0.        68.       0.        0.        1.
GW  4    6   44.       0.        0.        24.       29.9      0.        1.
GW  5    6   44.       0.        0.        24.       -29.5     0.        1.
GW  6    2   6.        0.        0.        2.        11.3      0.        1.
GW  7    2   6.        0.        0.        2.        -11.3     0.        1.
GW  8    2   6.        0.        0.        2.        0.        10.       1.
GE
FR  0    1    0    0   3.
EX  1    1    1    0   0.        0.        0.
RP  0    1    1 1000   0.        0.        0.
EX  1    1    1    0   90.       30        -90.
RP  0    1    1 1000   90.       30.
EN
```

Examples 7 and 8 Output

```
**********************************

   NUMERICAL ELECTROMAGNETICS CODE

**********************************


- - - - COMMENTS - - - -

SAMPLE PROBLEMS FOR NEC - SCATTERING BY A WIRE.
    1. STRAIGHT WIRE - FREE SPACE
    2. STRAIGHT WIRE - PERFECT GROUND
    3. STRAIGHT WIRE - FINITELY CONDUCTING GROUND
                       (SIG.=1.E-4 MHOS/M., EPS.=6.)


- - - STRUCTURE SPECIFICATION - - -

   COORDINATES MUST BE INPUT IN
   METERS OR BE SCALED TO METERS
   BEFORE STRUCTURE INPUT IS ENDED

WIRE                                                                NO. OF   FIRST  LAST   TAG
NO.       X1          Y1          Z1          X2          Y2          Z2       RADIUS  SEG.    SEG.   SEG.   NO.
   1  -55.00000    0.         10.00000    55.00000    0.         10.00000    0.01000    15       1     15     0

 GROUND PLANE SPECIFIED.

 WHERE WIRE ENDS TOUCH GROUND, CURRENT WILL BE INTERPOLATED TO IMAGE IN GROUND PLANE.

 TOTAL SEGMENTS USED=   15     NO. SEG. IN A SYMMETRIC CELL=   15     SYMMETRY FLAG=  0


        - MULTIPLE WIRE JUNCTIONS -
JUNCTION    SEGMENTS  (- FOR END 1, + FOR END 2)
 NONE


- - - - SEGMENTATION DATA - - - -

   COORDINATES IN METERS

   1+ AND 1- INDICATE THE SEGMENTS BEFORE AND AFTER 1

SEG.    COORDINATES OF SEG. CENTER      SEG.      ORIENTATION ANGLES      WIRE      CONNECTION DATA      TAG
NO.        X          Y          Z      LENGTH      ALPHA      BETA      RADIUS     1-     1     1+     NO.
   1  -51.33333    0.         10.00000   7.33333    0.         0.        0.01000     0     1     2      0
   2  -44.00000    0.         10.00000   7.33333    0.         0.        0.01000     1     2     3      0
   3  -36.66667    0.         10.00000   7.33333    0.         0.        0.01000     2     3     4      0
   4  -29.33333    0.         10.00000   7.33333    0.         0.        0.01000     3     4     5      0
   5  -22.00000    0.         10.00000   7.33333    0.         0.        0.01000     4     5     6      0
   6  -14.66667    0.         10.00000   7.33333    0.         0.        0.01000     5     6     7      0
   7   -7.33333    0.         10.00000   7.33333    0.         0.        0.01000     6     7     8      0
   8   -0.00000    0.         10.00000   7.33333    0.         0.        0.01000     7     8     9      0
   9    7.33333    0.         10.00000   7.33333    0.         0.        0.01000     8     9    10      0
  10   14.66667    0.         10.00000   7.33333    0.         0.        0.01000     9    10    11      0
  11   22.00000    0.         10.00000   7.33333    0.         0.        0.01000    10    11    12      0
  12   29.33333    0.         10.00000   7.33333    0.         0.        0.01000    11    12    13      0
  13   36.66667    0.         10.00000   7.33333    0.         0.        0.01000    12    13    14      0
  14   44.00000    0.         10.00000   7.33333    0.         0.        0.01000    13    14    15      0
  15   51.33333    0.         10.00000   7.33333    0.         0.        0.01000    14    15     0      0


***** DATA CARD NO.  1  FR  0   1    0    0  3.00000E+00  0.          0.          0.          0.          0.
***** DATA CARD NO.  2  EX  1   2    1    0  0            0.          0.          4.50000E+01 0.          0.
***** DATA CARD NO.  3  RP  0   2    1 1000  0.           0.          4.50000E+01 0.          0.          0.
```

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 3.0000E+00 MHZ
WAVELENGTH= 9.9933E+01 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE

- - - MATRIX TIMING - - -

FILL= 0.083 SEC., FACTOR= 0.010 SEC.

- - - EXCITATION - - -

PLANE WAVE THETA= 0. DEG. PHI= 0. DEG. ETA= 0. DEG. TYPE =LINEAR= AXIAL RATIO=-0.

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	0	-0.5137	0.	0.1001	0.07338	-8.8823E-04	2.5872E-03	2.7186E-03	109.089
2	0	-0.4403	0.	0.1001	0.07338	1.5904E-03	2.1079E-03	2.7176E-03	53.979
3	0	-0.3669	0.	0.1001	0.07338	8.8156E-03	-4.2490E-03	9.7861E-03	-25.734
4	0	-0.2935	0.	0.1001	0.07338	1.9218E-02	-1.4937E-02	2.4338E-02	-37.998
5	0	-0.2201	0.	0.1001	0.07338	3.0734E-02	-2.7408E-02	4.1180E-02	-41.726
6	0	-0.1468	0.	0.1001	0.07338	4.1101E-02	-3.8982E-02	5.6609E-02	-43.440
7	0	-0.0734	0.	0.1001	0.07338	4.8271E-02	-4.6991E-02	6.7367E-02	-44.230
8	0	-0.0000	0.	0.1001	0.07338	5.0829E-02	-4.9887E-02	7.1220E-02	-44.484
9	0	0.0734	0.	0.1001	0.07338	4.8271E-02	-4.6991E-02	6.7367E-02	-44.230
10	0	0.1468	0.	0.1001	0.07338	4.1101E-02	-3.8982E-02	5.6609E-02	-43.440
11	0	0.2201	0.	0.1001	0.07338	3.0734E-02	-2.7408E-02	4.1180E-02	-41.726
12	0	0.2935	0.	0.1001	0.07338	1.9218E-02	-1.4937E-02	2.4338E-02	-37.998
13	0	0.3669	0.	0.1001	0.07338	8.8156E-03	-4.2490E-03	9.7861E-03	-25.734
14	0	0.4403	0.	0.1001	0.07338	1.5904E-03	2.1079E-03	2.7176E-03	53.979
15	0	0.5137	0.	0.1001	0.07338	-8.8823E-04	2.5872E-03	2.7186E-03	109.089

- - - RADIATION PATTERNS - - -

- - ANGLES - - THETA DEGREES	PHI DEGREES	- POWER GAINS - VERT. DB	HOR. DB	TOTAL DB	- - - POLARIZATION - - - AXIAL RATIO	TILT DEG.	SENSE	- - - E(THETA) - - - MAGNITUDE VOLTS/M	PHASE DEGREES	- - - E(PHI) - - - MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	-12.86	-999.99	-12.86	0.	0.	LINEAR	6.41328E+00	-99.83	0.	0.
45.00	0.	-18.33	-999.99	-18.33	0.	0.	LINEAR	3.41597E+00	-108.66	0.	0.

- - - EXCITATION - - -

PLANE WAVE THETA= 45.00 DEG. PHI= 0. DEG. ETA= 0. DEG. TYPE =LINEAR= AXIAL RATIO=-0.

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	0	-0.5137	0.	0.1001	0.07338	-1.4018E-02	-2.8708E-02	3.0182E-02	-117.895
2	0	-0.4403	0.	0.1001	0.07338	-3.9114E-02	-6.9420E-02	7.9681E-02	-119.388
3	0	-0.3669	0.	0.1001	0.07338	-5.8271E-02	-9.8999E-02	1.1316E-01	-120.995
4	0	-0.2935	0.	0.1001	0.07338	-6.7872E-02	-1.0687E-01	1.2660E-01	-122.420
5	0	-0.2201	0.	0.1001	0.07338	-6.5359E-02	-9.8633E-02	1.1838E-01	-123.530
6	0	-0.1468	0.	0.1001	0.07338	-5.0273E-02	-7.4956E-02	9.0258E-02	-123.849
7	0	-0.0734	0.	0.1001	0.07338	-2.4529E-02	-4.1065E-02	4.7838E-02	-120.860
8	0	-0.0000	0.	0.1001	0.07338	7.0285E-03	-3.6791E-03	8.0498E-03	-25.172
9	0	0.0734	0.	0.1001	0.07338	4.1299E-02	3.0302E-02	5.1220E-02	36.271
10	0	0.1468	0.	0.1001	0.07338	6.9810E-02	5.8139E-02	9.0937E-02	39.263
11	0	0.2201	0.	0.1001	0.07338	8.8359E-02	6.7301E-02	1.1107E-01	37.287
12	0	0.2935	0.	0.1001	0.07338	9.2958E-02	6.8029E-02	1.1402E-01	36.386
13	0	0.3669	0.	0.1001	0.07338	8.2371E-02	5.3309E-02	9.8118E-02	32.910
14	0	0.4403	0.	0.1001	0.07338	5.7746E-02	3.3261E-02	6.6640E-02	29.941
15	0	0.5137	0.	0.1001	0.07338	2.1820E-02	1.0871E-02	2.4378E-02	26.483

- - - RADIATION PATTERNS - - -

- - ANGLES - - THETA DEGREES	PHI DEGREES	- POWER GAINS - VERT. DB	HOR. DB	TOTAL DB	- - - POLARIZATION - - - AXIAL RATIO	TILT DEG.	SENSE	- - - E(THETA) - - - MAGNITUDE VOLTS/M	PHASE DEGREES	- - - E(PHI) - - - MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	-18.38	-999.99	-18.38	0.	0.	LINEAR	3.39898E+00	-108.66	0.	0.
45.00	0.	-10.40	-999.99	-10.40	0.	0.	LINEAR	8.91378E+00	71.99	0.	0.

***** DATA CARD NO.	4	GN	1	-0	-0	-0	0.	0.	0.	0.	0.	0.	0.
***** DATA CARD NO.	5	EX	1	1	1	0	4.50000E+01	0.	0.	0.	0.	0.	0.
***** DATA CARD NO.	6	RP	0	19	1	1000	9.00000E+01	0.	-1.00000E+01	0.	0.	0.	0.

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
PERFECT GROUND

- - - MATRIX TIMING - - -

FILL= 0.142 SEC., FACTOR= 0.010 SEC.

- - - EXCITATION - - -

PLANE WAVE THETA= 45.00 DEG, PHI= 0. DEG, ETA= 0. DEG, TYPE -LINEAR= AXIAL RATIO=-0.

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG NO	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	0	-0.5137	0.	0.1001	0.07338	9.9565E-03	-2.2201E-02	2.4211E-02	-66.493
2	0	-0.4403	0.	0.1001	0.07338	2.3109E-02	-6.0450E-02	6.4745E-02	-69.013
3	0	-0.3669	0.	0.1001	0.07338	2.9784E-02	-9.0239E-02	9.3124E-02	-71.359
4	0	-0.2935	0.	0.1001	0.07338	2.9989E-02	-1.0121E-01	1.0556E-01	-73.495
5	0	-0.2201	0.	0.1001	0.07338	2.5316E-02	-9.6764E-02	1.0008E-01	-75.338
6	0	-0.1468	0.	0.1001	0.07338	1.7898E-02	-7.9365E-02	7.7489E-02	-76.569
7	0	-0.0734	0.	0.1001	0.07338	1.0530E-02	-4.0581E-02	4.1898E-02	-75.484
8	0	-0.0000	0.	0.1001	0.07338	5.0481E-03	1.5152E-03	5.2708E-03	16.708
9	0	0.0734	0.	0.1001	0.07338	2.8275E-03	4.3477E-02	4.3569E-02	86.279

10	0	0.1468	0.	0.1001	0.07338	4.0010E-03	7.7881E-02	7.7884E-02	87.059
11	0	0.2201	0.	0.1001	0.07338	7.5610E-03	9.8725E-02	9.9014E-02	85.620
12	0	0.2935	0.	0.1001	0.07338	1.1639E-02	1.0254E-01	1.0320E-01	83.524
13	0	0.3669	0.	0.1001	0.07338	1.3998E-02	8.8976E-02	9.0073E-02	81.061
14	0	0.4403	0.	0.1001	0.07338	1.2568E-02	6.0735E-02	6.2024E-02	78.296
15	0	0.5137	0.	0.1001	0.07338	5.8541E-03	2.2837E-02	2.2984E-02	75.251

- - - RADIATION PATTERNS - - -

- - ANGLES - -		- POWER GAINS -			- - - POLARIZATION - - -			- - - E(THETA) - - -		- - - E(PHI) - - -	
THETA DEGREES	PHI DEGREES	VERT. DB	HOR. DB	TOTAL DB	AXIAL RATIO	TILT DEG.	SENSE	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES
90.00	0.	-999.99	-999.99	-999.99	0.	0.		3.519195E-22	-178.80	0.	0.
80.00	0.	-38.78	-999.99	-38.78	0.	0.	LINEAR	4.083777E-01	-178.83	0.	0.
70.00	0.	-24.91	-999.99	-24.91	0.	0.	LINEAR	1.808232E+00	-178.47	0.	0.
60.00	0.	-18.29	-999.99	-18.29	0.	0.	LINEAR	3.431811E+00	-178.38	0.	0.
50.00	0.	-14.20	-999.99	-14.20	0.	0.	LINEAR	5.499833E+00	-178.28	0.	0.
40.00	0.	-12.00	-999.99	-12.00	0.	0.	LINEAR	7.083475E+00	-178.08	0.	0.
30.00	0.	-11.77	-999.99	-11.77	0.	0.	LINEAR	7.870188E+00	-174.81	0.	0.
20.00	0.	-14.39	-999.99	-14.39	0.	0.	LINEAR	8.377882E+00	-170.28	0.	0.
10.00	0.	-25.57	-999.99	-25.57	0.	0.	LINEAR	1.489182E+00	-170.99	0.	0.
0.	0.	-18.38	-999.99	-18.38	0.	0.	LINEAR	3.399330E+00	3.10	0.	0.
-10.00	0.	-11.31	-999.99	-11.31	0.	0.	LINEAR	7.867114E+00	4.34	0.	0.
-20.00	0.	-8.98	-999.99	-8.98	0.	0.	LINEAR	1.008508E+01	4.77	0.	0.
-30.00	0.	-8.95	-999.99	-8.95	0.	0.	LINEAR	1.008328E+01	5.06	0.	0.
-40.00	0.	-10.60	-999.99	-10.60	0.	0.	LINEAR	8.316018E+00	5.29	0.	0.
-50.00	0.	-13.78	-999.99	-13.78	0.	0.	LINEAR	5.771982E+00	5.48	0.	0.
-60.00	0.	-18.59	-999.99	-18.59	0.	0.	LINEAR	3.317982E+00	5.66	0.	0.
-70.00	0.	-25.71	-999.99	-25.71	0.	0.	LINEAR	1.480902E+00	5.83	0.	0.
-80.00	0.	-37.80	-999.99	-37.80	0.	0.	LINEAR	3.991782E-01	5.98	0.	0.
-90.00	0.	-999.99	-999.99	-999.99	0.	0.		3.055656E-22	5.99	0.	0.

***** DATA CARD NO. 7 GN -0 -0 -0 -0 8.00000E+00 1.00000E-04 0. 0. 0. 0.
***** DATA CARD NO. 8 RP 0 19 1 1000 9.00000E+01 0. -1.00000E+01 0. 0. 0.

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FINITE GROUND REFLECTION COEFFICIENT APPROXIMATION
RELATIVE DIELECTRIC CONST.= 6.000
CONDUCTIVITY= 1.000E-04 MHOS/METER
COMPLEX DIELECTRIC CONSTANT= 6.00000E+00-5.99200E-01

- - - MATRIX TIMING - - -

FILL= 0.154 SEC., FACTOR= 0.010 SEC.

- - - EXCITATION - - -

PLANE WAVE THETA= 45.00 DEG. PHI= 0. DEG. ETA= 0. DEG. TYPE -LINEAR= AXIAL RATIO=-0.

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO	TAG NO	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	0	-0.5137	0.	0.1001	0.07338	-7.4247E-03	-2.3607E-02	2.4747E-02	-107.459
2	0	-0.4403	0.	0.1001	0.07338	-8.1838E-02	-8.1988E-02	8.5687E-02	-109.413
3	0	-0.3669	0.	0.1001	0.07338	-3.3971E-02	-8.7378E-02	9.3748E-02	-111.245

4	0	-0.2935	0.	0.1001	0.07338	-4.1013E-02	-9.7068E-02	1.0538E-01	-112.905
5	0	-0.2201	0.	0.1001	0.07338	-4.0667E-02	-9.0199E-02	9.8942E-02	-114.268
6	0	-0.1468	0.	0.1001	0.07338	-3.1928E-02	-8.6766E-02	7.5817E-02	-114.805
7	0	-0.0734	0.	0.1001	0.07338	-1.9433E-02	-3.7267E-02	4.0336E-02	-112.496
8	0	-0.0000	0.	0.1001	0.07338	6.5278E-03	-1.8008E-03	6.7717E-03	-15.423
9	0	0.0734	0.	0.1001	0.07338	3.0350E-02	3.1125E-02	4.3473E-02	45.723
10	0	0.1468	0.	0.1001	0.07338	5.1732E-02	5.5859E-02	7.6134E-02	47.197
11	0	0.2201	0.	0.1001	0.07338	6.6473E-02	6.9852E-02	9.6461E-02	45.824
12	0	0.2935	0.	0.1001	0.07338	7.1286E-02	6.8296E-02	9.8722E-02	43.773
13	0	0.3669	0.	0.1001	0.07338	6.4446E-02	5.8217E-02	8.6520E-02	41.099
14	0	0.4403	0.	0.1001	0.07338	4.8116E-02	3.8001E-02	6.1304E-02	37.978
15	0	0.5137	0.	0.1001	0.07338	1.7790E-02	1.2195E-02	2.1568E-02	34.432

- - - RADIATION PATTERNS - - -

- - ANGLES - -		- POWER GAINS -			- - - POLARIZATION - - -			- - - E(THETA) - - -		- - - E(PHI) - - -	
THETA DEGREES	PHI DEGREES	VERT. DB	HOR. DB	TOTAL DB	AXIAL RATIO	TILT DEG.	SENSE	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES
90.00	0.	-999.99	-999.99	-999.99	0.	0.		1.0826E-10	-129.89	0.	0.
90.00	0.	-21.13	-999.99	-21.13	0.	0.	LINEAR	2.4785E+00	97.90	0.	0.
70.00	0	-17.33	-999.99	-17.33	0.	0.	LINEAR	3.8334E+00	88.96	0.	0.
60.00	0.	-15.22	-999.99	-15.22	0.	0.	LINEAR	4.8806E+00	78.85	0.	0.
50.00	0.	-13.63	-999.99	-13.63	0.	0.	LINEAR	5.8689E+00	91.02	0.	0.
40.00	0.	-12.74	-999.99	-12.74	0.	0.	LINEAR	6.5003E+00	101.35	0.	0
30.00	0.	-13.18	-999.99	-13.18	0.	0.	LINEAR	6.1787E+00	109.14	0.	0.
20.00	0.	-16.17	-999.99	-16.17	0.	0.	LINEAR	4.3812E+00	115.33	0.	0.
10.00	0.	-27.81	-999.99	-27.81	0.	0.	LINEAR	1.1467E+00	129.38	0.	0.
0.	0.	-19.82	-999.99	-19.82	0.	0.	LINEAR	2.8784E+00	-70.02	0.	0.
-10.00	0.	-12.92	-999.99	-12.92	0.	0.	LINEAR	6.3684E+00	-67.00	0.	0.
-20.00	0.	-10.50	-999.99	-10.50	0.	0.	LINEAR	8.4141E+00	-68.17	0.	0.
-30.00	0.	-10.18	-999.99	-10.18	0.	0.	LINEAR	8.7334E+00	-71.81	0.	0.
-40.00	0.	-11.20	-999.99	-11.20	0.	0.	LINEAR	7.7634E+00	-78.11	0.	0.
-50.00	0.	-13.08	-999.99	-13.08	0.	0.	LINEAR	6.2988E+00	-87.34	0.	0.
-60.00	0.	-15.38	-999.99	-15.38	0.	0.	LINEAR	4.7995E+00	-98.85	0.	0.
-70.00	0.	-18.01	-999.99	-18.01	0.	0.	LINEAR	3.9470E+00	-110.27	0.	0.
-80.00	0.	-22.11	-999.99	-22.11	0.	0.	LINEAR	2.2104E+00	-118.80	0.	0.
-90.00	0.	-999.99	-999.99	-999.99	0.	0.		8.3892E-11	97.85	0.	0.

***** DATA CARD NO. 9 NX -0 -0 -0 -0 0. 0 0. 0. 0. 0.

****

NUMERICAL ELECTROMAGNETICS CODE

****

- - - - COMMENTS - - - -

SAMPLE PROBLEM FOR NEC
STICK MODEL OF AIRCRAFT - FREE SPACE

- - - STRUCTURE SPECIFICATION - - -

COORDINATES MUST BE INPUT IN
METERS OR BE SCALED TO METERS
BEFORE STRUCTURE INPUT IS ENDED

WIRE NO.	X1	Y1	Z1	X2	Y2	Z2	RADIUS	NO. OF SEG.	FIRST SEG.	LAST SEG.	TAG NO.
1	0.	0.	0.	6.00000	0.	0.	1.00000	1	1	1	1
2	6.00000	0.	0.	44.00000	0.	0.	1.00000	6	2	7	2
3	44.00000	0.	0	68.00000	0.	0.	1.00000	4	8	11	3
4	44.00000	0.	0.	24.00000	20.90000	0.	1.00000	6	12	17	4
5	44.00000	0.	0.	24.00000	-20.90000	0.	1.00000	6	18	23	5
6	6.00000	0.	0.	2.00000	11.30000	0.	1.00000	2	24	25	6
7	6.00000	0.	0.	2.00000	-11.30000	0.	1.00000	2	26	27	7
8	6.00000	0.	0.	2.00000	0.	10.00000	1.00000	2	28	29	8

TOTAL SEGMENTS USED= 29 NO. SEG. IN A SYMMETRIC CELL= 29 SYMMETRY FLAG= 0

- MULTIPLE WIRE JUNCTIONS -
(- FOR END 1, + FOR END 2)

JUNCTION	SEGMENTS				
1	1	-2	-24	-26	-28
2	7	-8	-12	-18	

- - - - SEGMENTATION DATA - - - -

COORDINATES IN METERS

(- AND + INDICATE THE SEGMENTS BEFORE AND AFTER I)

SEG. NO.	COORDINATES OF SEG. CENTER X	Y	Z	SEG LENGTH	ORIENTATION ANGLES ALPHA	BETA	WIRE RADIUS	CONNECTION DATA (-)	I	(+)	TAG NO.
1	3.00000	0.	0	6.00000	0.	0.	1.00000	0	1	2	1
2	9.16667	0.	0	6.33333	0.	0.	1.00000	-24	2	3	2
3	15.50000	0	0.	6.33333	0.	0.	1.00000	2	3	4	2
4	21.83333	0.	0.	6.33333	0.	0.	1.00000	3	4	5	2
5	28.16667	0.	0.	6.33333	0.	0.	1.00000	4	5	6	2
6	34.50000	0.	0.	6.33333	0	0.	1.00000	5	6	7	2
7	40.83333	0.	0.	6.33333	0.	0.	1.00000	6	7	8	2
8	47.00000	0.	0.	6.00000	0.	0.	1.00000	-12	8	9	3
9	53.00000	0.	0.	6.00000	0.	0.	1.00000	8	9	10	3
10	59.00000	0.	0.	6.00000	0.	0.	1.00000	9	10	11	3
11	65.00000	0.	0.	6.00000	0.	0.	1.00000	10	11	0	3
12	42.33333	2.48167	0.	5.99539	0.	123.77842	1.00000	-18	12	13	4
13	39.00000	7.47500	0.	5.99539	0.	123.77842	1.00000	12	13	14	4
14	35.66667	12.46833	0.	5.99539	0.	123.77842	1.00000	13	14	15	4
15	32.33333	17.46167	0.	5.99539	0.	123.77842	1.00000	14	15	16	4
16	29.00000	22.42500	0.	5.99539	0.	123.77842	1.00000	15	16	17	4
17	25.66667	27.40833	0.	5.99539	0.	123.77842	1.00000	16	17	0	4
18	42.33333	-2.48167	0.	5.99539	0.	-123.77842	1.00000	7	18	19	5
19	39.00000	-7.47500	0.	5.99539	0.	-123.77842	1.00000	18	19	20	5
20	35.66667	-12.46833	0.	5.99539	0.	-123.77842	1.00000	19	20	21	5
21	32.33333	-17.46167	0	5.99539	0.	-123.77842	1.00000	20	21	22	5
22	29.00000	-22.42500	0.	5.99539	0.	-123.77842	1.00000	21	22	23	5
23	25.66667	-27.40833	0.	5.99539	0.	-123.77842	1.00000	22	23	0	5
24	9.00000	2.82500	0.	5.99354	0.	109.49306	1.00000	-26	24	25	6
25	3.00000	8.47500	0.	5.99354	0.	109.49306	1.00000	24	25	0	6
26	9.00000	-2.82500	0.	5.99354	0.	-109.49306	1.00000	-28	26	27	7
27	3.00000	-8.47500	0.	5.99354	0.	-109.49306	1.00000	26	27	0	7
28	5.00000	0.	2.50000	5.38516	68.19859	180.00000	1.00000	1	28	29	8
29	3.00000	0	7.50000	5.38516	68.19859	180.00000	1.00000	28	29	0	8

```
***** DATA CARD NO.  1  FR  0  1   0    0  3.00000E+00  0.  0.  0.  0.  0.
***** DATA CARD NO.  2  EX  1  1   1    0  0.          0.  0.  0.  0.  0.
***** DATA CARD NO.  3  RP  0  1   1 1000  0           0.  0.  0.  0   0
```

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 3.0000E+00 MHZ
WAVELENGTH= 9.9933E+01 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE

- - - MATRIX TIMING - - -

FILL= 0.200 SEC., FACTOR= 0.062 SEC.

- - - EXCITATION - - -

PLANE WAVE THETA= 0. DEG. PHI= 0. DEG. ETA= 0. DEG. TYPE -LINEAR= AXIAL RATIO=-0.

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	1	0.0300	0.	0.	0.08004	1.4987E-03	4.6949E-03	4.9287E-03	72.295
2	2	0.0817	0.	0.	0.08338	3.2086E-02	-1.7022E-02	3.6331E-02	-27.930
3	2	0.1951	0.	0.	0.08338	3.7968E-02	-3.1078E-02	4.9084E-02	-39.303
4	2	0.2184	0.	0.	0.08338	4.4289E-02	-4.0460E-02	6.0398E-02	-48.151
5	2	0.2819	0.	0.	0.08338	4.9342E-02	-6.7068E-02	8.3264E-02	-53.858
6	2	0.3452	0.	0.	0.08338	5.2034E-02	-7.9829E-02	9.5290E-02	-56.903
7	2	0.4086	0.	0.	0.08338	5.1637E-02	-8.4841E-02	9.9320E-02	-58.674
8	3	0.4703	0.	0.	0.08004	2.0877E-01	-2.0895E-01	2.9537E-01	-45.024
9	3	0.5304	0.	0.	0.08004	1.7944E-01	-1.7850E-01	2.5239E-01	-45.010
10	3	0.5904	0.	0.	0.08004	1.2813E-01	-1.2792E-01	1.8077E-01	-44.885
11	3	0.6504	0.	0.	0.08004	5.9205E-02	-5.9276E-02	8.3074E-02	-44.947
12	4	0.4236	0.0249	0.	0.05999	-8.3233E-02	8.6192E-02	1.0634E-01	141.506
13	4	0.3903	0.0748	0.	0.05999	-8.3108E-02	8.5812E-02	1.0598E-01	141.709
14	4	0.3569	0.1247	0.	0.05999	-7.6189E-02	9.0728E-02	9.8179E-02	142.388
15	4	0.3235	0.1745	0.	0.05999	-6.2519E-02	4.6863E-02	7.7774E-02	143.499
16	4	0.2902	0.2244	0.	0.05999	-4.3490E-02	3.0212E-02	5.2959E-02	145.213
17	4	0.2568	0.2743	0.	0.05999	-1.9944E-02	1.2378E-02	2.3133E-02	147.657
18	5	0.4236	-0.0249	0.	0.05999	-8.3233E-02	8.6192E-02	1.0634E-01	141.506
19	5	0.3903	-0.0748	0.	0.05999	-8.3108E-02	8.5812E-02	1.0598E-01	141.709
20	5	0.3569	-0.1247	0.	0.05999	-7.6189E-02	9.0728E-02	9.8179E-02	142.388
21	5	0.3235	-0.1745	0.	0.05999	-6.2519E-02	4.6863E-02	7.7774E-02	143.499
22	5	0.2902	-0.2244	0.	0.05999	-4.3490E-02	3.0212E-02	5.2959E-02	145.213
23	5	0.2568	-0.2743	0.	0.05999	-1.9944E-02	1.2378E-02	2.3133E-02	147.657
24	6	0.0500	0.0283	0.	0.05998	-1.0118E-02	5.2353E-03	1.1392E-02	152.642
25	6	0.0300	0.0848	0.	0.05998	-4.8178E-03	1.7836E-03	4.9501E-03	159.880
26	7	0.0500	-0.0283	0.	0.05998	-1.0118E-02	5.2353E-03	1.1392E-02	152.642
27	7	0.0300	-0.0848	0.	0.05998	-4.8178E-03	1.7836E-03	4.9501E-03	159.880
28	8	0.0500	0.	0.0250	0.05389	-5.2940E-03	5.3490E-03	7.5230E-03	134.725
29	8	0.0300	0.	0.0751	0.05389	-1.5853E-03	2.0518E-03	2.5929E-03	127.691

- - - RADIATION PATTERNS - - -

- - ANGLES - - THETA DEGREES	PHI DEGREES	- POWER GAINS - VERT. DB	HOR. DB	TOTAL DB	- - - POLARIZATION - - - AXIAL RATIO	TILT DEG.	SENSE	- - - E(THETA) - - - MAGNITUDE VOLTS/M	PHASE DEGREES	- - - E(PHI) - - - MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	-2.98	-999.99	-2.98	0.00000	-0.00	LINEAR	2.00020E+01	-133.97	1.07231E-12	89.59

***** DATA CARD NO.	4	EX	1	1	1	0	9.00000E+01	3.00000E+01	-9.00000E+01	0.	0.	0.	0.	
***** DATA CARD NO.	5	RP	0	1	1	1000	9.00000E+01	3.00000E+01	0.	0.	0.	0.	0.	

- - - EXCITATION - - -

PLANE WAVE THETA= 90.00 DEG. PHI= 30.00 DEG. ETA= -90.00 DEG. TYPE -LINEAR- AXIAL RATIO=-0.

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG.	MAG.	PHASE
1	1	0.0300	0.	0.	0.06004	2.1952E-03	3.8163E-03	4.2304E-03	60.741
2	2	0.0917	0.	0.	0.06338	6.9490E-03	3.9228E-03	7.4328E-03	29.291
3	2	0.1551	0.	0.	0.06338	7.4381E-03	-9.7784E-03	9.4180E-03	-37.810
4	2	0.2185	0.	0.	0.06338	9.8857E-03	-1.9781E-02	2.2123E-02	-63.458
5	2	0.2819	0.	0.	0.06338	1.4283E-02	-3.5271E-02	3.8057E-02	-67.941
6	2	0.3452	0.	0.	0.06338	2.0095E-02	-4.8958E-02	5.2929E-02	-67.844
7	2	0.4086	0.	0.	0.06338	2.9574E-02	-5.7700E-02	6.3113E-02	-66.096
8	3	0.4703	0.	0.	0.06004	-3.8810E-02	1.9511E-01	1.9894E-01	103.978
9	3	0.5304	0.	0.	0.06004	-2.7543E-02	1.3176E-01	1.3461E-01	101.807
10	3	0.5904	0.	0.	0.06004	-1.4291E-02	9.3899E-02	9.5089E-02	98.648
11	3	0.6504	0.	0.	0.06004	-3.4931E-03	4.3257E-02	4.3398E-02	94.617
12	4	0.4236	0.0249	0.	0.05999	-2.3863E-02	-2.1177E-01	2.1308E-01	-96.378
13	4	0.3903	0.0748	0.	0.05999	-1.6402E-02	-2.0488E-01	2.0554E-01	-94.577
14	4	0.3569	0.1247	0.	0.05999	-7.9414E-03	-1.8818E-01	1.8835E-01	-92.462
15	4	0.3235	0.1745	0.	0.05999	-3.7954E-04	-1.4783E-01	1.4783E-01	-90.146
16	4	0.2902	0.2244	0.	0.05999	4.5370E-03	-1.0032E-01	1.0048E-01	-87.411
17	4	0.2568	0.2743	0.	0.05999	4.9311E-03	-4.4097E-02	4.4390E-02	-84.129
18	5	0.4236	-0.0249	0.	0.05999	9.4828E-02	-8.9035E-03	9.5046E-02	-5.375
19	5	0.3903	-0.0748	0.	0.05999	9.3142E-02	-9.8863E-03	9.3873E-02	-6.107
20	5	0.3569	-0.1247	0.	0.05999	8.5088E-02	-7.7983E-03	8.5443E-02	-5.237
21	5	0.3235	-0.1745	0.	0.05999	7.0545E-02	-3.6568E-03	7.0640E-02	-2.967
22	5	0.2902	-0.2244	0.	0.05999	5.0363E-02	3.7762E-04	5.0368E-02	0.430
23	5	0.2568	-0.2743	0.	0.05999	2.3841E-02	1.8773E-03	2.3915E-02	4.540
24	6	0.0900	0.0283	0.	0.05998	1.1756E-02	-3.7554E-02	3.9351E-02	-72.617
25	6	0.0300	0.0848	0.	0.05998	7.3150E-03	-2.2[illegible]9E-02	2.3709E-02	-72.026
26	7	0.0500	-0.0283	0.	0.05998	-1.0447E-02	3.6781E-02	3.8236E-02	105.896
27	7	0.0300	-0.0848	0.	0.05998	-4.9516E-03	2.0995E-02	2.1571E-02	103.270
28	8	0.0500	0.	0.0250	0.05389	-4.6029E-03	-1.8751E-03	4.9681E-03	-160.002
29	8	0.0300	0.	0.0751	0.05389	-2.6458E-03	-1.6850E-03	3.1098E-03	-147.830

- - - RADIATION PATTERNS - - -

- - ANGLES - - THETA DEGREES	PHI DEGREES	- POWER GAINS - VERT. DB	HOR. DB	TOTAL DB	- - - POLARIZATION - - - AXIAL RATIO	TILT DEG.	SENSE	- - - E(THETA) - - - MAGNITUDE VOLTS/M	PHASE DEGREES	- - - E(PHI) - - - MAGNITUDE VOLTS/M	PHASE DEGREES
90.00	30.00	-91.77	-9.79	-9.79	0.00010	89.94	RIGHT	7.27508E-02	-52.30	9.13416E+00	-52.98

***** DATA CARD NO.	6	EN	-0	-0	-0	-0	0.		0.		0.		0.	0

RUN TIME = 1.271

EXAMPLE 9, SCATTERING BY A SPHERE

Example 9 shows scattering by a sphere with ka of 2.9 (ka = circumference/wavelength). Bistatic scattering patterns are computed in the E and H planes, followed by near E and H field. The near fields within the sphere should be the negative of the incident field to produce zero total field. This condition is approximately satisfied in the example.

If the frequency is changed to ka = 2.744, however, large internal fields will exist in the TM_{101} mode of the spherical cavity which is resonant at this ka. Such internal resonances may occur in any closed structure and result in severe errors. The errors may be avoided by placing wires inside the sphere to destroy the resonance condition at a given frequency. Since the magnetic field integral equation enforces zero tangential magnetic field on the inside of the surface, the surface acts as a perfect magnetic conductor on the inside. Hence, the resonant fields are the dual of those that would exist in a perfect electric conductor. Unfortunately, while the correct magnetic currents for the internal fields would not radiate externally, the electric currents radiate strongly.

Example 9 Input

```
CM
CMBISTATIC SCATTERING BY A SPHERE.
CMPATCH DATA ARE INPUT FOR A SPHERE OF 1. M. RADIUS
CMTHE SPHERE IS THEN SCALED SO THAT KA=FREQUENCY IN MHZ.
CMTHE PATCH MODEL MAY BE USED FOR KA LESS THAN ABOUT 3.
CEFOR THIS RUN  *** KA=2.8 ***
SP              .13795      .13795      .98079      78.75       45.         .11957
SP              .51328      .21261      .83147      56.25       22.5        .17025
SP              .21261      .51328      .83147      56.25       67.5        .17025
SP              .80314      .21520      .55557      33.75       15.         .18907
SP              .58794      .58794      .55557      33.75       45.         .18907
SP              .21520      .80314      .55557      33.75       75.         .18907
SP              .86194      .19134      .19509      11.25       11.25       .19028
SP              .81549      .54490      .19509      11.25       33.75       .19028
SP              .54490      .81549      .19509      11.25       56.25       .19028
SP              .19134      .86194      .19509      11.25       78.75       .19028
GX     111
GS          47.71485
GE
FR          1           0          2.8
EX     1    1     1     0    90.         0.          0.
RP     0   18     1  1000    90.         0.         -10.         0.
RP     0    1    18  1000    90.         0.          0.         10.
NE     0    1     1    11     0.         0.          0.         0.          0.          5.
NE     0    1    11     1     0.         0.          0.         5.          5.          0.
NE     0   11     1     1     0.         0.          0.         5.          0.          0.
NH     0    1     1    11     0.         0.          0.         0.          0.          5.
NH     0    1    11     1     0.         0.          0.         0.          5.          0.
NH     0   11     1     1     0.         0.          0.         5.          0.          0.
EN
```

Example 9 Output

```
**********************************

  NUMERICAL ELECTROMAGNETICS CODE

**********************************
```

```
- - - - COMMENTS - - - -

BISTATIC SCATTERING BY A SPHERE.
PATCH DATA ARE INPUT FOR A SPHERE OF 1. M. RADIUS
THE SPHERE IS THEN SCALED SO THAT KA=FREQUENCY IN MHZ.
THE PATCH MODEL MAY BE USED FOR KA LESS THAN ABOUT 3.
FOR THIS RUN  *** KA=2.9 ***
```

```
- - - STRUCTURE SPECIFICATION - - -

   COORDINATES MUST BE INPUT IN
   METERS OR BE SCALED TO METERS
   BEFORE STRUCTURE INPUT IS ENDED
```

WIRE NO.	X1	Y1	Z1	X2	Y2	Z2	RADIUS	NO. OF SEG.	FIRST SEG.	LAST SEG.	TAG NO.
1P	0.13795	0.13795	0.98079	78.78000	45.00000	0.11987					
2P	0.51328	0.21261	0.83147	56.25000	22.50000	0.17025					
3P	0.21261	0.51328	0.83147	56.25000	67.50000	0.17025					
4P	0.80314	0.21520	0.55557	33.75000	15.00000	0.16987					
5P	0.58794	0.58794	0.55557	33.75000	45.00000	0.16987					
6P	0.21520	0.80314	0.55557	33.75000	75.00000	0.16987					
7P	0.38194	0.19134	0.19508	11.25000	11.25000	0.15028					
8P	0.81549	0.54490	0.19508	11.25000	33.75000	0.15028					
9P	0.54490	0.81549	0.19508	11.25000	56.25000	0.15028					
10P	0.19134	0.38194	0.19508	11.25000	78.75000	0.15028					

```
   STRUCTURE REFLECTED ALONG THE AXES X Y Z.  TAGS INCREMENTED BY   0
   STRUCTURE SCALED BY FACTOR  47.71485

 TOTAL SEGMENTS USED=    0     NO. SEG. IN A SYMMETRIC CELL=    0     SYMMETRY FLAG=  2
 TOTAL PATCHES USED=   80     NO. PATCHES IN A SYMMETRIC CELL=   10
STRUCTURE HAS 3 PLANES OF SYMMETRY
```

```
- - - SURFACE PATCH DATA - - -

COORDINATES IN METERS
```

PATCH NO.	COORD. OF PATCH CENTER X	Y	Z	UNIT NORMAL VECTOR X	Y	Z	PATCH AREA	COMPONENTS OF UNIT TANGENT VECTORS X1	Y1	Z1	X2	Y2	Z2
1	6.58224	6.58224	46.79805	0.1379	0.1379	0.9808	272.22356	-0.7071	0.7071	0.	-0.6935	-0.6935	0.1951
2	24.49098	10.14461	39.67330	0.5133	0.2126	0.8315	387.60610	-0.3827	0.9239	0.	-0.7682	-0.3182	0.5556
3	10.14461	24.49098	39.67330	0.2126	0.5133	0.8315	387.60610	-0.9239	0.3827	0	-0.3182	-0.7682	0.5556
4	38.32154	10.26819	20.50883	0.8031	0.2152	0.5556	386.74096	-0.2588	0.9659	0	-0.5366	-0.1438	0.8315
5	28.05335	28.05335	26.50883	0.5879	0.5879	0.5556	386.74096	-0.7071	0.7071	0	-0.3929	-0.3929	0.8315
6	10.26819	38.32154	26.50883	0.2152	0.8031	0.5556	386.74095	-0.9659	0.2588	0	-0.1438	-0.5366	0.8315
7	45.89863	9.12972	9.30865	0.9619	0.1913	0.1951	342.14065	-0.1951	0.9808	0.	-0.1913	-0.0381	0.9808
8	38.91082	25.99971	9.30865	0.8155	0.5449	0.1951	342.14065	-0.5556	0.8315	0.	-0.1622	-0.1084	0.9808
9	25.99971	38.91082	9.30865	0.5449	0.8155	0.1951	342.14065	-0.8315	0.5556	0.	-0.1084	-0.1622	0.9808
10	9.12972	45.89863	9.30865	0.1913	0.9619	0.1951	342.14065	-0.9808	0.1951	0.	-0.0381	-0.1913	0.9808
11	6.58224	6.58224	-46.79805	0.1379	0.1379	-0.9808	272.22356	-0.7071	0.7071	-0.	-0.6935	-0.6935	-0.1951
12	24.49098	10.14461	-39.67330	0.5133	0.2126	-0.8315	387.60610	-0.3827	0.9239	-0.	-0.7682	-0.3182	-0.5556
13	10.14461	24.49098	-39.67330	0.2126	0.5133	-0.8315	387.60610	-0.9239	0.3827	-0.	-0.3182	-0.7682	-0.5556
14	38.32154	10.26819	-26.50883	0.8031	0.2152	-0.5556	386.74096	-0.2588	0.9659	-0.	-0.5366	-0.1438	-0.8315
15	28.05335	28.05335	-26.50883	0.5879	0.5879	-0.5556	386.74096	-0.7071	0.7071	-0.	-0.3929	-0.3929	-0.8315
16	10.26819	38.32154	-26.50883	0.2152	0.8031	-0.5556	386.74058	-0.9659	0.2588	-0.	-0.1438	-0.5366	-0.8315
17	45.89863	9.12972	-9.30865	0.9619	0.1913	-0.1951	342.14065	-0.1951	0.9808	-0.	-0.1913	-0.0381	-0.9808
18	38.91082	25.99971	-9.30865	0.8155	0.5449	-0.1951	342.14065	-0.5556	0.8315	-0.	-0.1622	-0.1084	-0.9808
19	25.99971	38.91082	-9.30865	0.5449	0.8155	-0.1951	342.14065	-0.8315	0.5556	-0.	-0.1084	-0.1622	-0.9808
20	9.12972	45.89863	-9.30865	0.1913	0.9619	-0.1951	342.14065	-0.9808	0.1951	-0.	-0.0381	-0.1913	-0.9808
21	6.58224	-6.58224	46.79805	0.1379	-0.1379	0.9808	272.22356	-0.7071	-0.7071	0.	-0.6935	0.6935	0.1951

22	24.49098	-10.14461	39.67330	0.5133	-0.2126	0.8315	387.60610	-0.3827	-0.9239	0.	-0.7682	0.3182	0.5556
23	10.14461	-24.49098	39.67330	0.2126	-0.5133	0.8315	387.60610	-0.9239	-0.3827	0.	-0.3182	0.7682	0.5556
24	38.32154	-10.26819	26.50883	0.8031	-0.2152	0.5556	386.74096	-0.2588	-0.9659	0.	-0.5366	0.1438	0.8315
25	28.05335	-28.05335	26.50883	0.5879	-0.5879	0.5556	386.74096	-0.7071	-0.7071	0.	-0.3929	0.3929	0.8315
26	10.26819	-38.32154	26.50883	0.2152	-0.8031	0.5556	386.74096	-0.9659	-0.2588	0.	-0.1438	0.5366	0.8315
27	45.89863	-9.12972	9.30865	0.9819	-0.1913	0.1951	342.14065	-0.1951	-0.9808	0.	-0.1913	0.0381	0.9808
28	38.91082	-25.99971	9.30865	0.8155	-0.5449	0.1951	342.14065	-0.5556	-0.8315	0.	-0.1622	0.1084	0.9808
29	25.99971	-38.91082	9.30865	0.5449	-0.8155	0.1951	342.14065	-0.8315	-0.5556	0.	-0.1084	0.1622	0.9808
30	9.12972	-45.89863	9.30865	0.1913	-0.9819	0.1951	342.14065	-0.9808	-0.1951	0.	-0.0381	0.1913	0.9808
31	6.58224	-6.58224	-46.79805	0.1379	-0.1379	-0.9808	272.22356	-0.7071	-0.7071	-0.	-0.6935	0.6935	-0.1951
32	24.49098	-10.14461	-39.67330	0.5133	-0.2126	-0.8315	387.60610	-0.3827	-0.9239	-0.	-0.7682	0.3182	-0.5556
33	10.14461	-24.49098	-39.67330	0.2126	-0.5133	-0.8315	387.60610	-0.9239	-0.3827	-0.	-0.3182	0.7682	-0.5556
34	38.32154	-10.26819	-26.50883	0.8031	-0.2152	-0.5556	386.74096	-0.2588	-0.9659	-0.	-0.5366	0.1438	-0.8315
35	28.05335	-28.05335	-26.50883	0.5879	-0.5879	-0.5556	386.74096	-0.7071	-0.7071	-0.	-0.3929	0.3929	-0.8315
36	10.26819	-38.32154	-26.50883	0.2152	-0.8031	-0.5556	386.74096	-0.9659	-0.2588	-0.	-0.1438	0.5366	-0.8315
37	45.89863	-9.12972	-9.30865	0.9819	-0.1913	-0.1951	342.14065	-0.1951	-0.9808	-0.	-0.1913	0.0381	-0.9808
38	38.91082	-25.99971	-9.30865	0.8155	-0.5449	-0.1951	342.14065	-0.5556	-0.8315	-0.	-0.1622	0.1084	-0.9808
39	25.99971	-38.91082	-9.30865	0.5449	-0.8155	-0.1951	342.14065	-0.8315	-0.5556	-0.	-0.1084	0.1622	-0.9808
40	9.12972	-45.89863	-9.30865	0.1913	-0.9819	-0.1951	342.14065	-0.9808	-0.1951	-0.	-0.0381	0.1913	-0.9808
41	-6.58224	6.58224	46.79805	-0.1379	0.1379	0.9808	272.22356	0.7071	0.7071	0.	0.6935	-0.6935	0.1951
42	-24.49098	10.14461	39.67330	-0.5133	0.2126	0.8315	387.60610	0.3827	0.9239	0.	0.7682	-0.3182	0.5556
43	-10.14461	24.49098	39.67330	-0.2126	0.5133	0.8315	387.60610	0.9239	0.3827	0.	0.3182	-0.7682	0.5556
44	-38.32154	10.26819	26.50883	-0.8031	0.2152	0.5556	386.74096	0.2588	0.9659	0.	0.5366	-0.1438	0.8315
45	-28.05335	28.05335	26.50883	-0.5879	0.5879	0.5556	386.74096	0.7071	0.7071	0.	0.3929	-0.3929	0.8315
46	-10.26819	38.32154	26.50883	-0.2152	0.8031	0.5556	386.74096	0.9659	0.2588	0.	0.1438	-0.5366	0.8315
47	-45.89863	9.12972	9.30865	-0.9819	0.1913	0.1951	342.14065	0.1951	0.9808	0	0.1913	-0.0381	0.9808
48	-38.91082	25.99971	9.30865	-0.8155	0.5449	0.1951	342.14065	0.5556	0.8315	0.	0.1622	-0.1084	0.9808
49	-25.99971	38.91082	9.30865	-0.5449	0.8155	0.1951	342.14065	0.8315	0.5556	0.	0.1084	-0.1622	0.9808
50	-9.12972	45.89863	9.30865	-0.1913	0.9819	0.1951	342.14065	0.9808	0.1951	0.	0.0381	-0.1913	0.9808
51	-6.58224	6.58224	-46.79805	-0.1379	0.1379	-0.9808	272.22356	0.7071	0.7071	-0.	0.6935	-0.6935	-0.1951
52	-24.49098	10.14461	-39.67330	-0.5133	0.2126	-0.8315	387.60610	0.3827	0.9239	-0.	0.7682	-0.3182	-0.5556
53	-10.14461	24.49098	-39.67330	-0.2126	0.5133	-0.8315	387.60610	0.9239	0.3827	-0.	0.3182	-0.7682	-0.5556
54	-38.32154	10.26819	-26.50883	-0.8031	0.2152	-0.5556	386.74096	0.2588	0.9659	-0.	0.5366	-0.1438	-0.8315
55	-28.05335	28.05335	-26.50883	-0.5879	0.5879	-0.5556	386.74096	0.7071	0.7071	-0.	0.3929	-0.3929	-0.8315
56	-10.26819	38.32154	-26.50883	-0.2152	0.8031	-0.5556	386.74096	0.9659	0.2588	-0.	0.1438	-0.5366	-0.8315
57	-45.89863	9.12972	-9.30865	-0.9819	0.1913	-0.1951	342.14065	0.1951	0.9808	-0.	0.1913	-0.0381	-0.9808
58	-38.91082	25.99971	-9.30865	-0.8155	0.5449	-0.1951	342.14065	0.5556	0.8315	-0.	0.1622	-0.1084	-0.9808
59	-25.99971	38.91082	-9.30865	-0.5449	0.8155	-0.1951	342.14065	0.8315	0.5556	-0.	0.1084	-0.1622	-0.9808
60	-9.12972	45.89863	-9.30865	-0.1913	0.9819	-0.1951	342.14065	0.9808	0.1951	-0.	0.0381	-0.1913	-0.9808
61	-6.58224	-6.58224	46.79805	-0.1379	-0.1379	0.9808	272.22356	0.7071	-0.7071	0.	0.6935	0.6935	0.1951
62	-24.49098	-10.14461	39.67330	-0.5133	-0.2126	0.8315	387.60610	0.3827	-0.9239	0.	0.7682	0.3182	0.5556
63	-10.14461	-24.49098	39.67330	-0.2126	-0.5133	0.8315	387.60610	0.9239	-0.3827	0.	0.3182	0.7682	0.5556
64	-38.32154	-10.26819	26.50883	-0.8031	-0.2152	0.5556	386.74096	0.2588	-0.9659	0.	0.5366	0.1438	0.8315
65	-28.05335	-28.05335	26.50883	-0.5879	-0.5879	0.5556	386.74096	0.7071	-0.7071	0.	0.3929	0.3929	0.8315
66	-10.26819	-38.32154	26.50883	-0.2152	-0.8031	0.5556	386.74096	0.9659	-0.2588	0.	0.1438	0.5366	0.8315
67	-45.89863	-9.12972	9.30865	-0.9819	-0.1913	0.1951	342.14065	0.1951	-0.9808	0.	0.1913	0.0381	0.9808
68	-38.91082	-25.99971	9.30865	-0.8155	-0.5449	0.1951	342.14065	0.5556	-0.8315	0.	0.1622	0.1084	0.9808
69	-25.99971	-38.91082	9.30865	-0.5449	-0.8155	0.1951	342.14065	0.8315	-0.5556	0.	0.1084	0.1622	0.9808
70	-9.12972	-45.89863	9.30865	-0.1913	-0.9819	0.1951	342.14065	0.9808	-0.1951	0.	0.0381	0.1913	0.9808
71	-6.58224	-6.58224	-46.79805	-0.1379	-0.1379	-0.9808	272.22356	0.7071	-0.7071	-0.	0.6935	0.6935	-0.1951
72	-24.49098	-10.14461	-39.67330	-0.5133	-0.2126	-0.8315	387.60610	0.3827	-0.9239	-0.	0.7682	0.3182	-0.5556
73	-10.14461	-24.49098	-39.67330	-0.2126	-0.5133	-0.8315	387.60610	0.9239	-0.3827	-0.	0.3182	0.7682	-0.5556
74	-38.32154	-10.26819	-26.50883	-0.8031	-0.2152	-0.5556	386.74096	0.2588	-0.9659	-0.	0.5366	0.1438	-0.8315
75	-28.05335	-28.05335	-26.50883	-0.5879	-0.5879	-0.5556	386.74096	0.7071	-0.7071	-0.	0.3929	0.3929	-0.8315
76	-10.26819	-38.32154	-26.50883	-0.2152	-0.8031	-0.5556	386.74096	0.9659	-0.2588	-0.	0.1438	0.5366	-0.8315
77	-45.89863	-9.12972	-9.30865	-0.9819	-0.1913	-0.1951	342.14065	0.1951	-0.9808	-0.	0.1913	0.0381	-0.9808
78	-38.91082	-25.99971	-9.30865	-0.8155	-0.5449	-0.1951	342.14065	0.5556	-0.8315	-0.	0.1622	0.1084	-0.9808
79	-25.99971	-38.91082	-9.30865	-0.5449	-0.8155	-0.1951	342.14065	0.8315	-0.5556	-0.	0.1084	0.1622	-0.9808
80	-9.12972	-45.89863	-9.30865	-0.1913	-0.9819	-0.1951	342.14065	0.9808	-0.1951	-0.	0.0381	0.1913	-0.9808

```
***** DATA CARD NO.  1  FR  -0    1    -0    -0  2.90000E+00  0.          0.          0.          0.          0.
***** DATA CARD NO.  2  EX   1    1     1     0  9.00000E+01  0.          0.          0.          0.          0.
***** DATA CARD NO.  3  RP   0   19     1  1000  9.00000E+01  0.         -1.00000E+0  0.          0.          0.
```

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 2.9000E+00 MHZ
WAVELENGTH= 1.0338E+02 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FREE SPACE

- - - MATRIX TIMING - - -

FILL= 0.137 SEC., FACTOR= 0.173 SEC.

- - - EXCITATION - - -

PLANE WAVE THETA= 90.00 DEG, PHI= 0. DEG, ETA= 0. DEG, TYPE -LINEAR= AXIAL RATIO=-0.

- - - - SURFACE PATCH CURRENTS - - - -

DISTANCE IN WAVELENGTHS
CURRENT IN AMPS/METER

- - SURFACE COMPONENTS - - - - - RECTANGULAR COMPONENTS - - -

PATCH CENTER			TANGENT VECTOR 1		TANGENT VECTOR 2		X		Y		Z	
X	Y	Z	MAG.	PHASE	MAG.	PHASE	REAL	IMAG.	REAL	IMAG.	REAL	IMAG.
1												
0.084	0.084	0.453	2.8794E-03	-156.32	3.1198E-03	-157.39	3.06E-03	1.05E-03	1.33E-04	1.48E-05	-5.82E-04	-2.34E-04
2												
0.237	0.099	0.384	1.4256E-03	-91.29	4.7156E-03	-94.79	3.15E-04	4.18E-03	9.57E-05	1.79E-04	-2.19E-04	-2.81E-03
3												
0.099	0.237	0.384	3.2575E-03	-142.94	2.3684E-03	-147.56	3.04E-03	2.22E-03	5.39E-04	2.24E-04	-1.11E-03	-7.05E-04
4												
0.371	0.099	0.256	6.0841E-04	-43.12	4.9604E-03	-48.59	-1.99E-03	2.01E-03	-7.05E-05	1.07E-04	2.99E-03	-2.94E-03
5												
0.271	0.271	0.256	1.7787E-03	-79.48	3.9145E-03	-84.57	-3.75E-04	2.77E-03	8.40E-05	2.04E-04	3.08E-04	-3.24E-03
6												
0.099	0.371	0.256	2.2829E-03	-142.59	2.2579E-03	-151.48	2.04E-03	1.49E-03	5.95E-04	2.19E-04	-1.65E-03	-8.98E-04
7												
0.444	0.099	0.090	1.4688E-04	-14.13	5.2457E-03	-16.94	-9.00E-04	3.00E-04	-9.13E-05	2.30E-05	4.92E-03	-1.50E-03
8												
0.376	0.251	0.090	4.6333E-04	-40.19	4.4776E-03	-43.42	-7.24E-04	6.85E-04	-5.82E-05	8.50E-05	3.19E-03	-3.02E-03
9												
0.251	0.376	0.090	7.4095E-04	-85.74	3.3811E-03	-94.45	-1.74E-05	9.80E-04	7.32E-05	1.36E-04	-2.97E-04	-3.31E-03
10												
0.099	0.444	0.090	8.0344E-04	-147.10	2.2400E-03	-157.22	7.40E-04	4.81E-04	2.64E-04	8.08E-05	-2.03E-03	-8.91E-04
11												
0.084	0.084	-0.453	2.8794E-03	23.68	3.1198E-03	22.61	-3.06E-03	-1.05E-03	-1.33E-04	-1.48E-05	-5.82E-04	-2.34E-04
12												
0.237	0.099	-0.384	1.4256E-03	88.72	4.7156E-03	85.21	-3.15E-04	-4.18E-03	-9.57E-05	-1.79E-04	-2.19E-04	-2.81E-03
13												
0.099	0.237	-0.384	3.2575E-03	37.06	2.3684E-03	32.44	-3.04E-03	-2.22E-03	-5.39E-04	-2.24E-04	-1.11E-03	-7.05E-04
14												
0.371	0.099	-0.256	6.0841E-04	136.88	4.9604E-03	134.45	1.99E-03	-2.01E-03	7.05E-05	-1.07E-04	2.99E-03	-2.94E-03
15												
0.271	0.271	-0.256	1.7787E-03	100.52	3.9145E-03	95.43	3.75E-04	-2.77E-03	-8.40E-05	-2.04E-04	3.08E-04	-3.24E-03
16												
0.099	0.371	-0.256	2.2829E-03	37.41	2.2579E-03	28.52	-2.04E-03	-1.49E-03	-5.95E-04	-2.19E-04	-1.65E-03	-8.98E-04
17												
0.444	0.099	-0.090	1.4688E-04	165.87	5.2457E-03	163.06	9.00E-04	-3.00E-04	9.13E-05	-2.30E-05	4.92E-03	-1.50E-03
18												
0.376	0.251	-0.090	4.6333E-04	139.81	4.4776E-03	136.58	7.24E-04	-6.85E-04	5.82E-05	-8.50E-05	3.19E-03	-3.02E-03
19												
0.251	0.376	-0.090	7.4095E-04	94.27	3.3811E-03	85.55	1.74E-05	-9.80E-04	-7.32E-05	-1.36E-04	-2.97E-04	-3.31E-03
20												
0.099	0.444	-0.090	8.0344E-04	32.90	2.2400E-03	22.78	-7.40E-04	-4.81E-04	-2.64E-04	-8.08E-05	-2.03E-03	-8.91E-04
21												
0.084	-0.084	0.453	2.8794E-03	-156.32	3.1198E-03	-157.39	3.06E-03	1.05E-03	-1.33E-04	-1.48E-05	-5.82E-04	-2.34E-04
22												
0.237	-0.099	0.384	1.4256E-03	-91.29	4.7156E-03	-94.79	3.15E-04	4.18E-03	-9.57E-05	-1.79E-04	-2.19E-04	-2.81E-03
23												
0.099	-0.237	0.384	3.2575E-03	-142.94	2.3684E-03	-147.56	3.04E-03	2.22E-03	-5.39E-04	-2.24E-04	-1.11E-03	-7.05E-04

```
24
0.371 -0.099  0.256 6.084E-04  -43.12 4.960E-03  -45.95 -1.98E-03  2.01E-03  7.05E-05 -1.07E-04  2.89E-03 -2.94E-03
25
0.271 -0.271  0.256 1.778E-03  -79.48 3.914E-03  -84.97 -3.75E-04  2.77E-03  8.40E-05 -2.84E-04  3.08E-04 -3.24E-03
26
0.099 -0.371  0.256 2.282E-03 -142.59 2.257E-03 -151.48  2.04E-03  1.49E-03 -5.99E-04 -2.19E-04 -1.65E-03 -8.98E-04
27
0.444 -0.099  0.090 1.468E-04  -14.13 5.245E-03  -18.84 -9.88E-04  3.00E-04  5.13E-05 -2.30E-05  4.84E-03 -1.90E-03
28
0.376 -0.251  0.090 4.833E-04  -40.19 4.477E-03  -43.42 -7.24E-04  8.65E-04  5.84E-05 -8.90E-05  3.19E-03 -3.03E-03
29
0.251 -0.376  0.090 7.409E-04  -85.74 3.381E-03  -84.45 -1.74E-05  9.80E-04 -7.32E-05 -1.36E-04 -2.57E-04 -3.31E-03
30
0.099 -0.444  0.090 8.034E-04 -147.10 2.240E-03 -157.22  7.40E-04  4.61E-04 -2.64E-04 -9.08E-05 -2.03E-03 -8.51E-04
31
0.084 -0.084 -0.453 2.879E-03   23.68 3.119E-03   22.81 -3.88E-03 -1.65E-03  1.33E-04  1.49E-05 -5.62E-04 -2.34E-04
32
0.237 -0.099 -0.384 1.425E-03   88.72 4.715E-03   85.21 -3.19E-04 -4.18E-03  9.57E-05  1.73E-04 -2.19E-04 -2.81E-03
33
0.099 -0.237 -0.384 3.257E-03   37.06 2.366E-03   32.44 -3.04E-03 -2.22E-03  5.39E-04  2.24E-04 -1.11E-03 -7.05E-04
34
0.371 -0.099 -0.256 6.084E-04  138.08 4.960E-03  134.45  1.98E-03 -2.01E-03 -7.05E-05  1.07E-04  2.89E-03 -2.94E-03
35
0.271 -0.271 -0.256 1.778E-03  100.52 3.914E-03   95.43  3.75E-04 -2.77E-03  8.40E-05  2.84E-04  3.08E-04 -3.24E-03
36
0.099 -0.371 -0.256 2.282E-03   37.41 2.257E-03   28.52 -2.04E-03 -1.49E-03  5.99E-04  2.19E-04 -1.65E-03 -8.98E-04
37
0.444 -0.099 -0.090 1.468E-04  165.87 5.245E-03  163.06  9.88E-04 -3.00E-04 -5.13E-05  2.30E-05  4.84E-03 -1.90E-03
38
0.376 -0.251 -0.090 4.833E-04  139.81 4.477E-03  136.58  7.24E-04 -8.65E-04 -5.84E-05  8.90E-05  3.19E-03 -3.03E-03
39
0.251 -0.376 -0.090 7.409E-04   94.27 3.381E-03   88.55  1.74E-05 -9.80E-04  7.32E-05  1.36E-04 -2.57E-04 -3.31E-03
40
0.099 -0.444 -0.090 8.034E-04   32.90 2.240E-03   22.78 -7.40E-04 -4.61E-04  2.64E-04  9.08E-05 -2.03E-03 -8.51E-04
41
-0.084  0.084  0.453 2.913E-03  -36.78 2.523E-03  -37.39  3.04E-03 -2.30E-03  2.60E-04 -1.70E-04  3.91E-04 -2.99E-04
42
-0.237  0.099  0.384 1.952E-03 -104.63 3.657E-03 -105.40 -9.35E-04 -3.43E-03 -1.47E-04 -8.23E-04 -5.39E-04 -1.96E-03
43
-0.099  0.237  0.384 3.393E-03  -51.87 6.367E-04  -60.18  2.04E-03 -2.64E-03  5.98E-04 -5.97E-04  1.78E-04 -3.07E-04
44
-0.371  0.099  0.256 1.150E-03 -138.16 1.844E-03 -154.01 -1.17E-03 -4.71E-04 -5.73E-04 -8.68E-04 -1.47E-03 -4.23E-04
45
-0.271  0.271  0.256 2.822E-03 -114.23 1.083E-03 -121.04 -9.85E-04 -2.05E-03 -5.36E-04 -1.33E-03 -4.75E-04 -7.65E-04
46
-0.099  0.371  0.256 2.385E-03  -52.80 4.024E-04  137.80  1.35E-03 -1.80E-03  5.33E-04 -5.37E-04 -2.48E-04  2.25E-04
47
-0.444  0.099  0.090 3.320E-04 -151.23 2.509E-03   82.38  7.08E-05  4.45E-04 -2.98E-04 -2.51E-04  3.27E-04  2.44E-03
48
-0.376  0.251  0.090 8.649E-04 -139.37 1.209E-03   94.55 -3.80E-04 -1.17E-04 -5.35E-04 -5.99E-04 -8.42E-05  1.18E-03
49
-0.251  0.376  0.090 1.028E-03 -108.70 3.190E-04   82.48 -2.70E-04 -7.78E-04 -1.90E-04 -6.93E-04  4.10E-05  3.10E-04
50
-0.099  0.444  0.090 8.279E-04  -48.33 9.195E-04  137.33  5.14E-04 -5.83E-04  2.37E-04 -2.40E-04 -8.63E-04  6.11E-04
51
-0.084  0.084 -0.453 2.913E-03  143.24 2.523E-03  142.61 -3.04E-03  2.30E-03 -2.60E-04  1.70E-04  3.91E-04 -2.99E-04
52
-0.237  0.099 -0.384 1.952E-03   75.37 3.657E-03   74.61  9.35E-04  3.43E-03  1.47E-04  8.23E-04 -5.39E-04 -1.96E-03
53
-0.099  0.237 -0.384 3.393E-03  128.13 6.367E-04  119.84 -2.04E-03  2.64E-03 -5.98E-04  5.97E-04  1.78E-04 -3.07E-04
54
-0.371  0.099 -0.256 1.150E-03   41.84 1.844E-03   19.99  1.17E-03  4.71E-04  5.73E-04  8.68E-04  1.47E-03  4.23E-04
55
-0.271  0.271 -0.256 2.822E-03   65.77 1.083E-03   58.18  9.85E-04  2.05E-03  5.36E-04  1.33E-03  4.75E-04  7.65E-04
56
-0.099  0.371 -0.256 2.385E-03  127.20 4.024E-04  -42.20 -1.35E-03  1.80E-03 -5.33E-04  5.37E-04  2.48E-04 -2.25E-04
57
-0.444  0.099 -0.090 3.320E-04   28.77 2.509E-03  -97.64 -7.08E-05 -4.45E-04  2.98E-04  2.51E-04  3.27E-04  2.44E-03
58
-0.376  0.251 -0.090 8.649E-04   40.63 1.209E-03  -85.45  3.80E-04  1.17E-04  5.35E-04  5.99E-04 -8.42E-05  1.18E-03
59
-0.251  0.376 -0.090 1.028E-03   71.30 3.190E-04  -97.54  2.70E-04  7.78E-04  1.90E-04  6.93E-04  4.10E-05  3.10E-04
60
-0.099  0.444 -0.090 8.279E-04  131.67 9.195E-04  -42.67 -5.14E-04  5.83E-04 -2.37E-04  2.40E-04 -8.63E-04  6.11E-04
61
-0.084 -0.084  0.453 2.913E-03  -36.78 2.523E-03  -37.39  3.04E-03 -2.30E-03 -2.60E-04  1.70E-04  3.91E-04 -2.99E-04
62
-0.237 -0.099  0.384 1.952E-03 -104.63 3.657E-03 -105.40 -9.35E-04 -3.43E-03  1.47E-04  8.23E-04 -5.39E-04 -1.96E-03
63
-0.099 -0.237  0.384 3.393E-03  -51.87 6.367E-04  -60.18  2.04E-03 -2.64E-03 -5.98E-04  5.97E-04  1.78E-04 -3.07E-04
```

64
-0.371 -0.099 0.256 1.1507E-03 -138.18 1.0444E-03 -184.01 -1.17E-03 -4.71E-04 5.73E-04 6.68E-04 -1.47E-03 -4.23E-04
65
-0.271 -0.271 0.256 2.6220E-03 -114.23 1.0836E-03 -121.84 -9.85E-04 -2.05E-03 5.36E-04 1.33E-03 -4.75E-04 -7.85E-04
66
-0.099 -0.371 0.256 2.3855E-03 -52.80 4.0244E-04 137.80 1.35E-03 -1.00E-03 -5.33E-04 6.37E-04 -2.48E-04 2.25E-04
67
-0.444 -0.099 0.090 3.3208E-04 -151.23 2.5093E-03 82.46 7.08E-06 4.45E-04 2.98E-04 2.91E-04 3.27E-04 2.44E-03
68
-0.376 -0.251 0.090 8.6498E-04 -138.37 1.2097E-03 94.55 -3.80E-04 -1.17E-04 5.35E-04 5.98E-04 -9.42E-05 1.18E-03
69
-0.251 -0.376 0.090 1.0285E-03 -108.70 3.1884E-04 82.46 -2.70E-04 -7.78E-04 1.90E-04 5.93E-04 4.10E-05 3.10E-04
70
-0.099 -0.444 0.090 8.2755E-04 -48.33 9.1957E-04 137.33 5.14E-04 -5.83E-04 -2.37E-04 2.40E-04 -6.63E-04 6.11E-04
71
-0.094 -0.094 -0.453 2.9135E-03 143.24 2.5234E-03 142.61 -3.04E-03 2.30E-03 2.80E-04 -1.70E-04 3.91E-04 -2.99E-04
72
-0.237 -0.099 -0.384 1.9524E-03 75.37 3.8573E-03 74.61 9.35E-04 3.43E-03 -1.47E-04 -6.23E-04 -5.39E-04 -1.96E-03
73
-0.099 -0.237 -0.384 3.3932E-03 128.13 6.3674E-04 119.84 -2.04E-03 2.64E-03 5.58E-04 -5.87E-04 1.76E-04 -3.07E-04
74
-0.371 -0.099 -0.256 1.1507E-03 41.84 1.0444E-03 15.99 1.17E-03 4.71E-04 -5.73E-04 -6.68E-04 -1.47E-03 -4.23E-04
75
-0.271 -0.271 -0.256 2.6220E-03 65.77 1.0836E-03 58.16 9.85E-04 2.05E-03 -5.36E-04 -1.33E-03 -4.75E-04 -7.85E-04
76
-0.099 -0.371 -0.256 2.3855E-03 127.20 4.0244E-04 -42.20 -1.35E-03 1.00E-03 5.33E-04 -6.37E-04 -2.48E-04 2.25E-04
77
-0.444 -0.099 -0.090 3.3208E-04 28.77 2.5093E-03 -97.54 -7.08E-06 -4.45E-04 -2.98E-04 -2.91E-04 3.27E-04 2.44E-03
78
-0.376 -0.251 -0.090 8.6498E-04 40.63 1.2097E-03 -85.45 3.80E-04 1.17E-04 -5.35E-04 -5.98E-04 -9.42E-05 1.18E-03
79
-0.251 -0.376 -0.090 1.0285E-03 71.30 3.1884E-04 -97.54 2.70E-04 7.78E-04 -1.90E-04 -5.93E-04 4.10E-05 3.10E-04
80
-0.099 -0.444 -0.090 8.2755E-04 131.67 9.1957E-04 -42.67 -5.14E-04 5.83E-04 2.37E-04 -2.40E-04 -6.63E-04 6.11E-04

- - - RADIATION PATTERNS - - -

- - ANGLES - -		- POWER GAINS -			- - - POLARIZATION - - -			- - - E(THETA) - - -		- - - E(PHI) - - -	
THETA DEGREES	PHI DEGREES	VERT. DB	HOR. DB	TOTAL DB	AXIAL RATIO	TILT DEG.	SENSE	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES
90.00	0.	-4.44	-999.99	-4.44	0.00000	-0.00	LINEAR	1.74852E+01	163.80	2.18710E-14	-70.25
80.00	0.	-4.04	-999.99	-4.04	0.00000	0.00	LINEAR	1.83237E+01	161.67	5.30030E-14	-134.19
70.00	0.	-2.96	-999.99	-2.96	0.00000	0.00	LINEAR	2.07470E+01	156.06	3.63582E-14	-129.70
60.00	0.	-1.61	-999.99	-1.61	0.00000	0.00	LINEAR	2.42168E+01	152.14	7.78242E-14	-144.37
50.00	0.	-0.50	-999.99	-0.50	0.00000	0.00	LINEAR	2.75840E+01	148.81	9.46568E-14	-153.15
40.00	0.	-0.03	-999.99	-0.03	0.00000	0.00	LINEAR	2.90498E+01	148.61	7.09105E-14	169.28
30.00	0.	-0.50	-999.99	-0.50	0.00000	0.00	LINEAR	2.78598E+01	144.38	1.01132E-13	126.91
20.00	0.	-2.73	-999.99	-2.73	0.00000	0.00	LINEAR	2.13035E+01	139.32	1.55612E-13	143.83
10.00	0.	-7.57	-999.99	-7.57	0.00000	0.00	LINEAR	1.22053E+01	118.96	2.34637E-13	118.16
0.	0.	-8.84	-999.99	-8.84	0.00000	0.00	LINEAR	1.07998E+01	44.17	3.62102E-13	126.29
-10.00	0.	-1.91	-999.99	-1.91	0.00000	-0.00	LINEAR	2.34178E+01	14.76	3.86994E-13	138.13
-20.00	0.	1.94	-999.99	1.94	0.00000	-0.00	LINEAR	3.64487E+01	11.84	5.05636E-13	141.93
-30.00	0.	3.84	-999.99	3.84	0.00000	-0.00	LINEAR	4.53564E+01	10.56	5.87684E-13	145.94
-40.00	0	4.51	-999.99	4.51	0.00000	-0.00	LINEAR	4.99894E+01	27.10	5.63941E-13	143.84
-50.00	0	4.63	-999.99	4.63	0.00000	-0.00	LINEAR	4.96673E+01	44.19	5.92954E-13	162.05
-60.00	0.	5.12	-999.99	5.12	0.00000	-0.00	LINEAR	5.29843E+01	85.77	4.94763E-13	166.85
-70.00	0.	6.29	-999.99	6.29	0.00000	0.00	LINEAR	6.01727E+01	84.51	3.70544E-13	159.84
-80.00	0.	7.42	-999.99	7.42	0.00000	0.00	LINEAR	6.85141E+01	95.53	1.02413E-13	169.68
-90.00	0.	7.86	-999.99	7.86	0.00000	-0.00	LINEAR	7.20510E+01	99.00	2.78146E-14	-56.81

***** DATA CARD NO. 4 RP 0 1 10 1000 9.00000E+01 0. 0. 1.00000E+01 0. 0.

- - - RADIATION PATTERNS - - -

- - ANGLES - -		- POWER GAINS -			- - - POLARIZATION - - -			- - - E(THETA) - - -		- - - E(PHI) - - -	
THETA DEGREES	PHI DEGREES	VERT. DB	HOR DB	TOTAL DB	AXIAL RATIO	TILT DEG.	SENSE	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES
90.00	0.	-4.44	-999.99	-4.44	0.00000	-0.00	LINEAR	1.74852E+01	163.80	2.18710E-14	-70.25
90.00	10.00	-4.28	-999.99	-4.28	0.00000	0.00	LINEAR	1.78440E+01	161.73	1.13587E-11	144.10
90.00	20.00	-3.79	-999.99	-3.79	0.00000	0.00	LINEAR	1.88454E+01	156.08	2.58808E-11	139.09
90.00	30.00	-3.06	-999.99	-3.06	0.00000	0.00	LINEAR	2.04829E+01	148.15	4.87714E-11	133.98
90.00	40.00	-2.25	-999.99	-2.25	0.00000	0.00	LINEAR	2.25127E+01	139.17	7.44719E-11	129.35
90.00	50.00	-1.54	-999.99	-1.54	0.00000	0.00	LINEAR	2.44308E+01	129.63	1.05444E-10	124.77
90.00	60.00	-1.11	-999.99	-1.11	0.00000	0.00	LINEAR	2.56784E+01	119.17	1.32426E-10	118.12
90.00	70.00	-1.05	-999.99	-1.05	0.00000	0.00	LINEAR	2.58334E+01	108.70	1.47995E-10	108.17

90.00	80.00	-1.34	-999.99	-1.34	0.00000	0.00	LINEAR	2.499506E+01	90.48	1.582466E-10	83.46
90.00	90.00	-1.67	-999.99	-1.67	0.00000	0.00	LINEAR	2.405986E+01	88.78	2.029016E-10	51.14
90.00	100.00	-1.45	-999.99	-1.45	0.00000	0.00	LINEAR	2.488945E+01	42.25	3.227986E-1.	28.41
90.00	110.00	-0.38	-999.99	-0.38	0.00000	0.00	LINEAR	2.780706E+01	15.31	5.046456E-10	13.26
90.00	120.00	1.14	-999.99	1.14	0.00000	0.00	LINEAR	3.324136E+01	-0.45	7.076116E-10	6.43
90.00	130.00	2.70	-999.99	2.70	0.00000	0.00	LINEAR	3.979377E+01	-20.98	8.796386E-10	2.66
90.00	140.00	4.20	-999.99	4.20	0.00000	0.00	LINEAR	4.727787E+01	-46.85	9.653356E-10	0.52
90.00	150.00	5.60	-999.99	5.60	0.00000	0.00	LINEAR	5.555086E+01	-61.58	9.204036E-10	-0.77
90.00	160.00	6.78	-999.99	6.78	0.00000	0.00	LINEAR	6.386016E+01	-72.39	7.261476E-10	-1.50
90.00	170.00	7.58	-999.99	7.58	0.00000	0.00	LINEAR	6.978606E+01	-78.86	4.012206E-10	-1.89
90.00	180.00	7.86	-999.99	7.86	0.00000	-0.00	LINEAR	7.209106E+01	-81.00	2.993396E-14	165.20

***** DATA CARD NO. 5 NE 0 1 1 11 0. 0. 0. 0. 0. 9.000000E+00

- - - NEAR ELECTRIC FIELDS - - -

LOCATION			EX		EY		EZ	
X METERS	Y METERS	Z METERS	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	0.	5.3925E-12	-0.90	1.0166E-15	-137.49	9.9819E-01	0.03
0.	0.	5.0000	2.4040E-02	79.71	8.4036E-16	109.17	9.9612E-01	0.04
0.	0.	10.0000	4.8950E-02	79.76	2.4001E-15	151.51	9.9986E-01	0.04
0.	0.	15.0000	6.7822E-02	79.86	6.0384E-15	141.81	9.9823E-01	0.06
0.	0.	20.0000	8.7187E-02	80.01	1.0594E-14	149.35	9.9357E-01	0.10
0.	0.	25.0000	1.0747E-01	80.30	1.1298E-14	155.70	9.8943E-01	0.20
0.	0.	30.0000	1.3472E-01	80.92	1.7137E-14	149.89	9.8671E-01	0.29
0.	0.	35.0000	1.5187E-01	81.47	3.0035E-14	155.51	1.0307E+00	-0.45
0	0.	40.0000	1.0076E-01	-87.91	6.6201E-14	179.81	1.2788E+00	-3.24
0.	0.	45.0000	1.2887E+00	-93.80	1.3565E-13	155.41	9.2209E-01	1.06
0.	0.	50.0000	1.2772E+00	-96.81	1.0907E-13	158.78	7.4393E-01	137.47

***** DATA CARD NO. 6 NE 0 1 11 1 0. 0. 0. 0. 9.000000E+00 0.

- - - NEAR ELECTRIC FIELDS - - -

LOCATION			EX		EY		EZ	
X METERS	Y METERS	Z METERS	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES	MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	0.	5.3925E-12	-0.90	1.0166E-15	-137.49	9.9819E-01	0.03
0.	5.0000	0.	5.4000E-12	-0.92	2.0347E-15	-131.68	9.9811E-01	0.03
0.	10.0000	0.	5.4070E-12	-0.90	5.3031E-15	-130.08	9.9588E-01	0.02
0.	15.0000	0.	5.4116E-12	-0.93	8.1680E-15	-117.02	9.9984E-01	0.00
0.	20.0000	0.	5.4198E-12	-0.92	1.3949E-14	-107.28	9.9830E-01	-0.02
0	25.0000	0.	5.4198E-12	-0.84	2.4479E-14	-107.58	9.9960E-01	-0.05
0.	30.0000	0.	5.4089E-12	-0.34	4.3827E-14	-106.82	9.9795E-01	0.05
0.	35.0000	0.	5.3724E-12	2.37	8.0726E-14	-98.87	1.0108E+00	1.19
0	40.0000	0.	5.3836E-12	11.87	1.1552E-13	-93.37	1.0547E+00	6.03
0	45.0000	0.	5.5517E-12	24.18	4.8409E-14	-81.84	1.1040E+00	12.69
0.	50.0000	0.	4.8911E-12	20.52	8.6013E-14	77.17	9.8244E-01	9.30

***** DATA CARD NO. 7 NE 0 11 1 1 0. 0. 0. 9.000000E+00 0. 0.

- - - NEAR ELECTRIC FIELDS - - -

LOCATION X METERS	LOCATION Y METERS	LOCATION Z METERS	EX MAGNITUDE VOLTS/M	EX PHASE DEGREES	EY MAGNITUDE VOLTS/M	EY PHASE DEGREES	EZ MAGNITUDE VOLTS/M	EZ PHASE DEGREES
0.	0.	0.	5.3825E-12	-0.90	1.0186E-15	-137.48	9.9818E-01	0.03
5.0000	0	0.	5.3414E-12	19.62	5.9943E-17	-7.13	9.8888E-01	18.52
10.0000	0.	0.	5.2888E-12	32.42	6.2148E-16	83.98	9.6887E-01	33.41
15.0000	0.	0.	5.1782E-12	48.72	2.5019E-16	-146.31	9.4938E-01	50.89
20.0000	0.	0.	5.1012E-12	67.31	2.5209E-15	150.12	9.3104E-01	69.02
25.0000	0.	0.	5.0458E-12	86.35	6.9871E-16	-105.95	9.1938E-01	87.66
30.0000	0.	0.	5.0609E-12	103.90	1.1630E-15	141.48	9.0782E-01	106.78
35.0000	0.	0.	5.2775E-12	122.98	1.6290E-15	-87.31	8.9668E-01	130.00
40.0000	0.	0.	5.8445E-12	138.21	7.6925E-16	21.71	8.9988E-01	174.27
45.0000	0.	0.	2.2474E-12	160.16	2.7884E-15	74.17	1.3188E+00	-148.03
50.0000	0.	0.	3.1133E-12	-99.09	2.1228E-15	40.83	1.2074E+00	-148.86

***** DATA CARD NO. 8 NH 0 1 1 11 0. 0. 0. 0. 0. 5.00000E+00

- - - NEAR MAGNETIC FIELDS - - -

LOCATION X METERS	LOCATION Y METERS	LOCATION Z METERS	HX MAGNITUDE AMPS/M	HX PHASE DEGREES	HY MAGNITUDE AMPS/M	HY PHASE DEGREES	HZ MAGNITUDE AMPS/M	HZ PHASE DEGREES
0.	0.	0.	5.9821E-17	-48.31	2.2789E-03	1.96	2.4131E-18	-119.12
0.	0.	5.0000	6.1963E-17	-44.84	2.2878E-03	1.91	8.2838E-18	-96.25
0.	0.	10.0000	5.7935E-17	-41.41	2.3137E-03	1.77	1.9394E-17	-68.67
0.	0.	15.0000	7.0059E-17	-28.95	2.3568E-03	1.55	2.4843E-17	-81.73
0.	0.	20.0000	6.9512E-17	-25.89	2.4177E-03	1.26	3.0859E-17	-71.19
0.	0.	25.0000	6.4044E-17	-18.61	2.5014E-03	0.91	5.5405E-17	-43.29
0.	0.	30.0000	5.9037E-17	-16.16	2.6239E-03	0.48	6.4618E-17	-50.03
0.	0.	35.0000	5.6807E-17	-3.45	2.8061E-03	-0.04	8.3501E-17	-48.00
0.	0.	40.0000	5.3604E-17	2.69	2.9018E-03	-0.88	1.0220E-16	-15.88
0.	0.	45.0000	5.1418E-17	4.84	1.8298E-03	2.40	1.7884E-16	-11.27
0.	0.	50.0000	3.5975E-17	22.97	3.5955E-04	128.97	1.7377E-16	-19.01

***** DATA CARD NO. 9 NH 0 1 11 1 0. 0. 0. 0. 5.00000E+00 0

- - - NEAR MAGNETIC FIELDS - - -

LOCATION X METERS	LOCATION Y METERS	LOCATION Z METERS	HX MAGNITUDE AMPS/M	HX PHASE DEGREES	HY MAGNITUDE AMPS/M	HY PHASE DEGREES	HZ MAGNITUDE AMPS/M	HZ PHASE DEGREES
0.	0.	0.	5.9821E-17	-48.31	2.2789E-03	1.96	2.4131E-18	-119.12
0.	5.0000	0.	2.4437E-06	-33.79	2.2814E-03	1.94	1.2709E-16	-104.26
0.	10.0000	0.	4.8773E-06	-31.84	2.2888E-03	1.89	2.4384E-16	-102.28
0.	15.0000	0.	8.9547E-06	-28.51	2.3015E-03	1.81	3.1727E-16	-100.58
0.	20.0000	0.	8.0815E-06	-24.05	2.3196E-03	1.71	3.9005E-16	-100.21
0.	25.0000	0.	8.8609E-06	-20.06	2.3435E-03	1.58	3.4454E-16	-101.78
0	30.0000	0.	1.5590E-05	-18.85	2.3757E-03	1.46	2.8513E-16	-102.54
0.	35.0000	0.	4.6067E-05	-15.18	2.4241E-03	1.45	2.2627E-16	-138.35
0.	40.0000	0.	1.8253E-04	-9.27	2.4817E-03	1.51	8.2107E-16	172.81
0.	45.0000	0.	5.5127E-04	-7.05	2.4895E-03	0.45	2.7849E-15	169.33
0.	50.0000	0.	1.0005E-03	-9.09	2.1016E-03	-4.19	5.2122E-15	167.19

***** DATA CARD NO. 10 NH 0 11 1 1 0 0. 0. 5.00000E+00 0. 0

- - - NEAR MAGNETIC FIELDS - - -

LOCATION			HX		HY		HZ	
X METERS	Y METERS	Z METERS	MAGNITUDE AMPS/M	PHASE DEGREES	MAGNITUDE AMPS/M	PHASE DEGREES	MAGNITUDE AMPS/M	PHASE DEGREES
0.	0.	0.	5.9821E-17	-48.31	2.2789E-03	1.96	2.4131E-18	-115.12
5.0000	0.	0.	4.7469E-17	-36.27	2.3306E-03	21.82	1.9067E-18	148.08
10.0000	0.	0.	4.3046E-17	-9.13	2.4170E-03	40.81	3.1094E-18	-152.77
15.0000	0.	0.	4.8357E-17	15.08	2.5179E-03	58.74	3.1518E-18	-178.65
20.0000	0.	0.	6.3781E-17	34.78	2.6126E-03	75.71	3.1917E-18	164.11
25.0000	0.	0.	8.4841E-17	57.99	2.6847E-03	91.98	1.7174E-18	-73.50
30.0000	0.	0.	7.6970E-17	89.52	2.7211E-03	107.70	1.3053E-18	-119.89
35.0000	0.	0.	1.1043E-16	102.88	2.6696E-03	122.20	6.4703E-19	164.22
40.0000	0.	0.	1.3983E-16	125.87	2.2957E-03	132.88	4.7879E-19	87.30
45.0000	0.	0.	1.8744E-16	131.87	9.0508E-04	132.95	2.2408E-18	153.13
50.0000	0.	0.	1.4618E-16	130.28	6.7803E-04	-24.20	1.4868E-18	-141.75

***** DATA CARD NO. 11 EN -0 -0 -0 -0 0. 0. 0. 0. 0. 0.

RUN TIME = 1.19S

EXAMPLE 10, MONOPOLE ON RADIAL WIRE GROUND SCREEN

Example 10 is a monopole antenna on a sparse radial wire ground screen using the Sommerfeld/Norton ground method. Part of the interpolation grid from SOMNEC is reproduced so that the user can check that his code is operating correctly.

The NGF has been used to take advantage of the symmetry of the ground screen before adding the monopole on the axis of rotation. The addition of the monopole results in 12 new unknowns. This includes the six segments in the monopole and segments at the junction of the six radial wires. The basis functions for these junction segments are modified and have become new unknowns. The currents represented by these new unknowns are printed in their normal locations in the table of currents.

The NGF can be tested on any of the other examples in this section by splitting the structure at some point. The results should be unchanged, although small differences may occur on computers with less than a 60-bit word length.

SOMNEC Input

```
4      .001      10.      1
```

SOMNEC Output

```
NEC GROUND INTERPOLATION GRID
 DIELECTRIC CONSTANT= 4.00000E+00-1.79780E+00


 GRID 1
    R(1)= 0.        DR= 0.0200    NR= 11
 THET(1)= 0.        DTH= 0.1745   NTH= 10



EXV
 IR=  1
-2.74856E+01-9.85744E+01-2.30832E+01-8.27137E+01-1.82457E+01-6.90225E+01-1.58668E+01-5.89119E+01-1.28168E+01-4.59660E+01
-1.00040E+01-3.58781E+01-7.38475E+00-2.64128E+01-4.84846E+00-1.73813E+01-2.40468E+00-8.62414E+00 0.          0.
 IR=  2
-1.88878E+01-1.03932E+02-1.98709E+01-8.78788E+01-1.35622E+01-7.28713E+01-1.13519E+01-6.01052E+01-9.29501E+00-4.99487E+01
-7.32128E+00-3.78038E+01-5.43191E+00-2.78051E+01-3.89408E+00-1.83838E+01-1.70814E+00-9.11143E+00-6.11809E-06-2.60360E-05
 IR=  3
-1.41444E+01-1.10158E+02-1.88943E+01-8.23600E+01-1.11782E+01-7.08786E+01-9.62047E+00-6.33842E+01-8.03386E+00-5.11214E+01
-6.43283E+00-3.98504E+01-4.62878E+00-2.83059E+01-3.21650E+00-1.96893E+01-1.80789E+00-9.95801E+00-2.30303E-06-1.38508E-05
 IR=  4
-1.23604E+01-1.10159E+02-1.85845E+01-8.09895E+01-1.05936E+01-6.69413E+01-8.89804E+00-6.00981E+01-7.68434E+00-5.31640E+01
-6.34780E+00-4.13512E+01-4.70918E+00-3.03581E+01-3.19886E+00-1.99381E+01-1.60162E+00-9.88088E+00-1.53085E-06-9.40784E-06
 IR=  5
-1.25245E+01-1.21586E+02-1.80994E+01-1.00940E+02-1.10999E+01-6.34141E+01-9.76939E+00-6.01857E+01-8.25782E+00-5.46721E+01
-6.65317E+00-4.24246E+01-5.00534E+00-3.10933E+01-3.34040E+00-2.03878E+01-1.67063E+00-1.01080E+01-1.19853E-06-7.21220E-06
 IR=  6
-1.41308E+01-1.26286E+02-1.75374E+01-1.04152E+02-1.22763E+01-6.96036E+01-1.06801E+01-6.96831E+01-9.93917E+00-5.67152E+01
-7.13839E+00-4.31426E+01-5.33498E+00-3.19738E+01-3.54452E+00-2.08834E+01-1.76822E+00-1.02434E+01-1.01226E-06-5.94944E-06
 IR=  7
-1.58098E+01-1.30214E+02-1.68428E+01-1.08613E+02-1.38486E+01-8.71844E+01-1.18169E+01-7.08098E+01-8.73589E+00-5.63760E+01
-7.68809E+00-4.35008E+01-5.69622E+00-3.28697E+01-3.76407E+00-2.08671E+01-1.87139E+00-1.03898E+01-9.91783E-07-4.91318E-06
 IR=  8
-2.02787E+01-1.33315E+02-1.81786E+01-1.08371E+02-1.96318E+01-8.81870E+01-1.30428E+01-7.18863E+01-1.06683E+01-5.67312E+01
-8.23859E+00-4.38031E+01-6.05153E+00-3.20004E+01-3.97364E+00-2.09514E+01-1.98682E+00-1.03853E+01-8.03298E-07-4.22729E-06
 IR=  9
-2.43127E+01-1.35605E+02-2.09864E+01-1.09480E+02-1.74965E+01-8.86088E+01-1.42734E+01-7.16829E+01-1.13678E+01-5.68474E+01
-8.75917E+00-4.38632E+0 -6.37619E+00-3.20349E+01-4.16219E+00-2.09716E+01-2.09958E+00-1.03760E+01-7.33098E-07-3.70832E-06
 IR= 10
-2.87230E+01-1.37107E+02-2.39513E+01-1.10003E+02-1.93994E+01-8.90028E+01-1.54937E+01-7.14998E+01-1.21183E+01-5.67798E+01
-9.22080E+00-4.38032E+01-6.66008E+00-3.19928E+01-4.32519E+00-2.09487E+01-2.12985E+00-1.03638E+01-6.74484E-07-3.29752E-06
 IR= 11
-3.33563E+01-1.37857E+02-2.67975E+01-1.10006E+02-2.11478E+01-8.89734E+01-1.65907E+01-7.18424E+01-1.27821E+01-5.69735E+01
-9.62801E+00-4.38557E+01-6.90360E+00-3.19967E+01-4.46185E+00-2.09907E+01-2.19118E+00-1.03383E+01-6.23956E-07-2.95174E-06


EZV
 IR=  1
-2.74856E+01-9.85744E+01-2.74856E+01-9.85744E+01-2.74856E+01-9.85744E+01-2.74856E+01-9.85744E+01-2.74856E+01-9.85744E+01
-2.74856E+01-9.85744E+01-2.74856E+01-9.85744E+01-2.74856E+01-9.85744E+01-2.74856E+01-9.85744E+01-2.74856E+01-9.85744E+01
 IR=  2
-4.87776E+01-8.96703E+01-4.48514E+01-8.90911E+01-4.38409E+01-8.84498E+01-4.27784E+01-8.83208E+01-4.20381E+01-8.80780E+01
-4.14347E+01-8.78077E+01-4.09644E+01-8.77803E+01-4.06331E+01-8.77149E+01-4.04335E+01-8.76730E+01-4.03671E+01-8.76598E+01
 IR=  3
-6.27084E+01-7.98870E+01-5.91842E+01-7.84308E+01-5.61127E+01-7.76168E+01-5.39410E+01-7.71288E+01-5.14291E+01-7.68986E+01
-4.97483E+01-7.67349E+01-4.84731E+01-7.68935E+01-4.75804E+01-7.67028E+01-4.70919E+01-7.67087E+01-4.68771E+01-7.67079E+01
 IR=  4
-7.02[illegible]E+01-8.08278E+01-7.15458E+01-8.71713E+01-8.59529E+01-8.63540E+01-8.13789E+01-8.80804E+01-9.77137E+01-8.61271E+01
-[illegible]E+01-8.63353E+01-9.27482E+01-8.69829E+01-9.12859E+01-8.68339E+01-9.04125E+01-8.69805E+01-9.01505E+01-8.70359E+01
 IR=  5
-1.83459E+01-9.72283E+01-8.20744E+01-9.56067E+01-7.37230E+01-9.50057E+01-6.70696E+01-9.45111E+01-6.18734E+01-9.51864E+01
-5.76187E+01-9.69318E+01-5.50258E+01-9.78498E+01-5.30529E+01-9.84283E+01-5.19135E+01-9.88440E+01-9.15388E+01-9.87084E+01
 IR=  6
-1.05077E+02-4.50697E+01-9.09943E+01-4.39428E+01-7.98000E+01-4.43583E+01-7.11134E+01-4.99945E+01-6.45108E+01-4.70448E+01
-5.95383E+01-4.85241E+01-5.60032E+01-4.98095E+01-5.38068E+01-5.07795E+01-5.22263E+01-5.13840E+01-5.17797E+01-5.19888E+01
 IR=  7
-1.16392E+02-3.44730E+01-9.63558E+01-3.23359E+01-8.44707E+01-3.38269E+01-7.38285E+01-3.68928E+01-6.60320E+01-3.87504E+01
-[illegible]E+01-4.10431E+01-5.81173E+01-4.29459E+01-5.33794E+01-4.43942E+01-5.18076E+01-4.52150E+01-5.12975E+01-4.55041E+01
```

```
 IR=  8
-1.26434E+02-1.98118E+01-1.04430E+02-2.09072E+01-8.79636E+01-2.39798E+01-7.57229E+01-2.78450E+01-6.67249E+01-3.12369E+01
-6.02189E+01-3.43983E+01-5.56529E+01-3.69477E+01-5.26417E+01-3.87999E+01-5.09304E+01-3.99192E+01-5.03754E+01-4.02933E+01
 IR=  9
-1.34972E+02-6.60998E+00-1.09315E+02-9.75364E+00-9.04685E+01-1.49584E+01-7.87314E+01-1.98466E+01-6.68001E+01-2.44455E+01
-5.97175E+01-2.84979E+01-5.48029E+01-3.18960E+01-5.15877E+01-3.39866E+01-4.97710E+01-3.53591E+01-4.91834E+01-3.58159E+01
 IR=  10
-1.42331E+02 6.41451E+00-1.13130E+02 1.04034E+00-8.21460E+01-5.68188E+00-7.71170E+01-1.23603E+01-6.84153E+01-1.83134E+01
-5.80779E+01-2.32547E+01-5.36894E+01-2.70862E+01-5.03360E+01-2.98030E+01-4.84494E+01-3.14182E+01-4.78356E+01-3.19839E+01
 IR=  11
-1.48484E+02 1.83431E+01-1.18018E+02 1.14440E+01-8.31288E+01 2.64403E+00-7.70114E+01-5.83128E+00-6.66894E+01-1.27787E+01
-5.78030E+01-1.05901E+01-5.24325E+01-2.30353E+01-4.89693E+01-2.81544E+01-4.70310E+01-2.79993E+01-4.64072E+01-2.86093E+01


CRH
 IR=  1
-2.39885E+01-1.21846E+02-2.45059E+01-1.18233E+02-2.48788E+01-1.15786E+02-2.51842E+01-1.13988E+02-2.53569E+01-1.12619E+02
-2.56094E+01-1.11838E+02-2.56115E+01-1.10939E+02-2.56827E+01-1.10489E+02-2.57837E+01-1.10198E+02-2.57371E+01-1.10110E+02
 IR=  2
-3.33819E+01-1.14988E+02-3.35805E+01-1.11247E+02-3.35871E+01-1.08612E+02-3.35838E+01-1.06881E+02-3.34117E+01-1.05260E+02
-3.32905E+01-1.04225E+02-3.31812E+01-1.03491E+02-3.30959E+01-1.03000E+02-3.30423E+01-1.02719E+02-3.30241E+01-1.02629E+02
 IR=  3
-4.17804E+01-1.07573E+02-4.08233E+01-1.03741E+02-3.99366E+01-1.01057E+02-3.89171E+01-9.91858E+01-3.81126E+01-9.78134E+01
-3.74468E+01-9.69059E+01-3.69287E+01-9.62742E+01-3.65990E+01-9.58787E+01-3.63395E+01-9.56394E+01-3.62668E+01-9.55662E+01
 IR=  4
-4.91486E+01-9.98277E+01-4.66239E+01-9.60621E+01-4.43704E+01-9.38014E+01-4.24542E+01-9.20047E+01-4.09895E+01-9.09806E+01
-3.98490E+01-9.03347E+01-3.87210E+01-8.99379E+01-3.80739E+01-8.97171E+01-3.76999E+01-8.95854E+01-3.75753E+01-8.95483E+01
 IR=  5
-5.55037E+01-9.17698E+01-5.11943E+01-8.93875E+01-4.75927E+01-8.64296E+01-4.46807E+01-8.53527E+01-4.23903E+01-8.48088E+01
-4.06419E+01-8.45886E+01-3.93617E+01-8.44900E+01-3.84844E+01-8.44970E+01-3.79843E+01-8.45038E+01-3.78185E+01-8.45122E+01
 IR=  6
-6.08849E+01-8.35130E+01-5.48820E+01-8.08393E+01-4.97714E+01-7.96340E+01-4.59429E+01-7.92954E+01-4.30046E+01-7.93049E+01
-4.08527E+01-7.95462E+01-3.92937E+01-7.98347E+01-3.82477E+01-8.00864E+01-3.76467E+01-8.02932E+01-3.74508E+01-8.03113E+01
 IR=  7
-6.52608E+01-7.51991E+01-5.72491E+01-7.35053E+01-5.11089E+01-7.32835E+01-4.64828E+01-7.37104E+01-4.30500E+01-7.44308E+01
-4.05494E+01-7.51911E+01-3.87842E+01-7.58622E+01-3.76148E+01-7.63747E+01-3.69482E+01-7.66932E+01-3.67318E+01-7.68009E+01
 IR=  8
-6.87305E+01-6.68070E+01-5.89809E+01-6.84848E+01-5.17831E+01-6.73410E+01-4.84793E+01-6.86997E+01-4.26480E+01-7.01270E+01
-3.99087E+01-7.14187E+01-3.80027E+01-7.24884E+01-3.67536E+01-7.32361E+01-3.60464E+01-7.37018E+01-3.58178E+01-7.38567E+01
 IR=  9
-7.13188E+01-5.85440E+01-5.99823E+01-5.87375E+01-5.10662E+01-6.18728E+01-4.80875E+01-6.41913E+01-4.19483E+01-6.83343E+01
-3.89505E+01-6.81448E+01-3.70589E+01-6.95631E+01-3.57684E+01-7.09731E+01-3.50387E+01-7.11798E+01-3.48039E+01-7.13784E+01
 IR=  10
-7.30792E+01-5.04404E+01-6.03789E+01-5.33902E+01-5.19257E+01-6.69543E+01-4.93520E+01-6.01490E+01-4.10462E+01-6.29959E+01
-3.80978E+01-6.53059E+01-3.60273E+01-6.70899E+01-3.47188E+01-6.83046E+01-3.39863E+01-6.90351E+01-3.37505E+01-6.92763E+01
 IR=  11
-7.40683E+01-4.25899E+01-6.02893E+01-4.74359E+01-5.08328E+01-5.22727E+01-4.94142E+01-5.66350E+01-4.00078E+01-6.00591E+01
-3.69992E+01-6.28394E+01-3.49549E+01-6.48228E+01-3.36530E+01-6.63650E+01-3.29278E+01-6.72113E+01-3.26946E+01-6.74895E+01
 3.97417E+01 9.21195E+01 3.80476E+01 9.51982E+01 3.67047E+01 9.74106E+01 3.58341E+01 9.90529E+01 3.47056E+01 1.00277E+02
 3.41268E+01 1.01185E+02 3.36340E+01 1.01841E+02 3.32920E+01 1.02286E+02 3.30908E+01 1.02594E+02 3.30241E+01 1.02629E+02
 IR=  3
 9.09754E+01 8.48512E+01 4.71987E+01 8.78423E+01 4.42543E+01 8.97820E+01 4.19043E+01 9.14610E+01 4.00516E+01 9.27867E+01
 3.86227E+01 9.38147E+01 3.75835E+01 9.45963E+01 3.68331E+01 9.51509E+01 3.64086E+01 9.54600E+01 3.62682E+01 9.55662E+01
 IR=  4
 8.08619E+01 7.69197E+01 5.47880E+01 7.97316E+01 4.99912E+01 8.21080E+01 4.62345E+01 8.41188E+01 4.33254E+01 8.57969E+01
 4.11215E+01 8.71574E+01 3.95129E+01 8.82078E+01 3.84140E+01 8.89855E+01 3.77835E+01 8.94000E+01 3.75753E+01 8.95483E+01
 IR=  5
 6.96927E+01 8.04670E+01 6.10132E+01 7.16782E+01 5.43068E+01 7.46059E+01 4.91640E+01 7.72087E+01 4.52663E+01 7.94395E+01
 4.23605E+01 8.12704E+01 4.02861E+01 8.28929E+01 3.88012E+01 8.37158E+01 3.80814E+01 8.43108E+01 3.78185E+01 8.45122E+01
 IR=  6
 7.73745E+01 5.96316E+01 6.80254E+01 6.36095E+01 5.74809E+01 6.73967E+01 5.10409E+01 7.08033E+01 4.62743E+01 7.37247E+01
 4.27933E+01 7.61152E+01 4.03296E+01 7.79631E+01 3.86938E+01 7.82732E+01 3.77549E+01 8.00583E+01 3.74806E+01 8.03113E+01
 IR=  7
 8.39264E+01 5.05403E+01 6.99535E+01 5.56812E+01 5.96600E+01 6.08539E+01 6.21185E+01 6.49190E+01 4.86171E+01 6.96211E+01
 4.26690E+01 7.16177E+01 3.99104E+01 7.39123E+01 3.80953E+01 7.95486E+01 3.70654E+01 7.84839E+01 3.67316E+01 7.68009E+01
 IR=  8
 8.93816E+01 4.13159E+01 7.29148E+01 4.79204E+01 6.10690E+01 5.41202E+01 5.29642E+01 5.99502E+01 4.64816E+01 6.40807E+01
 4.21784E+01 6.75988E+01 3.92033E+01 7.04406E+01 3.72848E+01 7.22543E+01 3.61709E+01 7.34838E+01 3.58178E+01 7.38567E+01
 IR=  9
 9.17814E+01 3.20699E+01 7.50180E+01 4.04582E+01 6.18281E+01 4.81179E+01 5.25380E+01 5.48766E+01 4.80046E+01 6.00515E+01
 4.1 .0DE+01 6.42846E+01 3.83206E+01 6.74591E+01 3.63020E+01 6.96586E+01 3.51690E+01 7.09504E+01 3.48039E+01 7.13784E+01
 IR=  10
 9.21788E+01 2.29022E+01 7.63647E+01 3.33302E+01 6.20474E+01 4.29555E+01 5.21490E+01 5.02704E+01 4.52856E+01 5.64810E+01
 4.05467E+01 6.13077E+01 3.73370E+01 6.48922E+01 3.52740E+01 6.73591E+01 3.41212E+01 6.88019E+01 3.37505E+01 6.92763E+01
 IR=  11
 9.96324E+01 1.39035E+01 7.70502E+01 2.85747E+01 6.18331E+01 3.74303E+01 5.14831E+01 4.82987E+01 4.43987E+01 5.33201E+01
 3.95576E+01 5.87091E+01 3.83035E+01 6.26757E+01 3.42239E+01 6.53899E+01 3.30883E+01 6.69709E+01 3.26946E+01 6.74895E+01
```

```
GRID 2
   R(1)= 0.2000     DR= 0.0500     NR= 17
THET(1)= 0.         DTH= 0.0873    NTH= 5


CRV
 (R= 1
-3.335832E+01-1.378957E+02-2.999523E+01-1.229388E+02-2.875795E+01-1.100066E+02-2.381882E+01-9.889708E+01-2.111478E+01-8.957346E+01
 (R= 2
-4.512125E+01-1.387655E+02-3.095508E+01-1.212882E+02-3.361377E+01-1.061861E+02-2.903321E+01-9.687468E+01-2.910682E+01-8.689077E+01
 (R= 3
-6.604685E+01-1.321566E+02-4.688682E+01-1.170845E+02-3.937305E+01-1.044125E+02-3.320044E+01-9.383498E+01-2.813532E+01-8.421088E+01
 (R= 4
-8.529317E+01-1.249899E+02-5.324395E+01-1.110705E+02-4.378188E+01-9.995105E+01-3.823868E+01-8.971477E+01-3.022968E+01-8.107811E+01
 (R= 5
-7.230800E+01-1.184935E+02-5.705877E+01-1.042082E+02-4.877777E+01-9.419568E+01-3.680221E+01-8.595088E+01-3.149368E+01-7.794935E+01
 (R= 6
-7.711276E+01-1.087898E+02-6.080095E+01-9.704305E+01-4.958305E+01-8.879111E+01-3.928621E+01-8.145947E+01-3.209756E+01-7.478944E+01
```

NEC Input

```
'
CMSOMMERFELD'S FUNCTION FOR RADIAL WIRE SCREEN OVER FINITE GROUND
CMSCREEN RADIUS = 30. M     (1. WAVELENGTH RADIUS)
CESCREEN HEIGHT = .01 M     8 RADIAL WIRES
GW0,12,0.,0.,.01,30.,0.,.01,.003,
GR0,8,
GE1,
FR0,1,0,0,10.,
GN2,0,0,0,4.,.001,
NG
NX
CEMONOPOLE ON RADIAL WIRE GROUND SCREEN.
GF
GW1,8,0.,0.,.01,0.,0.,7.51,.003,
GE1,
EX0,1,1,0,1.,
RP0,19,2,1001,0.,0.,5.,90.,
EN
```

NEC Output

```
**************************************

  NUMERICAL ELECTROMAGNETICS CODE

**************************************


 - - - COMMENTS - - -

GREEN'S FUNCTION FOR RADIAL WIRE SCREEN OVER FINITE GROUND
SCREEN RADIUS = 30. M     (1. WAVELENGTH RADIUS)
SCREEN HEIGHT = .01 M     8 RADIAL WIRES


 - - - STRUCTURE SPECIFICATION - - -

    COORDINATES MUST BE INPUT IN
    METERS OR BE SCALED TO METERS
    BEFORE STRUCTURE INPUT IS ENDED

WIRE                                                                NO. OF  FIRST  LAST   TAG
NO.       X1          Y1          Z1          X2          Y2          Z2        RADIUS  SEG.   SEG.   SEG.   NO.
   1      0.          0.        0.01000    30.00000     0.         0.01000   0.00300    12      1     12      0
    STRUCTURE ROTATED ABOUT Z-AXIS  8 TIMES.  LABLES INCREMENTED BY    0

 GROUND PLANE SPECIFIED.

 WHERE WIRE ENDS TOUCH GROUND, CURRENT WILL BE INTERPOLATED TO IMAGE IN GROUND PLANE.

  TOTAL SEGMENTS USED=   72     NO. SEG. IN A SYMMETRIC CELL=   12     SYMMETRY FLAG= -1
STRUCTURE HAS   8 FOLD ROTATIONAL SYMMETRY


       - MULTIPLE WIRE JUNCTIONS -
JUNCTION    SEGMENTS  (- FOR END 1, + FOR END 2)
   1         -1  -13  -25  -37  -49  -61


 - - - - SEGMENTATION DATA - - - -

    COORDINATES IN METERS

    1+ AND 1- INDICATE THE SEGMENTS BEFORE AND AFTER 1

SEG.    COORDINATES OF SEG. CENTER      SEG      ORIENTATION ANGLES      WIRE     CONNECTION DATA     TAG
NO.        X          Y          Z      LENGTH     ALPHA      BETA     RADIUS     1-     1     1+    NO.
  1     1.25000    0.        0.01000   2.50000    0.         0.       0.00300    -13    1     2      0
  2     3.75000    0         0.01000   2.50000    0.         0.       0.00300     1     2     3      0
  3     6.25000    0         0.01000   2.50000    0          0.       0.00300     2     3     4      0
  4     8.75000    0         0.01000   2.50000    0.         0.       0.00300     3     4     5      0
  5    11.25000    0         0.01000   2.50000    0.         0.       0.00300     4     5     6      0
  6    13.75000    0.        0.01000   2.50000    0.         0.       0.00300     5     6     7      0
  7    16.25000    0.        0.01000   2.50000    0.         0.       0.00300     6     7     8      0
  8    18.75000    0.        0.01000   2.50000    0          0.       0.00300     7     8     9      0
  9    21.25000    0.        0.01000   2.50000    0.         0.       0.00300     8     9     10     0
 10    23.75000    0.        0.01000   2.50000    0.         0.       0.00300     9     10    11     0
 11    26.25000    0.        0.01000   2.50000    0.         0.       0.00300     10    11    12     0
 12    28.75000    0.        0.01000   2.50000    0.         0.       0.00300     11    12    0      0
 13     0.62500    1.08253   0.01000   2.50000    0.        60.00000  0.00300    -25    13    14     0
 14     1.87500    3.24760   0.01000   2.50000    0         60.00000  0.00300     13    14    15     0
 15     3.12500    5.41266   0.01000   2.50000    0.        60.00000  0.00300     14    15    16     0
 16     4.37500    7.57772   0.01000   2.50000    0.        60.00000  0.00300     15    16    17     0
 17     5.62500    9.74279   0.01000   2.50000    0.        60.00000  0.00300     16    17    18     0
 18     6.87500   11.90785   0.01000   2.50000    0.        60.00000  0.00300     17    18    19     0
 19     8.12500   14.07291   0.01000   2.50000    0.        60.00000  0.00300     18    19    20     0
 20     9.37500   16.23798   0.01000   2.50000    0.        60.00000  0.00300     19    20    21     0
 21    10.62500   18.40304   0.01000   2.50000    0.        60.00000  0.00300     20    21    22     0
 22    11.87500   20.56810   0.01000   2.50000    0.        60.00000  0.00300     21    22    23     0
 23    13.12500   22.73317   0.01000   2.50000    0         60.00000  0.00300     22    23    24     0
 24    14.37500   24.89823   0.01000   2.50000    0.        60.00000  0.00300     23    24    0      0
```

25	-0.62500	1.08253	0.01000	2.50000	0.	120.00000	0.00300	-37	25	26	0
26	-1.87500	3.24760	0.01000	2.50000	0.	120.00000	0.00300	25	26	27	0
27	-3.12500	5.41266	0.01000	2.50000	0.	120.00000	0.00300	26	27	28	0
28	-4.37500	7.57772	0.01000	2.50000	0.	120.00000	0.00300	27	28	29	0
29	-5.62500	9.74279	0.01000	2.50000	0.	120.00000	0.00300	28	29	30	0
30	-6.87500	11.90785	0.01000	2.50000	0.	120.00000	0.00300	29	30	31	0
31	-8.12500	14.07291	0.01000	2.50000	0.	120.00000	0.00300	30	31	32	0
32	-9.37500	16.23798	0.01000	2.50000	0.	120.00000	0.00300	31	32	33	0
33	-10.62500	18.40304	0.01000	2.50000	0.	120.00000	0.00300	32	33	34	0
34	-11.87500	20.56810	0.01000	2.50000	0.	120.00000	0.00300	33	34	35	0
35	-13.12500	22.73317	0.01000	2.50000	0.	120.00000	0.00300	34	35	36	0
36	-14.37500	24.89823	0.01000	2.50000	0.	120.00000	0.00300	35	36	0	0
37	-1.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	-48	37	38	0
38	-3.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	37	38	39	0
39	-6.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	38	39	40	0
40	-8.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	39	40	41	0
41	-11.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	40	41	42	0
42	-13.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	41	42	43	0
43	-16.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	42	43	44	0
44	-18.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	43	44	45	0
45	-21.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	44	45	46	0
46	-23.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	45	46	47	0
47	-26.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	46	47	48	0
48	-28.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	47	48	0	0
49	-0.62500	-1.08253	0.01000	2.50000	0.	-120.00000	0.00300	-61	49	50	0
50	-1.87500	-3.24760	0.01000	2.50000	0.	-120.00000	0.00300	49	50	51	0
51	-3.12500	-5.41266	0.01000	2.50000	0.	-120.00000	0.00300	50	51	52	0
52	-4.37500	-7.57772	0.01000	2.50000	0.	-120.00000	0.00300	51	52	53	0
53	-5.62500	-9.74279	0.01000	2.50000	0.	-120.00000	0.00300	52	53	54	0
54	-6.87500	-11.90785	0.01000	2.50000	0.	-120.00000	0.00300	53	54	55	0
55	-8.12500	-14.07291	0.01000	2.50000	0.	-120.00000	0.00300	54	55	56	0
56	-9.37500	-16.23798	0.01000	2.50000	0.	-120.00000	0.00300	55	56	57	0
57	-10.62500	-18.40304	0.01000	2.50000	0.	-120.00000	0.00300	56	57	58	0
58	-11.87500	-20.56810	0.01000	2.50000	0.	-120.00000	0.00300	57	58	59	0
59	-13.12500	-22.73317	0.01000	2.50000	0.	-120.00000	0.00300	58	59	60	0
60	-14.37500	-24.89823	0.01000	2.50000	0.	-120.00000	0.00300	59	60	0	0
61	0.62500	-1.08253	0.01000	2.50000	0.	-60.00000	0.00300	-1	61	62	0
62	1.87500	-3.24760	0.01000	2.50000	0.	-60.00000	0.00300	61	62	63	0
63	3.12500	-5.41266	0.01000	2.50000	0.	-60.00000	0.00300	62	63	64	0
64	4.37500	-7.57772	0.01000	2.50000	0.	-60.00000	0.00300	63	64	65	0
65	5.62500	-9.74279	0.01000	2.50000	0.	-60.00000	0.00300	64	65	66	0
66	6.87500	-11.90785	0.01000	2.50000	0.	-60.00000	0.00300	65	66	67	0
67	8.12500	-14.07291	0.01000	2.50000	0.	-60.00000	0.00300	66	67	68	0
68	9.37500	-16.23798	0.01000	2.50000	0.	-60.00000	0.00300	67	68	69	0
69	10.62500	-18.40304	0.01000	2.50000	0.	-60.00000	0.00300	68	69	70	0
70	11.87500	-20.56810	0.01000	2.50000	0.	-60.00000	0.00300	69	70	71	0
71	13.12500	-22.73317	0.01000	2.50000	0.	-60.00000	0.00300	70	71	72	0
72	14.37500	-24.89823	0.01000	2.50000	0.	-60.00000	0.00300	71	72	0	0

***** DATA CARD NO.	1	FR	0	1	0	0	1.00000E+01	0.	0.	0.	0.	0.
***** DATA CARD NO	2	GN	2	0	0	0	4.00000E+00	1.00000E-03	0.	0.	0.	0.
***** DATA CARD NO.	3	MG	-0	-0	-0	-0	0.	0.	0.	0.	0.	0.

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 1.0000E+01 MHZ
WAVELENGTH= 2.9980E+01 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FINITE GROUND. SOMMERFELD SOLUTION
RELATIVE DIELECTRIC CONST.= 4.000
CONDUCTIVITY= 1.000E-03 MHOS/METER
COMPLEX DIELECTRIC CONSTANT= 4.00000E+00-1.79750E+00

- - - MATRIX TIMING - - -

FILL= 1.687 SEC., FACTOR= 0.032 SEC.

****NUMERICAL GREEN'S FUNCTION FILE ON TAPE 20 ****
MATRIX STORAGE = 864 COMPLEX NUMBERS

***** DATA CARD NO. 4 NX -0 -0 -0 -0 0. 0. 0. 0. 0. 0.

****

NUMERICAL ELECTROMAGNETICS CODE

****

- - - - COMMENTS - - - -

MONOPOLE ON RADIAL WIRE GROUND SCREEN.

****
****
**
** NUMERICAL GREEN'S FUNCTION **
** NO. SEGMENTS = 78 NO. PATCHES = 0 **
** NO. SYMMETRIC SECTIONS = 6 **
** N.G.F. MATRIX - CORE STORAGE = 864 COMPLEX NUMBERS, CASE 2 **
** FREQUENCY = 1.000000E+01 MHZ. **
** FINITE GROUND. SOMMERFELD SOLUTION **
** GROUND PARAMETERS - DIELECTRIC CONSTANT = 4.000000E+00 **
** CONDUCTIVITY = 1.000000E-03 MHOS/M. **
**
** GREEN'S FUNCTION FOR RADIAL WIRE SCREEN OVER FINITE GROUND **
** SCREEN RADIUS = 30. M (1. WAVELENGTH RADIUS) **
** SCREEN HEIGHT = .01 M 6 RADIAL WIRES **
**
****
****

- - - STRUCTURE SPECIFICATION - - -

COORDINATES MUST BE INPUT IN
METERS OR BE SCALED TO METERS
BEFORE STRUCTURE INPUT IS ENDED

WIRE NO	X1	Y1	Z1	X2	Y2	Z2	RADIUS	NO. OF SEG.	FIRST SEG.	LAST SEG.	TAG NO.
1	0.	0.	0.01000	0.	0.	7.81000	0.00300	6	73	78	1

GROUND PLANE SPECIFIED.

WHERE WIRE ENDS TOUCH GROUND, CURRENT WILL BE INTERPOLATED TO IMAGE IN GROUND PLANE.

TOTAL SEGMENTS USED= 78 NO. SEG. IN A SYMMETRIC CELL= 78 SYMMETRY FLAG= 0

- MULTIPLE WIRE JUNCTIONS -

JUNCTION	SEGMENTS (- FOR END 1, + FOR END 2)
1	-1 -13 -25 -37 -49 -61 -73

- - - - SEGMENTATION DATA - - - -

COORDINATES IN METERS

I+ AND I- INDICATE THE SEGMENTS BEFORE AND AFTER I

SEG. NO.	COORDINATES OF SEG. CENTER X	Y	Z	SEG. LENGTH	ORIENTATION ANGLES ALPHA	BETA	WIRE RADIUS	CONNECTION DATA I-	I	I+	TAG NO.
1	1.25000	0.	0.01000	2.50000	-0.00000	0.	0.00300	-13	1	2	0
2	3.75000	0.	0.01000	2.50000	0.	0.	0.00300	1	2	3	0
3	6.25000	0.	0.01000	2.50000	0.	0.	0.00300	2	3	4	0
4	8.75000	0.	0.01000	2.50000	0.	0.	0.00300	3	4	5	0
5	11.25000	0.	0.01000	2.50000	0.	0.	0.00300	4	5	6	0
6	13.75000	0.	0.01000	2.50000	0.	0.	0.00300	5	6	7	0
7	16.25000	0.	0.01000	2.50000	0.	0.	0.00300	6	7	8	0
8	18.75000	0.	0.01000	2.50000	0.	0.	0.00300	7	8	9	0
9	21.25000	0.	0.01000	2.50000	0.	0.	0.00300	8	9	10	0
10	23.75000	0.	0.01000	2.50000	0.	0.	0.00300	9	10	11	0
11	26.25000	0.	0.01000	2.50000	0.	0.	0.00300	10	11	12	0
12	28.75000	0.	0.01000	2.50000	0.	0.	0.00300	11	12	0	0
13	0.62500	1.08253	0.01000	2.50000	-0.00000	60.00000	0.00300	-25	13	14	0
14	1.87500	3.24760	0.01000	2.50000	0.	60.00000	0.00300	13	14	15	0
15	3.12500	5.41266	0.01000	2.50000	0.	60.00000	0.00300	14	15	16	0
16	4.37500	7.57772	0.01000	2.50000	0.	60.00000	0.00300	15	16	17	0
17	5.62500	9.74279	0.01000	2.50000	0.	60.00000	0.00300	16	17	18	0
18	6.87500	11.90785	0.01000	2.50000	0.	60.00000	0.00300	17	18	19	0
19	8.12500	14.07291	0.01000	2.50000	0.	60.00000	0.00300	18	19	20	0
20	9.37500	16.23798	0.01000	2.50000	0.	60.00000	0.00300	19	20	21	0
21	10.62500	18.40304	0.01000	2.50000	0.	60.00000	0.00300	20	21	22	0
22	11.87500	20.56810	0.01000	2.50000	0.	60.00000	0.00300	21	22	23	0
23	13.12500	22.73317	0.01000	2.50000	0.	60.00000	0.00300	22	23	24	0
24	14.37500	24.89823	0.01000	2.50000	0.	60.00000	0.00300	23	24	0	0
25	-0.62500	1.08253	0.01000	2.50000	-0.00000	120.00000	0.00300	-37	25	26	0
26	-1.87500	3.24760	0.01000	2.50000	0.	120.00000	0.00300	25	26	27	0
27	-3.12500	5.41266	0.01000	2.50000	0.	120.00000	0.00300	26	27	28	0
28	-4.37500	7.57772	0.01000	2.50000	0.	120.00000	0.00300	27	28	29	0
29	-5.62500	9.74279	0.01000	2.50000	0.	120.00000	0.00300	28	29	30	0
30	-6.87500	11.90785	0.01000	2.50000	0.	120.00000	0.00300	29	30	31	0
31	-8.12500	14.07291	0.01000	2.50000	0.	120.00000	0.00300	30	31	32	0
32	-9.37500	16.23798	0.01000	2.50000	0.	120.00000	0.00300	31	32	33	0
33	-10.62500	18.40304	0.01000	2.50000	0.	120.00000	0.00300	32	33	34	0
34	-11.87500	20.56810	0.01000	2.50000	0.	120.00000	0.00300	33	34	35	0
35	-13.12500	22.73317	0.01000	2.50000	0.	120.00000	0.00300	34	35	36	0
36	-14.37500	24.89823	0.01000	2.50000	0.	120.00000	0.00300	35	36	0	0
37	-1.25000	-0.00000	0.01000	2.50000	-0.00000	-180.00000	0.00300	-49	37	38	0
38	-3.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	37	38	39	0
39	-6.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	38	39	40	0
40	-8.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	39	40	41	0
41	-11.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	40	41	42	0
42	-13.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	41	42	43	0
43	-16.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	42	43	44	0
44	-18.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	43	44	45	0
45	-21.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	44	45	46	0
46	-23.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	45	46	47	0
47	-26.25000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	46	47	48	0
48	-28.75000	-0.00000	0.01000	2.50000	0.	-180.00000	0.00300	47	48	0	0
49	-0.62500	-1.08253	0.01000	2.50000	-0.00000	-120.00000	0.00300	-61	49	50	0
50	-1.87500	-3.24760	0.01000	2.50000	0.	-120.00000	0.00300	49	50	51	0
51	-3.12500	-5.41266	0.01000	2.50000	0.	-120.00000	0.00300	50	51	52	0
52	-4.37500	-7.57772	0.01000	2.50000	0.	-120.00000	0.00300	51	52	53	0
53	-5.62500	-9.74279	0.01000	2.50000	0.	-120.00000	0.00300	52	53	54	0
54	-6.87500	-11.90785	0.01000	2.50000	0.	-120.00000	0.00300	53	54	55	0
55	-8.12500	-14.07291	0.01000	2.50000	0.	-120.00000	0.00300	54	55	56	0
56	-9.37500	-16.23798	0.01000	2.50000	0.	-120.00000	0.00300	55	56	57	0
57	-10.62500	-18.40304	0.01000	2.50000	0.	-120.00000	0.00300	56	57	58	0
58	-11.87500	-20.56810	0.01000	2.50000	0.	-120.00000	0.00300	57	58	59	0
59	-13.12500	-22.73317	0.01000	2.50000	0.	-120.00000	0.00300	58	59	60	0
60	-14.37500	-24.89823	0.01000	2.50000	0.	-120.00000	0.00300	59	60	0	0
61	0.62500	-1.08253	0.01000	2.50000	-0.00000	-60.00000	0.00300	-73	61	62	0
62	1.87500	-3.24760	0.01000	2.50000	0.	-60.00000	0.00300	61	62	63	0
63	3.12500	-5.41266	0.01000	2.50000	0.	-60.00000	0.00300	62	63	64	0
64	4.37500	-7.57772	0.01000	2.50000	0.	-60.00000	0.00300	63	64	65	0
65	5.62500	-9.74279	0.01000	2.50000	0.	-60.00000	0.00300	64	65	66	0
66	6.87500	-11.90785	0.01000	2.50000	0.	-60.00000	0.00300	65	66	67	0
67	8.12500	-14.07291	0.01000	2.50000	0.	-60.00000	0.00300	66	67	68	0
68	9.37500	-16.23798	0.01000	2.50000	0.	-60.00000	0.00300	67	68	69	0
69	10.62500	-18.40304	0.01000	2.50000	0.	-60.00000	0.00300	68	69	70	0
70	11.87500	-20.56810	0.01000	2.50000	0.	-60.00000	0.00300	69	70	71	0

71	13.12500	-22.73317	0.01000	2.50000	0.	-60.00000	0.00300	70	71	72	0
72	14.37500	-24.89823	0.01000	2.50000	0.	-60.03000	0.00300	71	72	0	0
73	0.00000	0.	0.63500	1.25000	90.00000	180.00000	0.00300	-1	73	74	1
74	0.	0.	1.88500	1.25000	90.00000	0.	0.00300	73	74	75	1
75	0.	0.	3.13500	1.25000	90.00000	0.	0.00300	74	75	76	1
76	0.	0.	4.38500	1.25000	90.00000	0.	0.00300	75	76	77	1
77	0	0.	5.63500	1.25000	90.00000	0.	0.00300	76	77	78	1
78	0	0	6.88500	1.25000	90.00000	0.	0.00300	77	78	0	1

N.G.F. - NUMBER OF NEW UNKNOWNS IS 12

***** DATA CARD NO. 1 EX 0 1 1 0 1.00000E+00 0. 0. 0. 0. 0.
***** DATA CARD NO. 2 RP 0 19 2 1001 0. 0. 9.00000E+00 9.00000E+01 0. 0.

- - - - - - FREQUENCY - - - - - -

FREQUENCY= 1.0000E+01 MHZ
WAVELENGTH= 2.9980E+01 METERS

APPROXIMATE INTEGRATION EMPLOYED FOR SEGMENTS MORE THAN 1.000 WAVELENGTHS APART

- - - STRUCTURE IMPEDANCE LOADING - - -

THIS STRUCTURE IS NOT LOADED

- - - ANTENNA ENVIRONMENT - - -
FINITE GROUND, SOMMERFELD SOLUTION
RELATIVE DIELECTRIC CONST.= 4.000
CONDUCTIVITY= 1.000E-03 MHOS/METER
COMPLEX DIELECTRIC CONSTANT= 4.00000E+00-1.79760E+00

- - - MATRIX TIMING - - -

FILL= 3.682 SEC., FACTOR= 0.190 SEC.

- - - ANTENNA INPUT PARAMETERS - - -

TAG NO.	SEG. NO	VOLTAGE (VOLTS) REAL	IMAG.	CURRENT (AMPS) REAL	IMAG.	IMPEDANCE (OHMS) REAL	IMAG.	ADMITTANCE (MHOS) REAL	IMAG.	POWER (WATTS)
1	73	1.00000E+00	0.	1.02942E-02	-2.09843E-03	9.32739E+01	1.90094E+01	1.02942E-02	-2.09843E-03	5.14708E-03

- - - CURRENTS AND LOCATION - - -

DISTANCES IN WAVELENGTHS

SEG. NO.	TAG NO.	COORD. OF SEG. CENTER X	Y	Z	SEG. LENGTH	- - - CURRENT (AMPS) - - - REAL	IMAG	MAG.	PHASE
1	0	0.0417	0.	0.0003	0.08339	-1.6168E-03	6.4601E-04	1.7411E-03	158.221
2	0	0.1291	0.	0.0003	0.08339	-1.0095E-03	1.1150E-03	1.5041E-03	132.155
3	0	0.2085	0.	0.0003	0.08339	-7.9255E-05	1.1886E-03	1.1912E-03	93.821
4	0	0.2919	0.	0.0003	0.08339	8.1953E-04	8.3826E-04	1.1686E-03	45.709
5	0	0.3753	0.	0.0003	0.08339	1.3339E-03	2.6378E-04	1.3598E-03	11.196
6	0	0.4586	0.	0.0003	0.08339	1.2978E-03	-2.6827E-04	1.3254E-03	-11.782
7	0	0.5420	0.	0.0003	0.08339	7.5781E-04	-5.5815E-04	9.4117E-04	-36.373
8	0	0.6254	0.	0.0003	0.08339	-3.7594E-05	-5.5184E-04	5.5298E-04	-93.999
9	0	0.7088	0.	0.0003	0.08339	-7.5140E-04	-3.4775E-04	8.2787E-04	-155.165
10	0	0.7922	0.	0.0003	0.08339	-1.0988E-03	-1.1390E-04	1.1088E-03	-174.072
11	0	0.8756	0.	0.0003	0.08339	-9.4915E-04	1.0517E-05	9.4933E-04	178.882

12	0	0.0590	0.	0.0003	0.08339	-3.8115E-04	2.3433E-05	3.8187E-04	176.482
13	0	0.0208	0.0361	0.0003	0.08339	-1.6169E-03	6.4601E-04	1.7411E-03	158.221
14	0	0.0625	0.1083	0.0003	0.08339	-1.0095E-03	1.1150E-03	1.5041E-03	132.155
15	0	0.1042	0.1805	0.0003	0.08339	-7.9255E-05	1.1068E-03	1.1082E-03	93.821
16	0	0.1459	0.2528	0.0003	0.08339	8.1553E-04	8.3826E-04	1.1695E-03	45.788
17	0	0.1876	0.3250	0.0003	0.08339	1.3339E-03	2.6378E-04	1.3598E-03	11.186
18	0	0.2293	0.3972	0.0003	0.08339	1.2978E-03	-2.6927E-04	1.3254E-03	-11.722
19	0	0.2710	0.4694	0.0003	0.08339	7.5781E-04	-5.5815E-04	9.4117E-04	-36.373
20	0	0.3127	0.5416	0.0003	0.08339	-3.7594E-05	-5.5184E-04	5.5282E-04	-93.899
21	0	0.3544	0.6138	0.0003	0.08339	-7.5140E-04	-3.4775E-04	8.2787E-04	-155.165
22	0	0.3961	0.6861	0.0003	0.08339	-1.0969E-03	-1.1390E-04	1.1028E-03	-174.072
23	0	0.4378	0.7583	0.0003	0.08339	-9.4915E-04	1.9517E-05	9.4933E-04	178.882
24	0	0.4795	0.8305	0.0003	0.08339	-3.8115E-04	2.3433E-05	3.8187E-04	176.482
25	0	-0.0208	0.0361	0.0003	0.08339	-1.6169E-03	6.4601E-04	1.7411E-03	158.221
26	0	-0.0625	0.1083	0.0003	0.08339	-1.0095E-03	1.1150E-03	1.5041E-03	132.155
27	0	-0.1042	0.1805	0.0003	0.08339	-7.9255E-05	1.1068E-03	1.1082E-03	93.821
28	0	-0.1459	0.2528	0.0003	0.08339	8.1553E-04	8.3826E-04	1.1695E-03	45.788
29	0	-0.1876	0.3250	0.0003	0.08339	1.3339E-03	2.6378E-04	1.3598E-03	11.186
30	0	-0.2293	0.3972	0.0003	0.08339	1.2978E-03	-2.6927E-04	1.3254E-03	-11.722
31	0	-0.2710	0.4694	0.0003	0.08339	7.5781E-04	-5.5815E-04	9.4117E-04	-36.373
32	0	-0.3127	0.5416	0.0003	0.08339	-3.7594E-05	-5.5184E-04	5.5282E-04	-93.899
33	0	-0.3544	0.6138	0.0003	0.08339	-7.5140E-04	-3.4775E-04	8.2787E-04	-155.165
34	0	-0.3961	0.6861	0.0003	0.08339	-1.0969E-03	-1.1390E-04	1.1028E-03	-174.072
35	0	-0.4378	0.7583	0.0003	0.08339	-9.4915E-04	1.9517E-05	9.4933E-04	178.882
36	0	-0.4795	0.8305	0.0003	0.08339	-3.8115E-04	2.3433E-05	3.8187E-04	176.482
37	0	-0.0417	-0.0000	0.0003	0.08339	-1.6169E-03	6.4601E-04	1.7411E-03	158.221
38	0	-0.1251	-0.0000	0.0003	0.08339	-1.0095E-03	1.1150E-03	1.5041E-03	132.155
39	0	-0.2085	-0.0000	0.0003	0.08339	-7.9255E-05	1.1068E-03	1.1082E-03	93.821
40	0	-0.2919	-0.0000	0.0003	0.08339	8.1553E-04	8.3826E-04	1.1695E-03	45.788
41	0	-0.3753	-0.0000	0.0003	0.08339	1.3339E-03	2.6378E-04	1.3598E-03	11.186
42	0	-0.4586	-0.0000	0.0003	0.08339	1.2978E-03	-2.6927E-04	1.3254E-03	-11.722
43	0	-0.5420	-0.0000	0.0003	0.08339	7.5781E-04	-5.5815E-04	9.4117E-04	-36.373
44	0	-0.6254	-0.0000	0.0003	0.08339	-3.7594E-05	-5.5184E-04	5.5282E-04	-93.899
45	0	-0.7088	-0.0000	0.0003	0.08339	-7.5140E-04	-3.4775E-04	8.2787E-04	-155.165
46	0	-0.7922	-0.0000	0.0003	0.08339	-1.0969E-03	-1.1390E-04	1.1028E-03	-174.072
47	0	-0.8756	-0.0000	0.0003	0.08339	-9.4915E-04	1.9517E-05	9.4933E-04	178.882
48	0	-0.9590	-0.0000	0.0003	0.08339	-3.8115E-04	2.3433E-05	3.8187E-04	176.482
49	0	-0.0208	-0.0361	0.0003	0.08339	-1.6169E-03	6.4601E-04	1.7411E-03	158.221
50	0	-0.0625	-0.1083	0.0003	0.08339	-1.0095E-03	1.1150E-03	1.5041E-03	132.155
51	0	-0.1042	-0.1805	0.0003	0.08339	-7.9255E-05	1.1068E-03	1.1082E-03	93.821
52	0	-0.1459	-0.2528	0.0003	0.08339	8.1553E-04	8.3826E-04	1.1695E-03	45.788
53	0	-0.1876	-0.3250	0.0003	0.08339	1.3339E-03	2.6378E-04	1.3598E-03	11.186
54	0	-0.2293	-0.3972	0.0003	0.08339	1.2978E-03	-2.6927E-04	1.3254E-03	-11.722
55	0	-0.2710	-0.4694	0.0003	0.08339	7.5781E-04	-5.5815E-04	9.4117E-04	-36.373
56	0	-0.3127	-0.5416	0.0003	0.08339	-3.7594E-05	-5.5184E-04	5.5282E-04	-93.899
57	0	-0.3544	-0.6138	0.0003	0.08339	-7.5140E-04	-3.4775E-04	8.2787E-04	-155.165
58	0	-0.3961	-0.6861	0.0003	0.08339	-1.0969E-03	-1.1390E-04	1.1028E-03	-174.072
59	0	-0.4378	-0.7583	0.0003	0.08339	-9.4915E-04	1.9517E-05	9.4933E-04	178.882
60	0	-0.4795	-0.8305	0.0003	0.08339	-3.8115E-04	2.3433E-05	3.8187E-04	176.482
61	0	0.0208	-0.0361	0.0003	0.08339	-1.6169E-03	6.4601E-04	1.7411E-03	158.221
62	0	0.0625	-0.1083	0.0003	0.08339	-1.0095E-03	1.1150E-03	1.5041E-03	132.155
63	0	0.1042	-0.1805	0.0003	0.08339	-7.9255E-05	1.1068E-03	1.1082E-03	93.821
64	0	0.1459	-0.2528	0.0003	0.08339	8.1553E-04	8.3826E-04	1.1695E-03	45.788
65	0	0.1876	-0.3250	0.0003	0.08339	1.3339E-03	2.6378E-04	1.3598E-03	11.186
66	0	0.2293	-0.3972	0.0003	0.08339	1.2978E-03	-2.6927E-04	1.3254E-03	-11.722
67	0	0.2710	-0.4694	0.0003	0.08339	7.5781E-04	-5.5815E-04	9.4117E-04	-36.373
68	0	0.3127	-0.5416	0.0003	0.08339	-3.7594E-05	-5.5184E-04	5.5282E-04	-93.899
69	0	0.3544	-0.6138	0.0003	0.08339	-7.5140E-04	-3.4775E-04	8.2787E-04	-155.165
70	0	0.3961	-0.6861	0.0003	0.08339	-1.0969E-03	-1.1390E-04	1.1028E-03	-174.072
71	0	0.4378	-0.7583	0.0003	0.08339	-9.4915E-04	1.9517E-05	9.4933E-04	178.882
72	0	0.4795	-0.8305	0.0003	0.08339	-3.8115E-04	2.3433E-05	3.8187E-04	176.482
73	1	0.0000	0.	0.0212	0.04189	1.0294E-02	-2.0984E-03	1.0501E-02	-11.511
74	1	0.	0.	0.0629	0.04189	9.6470E-03	-2.1748E-03	9.8890E-03	-12.703
75	1	0.	0.	0.1046	0.04189	8.3883E-03	-2.0833E-03	8.6190E-03	-13.951
76	1	0.	0.	0.1463	0.04189	6.5356E-03	-1.7186E-03	6.7573E-03	-14.717
77	1	0.	0.	0.1880	0.04189	4.2450E-03	-1.1713E-03	4.4037E-03	-15.428
78	1	0.	0.	0.2297	0.04189	1.9535E-03	-4.4833E-04	1.8164E-03	-16.030

- - - POWER BUDGET - - -

INPUT POWER = 5.1471E-03 WATTS
RADIATED POWER= 5.1471E-03 WATTS
STRUCTURE LOSS= 0. WATTS
NETWORK LOSS = 0. WATTS
EFFICIENCY = 100.00 PERCENT

- - - RADIATION PATTERNS - - -

- - ANGLES - - THETA DEGREES	PHI DEGREES	- POWER GAINS - VERT. DB	HOR DB	TOTAL DB	- - - POLARIZATION - - - AXIAL RATIO	TILT DEG.	SENSE	- - - E(THETA) - - - MAGNITUDE VOLTS/M	PHASE DEGREES	- - - E(PHI) - - - MAGNITUDE VOLTS/M	PHASE DEGREES
0.	0.	-999.99	-999.99	-999.99	0.	0.		1.618695E-11	37.96	8.448822E-12	-148.89
5.00	0.	-26.04	-999.99	-26.04	0.00000	0.00	LINEAR	2.771838E-02	128.17	6.171328E-12	-191.89
10.00	0.	-20.19	-999.99	-20.19	0.00000	0.00	LINEAR	5.436891E-02	120.49	9.350894E-12	-178.12
15.00	0.	-16.76	-999.99	-16.76	0.00000	0.00	LINEAR	8.079686E-02	111.66	7.783891E-12	184.19
20.00	0.	-14.10	-999.99	-14.10	0.00000	0.00	LINEAR	1.006897E-01	101.98	1.693396E-11	184.72
25.00	0.	-11.77	-999.99	-11.77	0.00000	0.00	LINEAR	1.438681E-01	90.77	1.933794E-11	173.32
30.00	0.	-9.71	-999.99	-9.71	0.00000	-0.00	LINEAR	1.817042E-01	80.97	2.043488E-11	-178.97
35.00	0.	-7.95	-999.99	-7.95	0.00000	-0.00	LINEAR	2.223895E-01	80.81	3.884218E-11	-168.65
40.00	0.	-6.54	-999.99	-6.54	0.00000	-0.00	LINEAR	2.618688E-01	77.87	5.204045E-11	-162.17
45.00	0.	-5.46	-180.75	-5.46	0.00000	-0.00	LINEAR	2.983357E-01	78.88	6.418888E-11	-157.24
50.00	0.	-4.69	-197.45	-4.69	0.00000	-0.00	LINEAR	3.237582E-01	78.34	7.448822E-11	-153.46
55.00	0.	-4.21	-180.87	-4.21	0.00000	-0.00	LINEAR	3.418816E-01	78.32	8.147776E-11	-150.50
60.00	0.	-4.03	-196.40	-4.03	0.00000	-0.00	LINEAR	3.493384E-01	78.62	8.411485E-11	-148.11
65.00	0.	-4.16	-196.64	-4.16	0.00000	-0.00	LINEAR	3.442288E-01	78.01	8.178386E-11	-146.12
70.00	0.	-4.58	-197.47	-4.58	0.00000	-0.00	LINEAR	3.243018E-01	78.31	7.431877E-11	-144.43
75.00	0.	-5.26	-199.08	-5.26	0.00000	-0.00	LINEAR	2.863768E-01	78.40	6.189386E-11	-142.99
80.00	0.	-7.03	-999.99	-7.03	0.00000	-0.00	LINEAR	2.256857E-01	78.16	4.484346E-11	-141.76
85.00	0.	-12.32	-999.99	-12.32	0.00000	-0.00	LINEAR	1.343538E-01	78.45	2.408298E-11	-140.73
90.00	0.	-999.99	-999.99	-999.99	0.	0.		8.838218E-12	-106.90	7.606897E-16	3.72
0.	90.00	-999.99	-999.99	-999.99	0.	0.		8.448822E-12	-148.89	1.618695E-11	-142.44
5.00	90.00	-26.04	-999.99	-26.04	0.00000	0.00	LINEAR	2.771758E-02	128.17	1.840158E-11	-145.19
10.00	90.00	-20.19	-999.99	-20.19	0.00000	-0.00	LINEAR	5.439581E-02	120.43	2.042894E-11	-149.26
15.00	90.00	-16.76	-999.99	-16.76	0.00000	-0.00	LINEAR	8.071818E-02	111.59	2.206886E-11	-154.58
20.00	90.00	-14.09	-999.99	-14.09	0.00000	-0.00	LINEAR	1.006897E-01	101.22	2.290866E-11	-161.30
25.00	90.00	-11.72	-999.99	-11.72	0.00000	-0.00	LINEAR	1.441568E-01	91.35	2.246857E-11	-170.02
30.00	90.00	-9.57	-999.99	-9.57	0.00000	-0.00	LINEAR	1.844985E-01	83.40	2.083477E-11	177.78
35.00	90.00	-7.72	-999.99	-7.72	0.00000	0.00	LINEAR	2.298268E-01	77.72	1.771108E-11	158.88
40.00	90.00	-6.21	-999.99	-6.21	0.00000	0.00	LINEAR	2.716844E-01	74.03	1.502944E-11	139.50
45.00	90.00	-5.05	-999.99	-5.05	0.00000	0.00	LINEAR	3.106857E-01	71.87	1.604336E-11	97.99
50.00	90.00	-4.21	-999.99	-4.21	0.00000	0.00	LINEAR	3.419981E-01	70.80	2.324437E-11	75.44
55.00	90.00	-3.69	-999.99	-3.69	0.00000	0.00	LINEAR	3.631788E-01	70.45	2.902635E-11	62.27
60.00	90.00	-3.48	-999.99	-3.48	0.00000	0.00	LINEAR	3.728261E-01	70.53	3.340845E-11	54.41
65.00	90.00	-3.59	-999.99	-3.59	0.00000	0.00	LINEAR	3.673805E-01	70.81	3.524877E-11	49.50
70.00	90.00	-4.11	-999.99	-4.11	0.00000	0.00	LINEAR	3.462744E-01	71.08	3.399515E-11	46.41
75.00	90.00	-5.19	-999.99	-5.19	0.00000	0.00	LINEAR	3.057277E-01	71.21	2.952615E-11	44.53
80.00	90.00	-7.26	-999.99	-7.26	0.00000	0.00	LINEAR	2.408004E-01	71.01	2.204296E-11	43.56
85.00	90.00	-11.76	-999.99	-11.76	0.00000	0.00	LINEAR	1.435111E-01	70.34	1.198117E-11	43.33
90.00	90.00	-999.99	-999.99	-999.99	0.	0.		1.017386E-11	-111.00	1.220898E-15	61.38

AVERAGE POWER GAIN= 2.402458E-01 SOLID ANGLE USED IN AVERAGING= 1.80001*PI STERADIANS.

***** DATA CARD NO. 3 FN -0 -0 -0 -0 0. 0. 0. 0. 0 0.

RUN TIME = 6.778

Section V
Execution Time

The program execution time depends on the number of patches and the number of wire segments used. The central processor time approximately follows the formula

$$T = T_1 + T_2 + T_3 + T_4 ,$$

$$T_1 = (A_1 k N_s^2 + A_2 k N_p^2 + A_3 k N_s N_p + A_4 N_c)/M ,$$

$$T_2 = B\,(N_s + 2N_p)^3/M^2 ,$$

$$T_3 = C N_e\,(N_s + 2N_p)^2/M ,$$

$$T_4 = D k N_f\,(N_s + 2N_p) ,$$

where

N_s = number of wire segments,
N_p = number of surface patches,
N_c = number of connections between a wire and a surface,
N_e = number of different excitations,
N_f = number of far-field calculation points,
M = number of degrees of symmetry,
k = 1 for structure in free space,
2 for perfect ground or reflection coefficient approximation, and
4 for Sommerfeld/Norton method.

T_1 is the time to fill the interaction matrix; T_2 is the time to factor the matrix; T_3 is the time to solve for the currents for all excitations; and T_4 is the time to calculate far fields.

The proportionality factors depend on the computer system on which the program is run. The factors in seconds for a CDC 7600 computer when the matrix fits in core are roughly

$A_1 = 3.\ (10^{-4})$,
$A_2 = 5.\ (10^{-5})$,
$A_3 = 5.\ (10^{-4})$,
$A_4 = 2.\ (10^{-2})$,
$B = 2.\ (10^{-6})$,
$C = 4.\ (10^{-6})$, and
$D = 6.\ (10^{-5})$.

When the extended thin-wire kernel is used, A_1 is increased by about 18 percent. If the approximation for large interaction distances is used with RKH = R_o, then A_1 is multiplied by (1. - 0.7F) where F is the fraction of all segment pairs for which the separation is greater than R_o.

Unless a large number of excitations or far fields are requested, T_1 and T_2 will account for nearly all of the running time. If the matrix does not fit in core storage, T_1 and T_2 will be larger than indicated above. They may be much larger if I/O time is included.

The code SOMNEC requires about 15 sec to write the Sommerfeld/Norton data file on a CDC 7600 computer.

Section VI
Differences Between NEC-2, NEC-1, and AMP2

The following are features of the NEC-1 code that differ from AMP2:

- A new current expansion is used with continuous current and current derivative along wires. The expansion enforces new conditions at multiple-wire junctions and allows for current flowing onto the end cap at an open wire end.
- Where a wire connects to a surface, the surface-current expansion is related to the current at the base of the wire rather than at the center of the last wire segment.
- An optional voltage source based on a discontinuity in current slope is available.
- In the thin-wire approximation, the current filament is on the wire axis and the observation points are on the surface.
- An optional extended thin-wire approximation is available.
- Either a perfectly or imperfectly conducting ground may be used with surface patches.
- Either a perfect or imperfect ground may be used with an incident plane wave.
- Some constants have been changed including the velocity of light (2.998×10^8 m/sec.) and the default frequency (299.8 MHz).
- The wire-segment connection numbers have new meanings.
- The radiated field is the field at a range R multiplied by R, with R approaching infinity. In AMP and AMP2, the field is multiplied by R/λ.
- Both near electric and magnetic fields may be computed. The NF card is no longer used.
- Charge density may be printed for wires.
- The PT card is no longer cancelled by a new EX card.

The following are features of NEC-2 that differ from NEC-1:

- The NGF option has been added.
- The restart option has been removed.
- The Sommerfeld/Norton method has been added.
- Maximum coupling between antennas may be computed.
- Wires may have tapered radius and segment lengths.
- Patches may be specified as triangles, rectangles, or quadrangles.
- Rectangular surfaces with multiple patches may be specified.
- The SS card for surfaces has been eliminated.

Section VII
File Storage Requirements

Depending on the requirements of a run, NEC-2 may use the following files.

11, 12, 13, 14, 15, 16 — scratch files for matrix manipulations.
20 — NGF file.
21 — Sommerfeld/Norton data.

The scratch files are used only when the matrix will not fit into core storage. For a case that does not use the NGF (but may write a NGF file), there are five options for matrix storage. If

N = the number of equations (number of segments plus twice the number of patches),
N_x = the number of equations for a symmetric section, and
I_R = number of complex numbers for the matrix in core storage (4000),

then the cases, indicated by the value of ICASE in the code, are:

ICASE

1 matrix in core, no symmetry ($N^2 \leq I_R$).

2 matrix in core, symmetry ($NN_x \leq I_R$).

3 matrix out of core, no symmetry ($N^2 > I_R$).

4 matrix out of core, symmetry, blocks fit in core ($NN_x > I_R$, $N_x^2 \leq I_R$).

5 matrix out of core, symmetry, blocks do not fit in core ($N_x^2 > I_R$).

File storage is used for cases 3, 4, and 5. Only the four files (11, 12, 13, and 14) are used when the NGF is not in use. The size of each file is approximately $2NN_x$ words. If the computer system requires that the user specify the file size, a safety margin should be included in the request. A more accurate estimate of the file size is

$$L = 2N\, N_c\, [N_x/N_c + 1] ,$$

where

$$N_c = \left[\frac{I_R}{2N} \right]$$

and [ ] indicates truncation. N_c, which is the number of matrix columns in an I/O block, must be at least 1.

When the NGF is used, all six scratch files may be required. For the NGF the matrix is partitioned into four sections as

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

A is the matrix for the NGF structure and is factored before the NGF file is written. The storage case for A is indicated in the NGF label by the value of ICASE (see example 10 in section IV). When the NGF is used, matrix A is read from file 20 and, if ICASE is 3, 4, or 5, is stored on file 13. The size of file 13 when the NGF is used is approximately:

ICASE	Length of file 13
3	$4N^2$
4	$2NN_x$
5	$4NN_x$

There are four options for storage of the matrices B, C, and D. These are associated with the integer ICASX as follows:

ICASX

1 A_R, B, C, and D fit in core together where
A_R = A for ICASE = 1 or 2,
= one I/O block of A for ICASE = 3 or 5,
= one submatrix for ICASE = 4.

2 B, C, and D fit in core but not with A_R. This is possible only for ICASE = 3, 4, or 5 when A does not need dedicated space in core. A_R and B must also fit in core together.

3 B, C, and D do not fit in core, but D fits in core alone. A and D must fit together if ICASE = 1 or 2.

4 D does not fit in core.

The sizes of matrices B, C, and D depend on the number of new unknowns N_n where

$$N_n = N_s + N_t + 2 N_p + 10 N_q ,$$

N_s = number of new segments added to NGF,

N_t = number of NGF segments connected to new segments or patches,

N_p = number of new patches,

N_q = number of NGF patches connected to new segments.

The sizes of matrices B and C are $2\ NN_n$ and the size of D is $2\ N_n^2$ words. The file lengths are approximately $2\ N_n^2$ words for files 11 and 12, and $2\ NN_n$ for files 14, 15, and 16. When ICASX is 1 these files are not used, and when ICASX is 2 file 16 is not used.

The length of the NGF file (20) is approximately $4\ N\ (N_x + 3)$. The length of the Sommerfeld/Norton data file (21) is about 2200 words.

Section VIII
Error Messages

1. CHECK DATA, PARAMETER SPECIFYING SEGMENT POSITION IN A GROUP OF EQUAL TAGS CANNOT BE ZERO.
   Routine: ISEGNO
   This error results from an input data error and may occur at any point where a tag number is used to identify a segment. Execution terminated. Data on the NT, TL, EX, and PT cards should be checked.

2. CONNECT - SEGMENT CONNECTION ERROR FOR SEGMENT _ .
   Routine: CONNECT
   Possible causes: number of segments at a junction exceeds limit; segment lengths are zero; array overflow.

3. DATA FAULT ON LOADING CARD NO. = _ _ ITAG STEP1 = _ _ IS GREATER THAN ITAG STEP2 = _ _ .
   Routine: MAIN
   When several segments are loaded, the number of the second segment specified must be greater than the number of the first segment. Execution terminated.

4. EOF ON UNIT _ _NBLKS = _ _NEOF = _ _.
   Routine: BLCKIN, entry point of BLCKOT
   An end of file has been encountered while reading data from the unit. NBLKS determines how many records are read from the unit. NEOF is a flag to indicate which call to BLCKIN initiated the read. If NEOF = 777, this diagnostic is normal and execution will continue. Otherwise, an error is indicated and execution will terminate.

5. ERROR -- ARC ANGLE EXCEEDS 360. DEGREES
   Routine: ARC
   Error on GA card.

6. ERROR - B LESS THAN A IN ROM2
   Routine: ROM2
   Program malfunction.

7. ERROR - FR/GN CARD IS NOT ALLOWED WITH N.G.F.
   Routine: Main
   See section III-5.

8. ERROR -- CORNERS OF QUADRILATERAL PATCH DO NOT LIE IN A PLANE.
   Routine: Patch
   The four corners of a quadrilateral patch (SP card) must lie in a plane.

9. ERROR - COUPLING IS NOT BETWEEN 0 AND 1
   Routine: Couple
   Inaccuracy in solution or error in data.

10. ERROR - GF MUST BE FIRST GEOMETRY DATA CARD
    Routine: DATAGN
    See section III-5.

11. ERROR IN GROUND PARAMETERS - COMPLEX DIELECTRIC CONSTANT FROM FILE IS_____ REQUESTED_____.
    Routine: MAIN
    Complex dielectric constant from file TAPE21 does not agree with data from GN and FR cards.

12. ERROR - INSUFFICIENT STORAGE FOR INTERACTION MATRICES.
    IRESRV, IMAT, NEQ, NEQ2 =
    Routine: FBNGF
    Array storage exceeded in NGF solution.

13. ERROR - INSUFFICIENT STORAGE FOR MATRIX
    Routine: FBLOCK
    Array storage for matrix is not sufficient for out-of-core solution.

14. ERROR - NETWORK ARRAY DIMENSIONS TOO SMALL.
    Routine: NETWK
    The number of different segments to which transmission lines or network ports are connected exceeds array dimensions. Execution terminated. Array size in the original NEC deck is 30. Refer to array dimension limitations in Part II for changing array sizes.

15. ERROR - LOADING MAY NOT BE ADDED TO SEGMENTS IN N.G.F. SECTION
    Routine: LOAD
    See section III-5.

16. ERROR - N.G.F. IN USE. CANNOT WRITE NEW N.G.F.
    Routine: MAIN

17. ERROR - NO. NEW SEGMENTS CONNECTED TO N.G.F. SEGMENTS OR PATCHES EXCEEDS LIMIT.
Routine: CONECT
Array dimension limit.

18. FAULTY DATA CARD LABEL AFTER GEOMETRY SECTION.
Routine: MAIN
A card with an unrecognizable mnemonic has been encountered in the program control cards following the geometry cards. Execution terminated.

19. GEOMETRY DATA CARD ERROR.
Routine: DATAGN
A geometry data card was expected, but the card mnemonic is not that of a geometry card. Execution terminated. After the GE card in a data deck, the possible geometry mnemonics are GE, GM, GR, GS, GW, GX, SP, and SS.
The GE card must be used to terminate the geometry cards.

20. GEOMETRY DATA ERROR - - PATCH _ _ LIES IN PLANE OF SYMMETRY.
Routine: REFLC

21. GEOMETRY DATA ERROR - - SEGMENT _ _ EXTENDS BELOW GROUND.
Routine: CONECT
When ground is specified on the GE card, no segment may extend below the XY plane. Execution terminated.

22. GEOMETRY DATA ERROR - - SEGMENT _ _ LIES IN GROUND PLANE.
Routine: CONECT
When ground is specified on the GE card, no segment should lie in the XY plane. Execution terminated.

23. GEOMETRY DATA ERROR - - SEGMENT _ _ LIES IN PLANE OF SYMMETRY.
Routine: REFLC
A segment may not lie in or cross a plane of symmetry about which the structure is reflected since the segment and its image will coincide or cross. Execution terminated.

24. IMPROPER LOAD TYPE CHOSEN, REQUESTED TYPE IS _ _.
Routine: LOAD
Valid load types (LDTYP on the LD card) are from 0 through 5.
Execution terminated.

25. INCORRECT LABEL FOR A COMMENT CARD.
Routine: MAIN
The program expected a comment card, with mnemonic CM or CE, but encountered a different mnemonic. Execution terminated. Comment cards must be the first cards in a data set, and the comments must be terminated by the CE mnemonic.

26. LOADING DATA CARD ERROR, NO SEGMENT HAS AN ITAG= _ _.
Routine: LOAD
ITAG specified on an LD card could not be found as a segment tag.
Execution terminated.

27. NO SEGMENT HAS AN ITAG OF _ _.
Routine: ISEGNO
This error results from faulty input data and can occur at any point where a tag number is used to identify a segment. Execution terminated. Tag numbers on the NT, TL, EX, CP, PQ, and PT cards should be checked.

28. NOTE, SOME OF THE ABOVE SEGMENTS HAVE BEEN LOADED TWICE, IMPEDANCES ADDED.
Routine: LOAD
A segment or segments have been loaded by two or more LD cards. The impedances of the loads have been added in series. This is only an informative message. Execution continues.

29. NUMBER OF EXCITATION CARDS EXCEEDS STORAGE ALLOTTED.
Routine: MAIN
The number of voltage source excitations exceeds array dimensions. Execution terminated. The dimensions in the original NEC deck allow 10 voltage sources. Refer to Array Dimension Limitations in Part II to change the dimensions.

30. NUMBER OF LOADING CARDS EXCEEDS STORAGE ALLOTTED.
Routine: MAIN
The number of LD cards exceeds array dimension. Execution terminated.

The dimension in the original NEC deck allows 30 LD cards. Refer to Part II to change the dimensions.

31. NUMBER OF NETWORK CARDS EXCEEDS STORAGE ALLOTTED.
Routine: MAIN
The number of NT and TL cards exceeds array dimension. Execution terminated. The dimension in the original NEC deck allows 30 cards. Refer to Array Dimension Limitations in Part II to change the dimensions.

32. NUMBER OF SEGMENTS IN COUPLING CALCULATION (CP) EXCEEDS LIMIT.
Routine: MAIN
Array dimension limit.

33. NUMBER OF SEGMENTS AND SURFACE PATCHES EXCEEDS DIMENSION LIMIT.
Routine: DATAGN
The sum of the number of segments and patches is limited by dimensions. The present limit is 300.

34. PATCH DATA ERROR.
Routine: DATAGN
Invalid data on SP, SM, or SC card; or SC card not found where required.

35. PIVOT(_ _) = _ _.
Routine: FACTR (in-core) or LFACTR (out-of-core)
This will be printed during the Gauss Doolittle factoring of the interaction matrix or the network matrix when a pivot element less than 10^{-10} is encountered, and indicates that the matrix is nearly singular. The number in parentheses shows on which pass through the matrix the condition occurred. This is usually an abnormal condition although execution will continue. It may result from coinciding segments or a segment of zero length.

36. RADIAL WIRE G.S. APPROXIMATION MAY NOT BE USED WITH SOMMERFELD GROUND OPTION.
Routine: MAIN

37. RECEIVING PATTERN STORAGE TOO SMALL, ARRAY TRUNCATED.
Routine: MAIN
The number of points requested in a receiving pattern exceeds array dimension. Execution will continue, but storage of normalized pattern

will be truncated. This array dimension is 200 in the original NEC deck. Refer to Array Dimension Limitations in Part II to change dimension.

38. ROM2 - - STEP SIZE LIMITED AT Z =
Routine: ROM2
Probably caused by a wire too close to the ground in the Sommerfeld/ Norton ground method. Execution continues but results may be inaccurate.

39. SBF - SEGMENT CONNECTION ERROR FOR SEGMENT_.
Routine: SBF
The number of segments at a junction exceeds dimension limit (30), or the connection numbers are not self-consistent.

40. SEGMENT DATA ERROR.
Routine: MAIN
A segment with zero length or zero radius was found. Execution terminated.

41. STEP SIZE LIMITED AT Z = _ _.
Routine: INTX, HFK
The numerical integration to compute interaction matrix elements, using the Romberg variable interval width method, was limited by the minimum allowed step size. Execution will continue. An inaccuracy may occur but is usually not serious. May result from thin wire or wire close to the ground.

42. STORAGE FOR IMPEDANCE NORMALIZATION TOO SMALL, ARRAY TRUNCATED.
Routine: MAIN
The number of frequencies on FR card exceeds the array dimension for impedance normalization. An impedance beyond the limit will not be normalized. Execution continues. The limit is 50 in the original NEC deck. Refer to Array Dimension Limitations in Part II to change limit.

43. SYMMETRY ERROR - NROW, NCOL =
Routine: FBLOCK
Array overflow or program malfunction.

44. TBF - SEGMENT CONNECTION ERROR FOR SEGMENT _.
Routine: TBF
Same as error 39.

45. TRIO - SEGMENT CONNECTION ERROR FOR SEGMENT _.

Routine: TRIO

Same as error 39.

46. WHEN MULTIPLE FREQUENCIES ARE REQUESTED, ONLY ONE NEAR FIELD CARD CAN BE USED - LAST CARD READ IS USED.

Routine: MAIN

Execution continues.

References

1. Numerical Electromagnetics Code (NEC-1), Part I: NEC Program Description — Theory, to be published, Lawrence Livermore Laboratory, Livermore, CA, 1977 (Content same as NOSC TD 116, Part I).
2. Numerical Electromagnetics Code (NEC-1), Part II: NEC Program Description — Code, to be published, Lawrence Livermore Laboratory, Livermore, CA, 1977 (Content same as NOSC TD 116, Part II).
3. Poggio, A. J. and Adams, R. W., Approximations for Terms Related to the Kernel in Thin-Wire Integral Equations, Lawrence Livermore Laboratory, Livermore, CA, Rept. UCRL-51985, December 19, 1977.
4. Albertsen, N. C., Hansen, J. E., and Jensen, N. E., Computation of Space-Craft Antenna Radiation Patterns, The Technical University of Denmark, Lyngby, Denmark, June 1972.
5. Sengupta, D. L., Electromagnetic and Acoustic Scattering by Simple Shapes, Chapter 10, J. J. Bowman, T. B. A Senior and P. L. E. Uslenghi, Editors, North-Holland Publishing Company, Amsterdam, 1969.

RAC/gw

U.S. Government Printing Office: 1988/1 585-070/7013